 


---

# On-Chip Voltage and Timing Diagnostic Circuits





Frank O'Mahony  
Advanced Design, Intel  
Hillsboro, Oregon



October 2014

# Why Measure Time/Voltage On-Chip?

 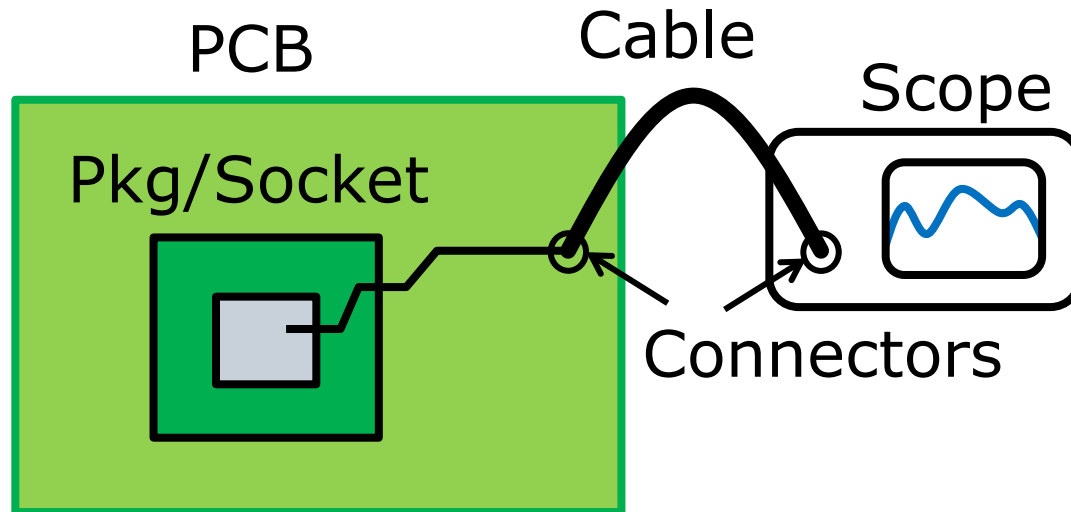1. Routing signals to equipment can filter and corrupt measurement
  - Loss, delay, discontinuities, loading, noise



# Why Measure Time/Voltage On-Chip?

---

2. Some measurements must be done w/o external equipment

## Wafer Sort



Ref: [www.besi.com](http://www.besi.com)

## In-Situ Test



Ref: [www.intel.com](http://www.intel.com)

# Presentation Flow

---

- We'll discuss key metrics and the limitations of off-chip measurements
- Then we'll see how to solve these with on-die measurement circuits
- My objective is that you will leave today with a set of simple but very useful techniques that you can apply to your own designs

# Outline

---

- Delay Measurement
- Power Supply Characterization
- I/O System Characterization

# Outline

---


## □ **Delay Measurement**

- Delay Metrics
- Off-chip measurement limitations
- On-Chip Phase Detector
- Code Density Test (CDT)

## □ Power Supply Characterization

## □ I/O System Characterization


# Delay/Skew Measurements

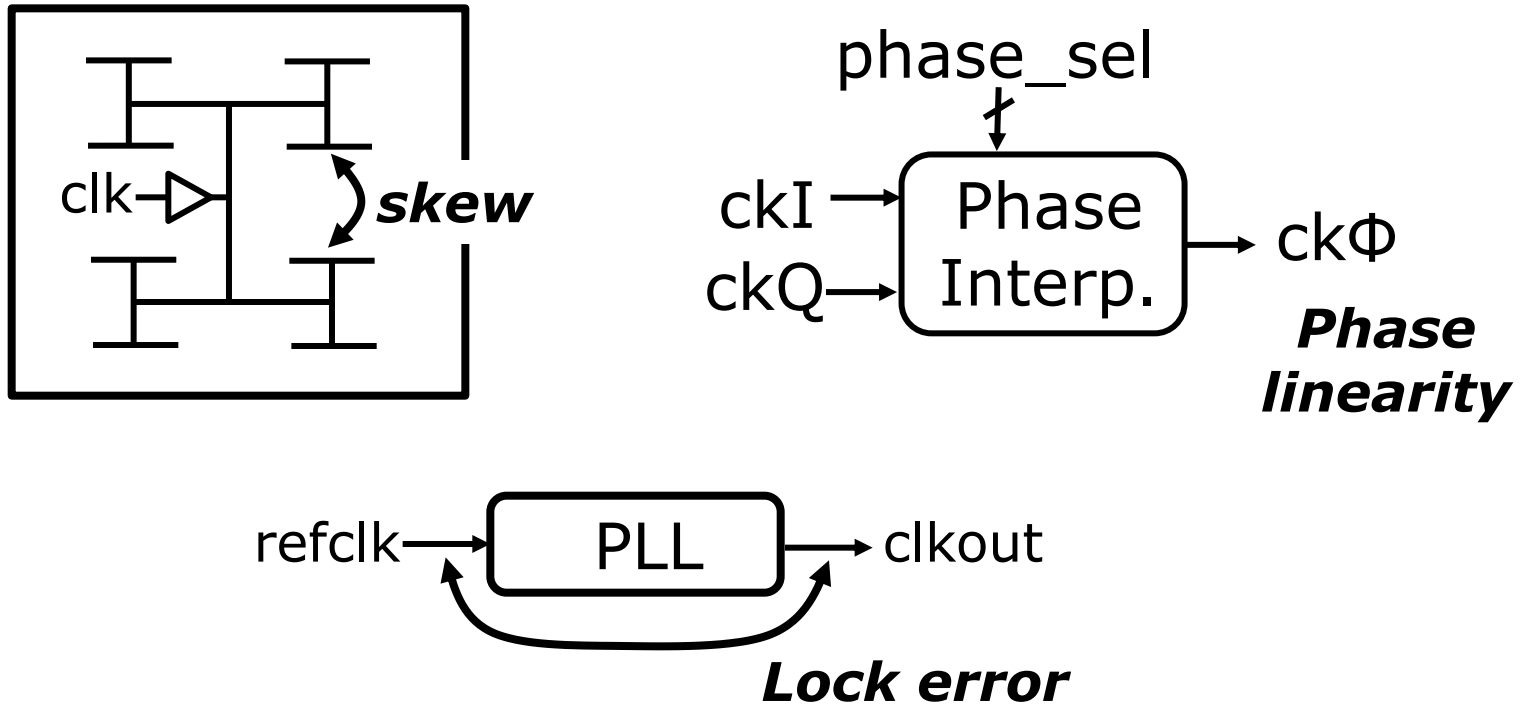


- Measuring the delay between two or more signals (often clocks) can be critical for circuit debug and characterization

# Off-Chip Clock Skew Measurement

Basic off-chip setup

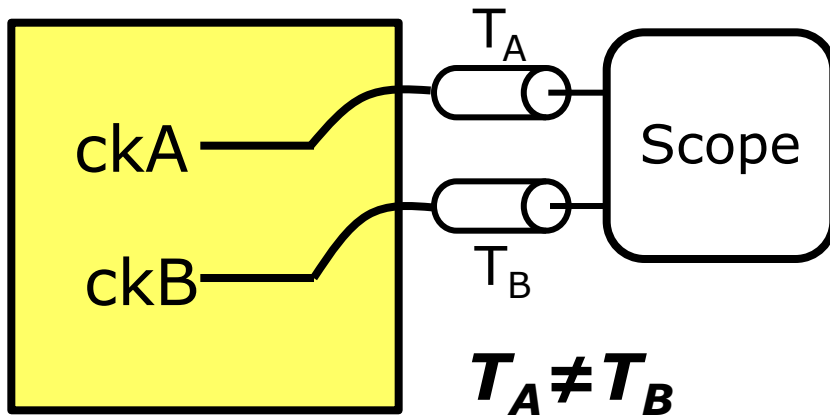


Improved off-chip setup

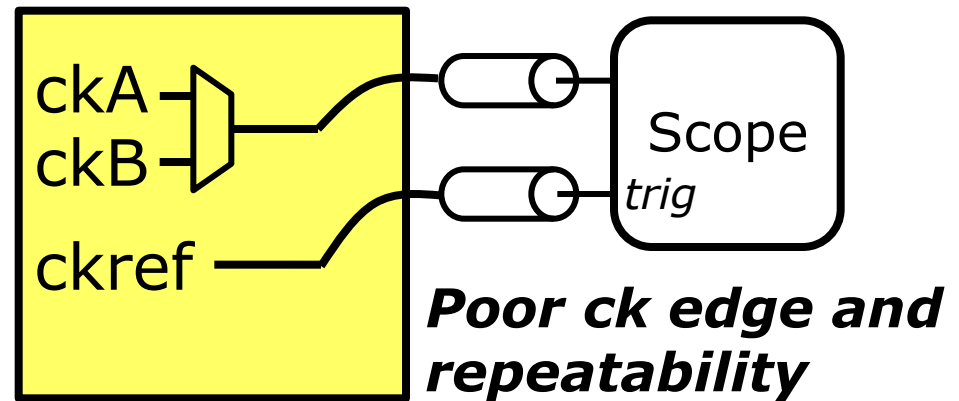

- External measurement limitations
  - Delay matching to equipment → delay error
  - Filtering for high-speed signals → delay error
    - $V_{CM}$  and edge rate differences cause error
  - Delay stability → poor repeatability





# On-Chip Phase Detector

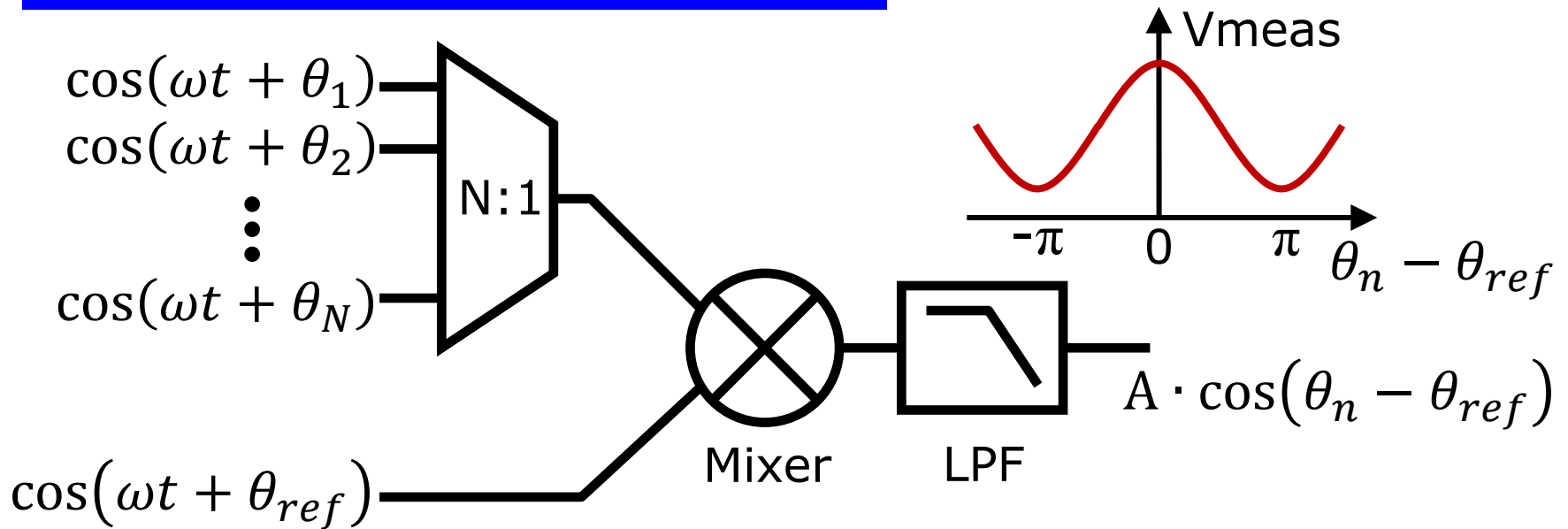

- Mix phase difference down to DC on chip
  - Other types of phase detectors can also work
- Measure DC component off- or on-chip
- Shared Mixer reduces mismatch. Still has MUX mismatch.
- Requires calibration for Voltage-to-Time constant ( $A$ )


# Example: 10GHz Clock Skew Measurements

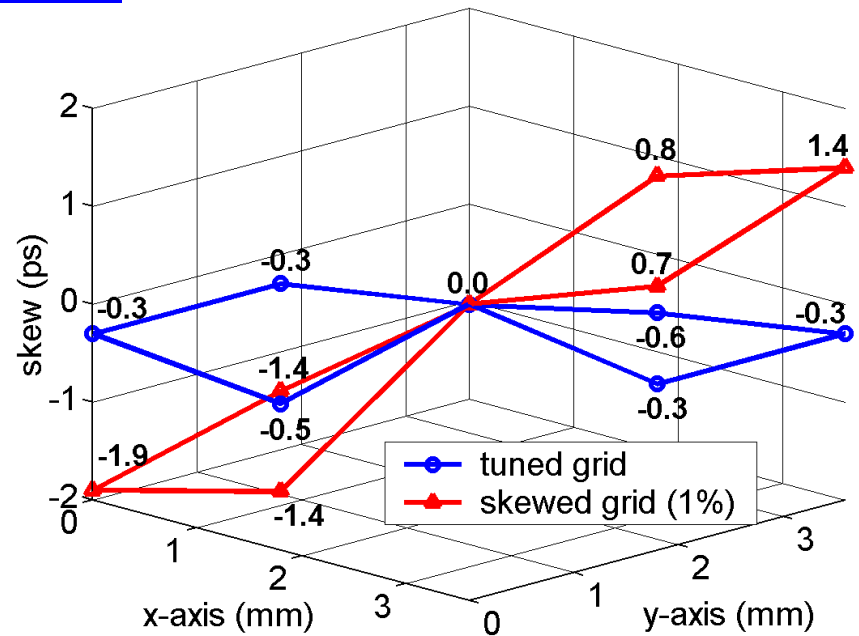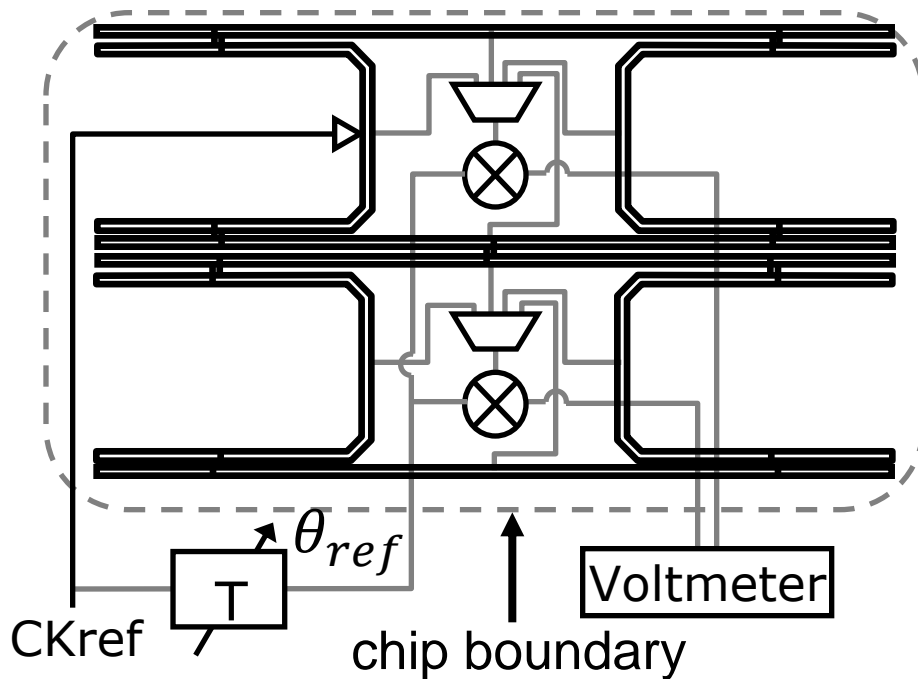

Ref: F. O'Mahony, ISSCC 2003




- Meas. resonant clock grid skew w/ sub-ps accuracy
- Minimize/match routing to phase detectors
- Measure externally with voltmeter
- Calibrate externally using adjustable delay line

# Code Density Test (CDT) Method

 

- Basic Idea: Count the # of Reference Edges that occur between two clock edges
- Likelihood of "Hit" is  $\Delta T/T$
- Asynchronous ring VCO provides uniform Edge PDF
  - Jitter and spread-spectrum improve the distribution


# Code Density Test (CDT) Method

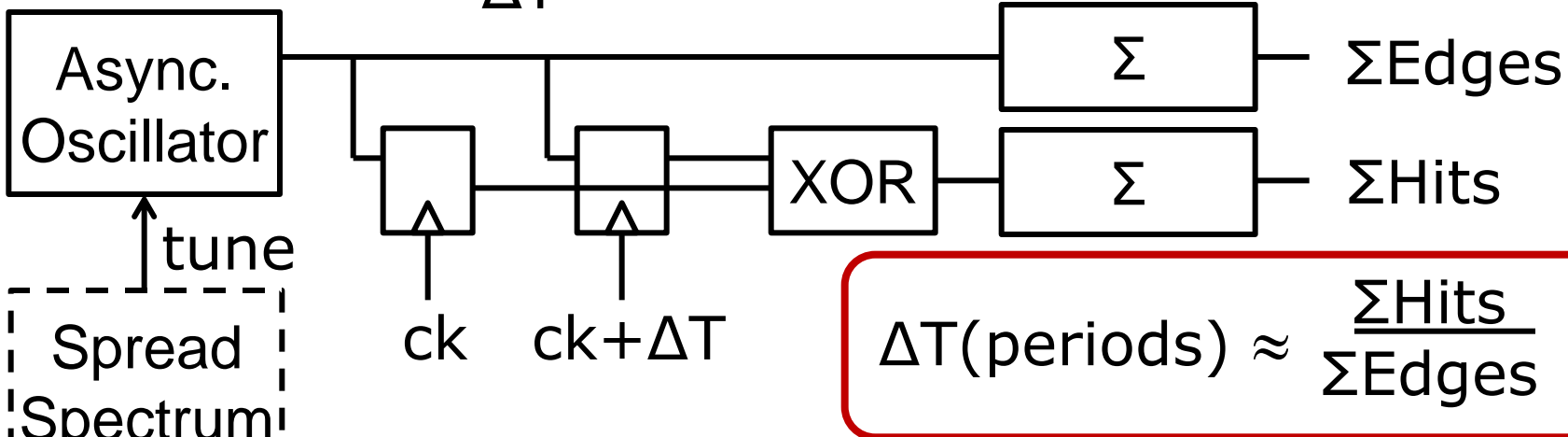  

$$\Delta T(\text{periods}) \approx \frac{\Sigma Hits}{\Sigma Edges}$$


Ref: M. Mansuri, VLSIC, 2012

# Time-Domain Circuit Operation

 

- Likelihood of "Hit" is  $\Delta T/T$
- Async. clock period must be  $> 2 \cdot \Delta T_{\max}$ 
  - A simple VCO frequency calibration ensures this
- Jitter helps by randomizing edge location

# Delay Measurement Accuracy

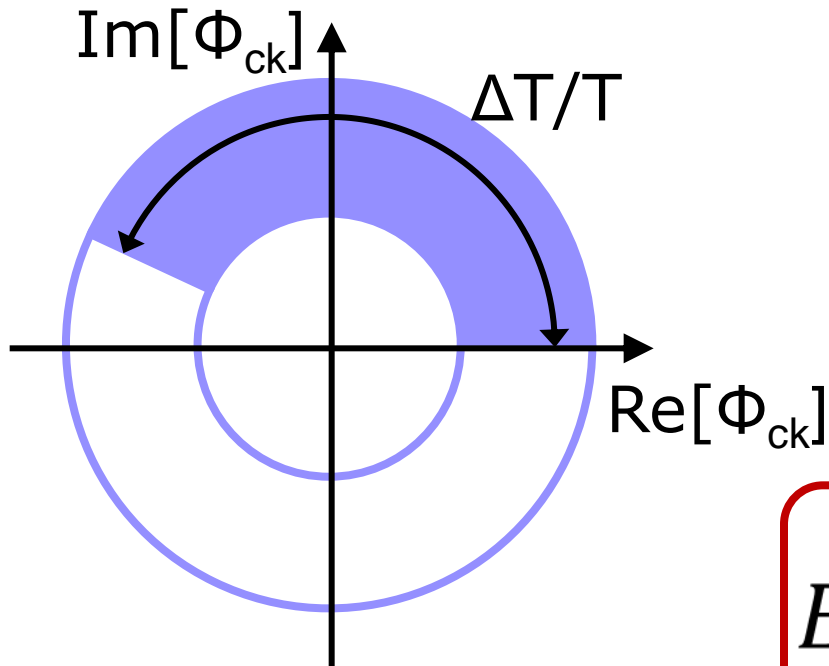

$$\mu = np, \sigma^2 = np(1 - p)$$


$$X = \Sigma Hits$$

$$p = \frac{\Delta T}{T}, n = \Sigma Edges,$$

$$E \left[ \frac{X}{n} \right] = p, \frac{\sigma}{n} = \left[ \frac{p(1-p)}{n} \right]^{0.5}$$


- Model w/ Binomial Distrib. (think “many coin flips”)
- Accuracy improves as  $(1/\Sigma Edges)^{0.5}$
- Higher Resolution  $\leftrightarrow$  Longer measurement time

# Synchronizer

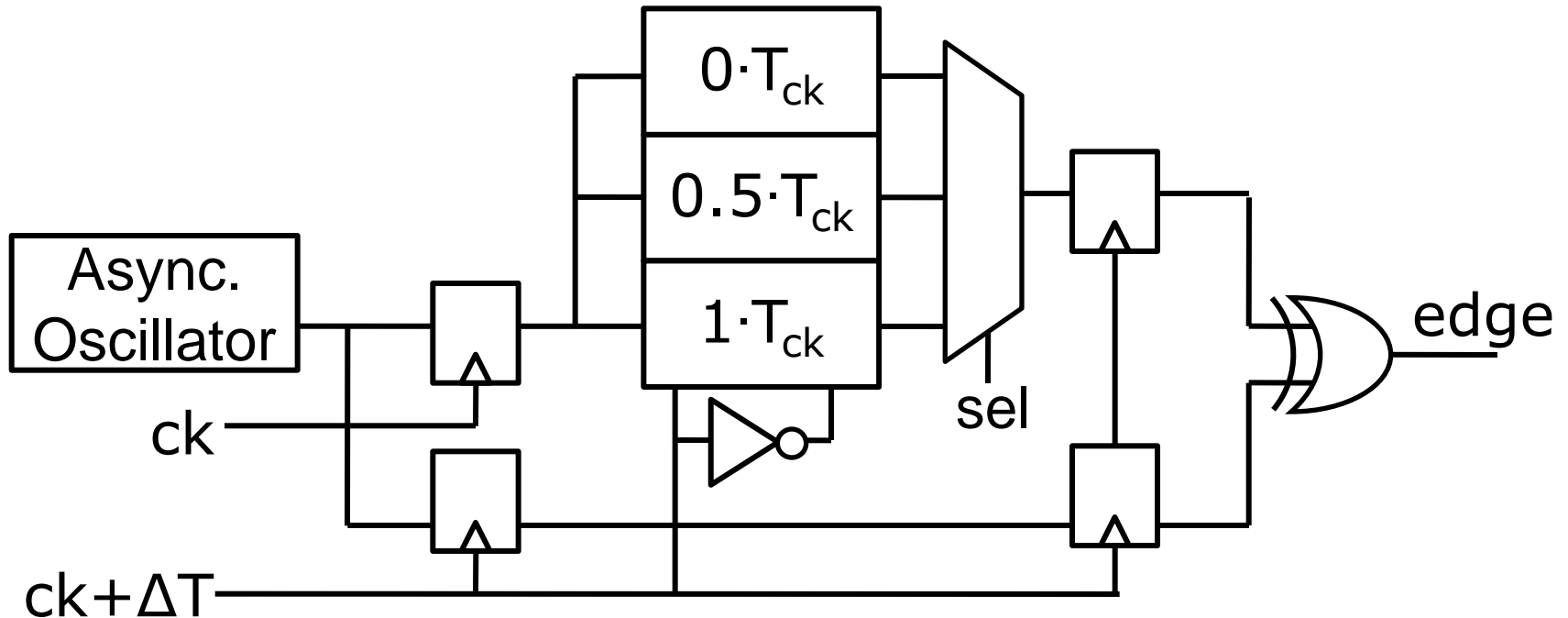

- Synchronizer aligns samples across full  $360^\circ$  range
- Clocks for  $\Delta T = N \cdot T_{ck} + \Delta t$  are identical. Synchronizer adds programmable # of cycles of delay.


# Delay Measurement Range

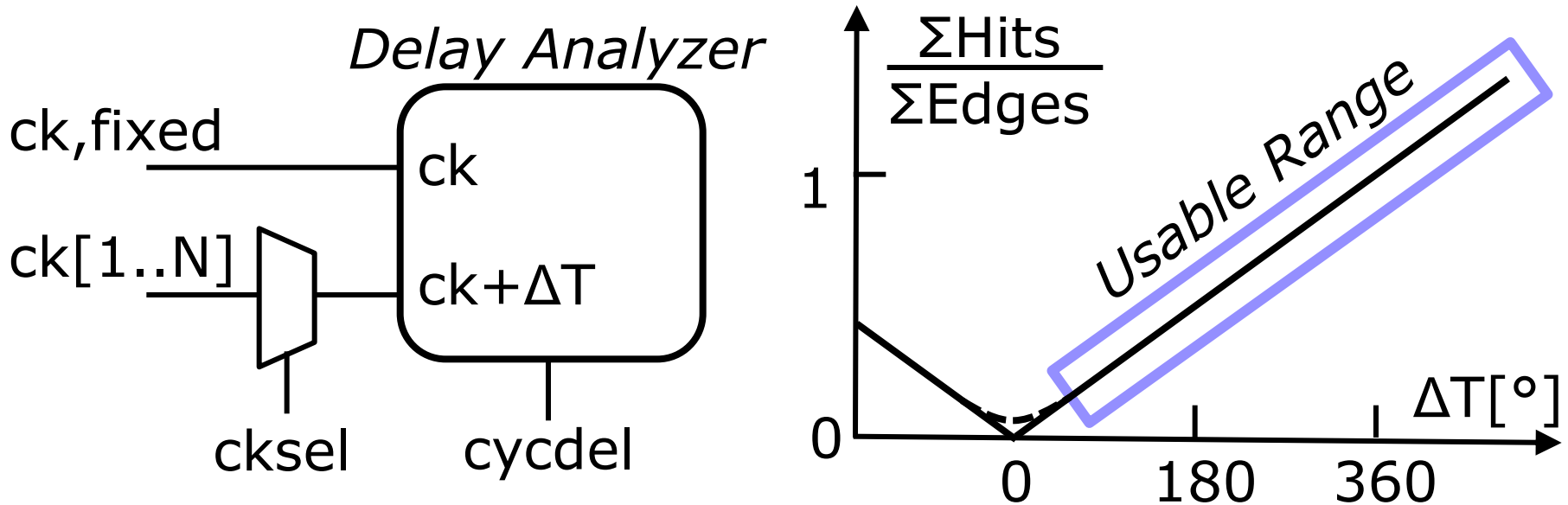

- Measure  $ck[1..N]$  relative to  $ck,fixed$ 
  - $ck[1..N]$  are all later than  $ck,fixed$
  - Removes circuit mismatch (e.g. FF's) except Mux
  - Use *cycdel* to select which edges to compare
  - Synchronizer extends range to  $>360^\circ$





# Detailed Circuit Implementation

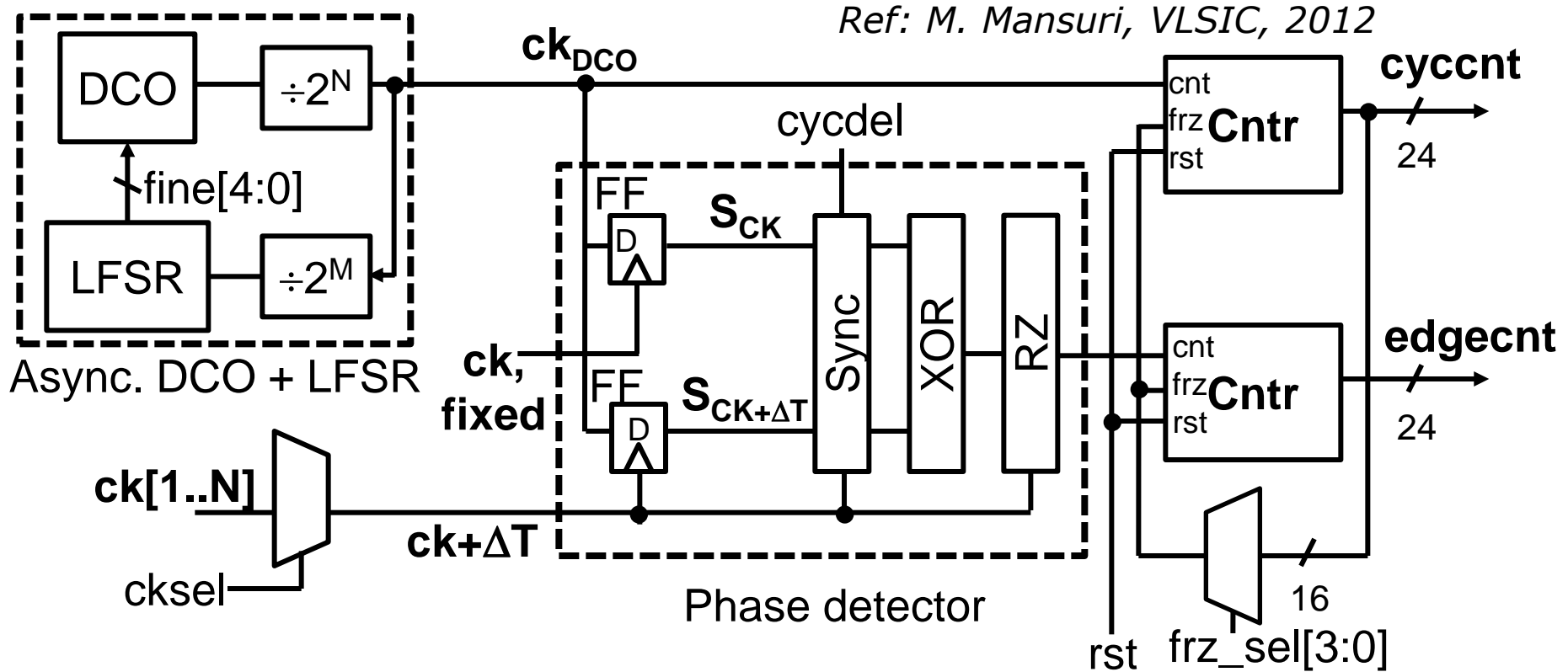


- Entirely digital implementation
- Counter depth depends on required accuracy
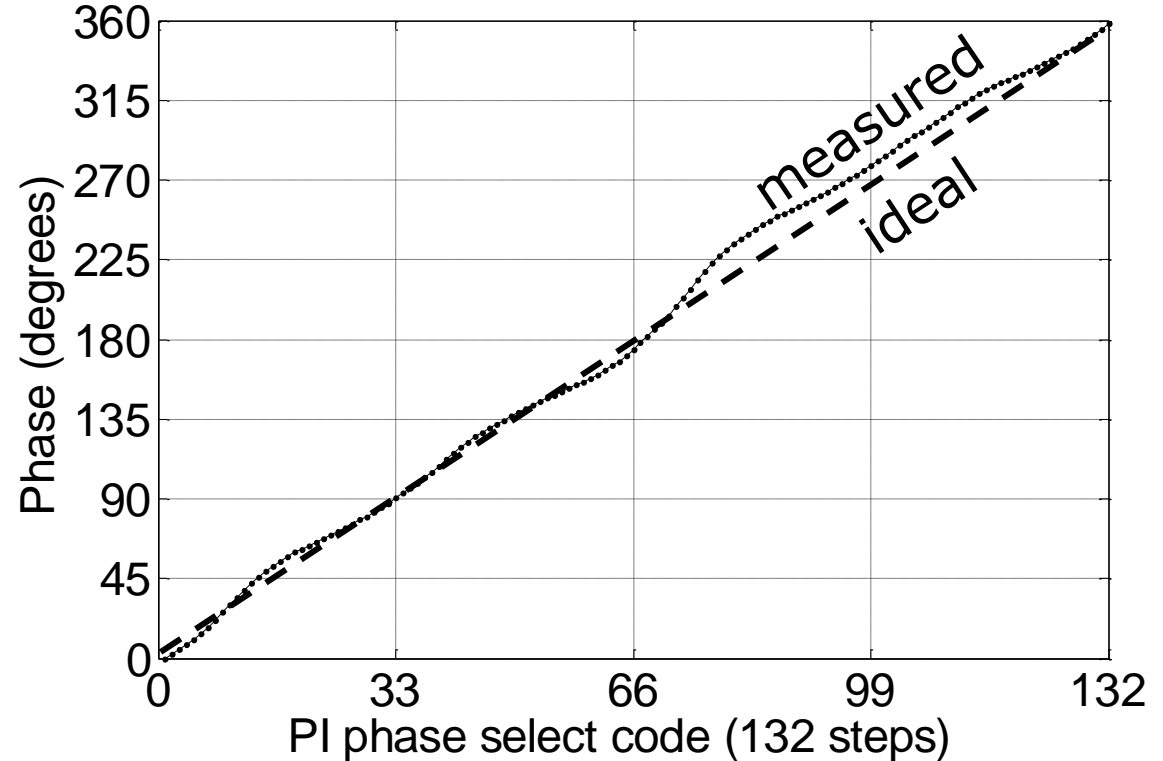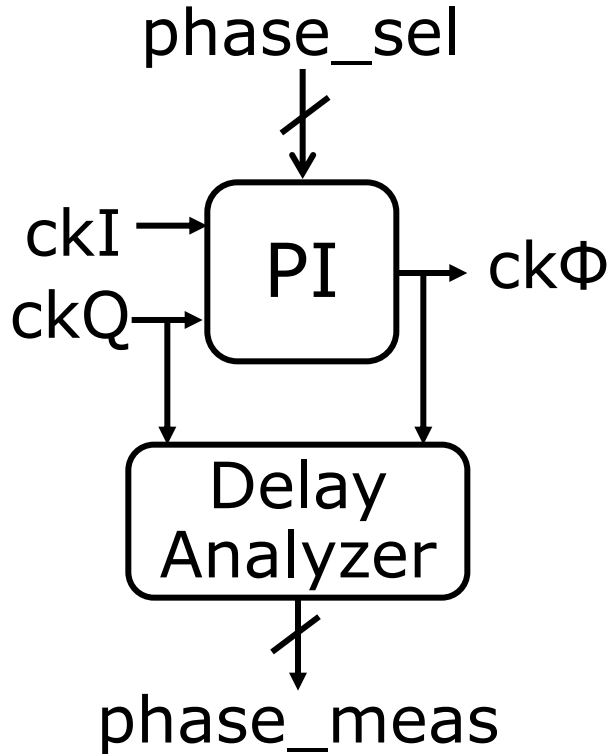
# Measured Phase Interpolator (PI) Linearity



- Fully on-die measurement of quadrature PI w/ CDT
- Phase transfer function provides INL/DNL

# Measured Phase Error – Repeatability

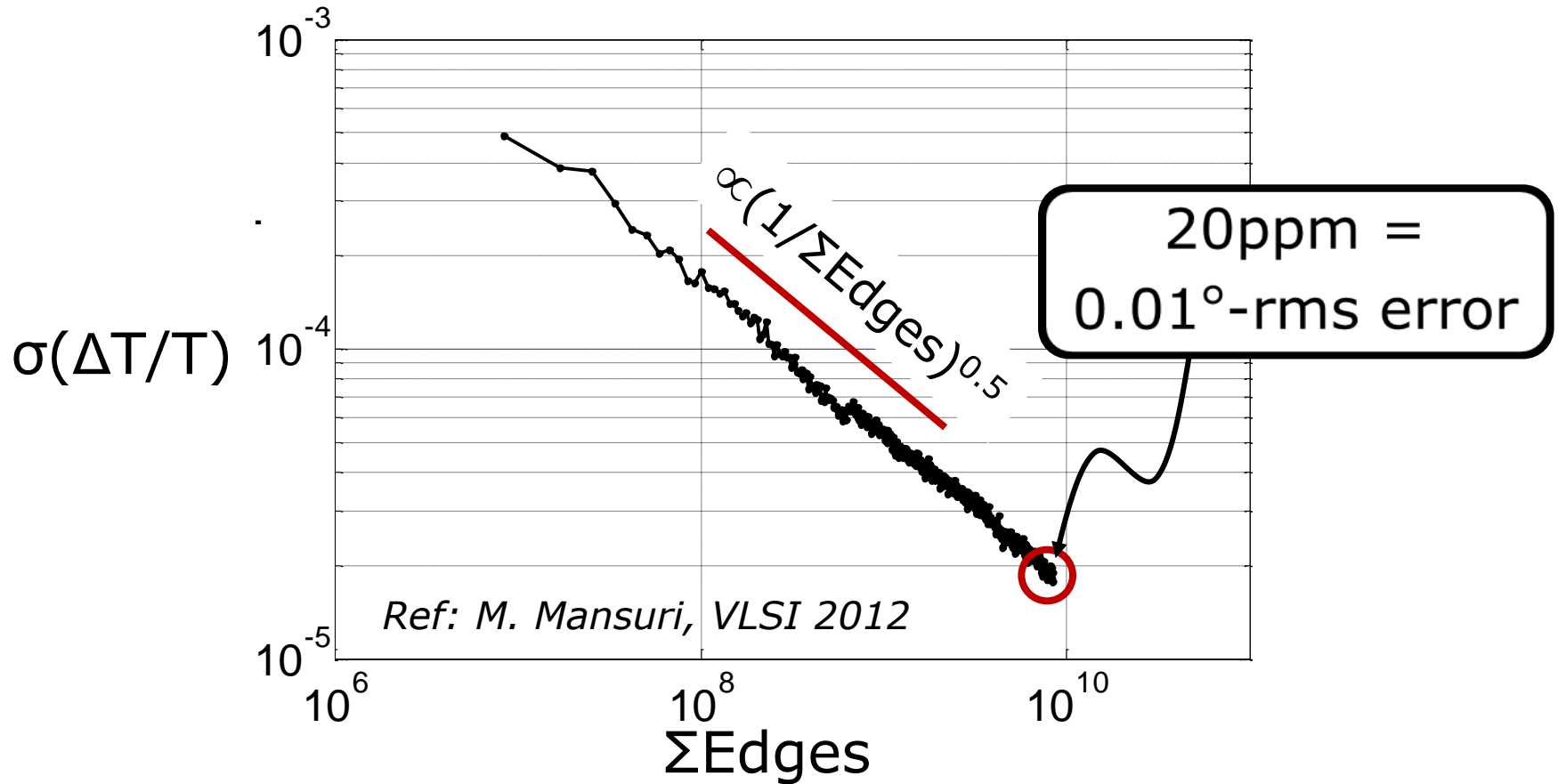

□ Measurement error reduces as  $(1/\Sigma\text{Edges})^{0.5}$


# Outline

---

- Delay Measurement
  
- **Power Supply Characterization**
  - Power Supply metrics
  - Off-chip measurement limitations
  - Real vs. Equivalent time measurement
  - Supply noise waveform
  - Supply impedance
  - Supply noise spectrum
  
- I/O System Characterization

# Power Supply Metrics




Power Supply Grid on Die

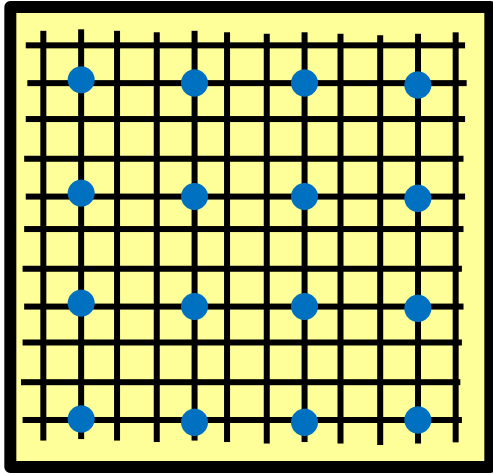

□ Used to design, model and debug the chip

□ Examples:

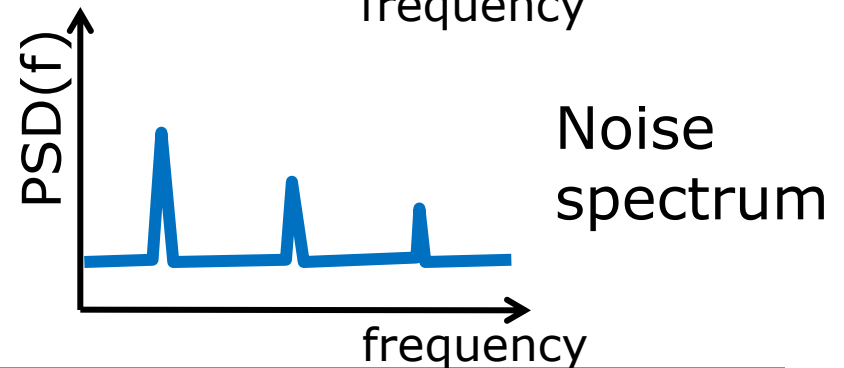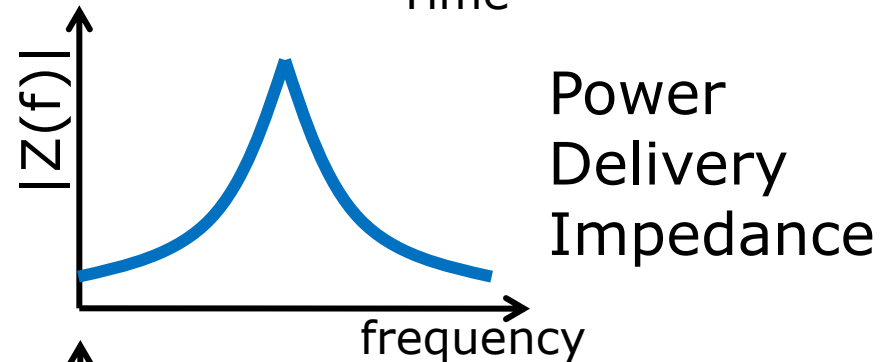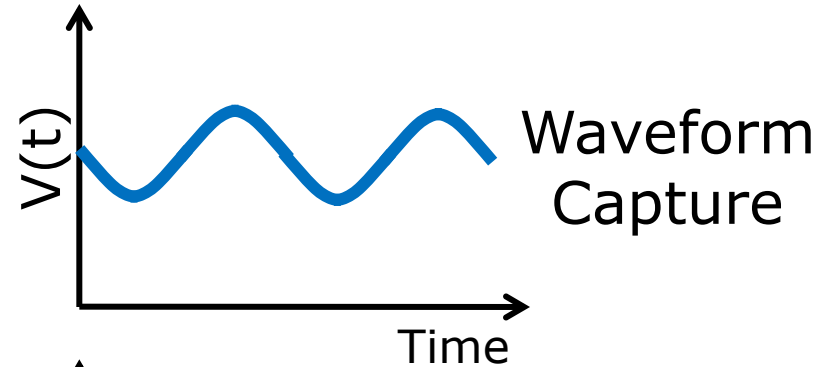
- Quantify Vcc droop  $\rightarrow V(t)$
- Verify Grid model  $\rightarrow Z(f)$
- Find aggressors  $\rightarrow PSD(f)$



 
# External Power Supply Measurements

---


- ❑ Packages commonly have supply probes
- ❑ Off-chip measurement limitations
  - External probing loads the power supply
  - Probe measurements are not local
  - Limited # of probe points due to pkg routing
  - Package filters the supply measurements




Oscilloscope

 

Time-Domain Reflectometer (TDR)

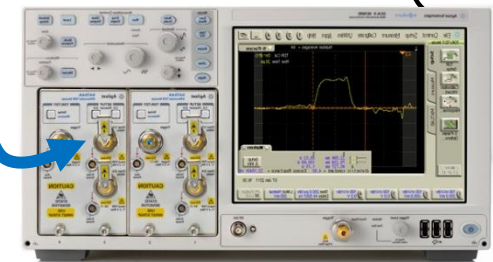


Spectrum Analyzer

 

# On-Die High-Speed ADC



---

Power Supply Grid on Die

 

- ❑ Ideally embed local ADCs to digitize these metrics
- ❑ High resolution (10+ bits) and BW (>1GHz) presents a significant implementation challenge


# Real vs. Equivalent-Time Measurement

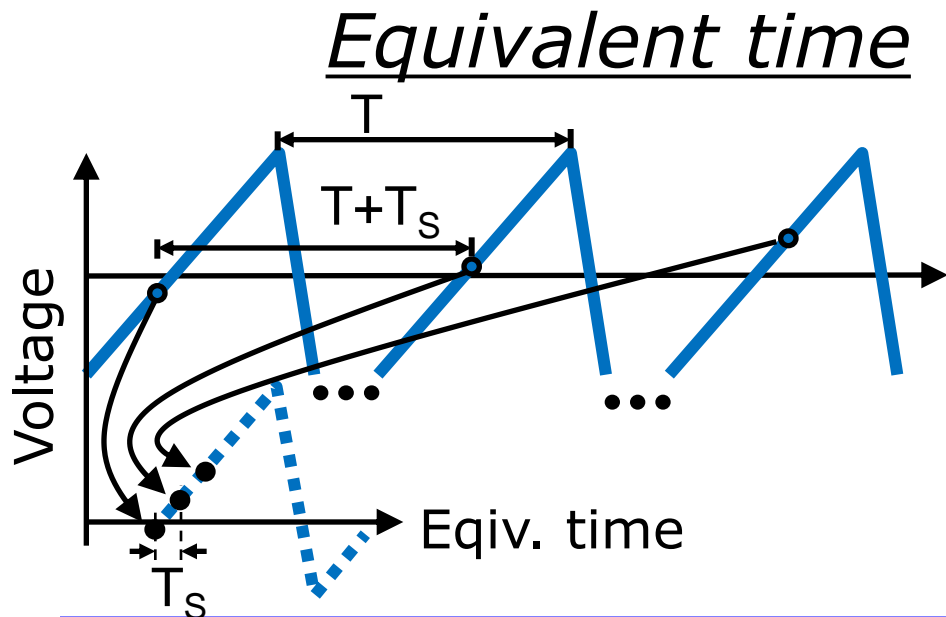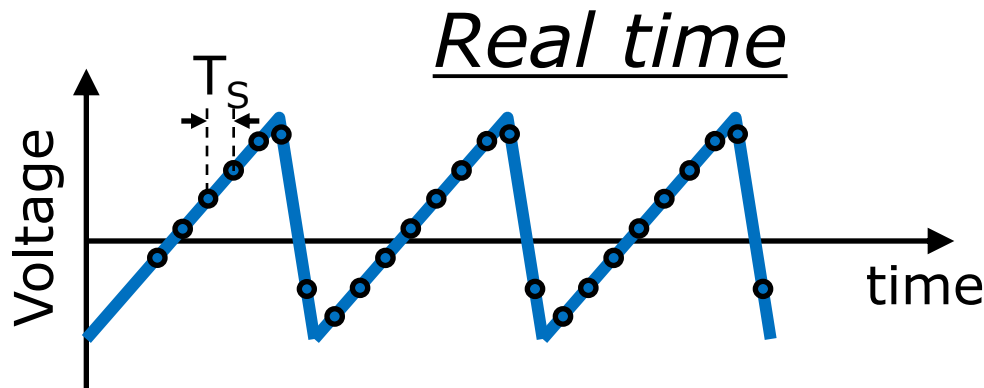

- ☺ One-shot meas.
  - ☺ Most complete info
    - Time, spectral
  - ☹ Limited by ADC  $f_{\text{samp}}$ , resolution
- 
- ☹ Periodic waveforms
  - ☹ No spectral info.
  - ☺ Effective BW and resolution not limited by ADC




# Equivalent-Time Measurement

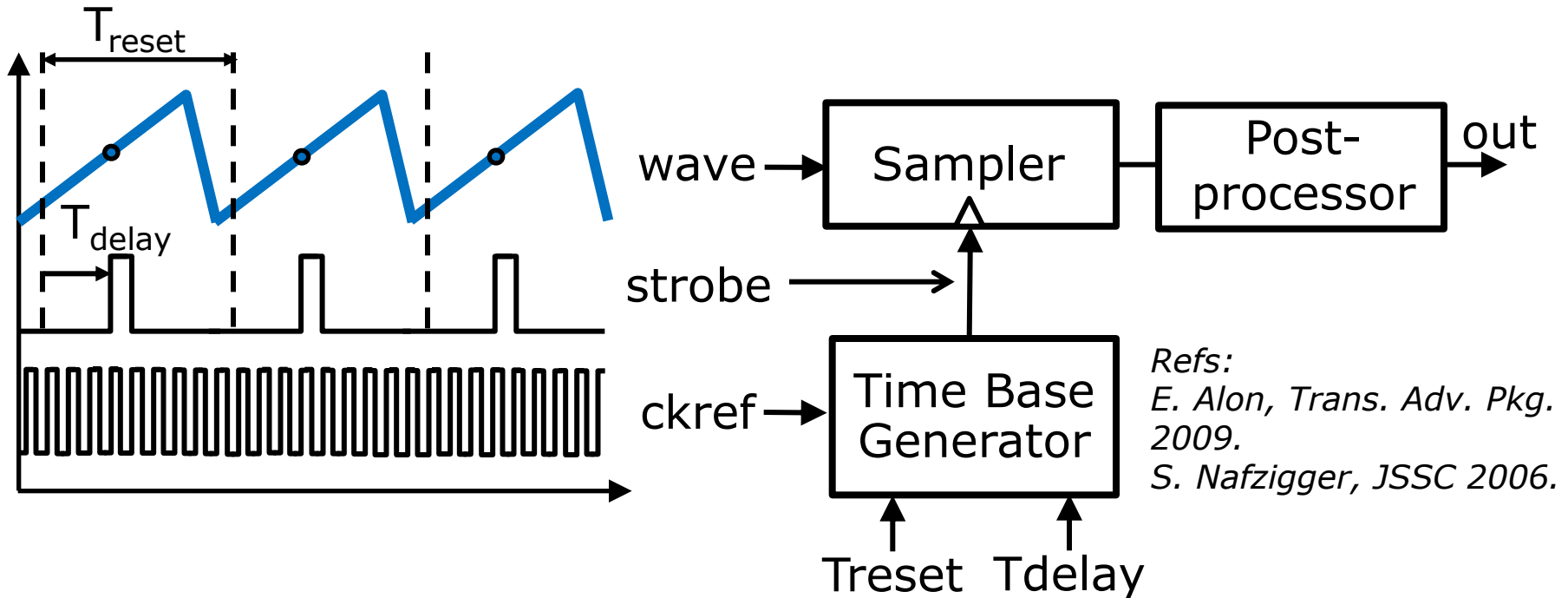


- Time Base Generator (TBG) provides strobe
- Sweeps strobe position in equivalent time
- Sampler output is postprocessed (e.g. averaged)

# Sampler Option #1: 1-bit Comparators

 


- Programmable threshold  $\rightarrow$  Voltage CDF/PDF
- Center of this PDF is the Average Voltage ( $\mu$ )
- CDF/PDF also captures Voltage Noise (e.g.  $\sigma$ )
  - ...along with comparator noise and strobe jitter
  - Extract fit to distribution (normal, uniform, sinusoid)

# Sampler Option #1: 1-bit Comparators

 


- Programmable threshold  $\rightarrow$  Voltage CDF/PDF
- Center of this PDF is the Average Voltage ( $\mu$ )
- CDF/PDF also captures Voltage Noise (e.g.  $\sigma$ )
  - ...along with comparator noise and strobe jitter
  - Extract fit to distribution (normal, uniform, sinusoid)

# Waveform Capture w/ 1-bit Comp.

 


- Combine 1-bit ADC with Equivalent-Time sampling to get full Waveform Capture

*Ref. K. Soumyanath, JSSC 1999.*

 


$Equiv. Time (T)$

# Waveform Capture w/ 1-bit Comp.

 


- Combine 1-bit ADC with Equivalent-Time sampling to get full Waveform Capture

*Ref. K. Soumyanath, JSSC 1999.*

 



Equiv. Time ( $T$ )

# Waveform Capture w/ 1-bit Comp.

 



- Combine 1-bit ADC with Equivalent-Time sampling to get full Waveform Capture

*Ref. K. Soumyanath, JSSC 1999.*

  

Equiv. Time ( $T$ )

 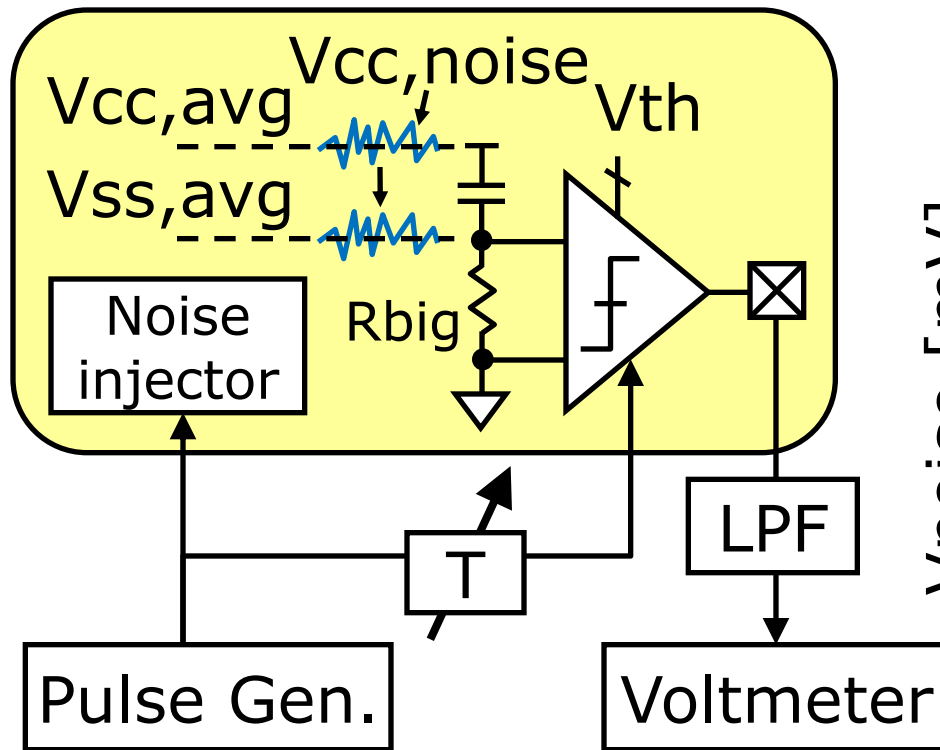
# Example: Simple Power Supply Measurement



Ref: F. O'Mahony, VLSIC 2006

- Re-used RX sampler from to sample  $V_{cc,noise}$
- AC couple  $V_{cc,noise}$  sets correct common mode for sampler
  - Limits measurement to  $freq > RC$
- Simplest TBG – strobe is the delayed noise signal


# Sampler Option #2: VCO-based ADC

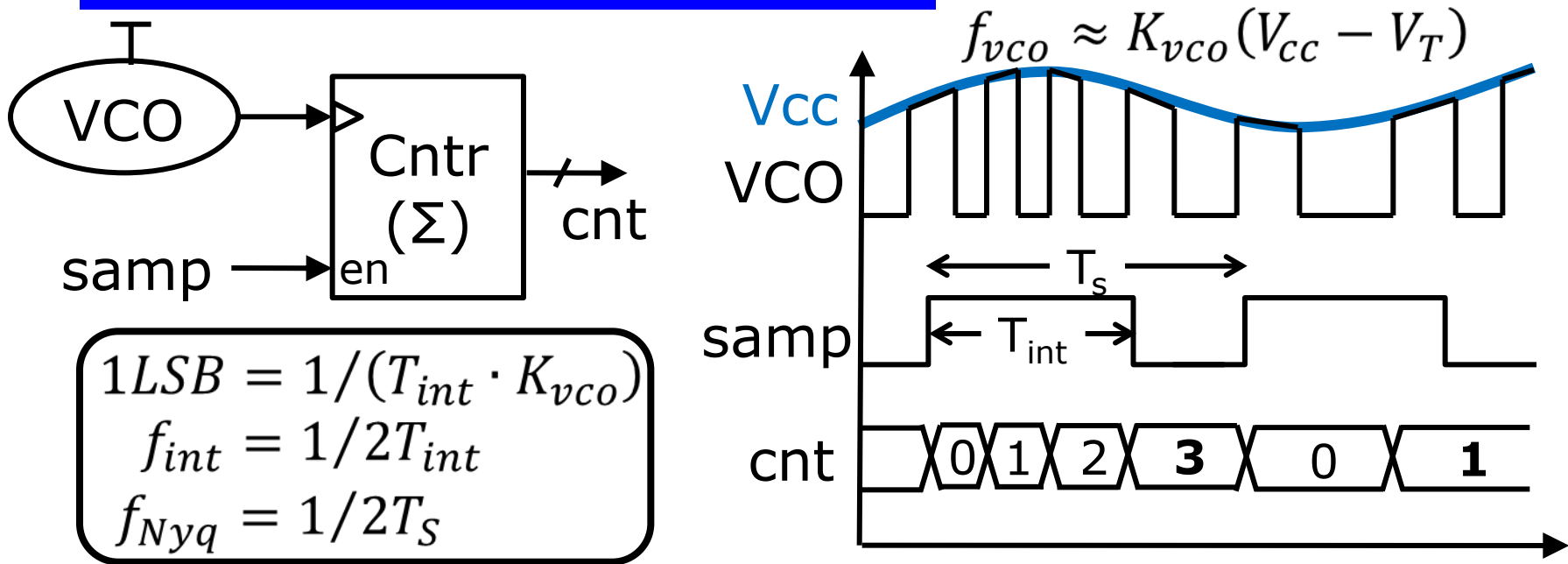


- Idea #1: Count Async. VCO edges during fixed  $\Delta T$ 
  - Pro: Directly attach VCO to power supply, real- or equivalent-time meas.
  - Con: Quant. error trades off with  $f_{int}$  and  $f_{Nyq}$
- *This is a variation of the Code Density Test!*



# Sampler Option #2: VCO-based ADC

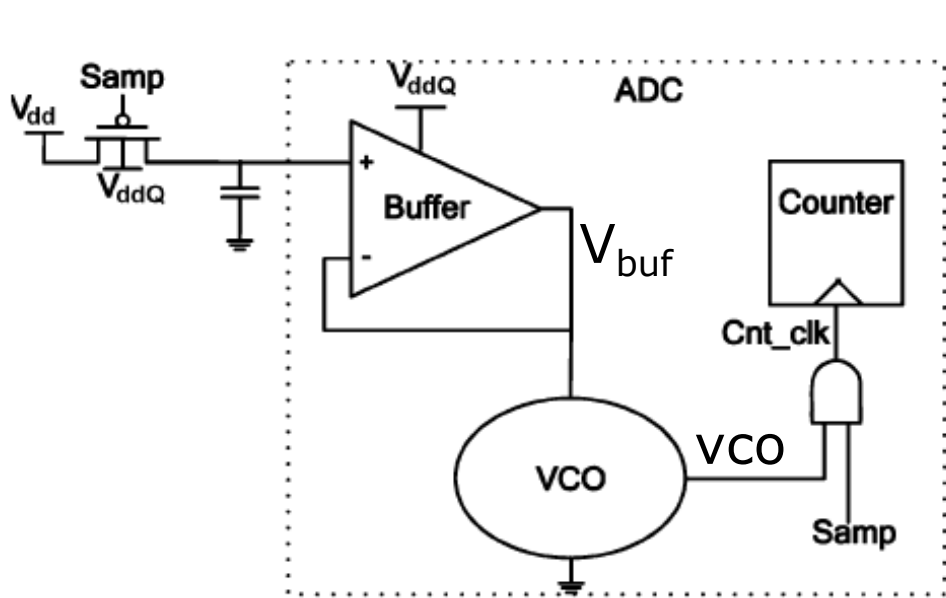

Ref: E. Alon, VLSIC 2004

 


□ Idea #2: Sample-and-Hold the supply voltage

- Pro: Quantization error is independent of  $f_{int}$  and  $f_{Nyq}^*$
- Con: S/H leakage, Supply voltage buffer, Equivalent-Time measurement only (or else  $f_{Nyq}$  degrades)

\*Note: This is the Equivalent-Time Nyquist frequency

# Sampler Option #2: VCO-based ADC

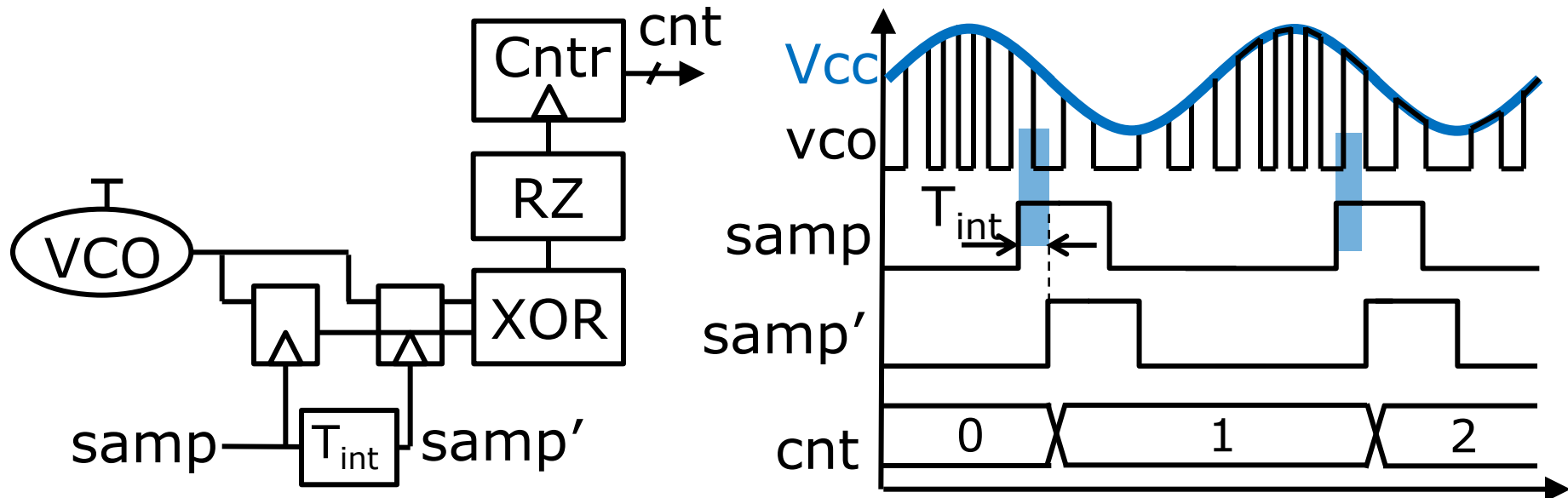


Ref: V. Abramzon, E. Alon, ESSCIRC 2005

## □ Idea #3: Very short aperture with averaging



- Pro: Quantization error independent of  $f_{int}$  and  $f_{Nyq}$ .  
Directly connect VCO to power supply. No sampling switch. Very short  $T_{int}$ , set by passive RC and calibrated.
- Con: Not capable of real-time measurement, increased measurement time

# Sampler Calibration

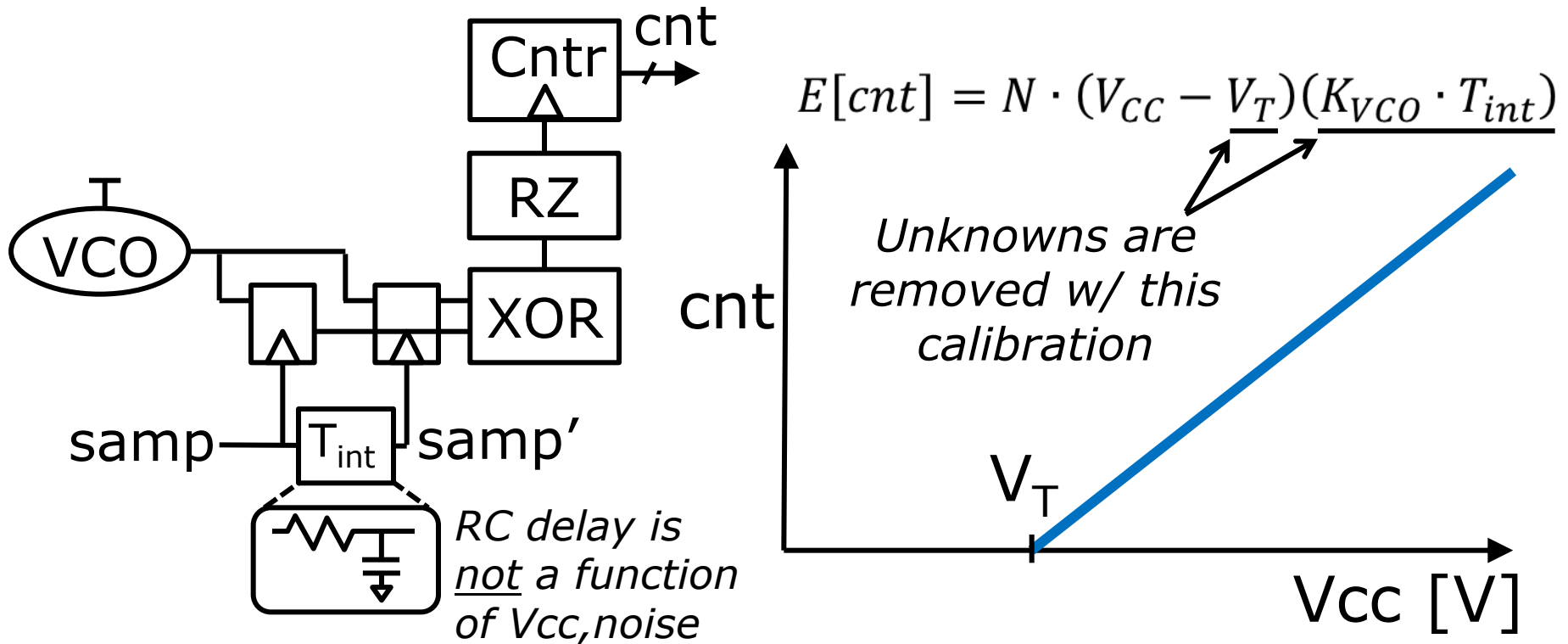


- Map  $V_{CC} \rightarrow cnt$  with DC sweep of  $V_{CC}$
- Can be approximated as linear fit
- Avoid operating close to  $V_T$  - Variation/Linearity

# Supply Noise Meas. on I/O Testchip

 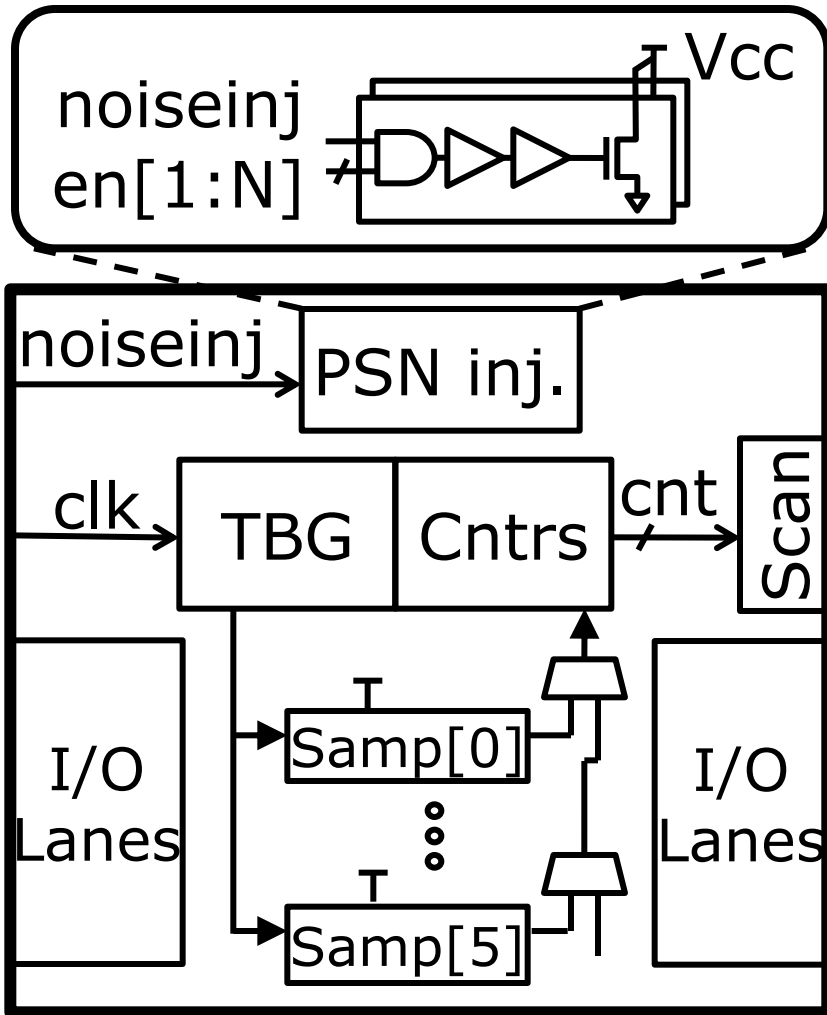


Ref: F. O'Mahony, ISSCC 2010

# Periodic Noise Waveform Capture

 

# Power Supply Impedance Meas.

 

Step Response  
(w/ current step)


$dV/dt$

Impulse Response

$DFT$



Freq. Response  
 **$Z(f)$**

# Impedance Measurement Example

 

□ Note that Q depends on the power grid loading

# Measuring PSD w/ Autocorrelation

  


$DFT$

Power Spectral  
Density  
**PSD(f)**





# Circuitry for PSD Meas.

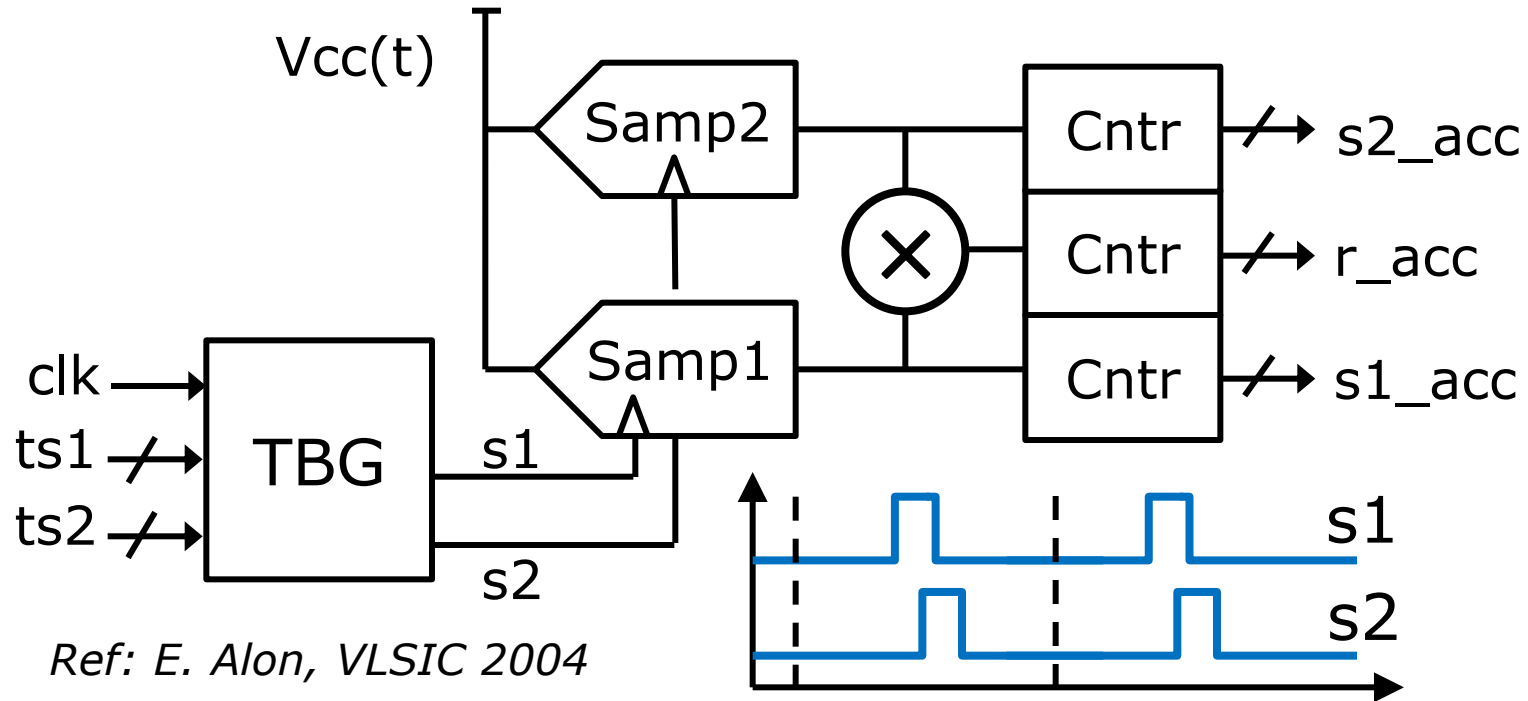

- Measure  $R(\tau)$  with dual samplers
- Digitally sweep  $\tau = ts2 - ts1$
- DFT of  $R(\tau) = \text{PSD}$  (post-process off-chip)

# PSD Measurement Example

---

  


# Outline

---


- Delay Measurement
- Power Supply Characterization
- **I/O System Characterization**
  - Bit Error Rate (BER) Eye
  - Waveform capture
  - RX noise
  - Clk-data jitter

# Transceiver Metrics

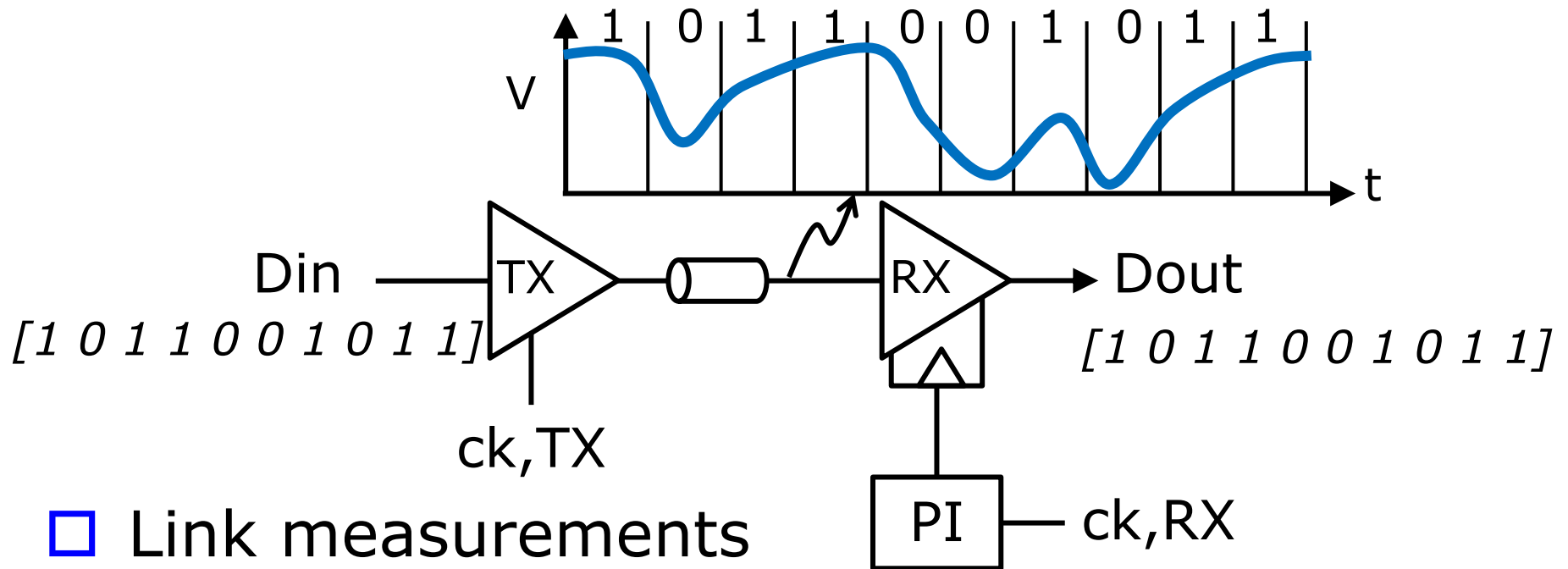


- Link measurements
  - BER eye / Eye Margins
  - Receiver noise
  - Clock/Data jitter
  - Waveform capture

# BER Eye and Margins

 

- Probability of error in Equivalent time
- Sweeps Voltage and Equivalent Time
- "Margin" represents how robust the link is
- Voltage margin (vert.), Timing margin (horiz.)


# BER Eye and Margins

 

- Probability of error in Equivalent time
- Sweeps Voltage and Equivalent Time
- "Margin" represents how robust the link is
- Voltage margin (vert.), Timing margin (horiz.)


# BER Eye Measurement

---

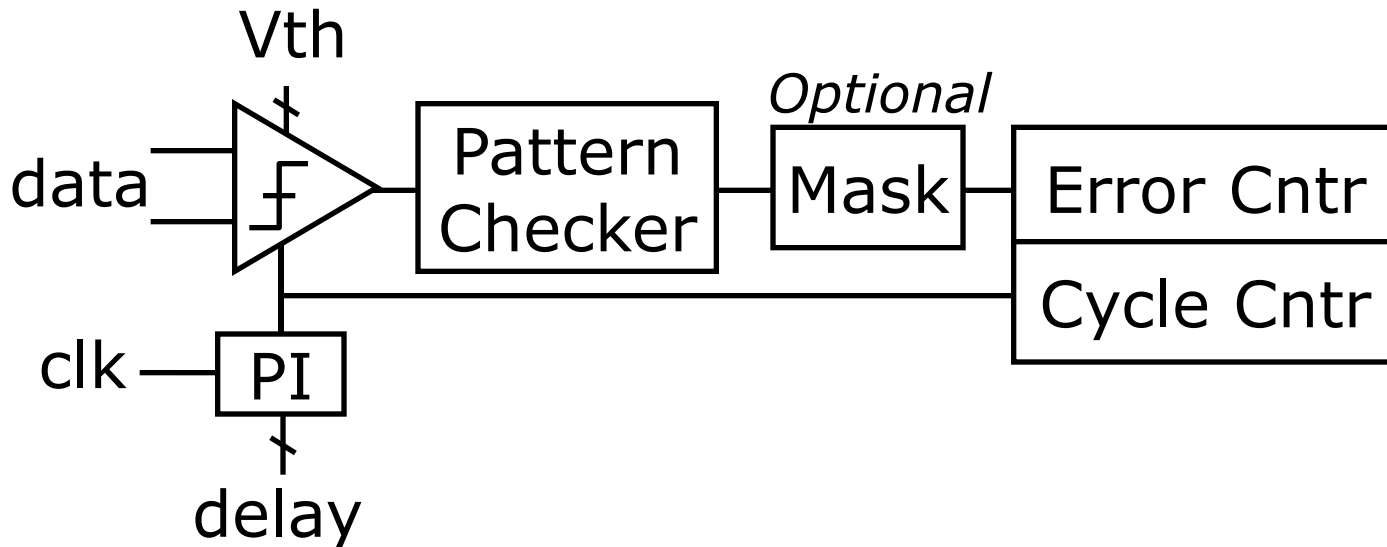

- Phase Interpolator (PI) → Time Sweep
- Sampler Offset → Voltage Sweep
- Masking can be used optionally to target certain characteristics
  - e.g. Loop-unrolled eye, Even/Odd eyes

# BER Eye Measurement

 


- Keep in mind  $N_{\text{err}}/N_{\text{bits}}$  is just an *estimation* of BER
- Rule of Thumb: 95% Confidence Level requires error-free transmission for  $N_{\text{bits}} = 3 \times \text{BER}_{\text{min}}$ 
  - e.g. No errors for  $3 \times 10^{12}$  bits indicates  $\text{BER} \leq 10^{-12}$  with 95% certainty

Ref: <http://cp.literature.agilent.com/litweb/pdf/5989-2933EN.pdf>



# BER Eye Measurement

 


- Keep in mind  $N_{\text{err}}/N_{\text{bits}}$  is just an *estimation* of BER
- Rule of Thumb: 95% Confidence Level requires error-free transmission for  $N_{\text{bits}} = 3 \times \text{BER}_{\text{min}}$ 
  - e.g. No errors for  $3 \times 10^{12}$  bits indicates  $\text{BER} \leq 10^{-12}$  with 95% certainty

Ref: <http://cp.literature.agilent.com/litweb/pdf/5989-2933EN.pdf>


# Measured BER Eye Example

---

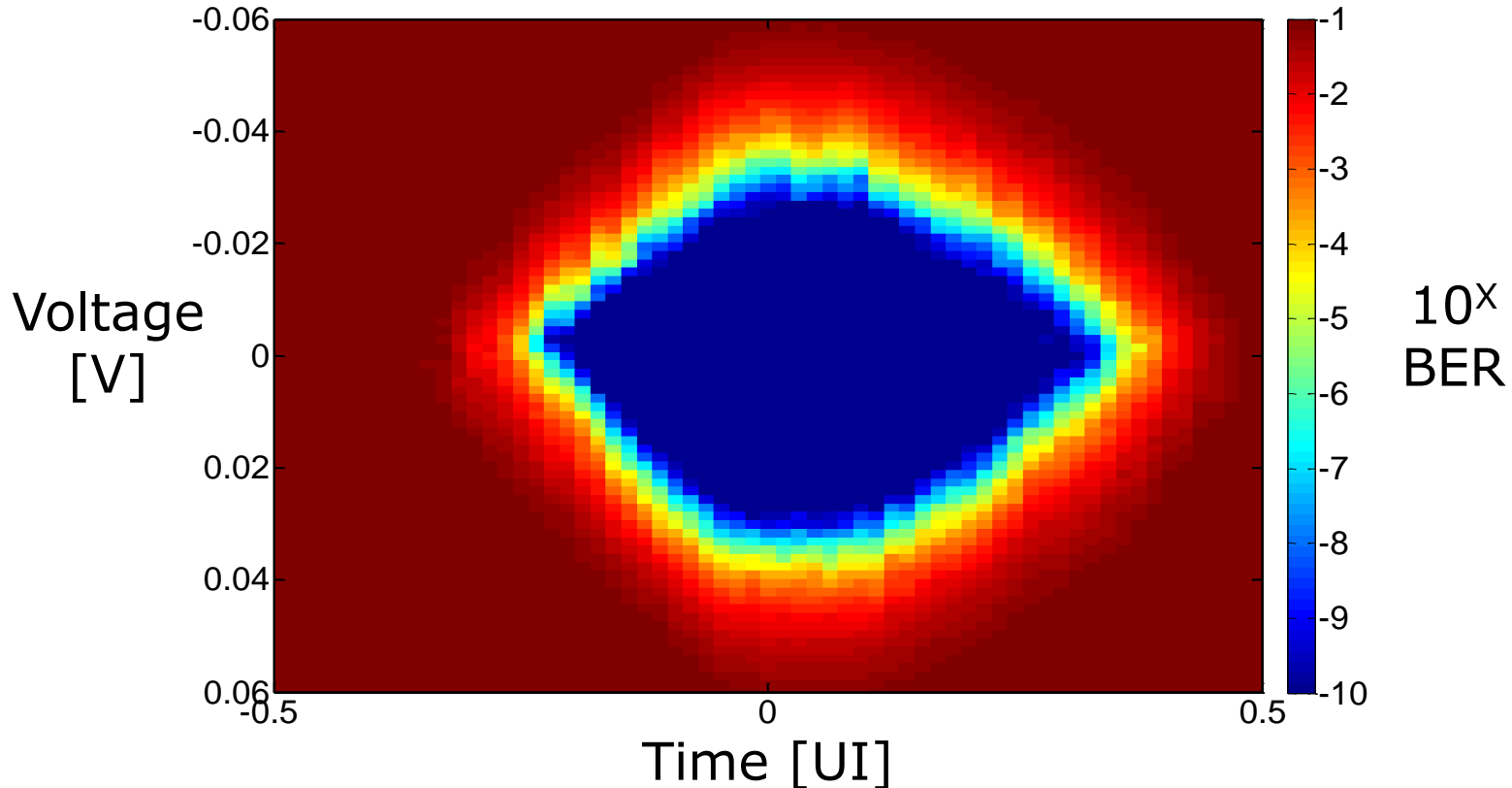



- Often measure a subset of points to save time
  - Voltage or Time Margin "bathtub" plots

# RX Sampler Characterization

 


- Voltage CDF (PDF) → RX characterization
- Reflects all RX noise as “input referred”
- Fully in-situ if TX provides  $V_{DC}$

# RX Sampler Characterization

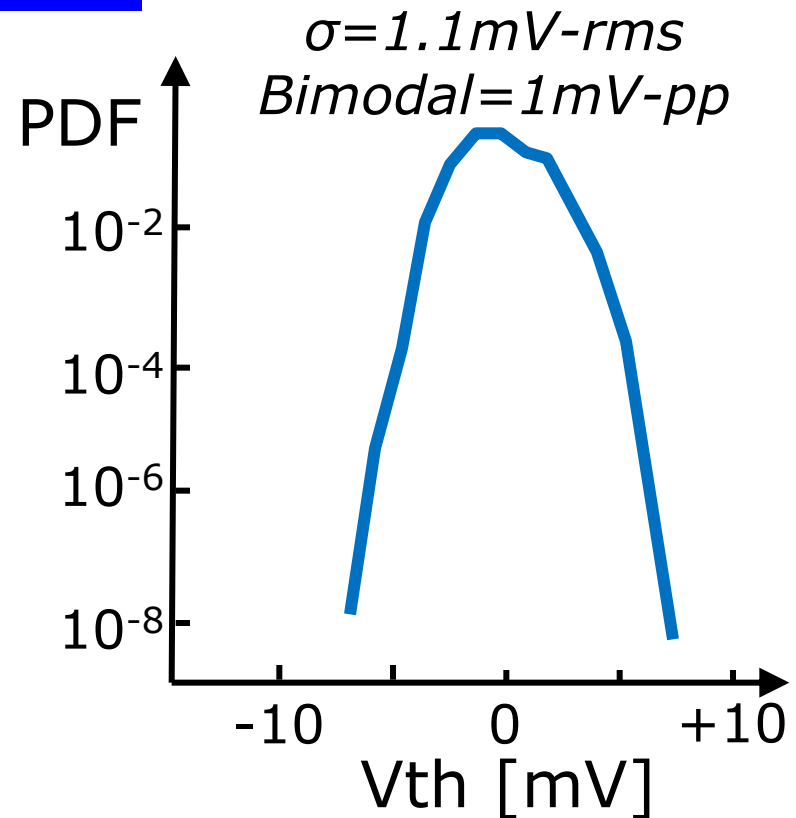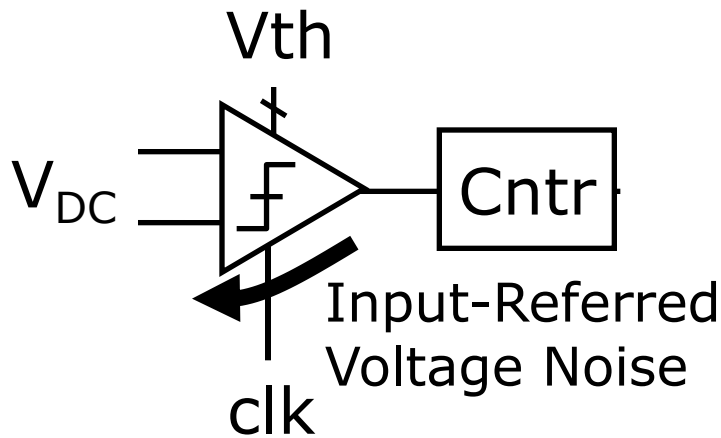

- Voltage CDF (PDF)  $\rightarrow$  RX characterization
- Reflects all RX noise as "input referred"
- Fully in-situ if TX provides  $V_{DC}$


# Clock-Data Jitter

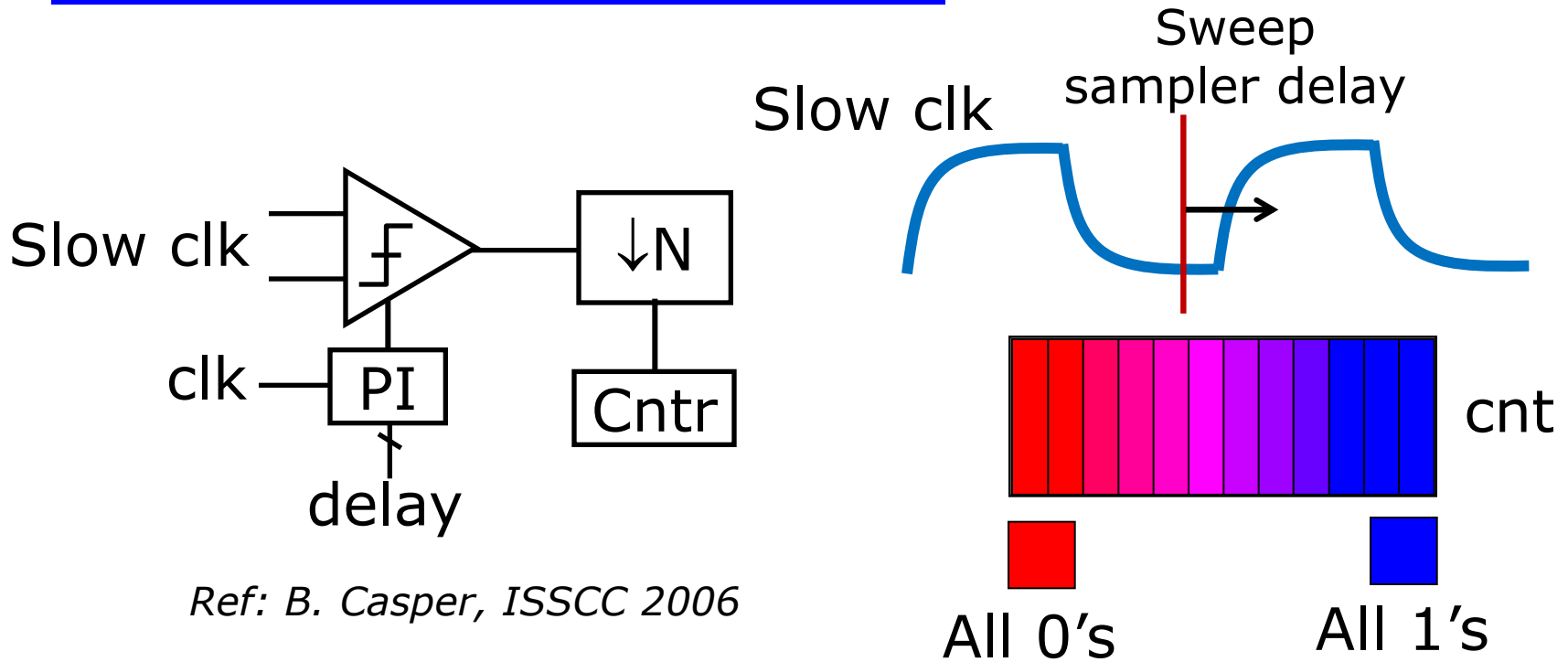


Ref: B. Casper, ISSCC 2006

- Time CDF (PDF) → RX clk-data jitter
- Fully in-situ if TX provides "slow clock"
- Applicable to any clock circuit

# Clock-Data Jitter

 



Ref: B. Casper, ISSCC 2006

 

- Time CDF (PDF) → RX clk-data jitter
- Fully in-situ if TX provides “slow clock”
- Applicable to any clock circuit
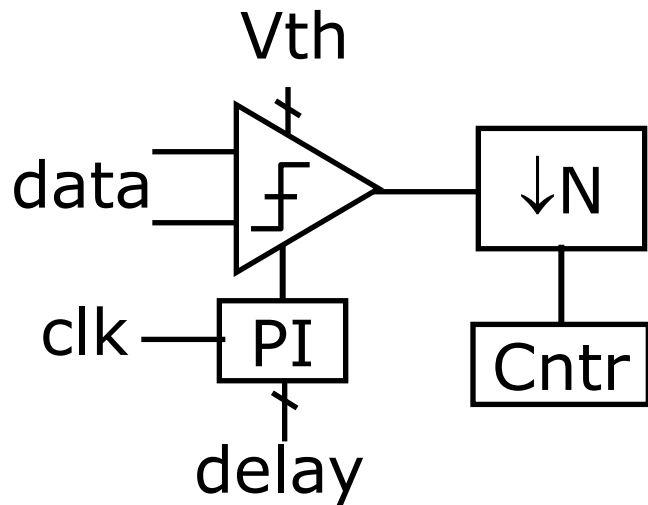 
# On-die waveform capture

- Mask 1:N periodic N-bit waveform
- CDF mean =  $V(t)$
- PI sweeps time





Ref: B. Casper, JSSC 2003

Equiv. Time
  
# On-die waveform capture

- Mask 1:N periodic N-bit waveform
- CDF mean =  $V(t)$
- PI sweeps time





Ref: B. Casper, JSSC 2003



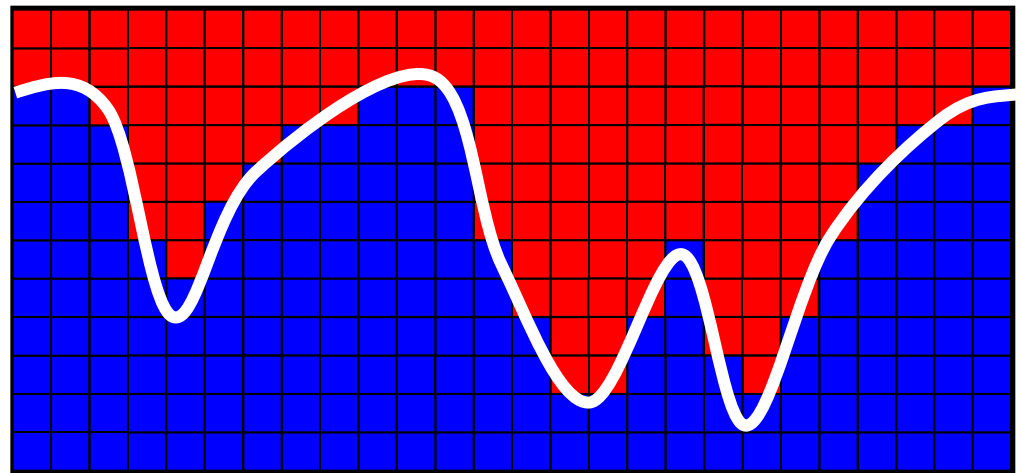 
# On-die waveform capture

- Mask 1:N periodic N-bit waveform
- CDF mean =  $V(t)$
- PI sweeps time




Equiv. Time

 

Ref: B. Casper, JSSC 2003

# Waveform Capture Example

---

 

# Summary

---

- On-die measurement is useful when:
  - No external equipment available
  - Accuracy lost by routing out to scopes
- A simple set of digital-friendly techniques provide accurate time and voltage on-chip
  - Code Density Test
  - Equivalent time/Sub-sampling/Bit Masking
  - Time/Voltage sweep with 1-bit ADC
- Use measurement circuits that are already on chip!
  - Offset comparators, phase shifters, digital counters, pattern checkers

# Key Refs: Delay Measurement

---

- F. O'Mahony et al. "A 10-GHz global clock distribution using coupled standing-wave oscillators," ISSCC 2003, paper 24.4. Expanded version in *JSSC*, Nov. 2003, pp. 1813-1820.
- J. Doernberg et al., "Full-speed testing of A/D converters," *JSSC*, pp. 820- 827, Dec 1984.
- L.-M Lee et. al, "A sub-10-ps multiphase sampling system using redundancy," *JSSC* Jan. 2006, pp. 265-273.
- L. Xia, et al., "Sub-2ps, static phase error calibration technique incorporating measurement uncertainty cancellation for multi-gigahertz time-interleaved T/H circuits," *TCAS-I*, Jan. 2012, pp.1-9.
- Mansuri, M. et al., "An on-die all-digital delay measurement circuit with 250fs accuracy," *Symp. VLSI Circuits (VLSIC)* 2012, pp.98-99.

# Key Refs: Power Supply Measurement

---

- E. Alon et al., "Circuits and Techniques for High-Resolution Measurement of On-Chip Power Supply Noise," *Symp. VLSI Circuits (VLSIC) 2004*, pp. 463-466.
- V.A. Abramzon et al., "Scalable circuits for supply noise measurement," *ESSCIRC 2005.*, pp. 463- 466.
- S. Naffziger et al., "The implementation of a 2-core, multi-threaded itanium family processor," *JSSC*, pp. 197-209, Jan. 2006.
- E. Alon, "On-Die Power Supply Noise Measurement Techniques," *IEEE Transactions on Advanced Packaging*, pp.248-259, May 2009.
- F. O'Mahony et al., "A Low-Jitter PLL and Repeaterless Clock Distribution Network for a 20Gb/s Link," *Symp. VLSI Circuits (VLSIC)*, 2006, pp.29

# Key References: I/O Characterization

---

- Soumyanath, K. et al., "Accurate on-chip interconnect evaluation: a time-domain technique," *JSSC*, pp.623-631, May 1999.
- M. Takamiya, M. Mizuno, and K. Nakamura, "An on-chip 100GHz-sampling rate 8-channel sampling oscilloscope with Embedded sampling clock generator," *ISSCC* 2002.
- B. Casper et al., "An 8-Gb/s simultaneous bidirectional link with on-die waveform capture," *JSSC*, pp. 2111- 2120, Dec. 2003.
- D. Oh et al., "In-situ characterization of 3D package systems with on-chip measurements," *Electronic Components and Technology Conference (ECTC)*, 2010 pp.1485-1492.
- M. Mueller et al., "Total Jitter Measurement at Low Probability Levels, Using Optimized BERT Scan Method", Agilent White Paper.  
<http://cp.literature.agilent.com/litweb/pdf/5989-2933EN.pdf>
- B. Casper et al., "A 20Gb/s Forwarded Clock Transceiver in 90nm CMOS," *ISSCC* 2006, pp.263-272.
- F. O'Mahony et al., "A 47x10 Gb/s 1.4 mW/Gb/s Parallel Interface in 45nm CMOS," *JSSC*, pp. 2828 - 2837, Dec. 2010.