



S I L I C O N L A B S

www.silabs.com

ISSCC 2011 RF Highlights

Ramin K. Poorfard

03/09/2010

- **Overall and RF Paper Statistics**



- **Trends in Wireless architectures**
 - SAW-less WBCDMA transceivers
 - Technology Scalable RF front-ends

- **RF Building Blocks**
 - Push-pull LNA's
 - Phase shifters
 - Harmonic reject mixers
 - Noise cancelling LNA's

Overall papers statistics

➤ **669 submission with 211 accepted (32% acceptance rate)**



➤ **28 paper sessions**

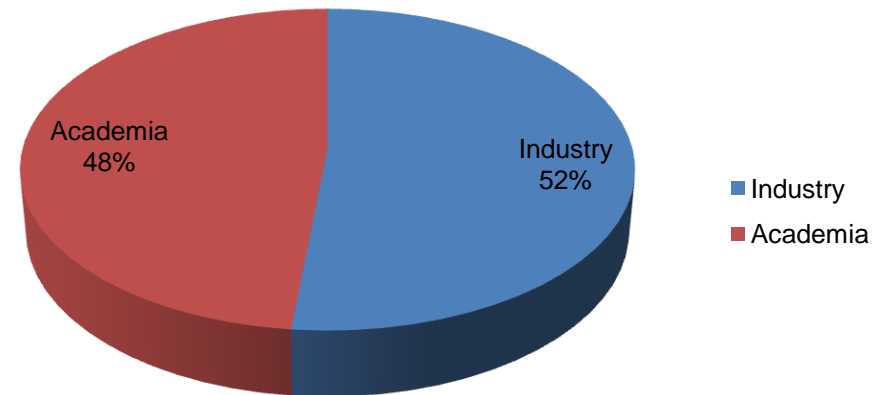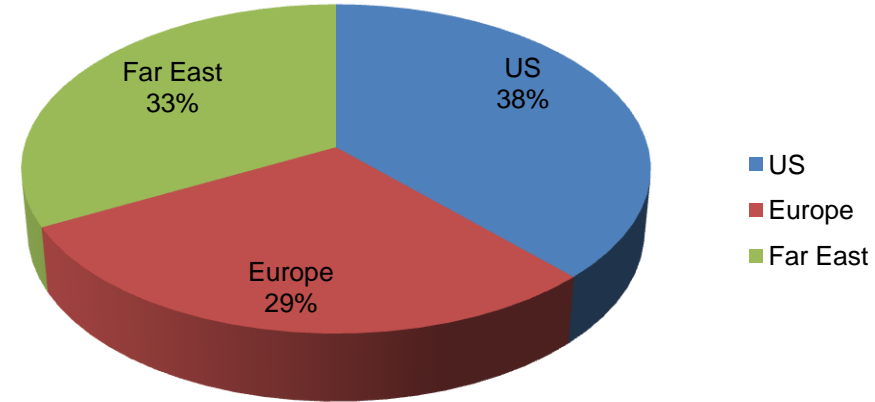

RF papers statistics

➤ RF session titles:

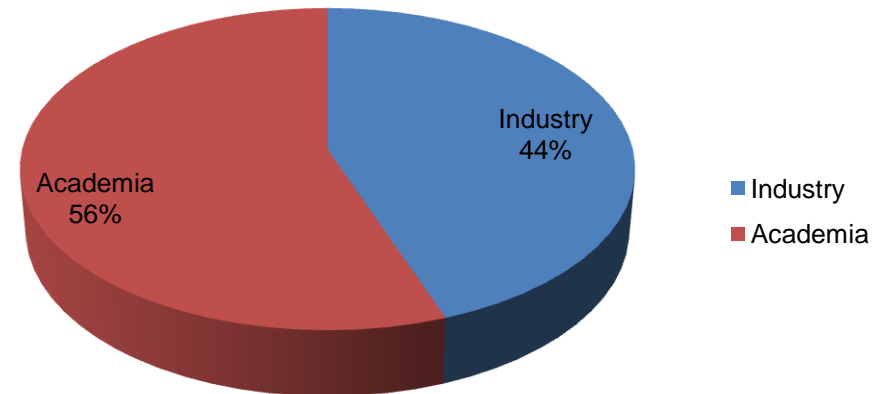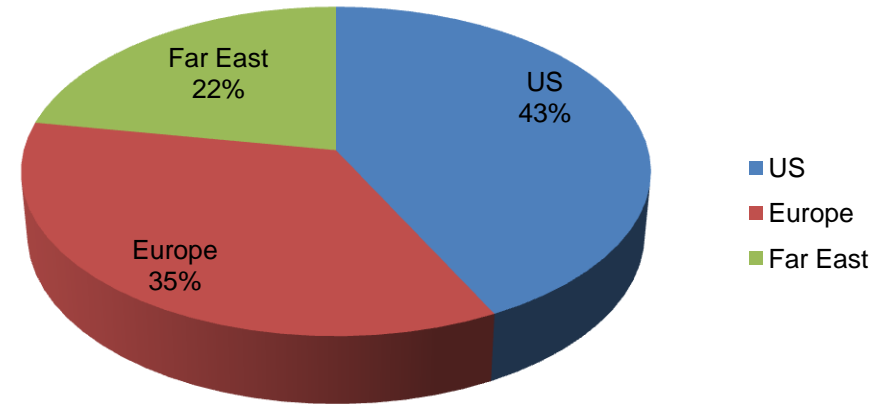- RF techniques
- PLLs
- Wireless & mm-Wave Connectivity
- mm-Wave Design Techniques
- Cellular
- Transmitter blocks
- Low power wireless



Trends in Wireless architectures

➤ RF topics were fairly diversified.

➤ Two trends, however, stood out.

1. SAW-less WBCDMA transceivers

- TX side solutions (Polar transmitters, 25% duty cycle passive mixing)
- RX side solutions (High IIP2 RX path)

2. Technology scalable RF circuits

- Wide-band Inductor-less designs
- High-IF architectures with no SAW filter


WBCDMA Issues

- **Simultaneous operation of TX and RX.**
- **The out-of-band TX noise can become in-band at RX.**
- **Large TX blockers also affect the RX through its nonlinearity.**
- **Duplexers are used to facilitate this.**
- **The TX/RX isolation, however, was not sufficient and further filtering was needed (Hence the extra SAW filters).**
- **The TX out-of-band noise can be overcome by using polar modulators**
 - Several papers were devoted to how to implement a practical polar modulator
- **A high dynamic RX chain would handle large TX blockers**
 - High IIP2 and IIP3 LNA and mixer architectures were proposed.

Polar modulators


- The Cartesian (I/Q) up-conversion, while simple, has extra noisy components (such as DACs, image filters and mixers)
- Also needs a low efficiency PA.
- Alternatively, one can convert I/Q to ρ (AM) and θ (PM).
- The AM path can be applied to the PA gain and/or supply hence improving the power efficiency.
- The PM can be done by modulating a VCO phase via a PLL.
- This approach is inherently less noisy. However, ...
- The delay between the two paths is crucial
 - Less than 1ns in WBCDMA
- The PM BW (8MHz) is wider than that of AM (3.84MHz) and is much wider the RF synthesizer BW (200 to 300kHz).
- Two point injection is usually used to solve this issue.

Two point injection

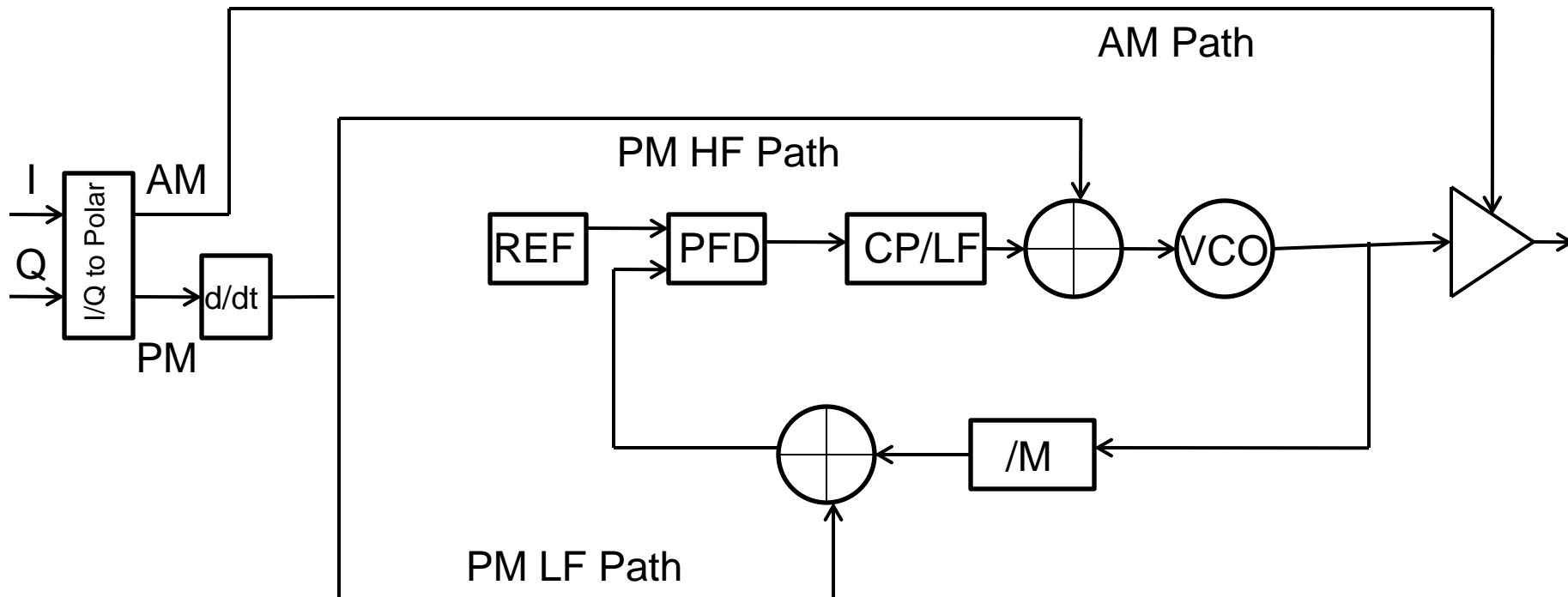


- Any injection at the VCO is HPF.
- Any injection at the PFD is LPF.
- Combined they can be ALL-pass filtered.
- VCO gain and linearity is a challenge.

3.1: Spur-Free All-Digital PLL

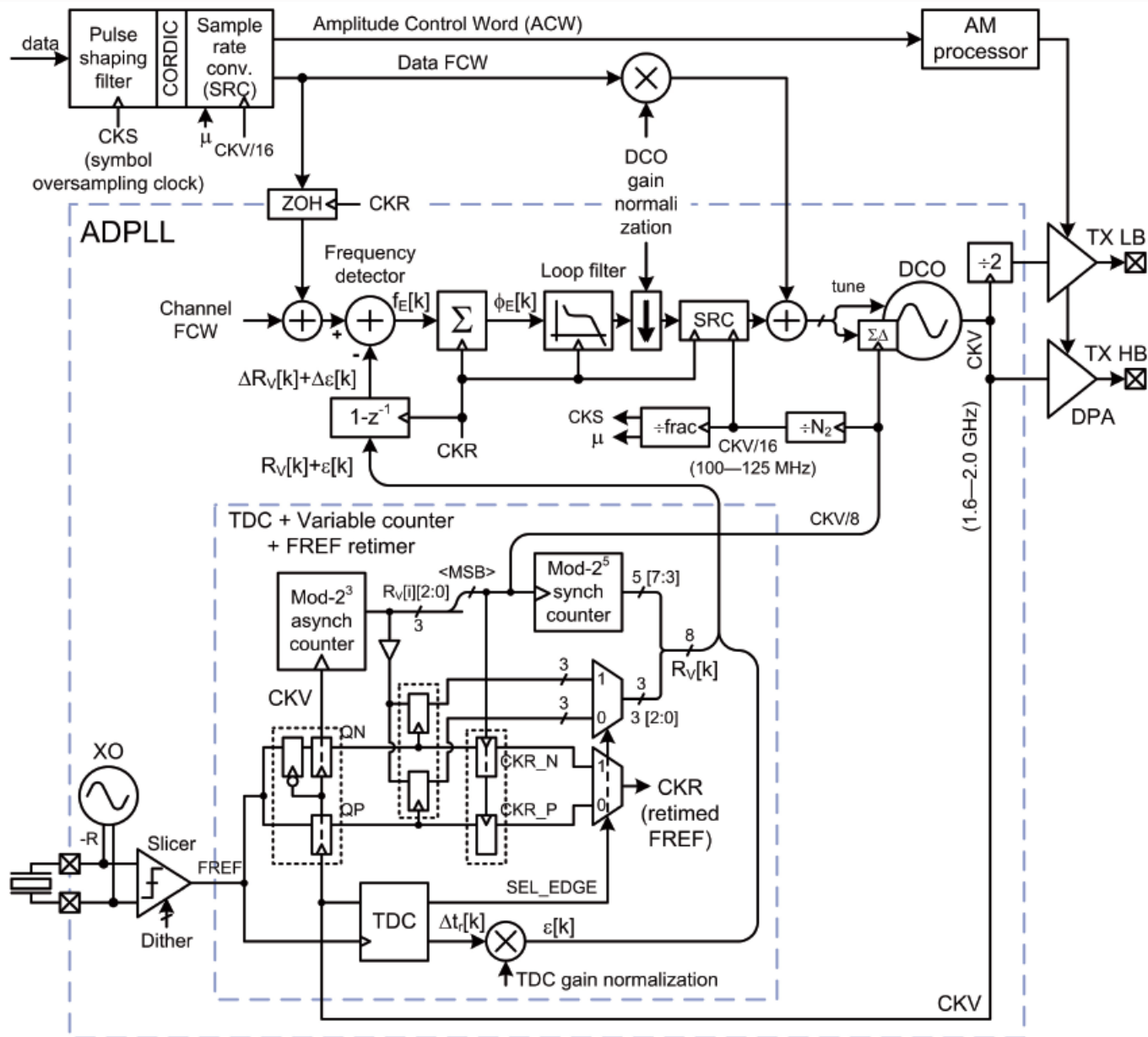


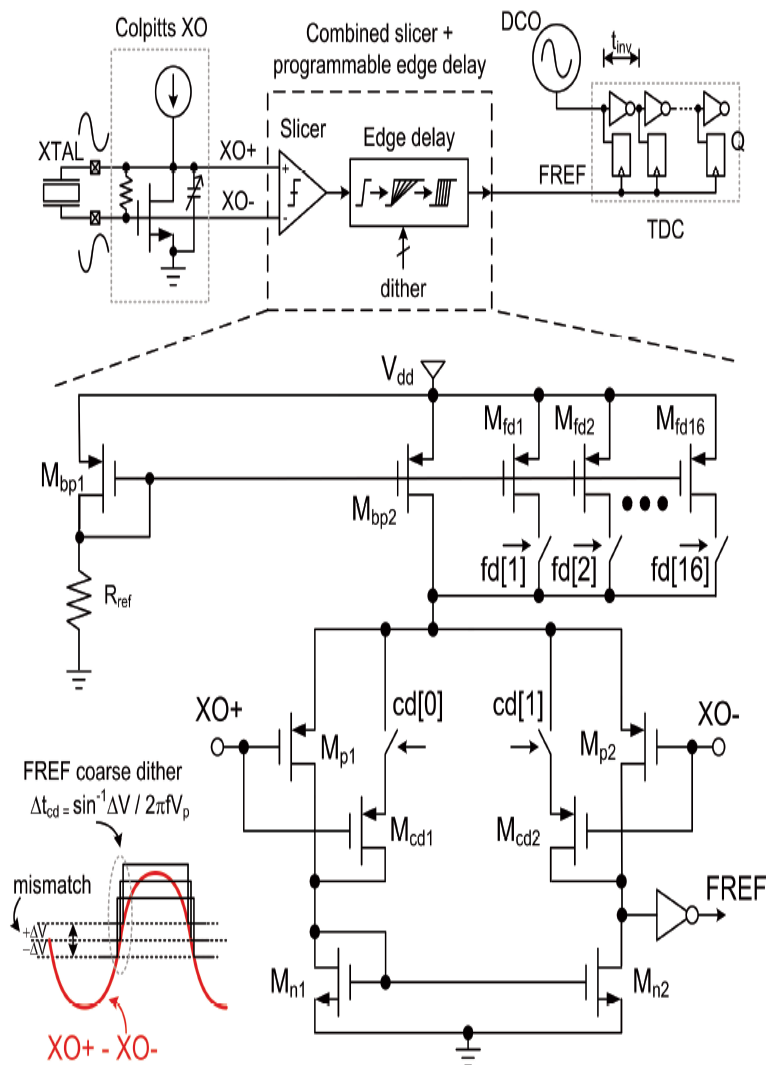
3.1: Spur-Free All-Digital PLL (cont.)

- Digital implementation handles the AM/PM delay problem.
- PLL blocks are implemented digitally, except VCO and PFD
 - ADC role is via Time-to-Digital Converters (TDC)
 - DAC role is played by switched cap varactor in the VCO
- Dithering is required to break periodic quantization noise
 - But it will increase phase noise
 - Use out-of-band tonal dither
- VCO gain calibration is still required.



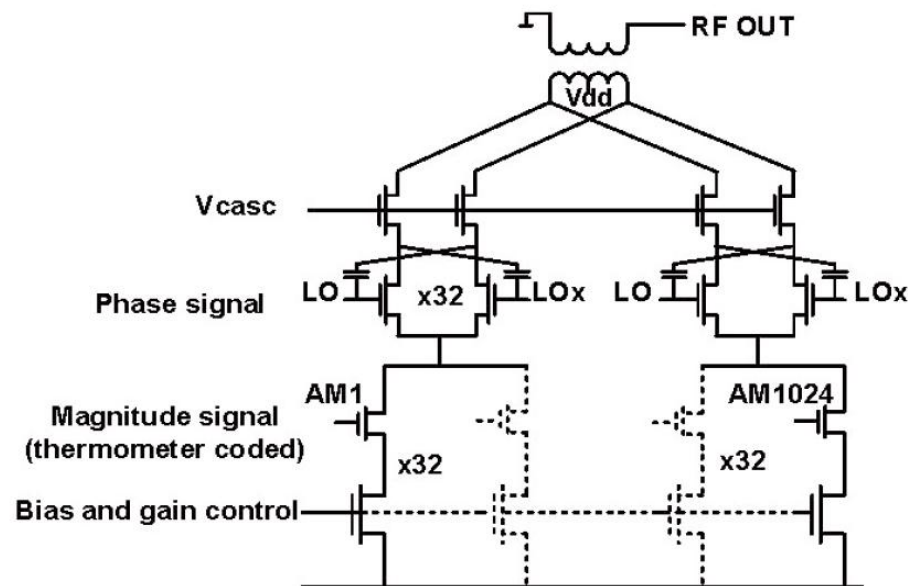
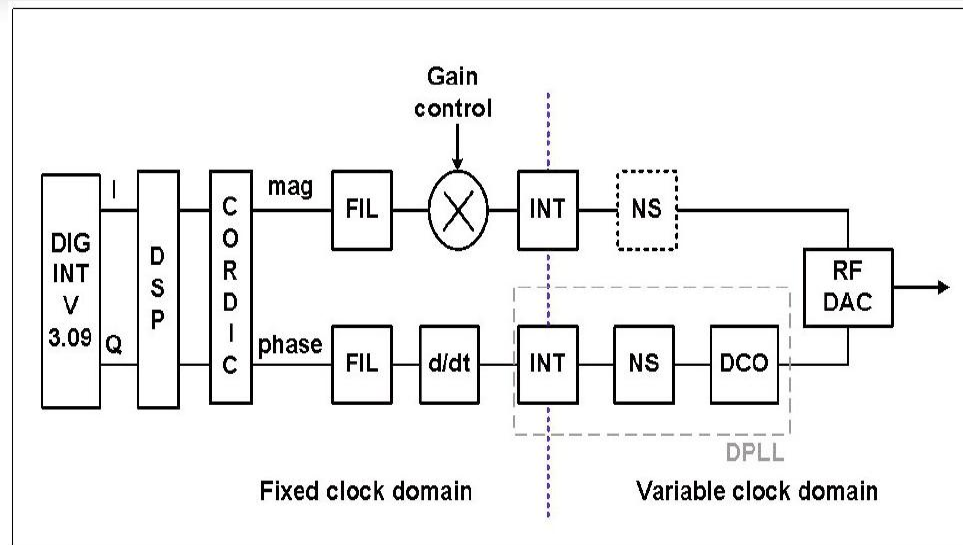
21.7 Polar transmitter employing RFDAC

- **All digital approach to solve the AM/PM problem.**
 - All digital PLL with two point injection
- **A High DR mixing DAC is used to merge the AM and PM paths.**
 - 10 thermometer, 4 binary
 - Oversampled to GHz range
 - 17-bit resolution in 3.84MHz (CDMA)
 - 19-bit resolution in 200kHz (EDGE)
- **LO leakage is managed by:**
 - Single ended tail currents
 - Cross coupled caps.
 - Shutting off LO signal to the unused portion of the mixer when the gain is lowered.
- **Interesting, but:**
 - Higher power
 - Low efficiency PA.



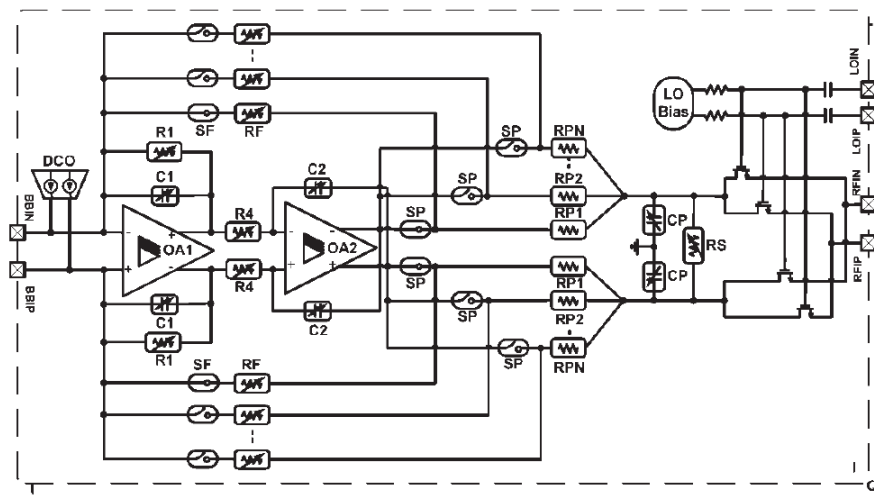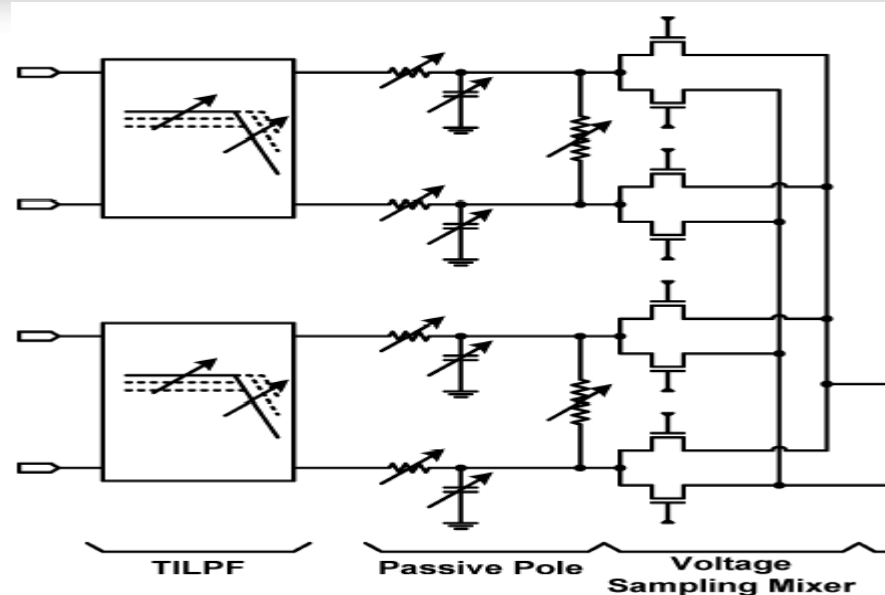21.6: Multiband LTE in 40nm CMOS

- **Passive mixers with 25% duty cycles are used.**
 - Seamlessly performs the adding function by utilizing non-overlapping LO's
 - Reduces the number of $V \rightarrow I$ and $I \rightarrow V$ converters, hence enhancing out-of-band noise and linearity.
- **The switching along with the load capacitor synthesizes a load resistance.**
 - Affects the mixer gain
 - Compensate via variable resistor
 - Also allows variable BW.
- **Variable resistor are nonlinear**
 - Put the switch in the feedback path.



Technology Scalable RF front-end

- **Finer line geometries allow digital circuit scaling.**
- **The conventional analog/RF circuits, however, do not.**
- **Two main reasons**
 - Matching requirements
 - Inductors
- **Low-IF and Zero-IF architectures eliminate the SAW filters but need high IIP2, low 1/f noise and small DC offsets**
 - All function of circuit area and hence non-scalable.
 - One paper proposed going back to high IF architectures which is insensitive to IIP2, 1/f noise and DC offset and therefore scalable.
 - A new method was proposed for highly selective filtering in lieu of SAW filters.
- **Narrow-band LNA's require on-chip inductances.**
 - Use wide-band LNA's (no inductor) with sufficient dynamic range instead.

3.5 Process scalable high-Q filters

➤ Zero-IF and Low-IF Architectures

- Large RC time constants for BB
- $1/f$ noise sensitive
- IIP2 sensitive
- DC offset sensitive




➤ These are all non-scalable

➤ Use High-IF architecture

- Back to the past, but scalable
- Small RC for BB
- No $1/f$ noise, IIP2 or DC offset issues
- Channel selection and Image rejection is an issue (SAW?)

➤ Need a BPF for channel selection and image rejection

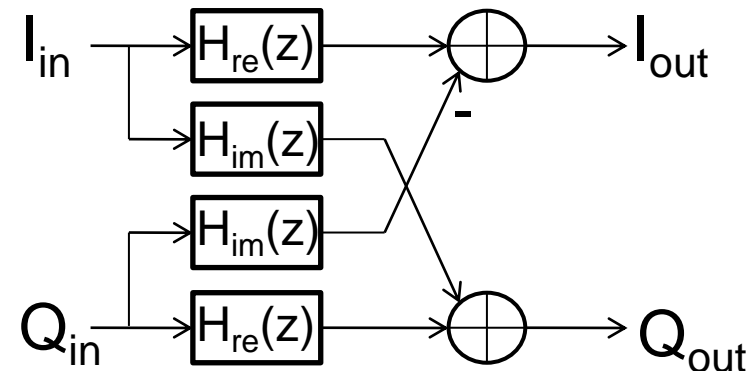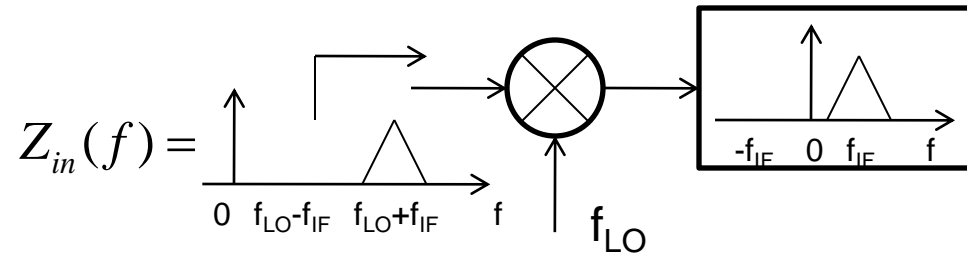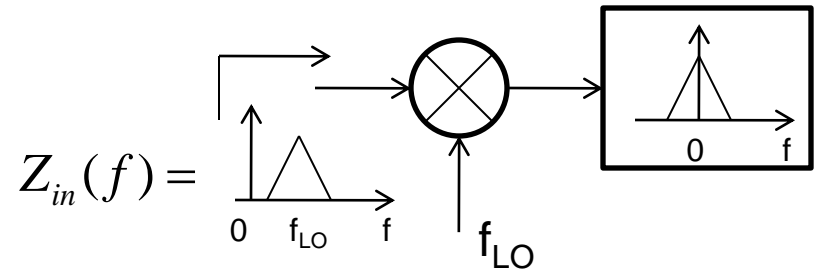- Channel selection: Use real_in/real_out Z for BPF centered at F_{sw} .
- Image Rejection: Use Complex_in/Complex_out Z



3.5: Process scalable high-Q filters (cont.)



➤ A complex loaded switched BPF at LNA input

- Protects the LNA from blockers and image.
- 10dB image rejection.
- The complex load is based on a 16-phase (16-path) switched capacitor.
- $16 \cdot F_{if}$ is chosen to push the folding frequencies to $15 \cdot F_{if}$ and $17 \cdot F_{if}$

➤ Use cascaded complex loaded switched BPF at BB for more IR.

➤ Issues:

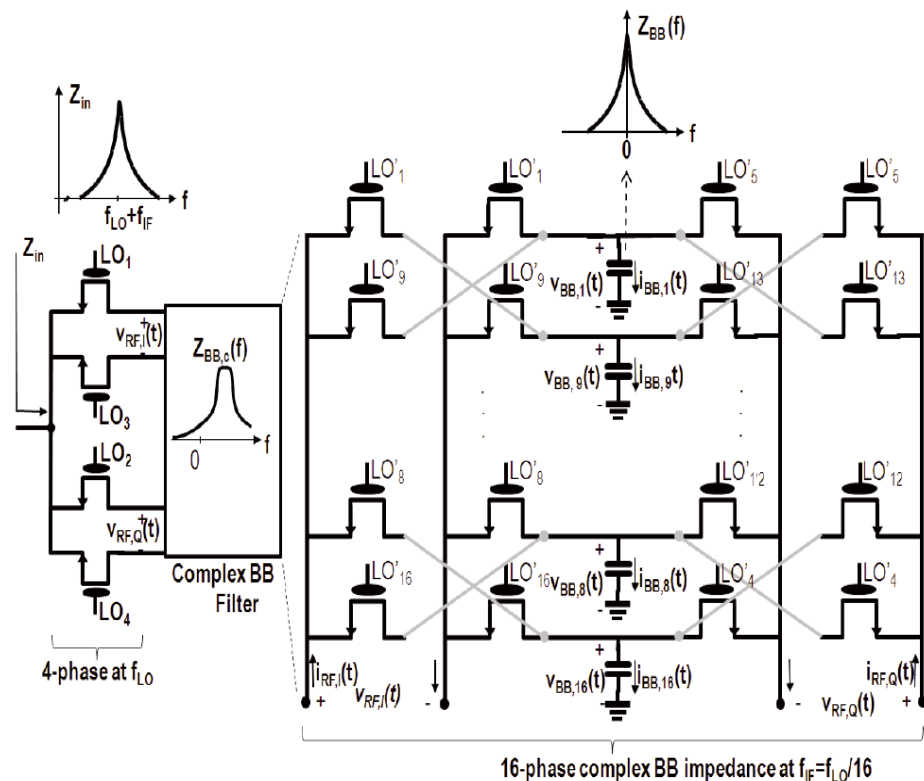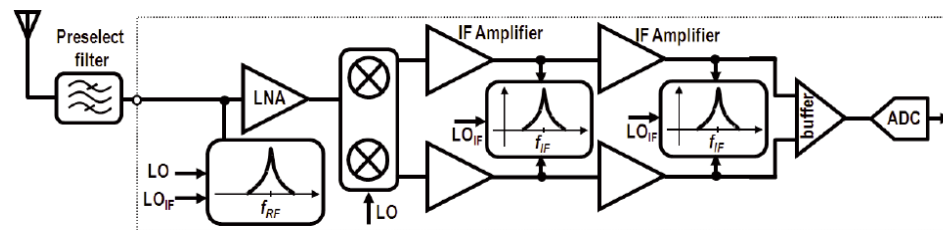- Some preselect filtering is still required to attenuate folding frequencies.
- Also, blockers at LO harmonics needs rejection.
- LO feed through to antenna.
- No Phase noise relaxation.
- Only 50dB image rejection.



21.4 Inductorless WBCDMA/EDGE in 65nm

➤ Multi-band RX need multiple LNA's

- No tunable pre-select filters

➤ Each NB LNA has inductors

- Too many inductors
- Not scalable

➤ Use WB shunt feedback



- To change the gain turn portion of the FB resistor into load.
- To keep the Z_{in} change the G_m .

➤ Current-mode mixer

- DC to RF virtual ground
- RI acting as degeneration for SW's making them linear.
- AC coupling help $1/f$ noise and IIP2



➤ Highly linear LNA and mixer

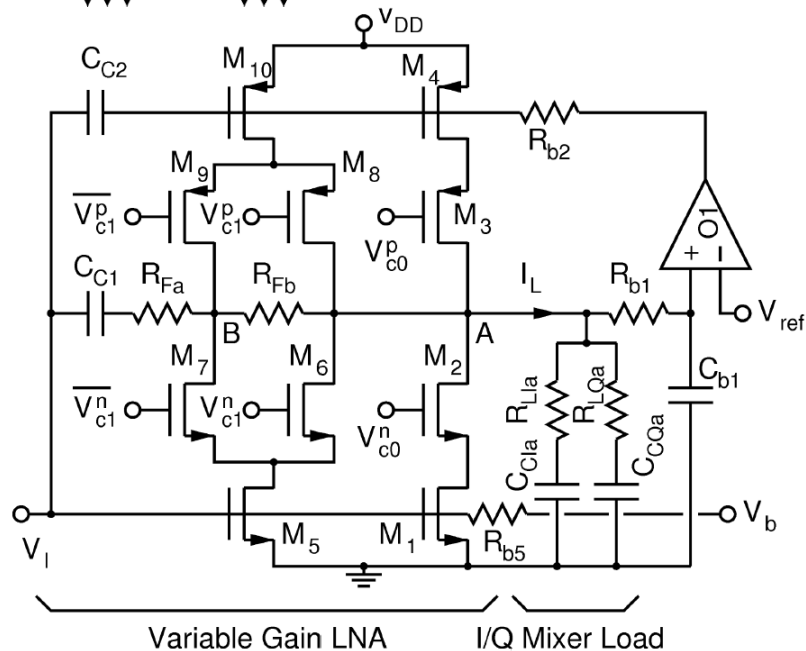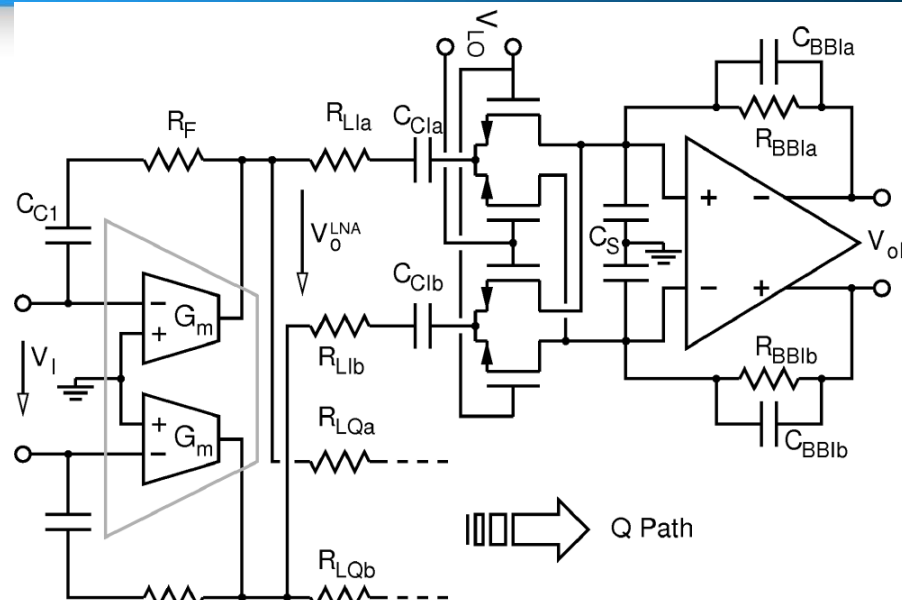- No need for inter-stage SAW
- LO coupling to RF minimized since there are no inductive coupling



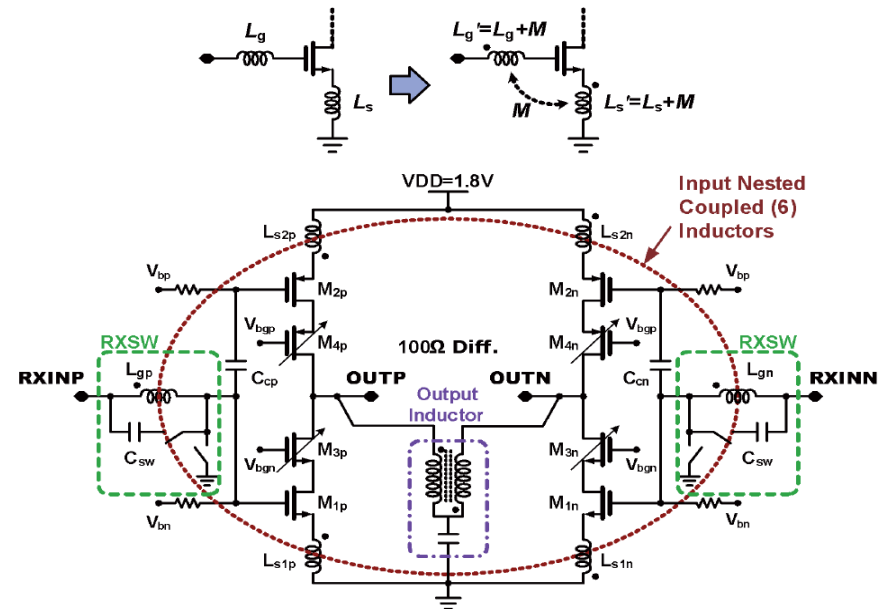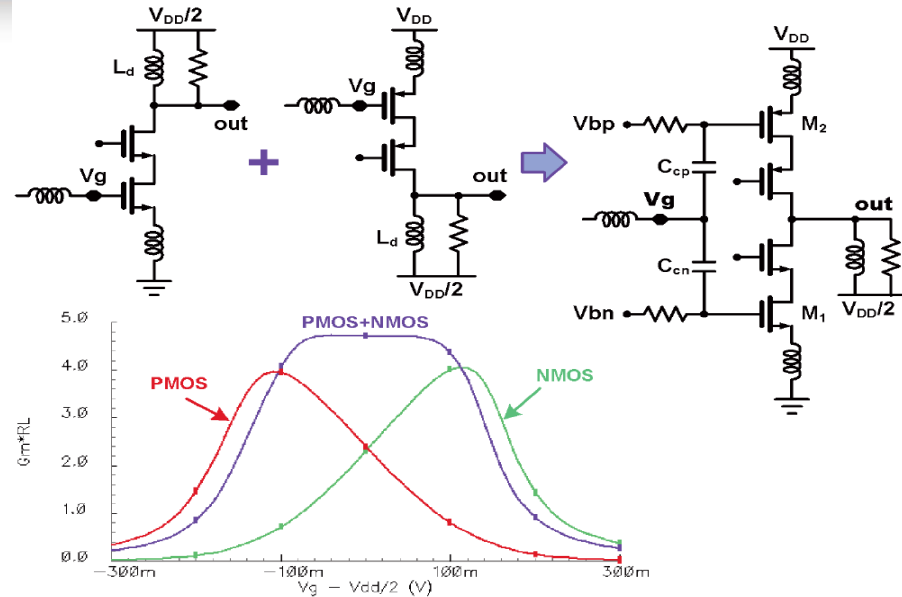3.3: Push Pull LNA in 32nm

- **Use both PMOS and NMOS Gm's**
 - Intel's 32nm High-K metal gate process has similar strength PMOS and NMOS
 - Similar value for L_p and L_n .
- **Stacked output to ensure reliability**
- **But twice as many inductors are used compared to the single-ended case.**
 - The gate inductors are used by the transmitter as well.
 - Since the current in the four inductors are either in-phase or out-of-phase, they can be closely coupled.
 - This will increase the effective inductance.
 - It also allows them to be laid out on top of one another.



3.7: Phase shifter in 65nm

➤ Multiple antenna Phased arrays

- Increase SNR
- Spatial interferer rejection

➤ Vector rotation



- Quadrature down conversion
- Sine and Cosine gains

➤ Sine and Cosine gains

- Non-uniform Sine step vs. phase step
- Gain need high resolution




➤ Approximate Sine and Cosine

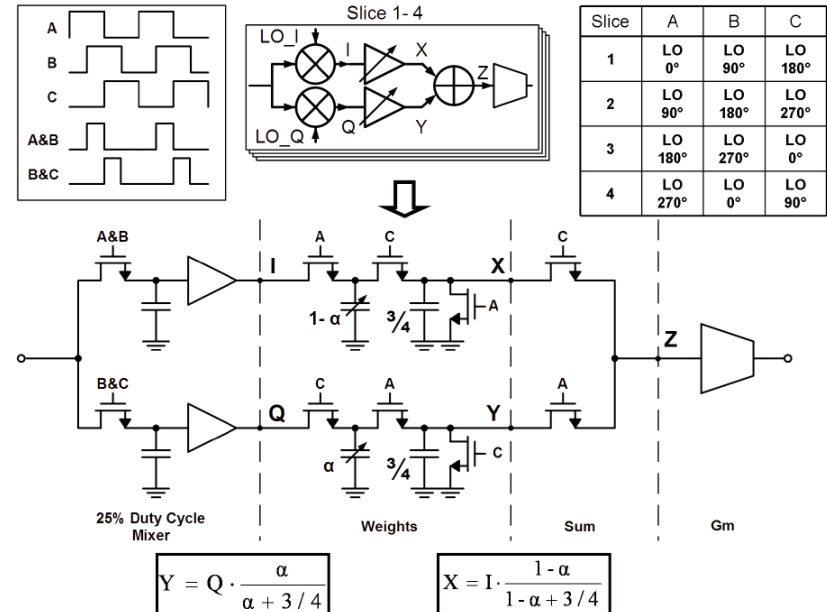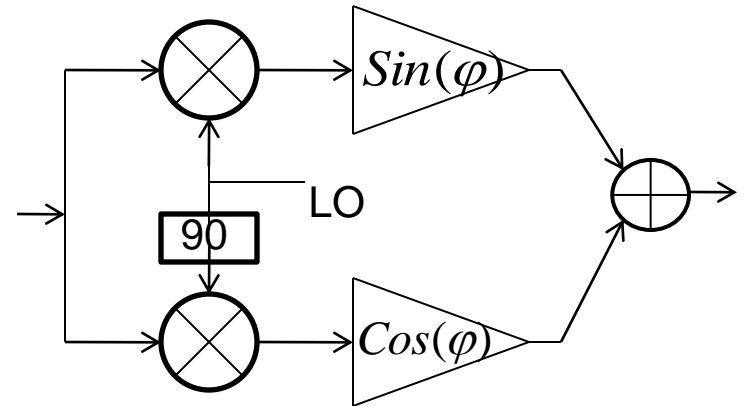- Use a fractional ratio
- Uniform phase step -> almost uniform alpha step (cap steps)
- Switch capacitor compatible
- The final summation is done via charge sharing as well.



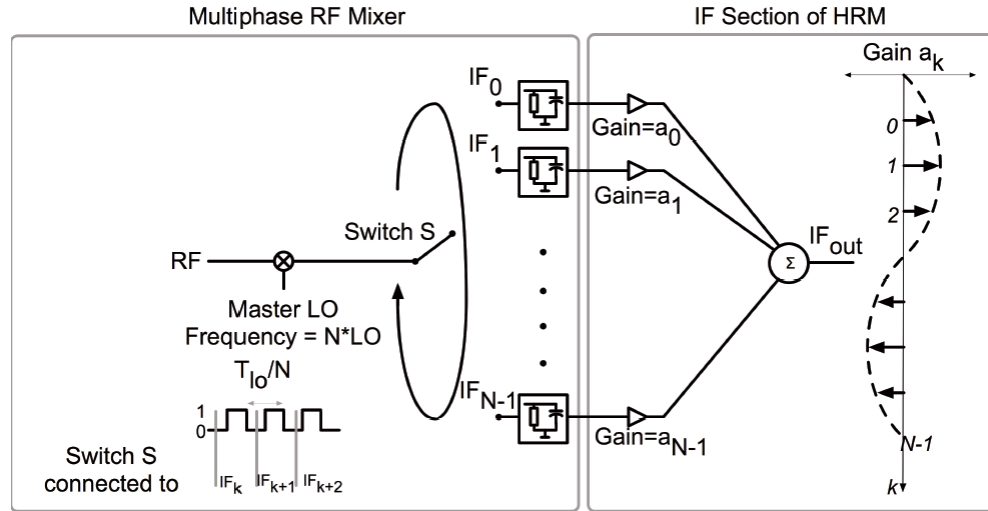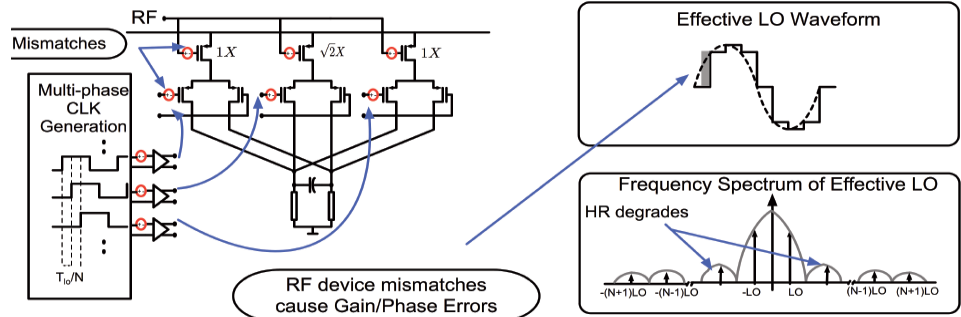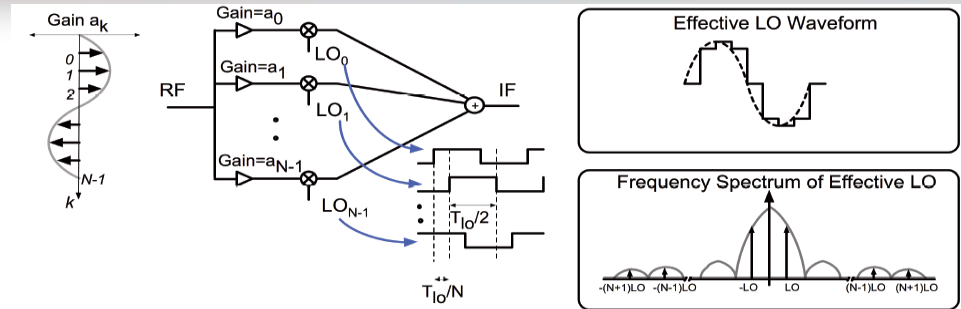3.8: Harmonic rejection mixer (HRM)

- **LO waveform is rectangular**
 - Rich in higher harmonics
- **Conventional HRM**
 - Uses RF weighting
 - Needs RF matching (hard to do)
- **Any imperfect matching causes HR deterioration**
- **What if the weighting is done in IF**
 - Lower frequency
 - Easier to match
- **Furthermore two layers of switches are used**
 - By commutating the second switch after the first one is done:
 - Second layer switch mismatch irrelevant
 - Robust 1/f noise and IIP2
 - Improved image rejection



9.7: Noise cancelling LNA

➤ TV application

- Wide-band input matching

➤ Conventional noise cancelling LNA

- Loop gain around M1 reduces its input impedance and noise.
- M2's gm is higher to reduce NF.

➤ But the output is not balanced.


- Higher IIP2
- Output buffers

➤ Use similar M1 and M2

- Use auxiliary G_{mx} for gain boosting around M1.
- Also biases the two gates.

➤ Use current balancer to enforce $i_{sig+} = -i_{sig-}$

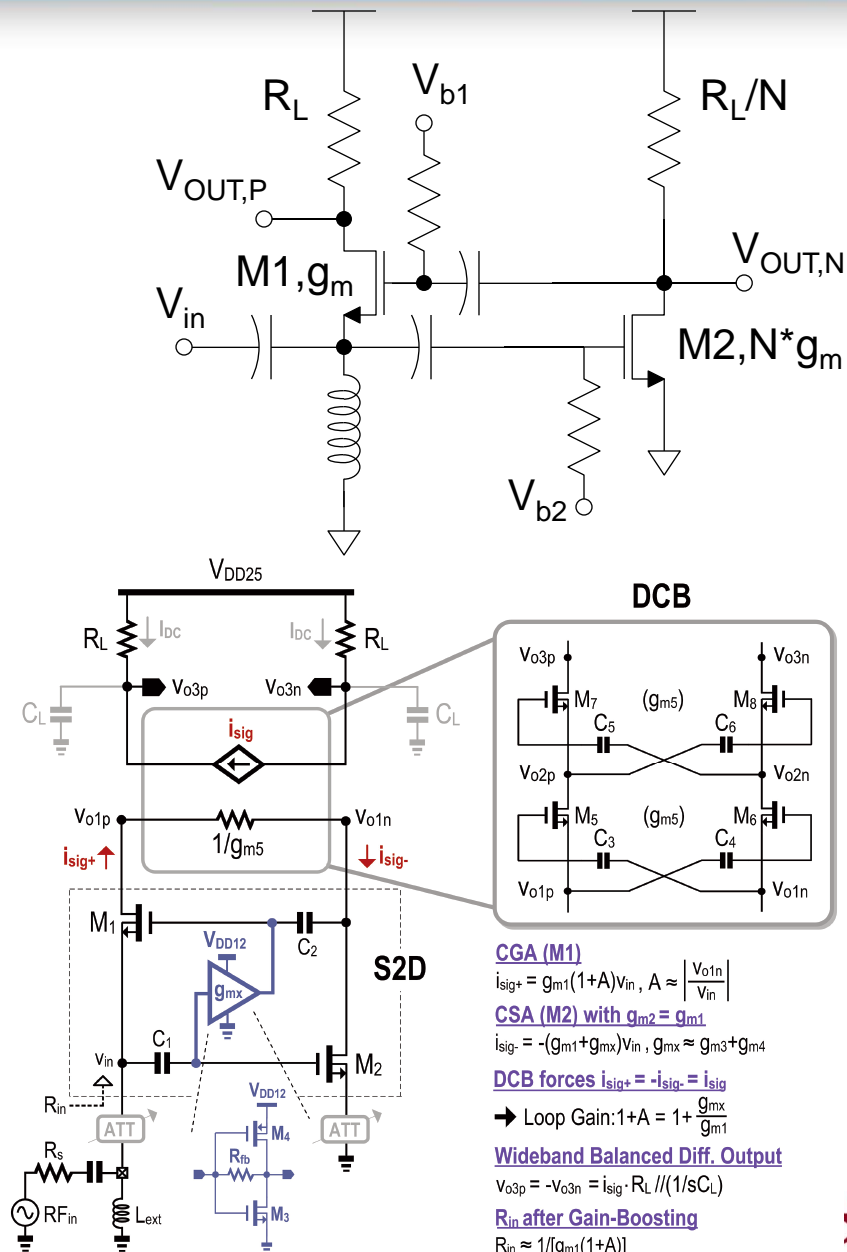- $R_{in,CM} \gg R_{in,DM}$
- R_{ds} will reduce the impact
- Use cascade stages.





SILICON LABS

www.silabs.com

www.silabs.com/redirect