



**IEEE SOLID-STATE
CIRCUITS SOCIETY**
Where ICs are in IEEE

Solid-State Circuits Society

“Where ICs are in the IEEE”



Professional Organization

- ▶ 10,000 members
- ▶ 70+ chapters located worldwide
- ▶ Foster information exchange in electronics
 - Distinguished Lectures
 - Online tutorials
 - International and regional conferences
 - Journals & magazines
- ▶ Part of IEEE with 400,000 members



Journal of Solid-State Circuits (JSSC)

- #1 technical source for circuits
- Most downloaded IEEE journal articles
- Top cited reference in US Patent applications



Solid-State Circuits Magazine

- Discusses historical milestones, trends and future developments
- Articles by leaders from industry and academia in a tutorial and editorial style



International and Regional Conferences

- 4 International Sponsored Conferences
- Technically co-sponsored conferences





Chapter & DL Events



Swedish SOC Conference (May 2011)



Annual SSCS DL Tour



Individual DL
Presentations

SSCS-Italy: International
Analog VLSI Workshop
(September 2011)





Why join IEEE and SSCS?

Knowledge ...

staying current with the fast changing world of solid-state circuit technology

Community ...

local and global activities, unparalleled networking opportunities, chapter activities, electing IEEE SSCS leadership

Profession ...

empowering members to build and own their careers, mentoring, making the world a better place

Recognition ...

Best Paper Awards, IEEE Fellow & Field Awards,
Student Travel Grants & Pre-doctoral Achievement Award

...



Getting Involved

- ▶ Organize chapter events
- ▶ Participate in & organize conferences
- ▶ As an author
- ▶ As a reviewer
- ▶ Compete in a student design contest
- ▶ Nominate senior members & fellows

Energy Limits in A/D Converters

August 29, 2012

Boris Murmann

murmann@stanford.edu



A/D Converter ca. 1954

◆ 19" × 15" × 26"

◆ 150 lbs

◆ 500W

◆ \$8,500.00

$$P/f_s = 500W/50kS/s = 10mJ$$




Courtesy,
Analogic Corporation
8 Centennial Drive
Peabody, MA 01960

<http://www.analogic.com>

*Figure 4.3: 1954 "DATRAC" 11-bit, 50-kSPS SAR ADC
Designed by Bernard M. Gordon at EPSCO*


http://www.analog.com/library/analogDialogue/archives/39-06/data_conversion_handbook.html

ADC Landscape in 2004

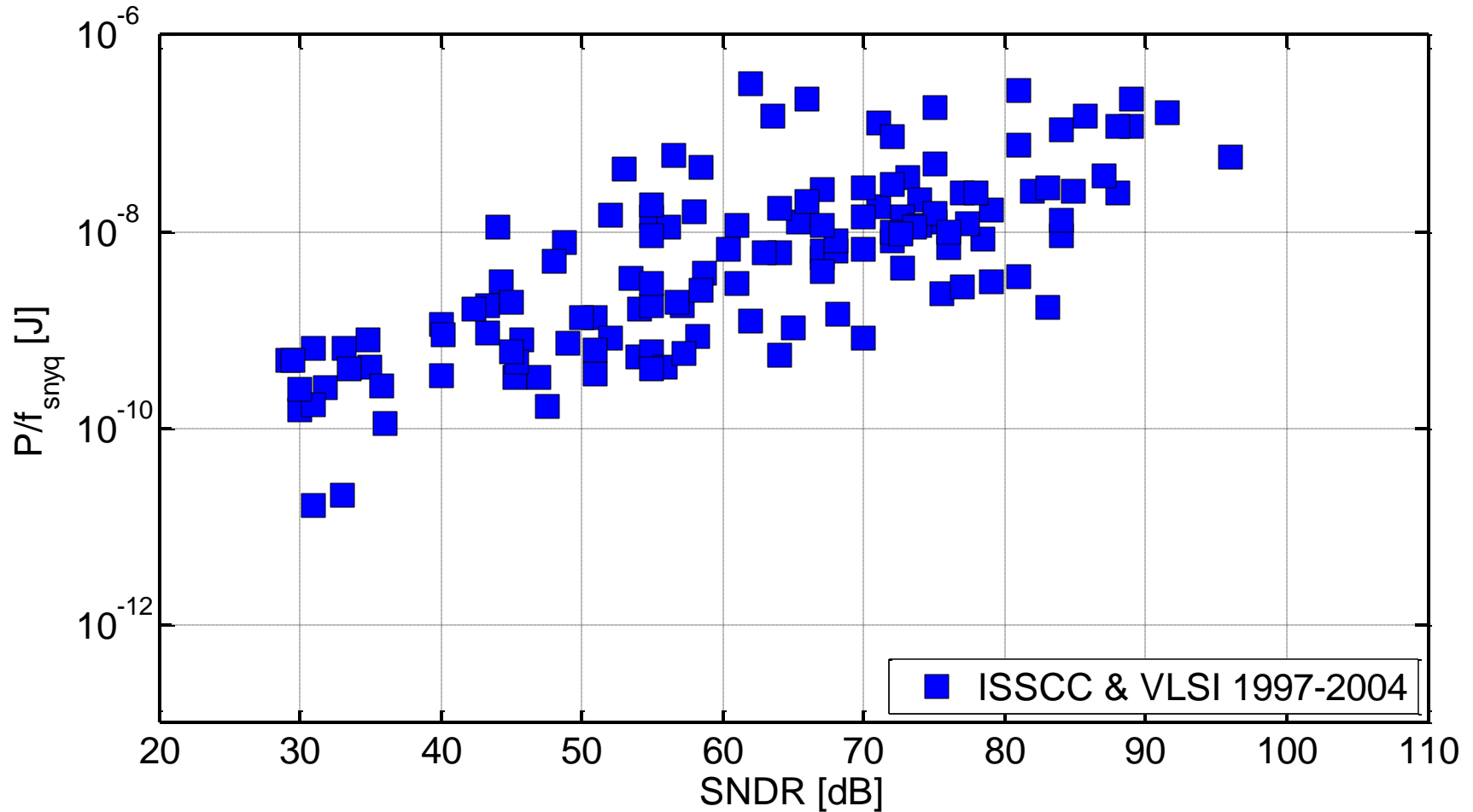

B. Murmann, "ADC Performance Survey 1997-2012," [Online]. Available: <http://www.stanford.edu/~murmman/adcsurvey.html>

ADC Landscape in 2012

 

B. Murmann, "ADC Performance Survey 1997-2012," [Online]. Available: <http://www.stanford.edu/~murmann/adcsurvey.html>


Observation

- **ADCs have become substantially “greener” over the years**
- **Questions**
 - **How much more improvement can we hope for?**
 - **What are the trends and limits for today’s popular architectures?**
 - **Can we benefit from further process technology scaling?**

Outline

- **Fundamental limit**
- **General trend analysis**
- **Architecture-specific analysis**
 - **Flash**
 - **Pipeline**
 - **SAR**
 - **Delta-Sigma**
- **Summary**

Fundamental Limit

 

$$\text{SNR} = \frac{\frac{1}{2} \left(\frac{V_{\text{FS}}}{2} \right)^2}{\frac{kT}{C}} \cdot \frac{f_s}{f_{\text{snyq}}} \quad \text{OSR}$$


$$P_{\text{min}} = CV_{\text{FS}} f_s \cdot V_{\text{DD}}$$

$$V_{\text{DD}} = V_{\text{FS}}$$


$$E_{\text{min}} = \frac{P_{\text{min}}}{f_{\text{snyq}}} = 8kT \cdot \text{SNR}$$

[Hosticka, Proc. IEEE 1985; Vittoz, ISCAS 1990]


ADC Landscape in 2004

 

ADC Landscape in 2012

 

Normalized Plot

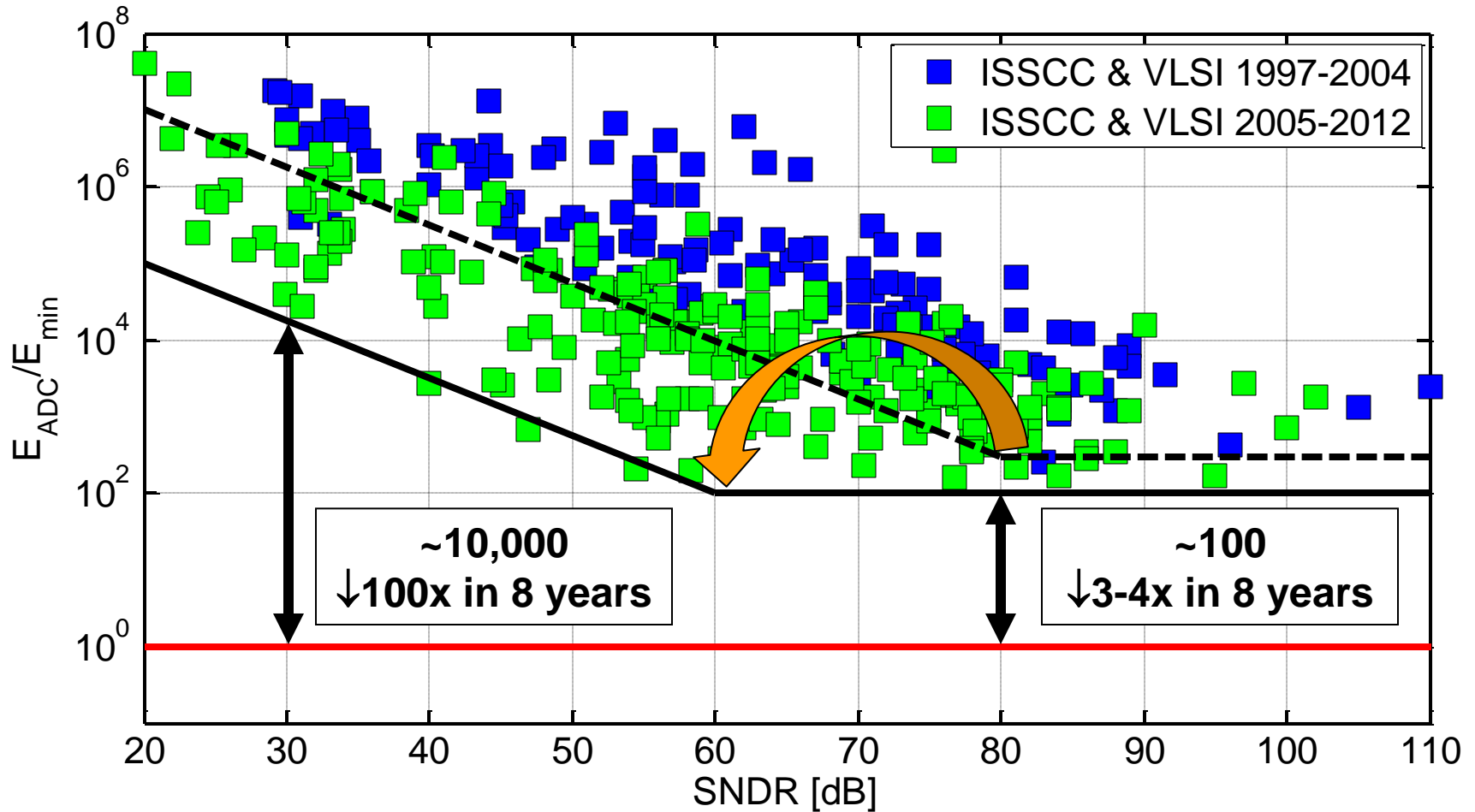

Aside: Figure of Merit Considerations

- There are (at least) two widely used ADC figures of merit (FOM) used in literature

- **Walden FOM**

- Energy increases 2x per bit (ENOB)
- Empirical


$$\text{FOM} = \frac{\text{Power}}{2^{\text{ENOB}} \cdot f_{\text{snyq}}}$$

- **Schreier FOM**

- Energy increases 4x per bit (DR)
- Thermal
- Ignores distortion


$$\text{FOM} = \text{DR}(\text{dB}) + 10 \log \left(\frac{\text{BW}}{\text{P}} \right)$$

FOM Lines

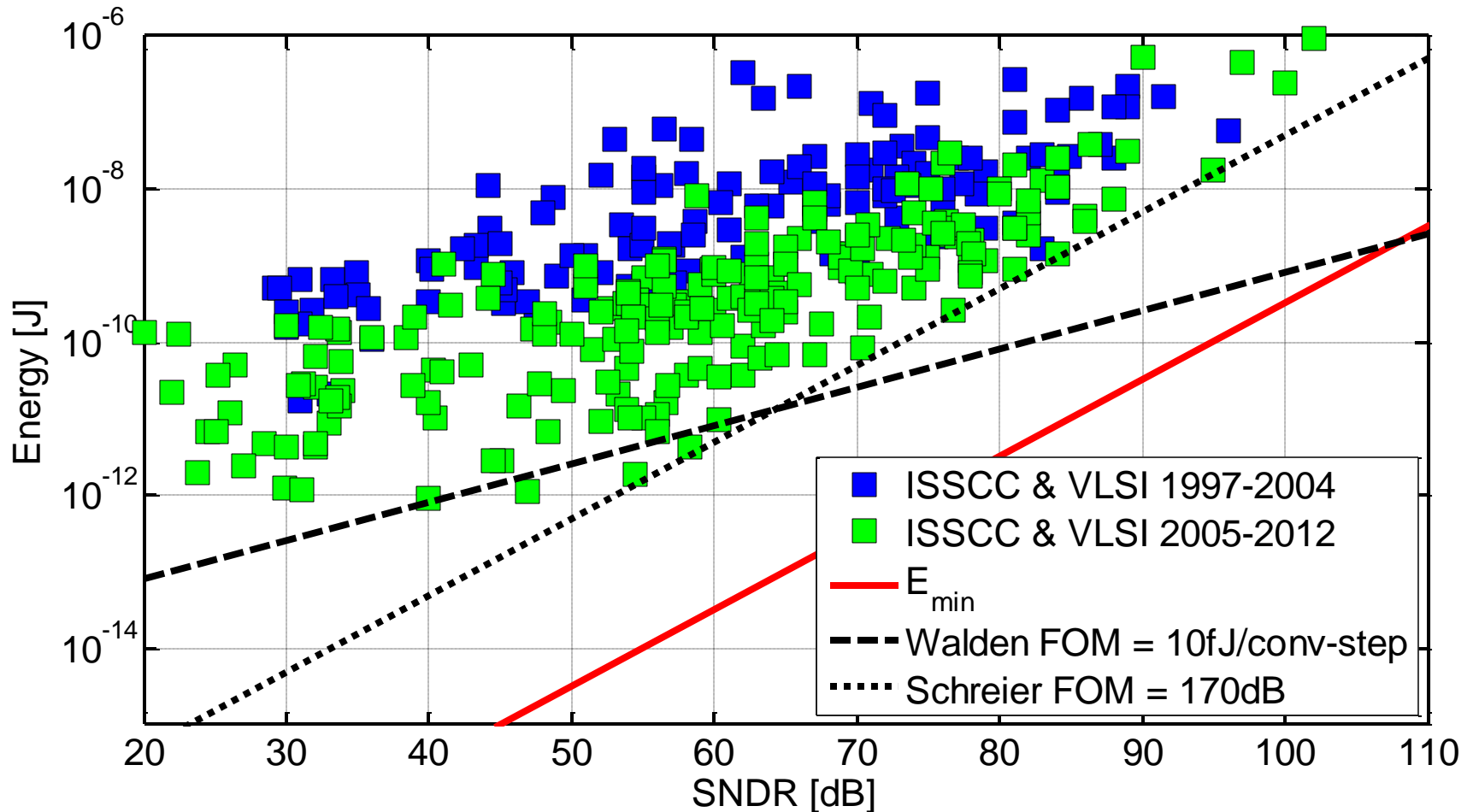


- **Best to use thermal FOM for designs above 60dB**

Walden FOM vs. Speed

 


- FOM “corner” around 100...300MHz


Schreier FOM vs. Speed

 

Energy by Architecture

 


Flash ADC

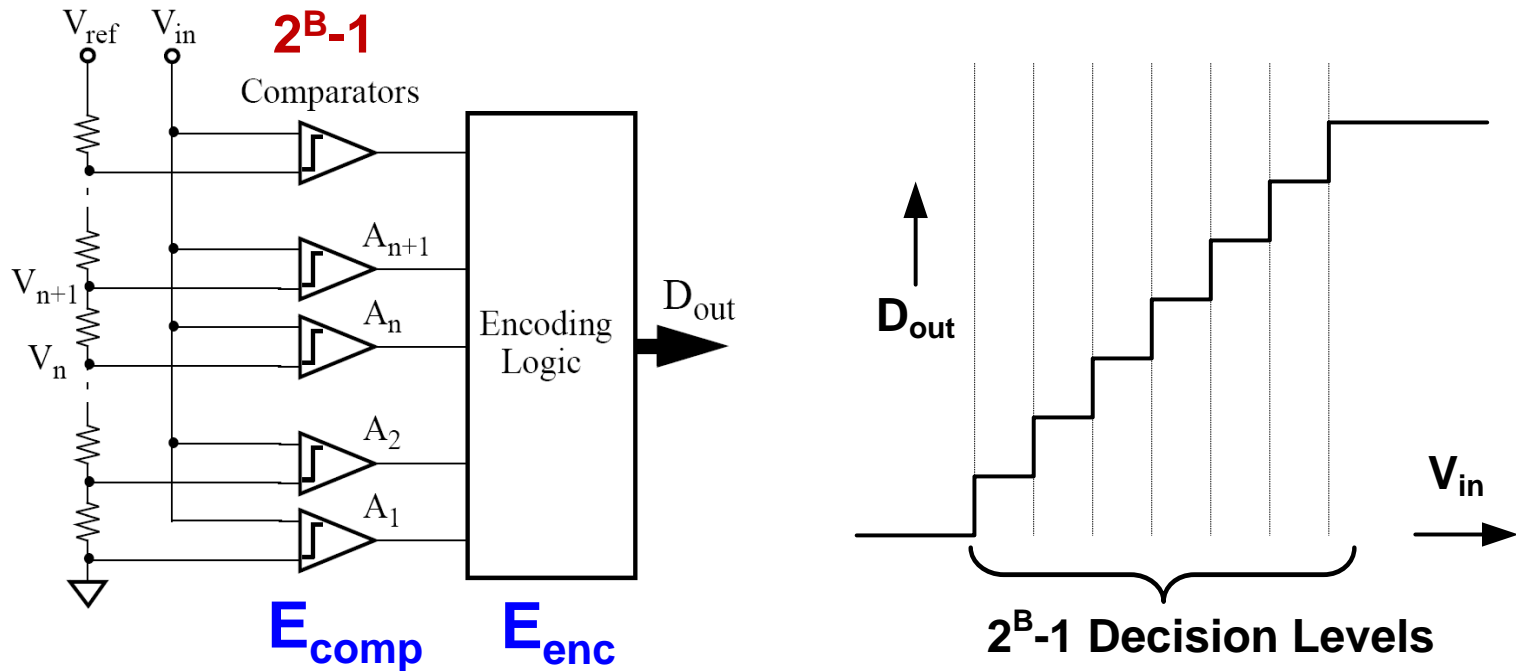

- **High Speed**
 - Limited by single comparator plus encoding logic
- **High complexity, high input capacitance**
 - Typically use for resolutions up to 6 bits


Encoder

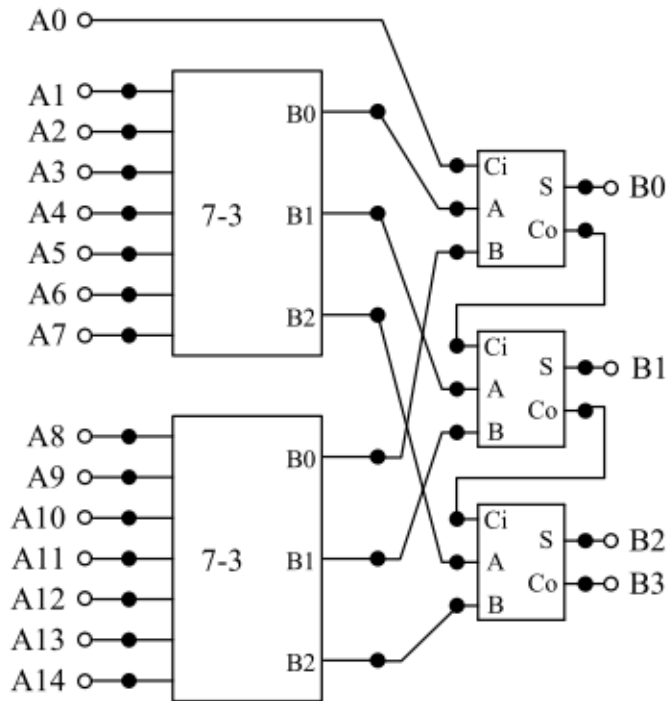- Assume a Wallace encoder (“ones counter”)
- Uses $\sim 2^B - B$ full adders, equivalent to $\sim 5 \cdot (2^B - B)$ gates



$$E_{\text{enc}} \cong 5 \cdot (2^B - B) \cdot E_{\text{gate}}$$

Matching-Limited Comparator

 

Simple Dynamic Latch

Assuming $C_{\text{cmin}} = 5\text{fF}$
for wires, clocking, etc.

$$\sigma_{\text{VOS}}^2 \cong \frac{A_{\text{VT}}^2}{\text{WL}} = A_{\text{VT}}^2 \frac{C_{\text{c}}}{C_{\text{ox}}}$$

Offset

$$C_{\text{c}} = \frac{A_{\text{VT}}^2 C_{\text{ox}}}{\sigma_{\text{VOS}}^2} + C_{\text{cmin}}$$

Required capacitance

$$3\sigma_{\text{VOS}} = \frac{1}{4} \frac{V_{\text{inpp}}}{2^{\text{B}}}$$

Confidence interval

$$\text{B} \cong \frac{\text{SNR}[\text{dB}] + 3}{6}$$


3dB penalty accounts for "DNL noise"

$$E_{\text{comp}} \cong \left(144 \cdot 2^{2\text{B}} \cdot \underbrace{C_{\text{ox}} A_{\text{VT}}^2}_{\text{Matching Energy}} \cdot \frac{V_{\text{DD}}^2}{V_{\text{inpp}}^2} + C_{\text{cmin}} V_{\text{DD}}^2 \right) \cdot (2^{\text{B}} - 1)$$

Typical Process Parameters

Process [nm]	A_{VT} [mV- μm]	C_{ox} [fF/ μm^2]	$A_{VT}^2 C_{ox} / kT$	E_{gate} [fJ]
250	8	9	139	80
130	4	14	54	10
65	3	17	37	3
32	1.5	43	23	1.5

Comparison to State-of-the-Art

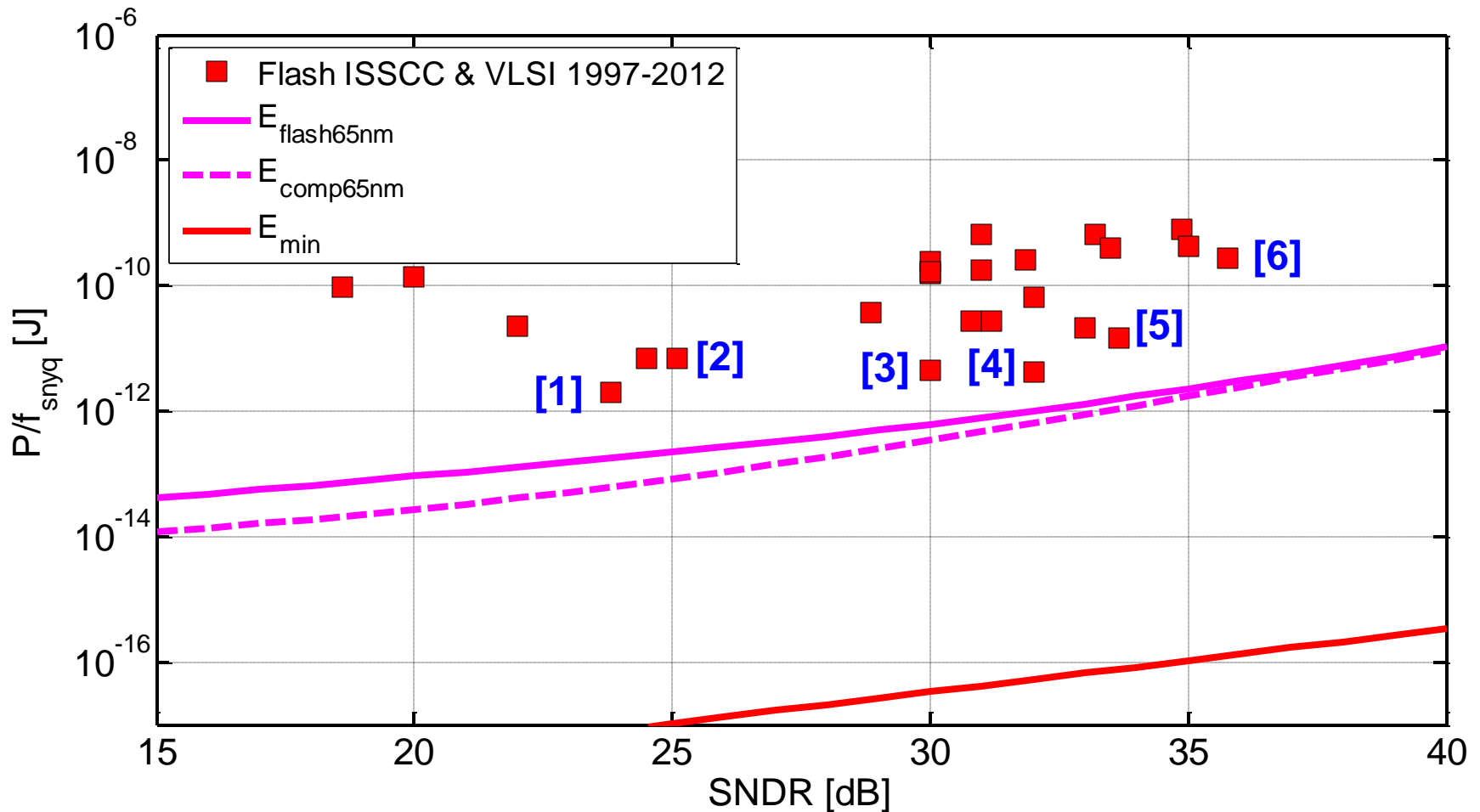

[1] Van der Plas, ISSCC 2006

[2] El-Chammas, VLSI 2010


[3] Verbruggen, VLSI 2008

[4] Daly, ISSCC 2008


[5] Chen, VLSI 2008

[6] Geelen, ISSCC 2001 (!)

Impact of Scaling

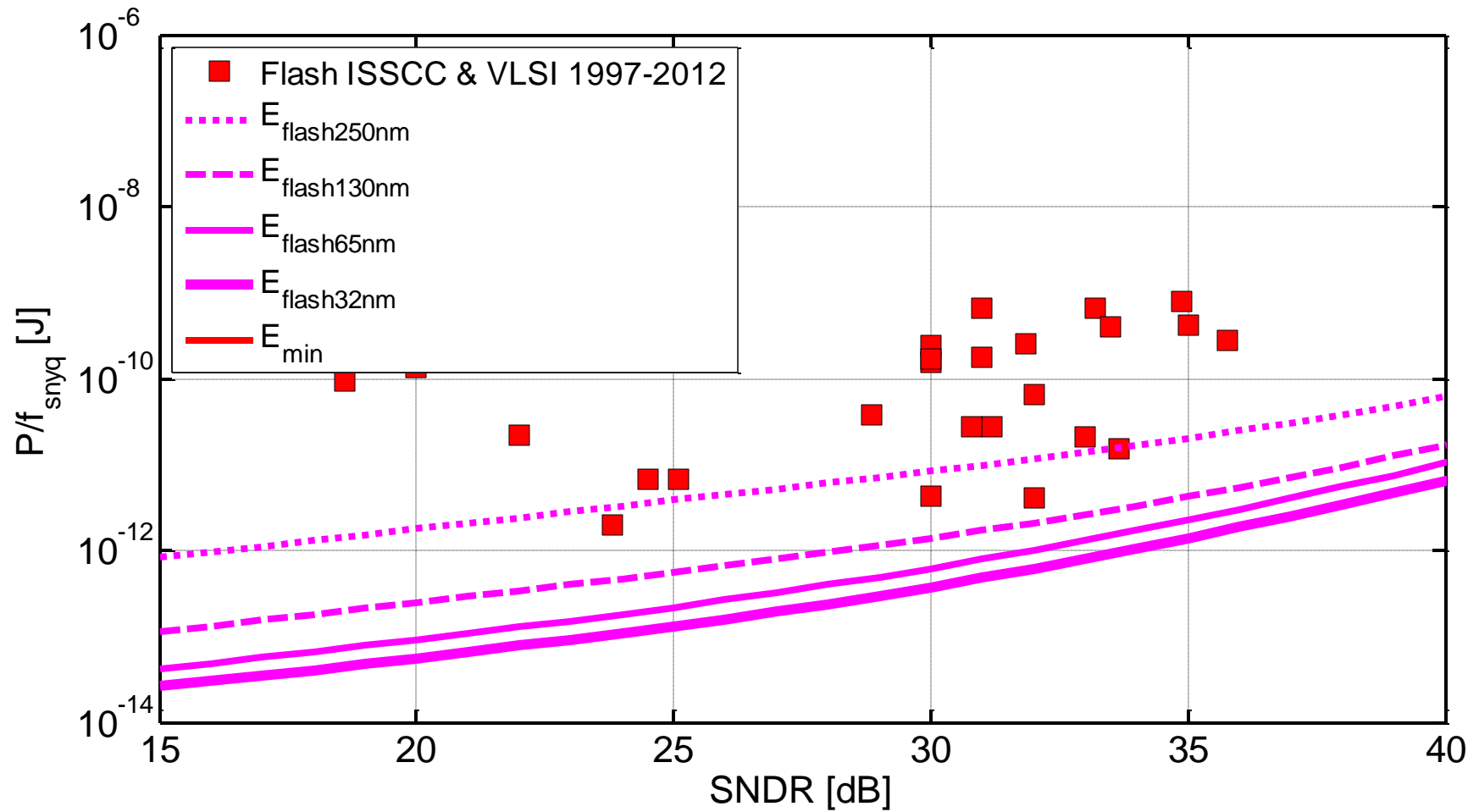


Impact of Calibration (1)

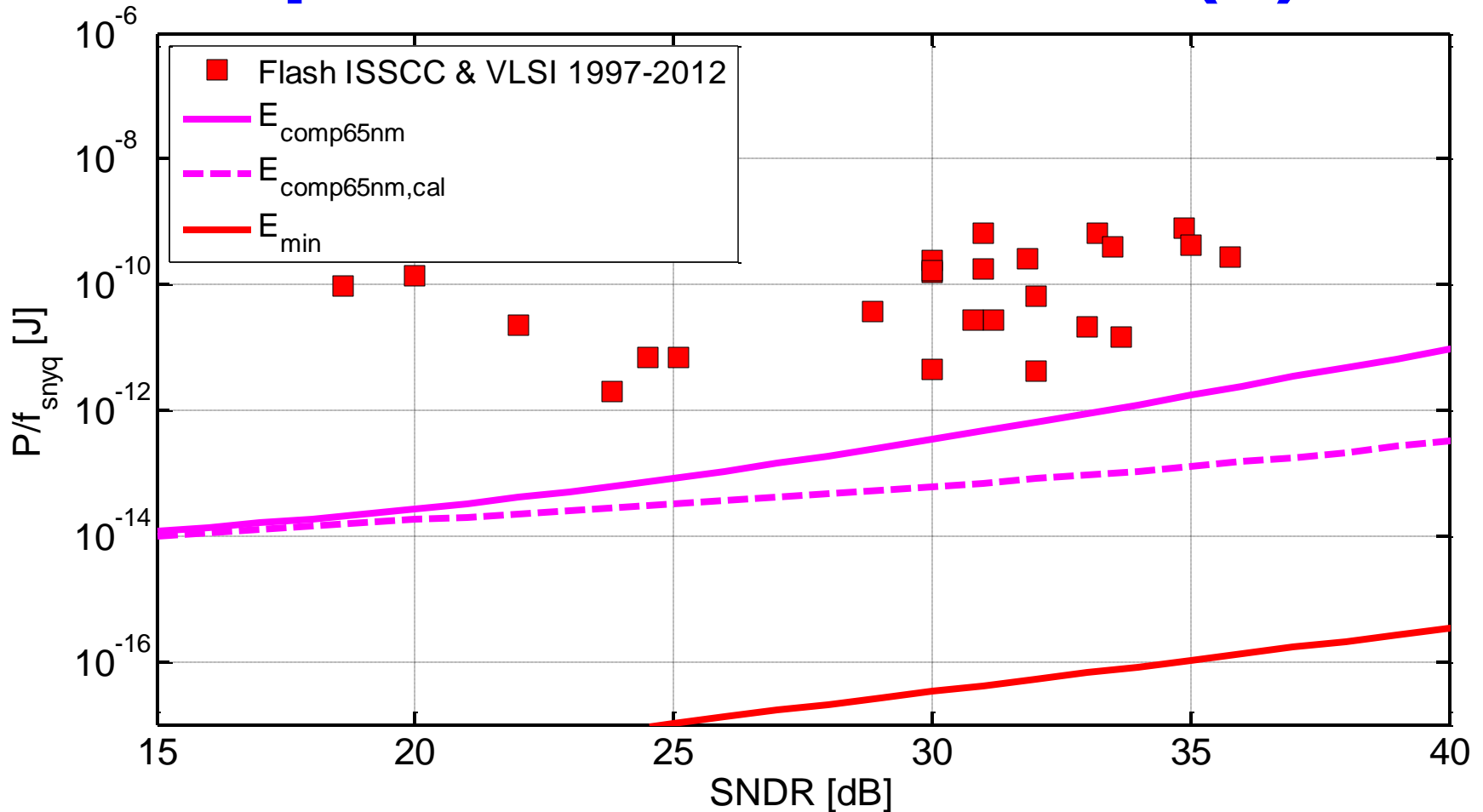

- Important to realize that only comparator power reduces

$$3\sigma_{\text{VOS}} = \frac{1}{4} \frac{V_{\text{inpp}}}{2^{B - B_{\text{cal}}}} \quad B_{\text{cal}} \approx 3$$


Impact of Calibration (2)

 

Ways to Approach E_{\min} (1)

- **Offset calibrate each comparator**
 - **Using trim-DACs**


[El-Chammas, VLSI 2010]

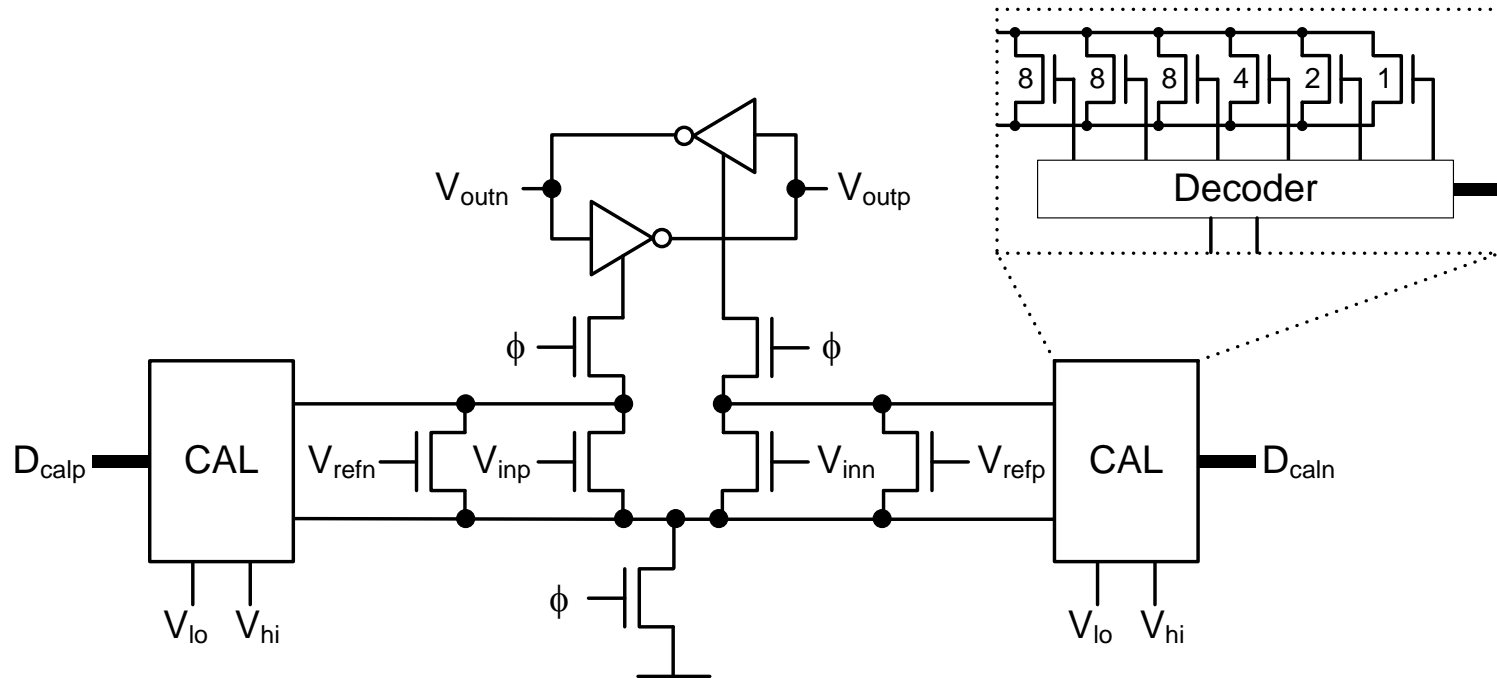


Ways to Approach E_{\min} (2)

- Find ways to reduce clock power
- Example: resonant clocking


[Ma, ESSCIRC 2011]

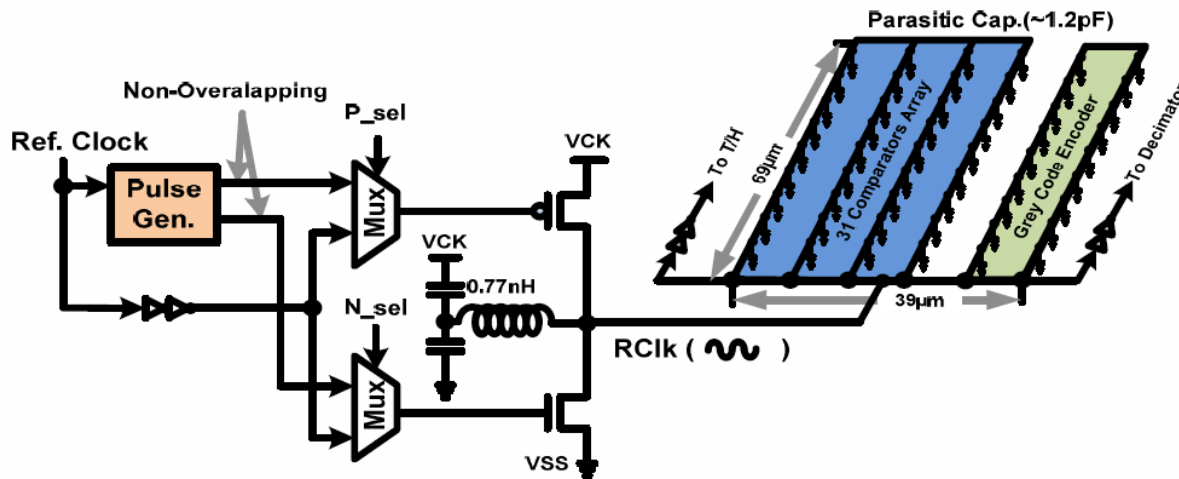



(54% below CV^2)

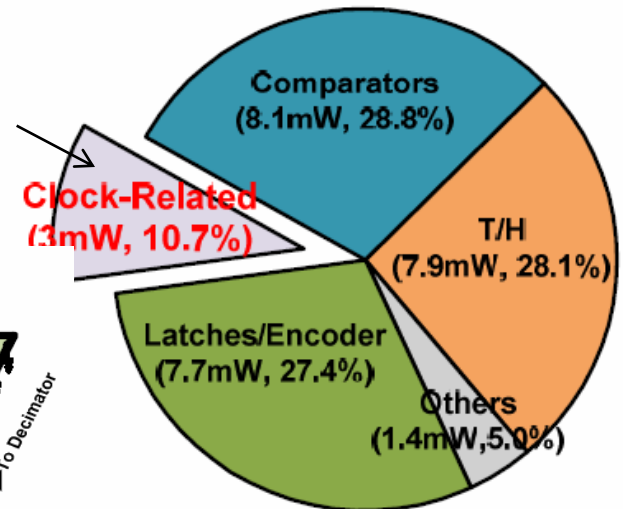

 Raison D'Être for Architectures Other than Flash...



Pipeline ADC

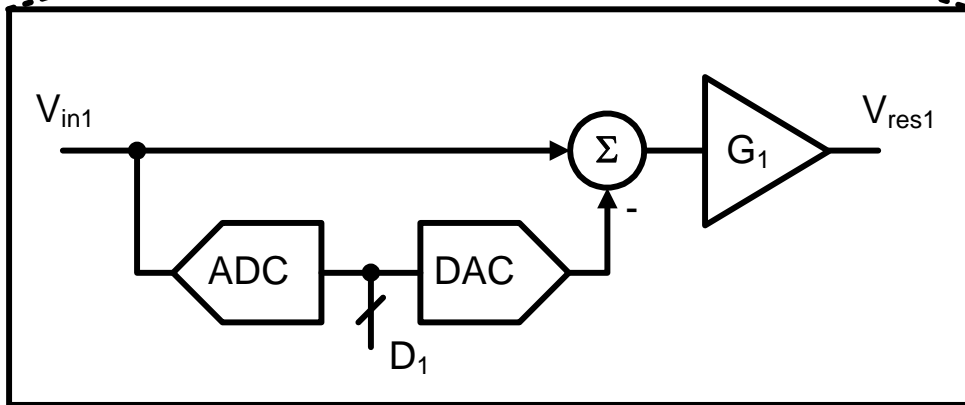 


- **Conversion occurs along a cascade of stages**
- **Each stage performs a coarse quantization and computes its error (V_{res})**
- **Stages operate concurrently**
 - Throughput is set by the speed of one single stage


Pipelining – A Very Old Idea



Typical Stage Implementation

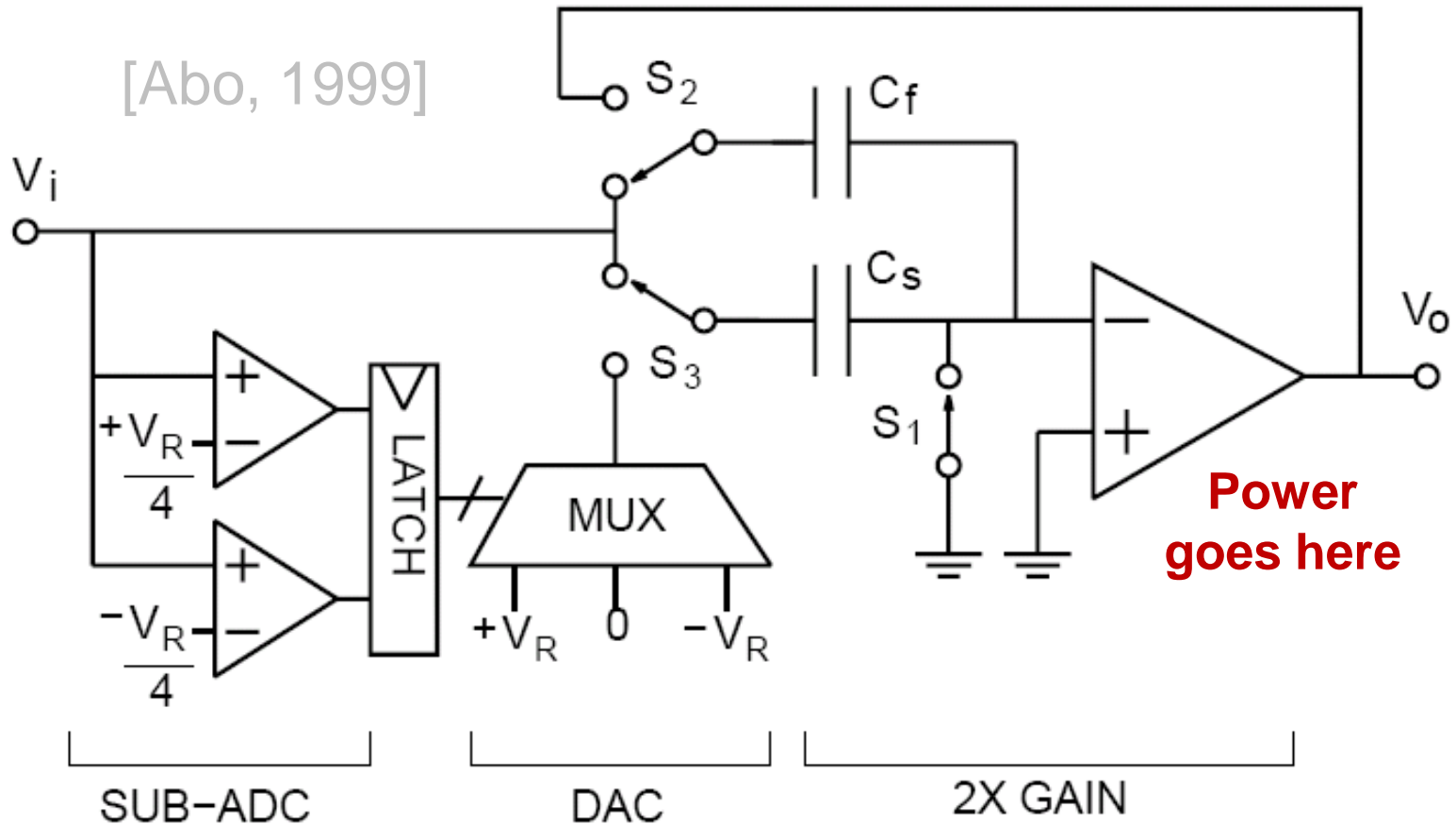

Simplified Model for Energy Calculation

 


- **Considering the most basic case**
 - Stage gain = 2 \rightarrow 1 bit resolution per stage
 - Capacitances scaled down by a factor of two from stage to stage (first order optimum)
 - No front-end track-and-hold
 - Neglect comparator energy

Simplified Gain Stage Model

Feedback factor
 
$$\beta = \frac{\frac{C}{2}}{C + \frac{C}{2}} = \frac{1}{3}$$



Assumptions

Closed-loop gain = 2

Infinite transistor f_T ($C_{gs}=0$)

Thermal noise factor $\gamma = 1$,
no flicker noise

Bias device has same
noise as amplifier device

Linear settling only (no
slewing)

$$C_{\text{eff}} = \frac{C}{2}(1-\beta) + \frac{C}{2} = \frac{5}{6}C$$

Effective load capacitance

$$N_{\text{out}} = 2 \frac{1}{\beta} \frac{kT}{C_{\text{eff}}} = 6 \frac{kT}{C_{\text{eff}}} = 5 \frac{kT}{C}$$

Total integrated output noise

Total Pipeline Noise

$$\begin{aligned} N_{\text{in,tot}} &= \underbrace{\frac{kT}{C} \left(1 + \frac{1}{2} \right)}_{\text{First sampler}} + 5 \frac{kT}{C} \left\{ \frac{1}{2^2} + \frac{1}{\frac{1}{2} 4^2} + \frac{1}{\frac{1}{4} 8^2} + \dots \right\} \\ &= \frac{3 kT}{2 C} + 5 \frac{kT}{C} \left\{ \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \dots \right\} \\ &\approx 4 \frac{kT}{C} \end{aligned}$$

Key Constraints

$$\text{SNR} \cong \frac{\frac{1}{2} \left(\frac{V_{\text{inpp}}}{2} \right)^2}{4 \frac{kT}{C}}$$

**Thermal noise
sets C**

$$\tau = \frac{C_{\text{eff}}}{\beta g_m} = \frac{T_s / 2}{\ln \left(\frac{1}{\epsilon_d} \right)} \cong \frac{T_s / 2}{\ln(\sqrt{\text{SNR}})}$$

**Settling time
sets g_m**

$$P = V_{\text{DD}} \left(\frac{g_m}{I_D} \right)$$

g_m sets power

Pulling It All Together

$$E_{\text{pipe}} = 640 \cdot kT \cdot \text{SNDR} \cdot \overbrace{\ln(\sqrt{\text{SNDR}})}^{\text{Settling "Number of } \tau"} \cdot \underbrace{\left(\frac{V_{DD}}{V_{\text{inpp}}}\right)^2}_{\text{Supply utilization}} \cdot \frac{1}{V_{DD}} \cdot \frac{1}{\frac{g_m}{I_D}} \cdot \frac{1}{\text{Transconductor efficiency}}$$

Excess noise
Non-unity feedback factor

- For SNDR = {60..80}dB, $V_{DD}=1V$, $g_m/I_D=1/(1.5kT/q)$, $V_{\text{inpp}}=2/3V$, the entire expression becomes

$$E_{\text{pipe}} \cong \{388...517\} \cdot kT \cdot \text{SNDR}$$

- For realistic numbers at low resolution, we must introduce a bound for minimum component sizes


Energy Bound

- Assume that in each stage $C_{\text{eff}} > C_{\text{effmin}} = 50\text{fF}$
- For n stages, detailed analysis shows that this leads to a minimum energy of

$$E_{\text{pipe,min}} = 2n \cdot C_{\text{eff min}} V_{\text{DD}} \frac{\ln(\sqrt{\text{SNDR}})}{\beta \left(\frac{g_m}{I_D} \right)}$$

- Adding this overhead to E_{pipe} gives the energy curve shown on the next slide

Comparison to State-of-the-Art

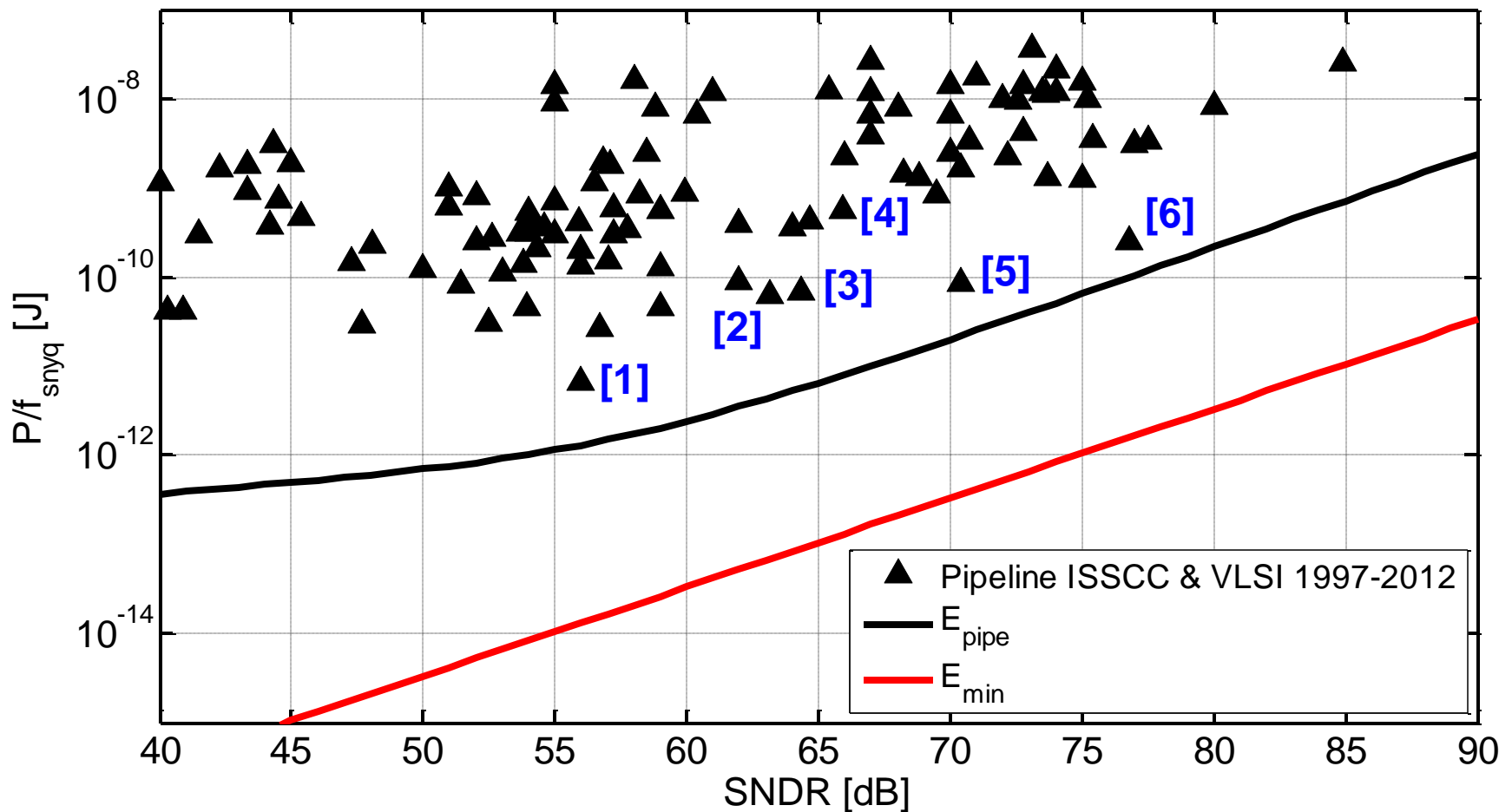

[1] Verbruggen, ISSCC 2012

[2] Chu, VLSI 2010


[3] Lee, VLSI 2010

[4] Anthony, VLSI 2008

[5] Lee, ISSCC 2012

[6] Hershberg, ISSCC 2012


Ways to Approach E_{\min} (1)

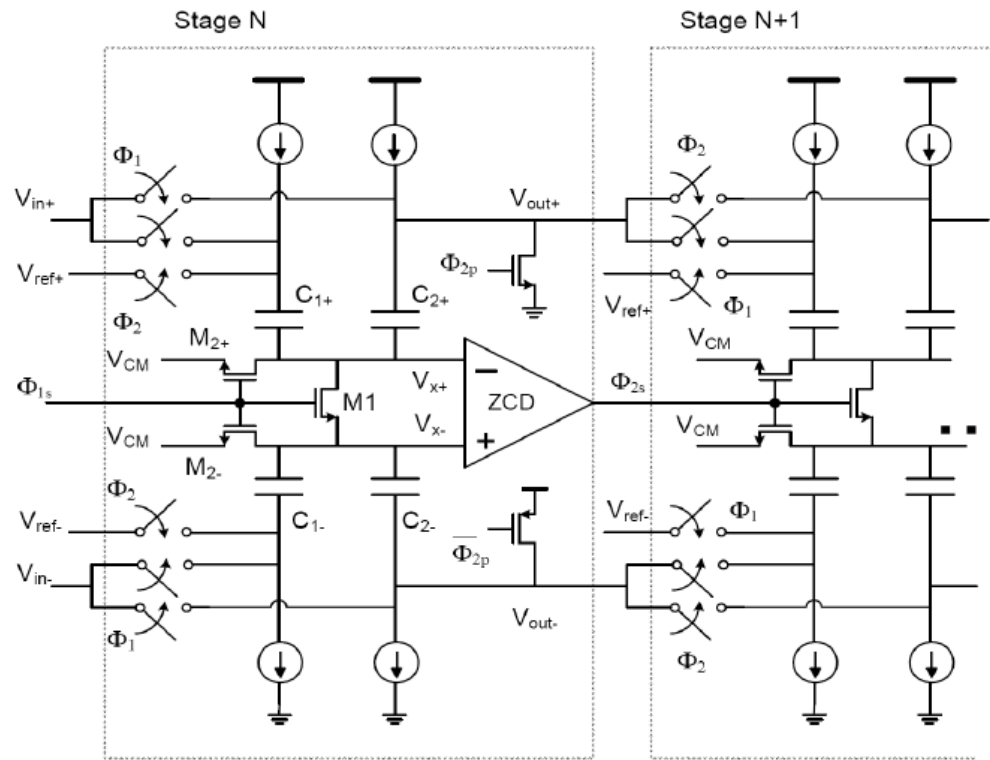

[Chu, VLSI 2010]

- **Comparator-based SC circuits replace op-amps with comparators**
- **Current ramp outputs**
 - **Essentially “class-B” (all charge goes to load)**

Ways to Approach E_{\min} (2)

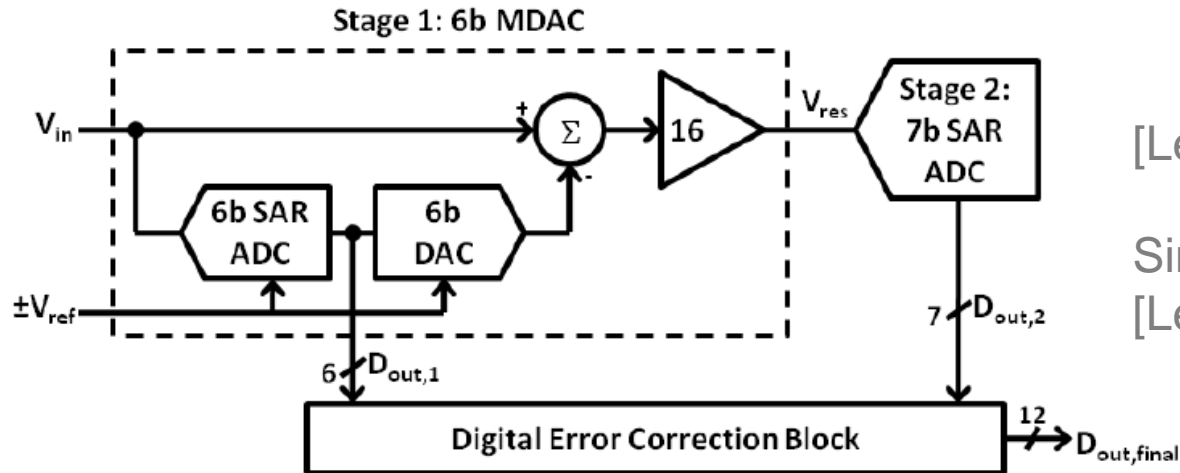


[Lee, VLSI 2010]

Similar:
[Lee, ISSCC 2012]

- Use only one residue amplifier
- Build sub-ADCs using energy efficient SAR ADCs
- Essential idea: minimize overhead as much as possible


Ways to Approach E_{\min} (3)

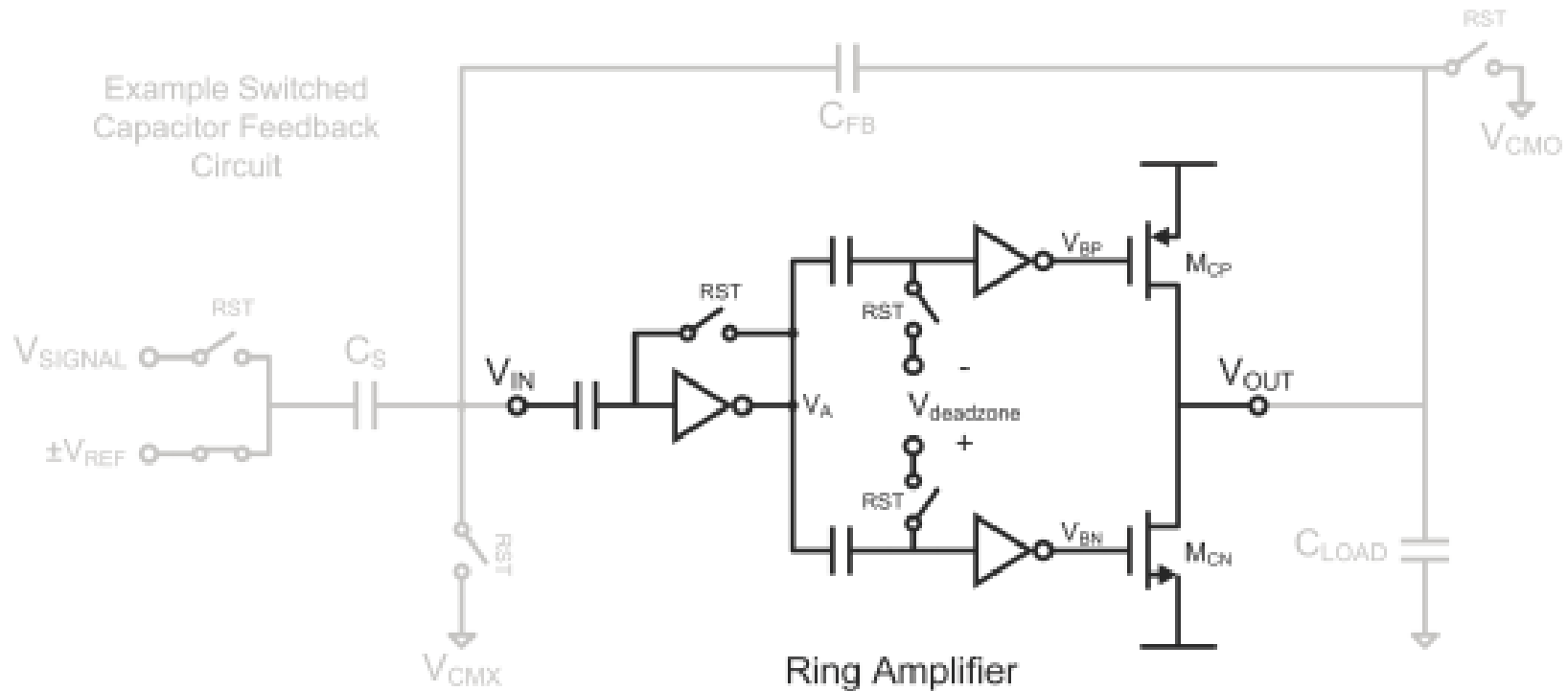

[Hershberg, ISSCC 2012]

- **Completely new idea: ring amplifier**
 - As in “ring oscillator”

Ways to Approach E_{\min} (4)

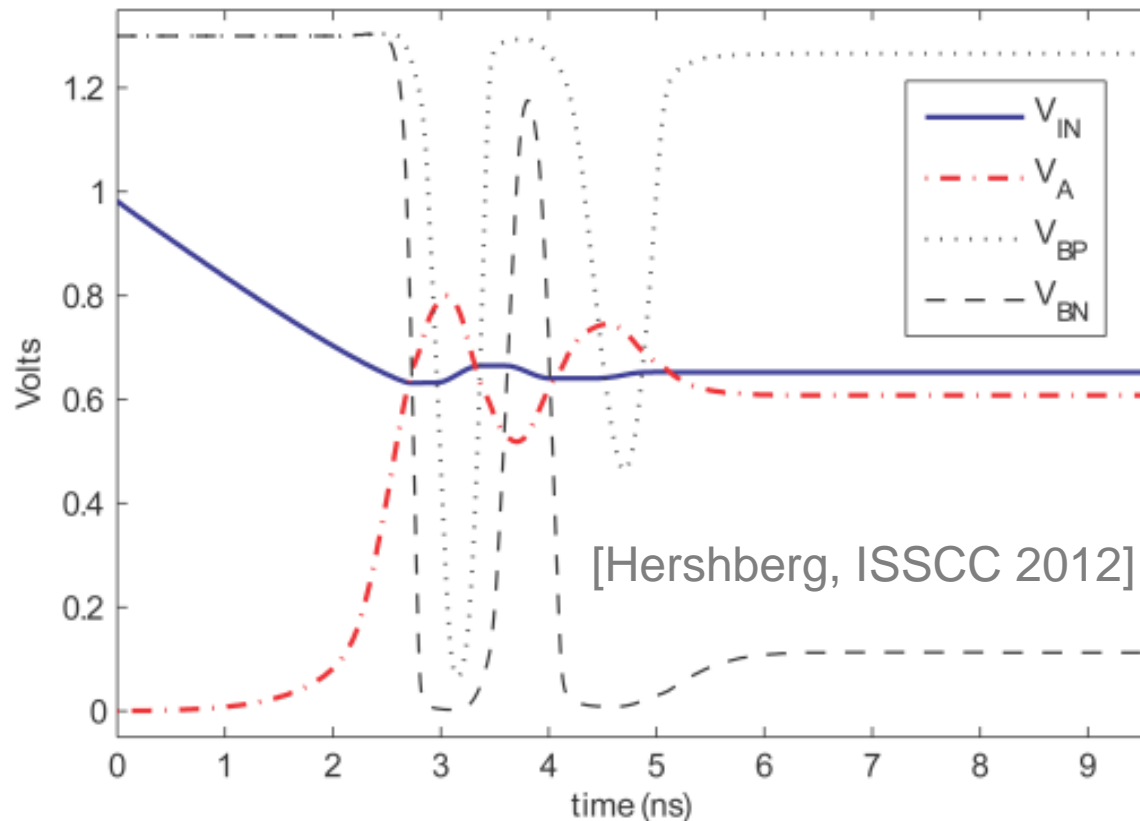

- **Class-C-like oscillations until charge transfer is complete**
 - **Very energy efficient**

Expected Impact of Technology Scaling

- **Low resolution (SNDR ~ 40-60dB)**
 - Continue to benefit from scaling
 - Expect energy reductions due to reduced C_{\min} and reduction of CV^2 -type contributors
- **High resolution (SNDR ~ 70dB+)**
 - It appears that future improvements will have to come from architectural innovation
 - Technology scaling will not help much and is in fact often perceived as a negative factor in noise limited designs (due to reduced V_{DD})
 - Let's have a closer look at this...


A Closer Look at the Impact of Technology Scaling

- As we have shown

$$E \propto \frac{1}{V_{DD}} \cdot \left(\frac{V_{DD}}{V_{inpp}} \right)^2 \cdot \frac{1}{\left(\frac{g_m}{I_D} \right)}$$


- **Low V_{DD} hurts, indeed, but one should realize that this is not the only factor**
- **Designers have worked hard to maintain (if not improve) V_{inpp}/V_{DD} in low-voltage designs**
- **How about g_m/I_D ?**

g_m/I_D Considerations (1)

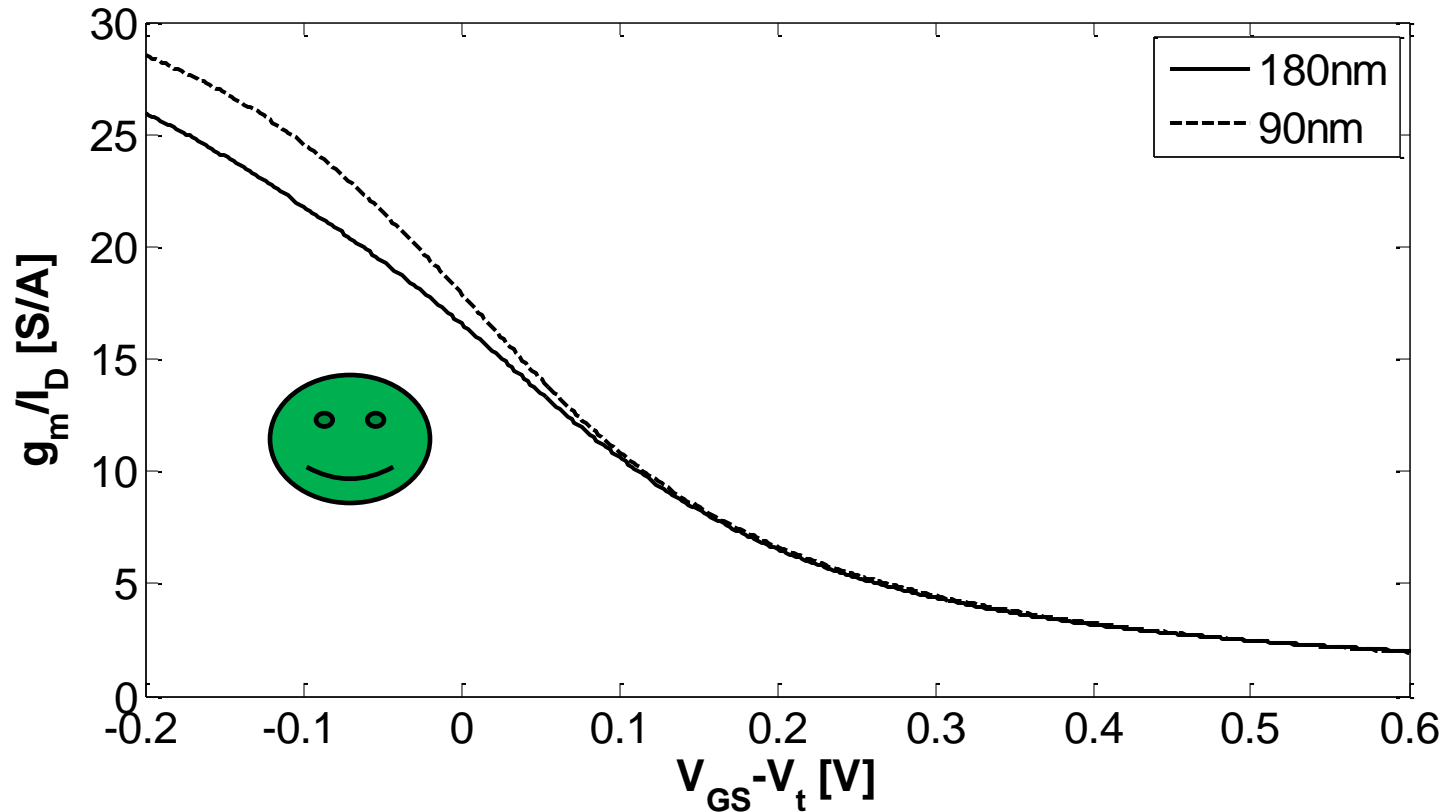


- Largest value occurs in subthreshold $\sim(1.5 \cdot kT/q)^{-1}$
- Range of g_m/I_D does not scale (much) with technology

g_m/I_D Considerations (2)

 


- f_T is small in subthreshold region
- Must look at g_m/I_D for given f_T requirement to compare technologies

g_m/I_D Considerations (3)

 


- **Example**
 - $f_T = 30\text{GHz}$
 - 90nm: $g_m/I_D = 18\text{S/A}$
 - 180nm: $g_m/I_D = 9\text{S/A}$
- **For a given f_T , 90nm device takes less current to produce same g_m**
 - Helps mitigate, if not eliminate penalty due to lower V_{DD} (!)

ADC Energy for 90nm and Below

 


Successive Approximation Register ADC

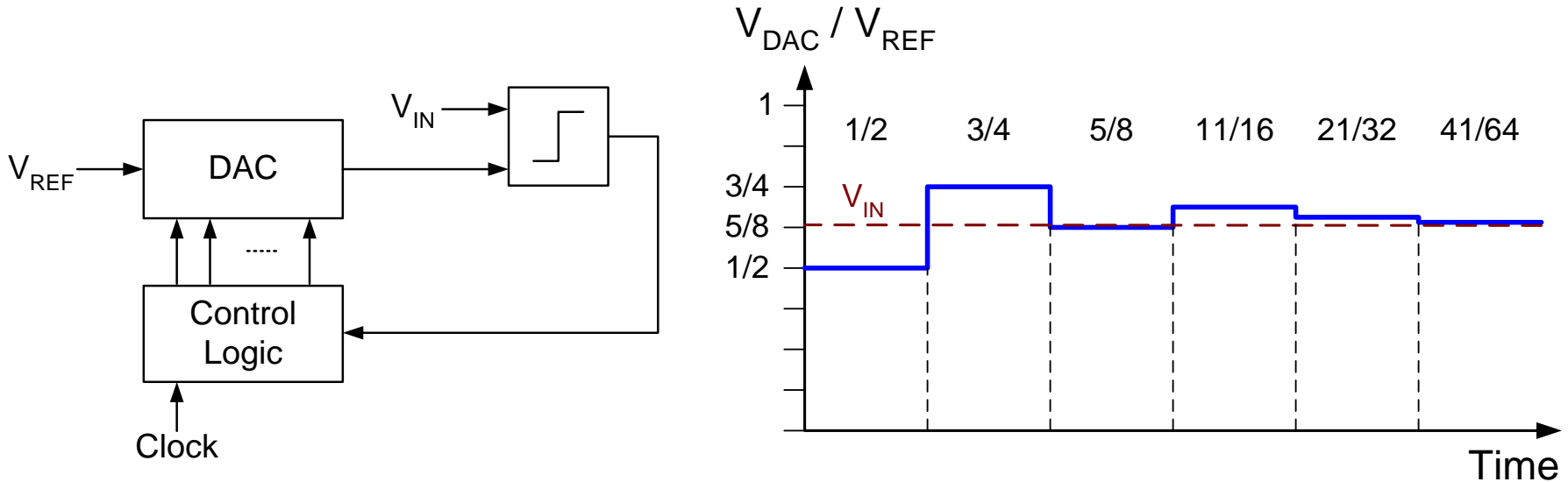

- **Input is approximated via a binary search**
- **Relatively low complexity**
- **Moderate speed, since at least $B+1$ clock cycles are needed for one conversion**
- **Precision is determined by DAC and comparator**

Classical Implementation

 

[McCreary, JSSC 12/1975]


$$E_{logic} \cong 8 \frac{\text{gates}}{\text{bit}} \cdot \frac{2fJ}{\text{gate}} \cdot B$$

(somewhat optimistic)

DAC Energy

- Is a strong function of the switching scheme
- Excluding adiabatic approaches, the “merged capacitor switching” scheme achieves minimum possible energy

[Hariprasath, Electronics Lett., 4/2010]

 

$$E_{\text{dac}} \cong \sum_{i=1}^{n-1} 2^{n-3-2i} (2^i - 1) CV_{\text{ref}}^2$$

For 10 bits:


$$E_{\text{dac}} \cong 85 CV_{\text{ref}}^2$$

DAC Unit Capacitor Size (C)

- Is either set by noise, matching, or minimum realizable capacitance (assume $C_{\min} = 0.5\text{fF}$)
- We will exclude matching limitations here, since these can be addressed through calibration
- Assuming that one third of the total noise power is allocated for the DAC, we have

$$\text{SNR} \cong \frac{\frac{1}{2} \left(\frac{V_{\text{inpp}}}{2} \right)^2}{\frac{kT}{2^B C} + N_{\text{comp}} + N_{\text{quant}}} \quad C = 24kT \cdot \text{SNR} \cdot \frac{1}{2^B \cdot V_{\text{inpp}}^2} + C_{\min}$$

Comparator

 

Simple Dynamic Latch

(Assuming $C_{\text{cmin}} = 5\text{fF}$)

$$N_{\text{in}} \cong \frac{kT}{C_c} \quad \text{Thermal Noise}$$


$$C_c = 24kT \cdot \text{SNR} \cdot \frac{1}{V_{\text{inpp}}^2} + C_{\text{cmin}}$$

$$B \cong \frac{\text{SNR}[\text{dB}] - 3}{6}$$

$$E_{\text{comp}} \cong \left(24kT \cdot \text{SNR} \cdot \frac{V_{\text{DD}}^2}{V_{\text{inpp}}^2} + C_{\text{cmin}} V_{\text{DD}}^2 \right) \cdot \frac{1}{2} \cdot B$$

**Switching
probability**

Comparison to State-of-the-Art

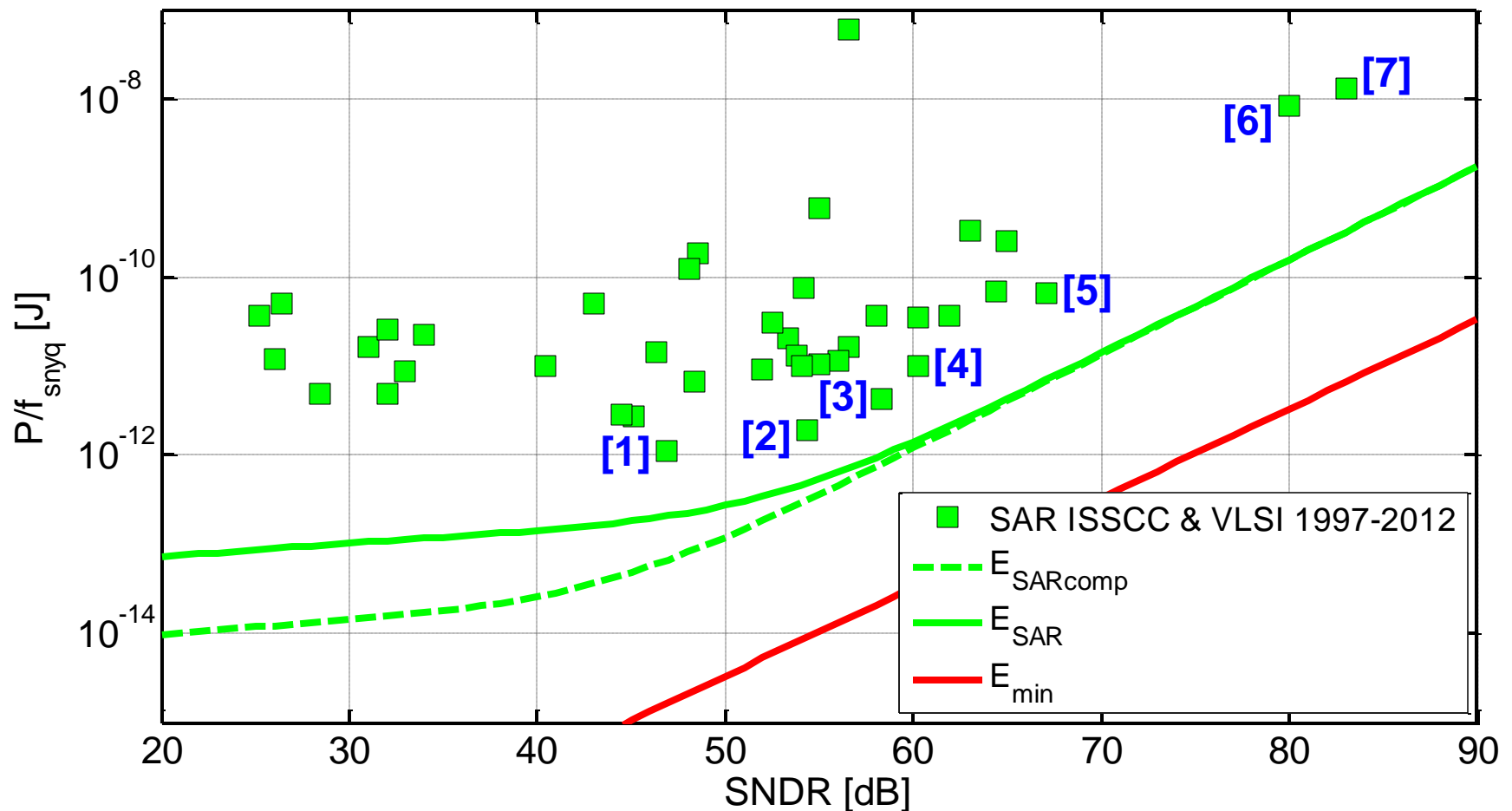


- [1] Shikata, VLSI 2011
- [2] Van Elzaker, ISSCC 2008
- [3] Harpe, ISSCC 2012
- [4] Liu, VLSI 2010

- [5] Liu, ISSCC 2010
- [6] Hurrell, ISSCC 2010
- [7] Hesener, ISSCC 2007

Ways to Approach E_{\min} (1)

[Giannini, ISSCC 2008]

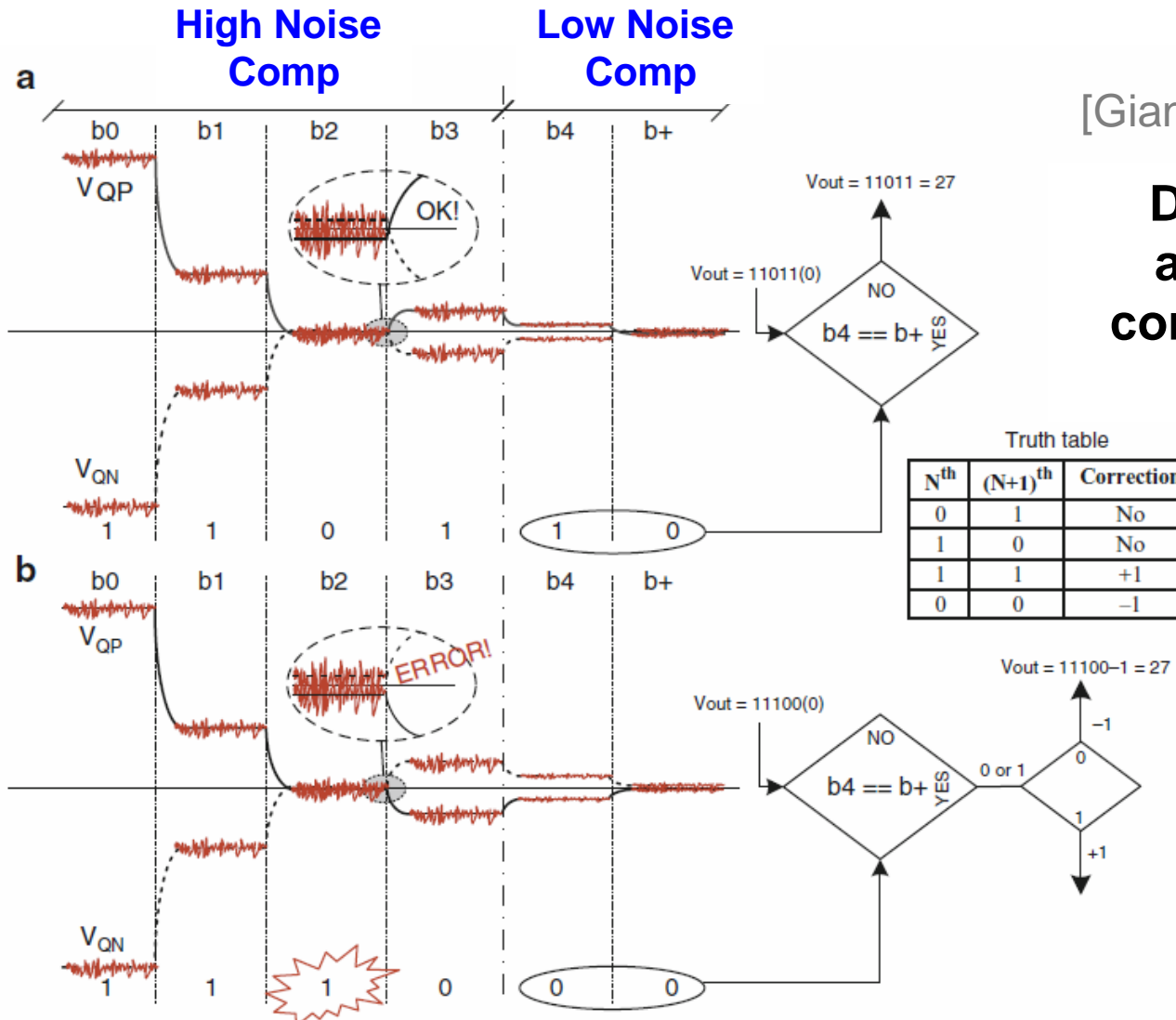
Dynamic Noise adjustment for comparator power savings



Ways to Approach E_{\min} (2)

- Minimize unit caps as much as possible for moderate resolution designs
 - Scaling helps!

0.5fF unit capacitors

 


[Shikata, VLSI 2011]

Delta-Sigma ADCs

- **Discrete time**
 - Energy is dominated by the first-stage switched-capacitor integrator
 - Energy analysis is similar to that of a pipeline stage
- **Continuous time**
 - Energy is dominated by the noise and distortion requirements of the first-stage continuous time integrator
 - Noise sets resistance level, distortion sets amplifier current level
 - Interestingly, this leads to about the same energy limits as in a discrete-time design

Overall Picture

 

Summary


- No matter how you look at it, today's ADCs are extremely well optimized
- The main trend is that the “thermal knee” shifts very rapidly toward lower resolutions
 - Thanks to process scaling and creative design
- At high resolution, we seem to be stuck at $E/E_{\min} \sim 100$
 - The factor 100 is due to architectural complexity and inefficiency: excess noise, signal < supply, non-noise limited circuitry, class-A biasing, ...
- This will be very hard to change
 - Scaling won't help (much)
 - Some of the recent data points already use class-B-like amplification
 - Can we somehow recycle the signal charge?
- Are there completely new ways to approach A/D conversion?

Darpa Has Seen the Future of Computing ... And It's Analog


BY ROBERT MCMILLAN 

08.22.12 6:30 AM

 Like 773

 Tweet 740

 +1 270

 

<http://www.wired.com/wiredenterprise/2012/08/upside/>