

# ***VCO-Based Quantizers – Has Their Time Arrived?***

***IEEE Distinguished Lecture  
Austin, TX***

**Michael H. Perrott**

**October 2012**

**Copyright © 2012 by Michael H. Perrott**



**All rights reserved.**

# Why Should We Consider VCO-Based Quantizers?

---

- **Advanced CMOS processes improve digital circuits**
  - Faster speed, higher density
- ***But*, analog circuits suffer**
  - Reduced intrinsic device gain ( $g_m r_o$ )
  - Reduced supply voltages
- **VCO-based quantizers utilize *time* as the signal**
  - Take advantage of digital improvements
  - Offer a simple design that is high speed, multi-bit

 
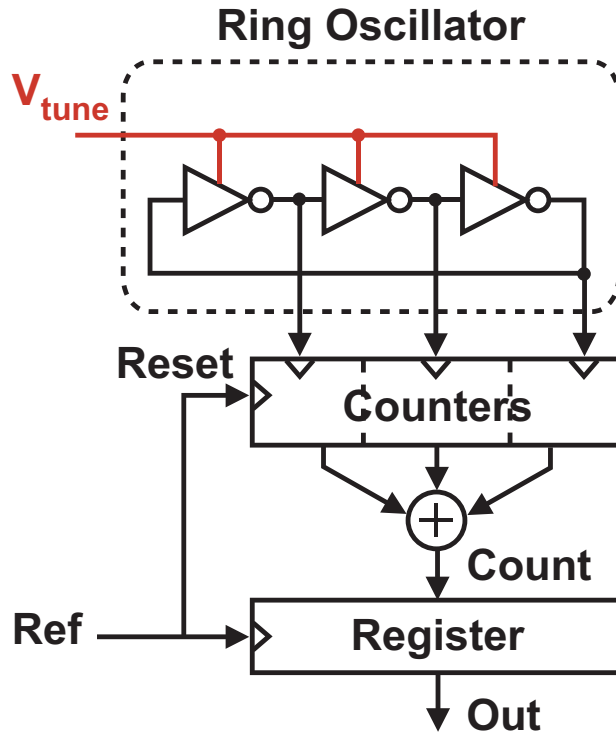
# Using a Voltage Controlled Oscillator as an ADC



Wismar, ESSCIRC 2006  
Kim, ISCAS 2006  
Alon, JSSC 2005


- **Input:** analog tuning of ring oscillator frequency
- **Output:** count of oscillator cycles per Ref clock period
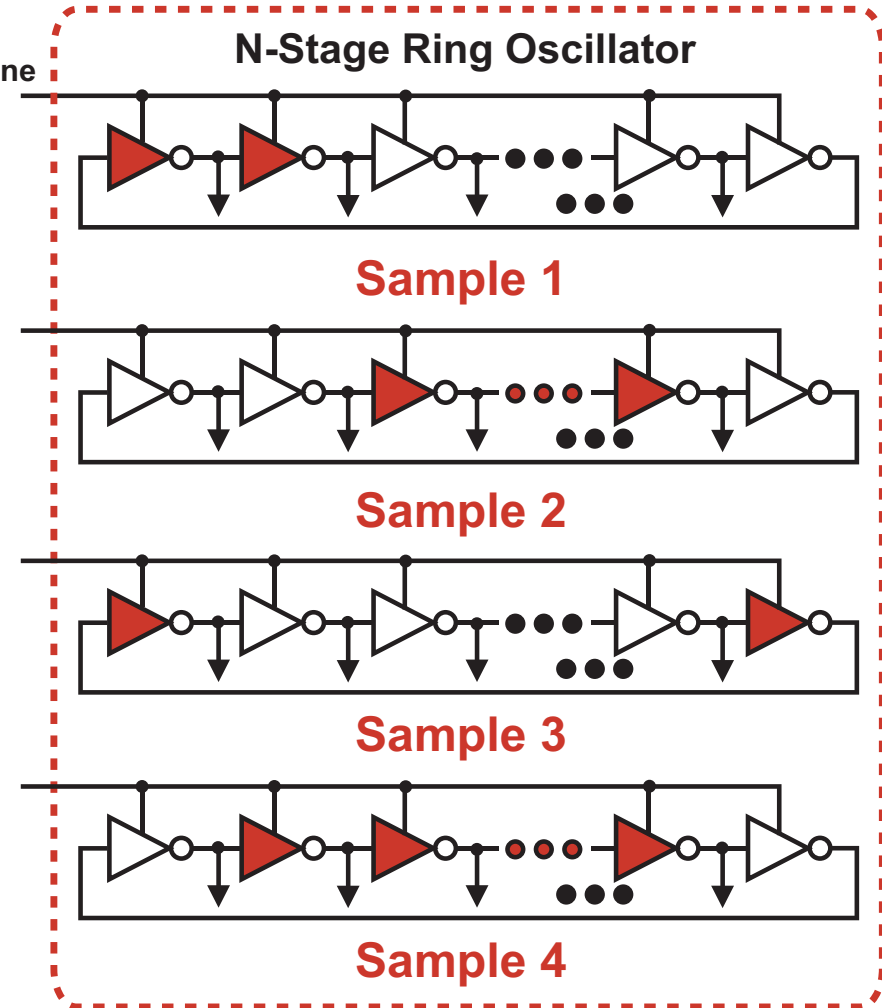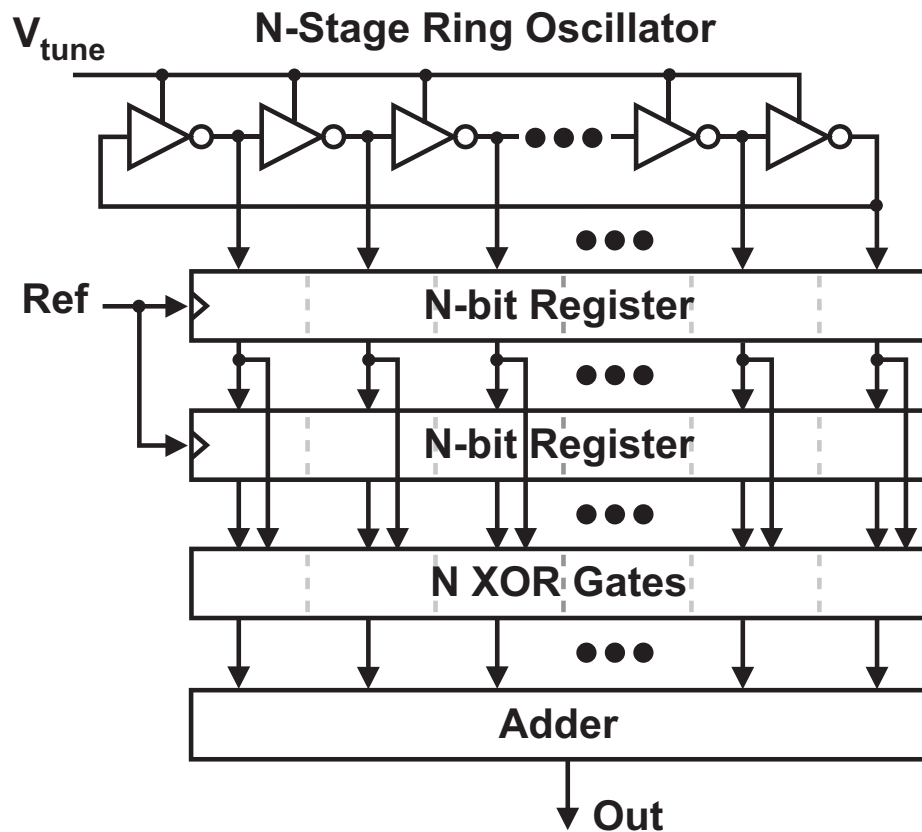
# Phase Sampling Can Be More Efficient than Counting




- $V_{\text{tune}}$  controls delay of cells
  - Alters the number of transitions per ref clock period
- Digital circuits compute transition count at each sample
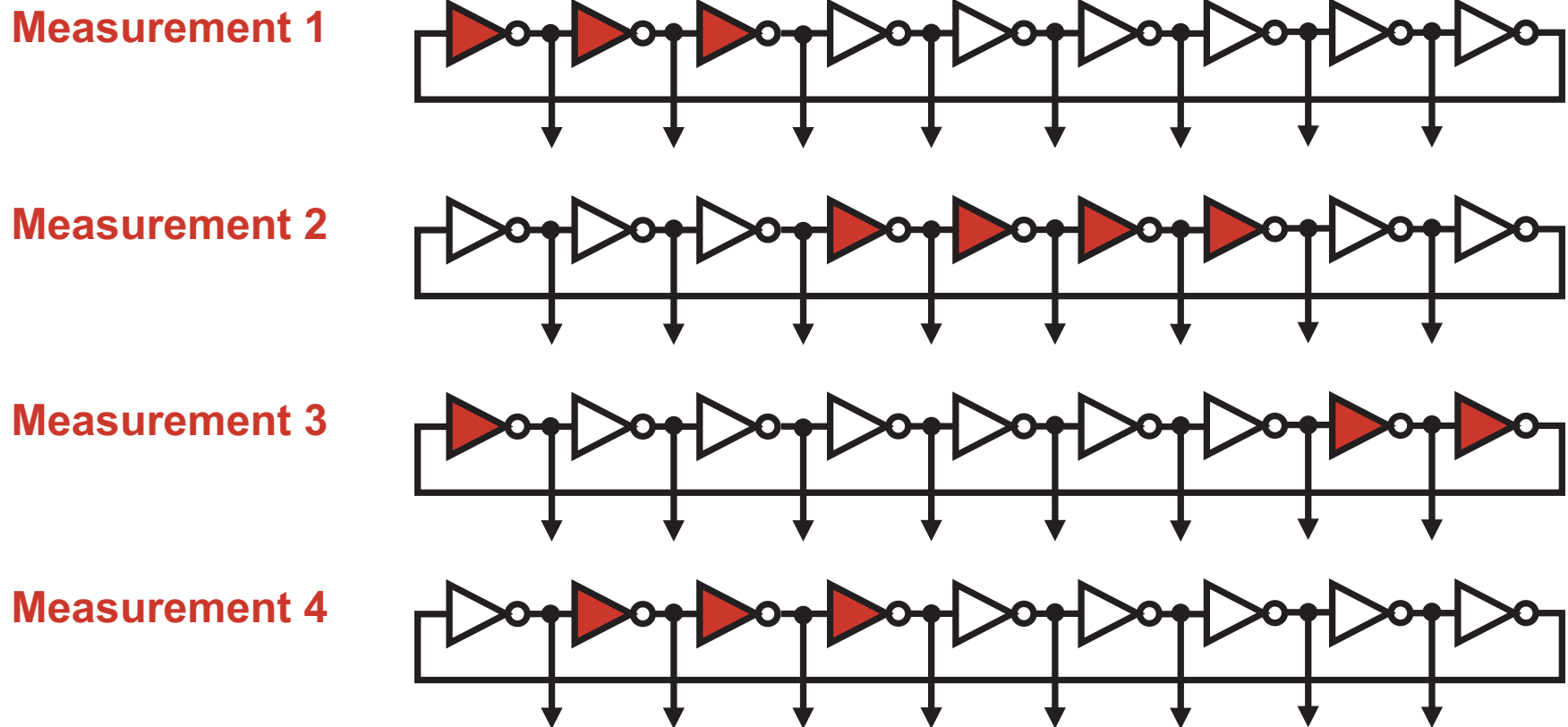
# VCO-Based Quantizer Shapes Delay Mismatch



- **Barrel shifting through delay elements**
  - Mismatch between delay elements is first order shaped


# Advantages of VCO-based Quantization

 

- **Highly digital implementation**
- **Offset and mismatch is not of critical concern**
- **Metastability behavior is potentially improved**
- **SNR improves due to quantization noise shaping**

**Implementation is high speed, low power, low area**

# Modeling a VCO-Based Quantizer

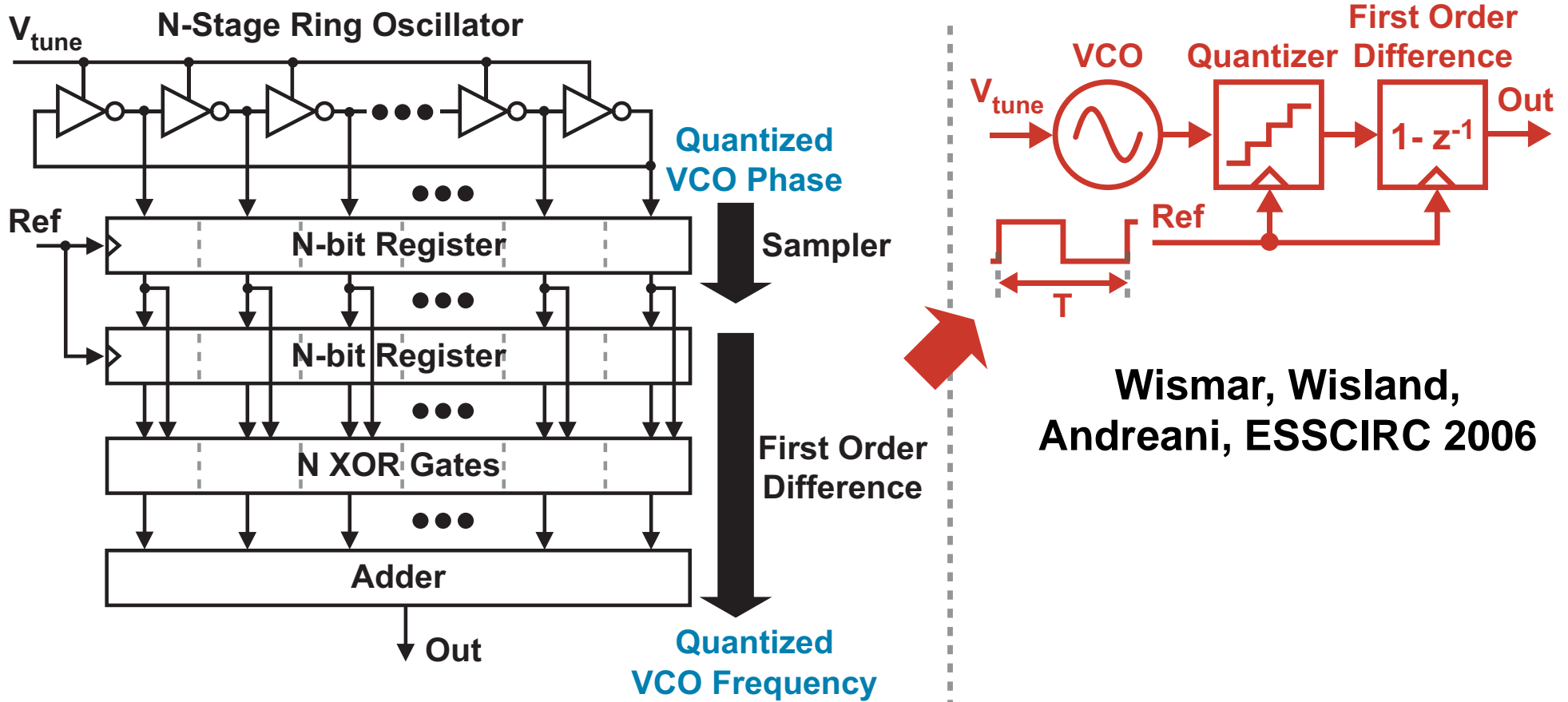


Wismar, Wisland,  
Andreani, ESSCIRC 2006


- VCO provides quantization, register provides sampling
  - Model as separate blocks for convenience
- XOR operation yields first order difference operation
  - Extracts VCO frequency from sampled VCO phase
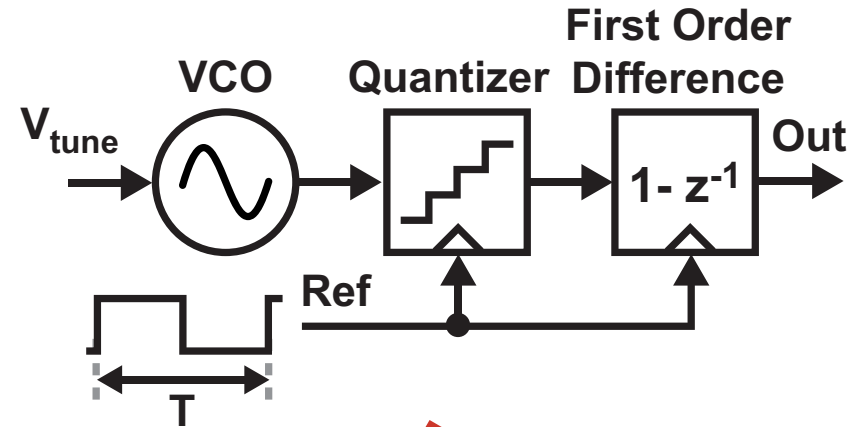
# Corresponding Frequency Domain Model

- VCO: nonlinear integrator
- Phase sampler: scale by  $1/T$
- Quantizer: adds noise
- First order diff: shapes noise




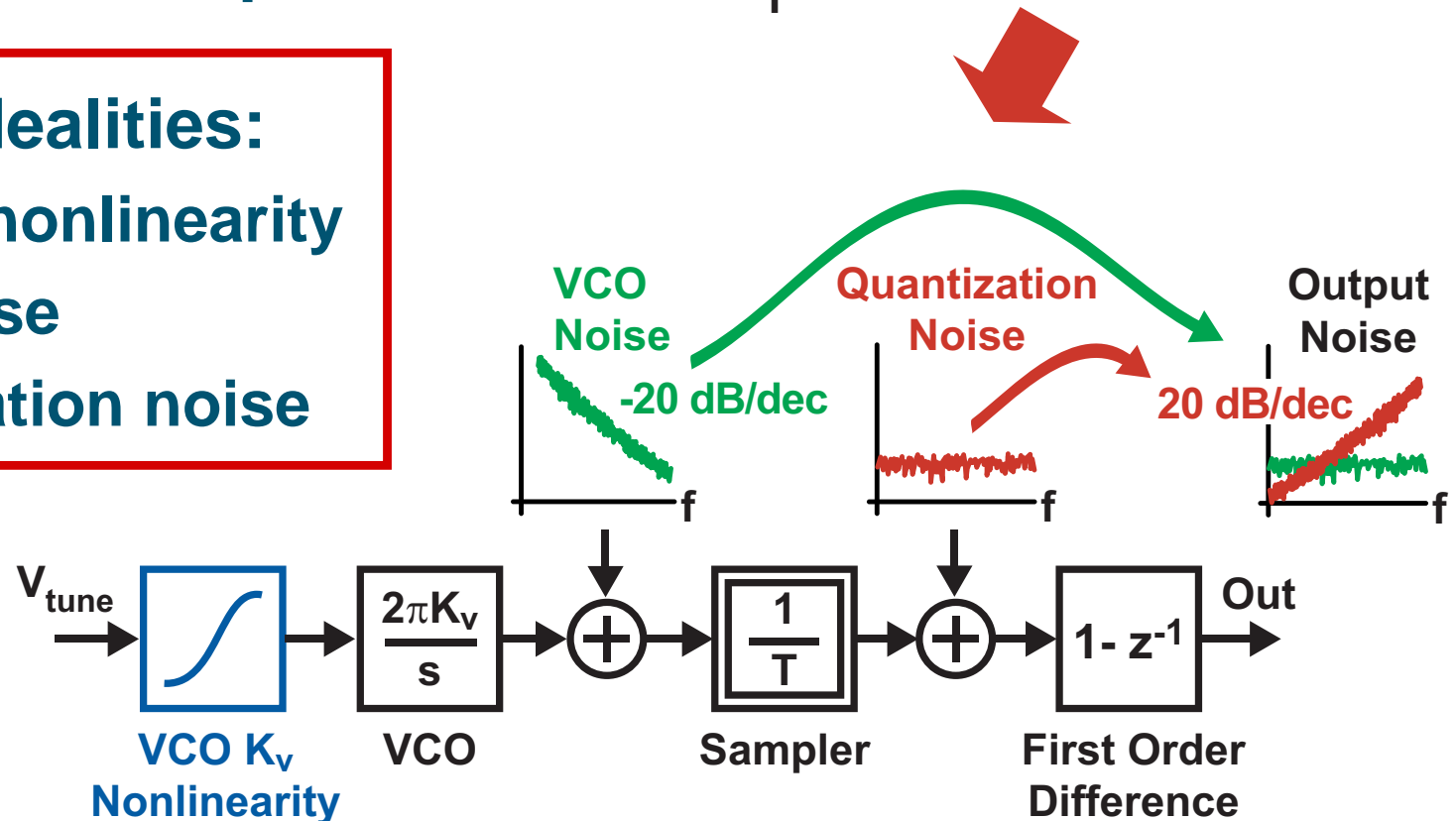
- Key non-idealities:
  - VCO  $K_V$  nonlinearity
  - VCO noise
  - Quantization noise





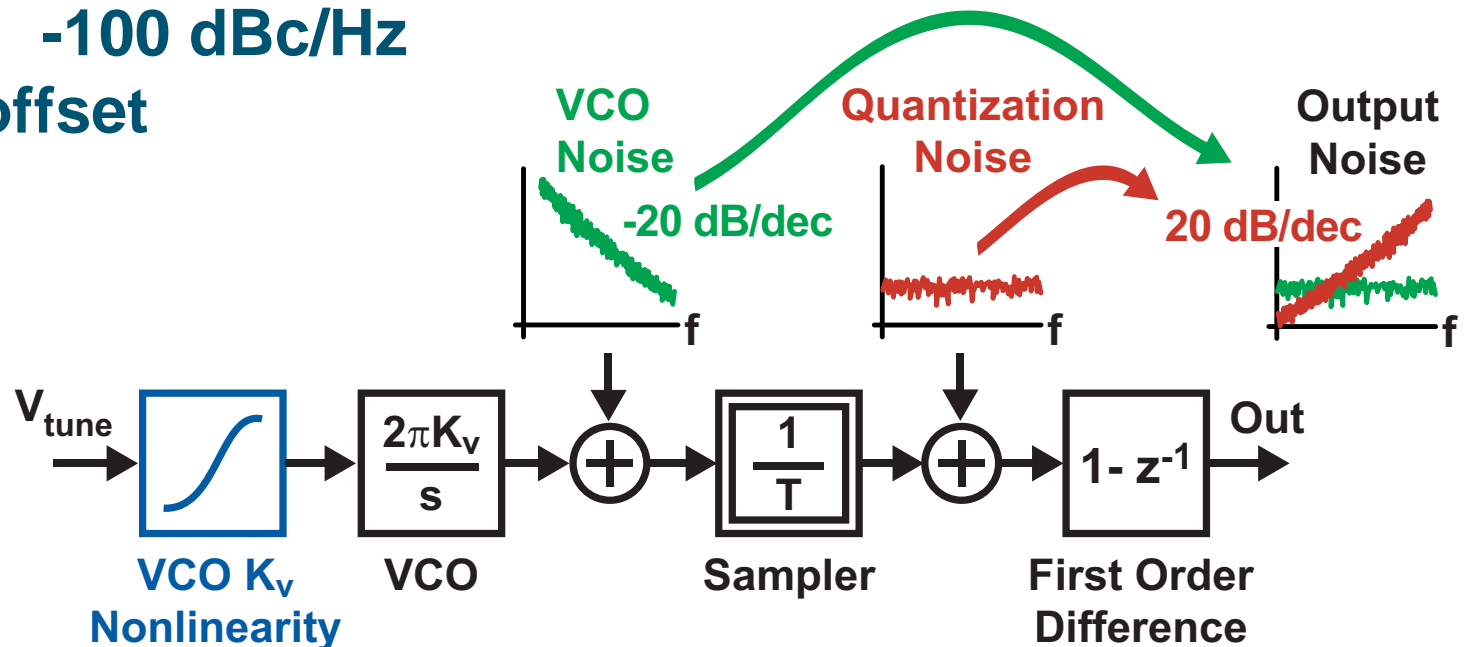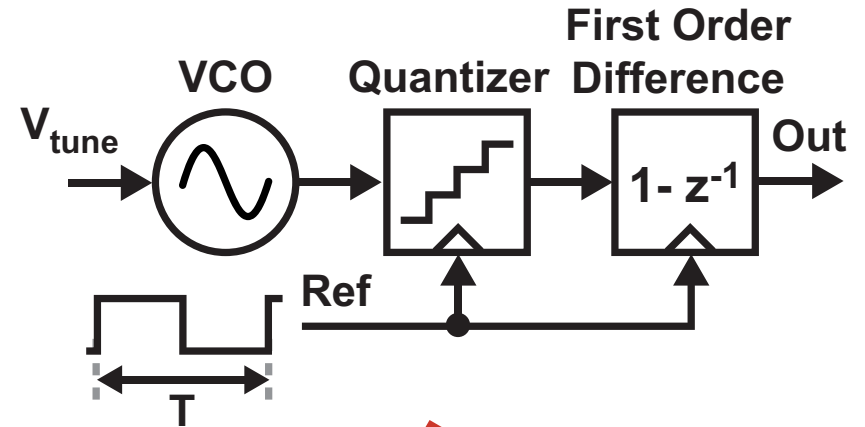
# Example Design Point for Illustration

- Ref clk:  $1/T = 1 \text{ GHz}$
- 31 stage ring oscillator
  - Nominal delay per stage: 65 ps
- $K_{VCO} = 500 \text{ MHz/V}$ 
  - $\pm 5\%$  linearity
- VCO noise: -100 dBc/Hz at 10 MHz offset




# Example SNDR with 20 MHz BW (1 GHz Sample Rate)

Simulated ADC Output Spectrum

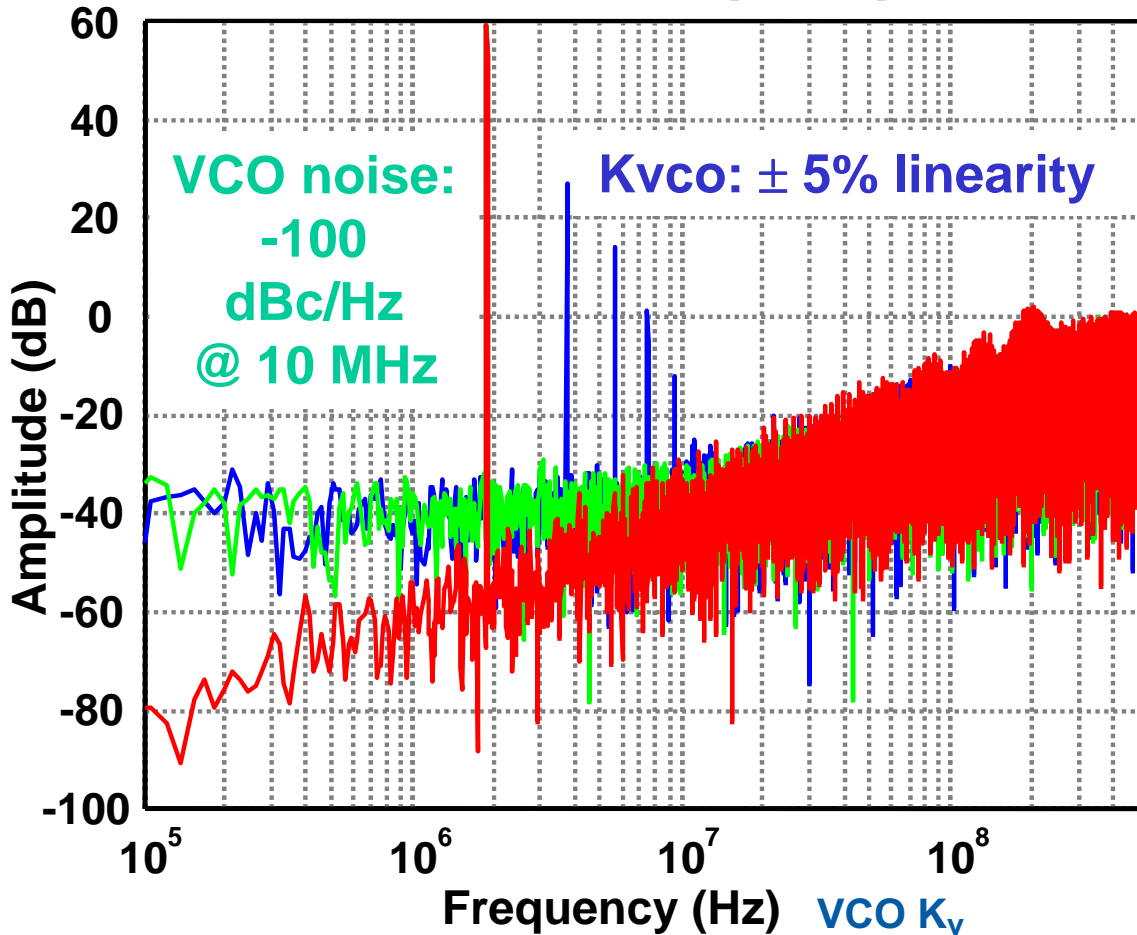


Conditions	SNDR
Ideal	68.2 dB
VCO Thermal Noise	65.4 dB
VCO Thermal + Nonlinearity	32.2 dB

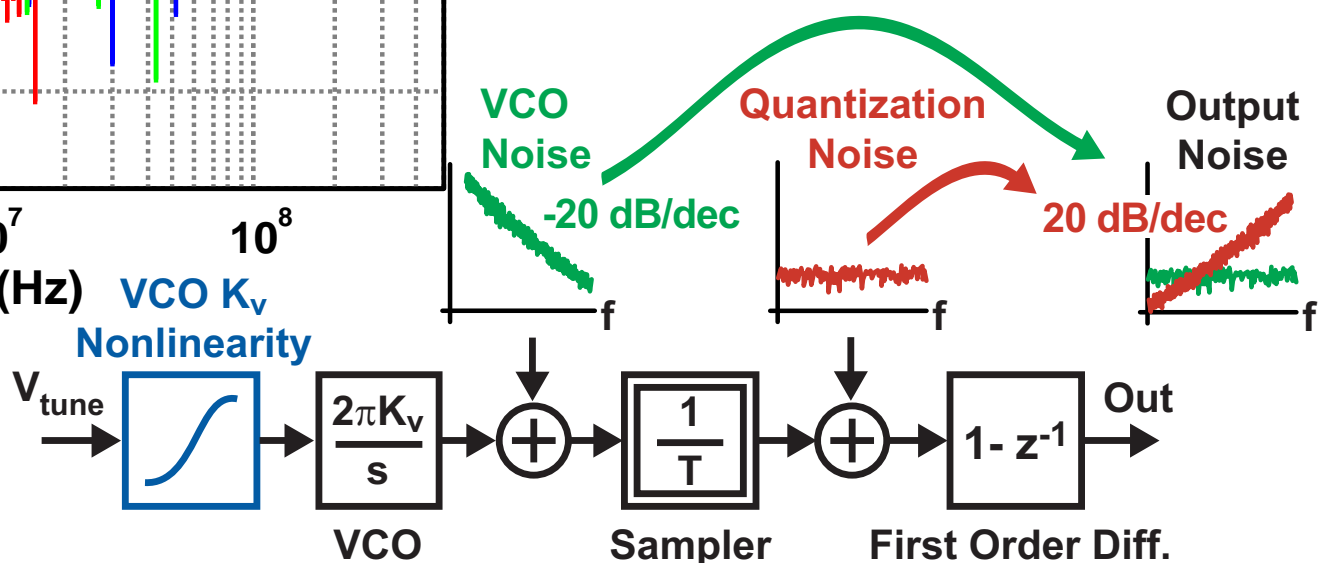


# Key Issues: Nonlinearity and VCO Phase Noise

- **VCO  $K_v$  nonlinearity**
  - Limits SNDR with distortion
  - Linear  $K_v$  oscillator difficult
- **VCO phase noise**
  - Degrades SNR and SNDR
  - Improves with area/power

Conditions	SNDR
<b>Ideal</b>	<b>68.2 dB</b>
<b>VCO Thermal Noise</b>	<b>65.4 dB</b>
<b>VCO Thermal + Nonlinearity</b>	<b>32.2 dB</b>

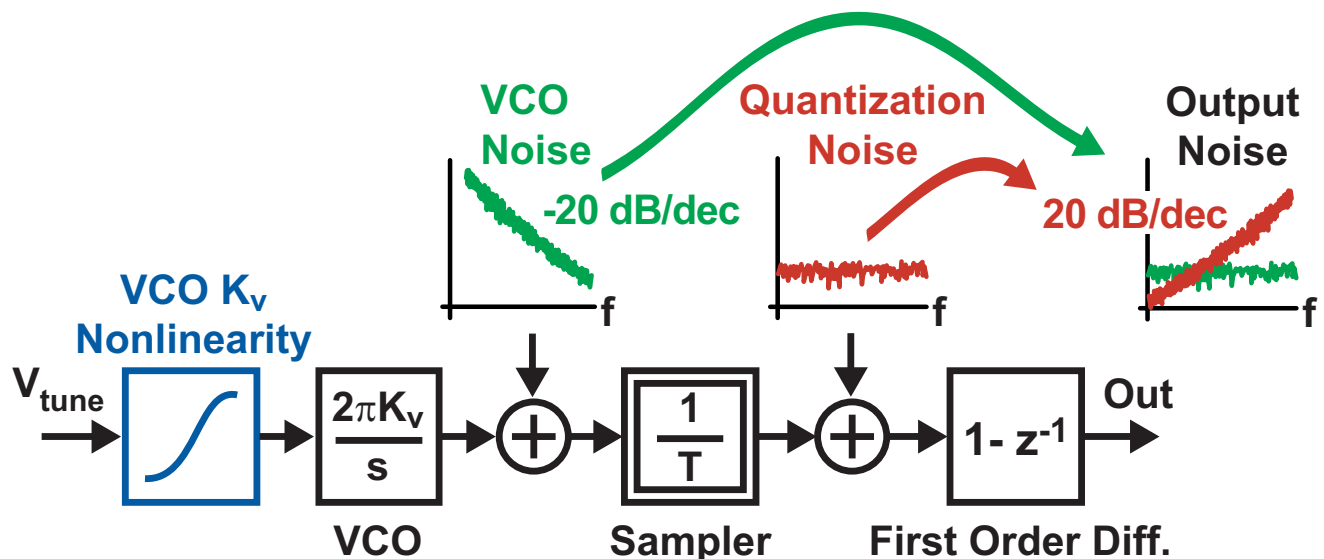


# Pseudo-Differential Implementation

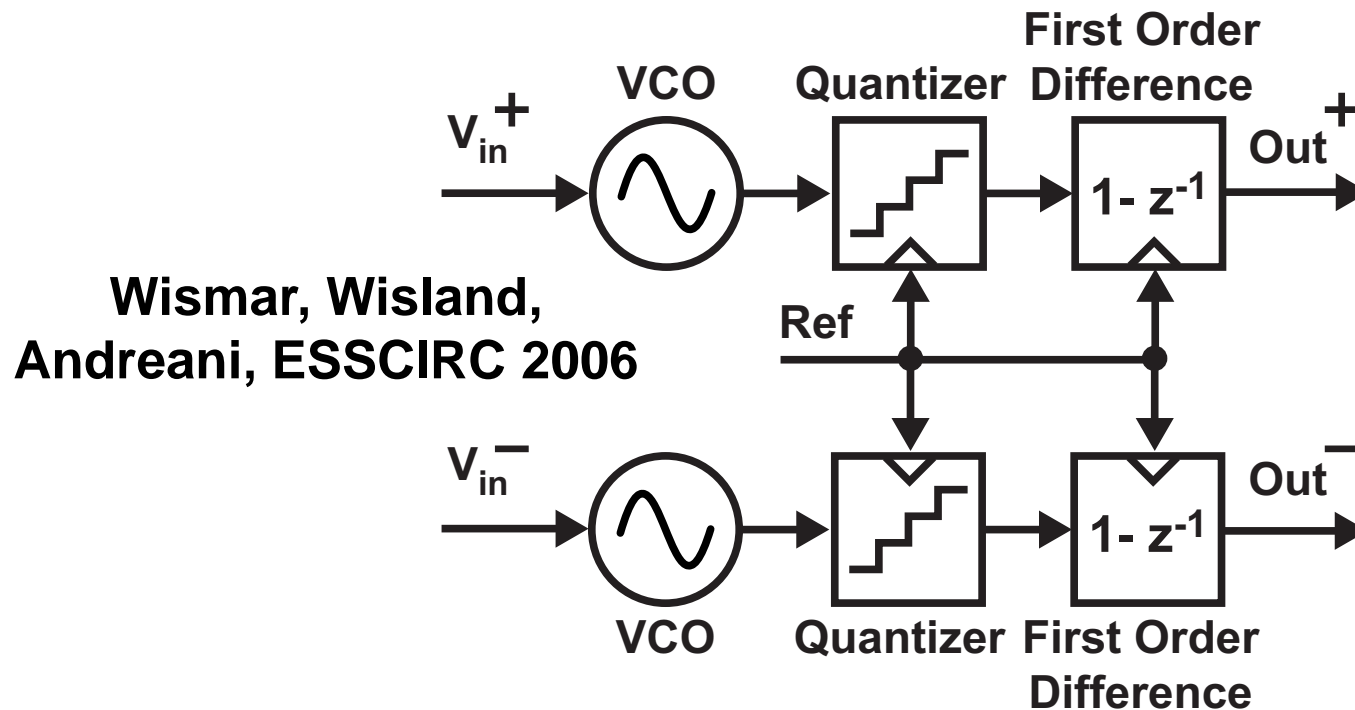


- Even order nonlinearity reduced
- VCO phase noise reduced 3dB (double area/power)
- Benchmark: 44 dB SNDR with 20 kHz BW
  - Impressive 0.2V supply, 440 nW power in 90nm CMOS

# Digital Correction of Nonlinearity

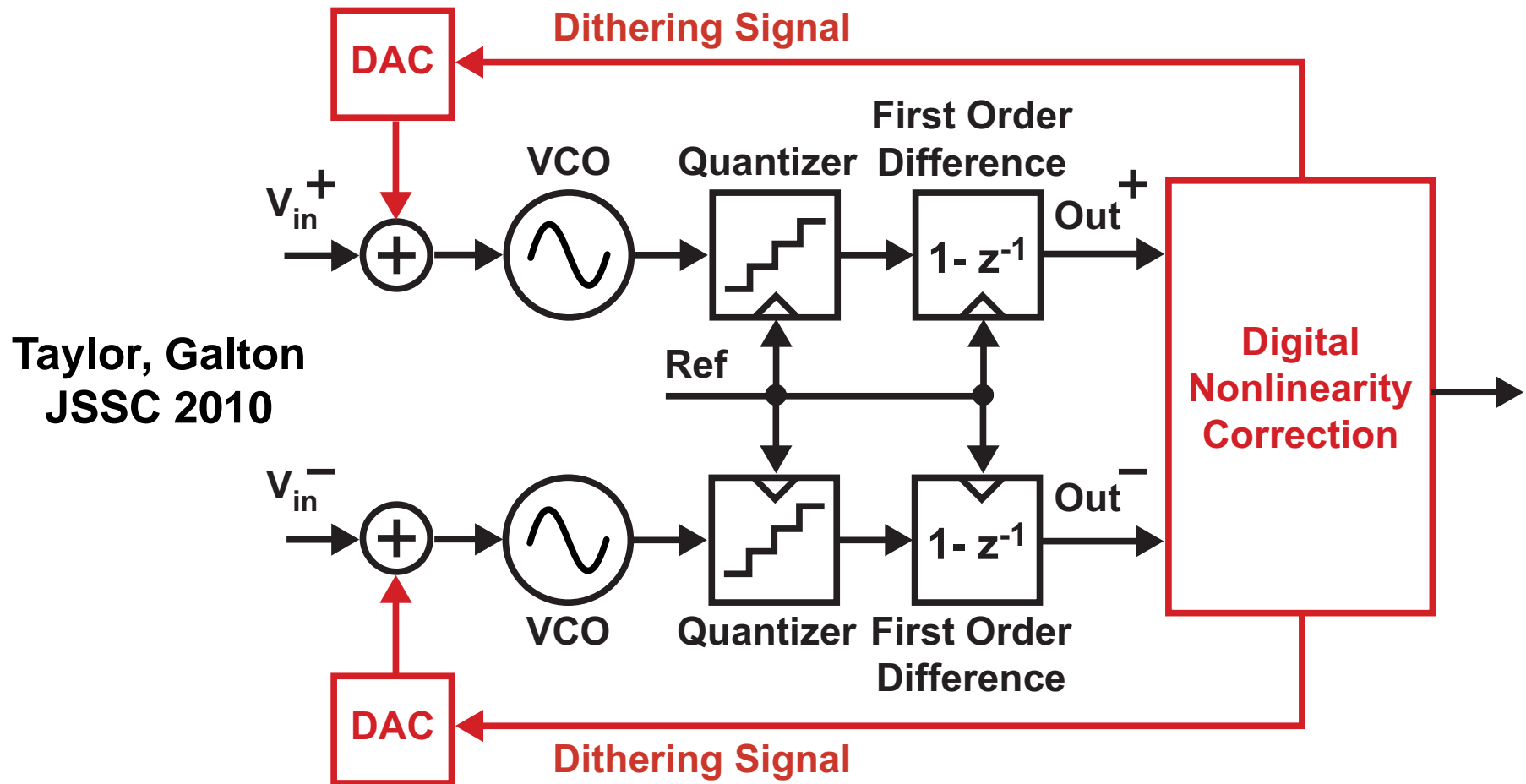


- **Highly digital implementation (65nm CMOS)**
  - ~70/78 dB SNDR at 18/4.5MHz BW (FOM: 297fJ/conv)
- **Issues: calibration time, only first order noise shaping**
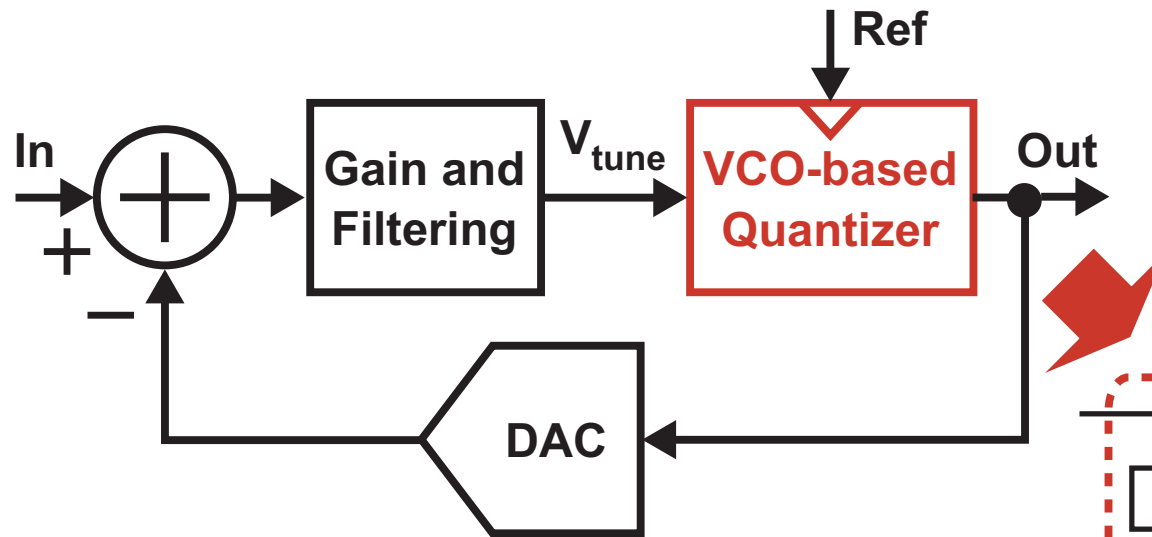
# Reducing the Impact of Nonlinearity using Feedback




Iwata, Sakimura,  
TCAS II, 1999  
Naiknaware, Tang,  
Fiez, TCAS II, 2000

 - **Continuous-time  $\Delta$ - $\Sigma$  ADC**
  - VCO-based quantizer provides multi-bit implementation with first order noise shaping
- **Gain before VCO quantizer**
  - Suppresses VCO nonlinearity
  - Suppresses VCO phase noise



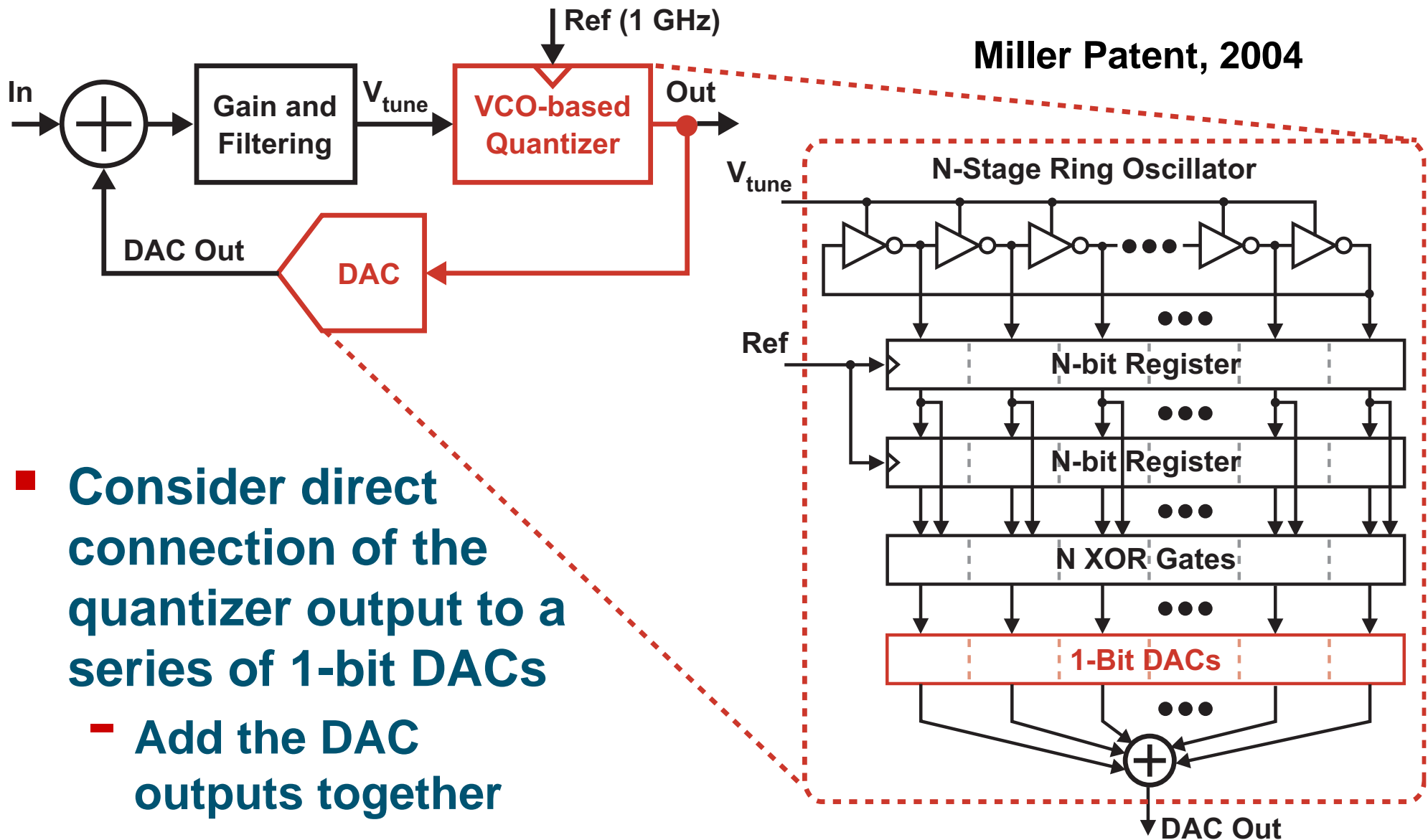
# Leveraging Barrel Shifting in the Quantizer



- Consider direct connection of the quantizer output to a series of 1-bit DACs
  - Add the DAC outputs together


**Intrinsic barrel shifting of the DAC elements is achieved!**
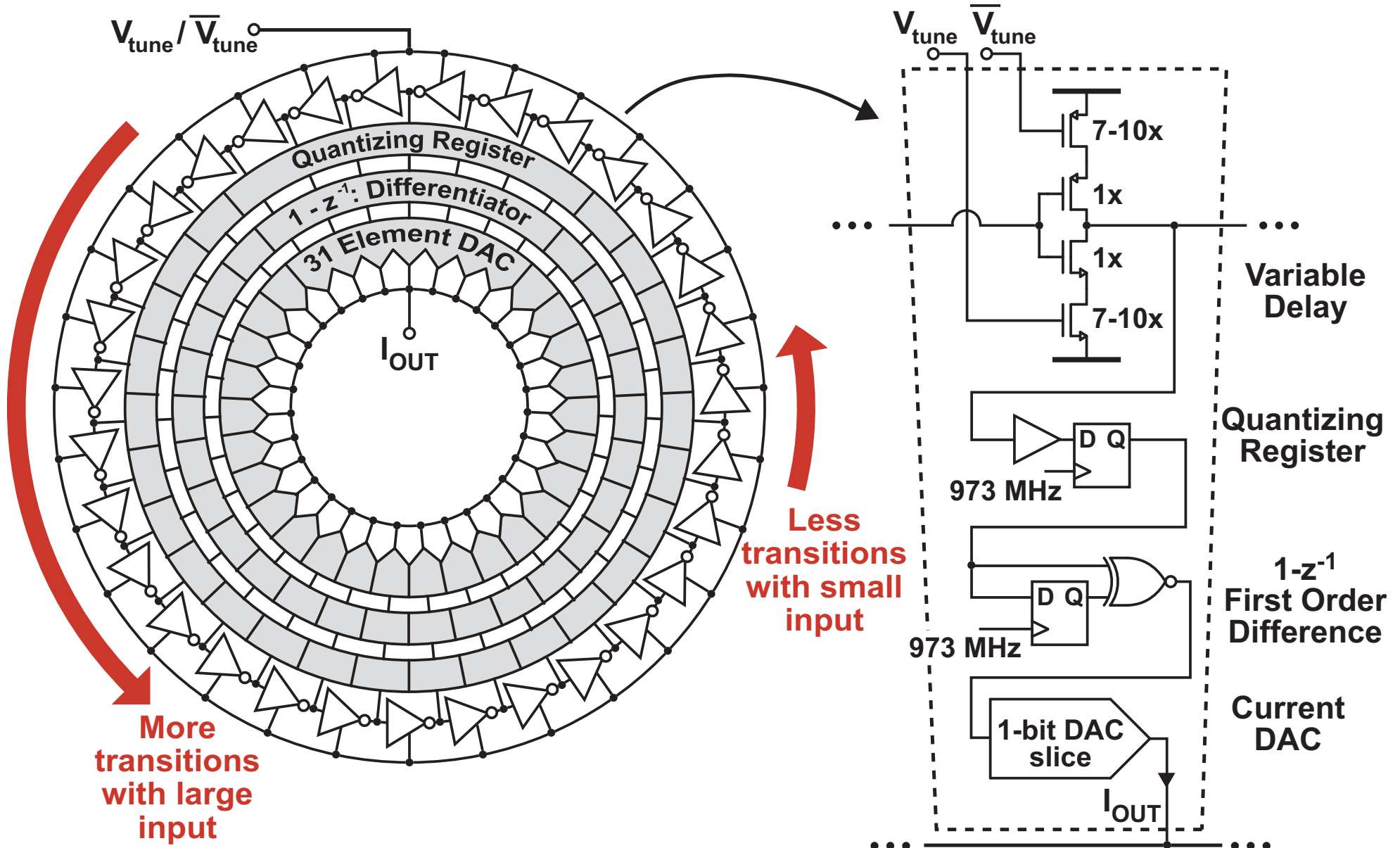
# A Geometric View of the VCO Quantizer/DEM and DAC





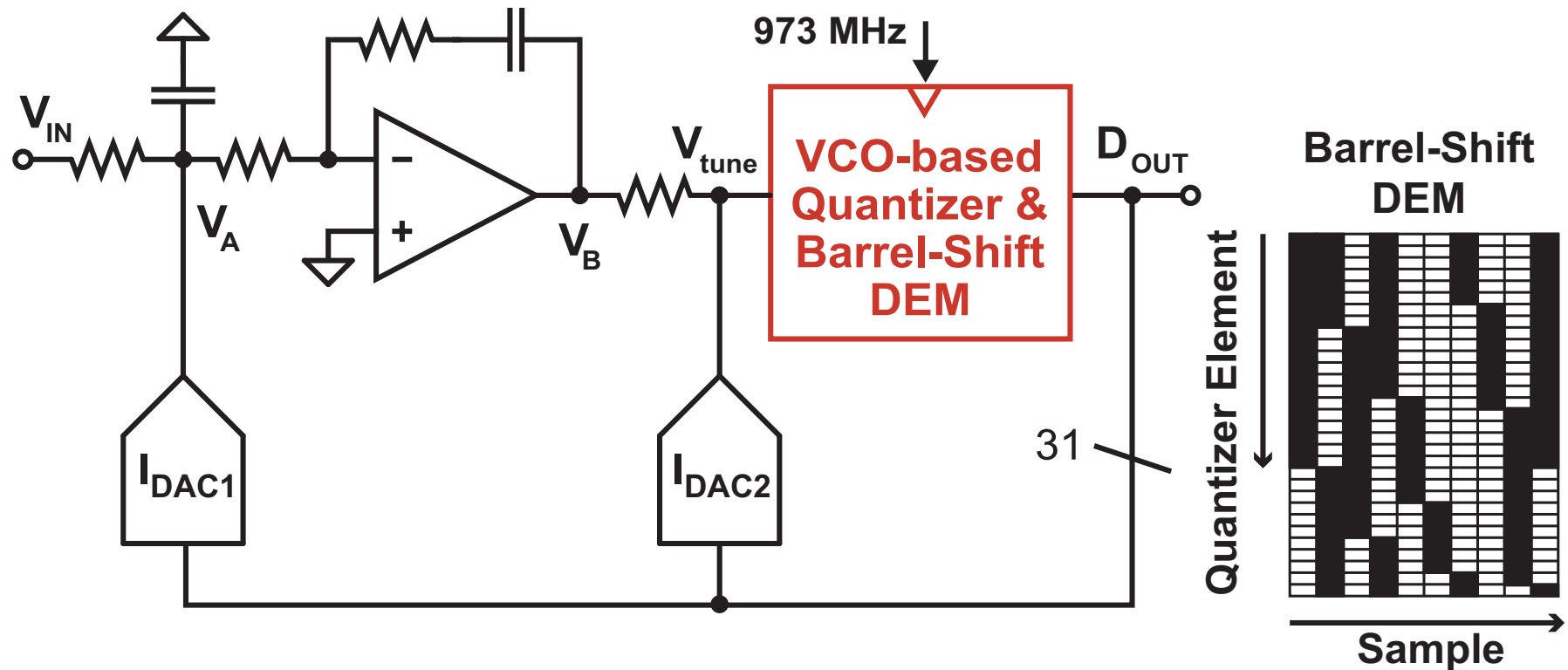
# A Second Order Continuous-Time Delta-Sigma ADC



- **Second order dynamics achieved with only one op-amp**
  - Op-amp forms one integrator
  - $I_{dac1}$  and passive network form another (lossy) integrator
  - Minor loop feedback compensates for quantizer delay
- **Third order noise shaping** due to VCO-based quantizer



# Custom IC Implementing the Prototype

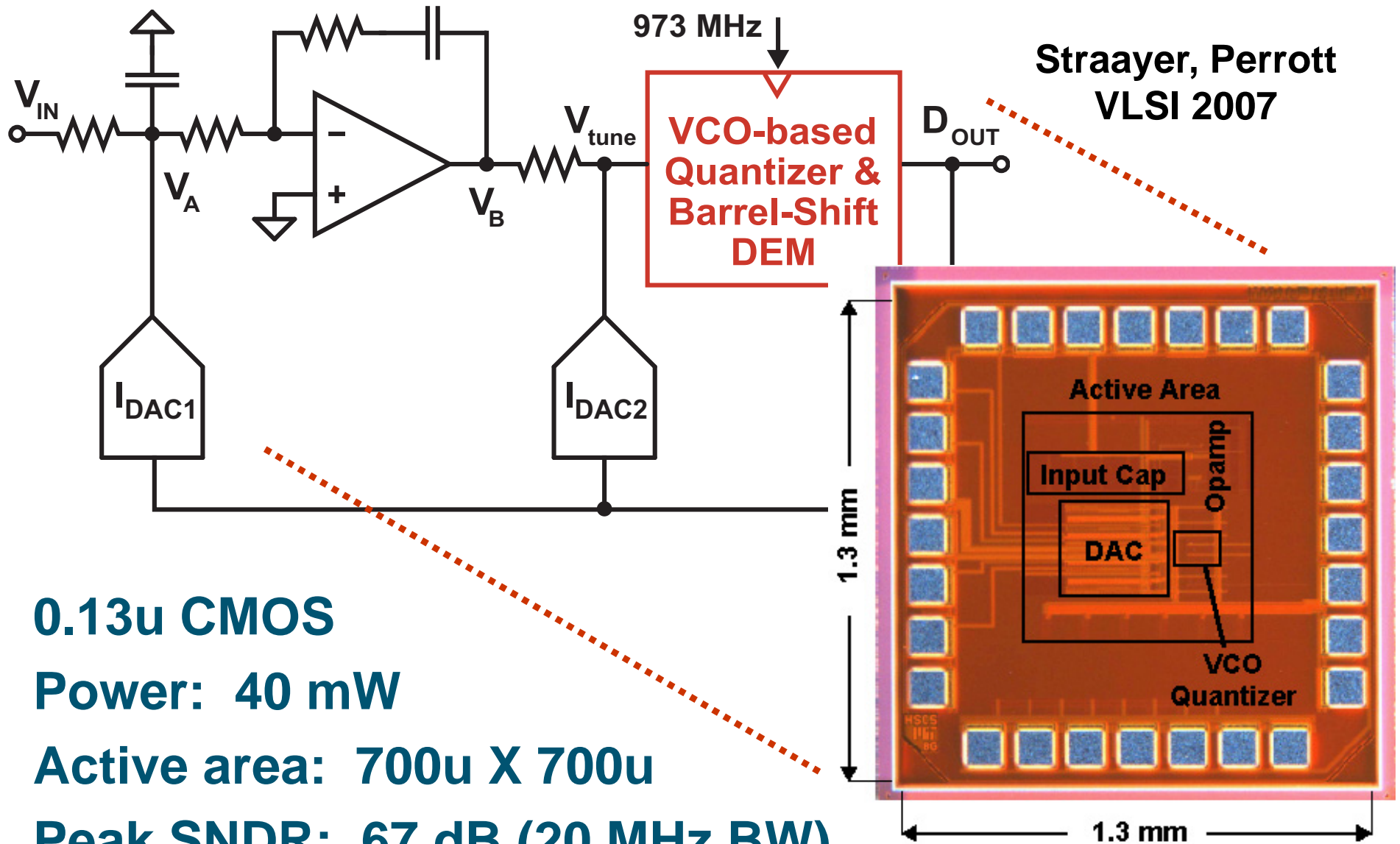

Straayer, Perrott  
VLSI 2007


- 0.13u CMOS
- Power: 40 mW
- Active area: 700u X 700u
- Peak SNDR: 67 dB (20 MHz BW)
- Efficiency: 0.5 pJ/conv. step

# Design of the VCO Core Inverter Cell

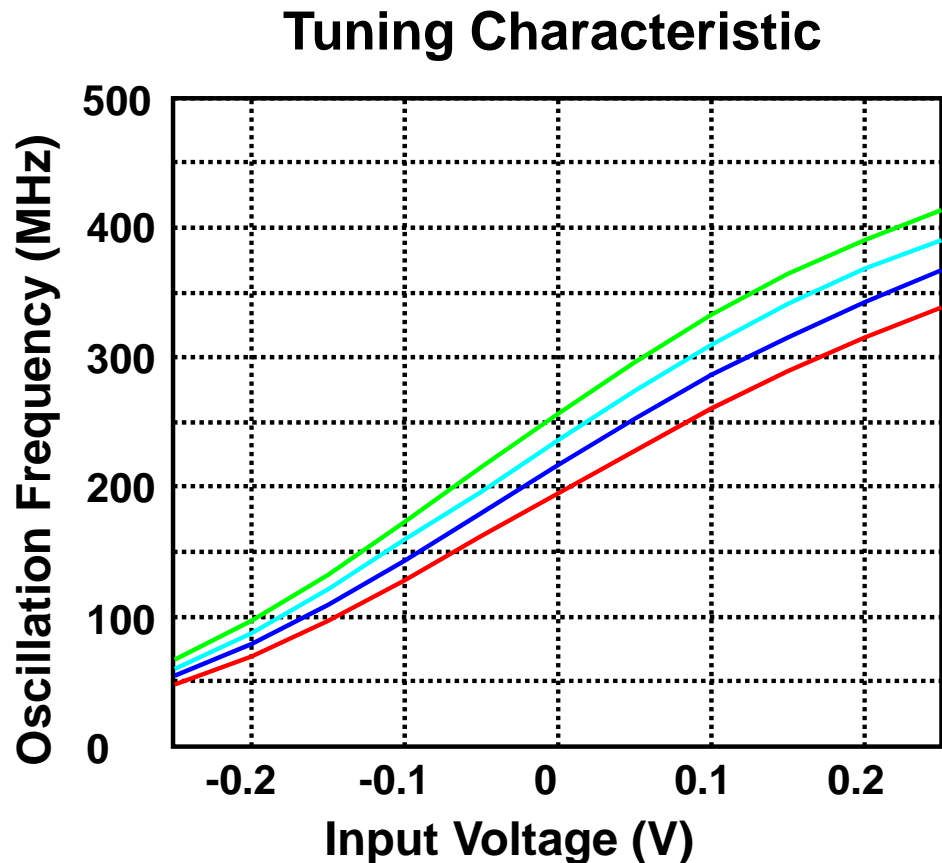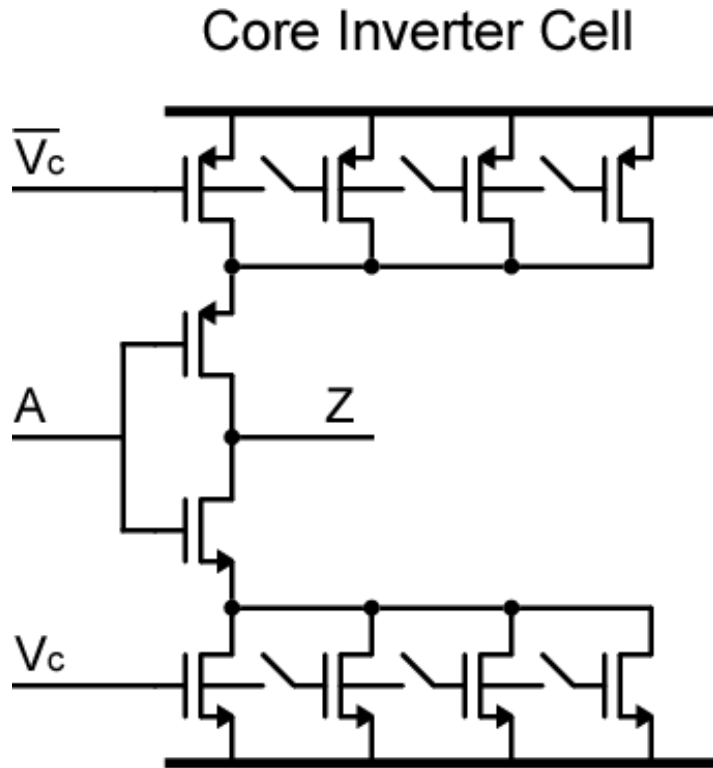

- 31 stages
- Fast for good resolution ( $< 100$  psec / stage)
- Large  $K_{VCO}$  (600-700 MHz) with good dynamic range
- 2 bits of coarse tuning for process variations
- $< 8$  mW for 1 GSPS 5-bit quantizer / DEM


# Opamp Design is Straightforward

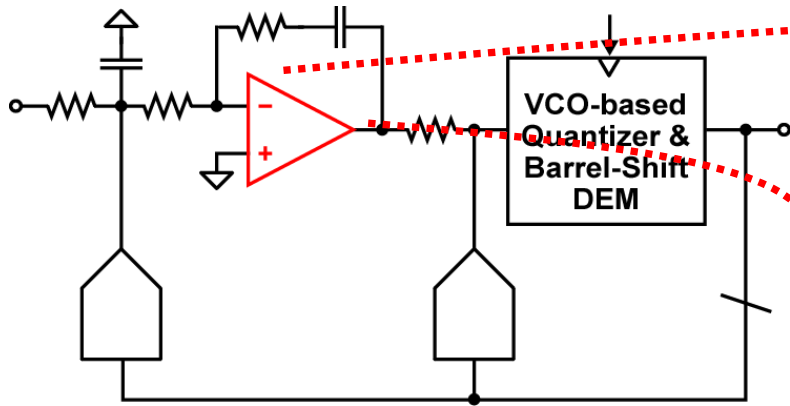
 
## Simulated Performance:


- $A_v = 55$  dB
- $GBW = 2$  GHz
- $P_{DISS} = 15$  mW

High SNR of VCO-based quantizer allows reduced opamp gain ( $A_v$ )



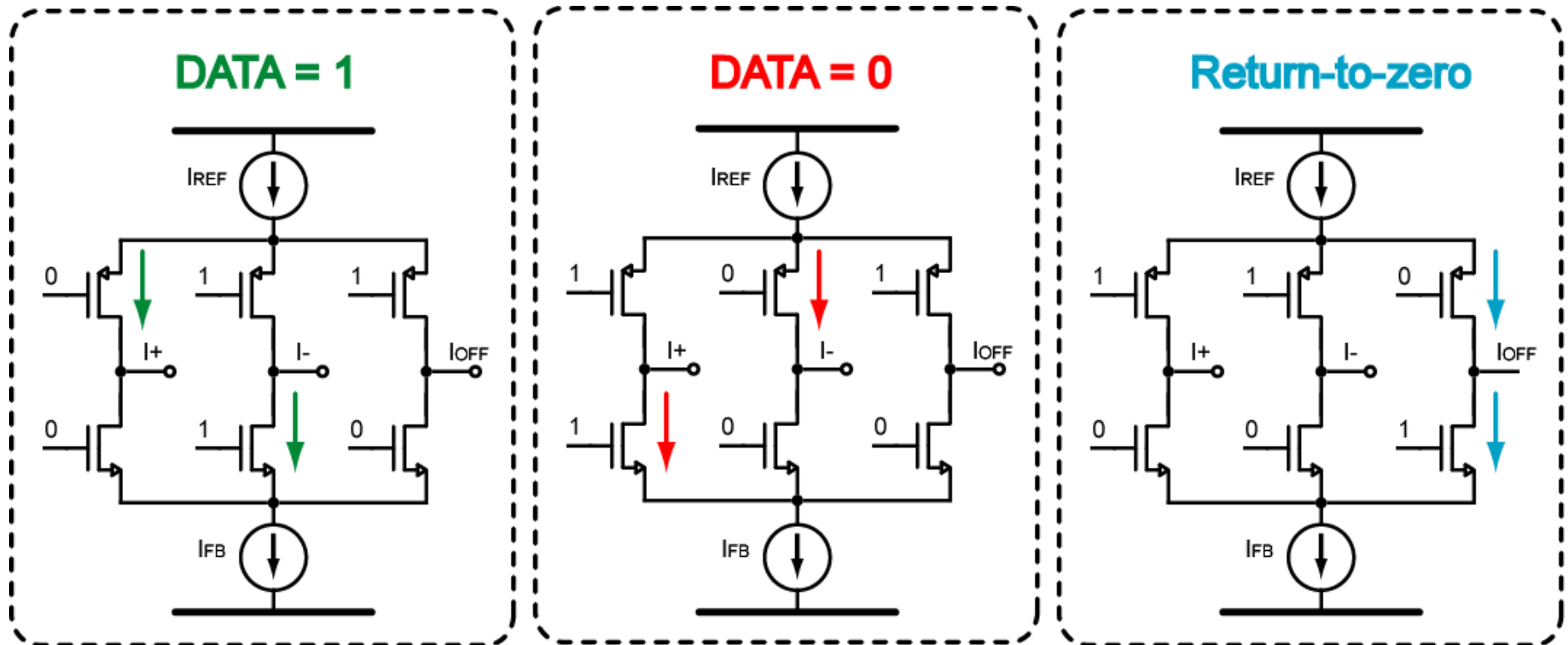
# Primary Feedback DAC Schematic


- Fully differential RZ pulses
- Triple-source current steering
- $I_{OFF}$  is terminated off-chip



# Measured Spectrum From Prototype

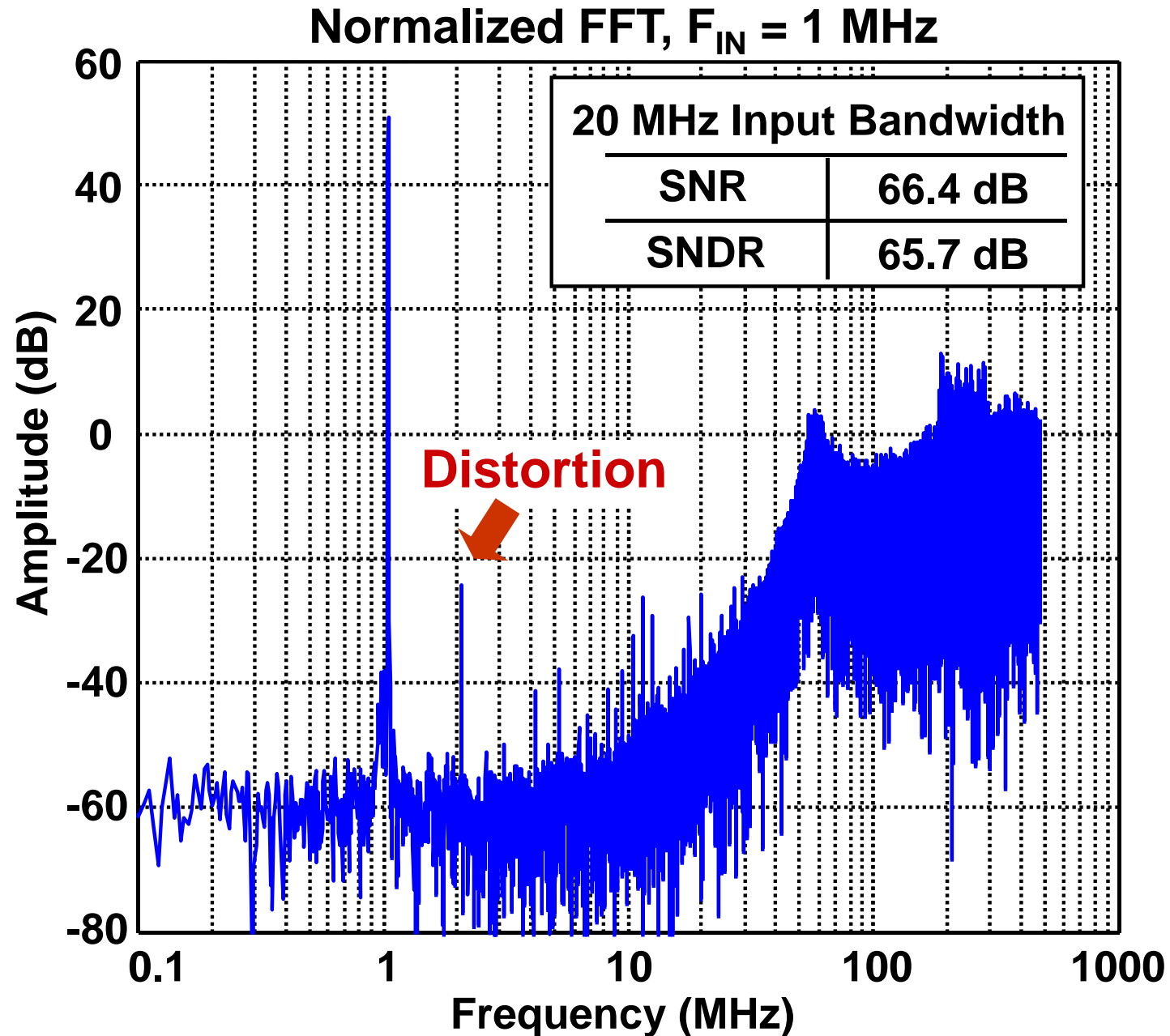

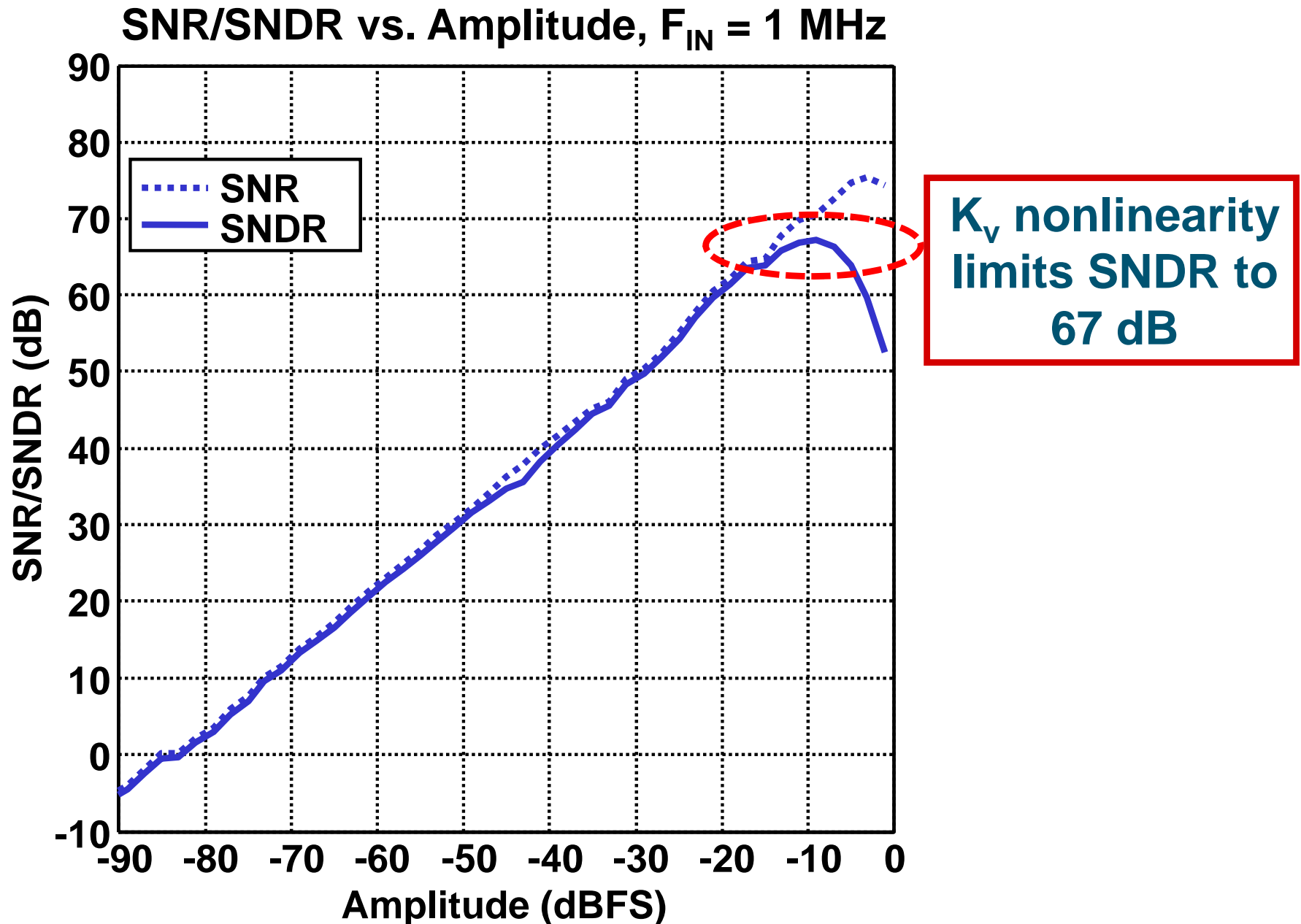
# Measured SNR/SNDR Vs. Input Amplitude (20 MHz BW)



***How Do We Overcome  $K_v$  Nonlinearity to Improve SNDR?***



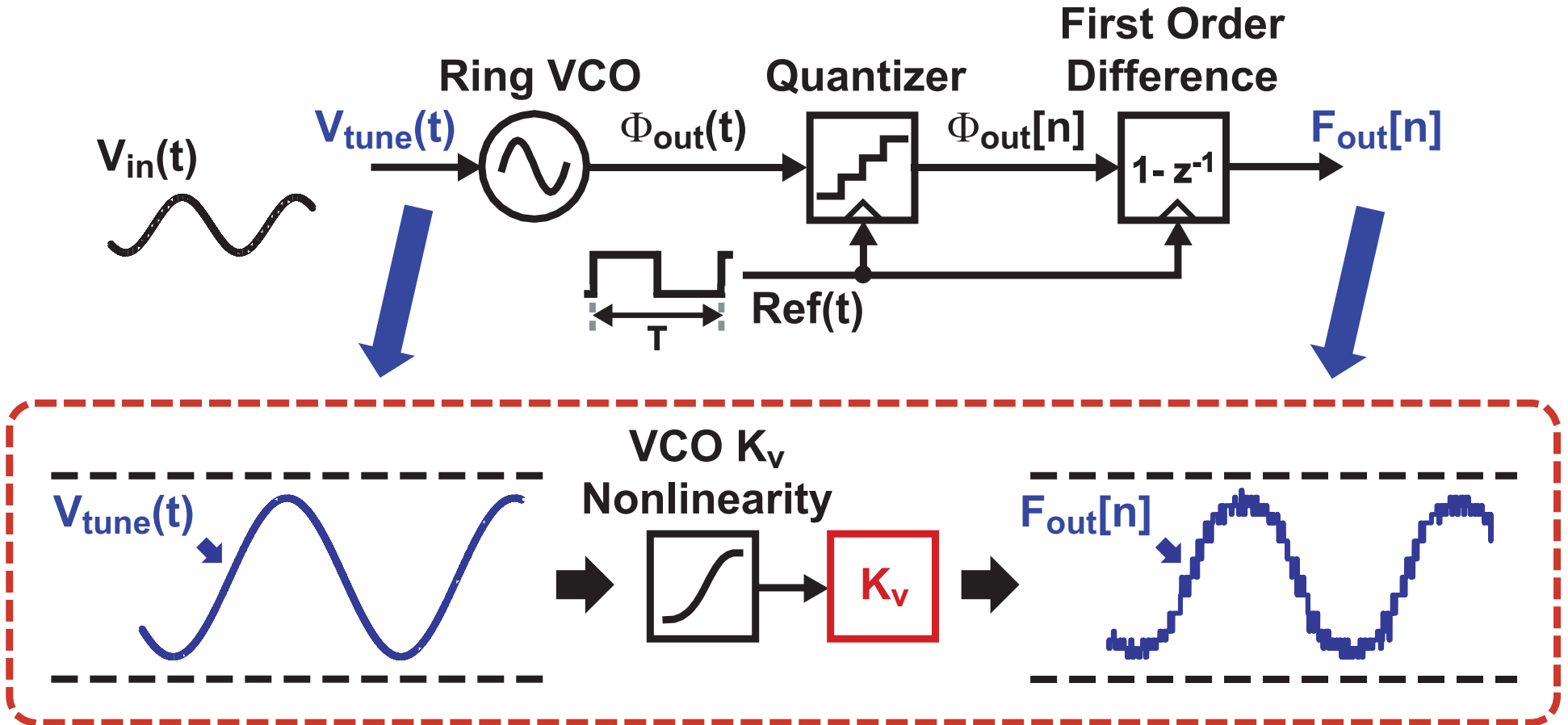
# Voltage-to-Frequency VCO-based ADC (1<sup>st</sup> Order $\Delta$ - $\Sigma$ )




- Typically, VCO frequency is desired output variable
  - Input uses full voltage-to-frequency ( $K_v$ ) characteristic
  - Strong distortion at extreme ends of the  $K_v$  curve
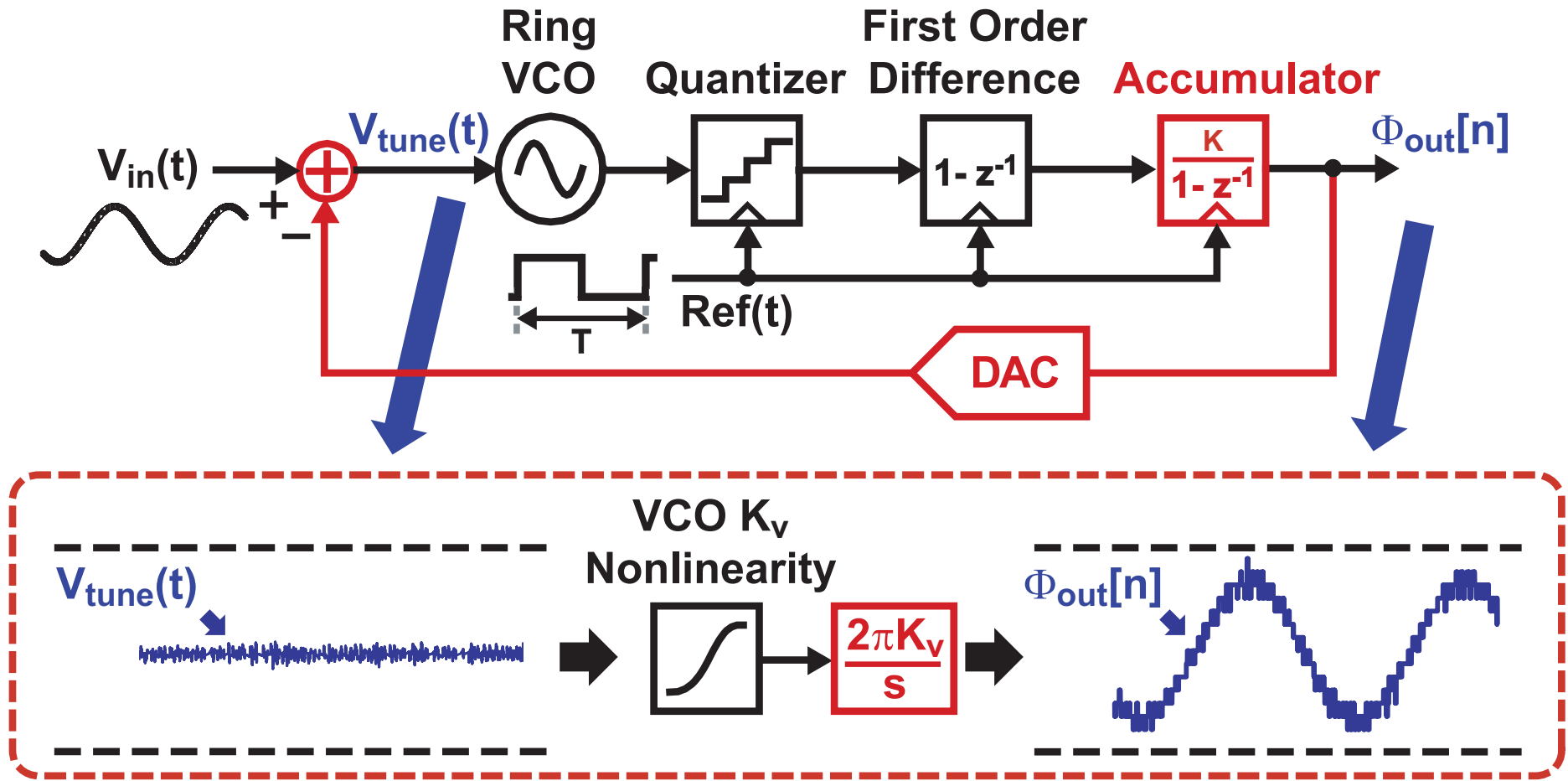
# Voltage-to-Phase Approach (1<sup>st</sup> Order $\Delta$ - $\Sigma$ )




- VCO output *phase* is now the output variable
  - Small perturbation on  $V_{tune}$  allows large VCO phase shift
  - VCO acts as a CT integrator with *infinite* DC gain
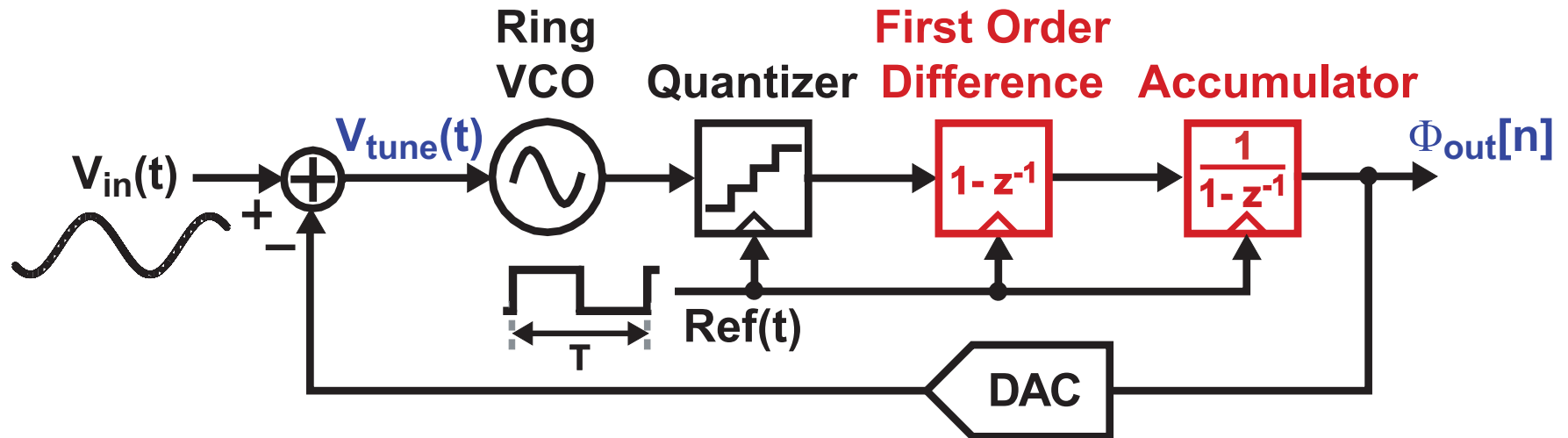
# High Speed Implementation of Phase-Based ADC




Park, Perrott  
JSSC 2009

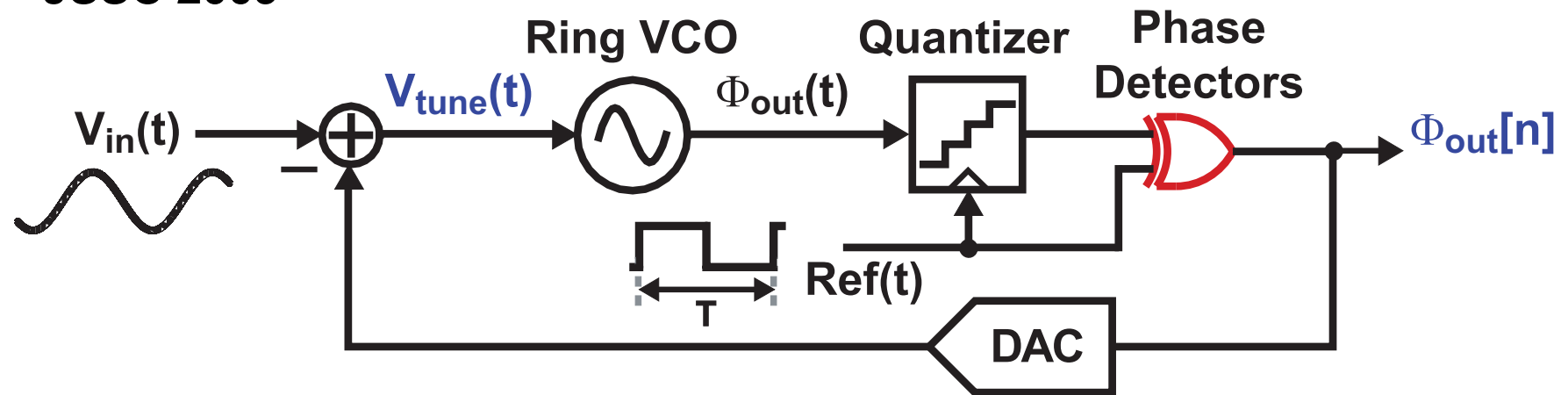


High SNDR requires higher order  $\Delta-\Sigma$  ...
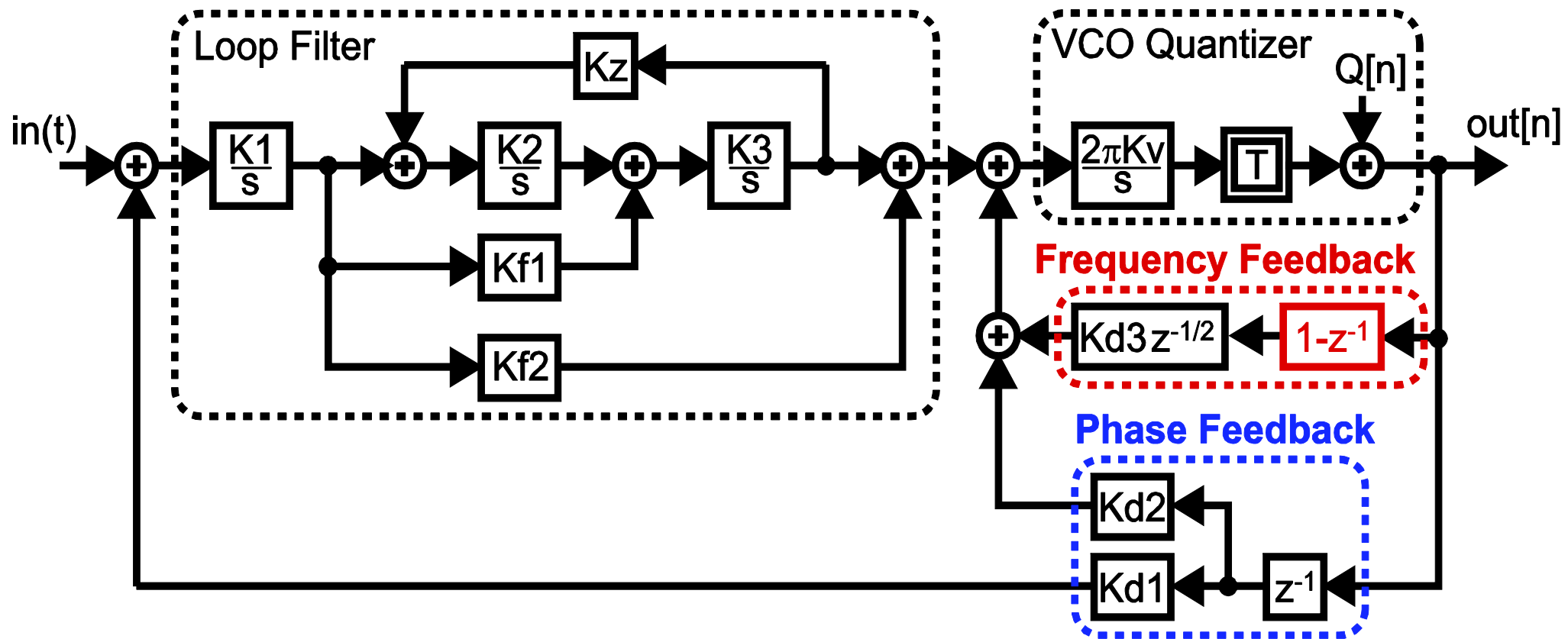
# Proposed 4<sup>th</sup> Order Architecture for Improved SNDR




- **Goal: ~80 dB SNDR with 20 MHz bandwidth**
  - Use 4<sup>th</sup> order loop filter, 4-bit VCO-based quantizer
  - 4-bit quantizer: tradeoff resolution versus DEM overhead
- **Combined frequency/phase feedback for stability/SNDR**

# Schematic of Proposed Architecture

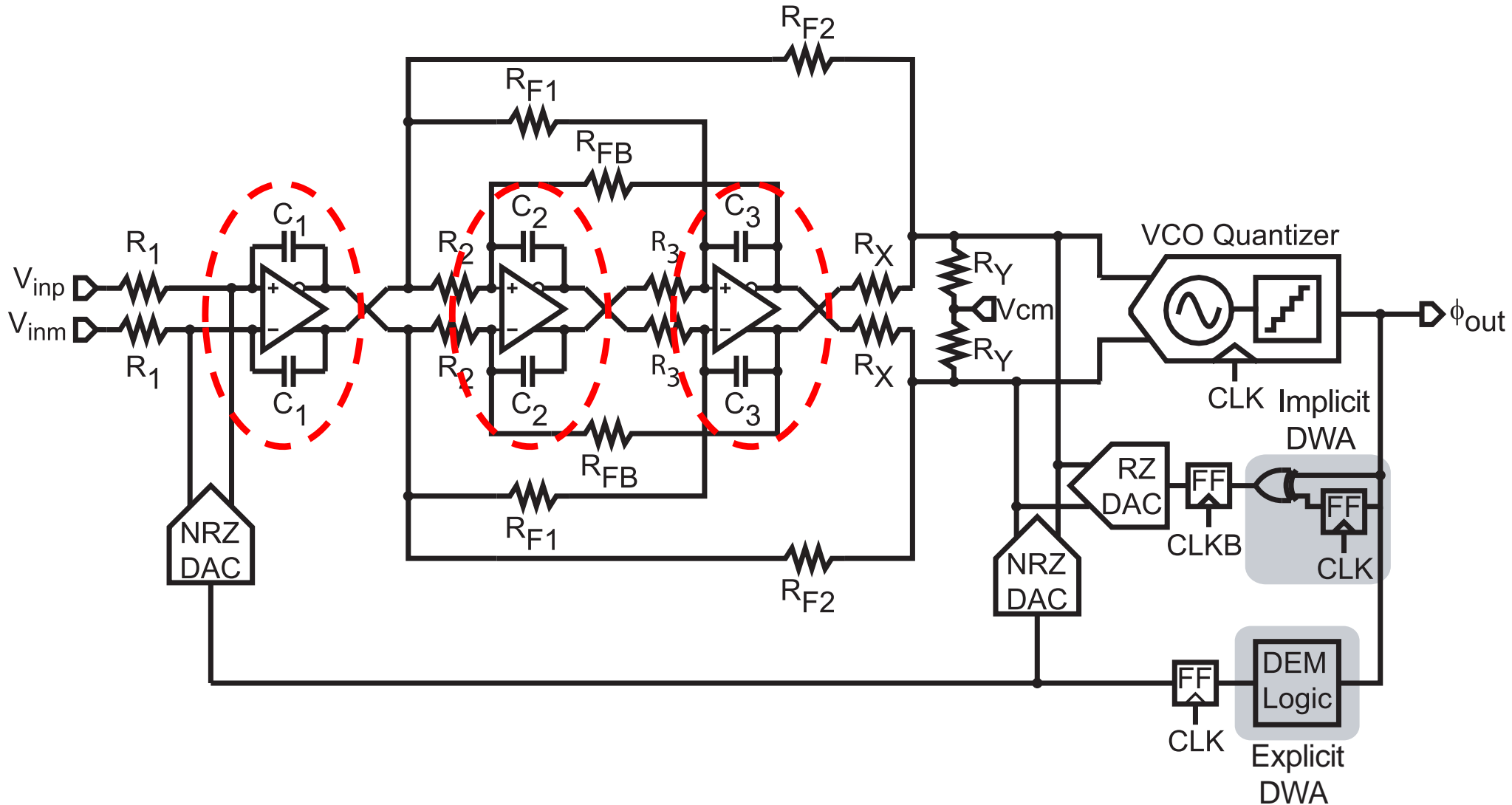

- Opamp-RC integrators
  - Better linearity than Gm-C, though higher power


# Schematic of Proposed Architecture

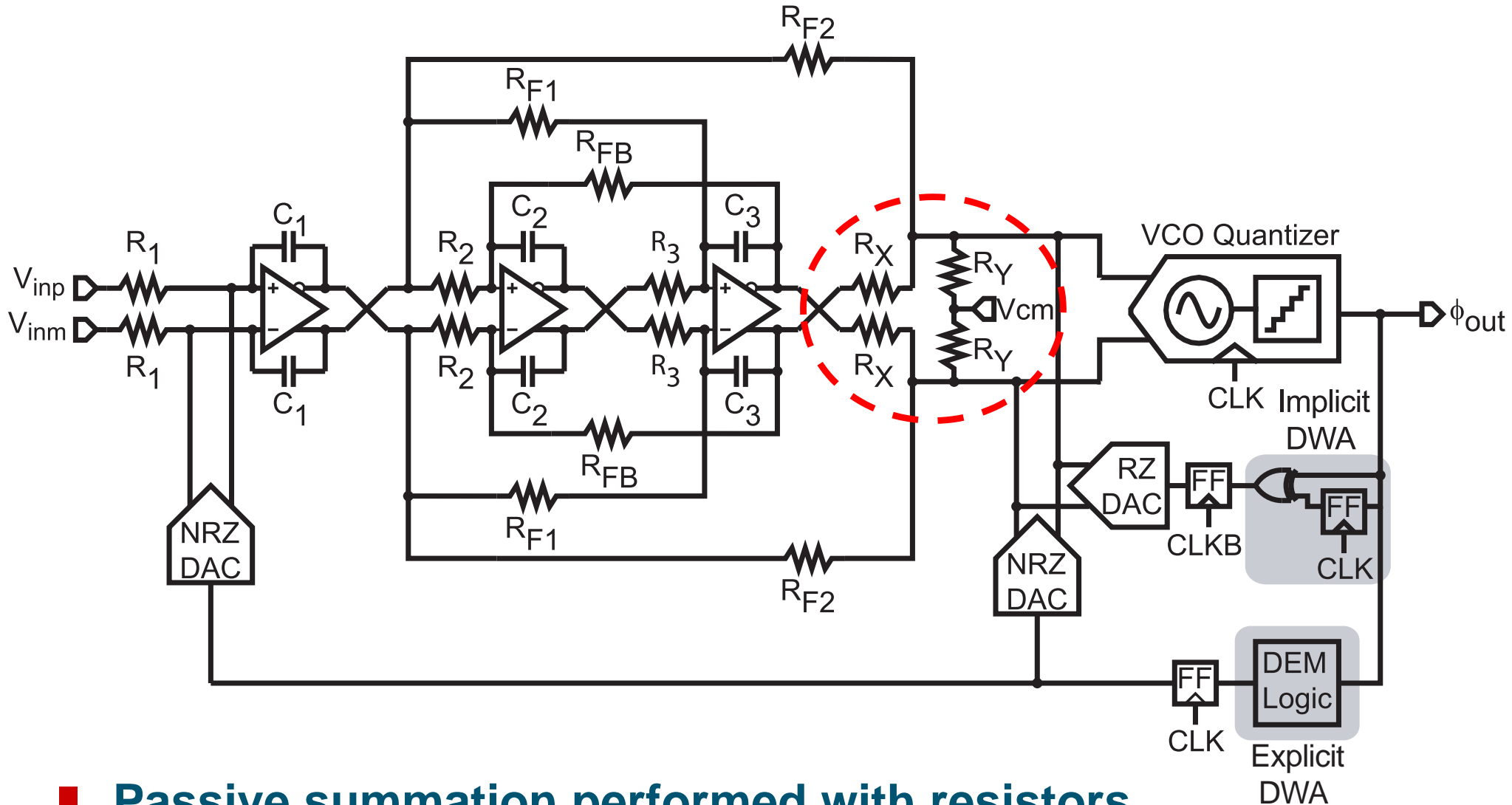

- **Passive summation performed with resistors**
  - Low power
  - Design carefully to minimize impact of parasitic pole


 
# Behavioral Simulation (available at [www.cppsim.com](http://www.cppsim.com))



## Key Nonidealities

- VCO Kv non-linearity
- Device noise
- Amplifier finite gain, finite BW
- DAC and VCO unit element mismatch




**85 dB SNDR!**

**VCO nonlinearity is *not* the bottleneck for achievable SNDR!**




## ***Circuit Details***

# VCO Integrator Schematic

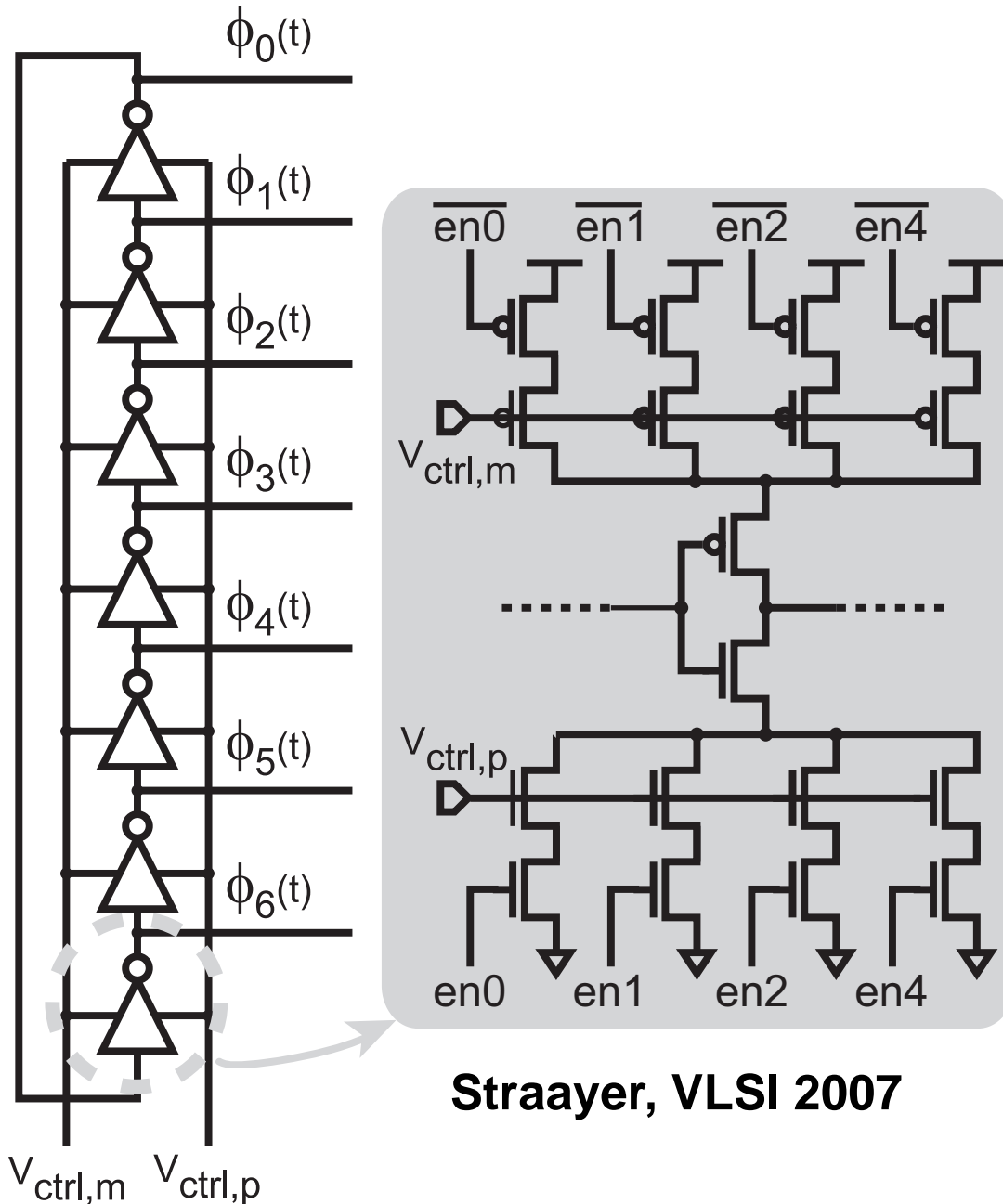

- **15 stage current starved ring-VCO**
  - 7 stage ring-VCO shown for simplicity
  - Pseudo differential control
  - PVT variation accommodated by enable switches on PMOS/NMOS
- **Rail-to-rail VCO output phase signals (VDD to GND)**


# VCO Quantizer Schematic

 

- Phase quantization with sense-amp flip-flop
- Single phase clocking
- Rail-to-rail quantizer output signals (VDD to GND)

Nikolic et al, JSSC 2000

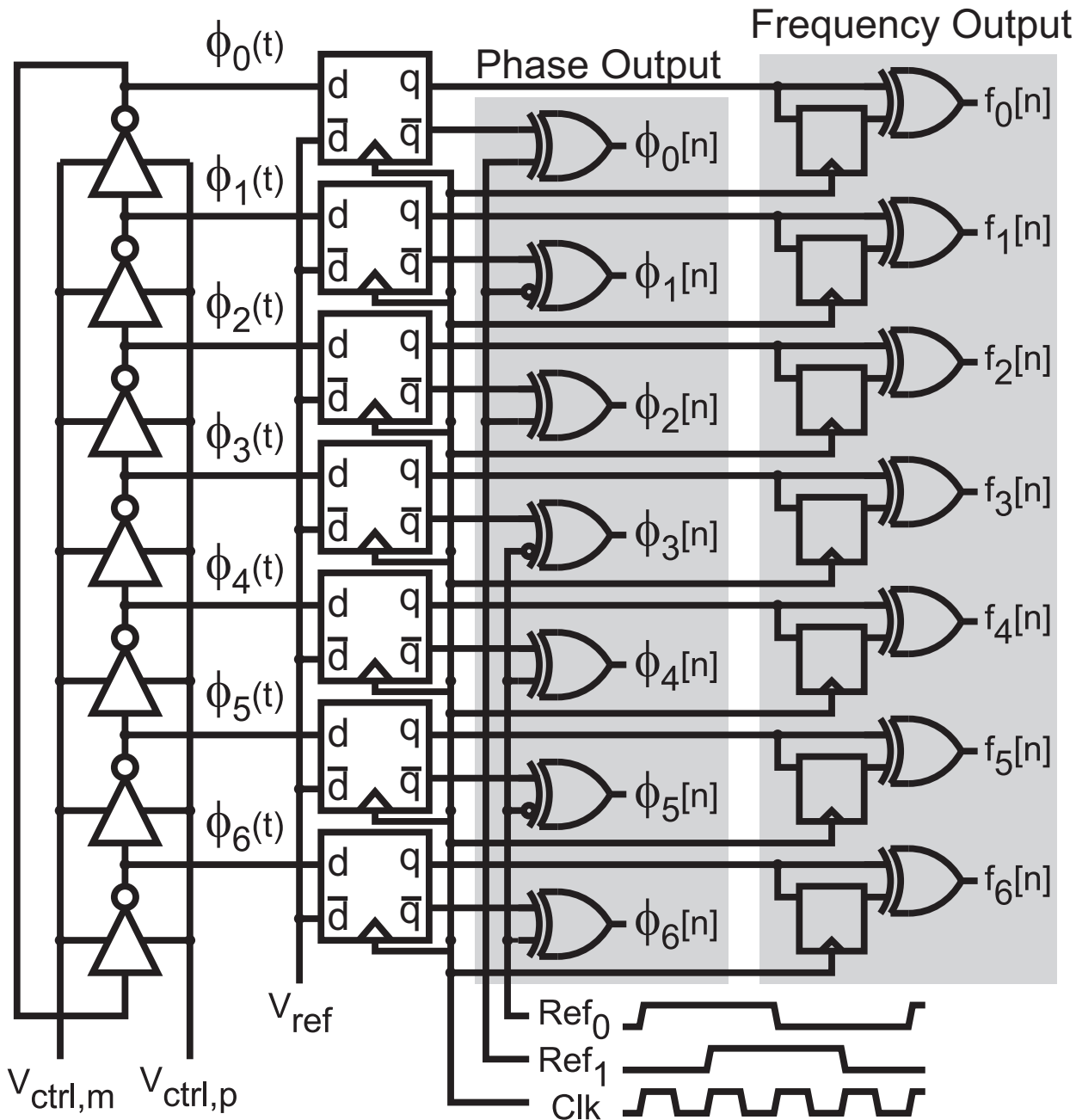
# Phase Quantizer, Phase and Frequency Detector



- **Highly digital implementation**
  - Phase sampled & quantized by SAFF
  - XOR phase and frequency detection with FF and XOR
- **Automatic DWA for frequency detector output code**
  - Must explicitly perform DWA on phase detector output code

# Main Feedback DAC Schematic

(same cell for  $V_{inm}$ )



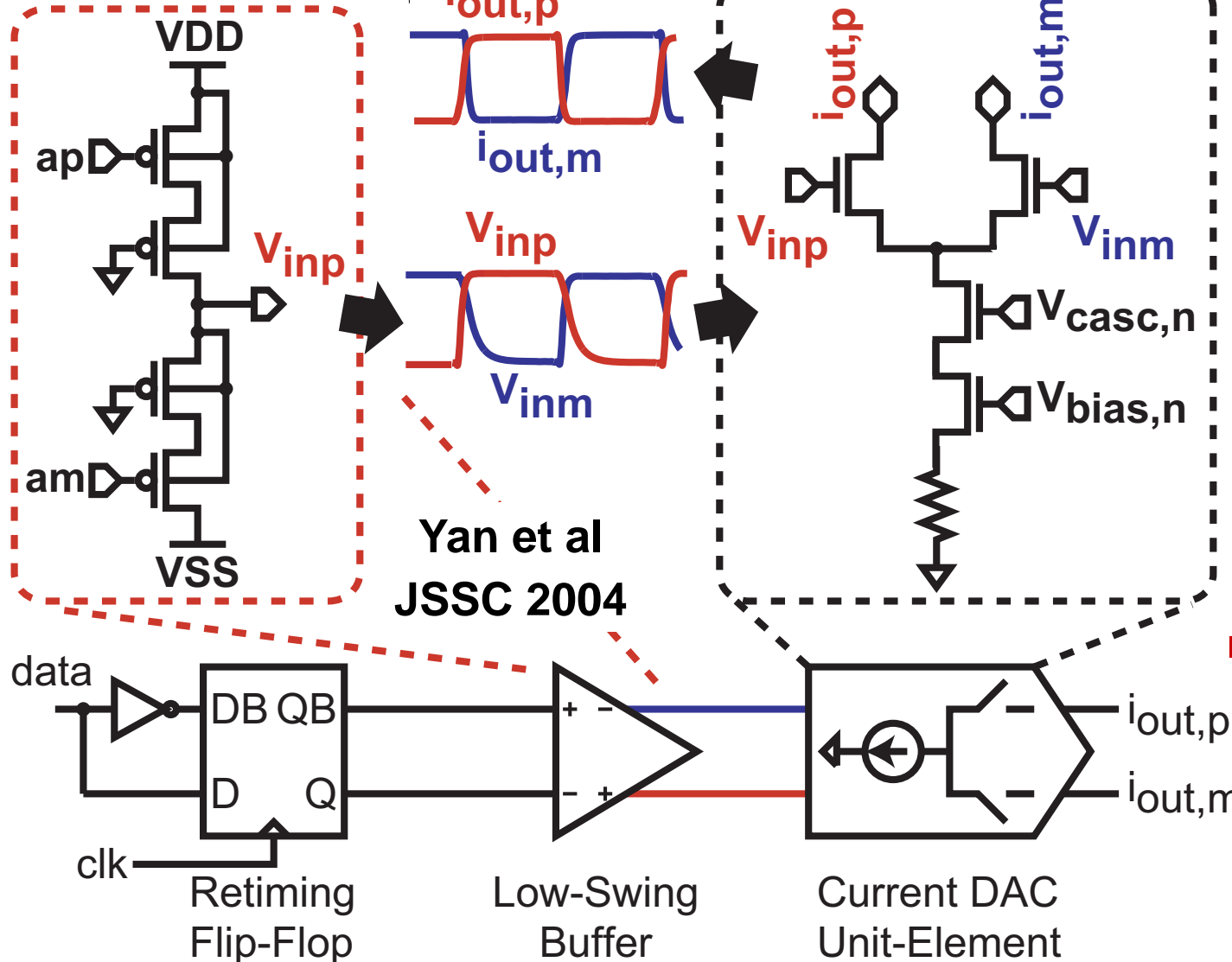


## Low-swing buffers

- Keeps switch devices in saturation
- Fast “on”/Slow “off” reduces glitches at DAC output
- Uses external  $V_{dd}/V_{ss}$


## Resistor degeneration minimizes $1/f$ noise

# Bit-Slice of Minor Loop RZ DAC

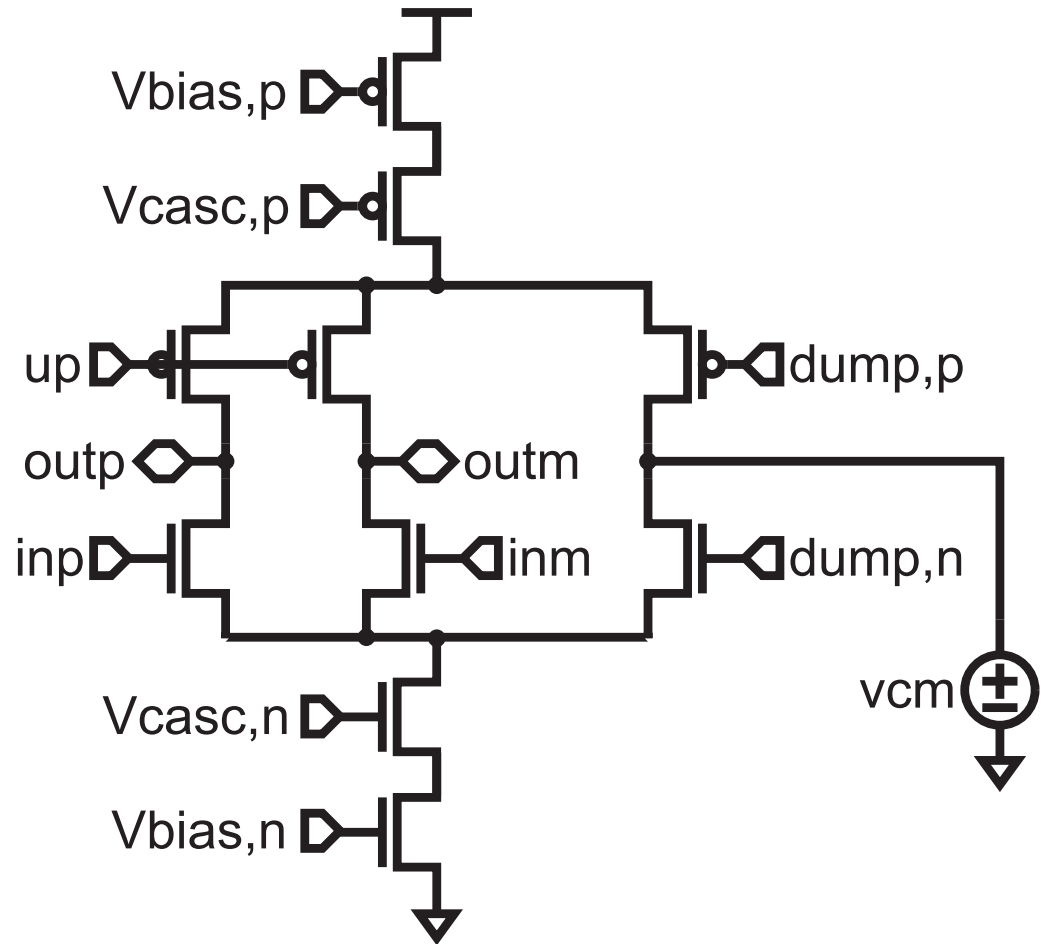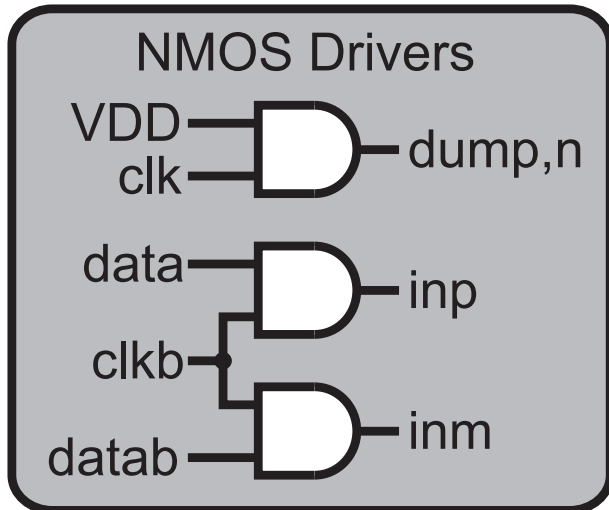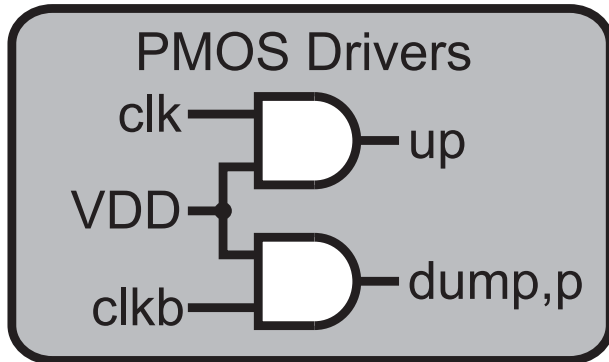

- RZ DAC unit elements transition every sample period
  - Breaks code-dependency of transient mismatch (ISI)
  - Uses full-swing logic signals for switching


# Opamp Schematic

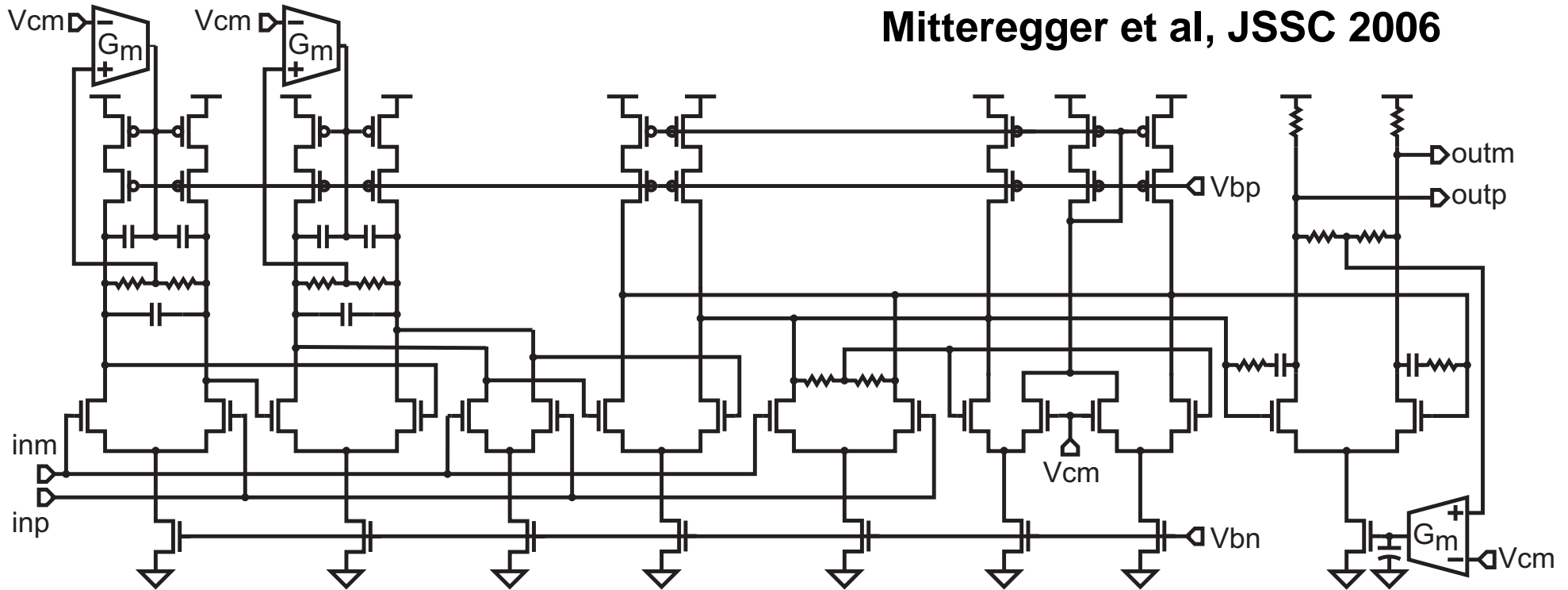

Parameter	Value
DC Gain	63 dB
Unity-Gain Frequency	4.0 GHz
Phase Margin	55°
Input Referred Noise Power (20 MHz BW)	11 $\mu$ V (rms)
Power ( $V_{DD} = 1.5$ V)	22.5 mW

- **Modified nested Miller opamp**
  - 4 cascaded gain stages, 2 feedforward stages
  - Behaves as 2-stage Miller near cross-over frequencies
  - Opamp 1 power is 2X of opamps 2 and 3 (for low noise)

# DEM Architecture (3-bit example)

 


- Achieves low-delay to allow 4-bit DEM at 900 MHz
  - Delay is half a sample period





# Die Photo (0.13u CMOS)

Die photo courtesy of Annie Wang (MTL)

 

- Active area
  - 0.45 mm<sup>2</sup>
- Sampling Freq
  - 900 MHz
- Input BW
  - 20 MHz
- Supply Voltage
  - 1.5 V
- Analog Power
  - 69 mW
- Digital Power
  - 18 mW


# Measured Results

 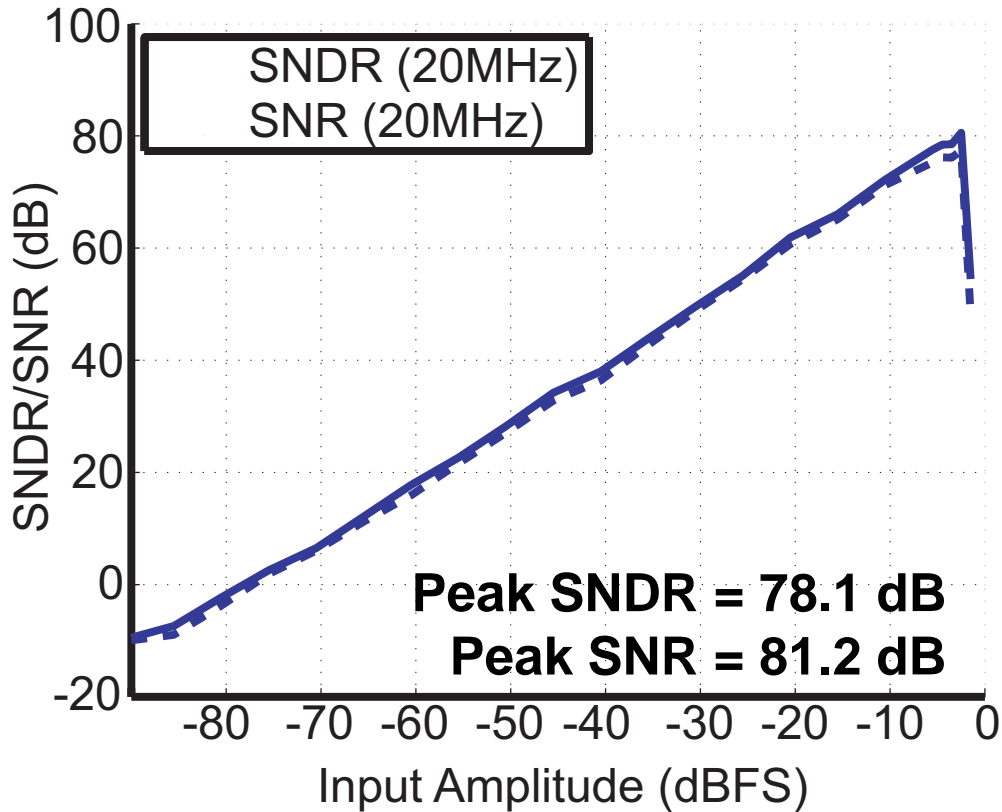

- **78 dB Peak SNDR performance in 20 MHz**
  - **Bottleneck: transient mismatch from main feedback DAC**
- **Architecture robust to VCO  $K_v$  non-linearity**

**Figure of Merit: 330 fJ/Conv with 78 dB SNDR**


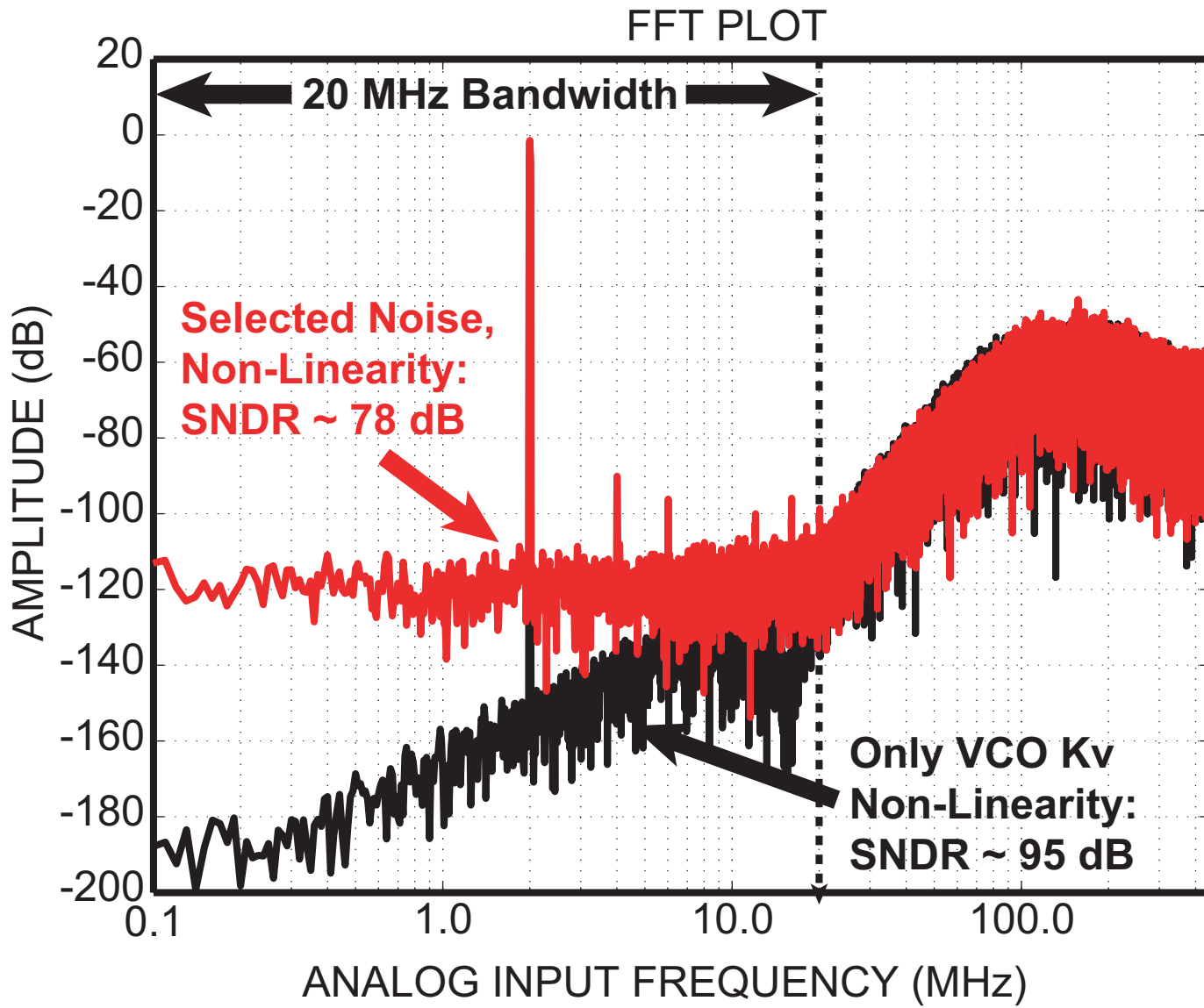
# Behavioral Model Reveals Key Performance Issue



- Amplifier nonlinearity degrades SNDR to 81 dB
- DAC transient mismatch degrades SNDR to 78 dB
  - DEM does not help this
  - Could be improved with dual RZ structure

**Transient DAC mismatch is likely the key bottleneck**

 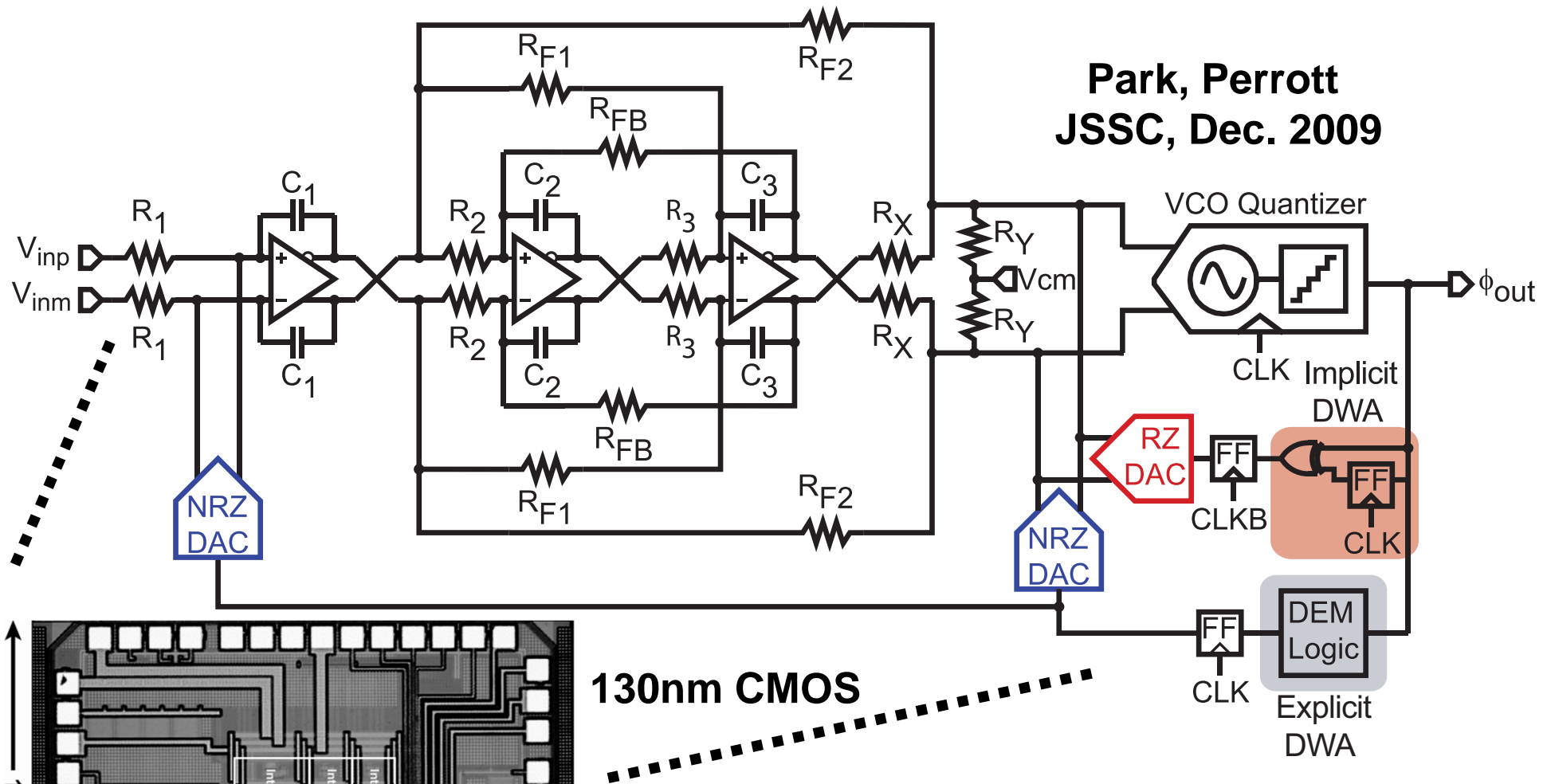
# Summary of Fourth Order CT Delta-Sigma ADC



130nm CMOS

- Peak SNDR of 78 dB with 20 MHz bandwidth
- Figure of merit: 330 fJ/conv


# Consider Time-to-Digital Conversion

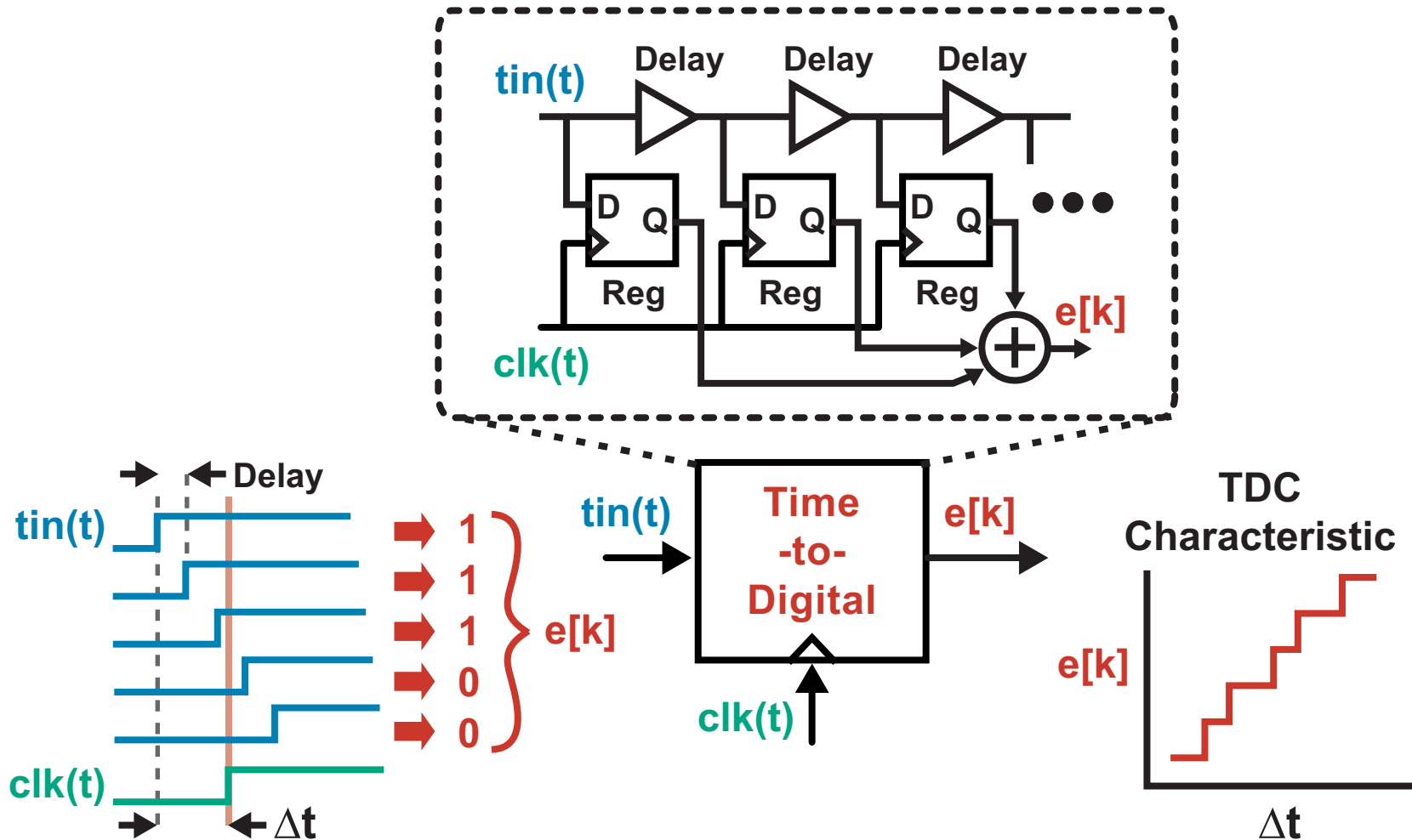

- Quantization in time achieved with purely digital gates
  - Easy implementation, resolution improving with Moore's law

How can we leverage this for quantizing an analog voltage?

# Adding Voltage-to-Time Conversion

 


Naraghi, Courcy, Flynn, *ISSCC* 2009

- **Analog voltage is converted into edge times**
  - Time-to-digital converter then turns the edge times into digitized values
- **Key issues**
  - Non-uniform sampling
  - Noise, nonlinearity

**Is there a simple implementation for the Voltage-to-Time Converter?**





# A Highly Digital Implementation

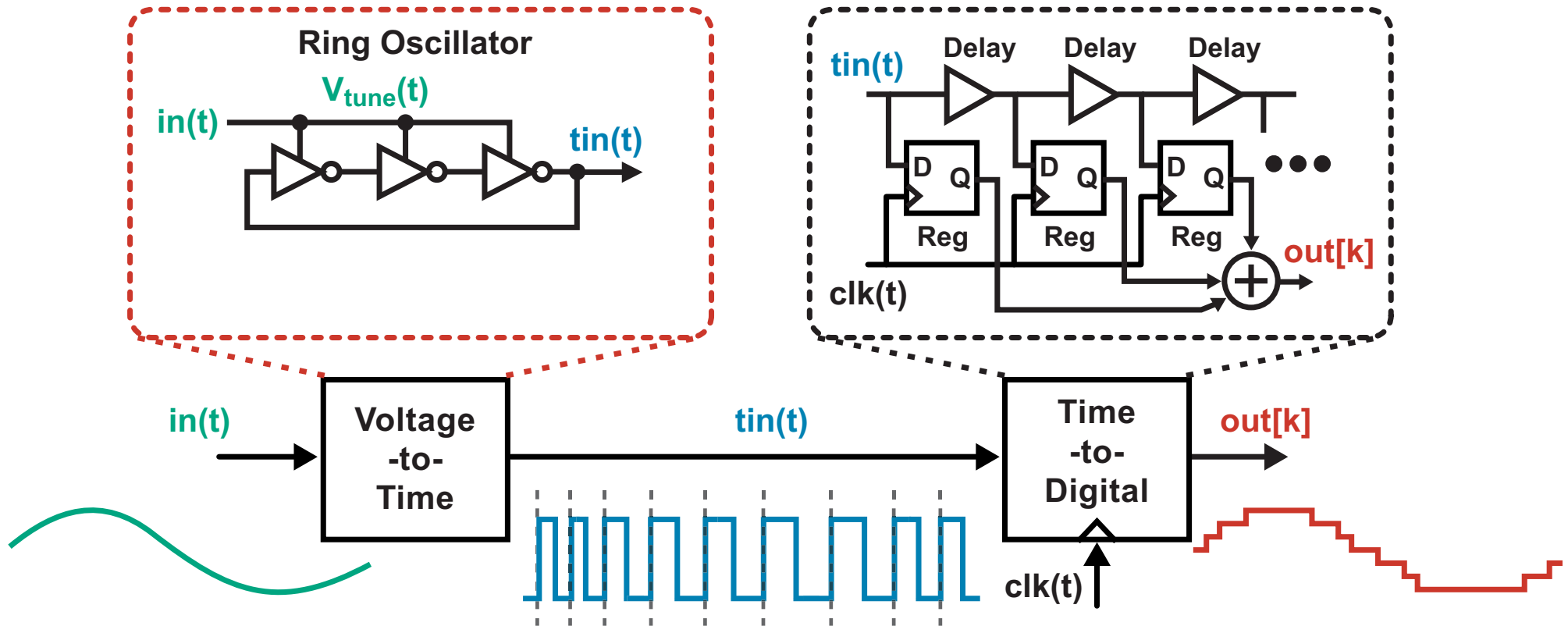

- A voltage-controlled ring oscillator offers a simple voltage-to-time structure
  - Non-uniform sampling is still an issue

We can further simplify this implementation and lower the impact of non-uniform sampling

    
# Making Use of the Ring Oscillator Delay Cells



- Utilize all ring oscillator outputs and remove TDC delays
  - Simpler implementation
- TDC output now samples/quantizes phase state of oscillator




# Improved Non-Uniform Sampling Behavior

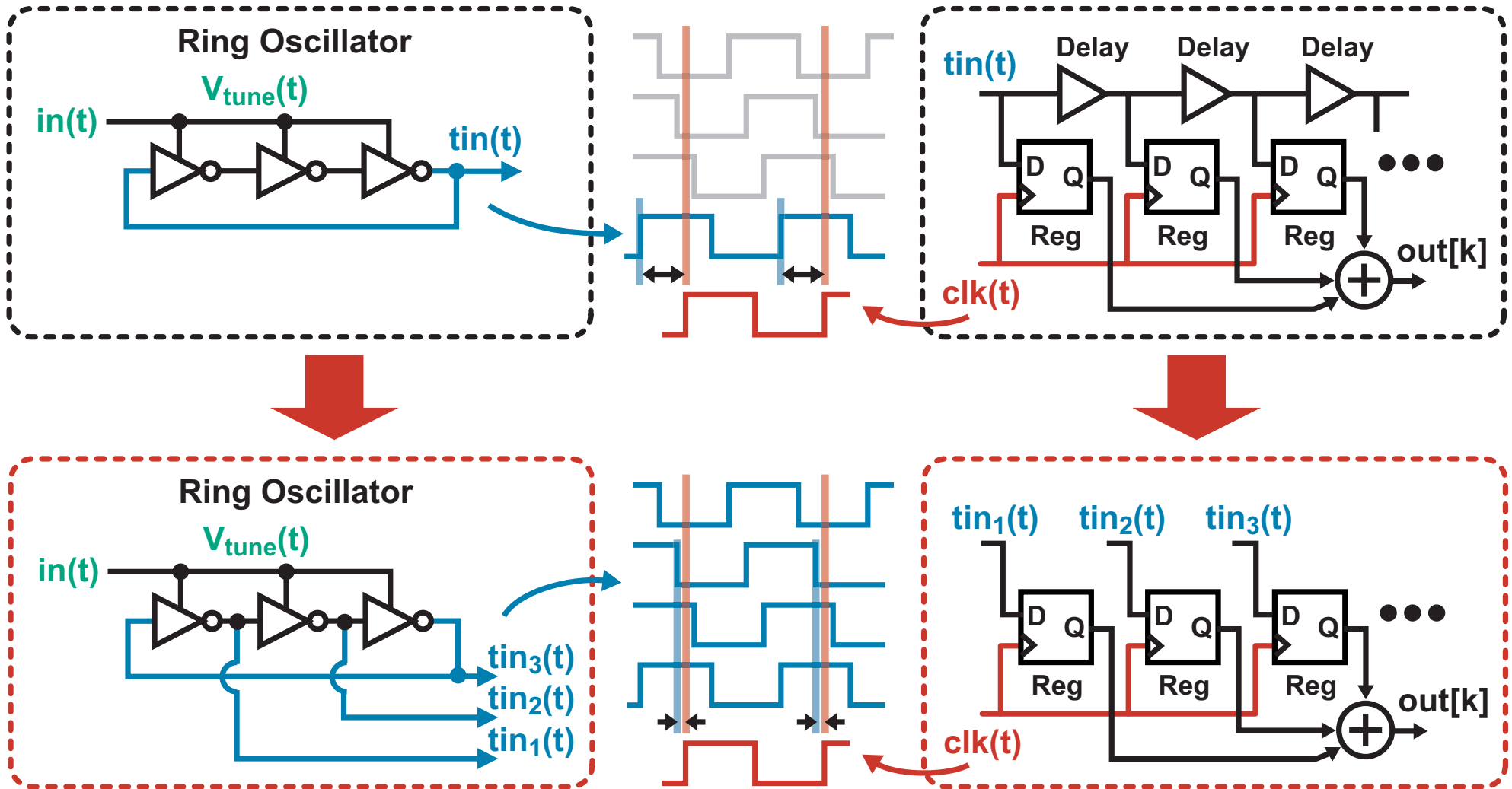

- Oscillator edges correspond to a sample window of the input
- Sampling the oscillator phase state yields sample windows that are much more closely aligned to the TDC clk

 
## Key Observation

- The VCO-Based ADC provides an excellent vehicle for using a conventional TDC for analog-to-digital conversion
  - Efficiently combines voltage-to-time and time-to-digital conversion
  - Minimizes issue of non-uniform sampling



VCO-based ADCs are very efficient “time-based” circuits


# Some Other VCO-based ADC Approaches

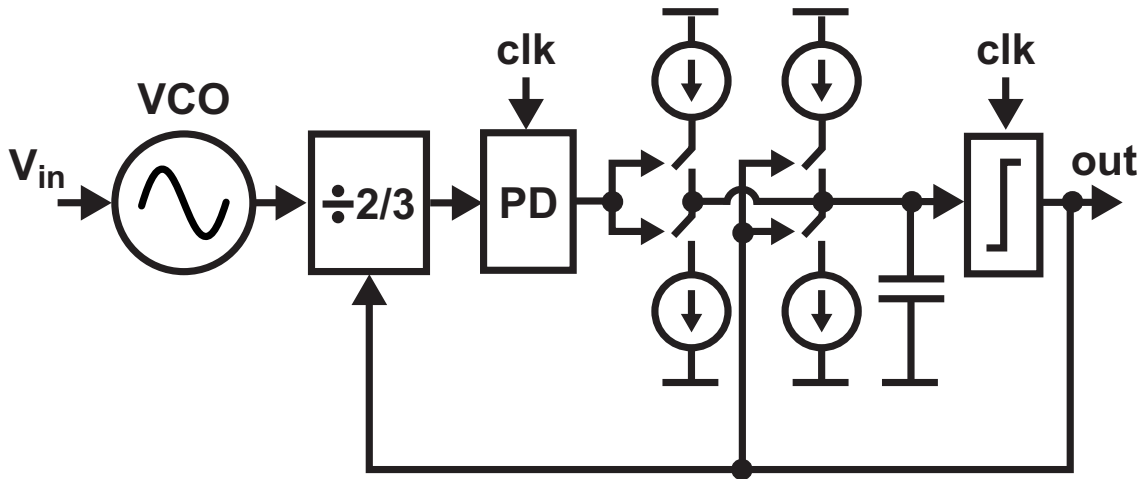


Park, Perrott  
ISCAS 2009

Yoon, Kim, Jang, Cho  
TCAS1 Dec 2008

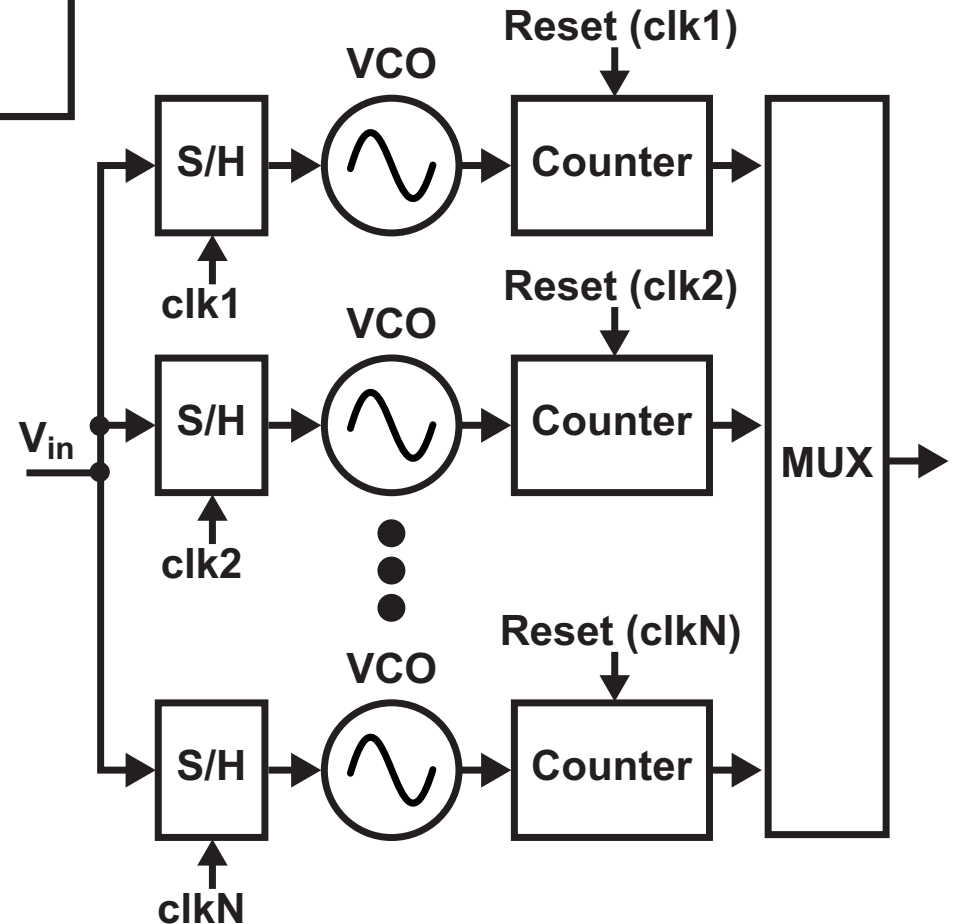- Increase noise shaping to second order by adding frequency divider and charge pumps
- Use interleaved VCO quantizers to create bandpass ADC




# Recent Performance of VCO-Based ADCs

 

**Approaching 100fJ/conv-step at 78dB SNDR**
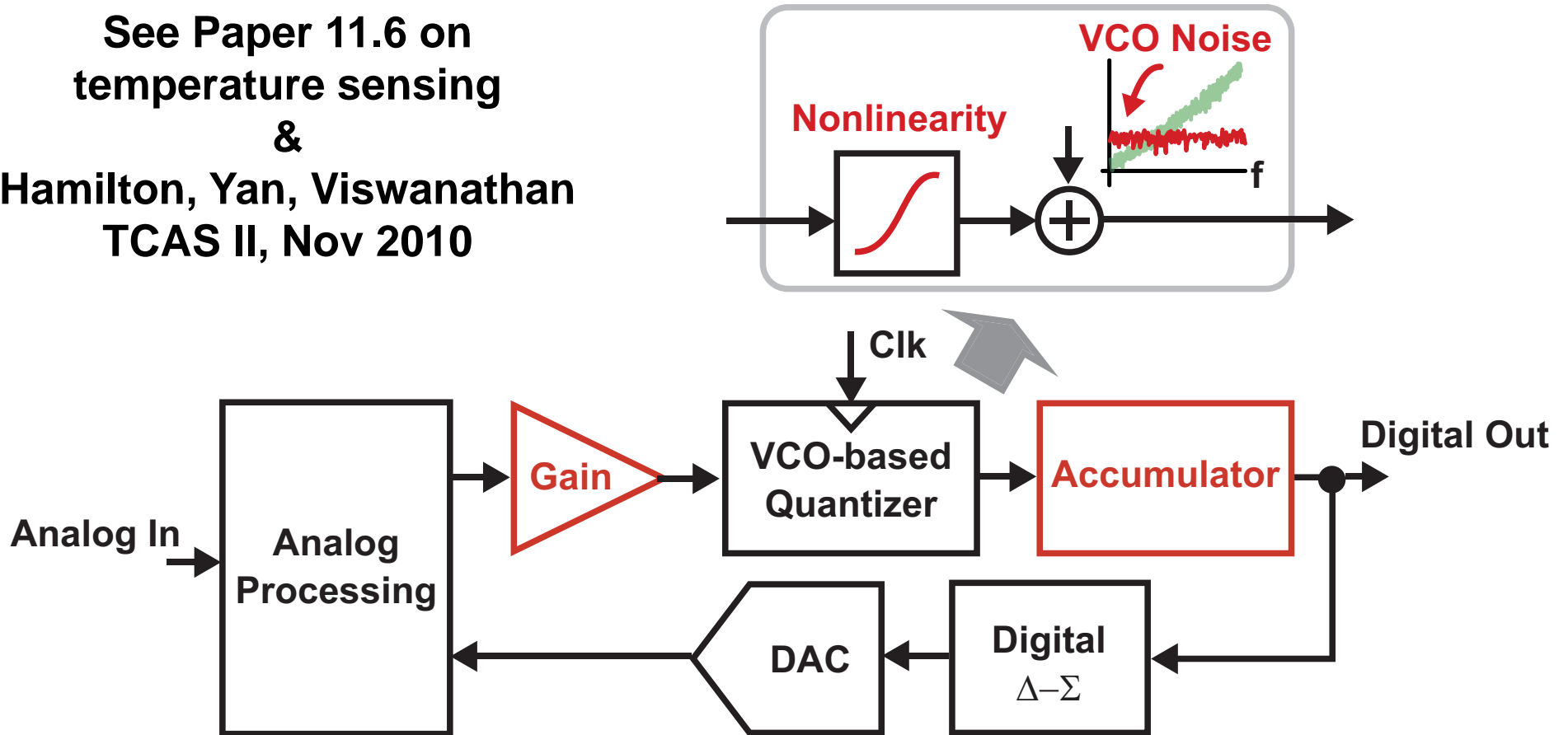
# A Simple Interface Between Analog and Digital

See Paper 11.6 on  
temperature sensing  
&  
Hamilton, Yan, Viswanathan  
TCAS II, Nov 2010



- **Accumulator reduces impact of nonlinearity**
- **Gain reduces impact of VCO phase noise**

**Plays well to the strengths and weaknesses of  
VCO-based quantizers**

## ***Conclusion on VCO-Based Quantizers***

---

- **Leverage Moore's law**
  - **Consist of ring oscillator(s) and digital logic**
  - **Improved speed, power, area with advanced CMOS**
- **Are relatively easy to design**
  - **First order shaping of quantization noise and mismatch**
  - **Infinite DC gain when used as an integrator**
- **Have shortcomings that can be overcome**
  - **Nonlinearity: utilize calibration or feedback**
  - **VCO phase noise: utilize feedback**

**Performance is now at state of the art at 78dB SNDR  
and improving steadily**