
Continuous-time $\Delta\Sigma$ Modulators with Improved Linearity and Reduced Clock Jitter Sensitivity using the SCRZ DAC

Shanthi Pavan

Indian Institute of Technology, Madras

Chennai 600 036

-
- Work of my M.S students
 - Timir Nandi, now at TI, India
 - Karthikeya Boominathan
 - Part of this presented at
 - CICC 2012
-

Outline

- Introduction
 - Limitations of conventional DAC pulses
 - Switched-C Return-to-Zero Principle
 - Modulator Architecture
 - Circuit Design
 - Measurement Results
 - Conclusion
-

Motivation

- Continuous-time DSMs
 - Resistive input impedance
 - Relaxed opamp gain requirements
 - Most high performance CTDSMs
 - Multibit loops
 - Focus of this research
 - Can we do better with single-bit loops ?
 - Case study
 - 14 bit ENOB, 2 MHz Bandwidth, 0.18 μ m CMOS
-

Multibit versus Single-bit Modulators

Design Targets

Dynamic Range	86dB (14 ENOB)	
Bandwidth	2 MHz	
Order	4	
Quantizer	1 bit	4 bit
Out of Band Gain		
OSR Needed		
Sampling Rate		


Design Targets

Dynamic Range	86dB (14 ENOB)	
Bandwidth	2 MHz	
Order	4	
Quantizer	1 bit	4 bit
Out of Band Gain	1.5	
OSR Needed	64	
Sampling Rate	256 MHz	

Design Targets

Dynamic Range	86dB (14 ENOB)	
Bandwidth	2 MHz	
Order	4	
Quantizer	1 bit	4 bit
Out of Band Gain	1.5	2.5
OSR Needed	64	20
Sampling Rate	256 MHz	80 MHz


ADC : 1 bit versus 4 bit

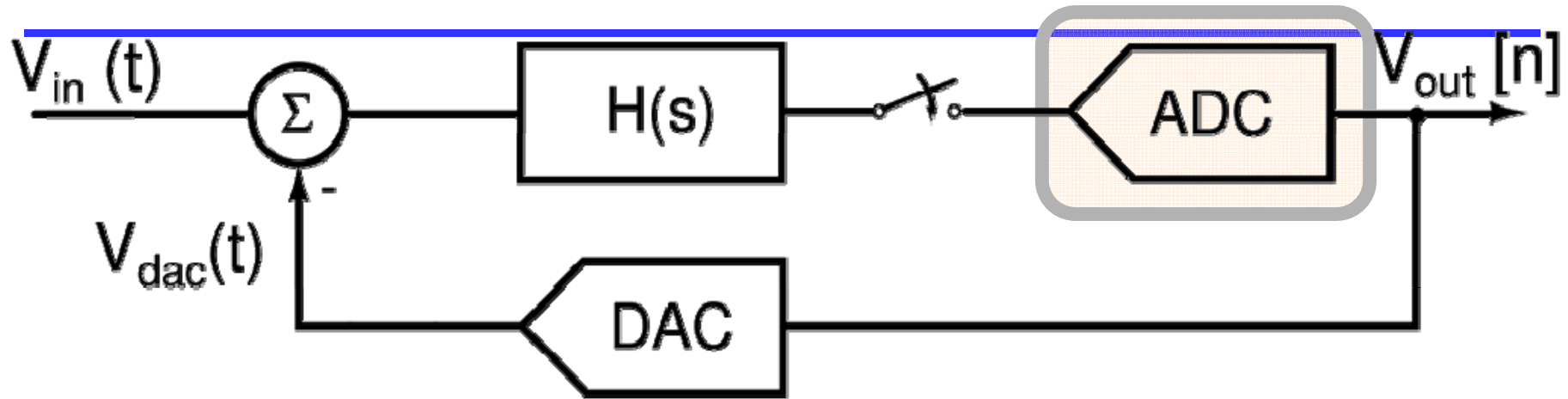

■ 4 bit ADC

- 15x more comparators @ $1/3^{\text{rd}}$ speed
 - 5x more ADC power, 15x more area
 - 15x loop filter & clock path loading
-


DAC : 1 bit versus 4 bit

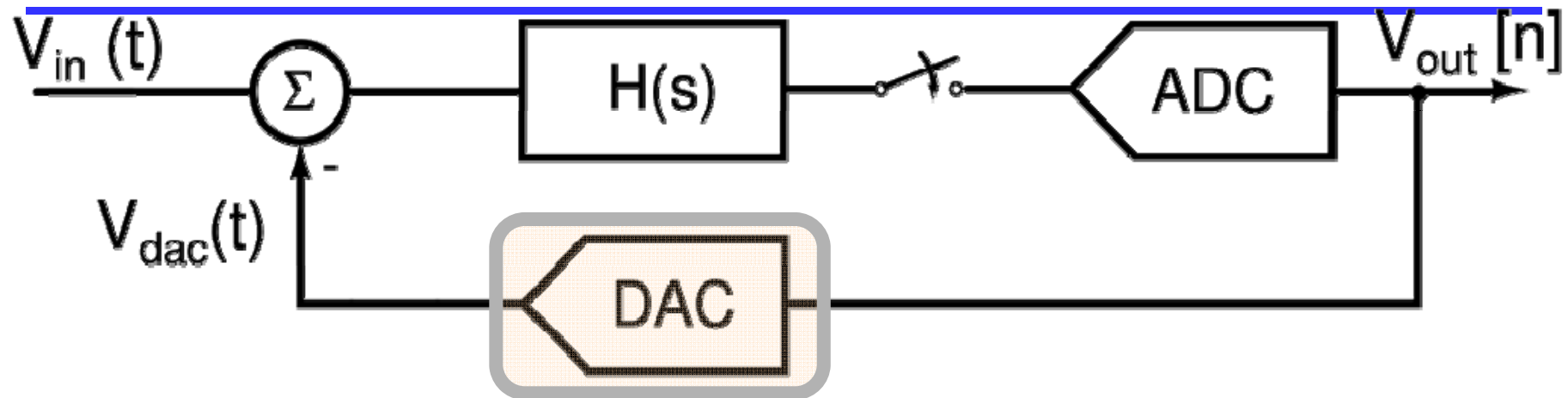

- 4 bit DAC

- Needs Dynamic Element Matching
 - DEM adds excess delay & power
 - Not very effective @ low OSR
-

DAC : 1 bit versus 4 bit


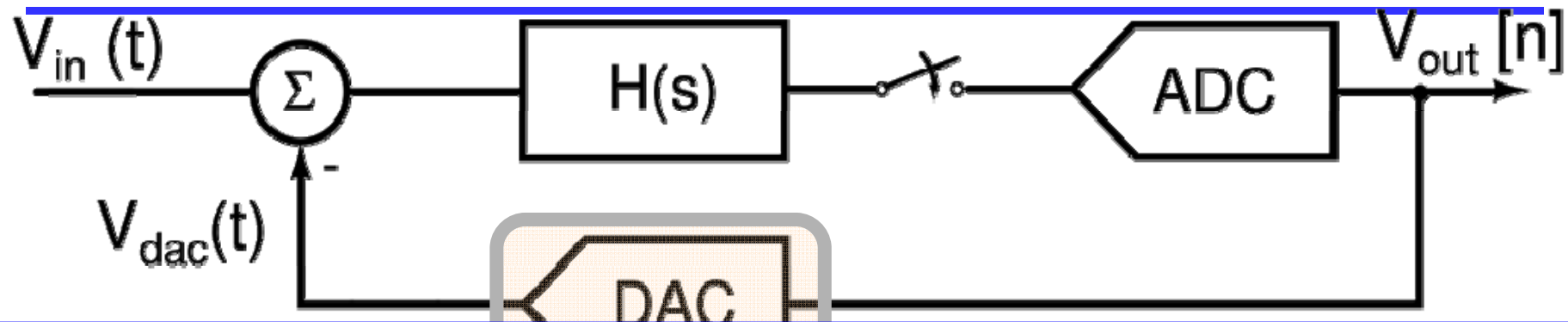


A single bit quantizer consumes
lesser power
though it operates at 3x the speed


Complex logic



Modeling Clock Jitter

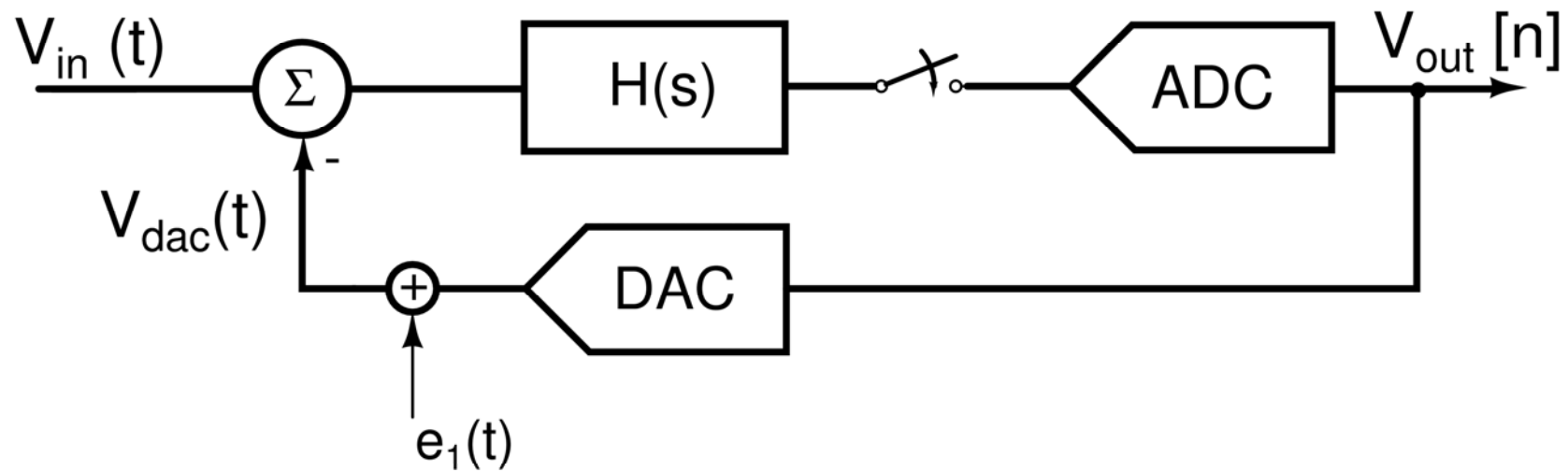 


Clock Jitter Comparison

 


A 4-bit modulator can tolerate 15 times more RMS white jitter compared to a single bit design

 
$$e[n] \approx (V_{out}[n] - V_{out}[n - 1]) \frac{\Delta t_n}{T_s}$$



Loop Filter Linearity

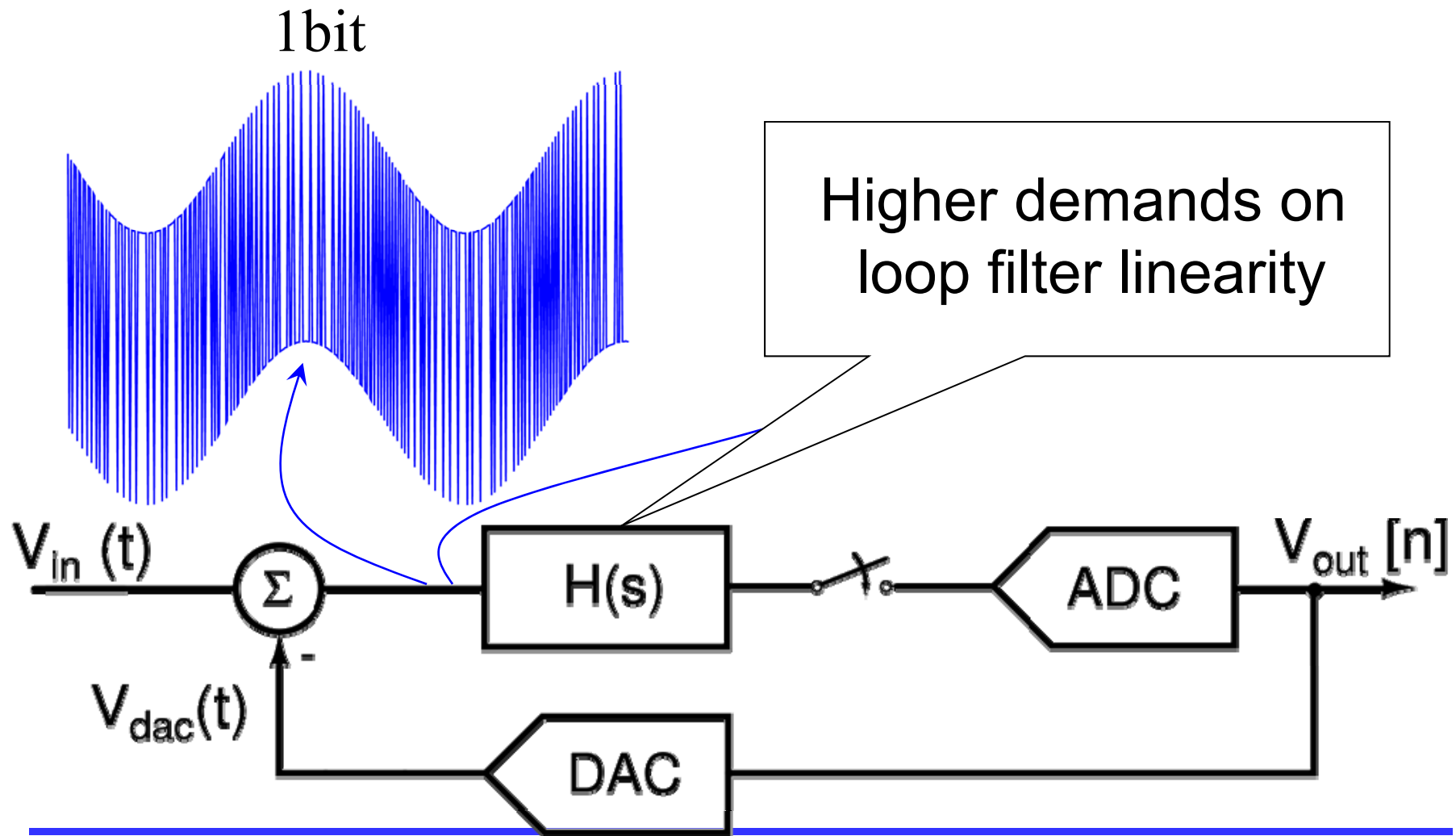

Choice of Quantizer

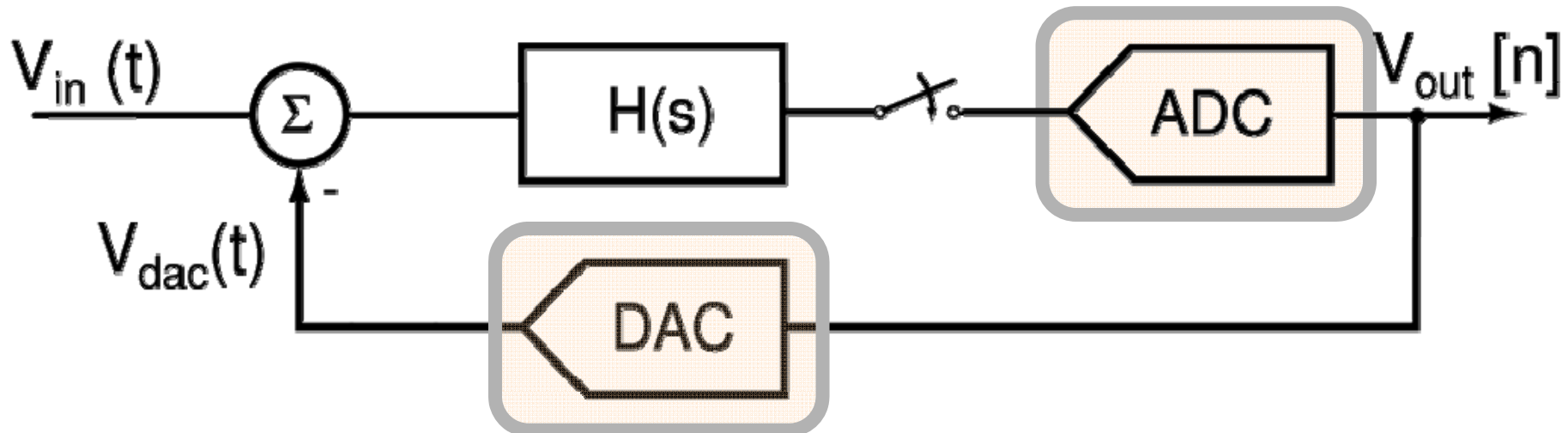

- Single bit quantizer

- Lower power ADC


- No DEM needed

- Sensitive to clock jitter

- Loop filter needs to be extremely linear


Try to fix this

DAC Pulse Shapes : NRZ

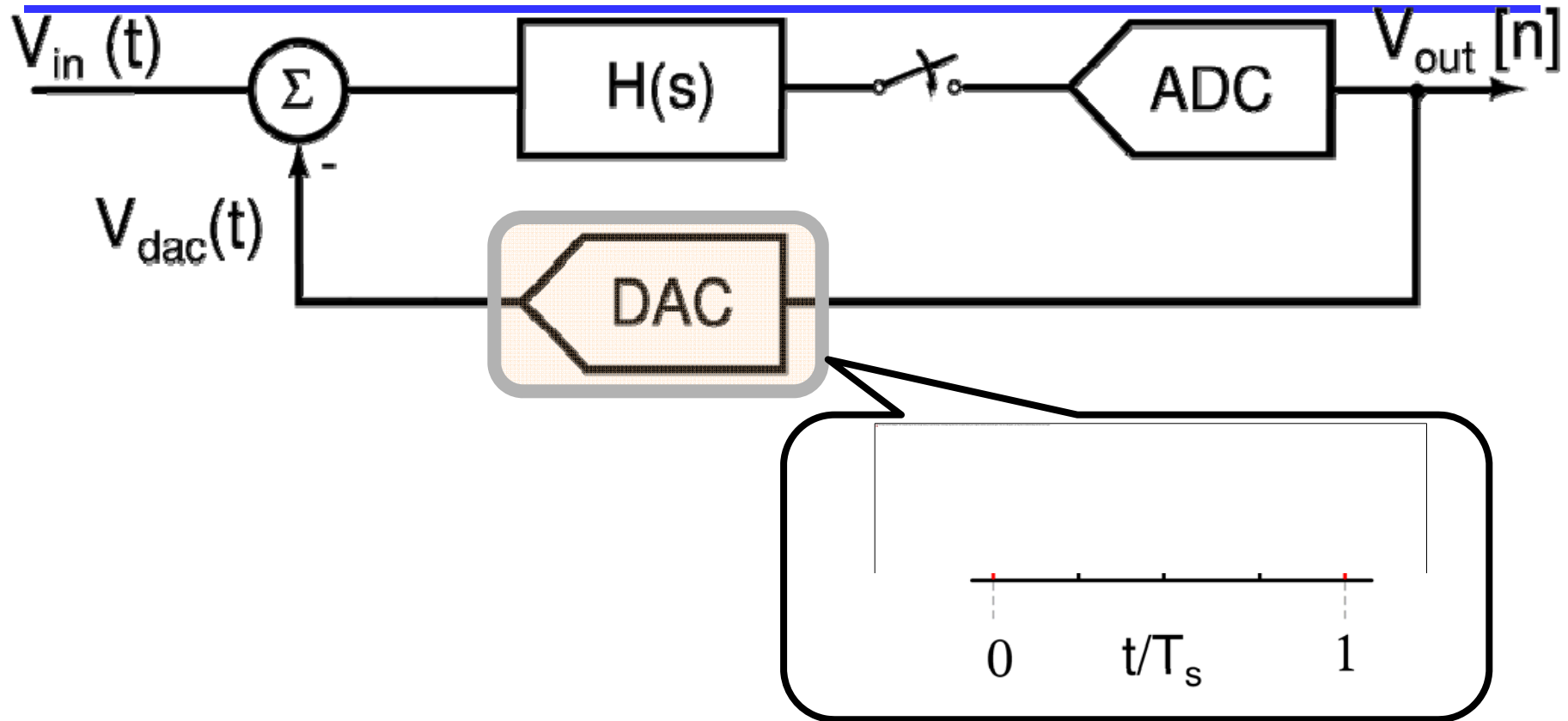

Inherently nonlinear (rise-fall asymmetry)


DAC Pulse Shapes : NRZ

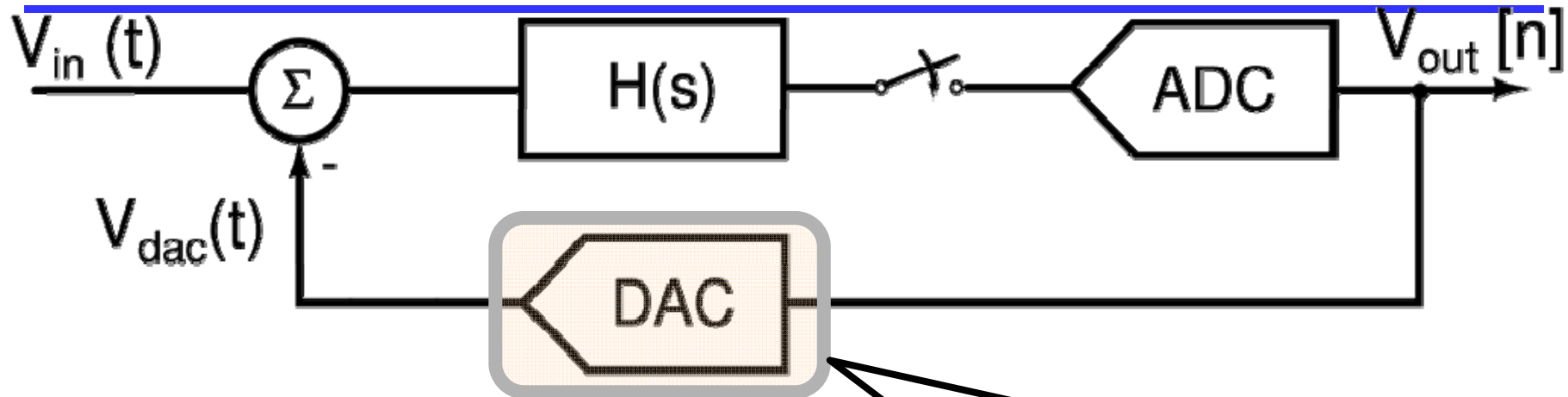


$$\frac{T_{rise} - T_{fall}}{T_s} = 1\%$$

$$HD_2 \approx 55 \text{ dB!}$$

 
$$HD_2 \approx 90 \text{ dB (diff.operation)}$$





DAC Pulse Shapes : NRZ


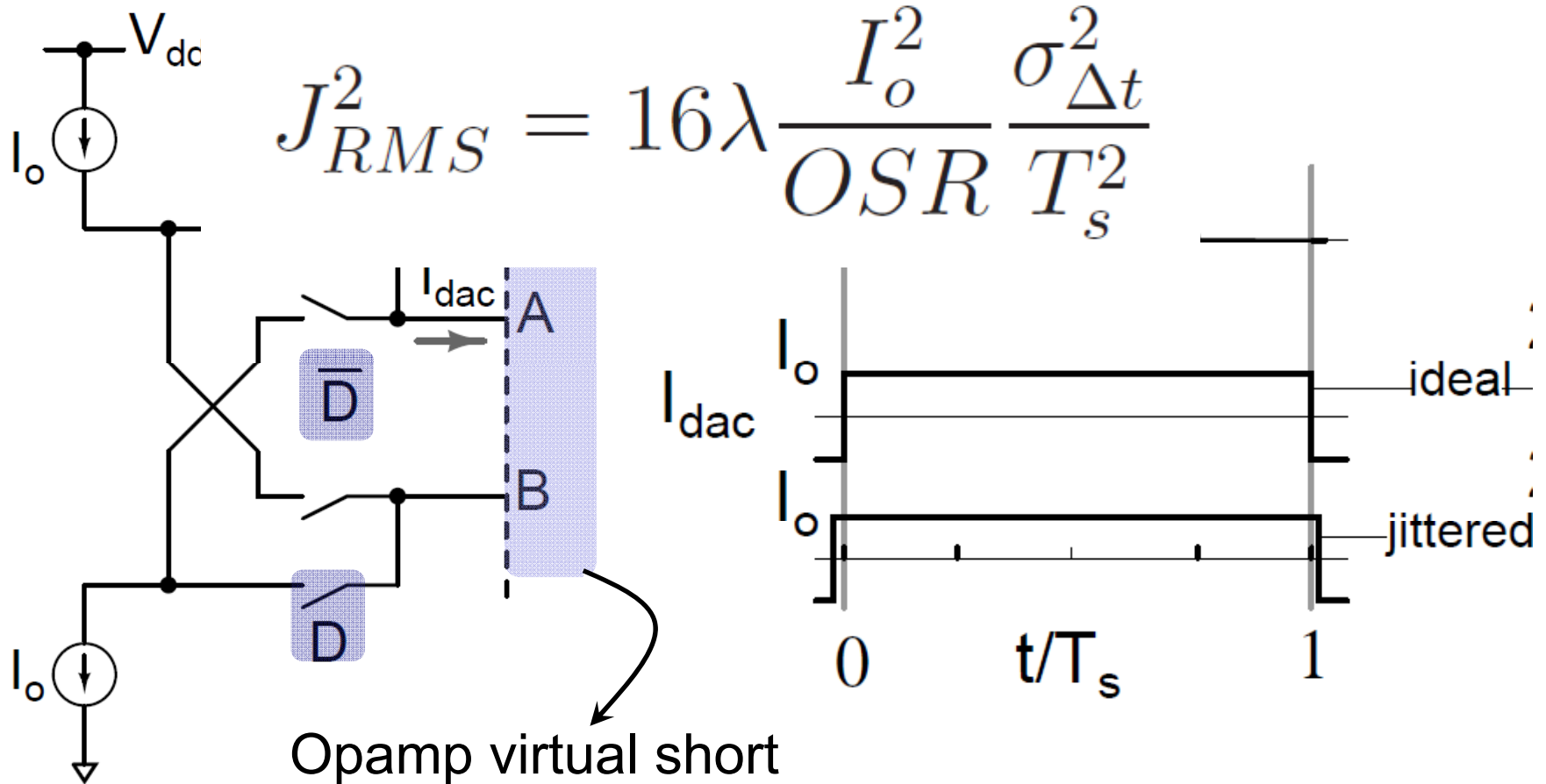


DAC Pulse Shapes : RZ

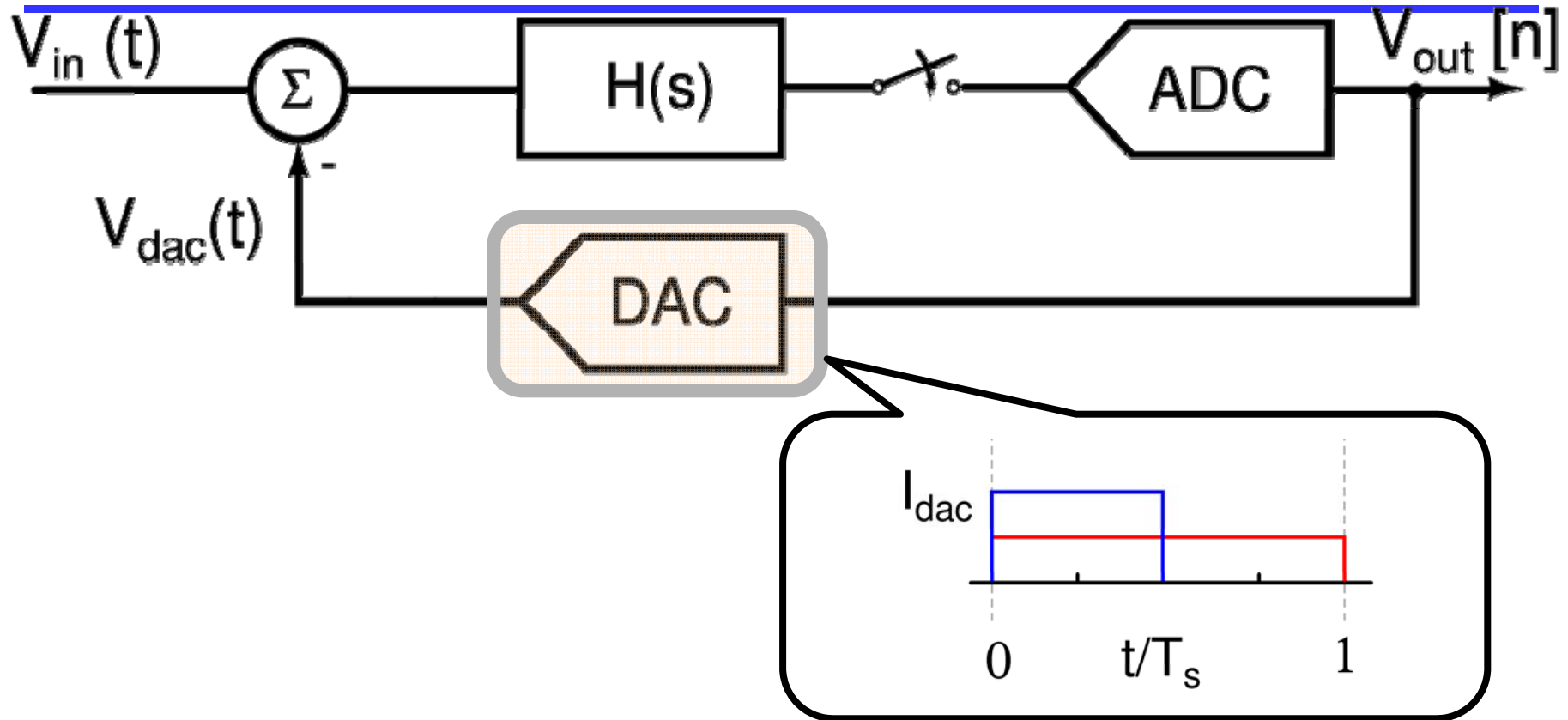


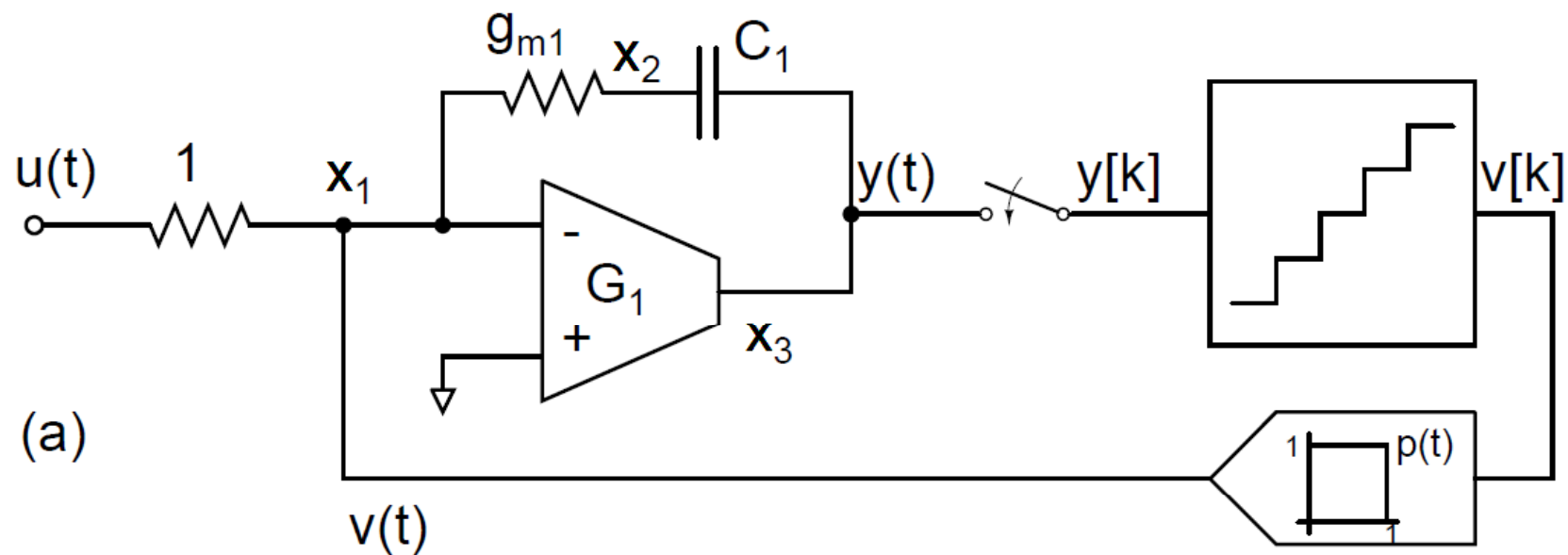 Digression : Weak Nonlinearities in CTDSMs



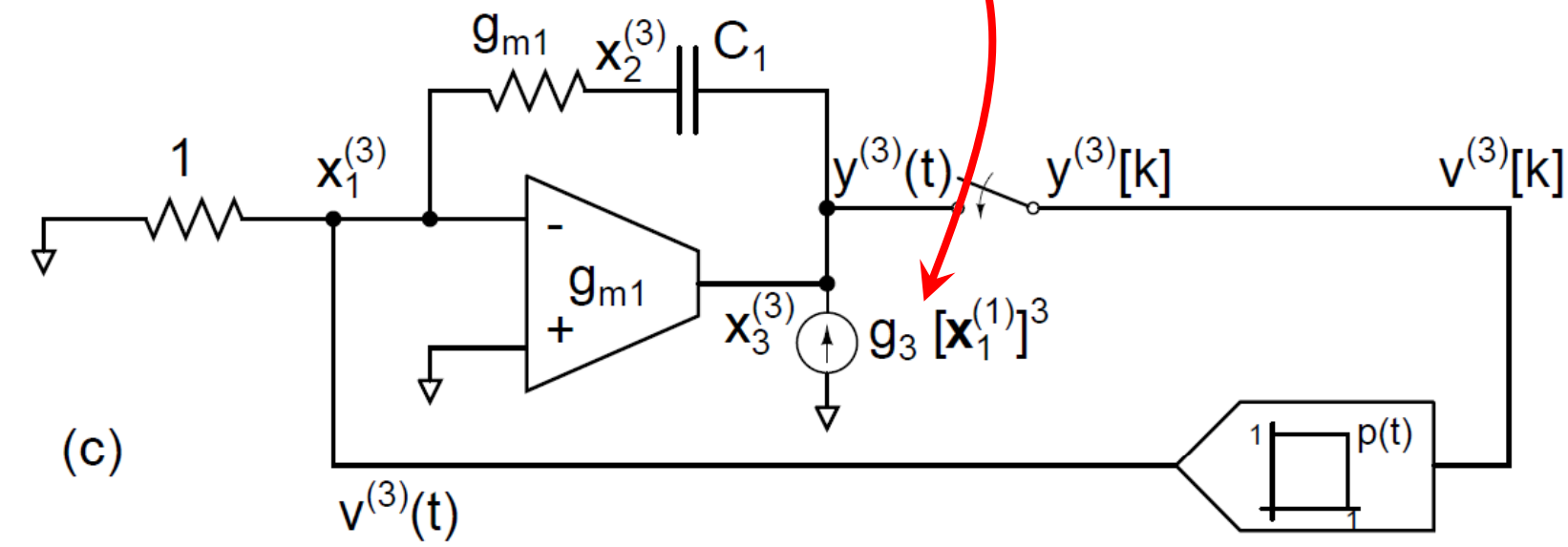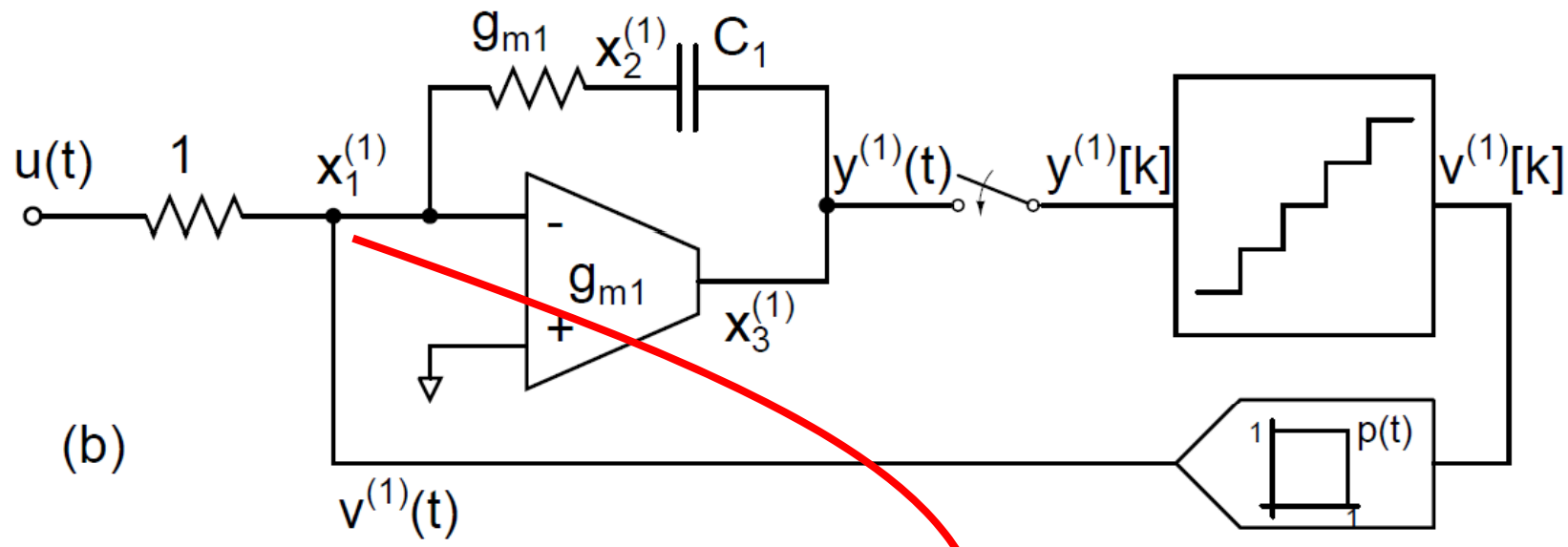



RZ DAC : Linearity

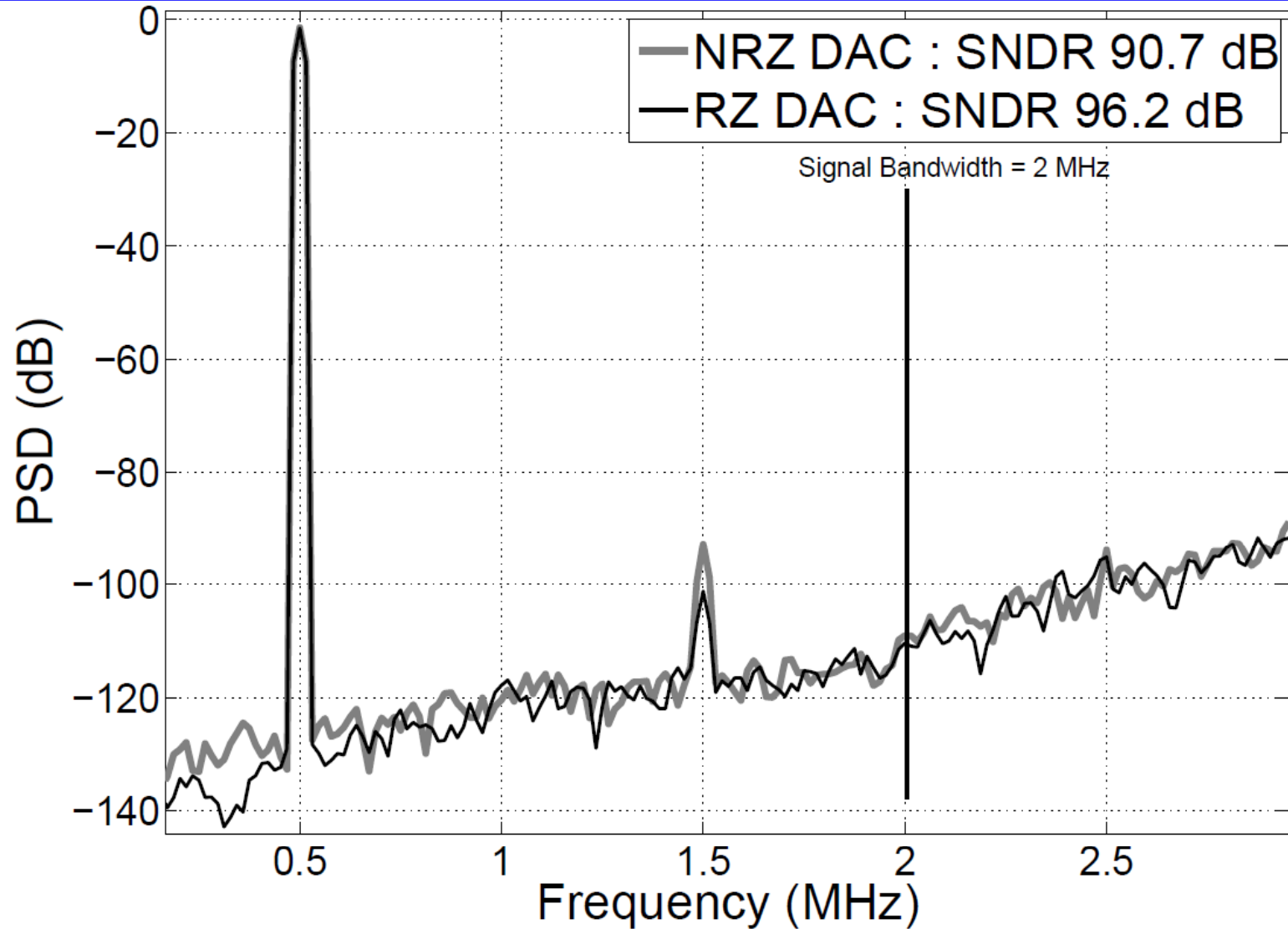


RZ DAC : Jitter

$$J_{RMS}^2 = 32 \frac{I_o^2}{OSR} \frac{\sigma_{\Delta t}^2}{T_s^2}$$

4.5 dB worse than an NRZ DAC

 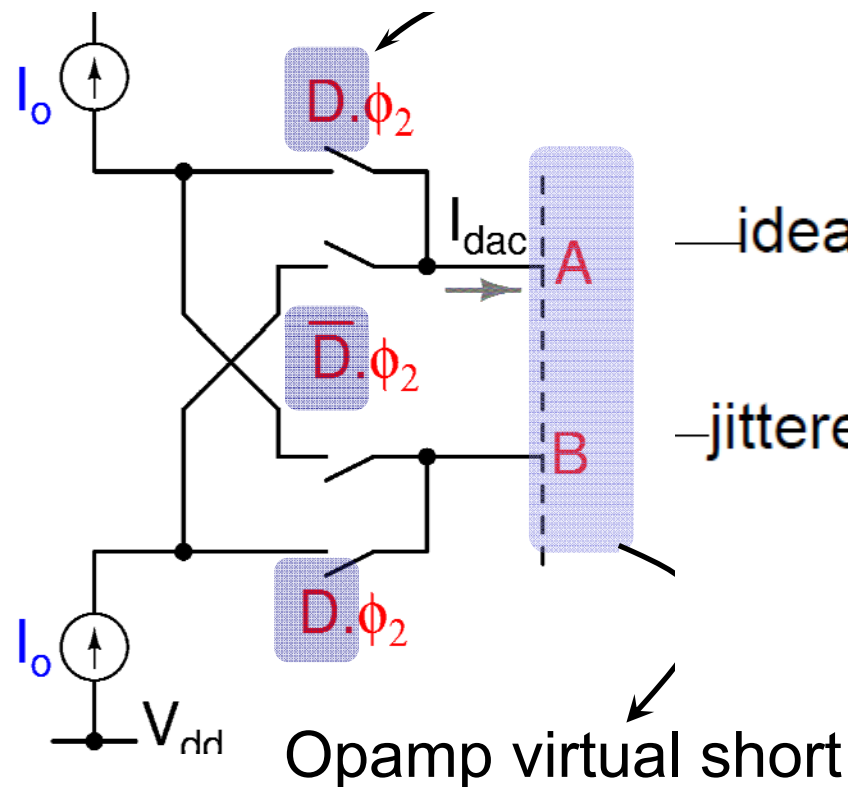


DAC Pulse Shapes : RZ

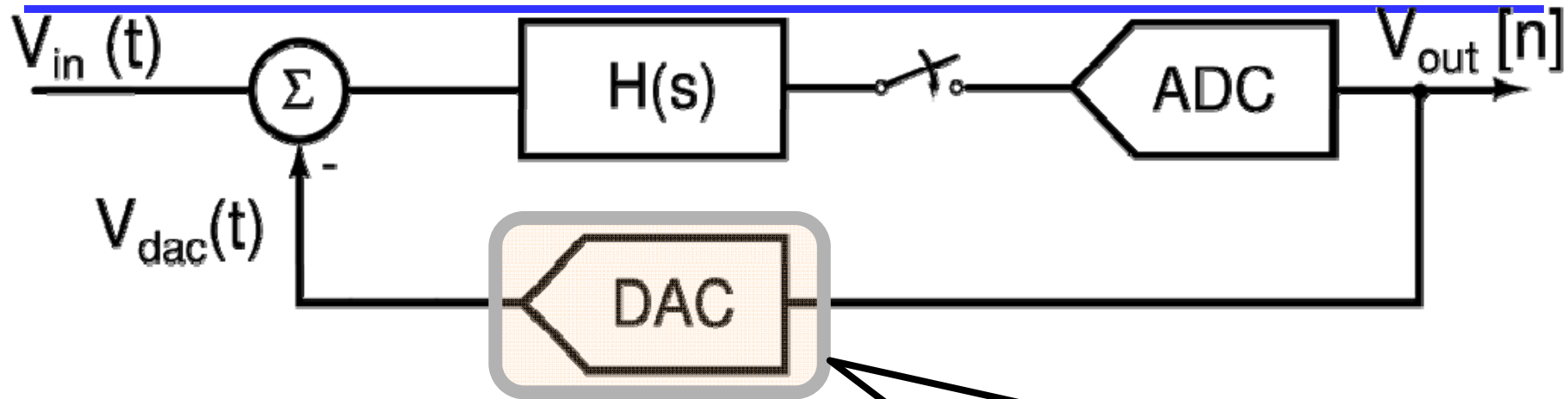



Excellent linearity

Terrible for jitter !

 


SC DAC

 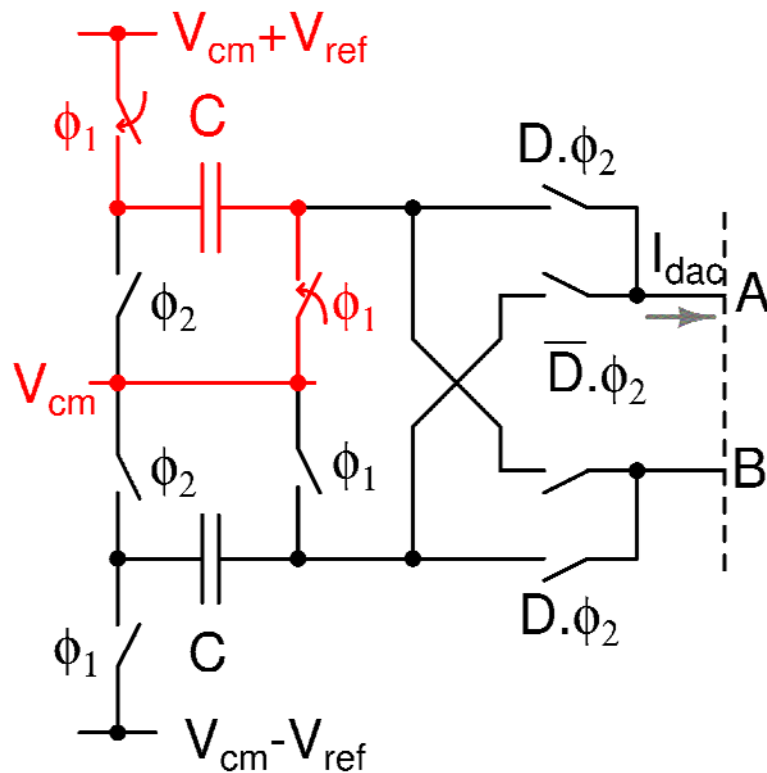- Capacitors are charged to $\pm V_{\text{ref}}$ during Φ_1
- They are discharged into the loopfilter during Φ_2
- Charge transferred = $\pm CV_{\text{ref}}$



SC DAC


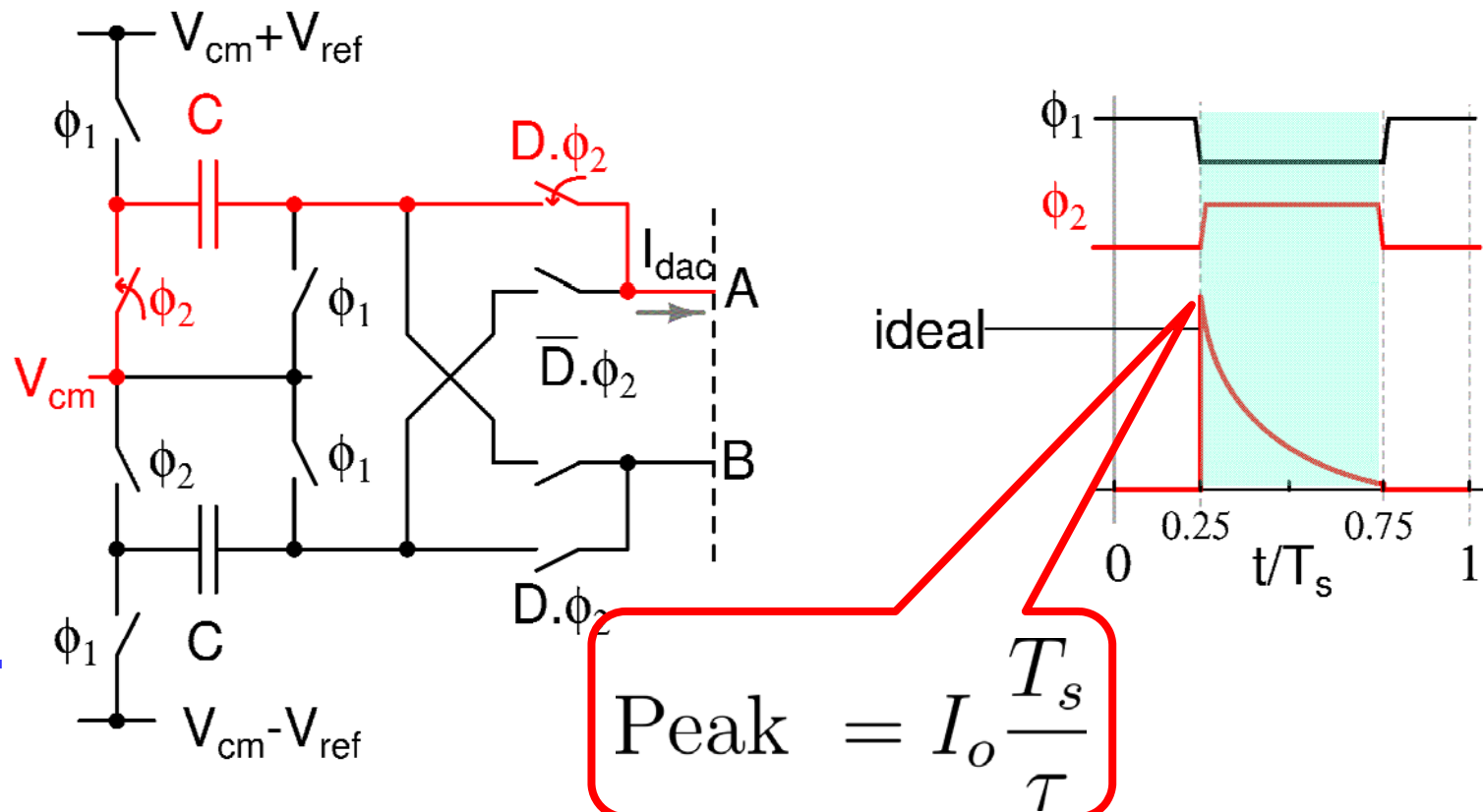
- Capacitors are charged to $\pm V_{\text{ref}}$ during Φ_1
- They are discharged into the loopfilter during Φ_2
- Charge transferred = $\pm CV_{\text{ref}}$



SC DAC with Jitter


- Transfers most of the charge in a short period
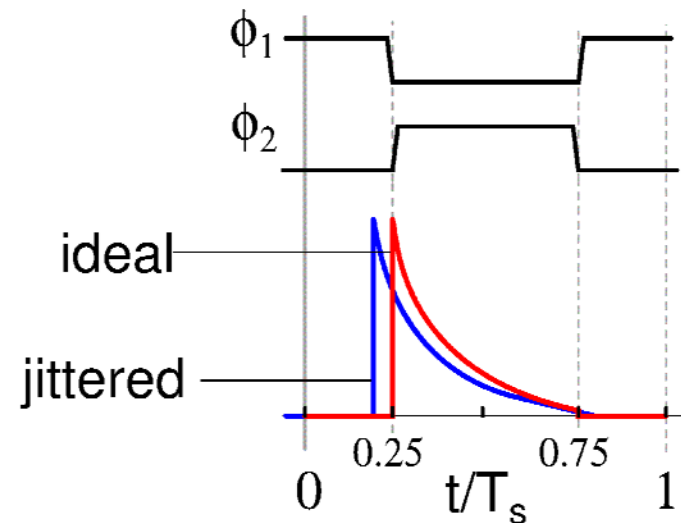 
$$J_{RMS}^2 = 8 \frac{I_o^2}{OSR} \left(\frac{T_s}{\tau} \right)^2 \exp \left(-\frac{T_s}{\tau} \right) \frac{\sigma_{\Delta t}^2}{T_s^2}$$




SC DAC

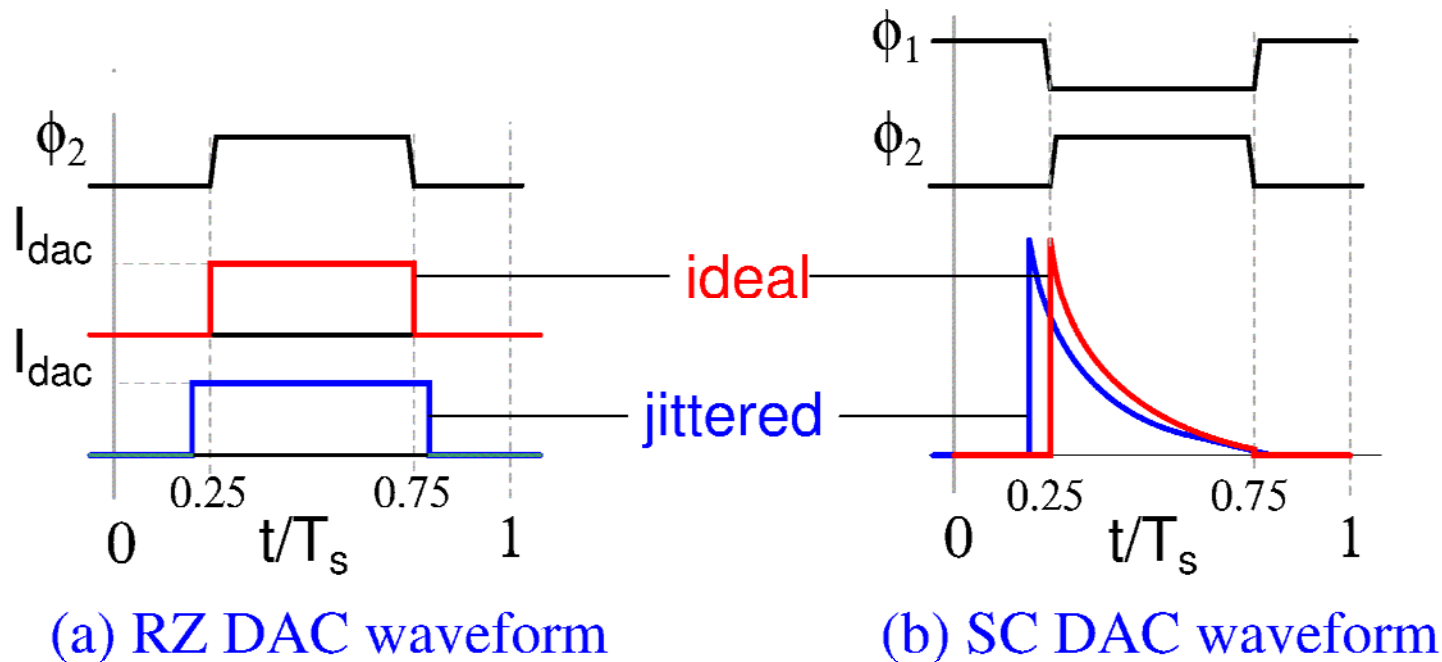- DAC output peak current is higher
- Higher demands on the linearity of the loop filter




DAC Pulse Shapes : SC

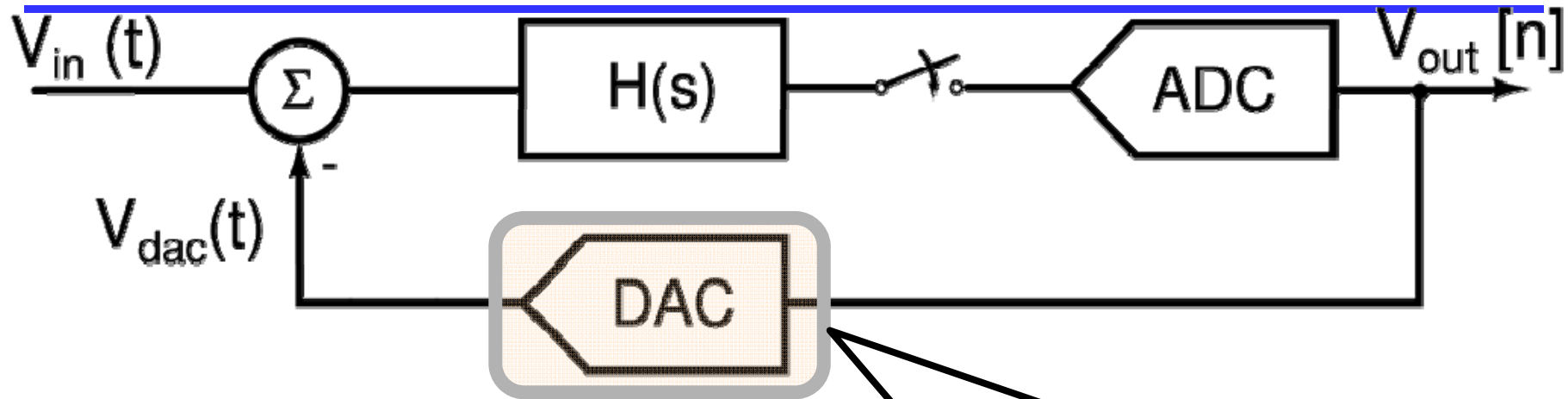


Terrible linearity !

Excellent for jitter

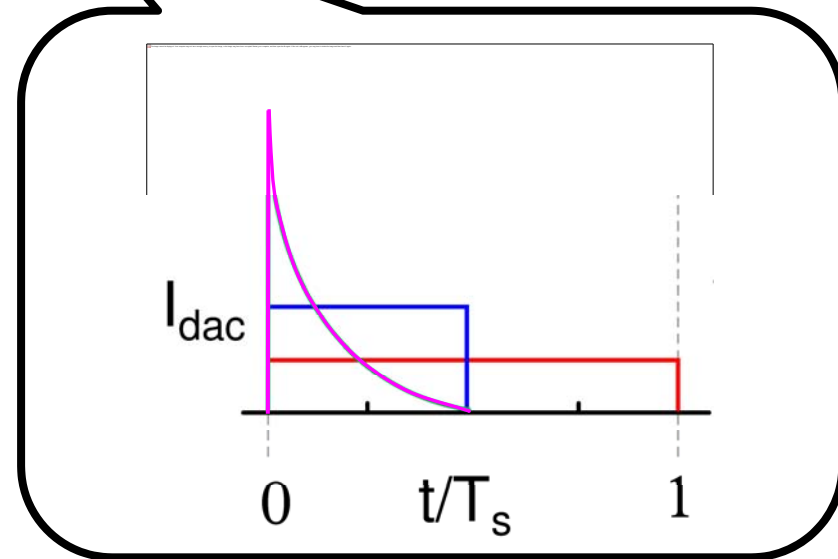


Introducing the SCRZ DAC

 


- RZ DAC
 - Excellent linearity
 - High jitter sensitivity
- SC DAC
 - Low jitter sensitivity
 - Poor linearity
- SCRZ DAC



Introducing the SCRZ DAC

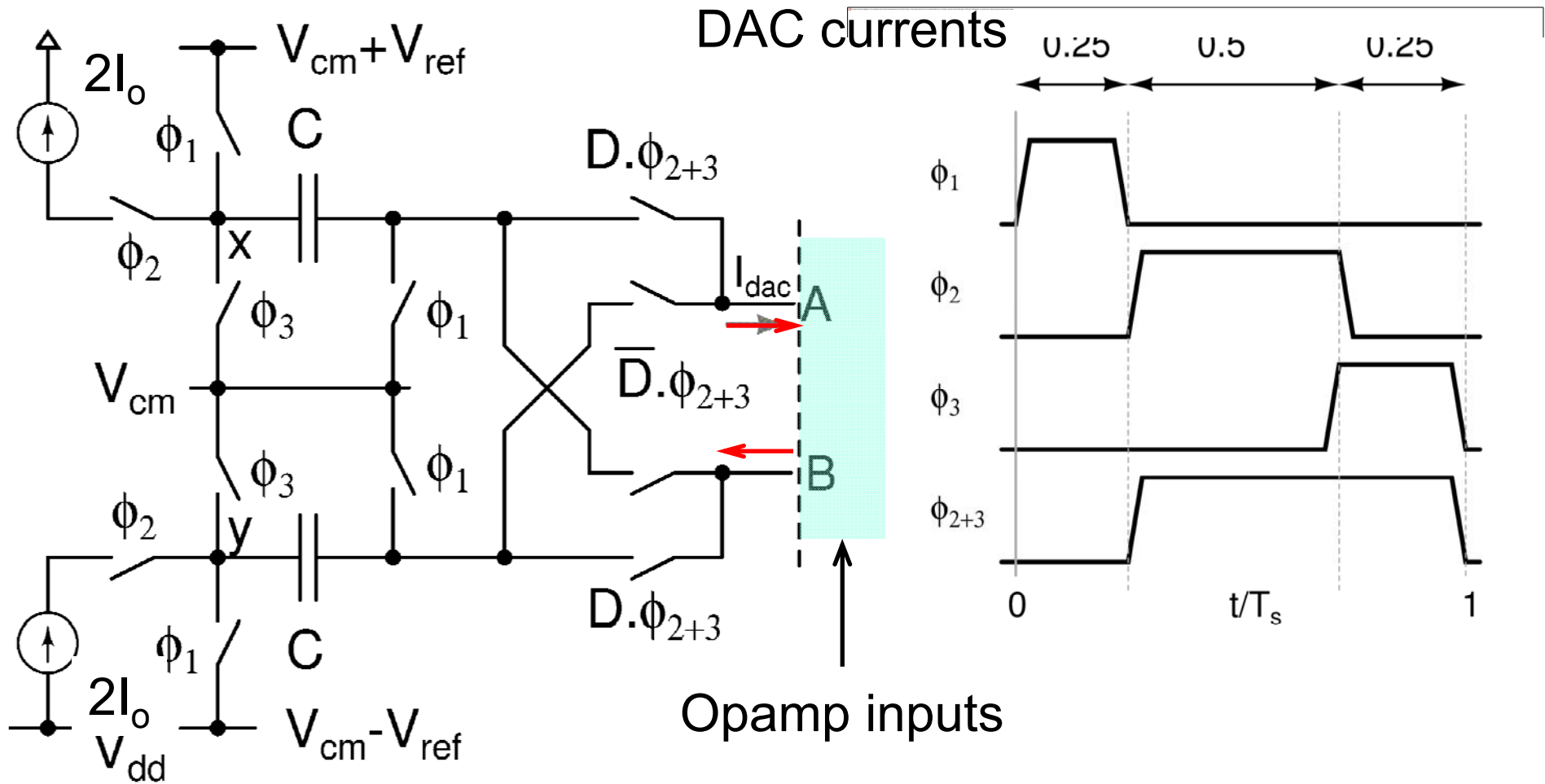

SCRZ DAC operation (Φ_1)

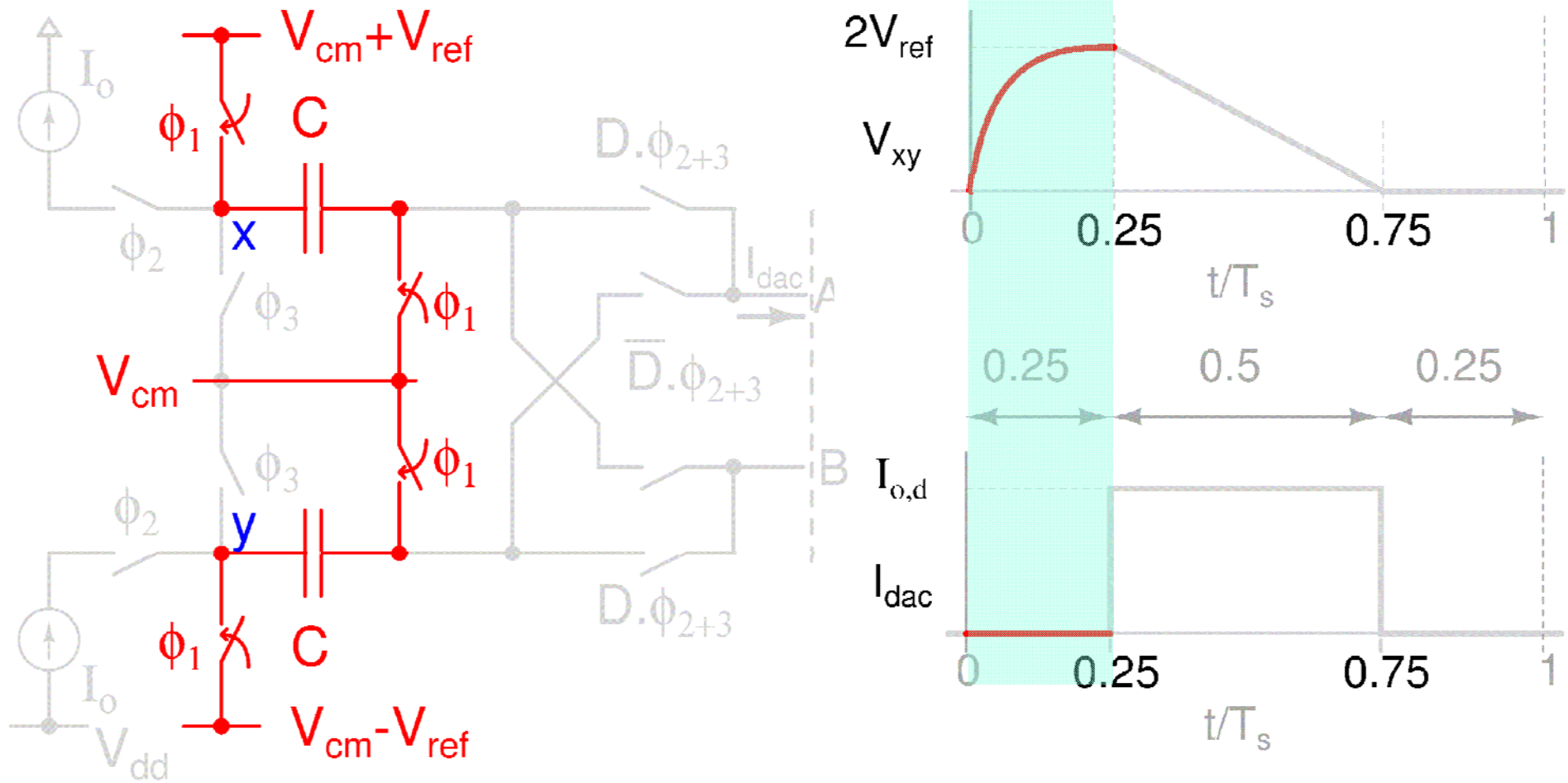



SCRZ DAC operation (Φ_2)

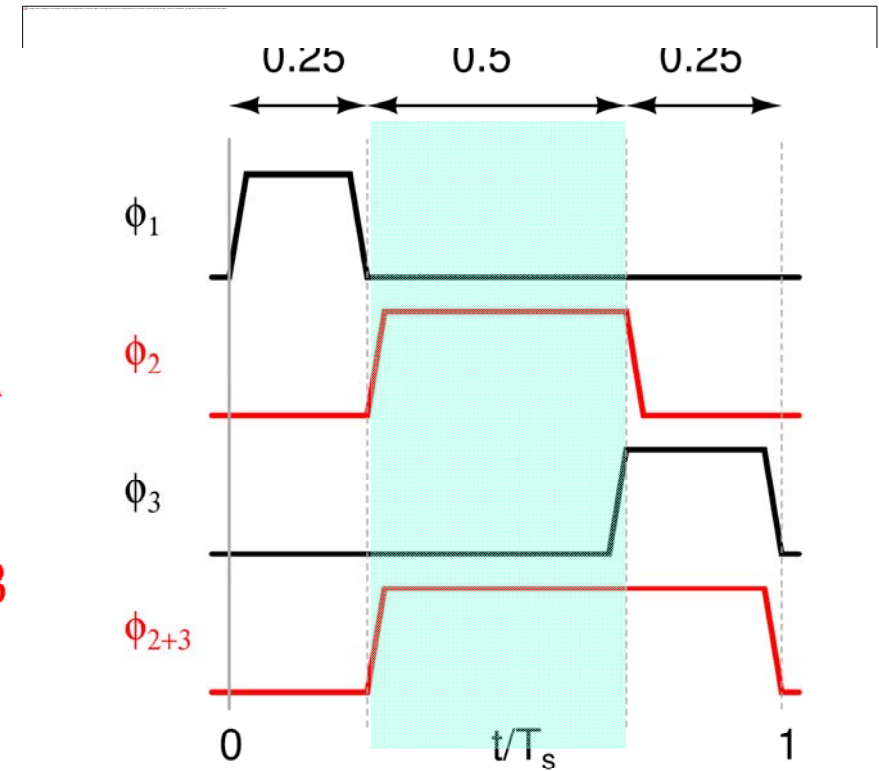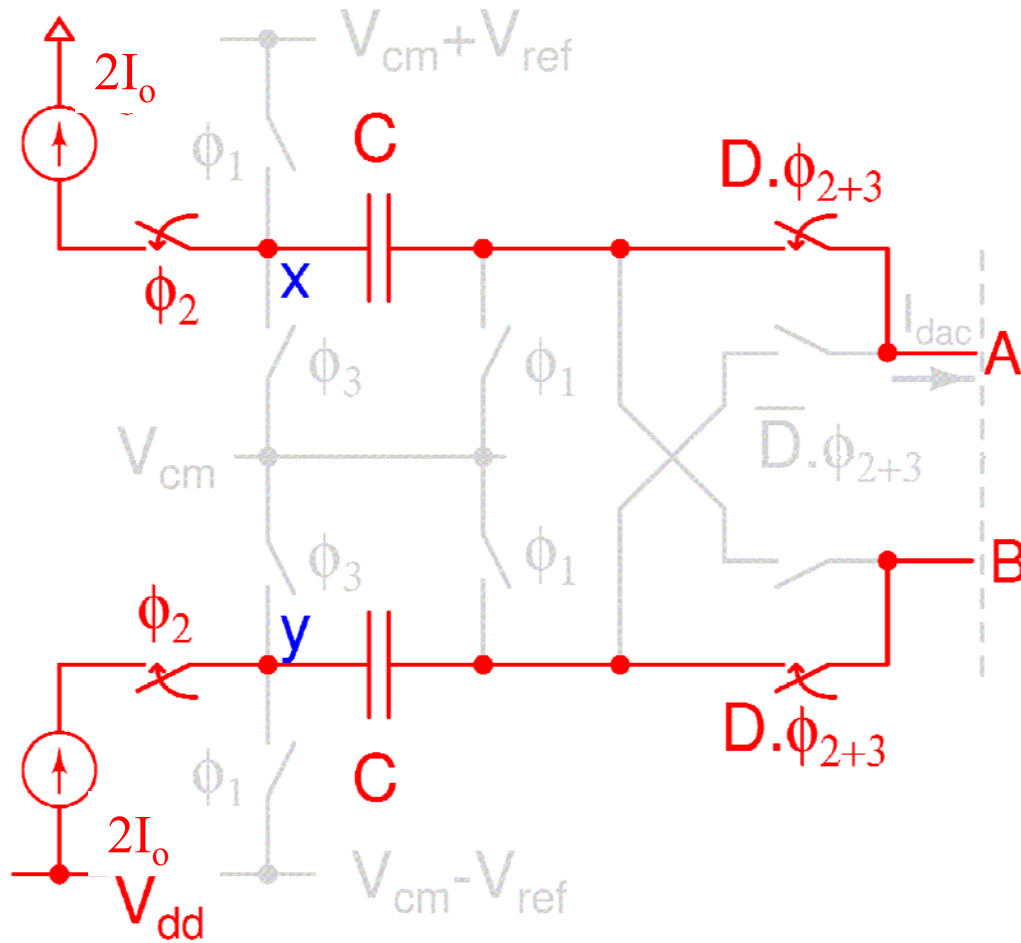



SCRZ DAC operation ($\Phi_2 = 0.5T_s$)

$$2I_o = CV_{ref}/(0.5T_s)$$



$V_{xy} = 0$

 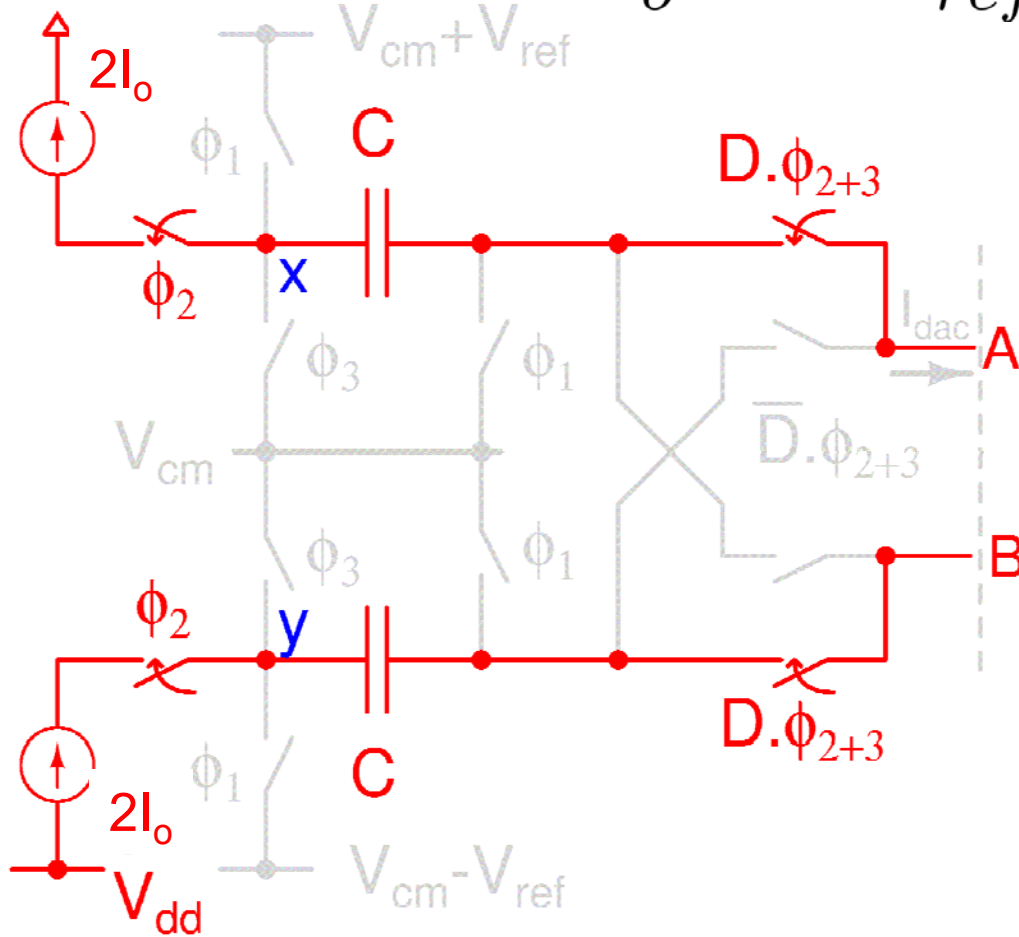

SCRZ DAC operation (Φ_3)

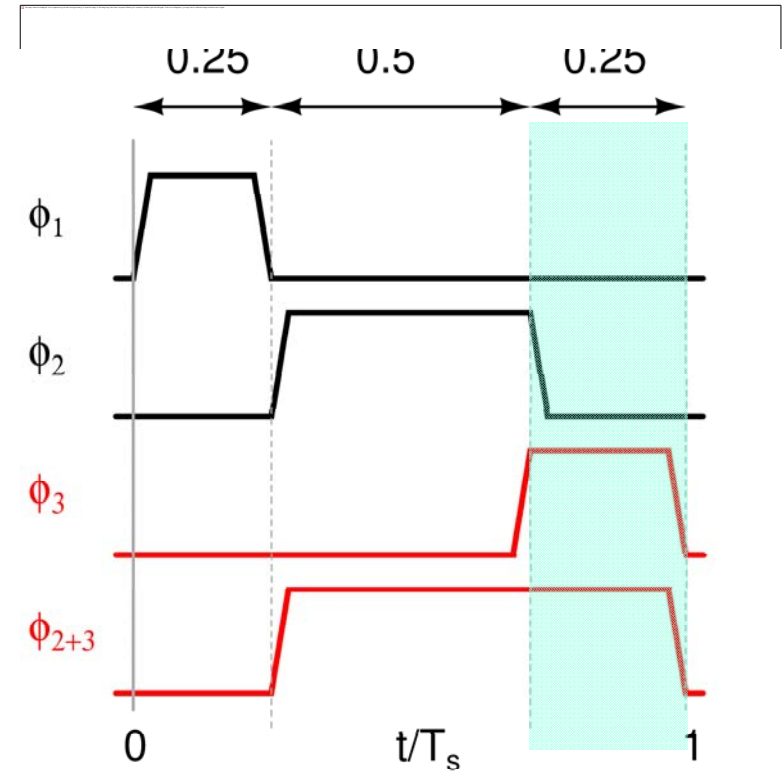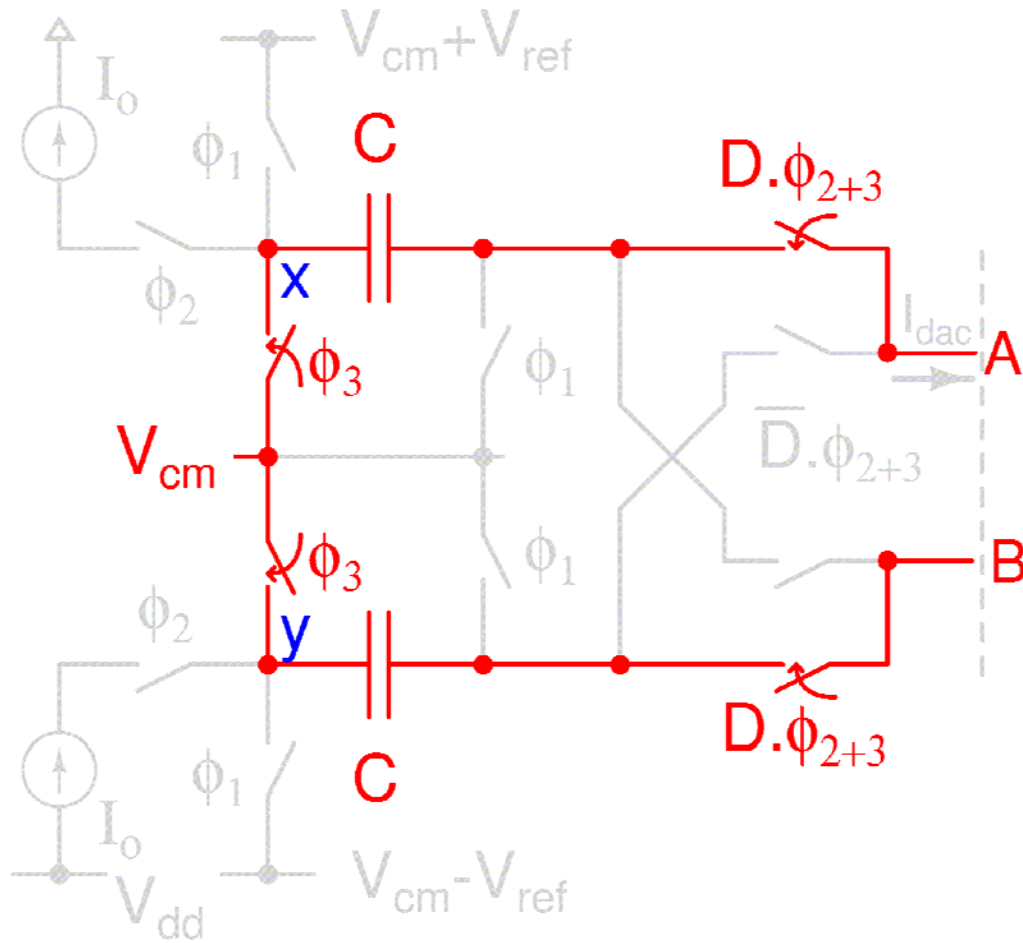


SCRZ DAC operation (Φ_3)

 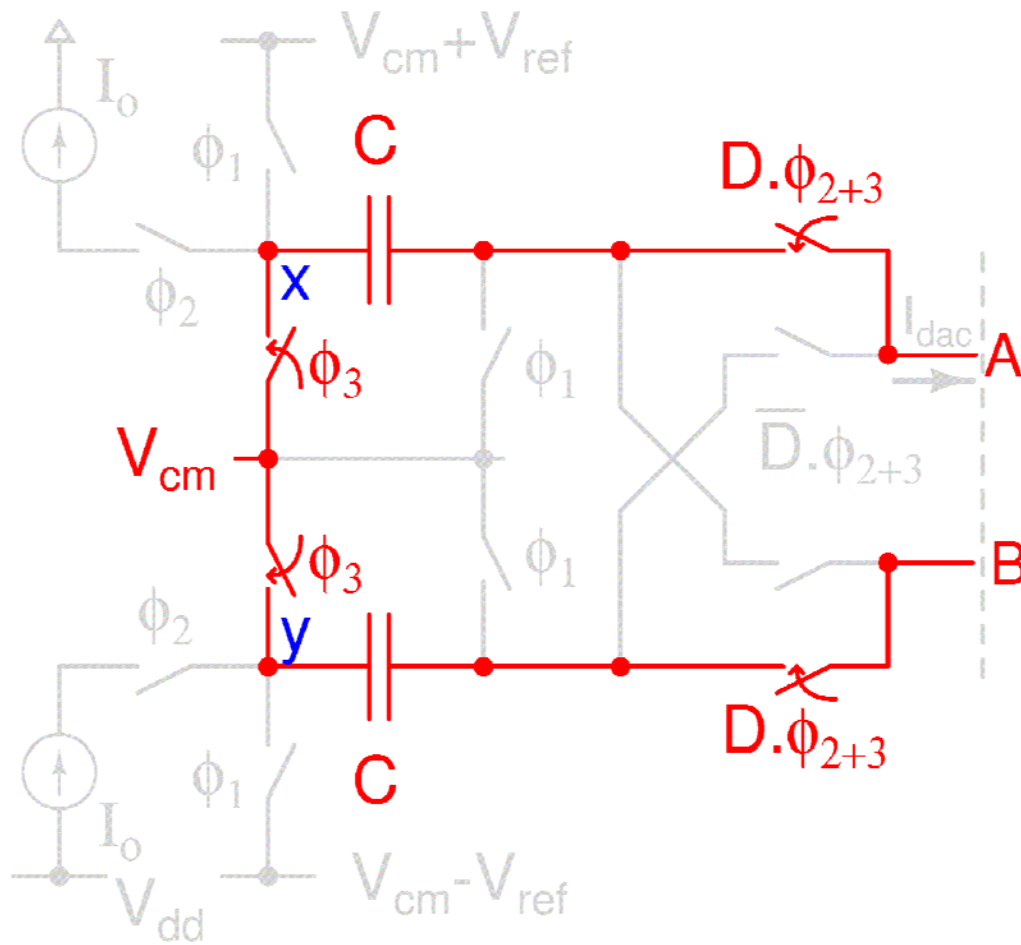


Summary : Ideal Waveforms

 - With an ideal clock
- With ideal current $2I_o = CV_{ref}/(0.5T_s)$
 - I_{dac} has an RZ pulse shape




Effect of jitter

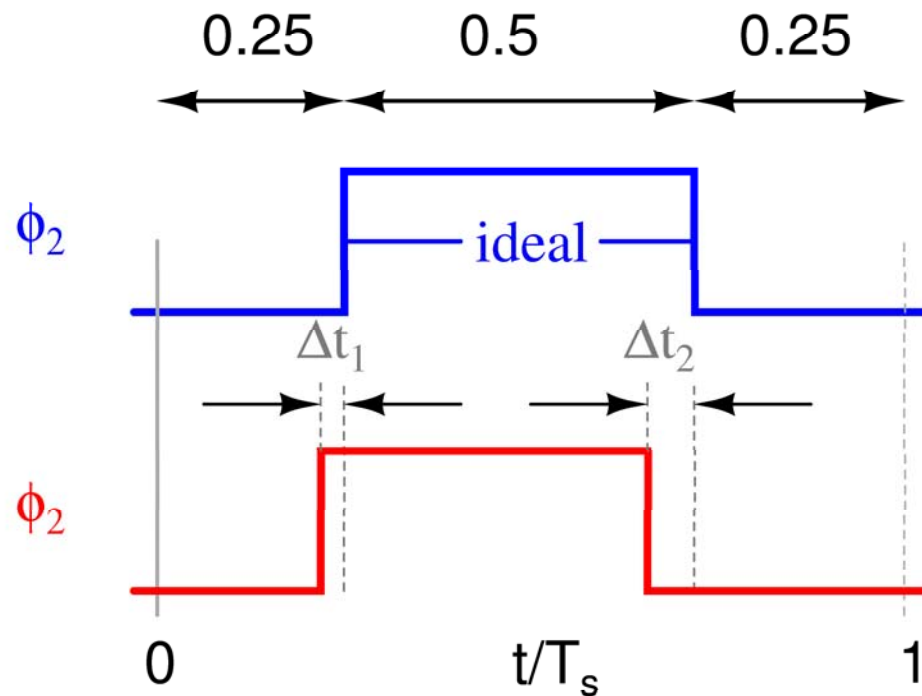
- Ideal – ϕ_2 half clock cycle wide
- Jittered - $0.5T_s + \tau$



Effect of jitter


 


I_{dac} lasts longer than $0.5T_s$

 


$V_{xy} < 0$ at end of ϕ_2


Waveforms (Φ_3)

 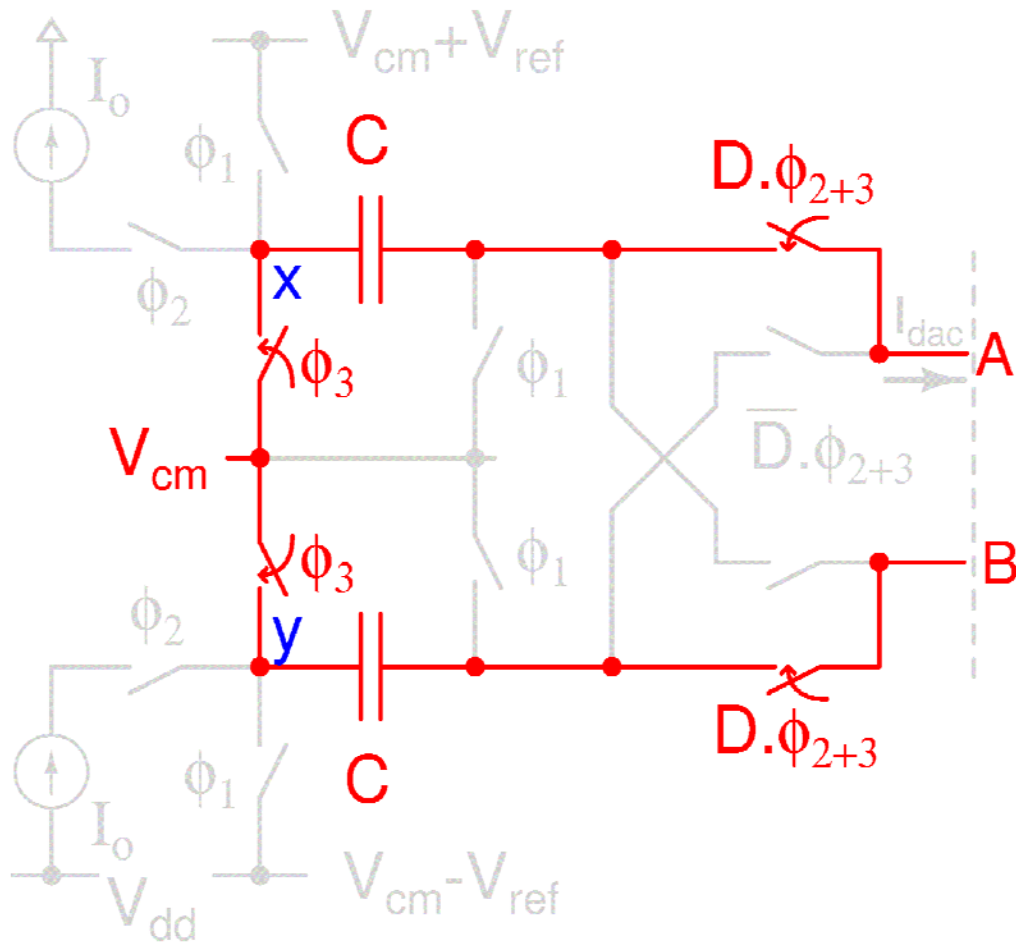

Total DAC Charge

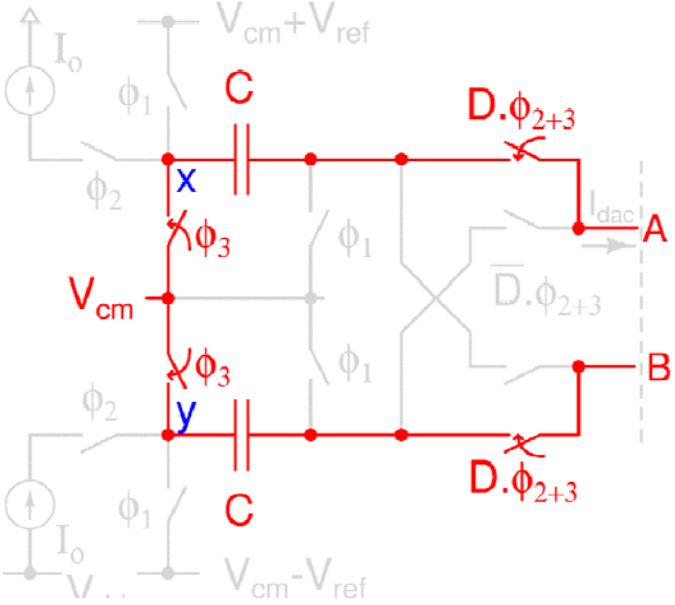

 
$$Q_{dac} = C(V_{xy,initial} - V_{xy,final})$$



$2V_{ref}$

Total DAC Charge

 


Irrespective of Jitter !


$$A_1 - A_2 = CV_{ref}$$

Role of current source

 - Shapes the capacitor discharge pulse
- Smaller peak current
- Relaxed requirement - linearity of the loop filter




(a) SCRZ Waveform

 

 (b) SC Waveform


Non ideality - Deviation of $2I_o$

- $2I_o(0.5T_s) = CV_{ref}$
- $I_{o,d} = 2CV_{ref}/T_s$
- Capacitors completely discharged at the end of Φ_2
- $I_{dac} = 0$ during Φ_3




If $2I_o < I_{o,d}$

 - Capacitors are incompletely discharged
- The residual charge is discharged during Φ_3
- I_{dac} is **positive** during Φ_3
- Net charge supplied by the DAC remains $\pm CV_{ref}$




If $2I_o > I_{o,d}$

 - Capacitors are over discharged
- The capacitors are charged during Φ_3
- I_{dac} is **negative** during Φ_3
- Net charge supplied by the DAC remains $\pm CV_{ref}$





Tune $2I_o$

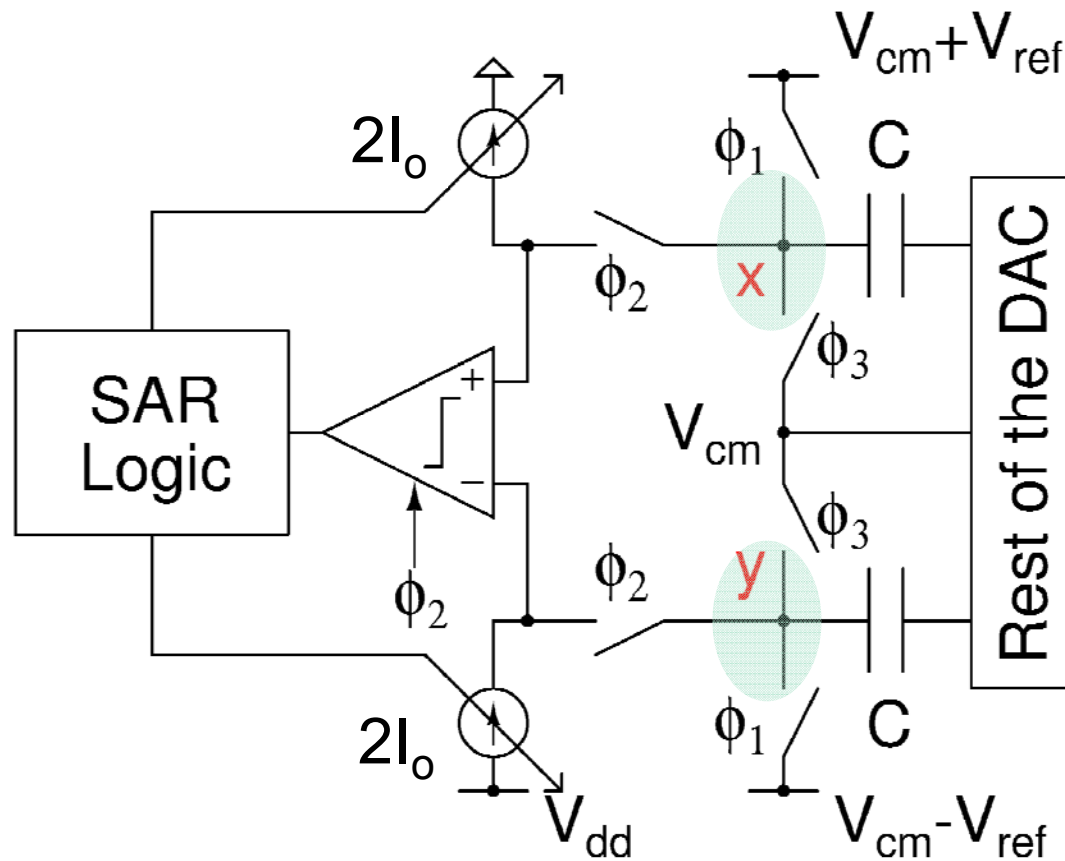
- Comparator- sign of V_{xy} at the end of Φ_2
- Control I_o to 6-bit accuracy





Compare : SC versus SCRZ DAC

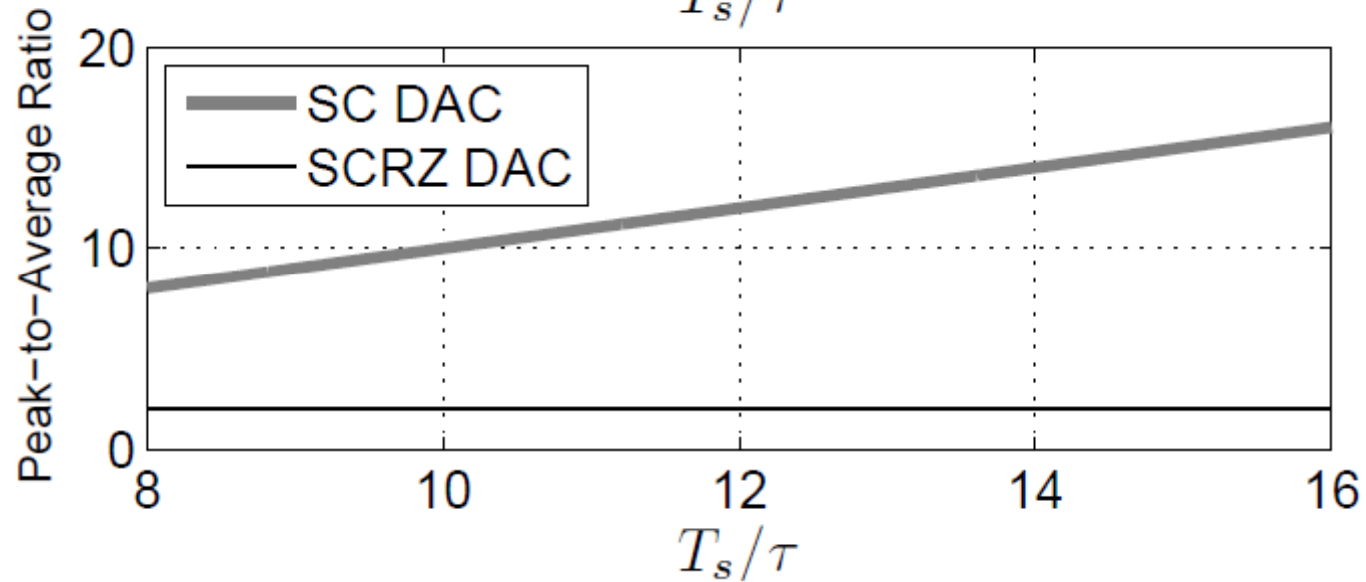 

Related Work : The SCSR DAC

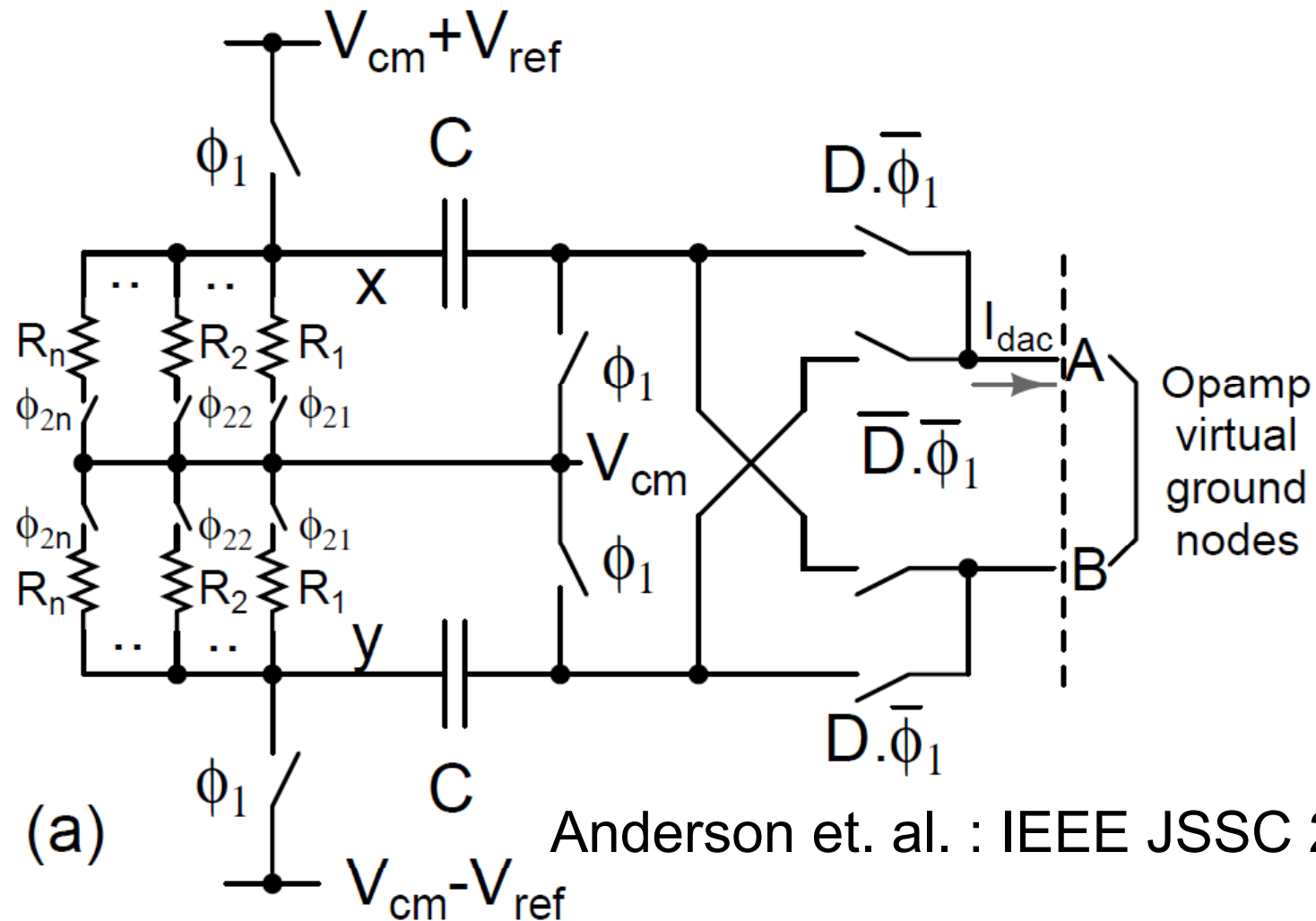


Related Work : The SCSR DAC

  


Target Modulator Specifications

- Signal Bandwidth = 2 MHz
 - Sampling frequency = 256 MHz
 - Quantizer range = $3.6 V_{pp,d}$
 - Target resolution = 14 Bits
 - 0.18 μm CMOS process
-

Noise Transfer Function

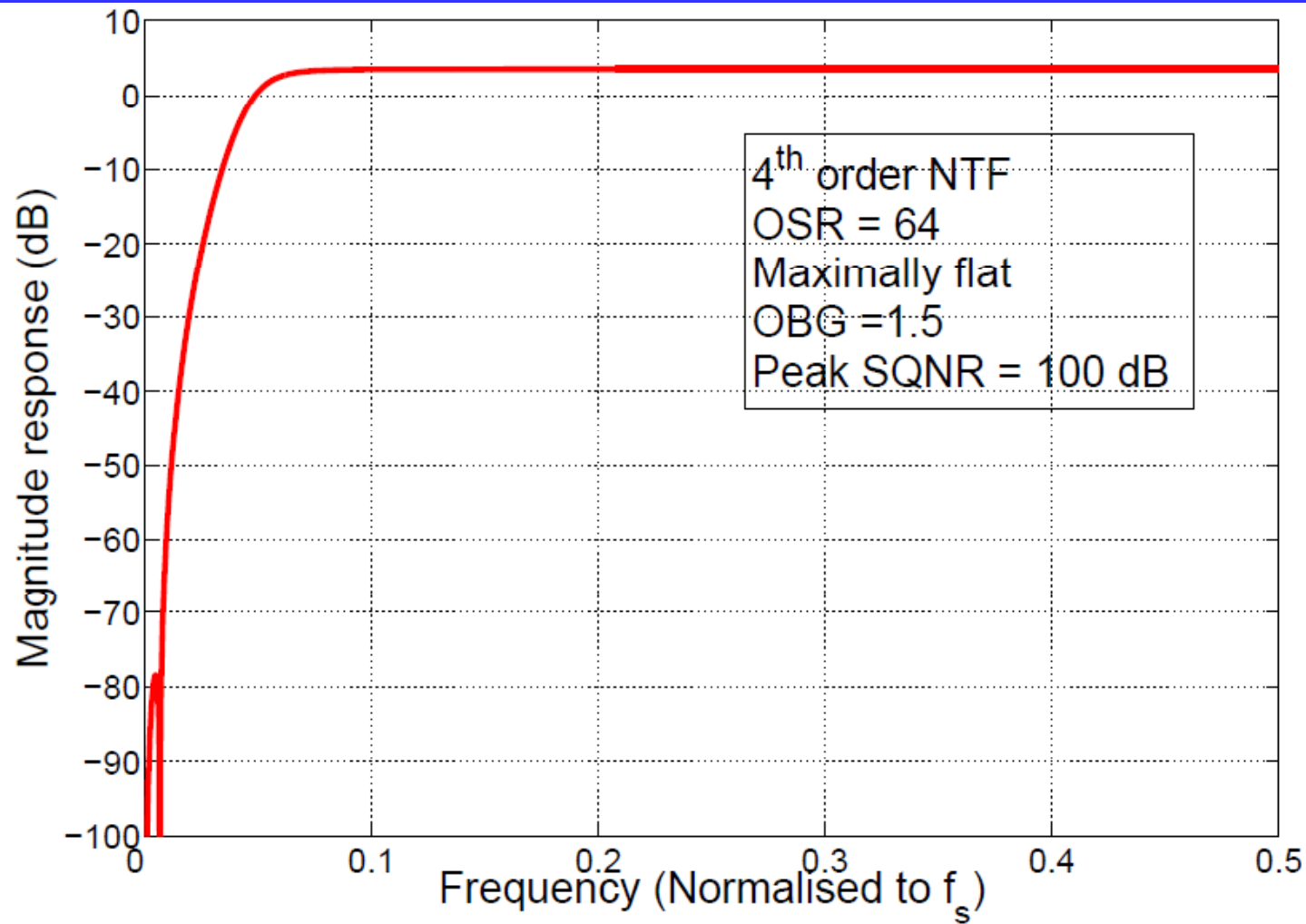


Modulator Architecture

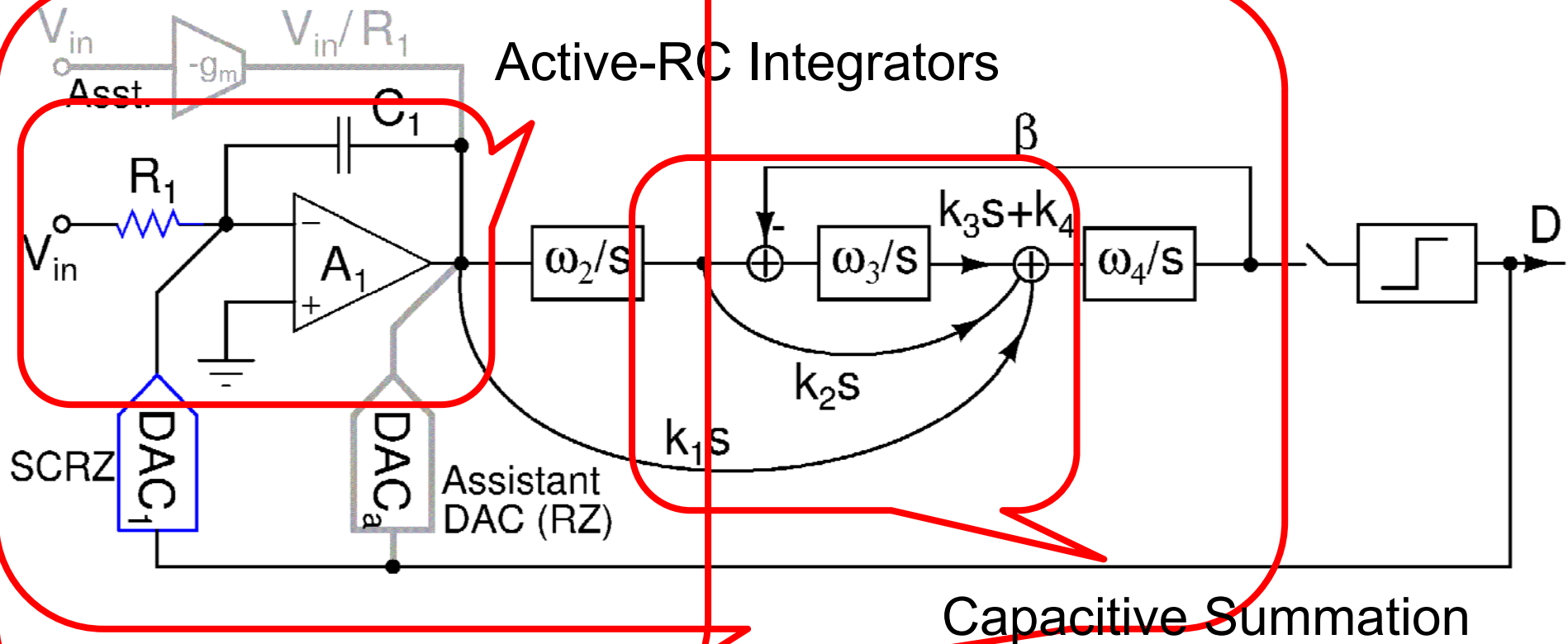


4th Order Cascade of Integrators
with Feed Forward (CIFF)

Assisted Opamp Technique

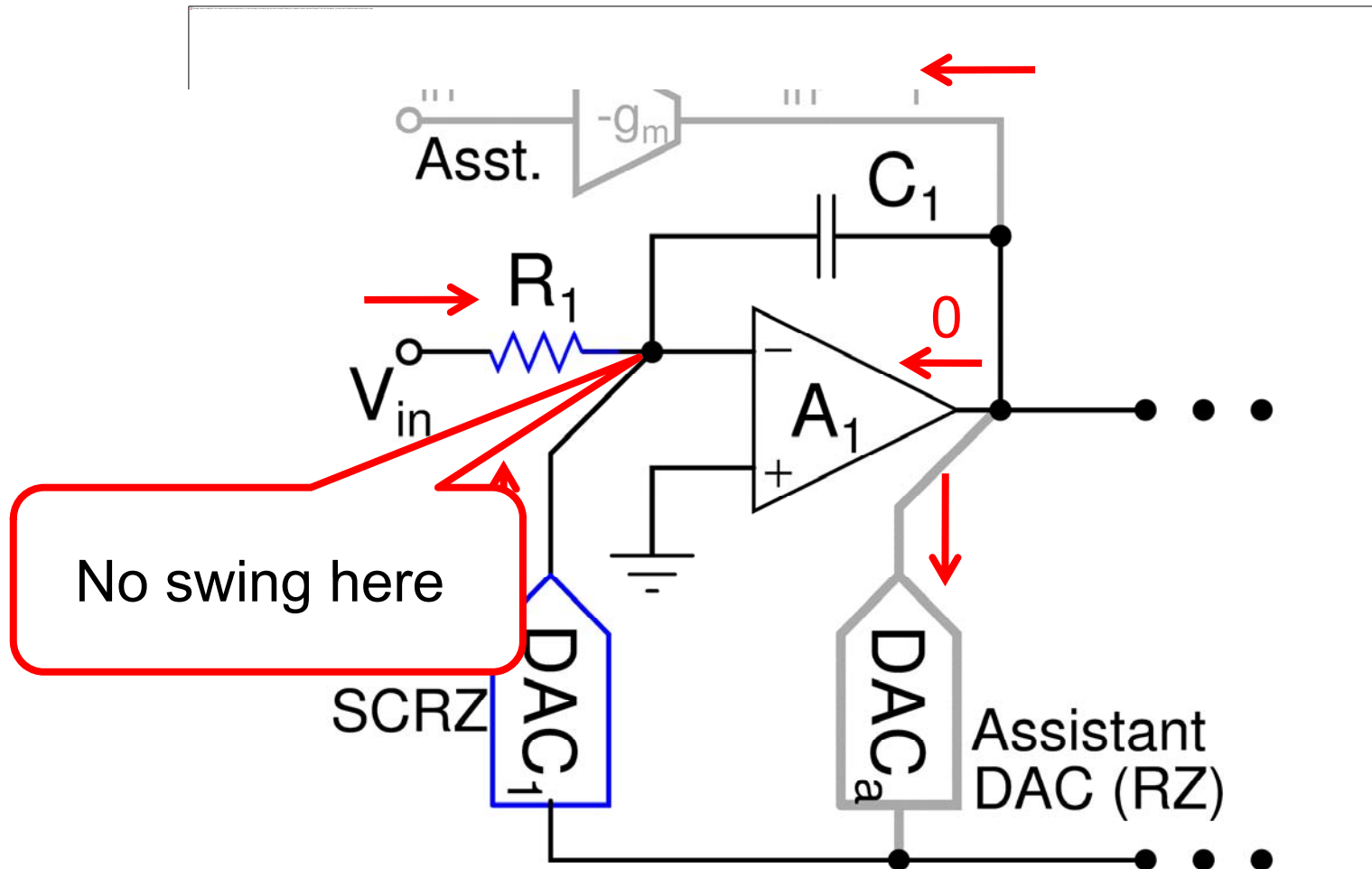


[1] S. Pavan and P. Sankar, "Power reduction in continuous-time delta sigma modulators using the assisted opamp technique," IEEE Journal of Solid-State Circuits., vol. 45, no. 7, pp 1365-1379, July 2010


Opamp Design

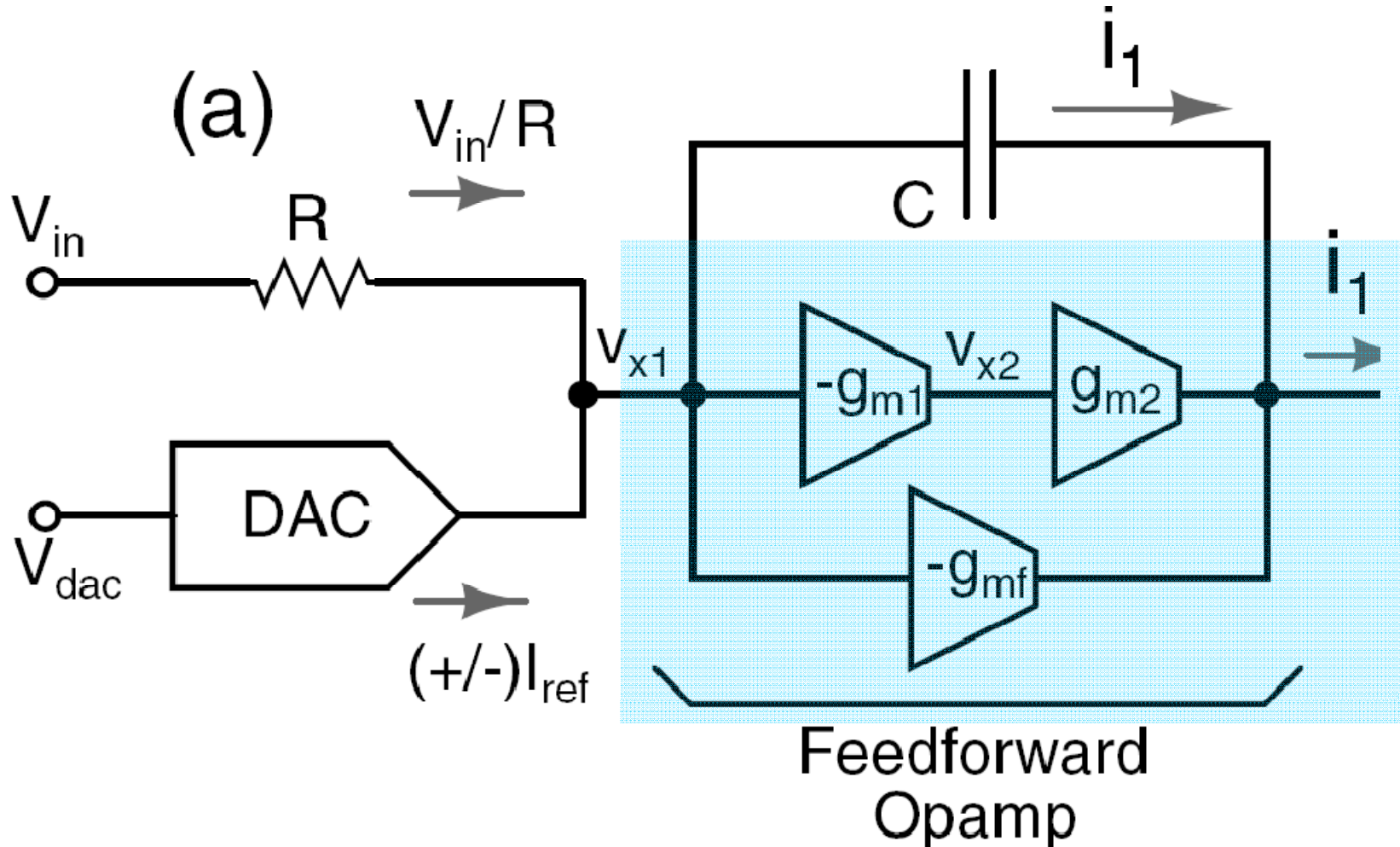


Two Stage Feedforward Compensation

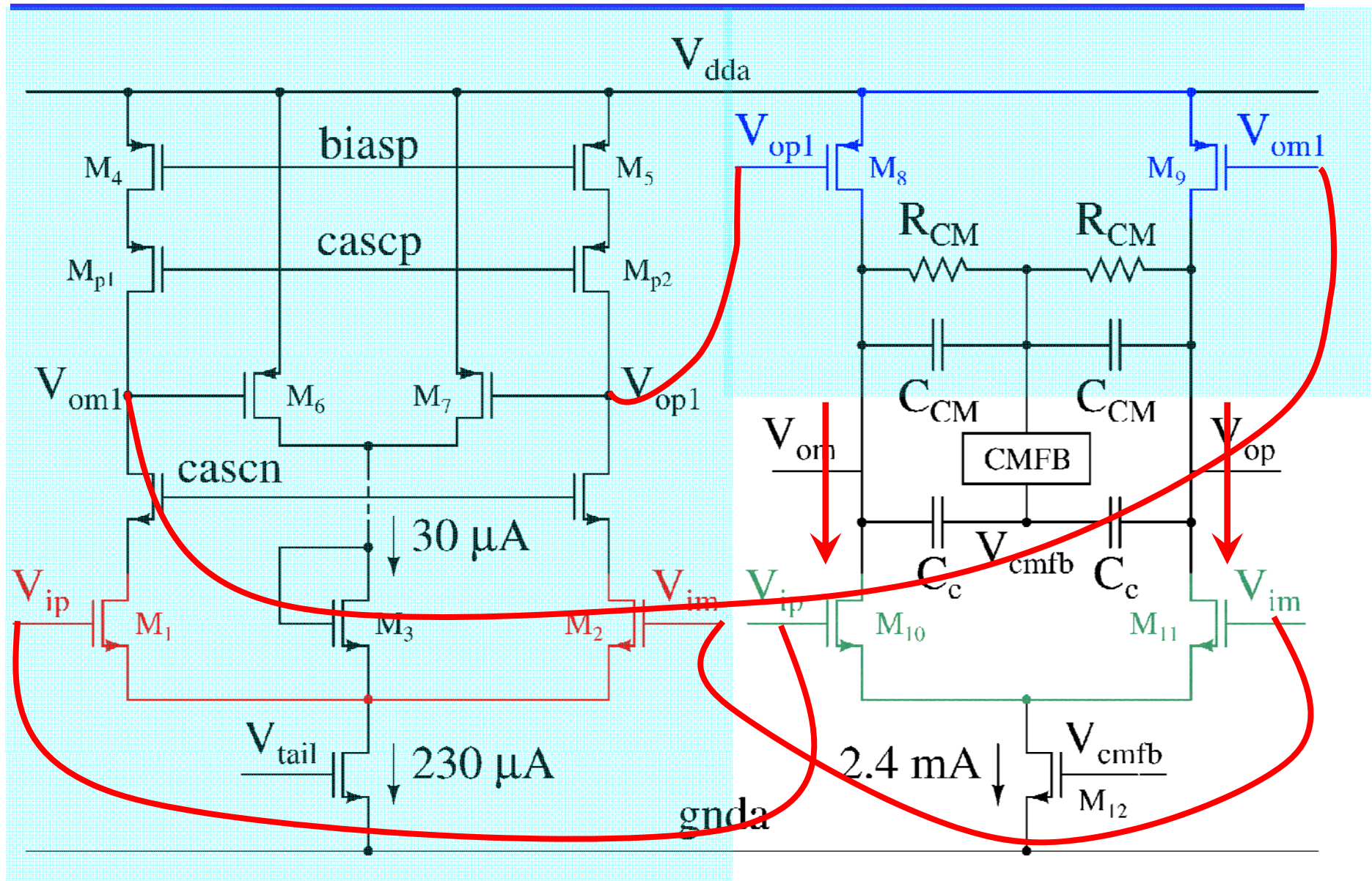


Chip layout and test board

 


Test Setup

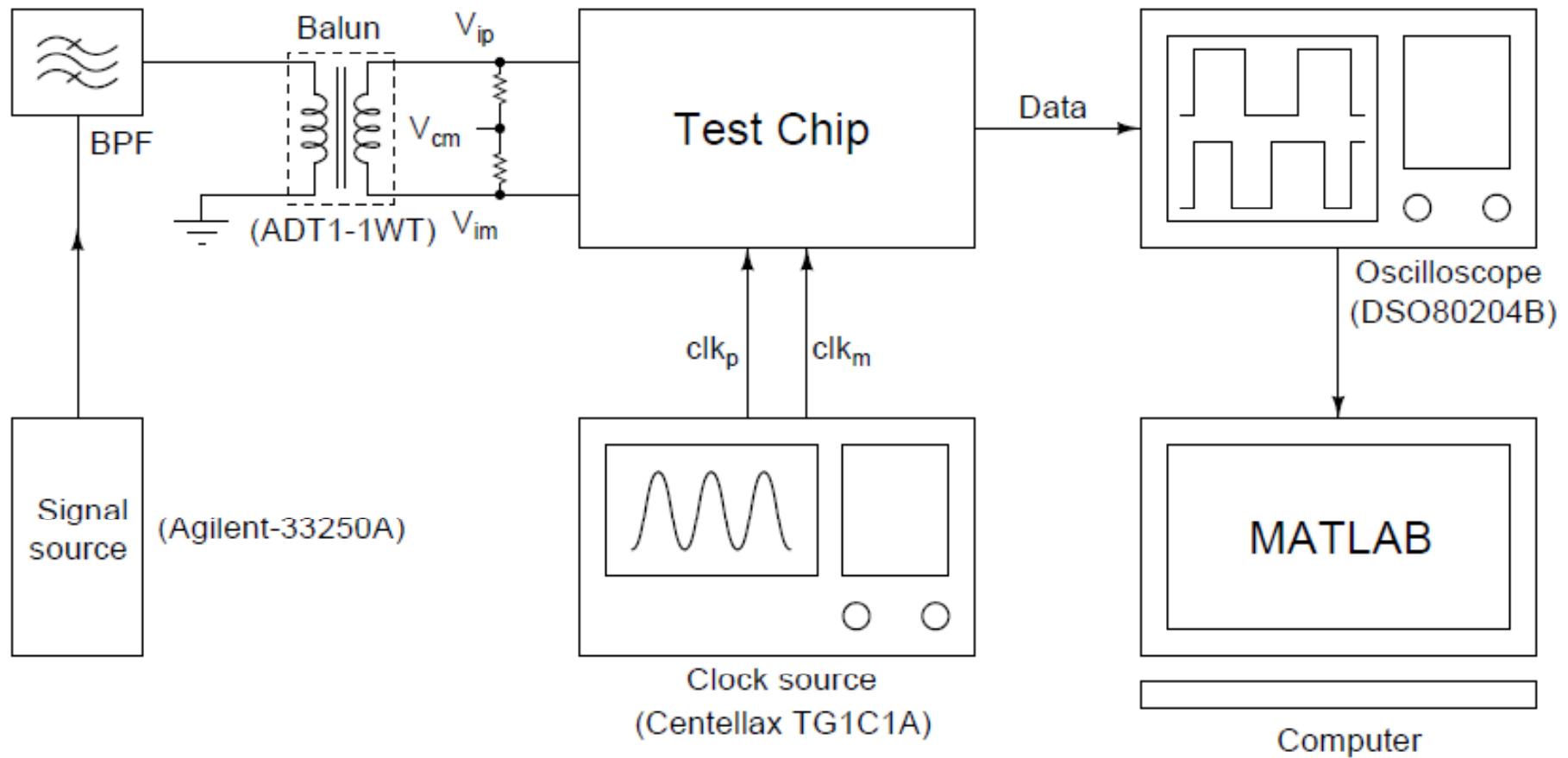


SN(D)R vs Input Amplitude

 


PSD of modulator

 


Controlled jitter experiment

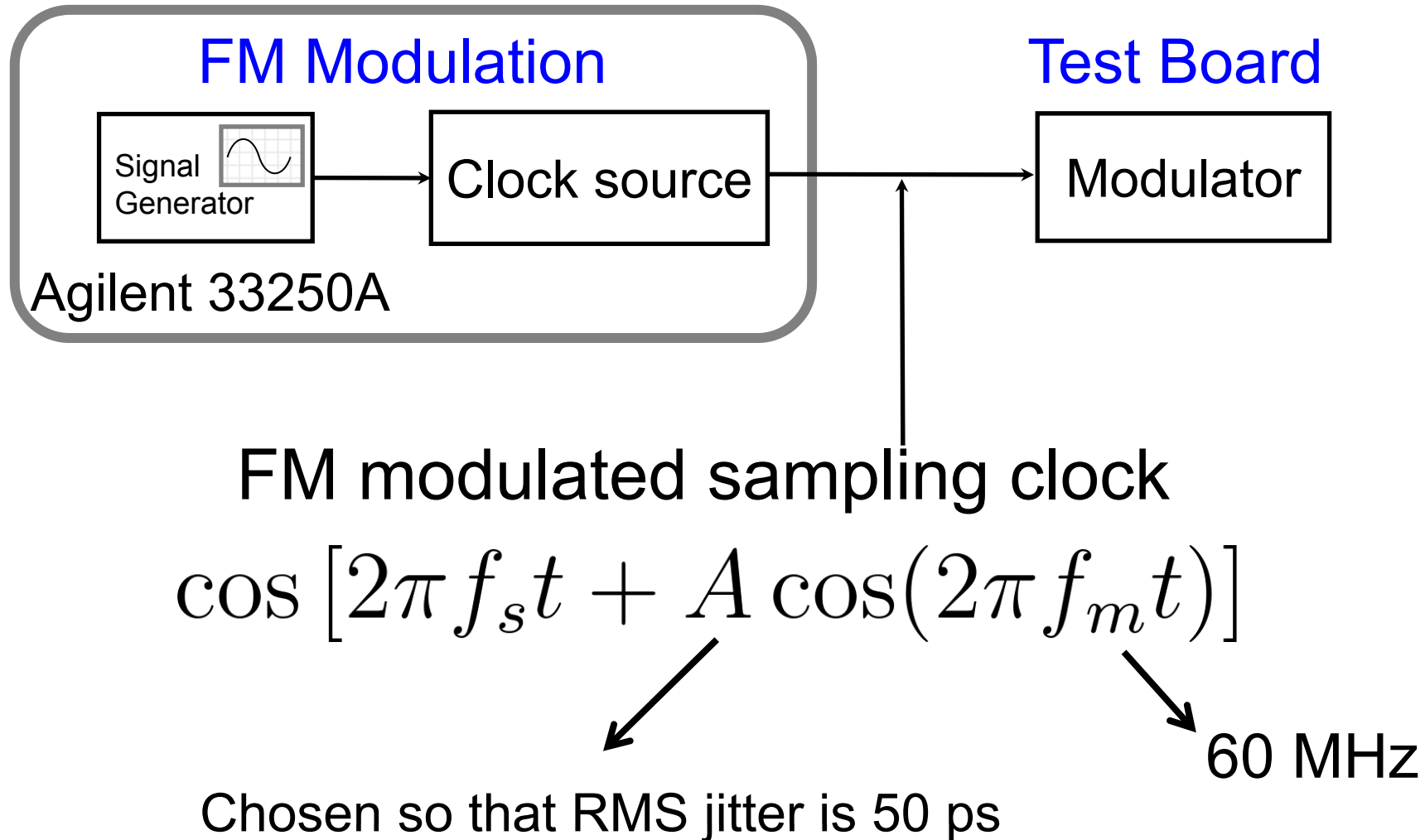

PSD of modulator (jittery clock)

 

Effect of opamp assistance

 

Performance Summary

Signal Bandwidth / Clock Rate	2 MHz / 256 MHz
Full Scale	3.6 V _{pp,diff}
Input Swing for peak SNR	-2.75 dBFS
Dynamic Range/ SNR/ SNDR	87.1 dB/ 84.5 dB/ 82.3 dB
Active area	0.38 mm ²
Process / Supply Voltage	180 nm CMOS / 1.8 V
Power (including references)	16.5 mW
FoM (SNR)	300 fJ/ v
FoM (SNDR)	387 fJ/ v
FoM (DR)	168 dB

Comparison with other works

Reference	This Work	Anderson JSSC09	Veldho JSSC03	Gealow VLSI11	Kim VLSI11
BW (MHz)	2	1.92	1.23	1.92	1.95
DR (dB)	87	70	83	83	79
SNR (dB)	84.5	66.4	83	-	74.3
SNDR (dB)	82.3	62.4	-	78	73.3
Power (mW)	16.5	5.0	4.1	2.8	8.55
FoM _{DR} (dB)	168	156	168	171	163
FoM _{SNR} (fJ/ v)	300	768	145	-	517
FoM _{SNDR} (fJ/ v)	387	1218	-	110	580
Tech. (nm)	180	90	180	40	65
Supply (V)	1.8	1.2	1.8	2.4/1.4	2.5
Sampling (MHz)	256	312	76.8	245.76	124.8
Feedback DAC	SCRZ	SCSR	SCR	CT-SI	CT-SC

Conclusions

- Conventional feedback DACs have problems
 - NRZ DAC : Rise-fall asymmetry
 - RZ DAC : Jitter sensitivity
 - SC DAC : Poor linearity
 - The SC-RZ DAC
 - Good marriage of the SC and RZ DACs
 - A high performance CTDSM incorporating an SC-RZ DAC
 - 87 dB DR in a 2MHz bandwidth
 - 16.6mW in a 180nm CMOS process
-