

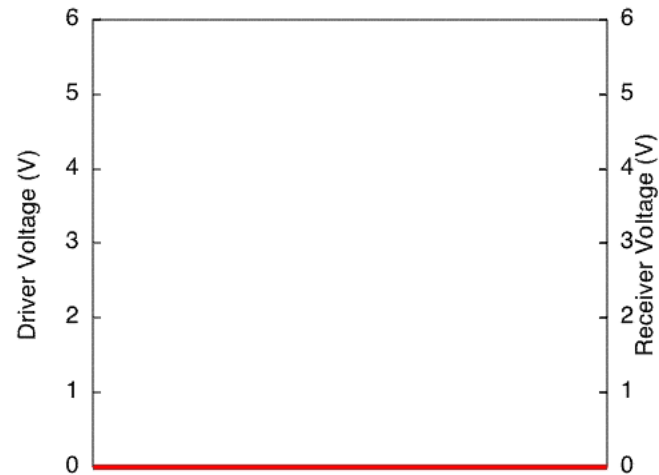

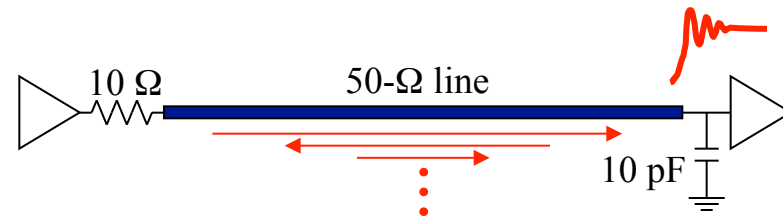
# Common Misconceptions about Inductance & Current Return Path



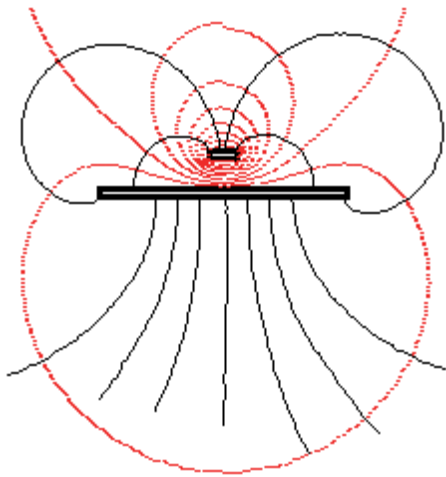Dr. Cheung-Wei Lam  
IEEE EMC Respected Speaker  
lam@alum.mit.edu



# Outline

- What are they?


$L$  = Inductance

$I^{\text{R}}$  = Current Return Path

- Why do we care?
- Common Misconceptions
- How do we control them?
- How do we identify problems?
- Summary

## L: What is it?

- Various kinds: *loop*, *mutual*, external, internal, kinetic, self, partial, self partial, mutual partial, partial mutual, ...
- Definition of inductance for closed loops:

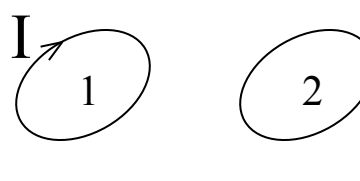
$$L_1 = \frac{\Psi_1}{I_1} \quad M_{21} = \frac{\Psi_{21}}{I_1}$$

- External, internal, kinetic
- Self, partial, self partial, mutual partial, partial mutual




# **L: What are they exactly?**

- Book:
  - **Clayton Paul, “Introduction to Electromagnetic Compatibility”**
- Paper:
  - **Al Ruehli, “Inductance Calculations in a Complex Integrated Circuit Environment,” IBM Journal of R&D, September 1972.**
- Articles:
  - **Bruce Archambeault, “Decoupling Capacitor Connection Inductance,” IEEE EMCS Newsletter, Spring 2009**
  - **Bruce Archambeault, “Part II: Resistive vs. Inductive Return Current Paths,” IEEE EMCS Newsletter, Fall 2008**

# L: Why do we care?

- Affects signal quality, crosstalk, EMI.
- Voltage Drop/Fluctuation
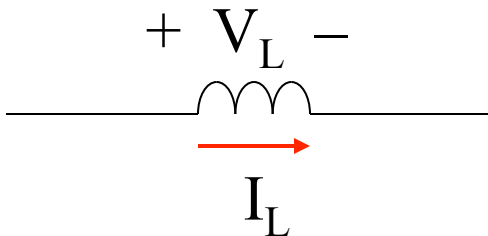
$$V_L = L \frac{dI_L}{dt}$$


- Crosstalk

$$V_2 = M_{21} \frac{dI_1}{dt} \quad M_{21} = L_{21}$$

# L: Why do we care?


- Transmission Line Discontinuity  
→ Signal Ringing




- Filtering & Decoupling

—  $Z_c(f)$

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

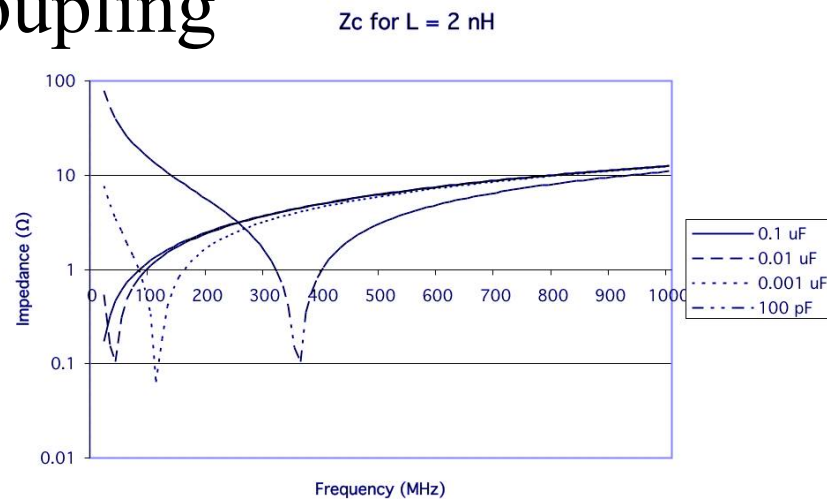

# I<sup>®</sup>: What is it?

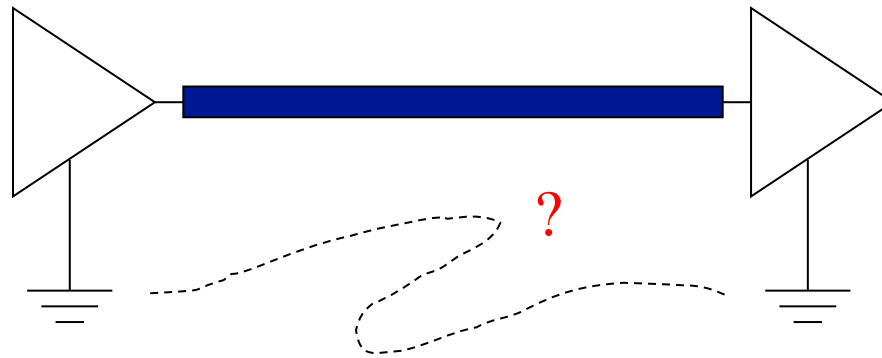

- Is ground a zero-impedance equipotential surface?  
—  $\mathbf{V_G} = \mathbf{I_G Z_G} = \mathbf{I_G (R_G + j\omega L_G)} \neq \mathbf{0}$




## I<sup>®</sup>: Why do we care?

- Increases current loop area  $A$ 
  - **EMI** ↑
- Increases loop inductance  $L$ 
  - **Signal Quality** ↓
  - **EMI** ↑
- Increases mutual inductance  $M$ 
  - **Crosstalk** ↑
  - **EMI** ↑
- Increases ground (return) inductance  $L_G$  or  $M_G$ 
  - **EMI** ↑



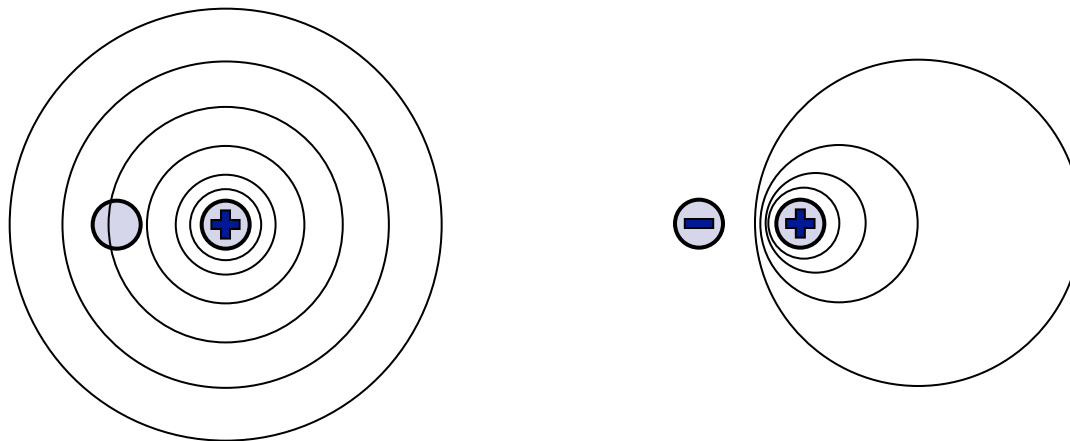
# L: Common Misconceptions

- Mistake loop L as sum of self inductances ( $L_{\text{self}}$ )!?
- Overlook the importance of return proximity!?




# L: Mounting Inductance

— Reduce length.

 




— Increase width.

 

— Think *return proximity!*






— Think *loop inductance!!*


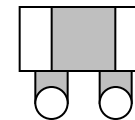
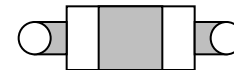
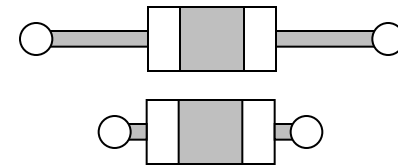

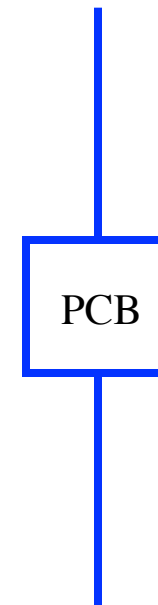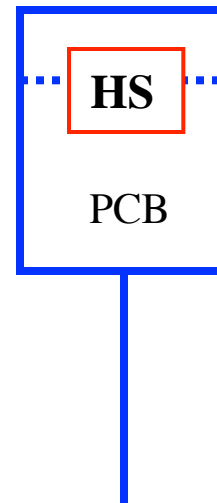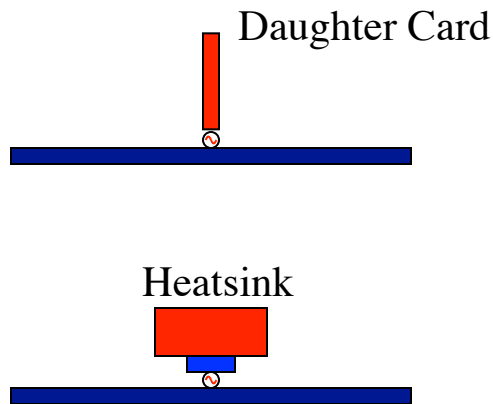
# L: Common Misconceptions

- Ground Drop  $\propto$  Self Inductance ( $L_{\text{Self}}$ )!?
  - **Ground Drop is a main source of CM radiation!**
  - $V_G = I_S Z_G = I_S (R_G + j\omega L_G)$




**L:**  $\Delta V = L_G \frac{dI_G}{dt}$

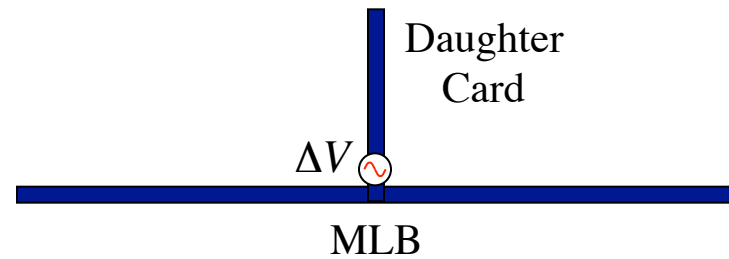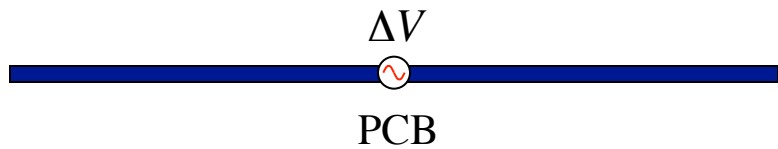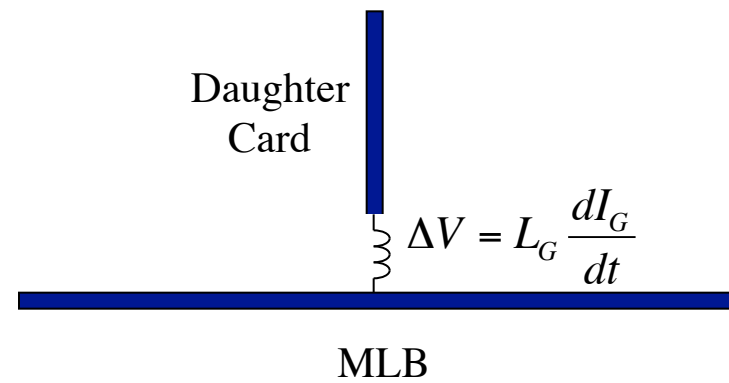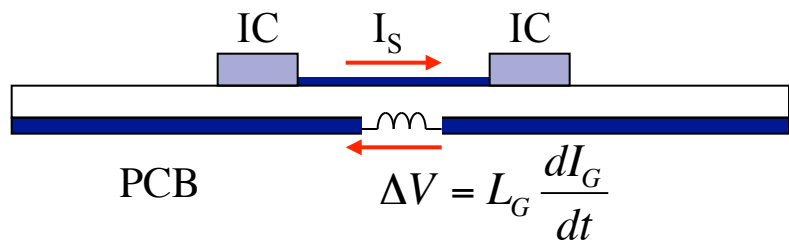


# L: Ground Inductance

- Transmission Line:  $L_T = L_S + L_G$

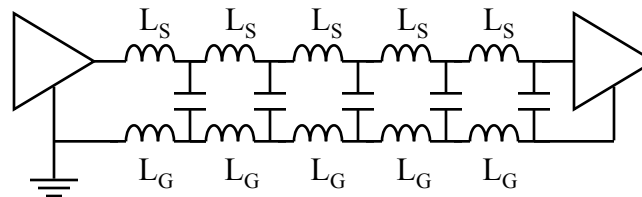

- $\Psi_G =$  magnetic flux around ground conductor


$$L_G = \frac{\Psi_G}{I_G}$$

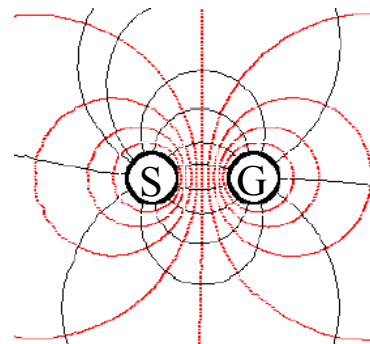

— Magnetic Field  
— Electric Field

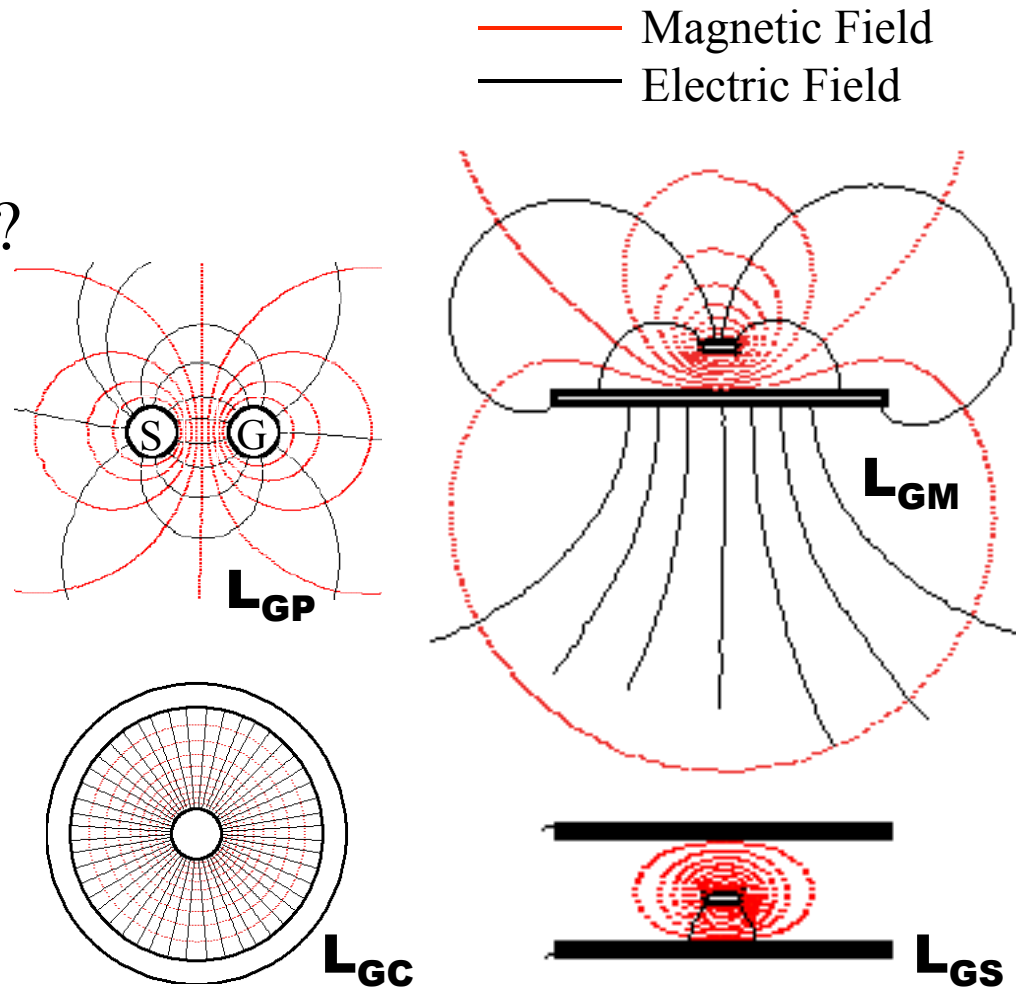
# L: $L_G = ?$

- $L_G = \text{self inductance!}$ 
  - $L_G = M_G$  (**DM** → **CM**)
    - Partial inductance
  - **Pairs (S, P, V, W)**
    - $L_{GP} = L_T/2$
  - **Microstrip**
    - $L_{GM} \ll L_T$
  - **Stripline**
    - $L_{GS} \ll L_{GM}$
  - **Coaxial**
    - $L_{GC} \approx 0$



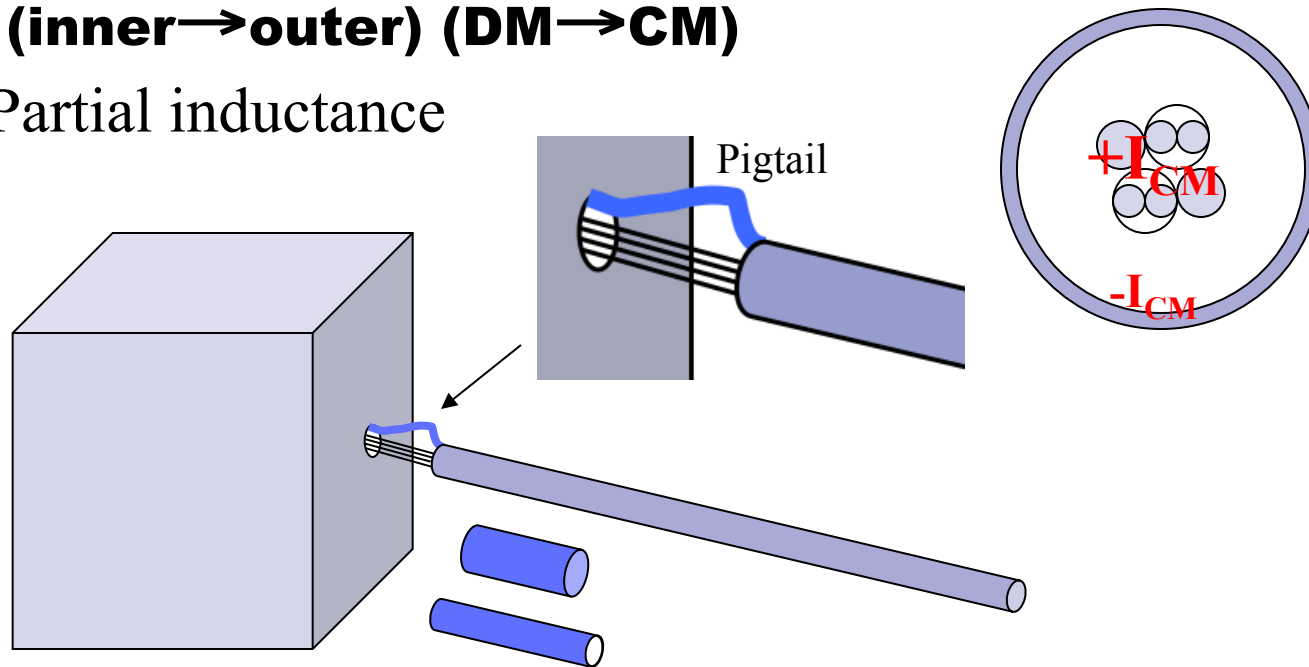
# L: Common Misconceptions

- Pigtail termination is bad because of its  $L_{\text{Self}}!$ ?
  - $M_p$  (inner  $\rightarrow$  outer) (DM  $\rightarrow$  CM)
    - Partial inductance



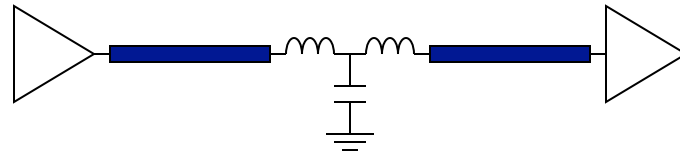
# L: Common Misconceptions

- Smaller is always better!?
  - **Excess capacitance causes reflections!**



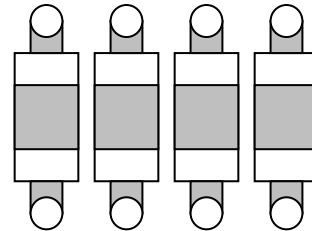- Inductance parallels down like resistors!?
  - **Don't forget M!**
  - **Spread out decoupling capacitors!**
  - **Alternate power/ground pins!**





- Overlook mounting inductance vs. component inductance!?
  - **Don't spend on expensive low-L filters unless layout has already been optimized.**



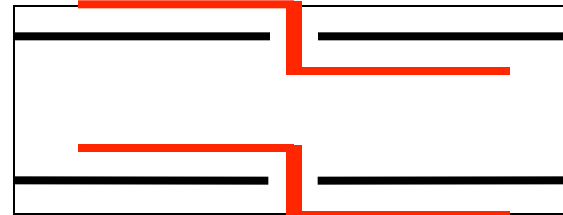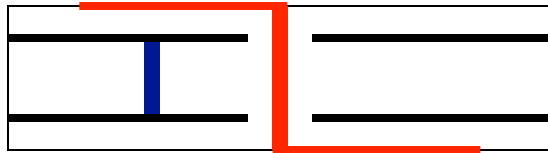
# L: Common Misconceptions

- Via Inductance =  $L_{\text{Self}}!$ ?  
— **Think *loop inductance!***




 - Overlook the dependence on current distribution!?  
— **Current distribution affects inductance!**



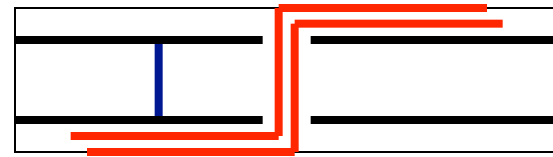
# M: Common Misconceptions

- Overlook the importance of return proximity!?
  - **Think separation.**
  - **Think *return proximity!***






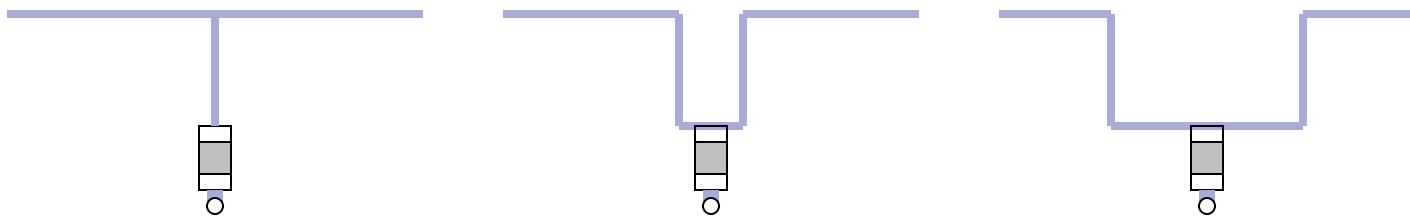- $L_{\text{Self}}$  degrades capacitor performance!?
  - **Think mutual inductance!**



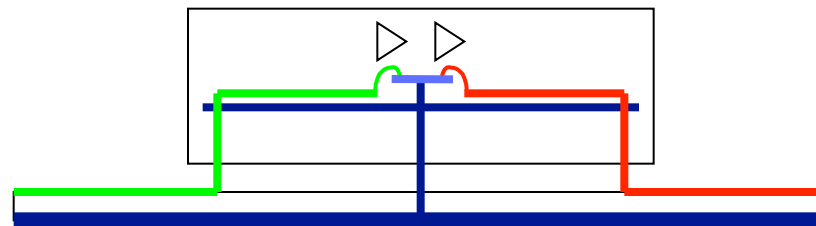
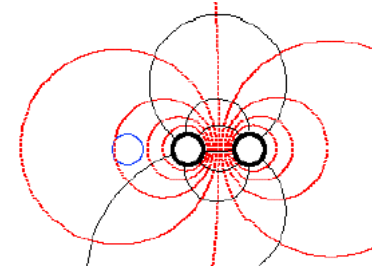
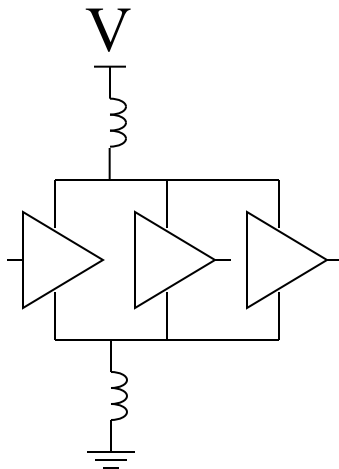
# M: Common Misconceptions

- Ground Bounce & Power Noise  $\propto L_{\text{Self}} (L_P)$  of Pin!?  
— **Think *loop-to-loop mutual inductance!***



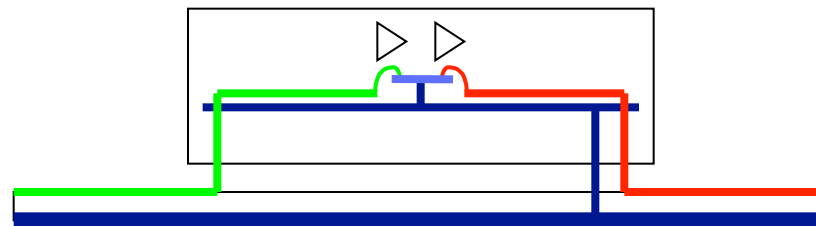
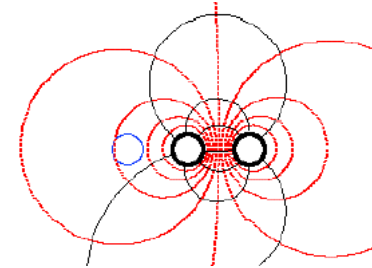
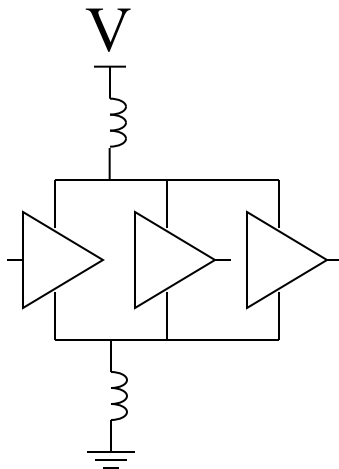
# M: Common Misconceptions

- Ground Bounce & Power Noise  $\propto L_{\text{Self}} (L_P)$  of Pin!?  
— **Think *loop-to-loop mutual inductance!***



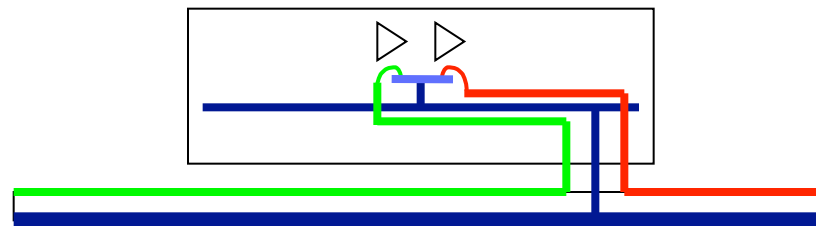
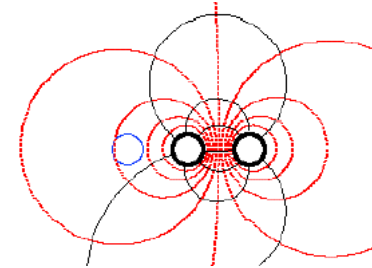
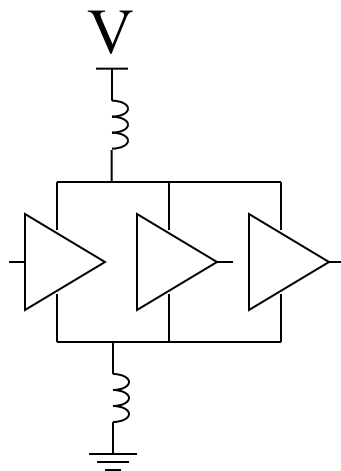
# M: Common Misconceptions

- Ground Bounce & Power Noise  $\propto L_{\text{Self}} (L_{\text{P}})$  of Pin!?  
— **Think *loop-to-loop mutual inductance!***



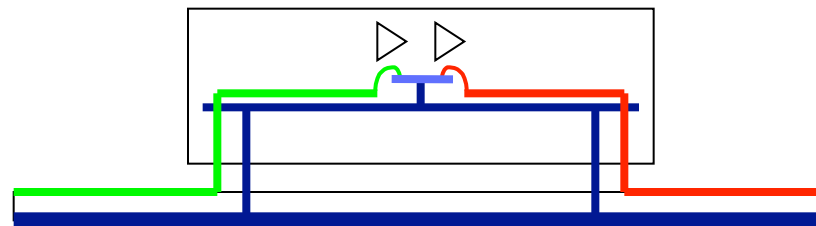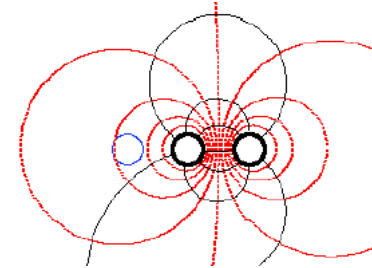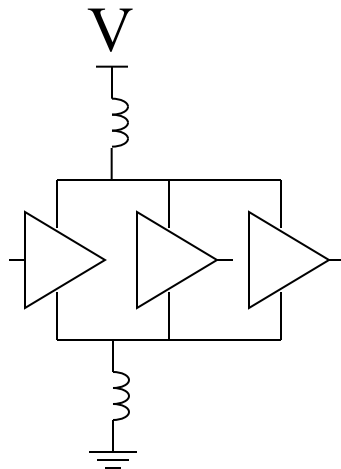
# M: Common Misconceptions

- Ground Bounce & Power Noise  $\propto L_{\text{Self}} (L_P)$  of Pin!?  
— **Think *loop-to-loop mutual inductance!***


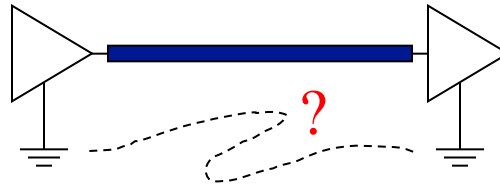
# I<sup>®</sup>: Common Misconceptions

- Signal ground is a current source/sink!?




- Ground plane is a zero-impedance equipotential surface!?
  - $V_G = I_G Z_G = I_G (R_G + j\omega L_G) \neq 0$
  - At kHz:  $R_G \gg j\omega L_G$ 
    - IR drop causes common-impedance coupling.
  - At MHz/GHz:  $R_G \ll j\omega L_G$ 
    - I<sup>®</sup> affects A, L, M, SI, EMI.
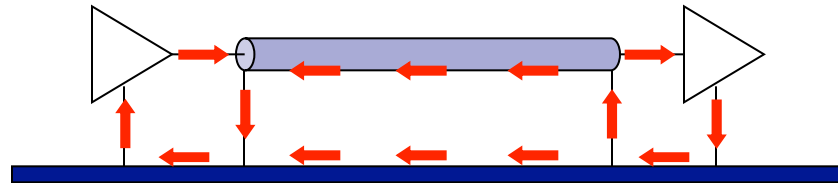
# I<sup>®</sup>: Common Misconceptions


- Current takes the least resistance path!?

- $Z_G = R_G + j\omega L_G$
- Think **R** at  $f \leq \text{kHz}$ .
- Think **L** at  $f \geq \text{MHz}$ !



- Current returns along intended paths!?

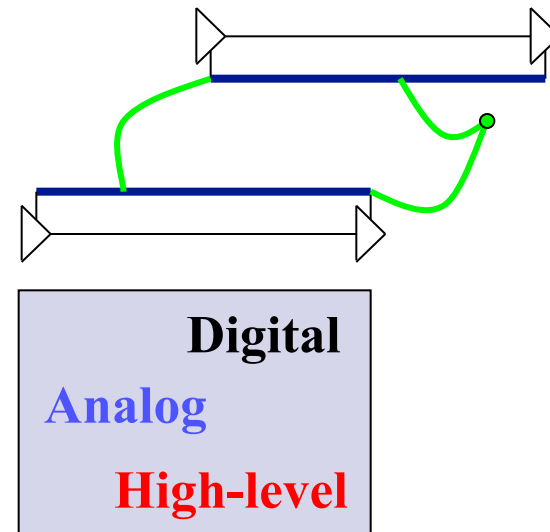
- **IR drop** → **common-Z coupling.**
- **Current spreads out** at  $f \leq \text{kHz}$ .
- **Single-point grounding** used for:
  - Low-level analog subsystems,
  - High-level noisy subsystems, e.g. motor drivers.






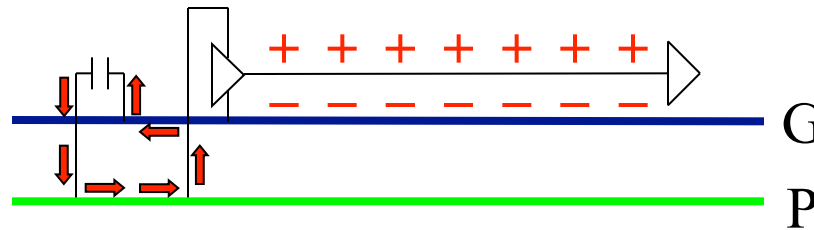
# !®: Common Misconceptions

- Current returns through ground but not power!?




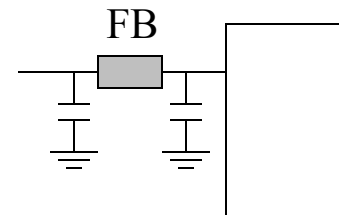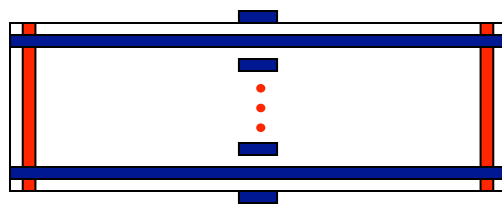- Ground and power planes are interchangeable!?
  - **Ground is connected to chassis, but not power.**
  - **Power isolation breaks the symmetry.**




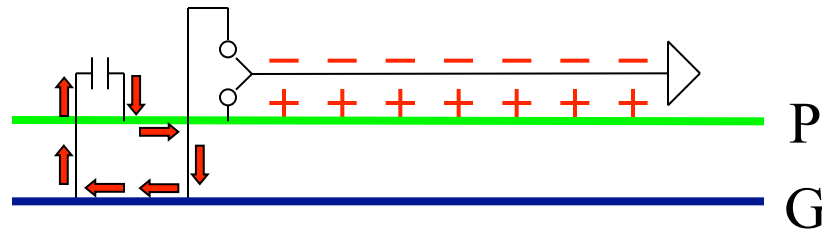
# !®: Common Misconceptions

- Current returns through ground but not power!?





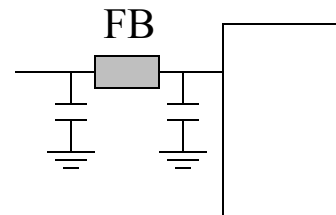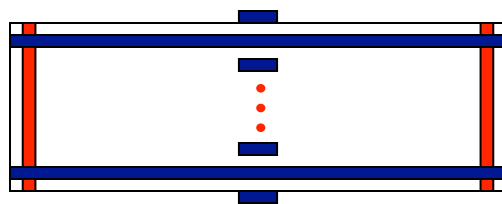- Ground and power planes are interchangeable!?
  - **Ground is connected to chassis, but not power.**
  - **Power isolation breaks the symmetry.**



# I®: Common Misconceptions


- Overlook horizontal return path!?

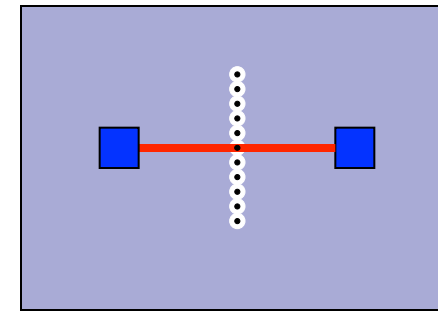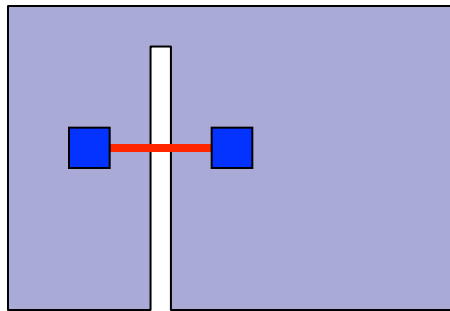



- Traces crossing plane cuts
  - **Avoid ground plane cuts.**
  - **Route around plane cuts.**
  - **Use stitching capacitors.**
- Overlapping via antipads
  - **Stagger vias.**
  - **Space vias apart.**
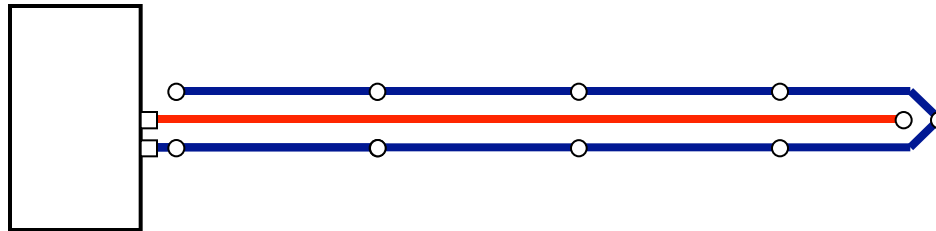
# I<sup>®</sup>: Common Misconceptions

- Overlook vertical return path!  
— **Trace to Plane**




- **Plane to Plane**

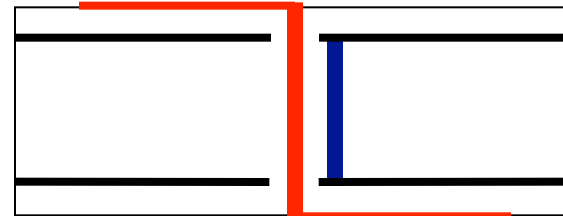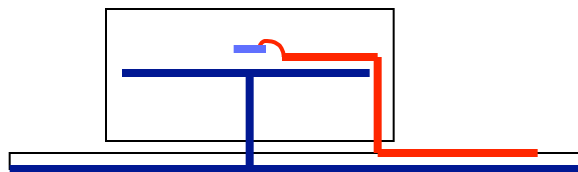

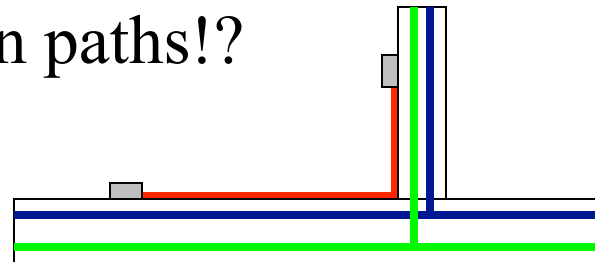
# I<sup>®</sup>: Common Misconceptions

- Overlook cross-board return paths!?
  - **Avoid discontinuity.**
  - **Provide capacitors.**




- Overlook off-board return paths!?


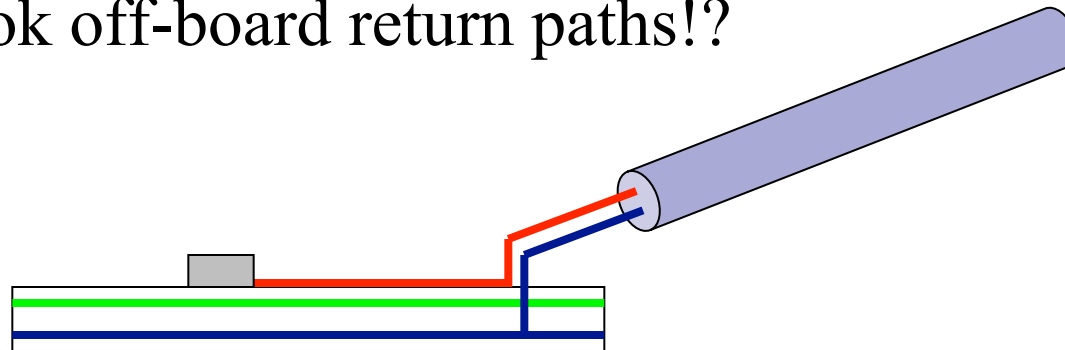

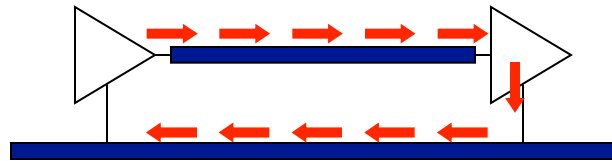
# I<sup>®</sup>: Common Misconceptions

- Current flows in loops.
  - **Think of signal path and return path separately!?**




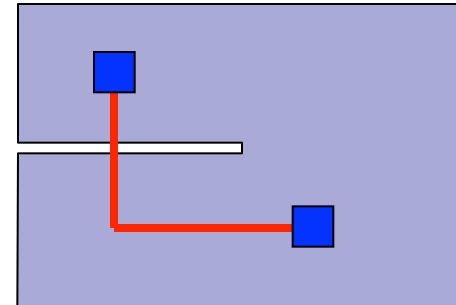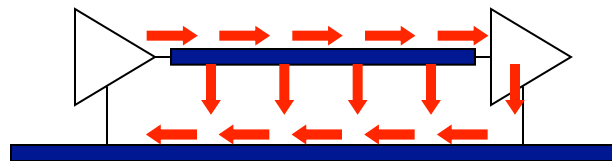- **Current flows in loops, but not this way.**
- **Current flows in pairs!**
  - Signal and return go hand-in-hand.




## I<sup>®</sup>: Exercise

- Trace out the current return path.

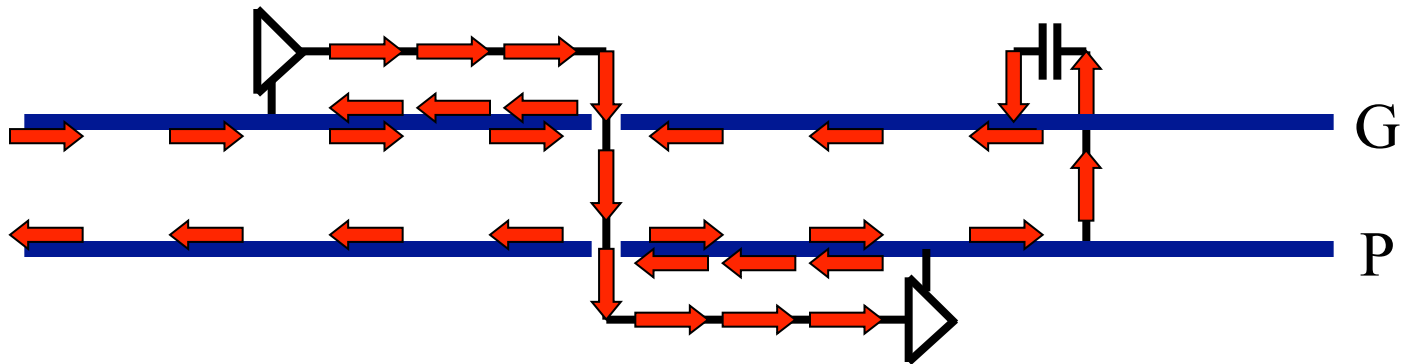

## I<sup>®</sup>: Exercise


- Trace out the current return path.

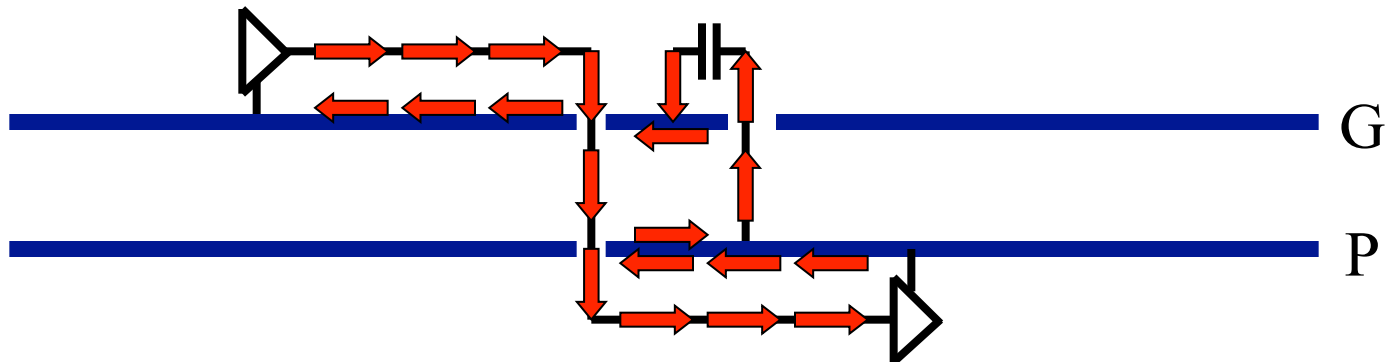




## I<sup>®</sup>: Exercise

- Trace out the current return path.

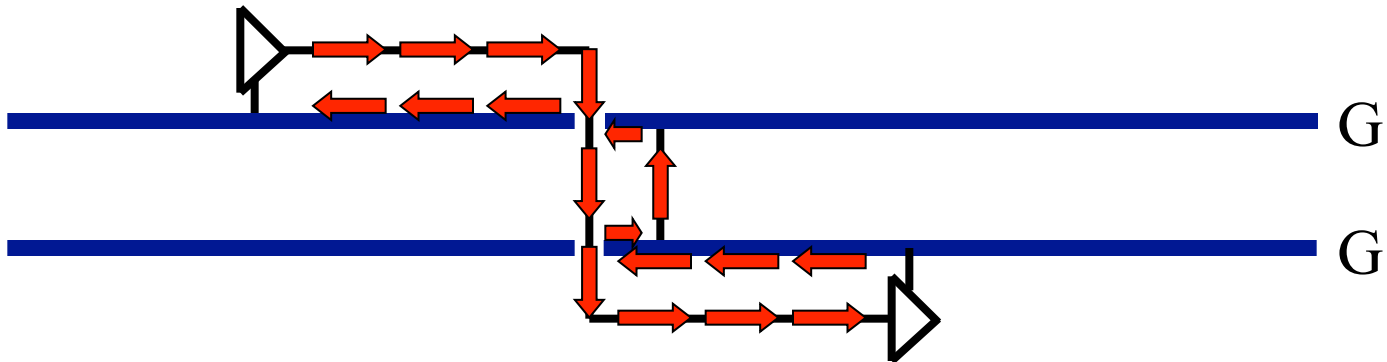
 
# L: How do we control them?

- $L \rightarrow$  Signal Ringing
  - **Small loop (adjacent return, short, wide).**
- $M_{21} \rightarrow$  Crosstalk (Inductive Coupling)
  - **Separation, return proximity, twisting, shielding.**
- $L_G (M_G) \rightarrow$  Ground Drop  $\rightarrow E_{CM}$ 
  - **Coaxial, stripline, microstrip.**
  - **Small H, large W, away from edge, guard traces.**
- $L_C \rightarrow$  Decoupling
  - **Small loop (short wide traces, adjacent vias).**
  - **Use multiple capacitors and spread them out.**
- $M_C \rightarrow$  Filtering
  - **Minimize M (eliminate stub, short trace to ground).**





# I<sup>®</sup>: How do we control them?

- At kHz:  $R_G \gg j\omega L_G$ 
  - **Low-level analog or high-level noisy subsystems**
    - Single-point grounding prevents common-Z coupling.
- At MHz/GHz:  $R_G \ll j\omega L_G$ 
  - **Horizontal return**
    - Use ground planes/grids instead of ground traces.
    - Avoid traces crossing plane cuts.
  - **Vertical return**
    - Provide adjacent return pins for noisy or susceptible pins.
    - Provide adjacent vias, stitching capacitors as return bridges.
    - Provide sufficient vias for guard traces.

# L & I®: How do we identify problems?

<b>Options</b>	<b>Pros</b>	<b>Cons</b>
Fix when Fail	Less design time	Risks: time, cost, ...
<b>Layout Review</b>	Identify problems early	Labor intensive
<b>Layout Checking Tool</b>	Identify problems quickly Less labor intensive	Report 100's of violations Require expertise & time to identify critical violations
<b>Automated &amp; Customized Layout Checking Tool</b>	Identify problems quickly No setup required Report critical violations	Require automation and customization development



# Summary

- L & I<sup>Ⓡ</sup> affects signal quality, crosstalk and EMI.
- Inductance (L)
  - **Forget self inductance.**
  - **Think loop inductance and mutual inductance!**
  - **Think return proximity!**
- Current Return Path (I<sup>Ⓡ</sup>)
  - **Low f: Current spreads out as  $R_G \gg j\omega L_G$ .**
  - **High f: Trace out I<sup>Ⓡ</sup> to identify discontinuities.**