
Designing with EMC in Mind

How to Apply Shielded Cables to Solve More Problems than You Create

Thomas A. Jerse





The Citadel
Charleston, SC

Santa Clara Valley Chapter – 5/11/10

The Job

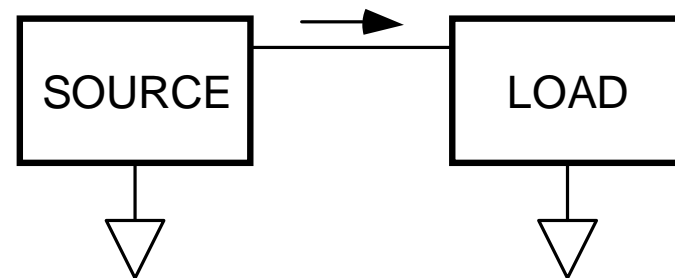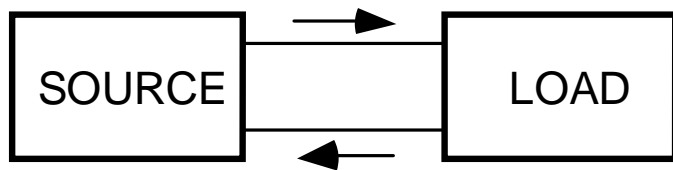Designing for electromagnetic compatibility (EMC) is primarily the orchestration of return current flow.




Topics

- **Return Current Behavior**
- **Cable shields**
- **Cable grounding**
- **Ground-loop and common-mode coupling**
- **Common-mode emissions from cables**
- **Transfer impedance**
- **Bringing cables through shield walls**

The Key

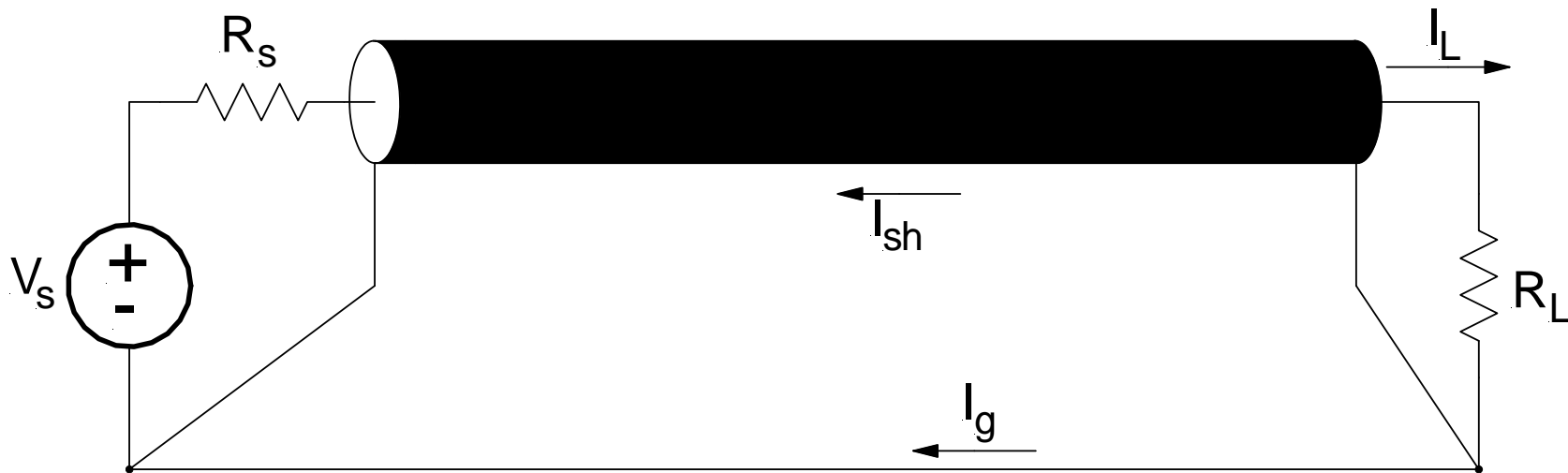The successful application of cables depends on a knowledge of the return current flow.



The Rules

- **At low frequencies, the return current apportions itself among paths according to the resistances involved.**
- **At high frequencies, the return current apportions itself among paths according to the inductances involved.**

The Good News

- The return current apportions itself in such a way that it incurs the smallest voltage drop possible on its way back to the source.
- That is, the return current seeks the minimum impedance.


$$\vec{E} = -\nabla V \qquad P = \frac{1}{2} \Re \{ VI^* \}$$

In Other Words


- At low frequencies, current apportions itself so that the net resistance seen in the aggregate of the paths it travels on the way back to the source is the smallest available.
- At high frequencies, current apportions itself so that the net inductance seen in the aggregate of the paths it travels on the way back to the source is the smallest available.

$$\psi = LI$$



Cable - One Return Path

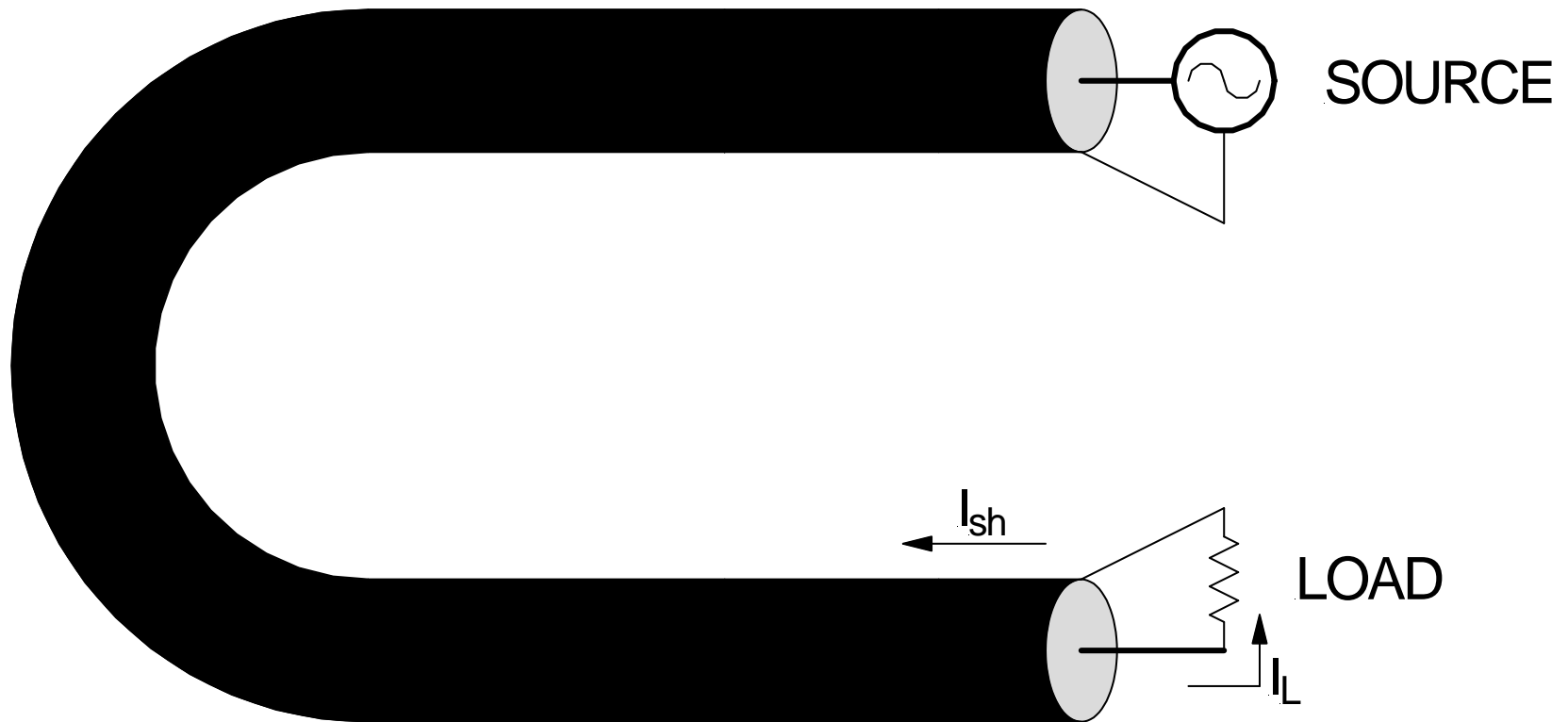


Cable - Two Return Paths

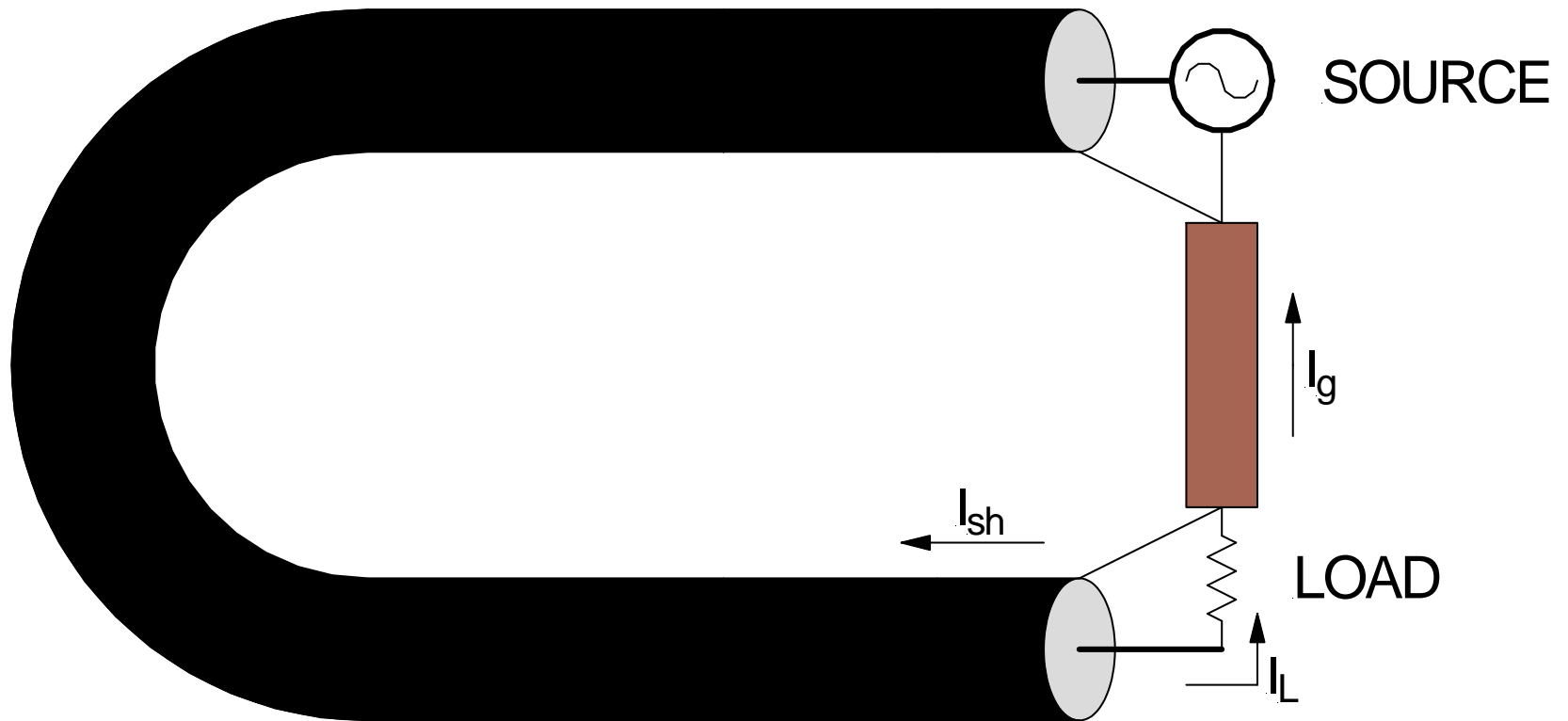


Current Distribution

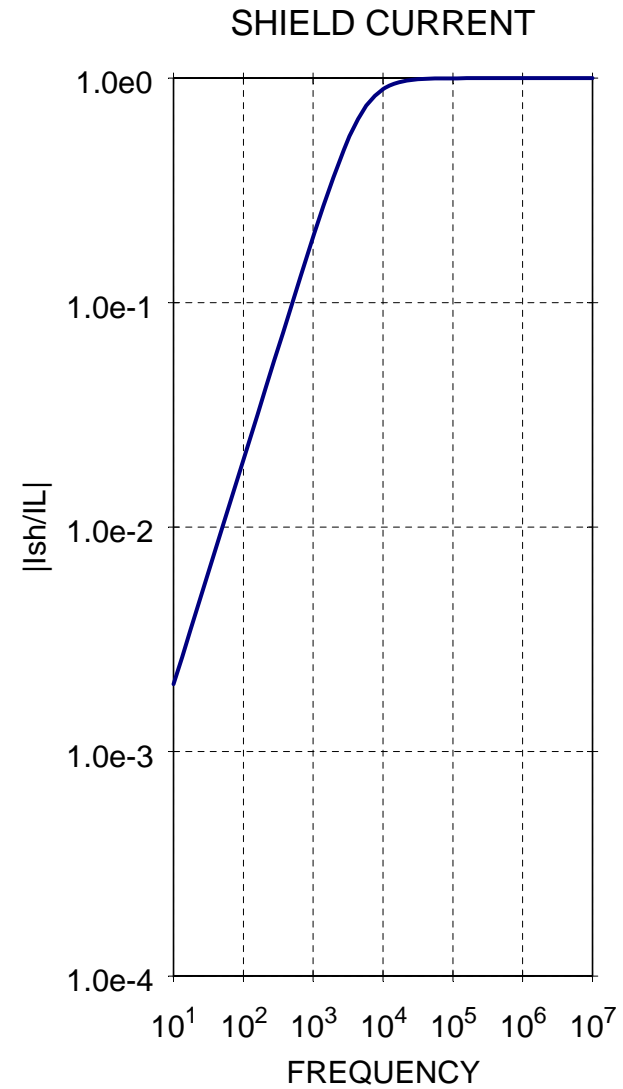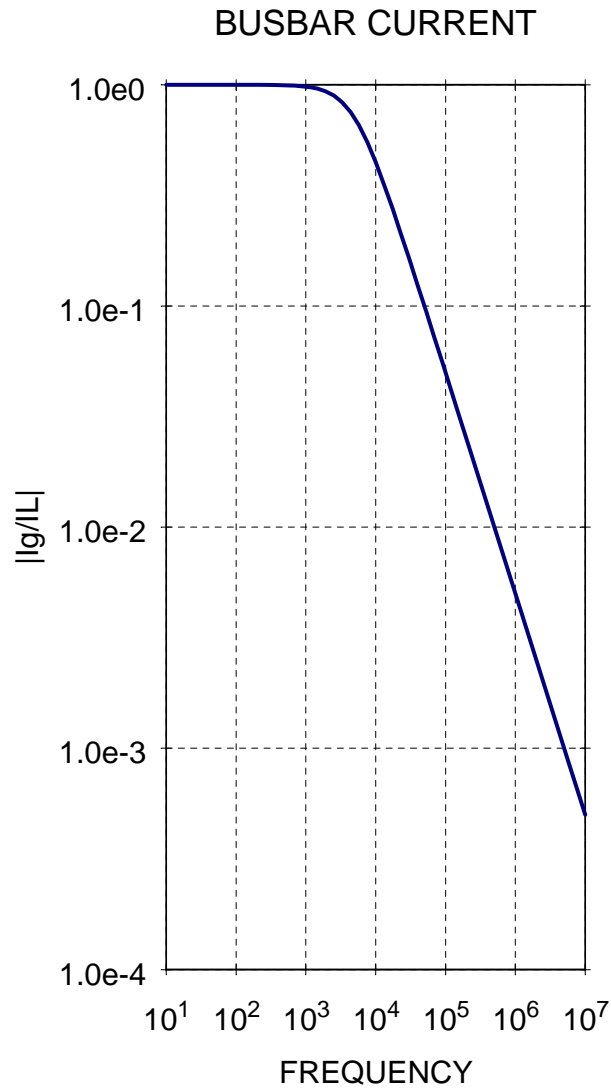


Shielded Cable

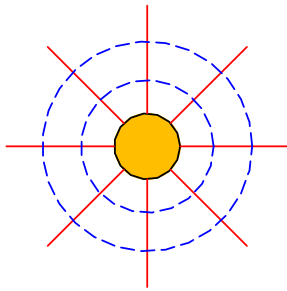

NO SHIELD

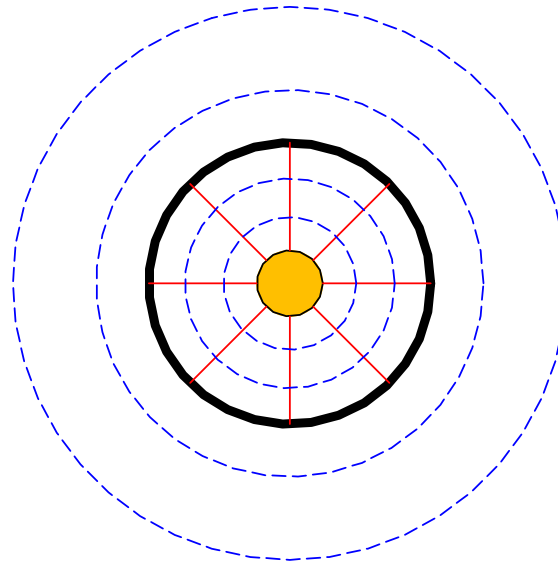


SHIELD GROUNDED
AT ONE END

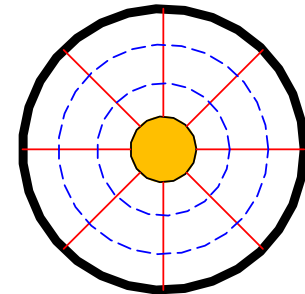


SHIELD CARRYING
RETURN CURRENT

Gauss's Law

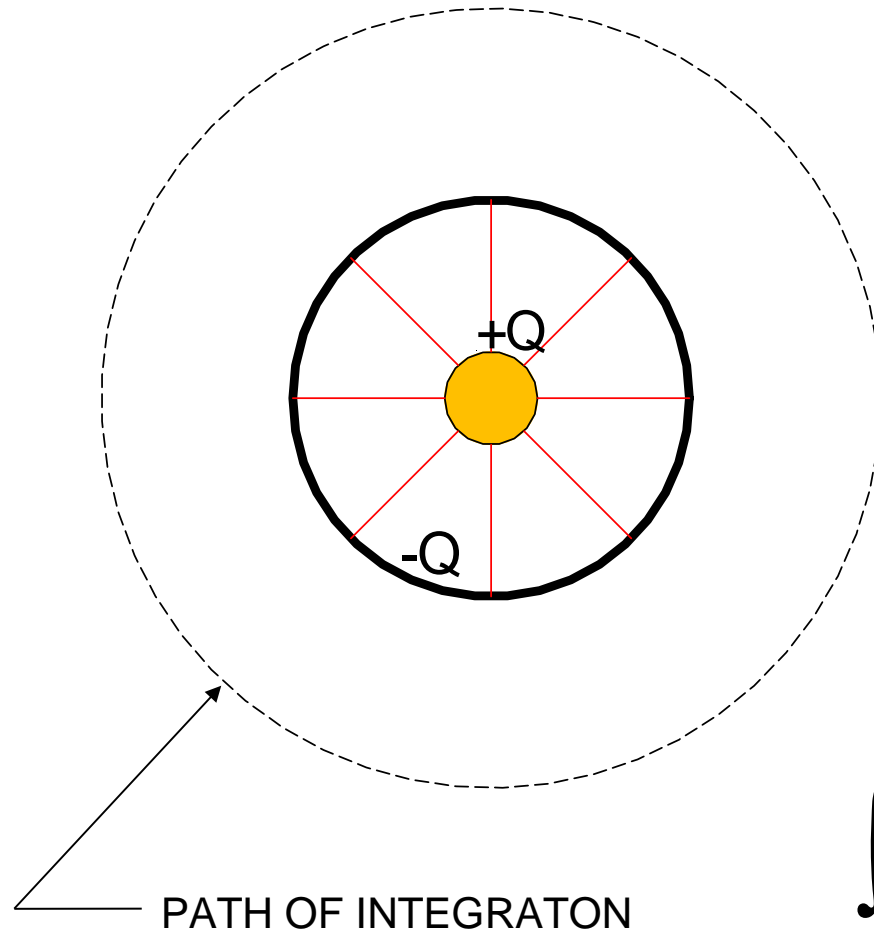


$$\iint \epsilon \vec{E} \cdot d\vec{S} = Q_{\text{enclosed}}$$

Ampere's Law

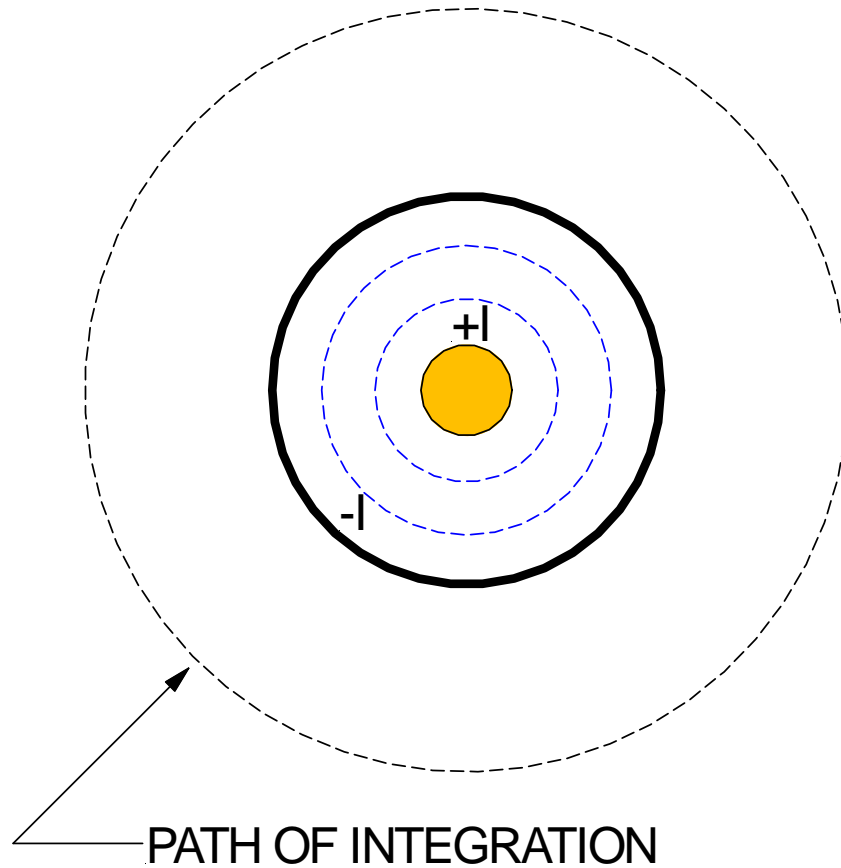


$$\oint \vec{H} \cdot d\vec{\ell} = I_{\text{enclosed}}$$

Return Current Flow

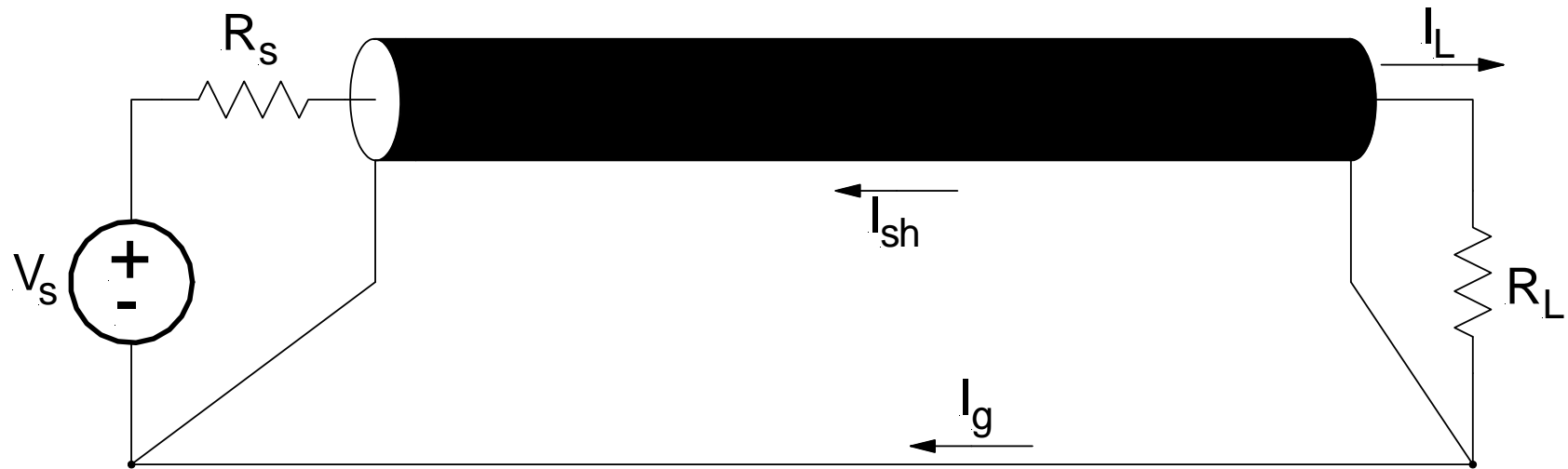

WHERE DOES THE RETURN CURRENT FLOW?


Analysis of Shield Cutoff

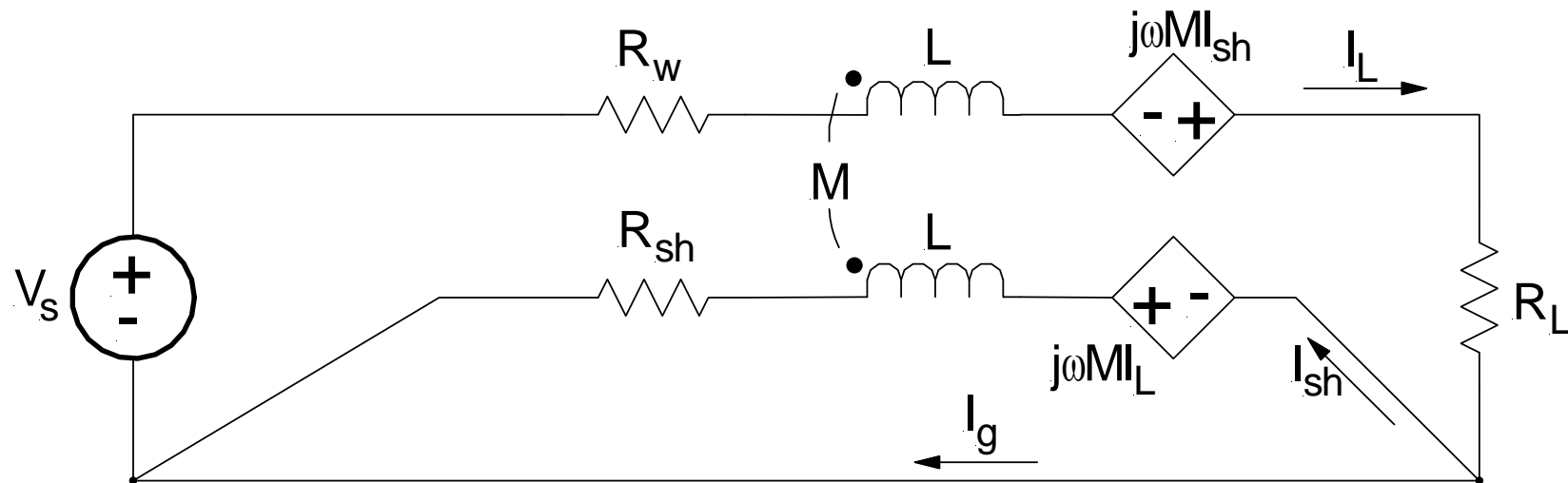

$$I_{sh} R_{sh} + j\omega L I_{sh} - j\omega M I_L = 0$$

$$\frac{I_{sh}}{I_L} = \frac{j\omega M}{R_{sh} + j\omega L}$$

Magnetic Coupling

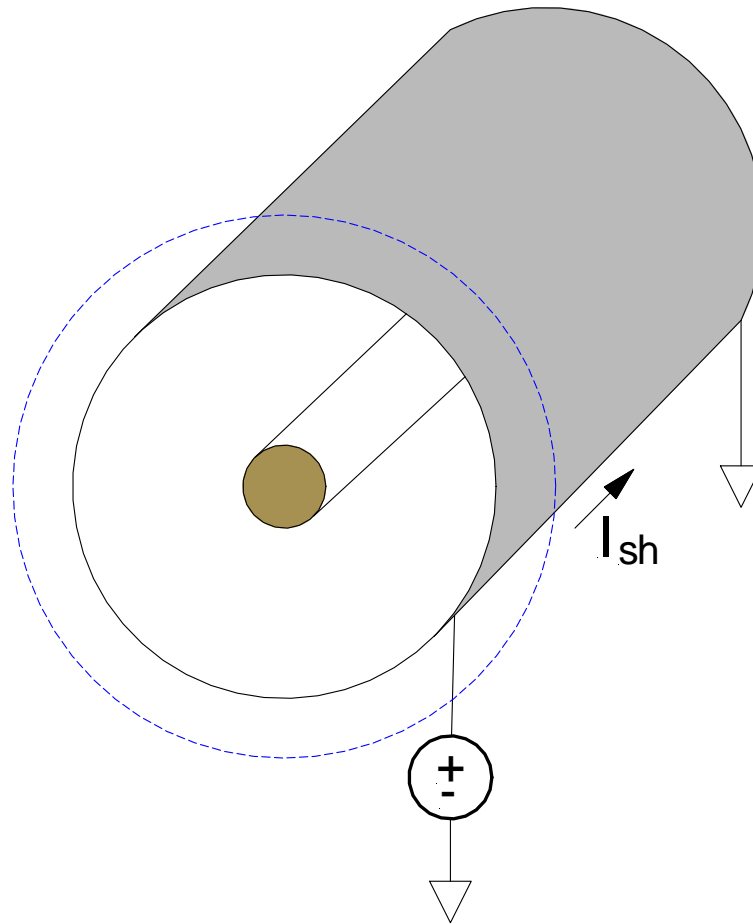


$$M = L$$

Shield Current


$$\frac{I_{sh}}{I_L} = \frac{j\omega L}{R_{sh} + j\omega L}$$

SHIELD CUTOFF FREQUENCY

$$f_c = \frac{R_{sh}}{2\pi L}$$

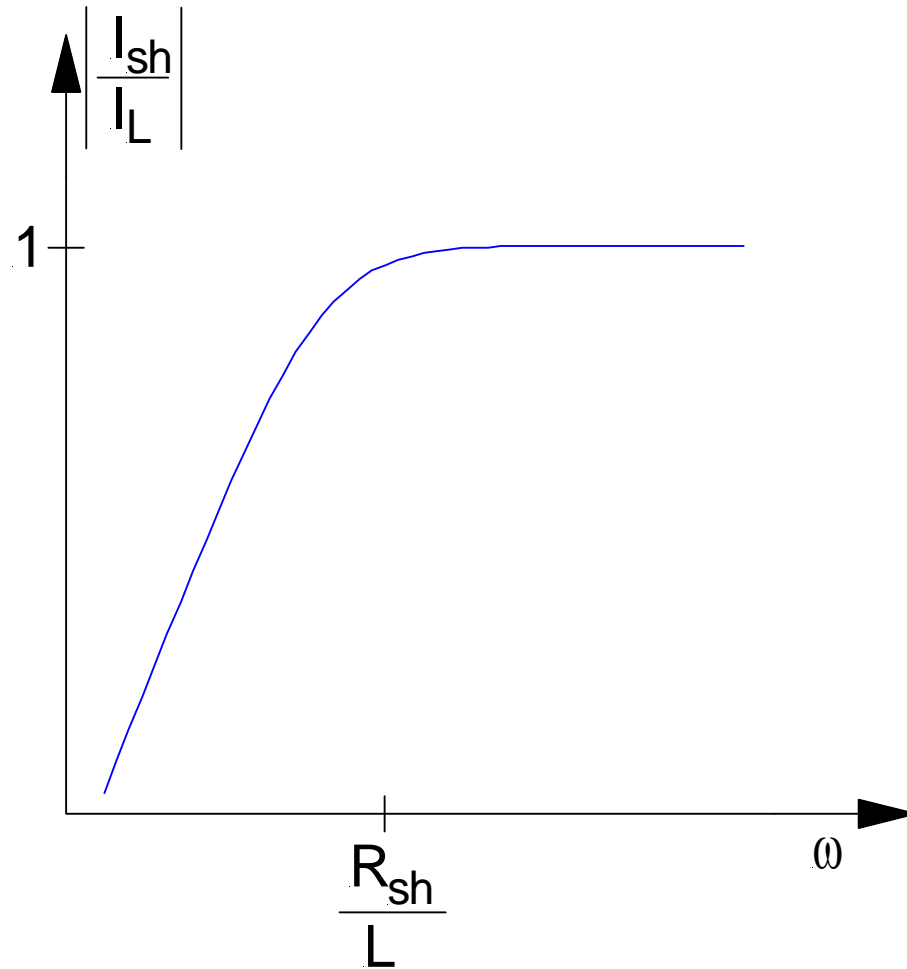


Poor Shield Grounding

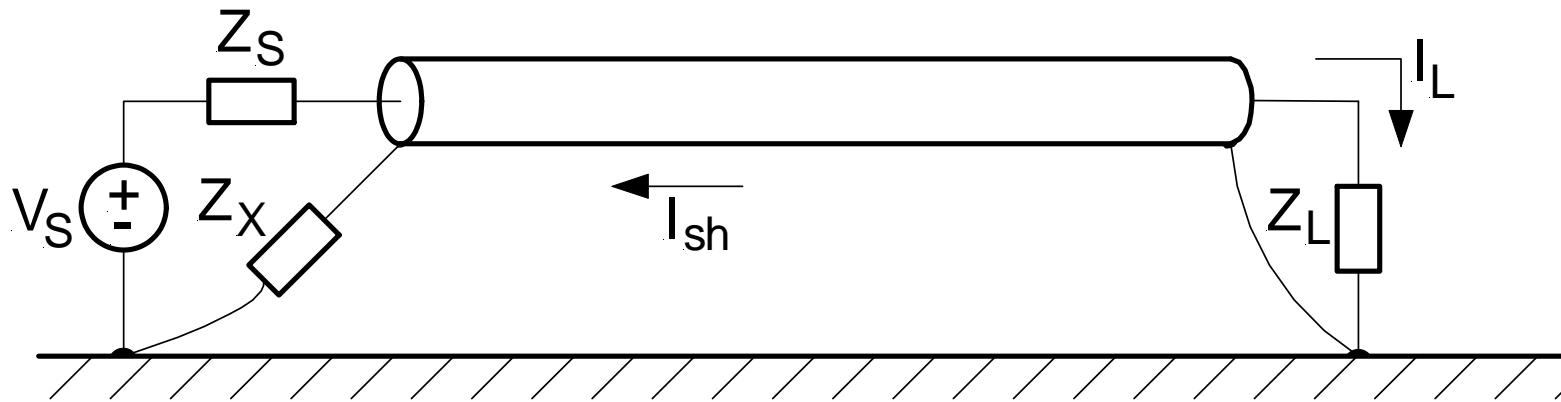


$$Z_x = R_x + j\omega L_x$$

$$\frac{I_{sh}}{I_L} = \frac{j\omega L}{R_x + R_{sh} + j\omega(L + L_x)}$$


Shield Current

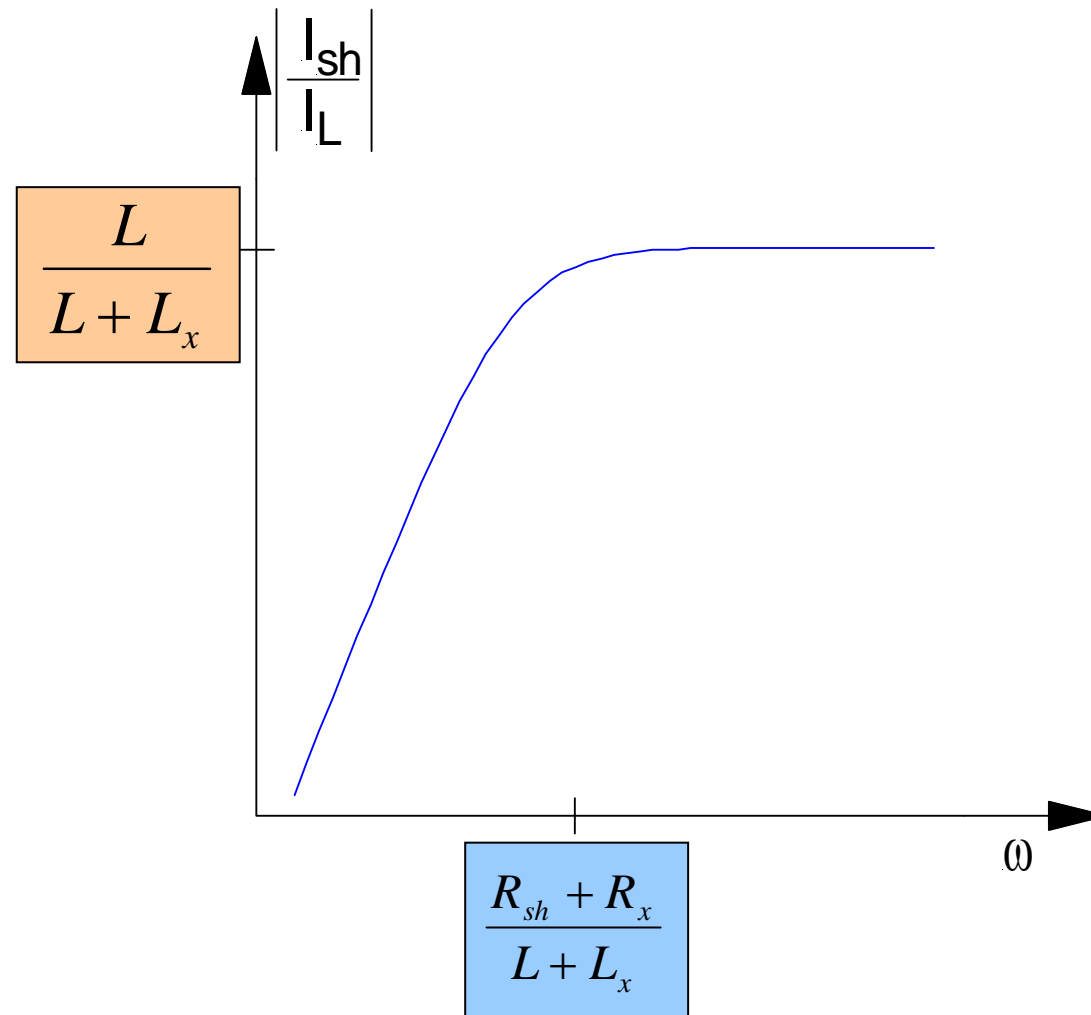


Pigtail

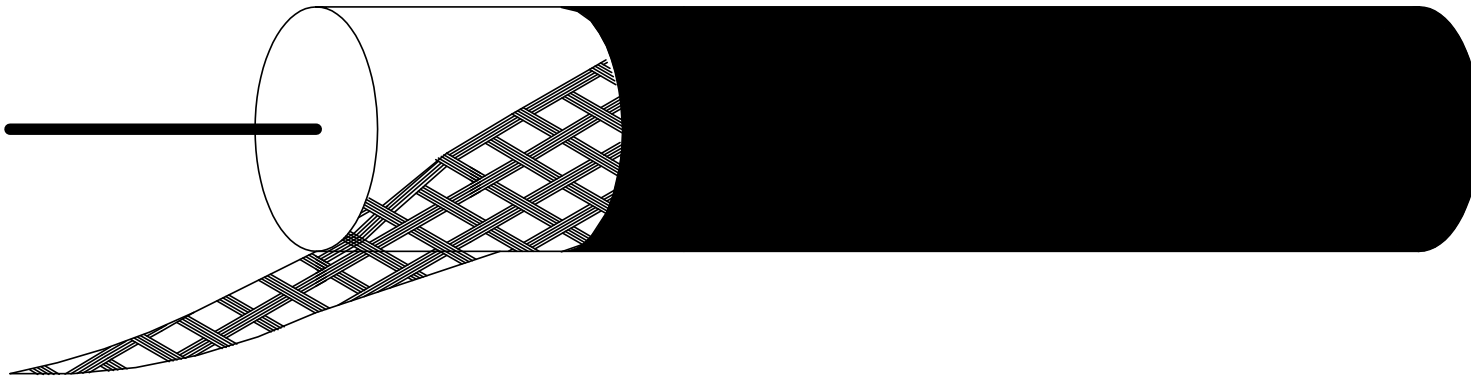

Z_x

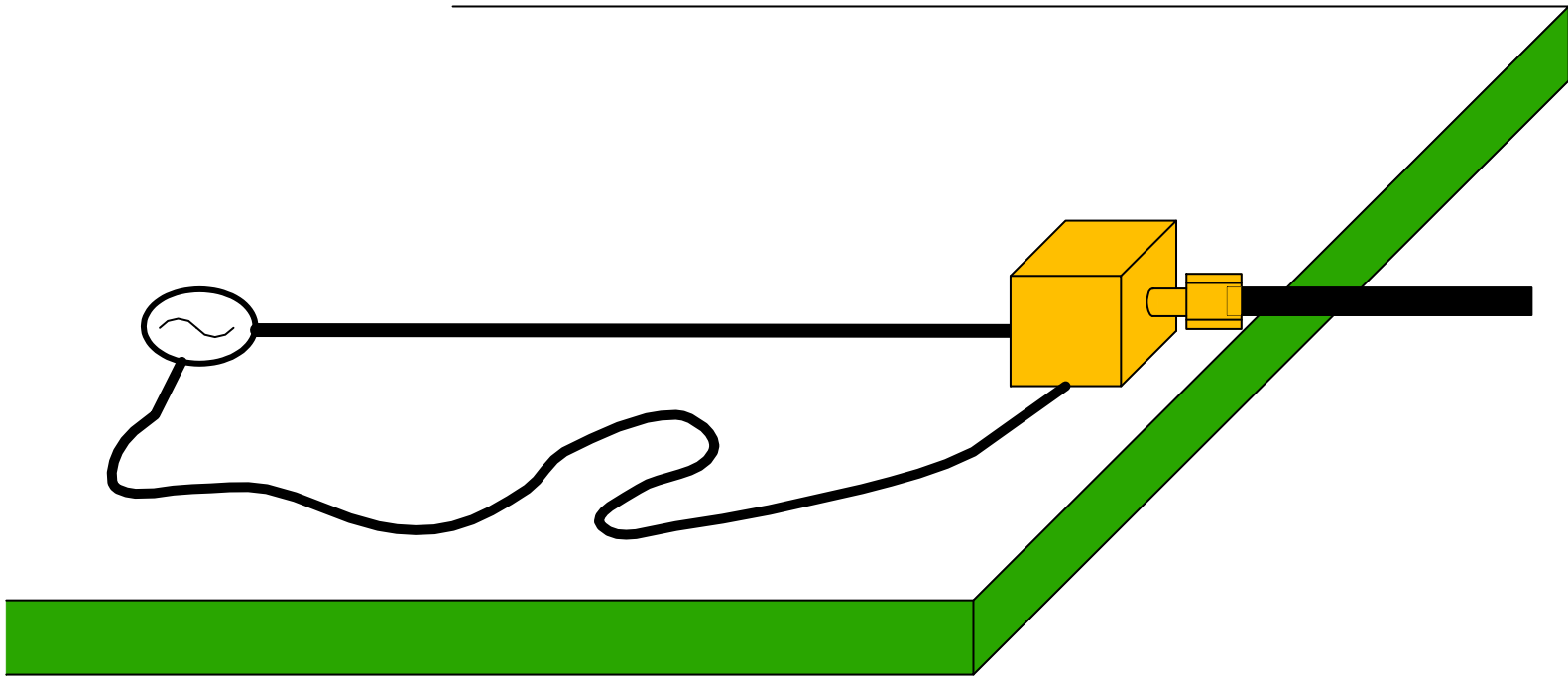


Minimum Z_x

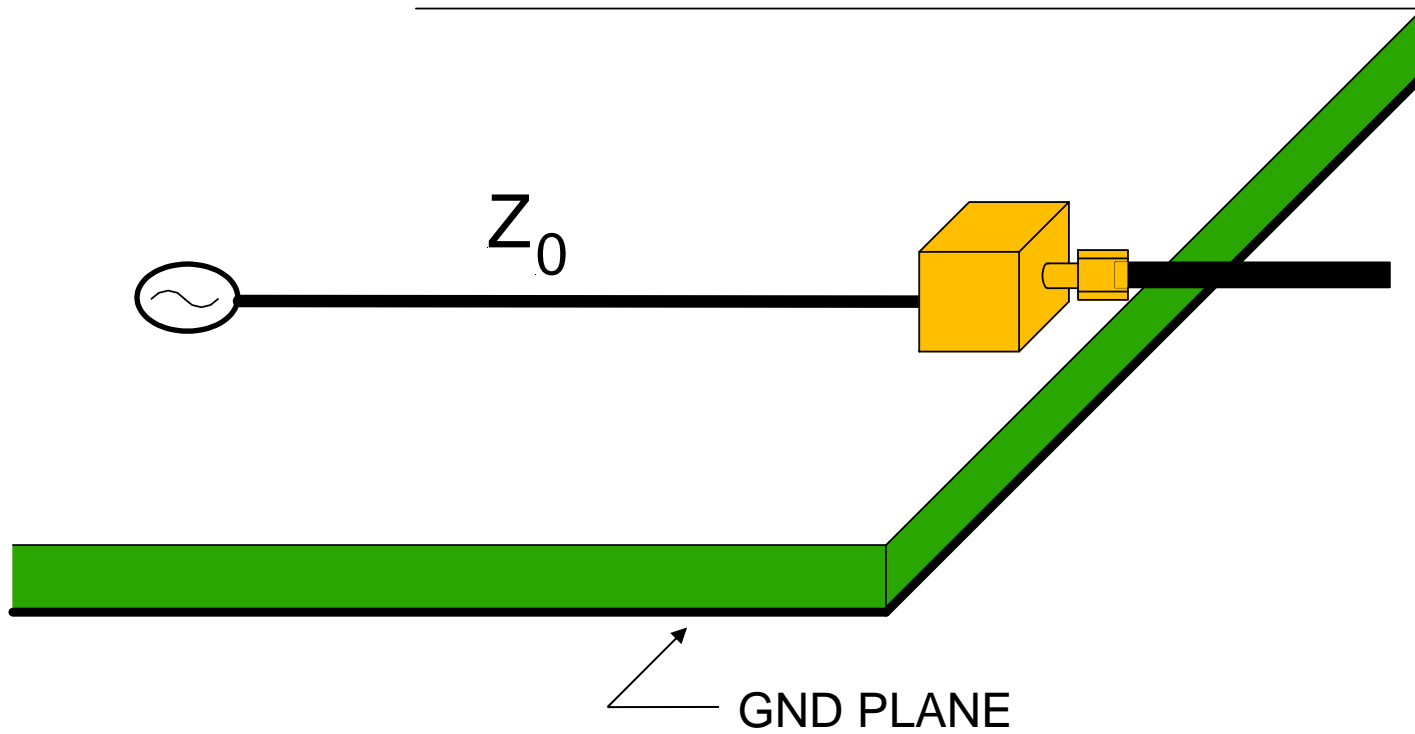


Common-Mode Radiation

- In a system, cables are often the principal radiators of CM emissions.
- Sources of CM current
 - Poor cable grounding
 - Connection to a noisy ground


Differential Mode Radiation

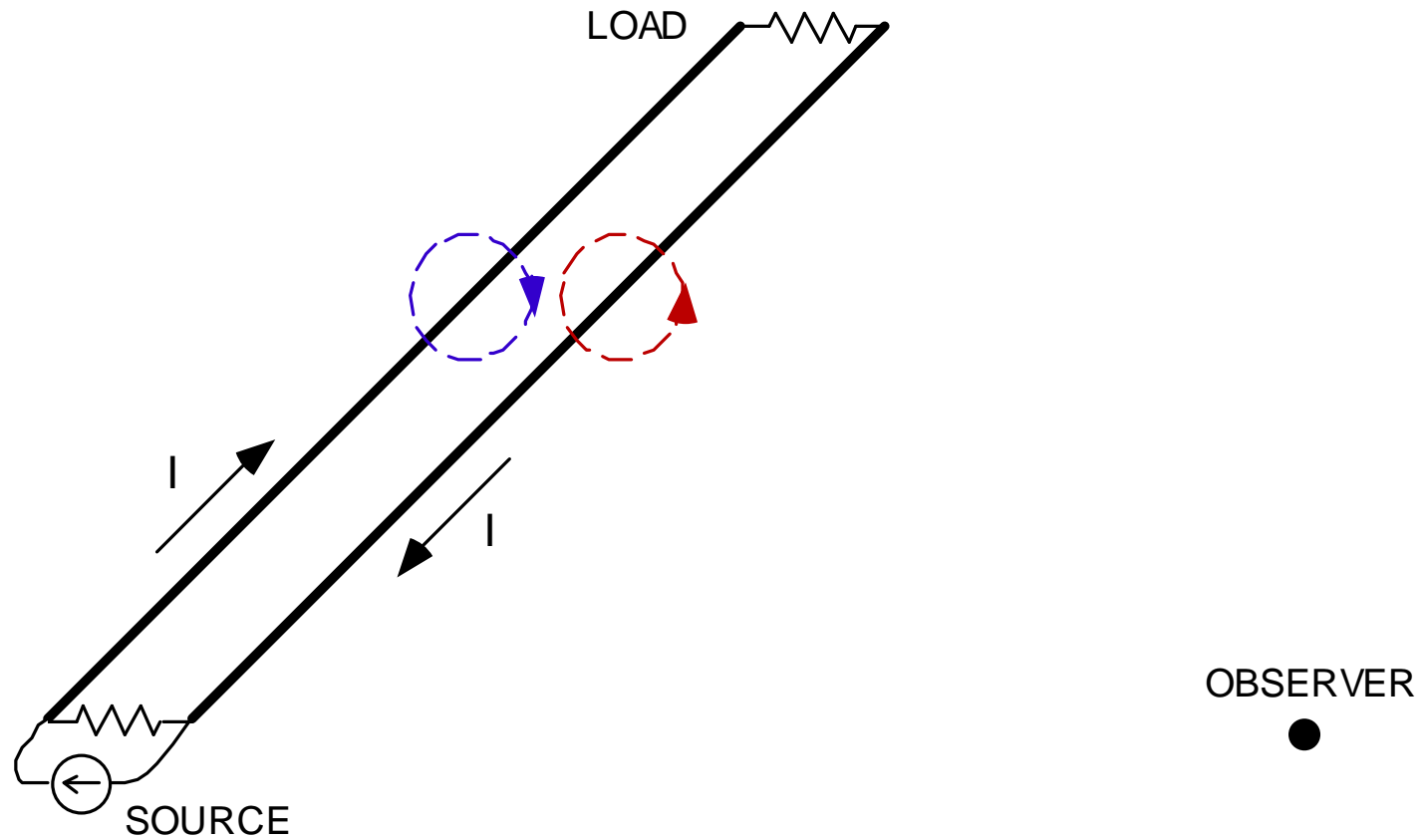

Common-Mode Radiation

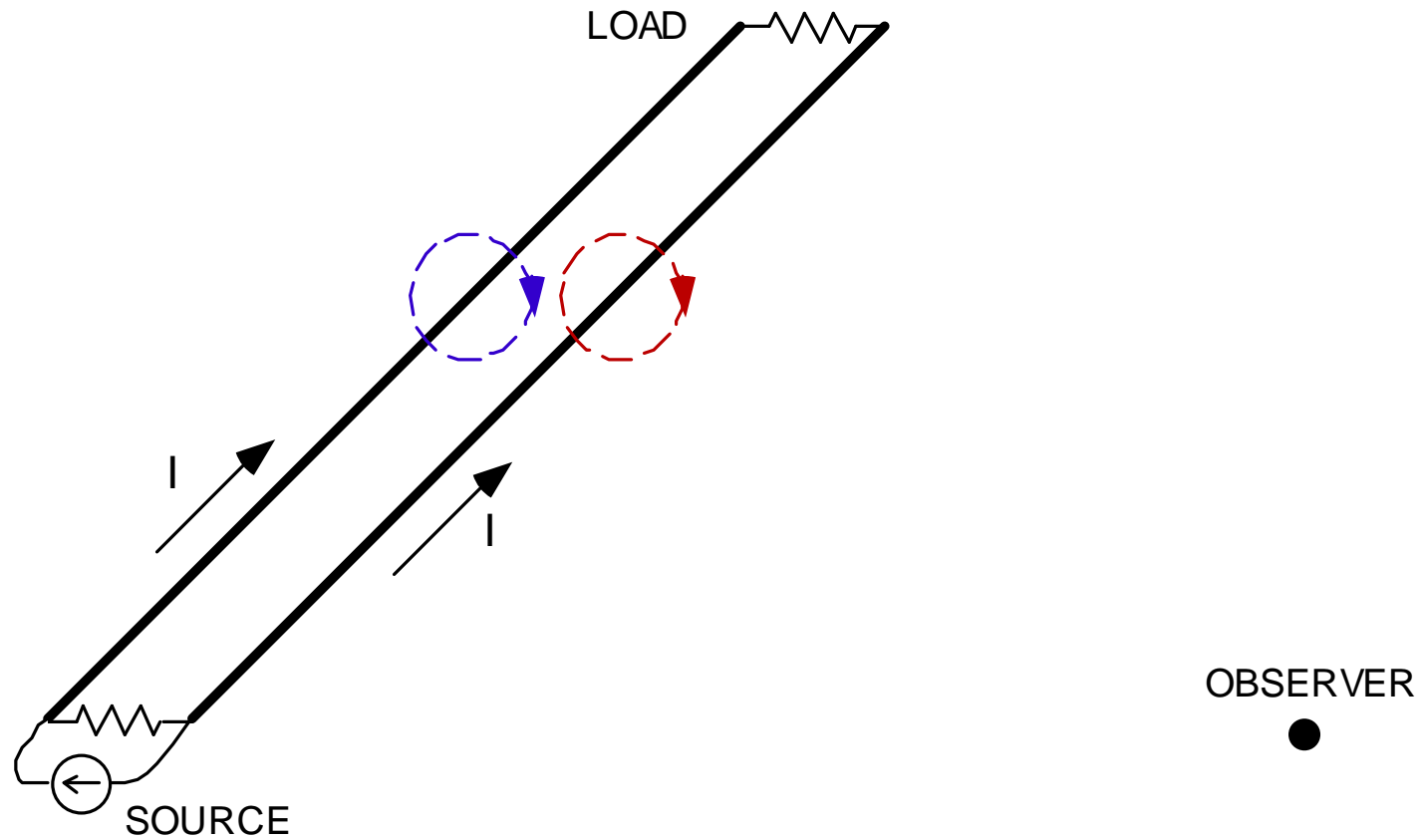

Poor Shield Grounding

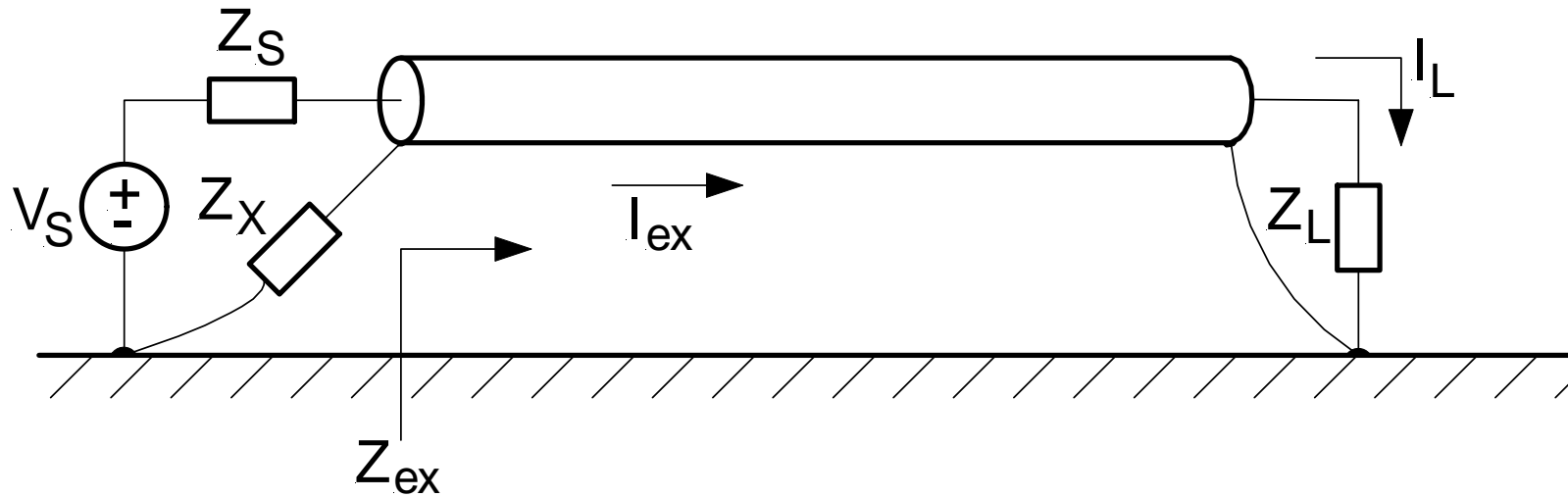

I_{ex} IS A COMMON-MODE CURRENT.

At High Frequencies


- The skin effect causes the coax to behave like a triax.
- I_{ex} will flow on the outside of the shield.

Skin Effect


- Describes tendency of high frequency current to ride on conductor surface
- Skin depth, δ , represents distance where current density is attenuated by e^{-1} .

$$\delta = \sqrt{\frac{1}{\pi f \sigma \mu}}$$

Separation of Currents

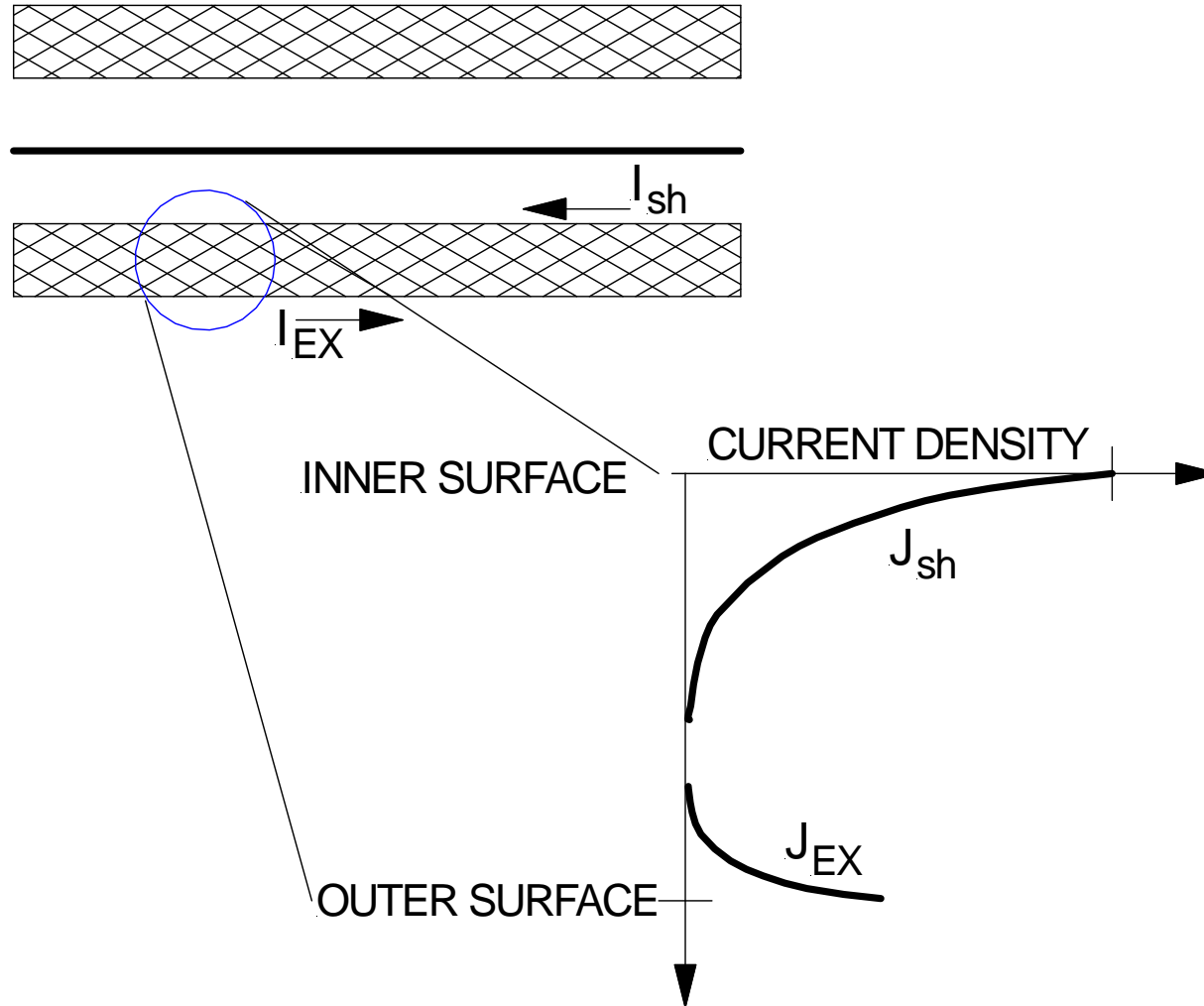


80-dB Separation Frequency

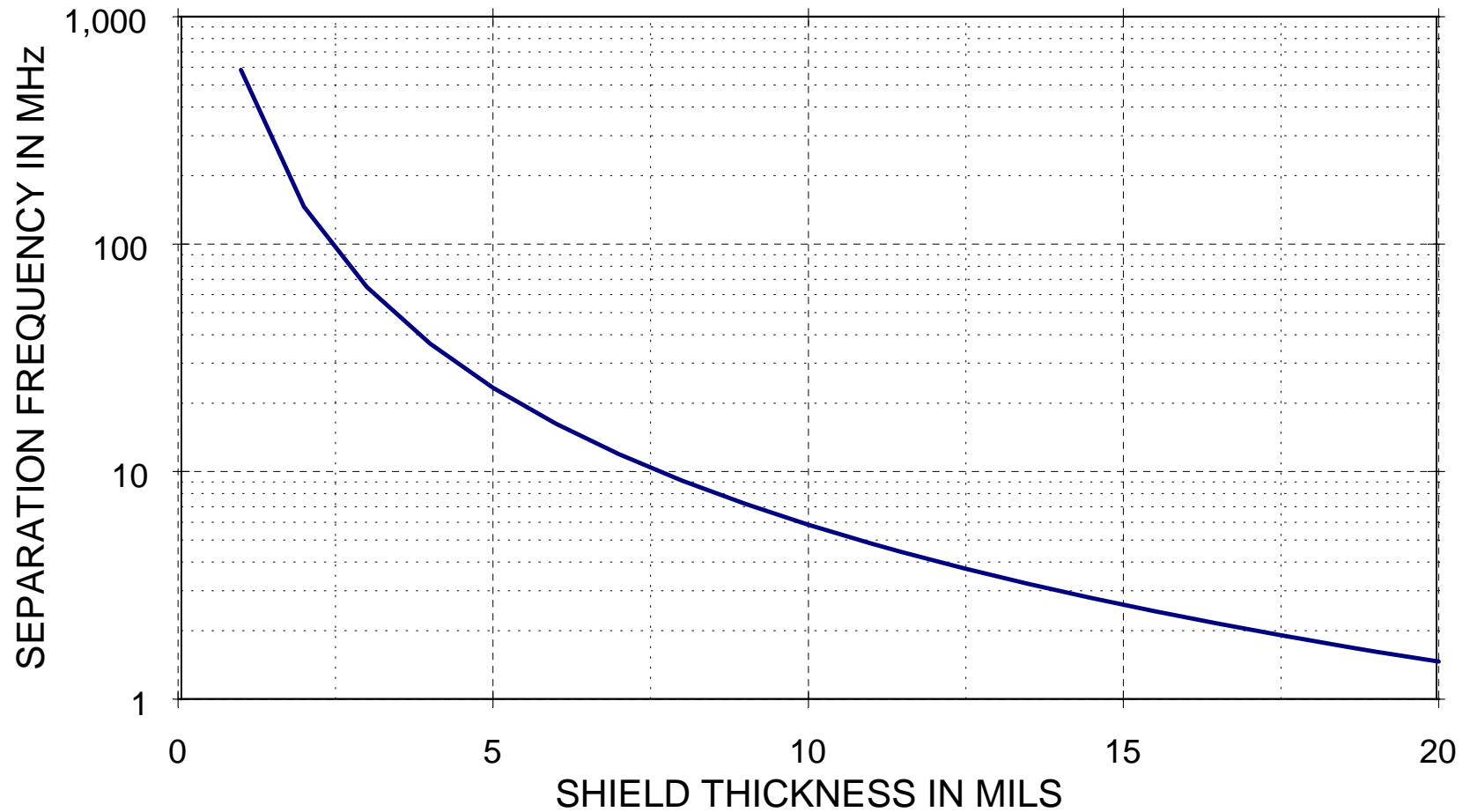

COPPER SHIELD

Poor Shield Grounding

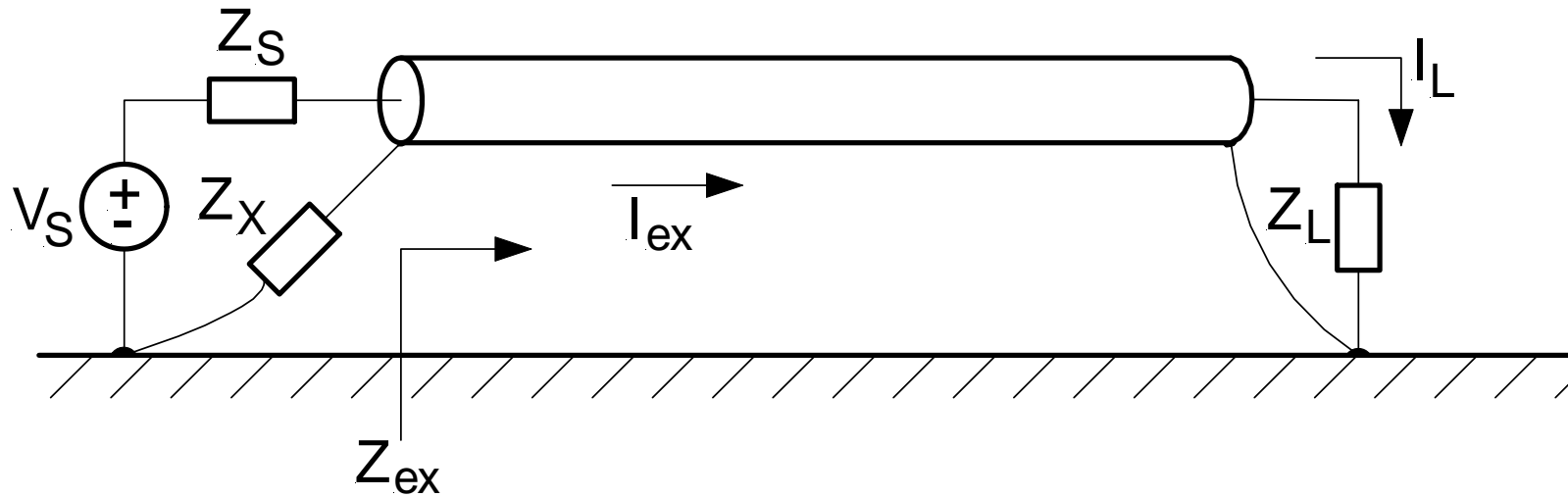


$$I_{ex} = I_L \frac{Z_x}{Z_x + Z_{ex}}$$

$$Z_{ex}$$

- **Function of frequency with numerous resonances.**
- **Depends on the cable layout, particularly its position with respect to any ground planes.**

FIX CABLES IN POSITION


Raising Z_{ex}

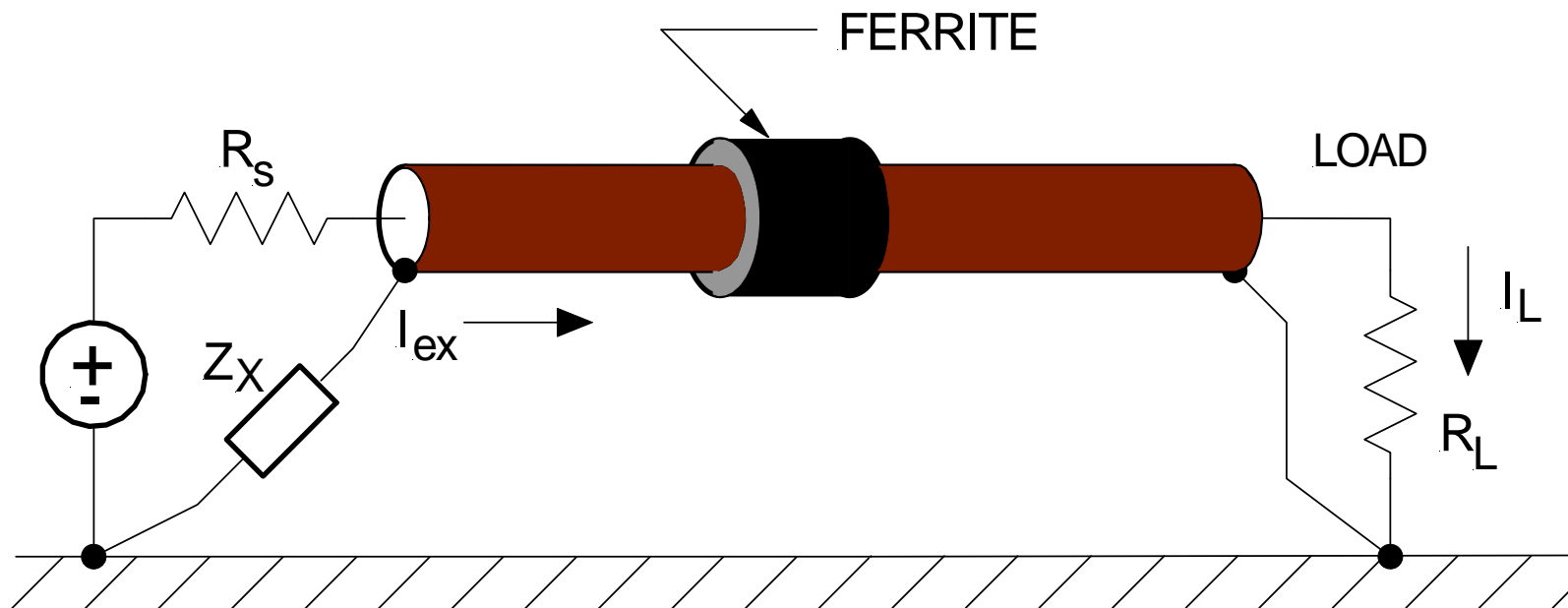

Differential Ground Voltage


- The ground potential at the two ends of the cable may differ.
- Symptom—noise voltage coupled across load
- Causes
 - Ground loop coupling
 - Common-mode coupling

Ground-Loop Coupling

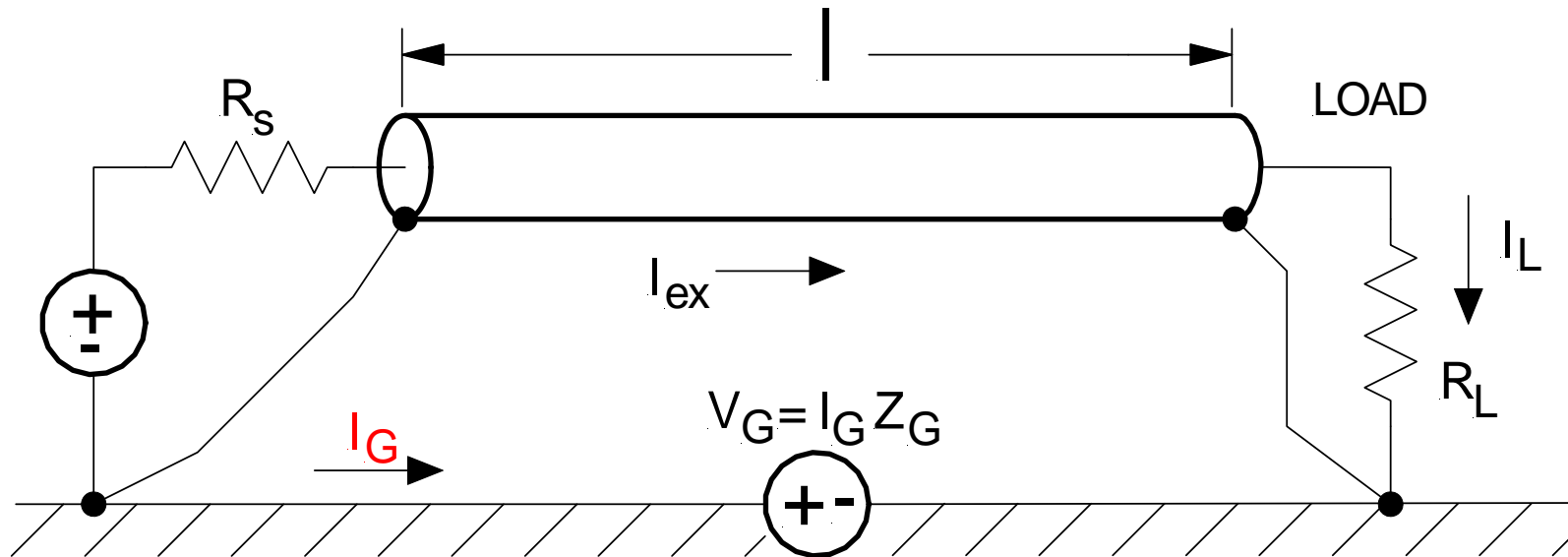


$$I_L = \frac{V_s}{(R_s + R_L) \left(1 + j\omega \frac{L}{R_{sh}} \right)}$$


Common-Mode Coupling

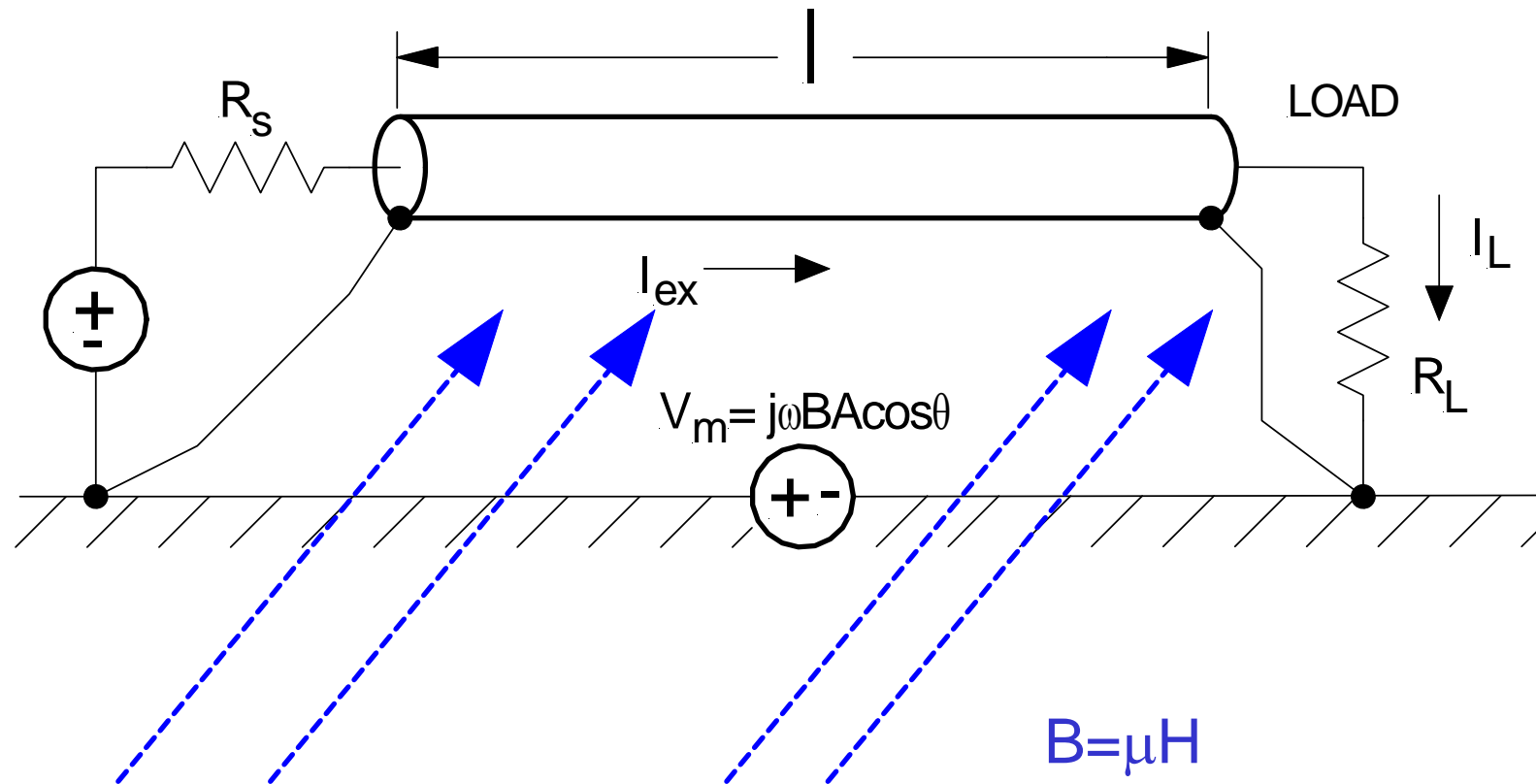


Common-Mode Choke

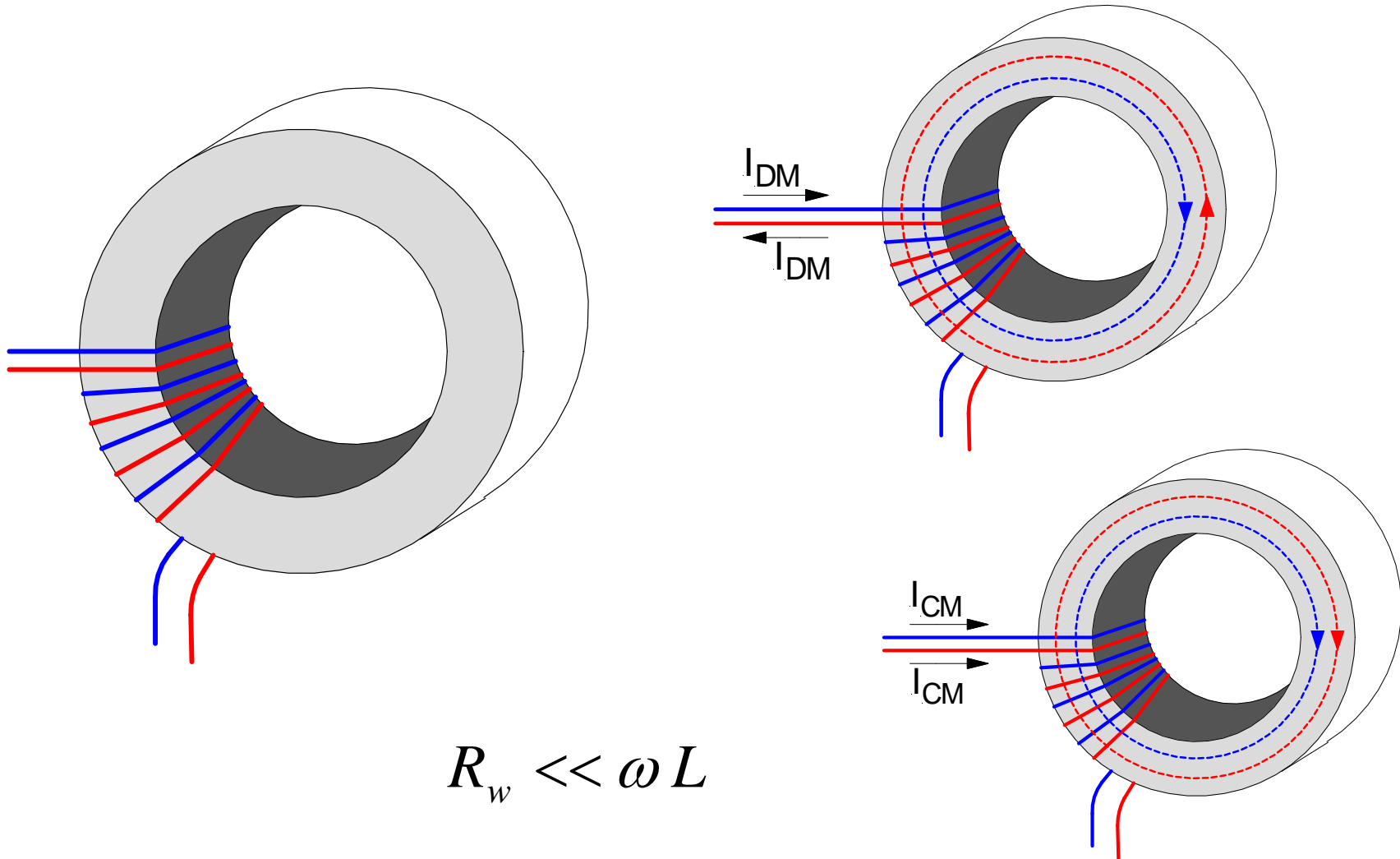


Shielded Twisted Pair

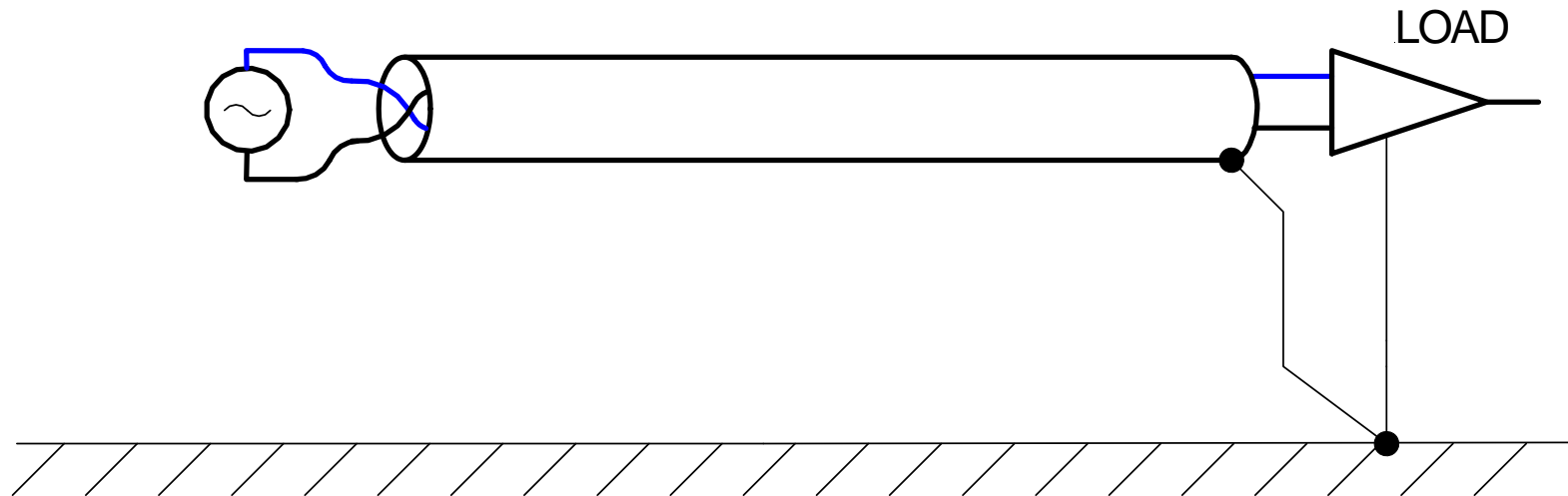

Differential to Common-Mode Conversion

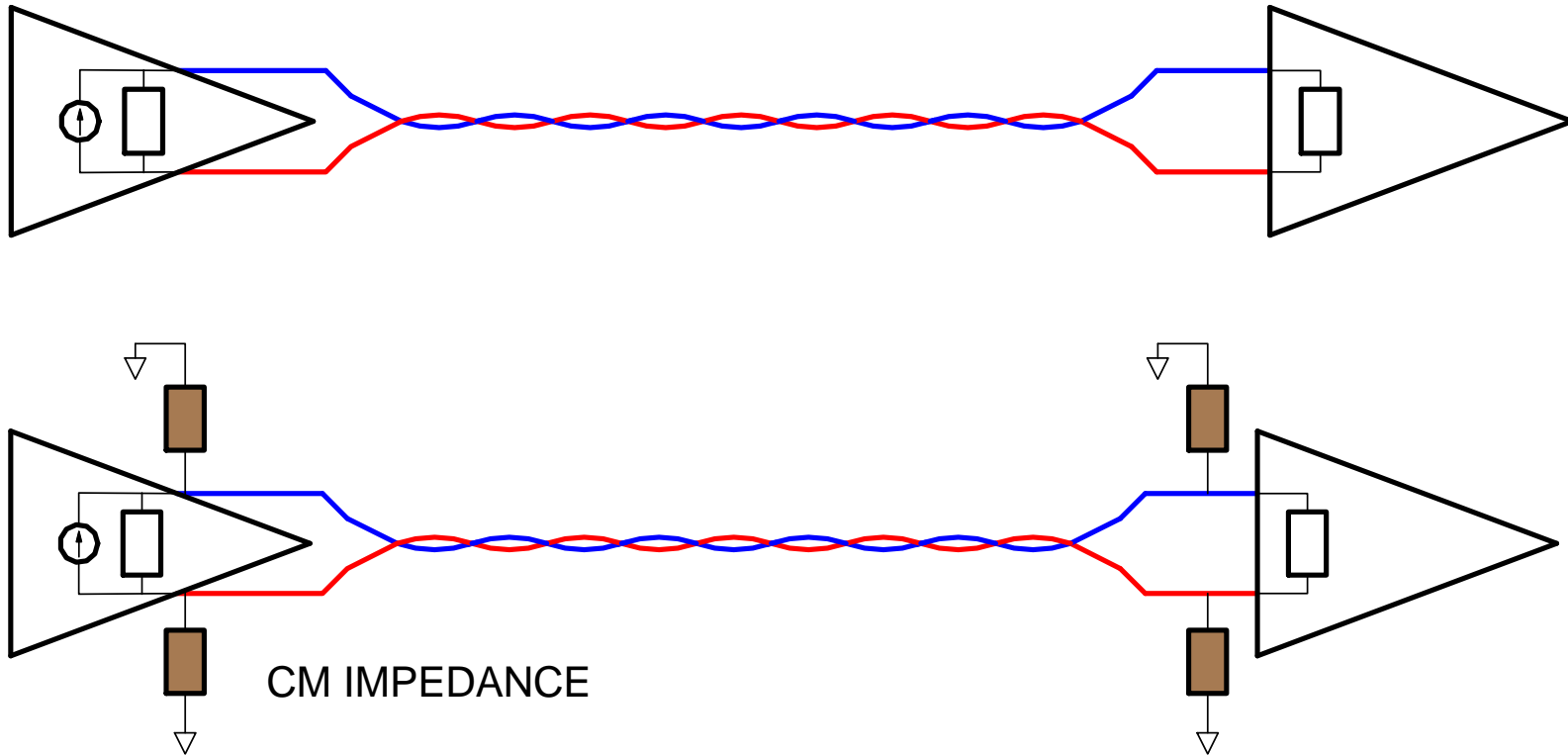


DM-to-CM Conversion

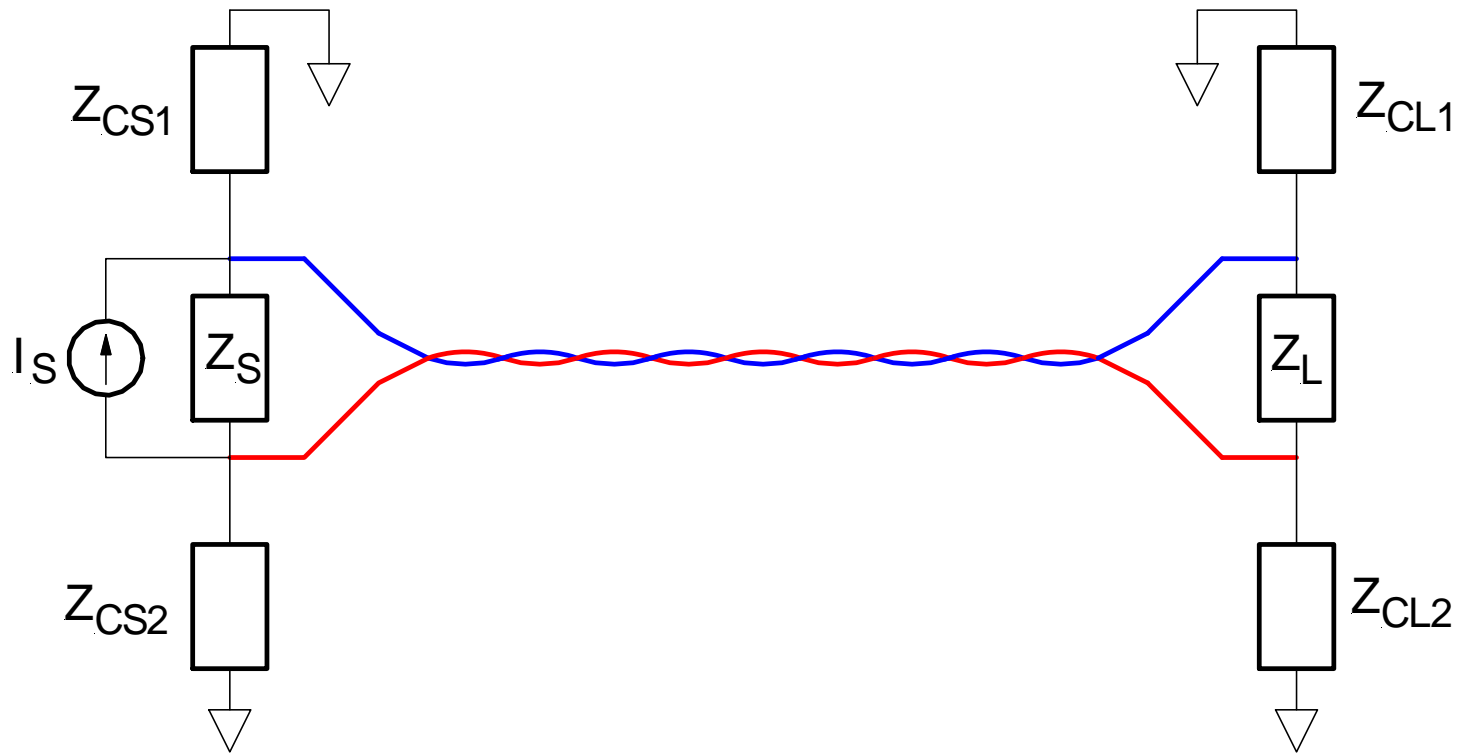



$$I_{CM} = 0 \quad \text{WHEN} \quad Z_{CS1} Z_{CL2} = Z_{CS2} Z_{CL1}$$

Cable Transfer Impedance

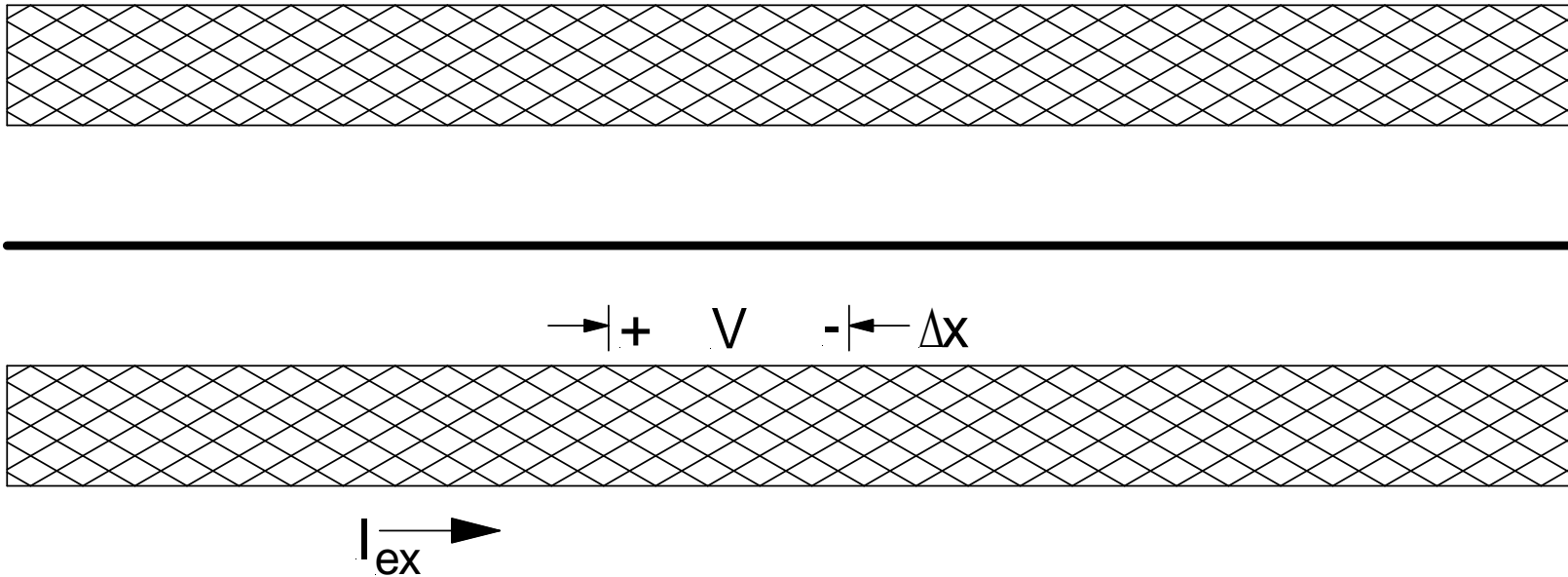

$$Z_T = \frac{V}{I_{ex} \Delta x}$$

Coupling Calculation

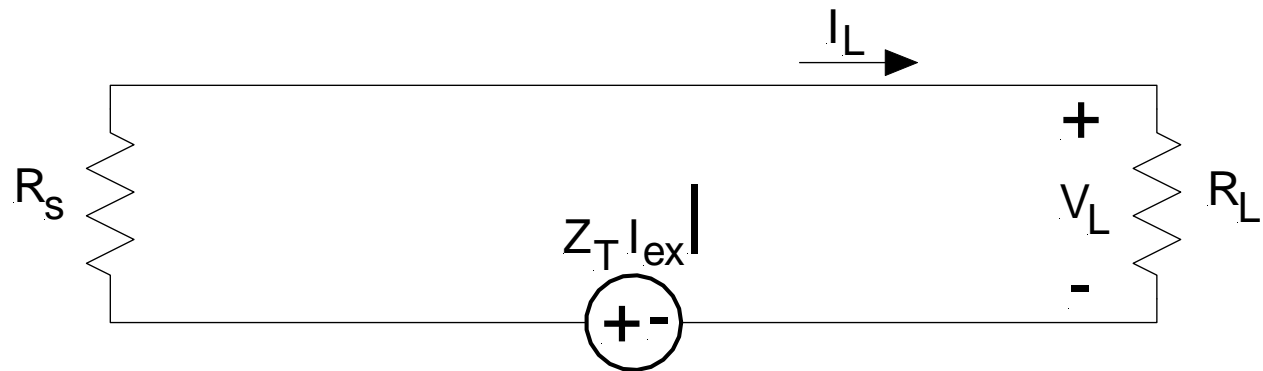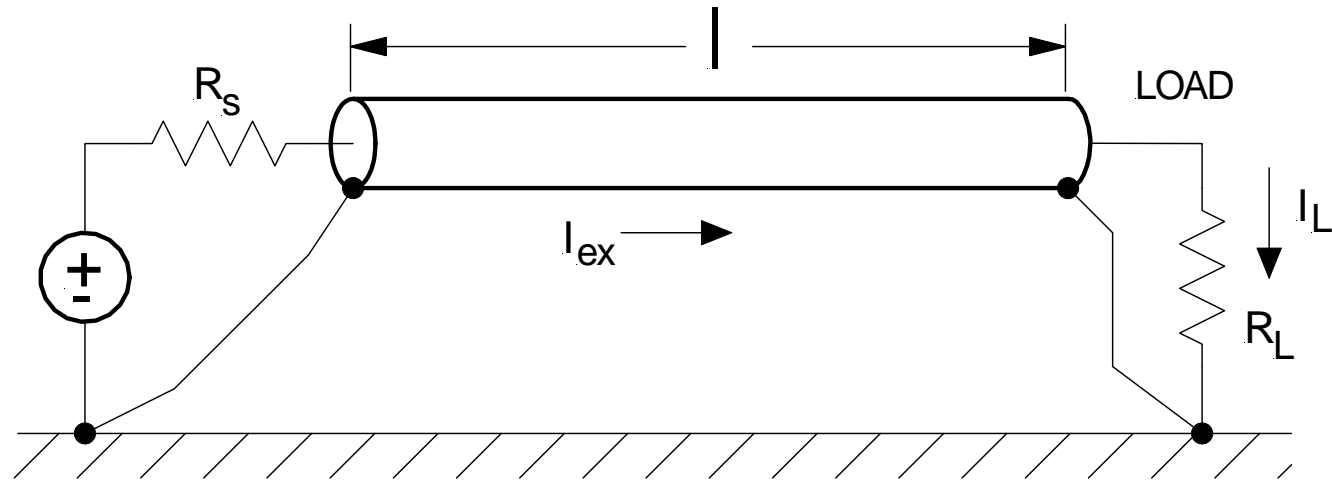

Shielding Effectiveness Measures

- **Traditional**

$$S = 20 \log_{10} \left(\frac{I_{ex}}{I_L} \right) \text{ [dB]}$$


$$S = 20 \log_{10} \left(\frac{Z_T \ell}{R_s + R_L} \right)$$

- **Transfer**

$$Z_{TL} = 20 \log_{10} \left(\frac{V_L}{I_{ex}} \right) \text{ [dB}\Omega\text{]}$$

$$Z_{TL} = 20 \log_{10} \left(\frac{Z_T \ell R_L}{R_s + R_L} \right)$$

Z_T of a Solid Shield

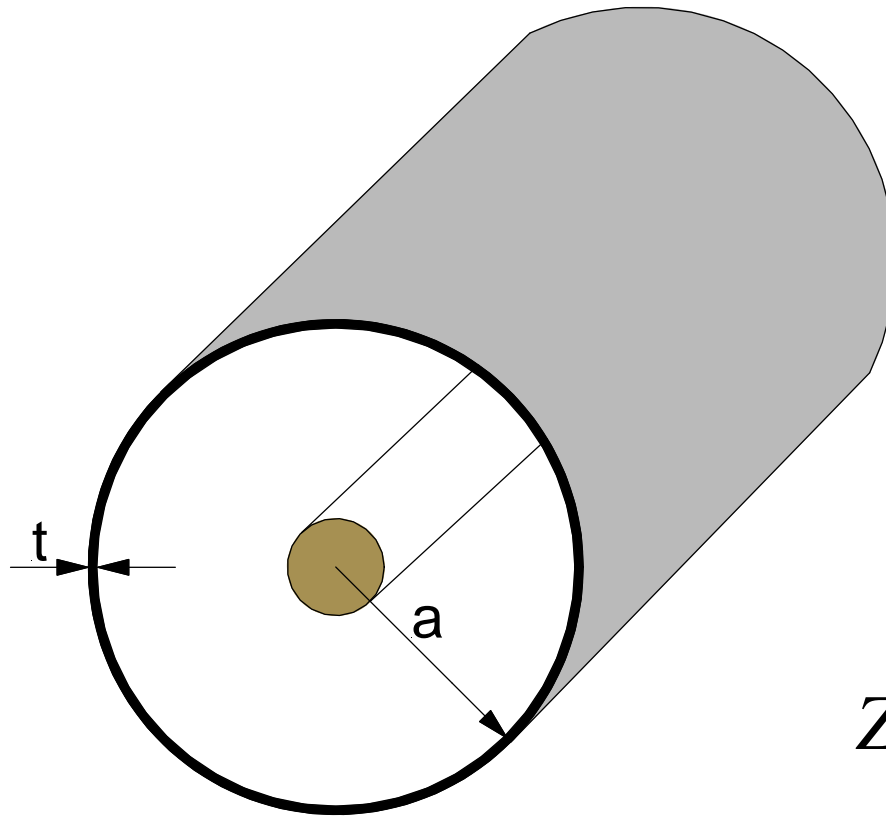

DC RESISTANCE


$$R_0 = \frac{1}{2\pi a t \sigma} \quad [\Omega/\text{m}]$$

a = MEAN RADIUS

$$Z_T = R_0 \frac{(1 + j) \frac{t}{\delta}}{\sinh \left[(1 + j) \frac{t}{\delta} \right]}$$

δ = SKIN DEPTH


Solid Shield Example

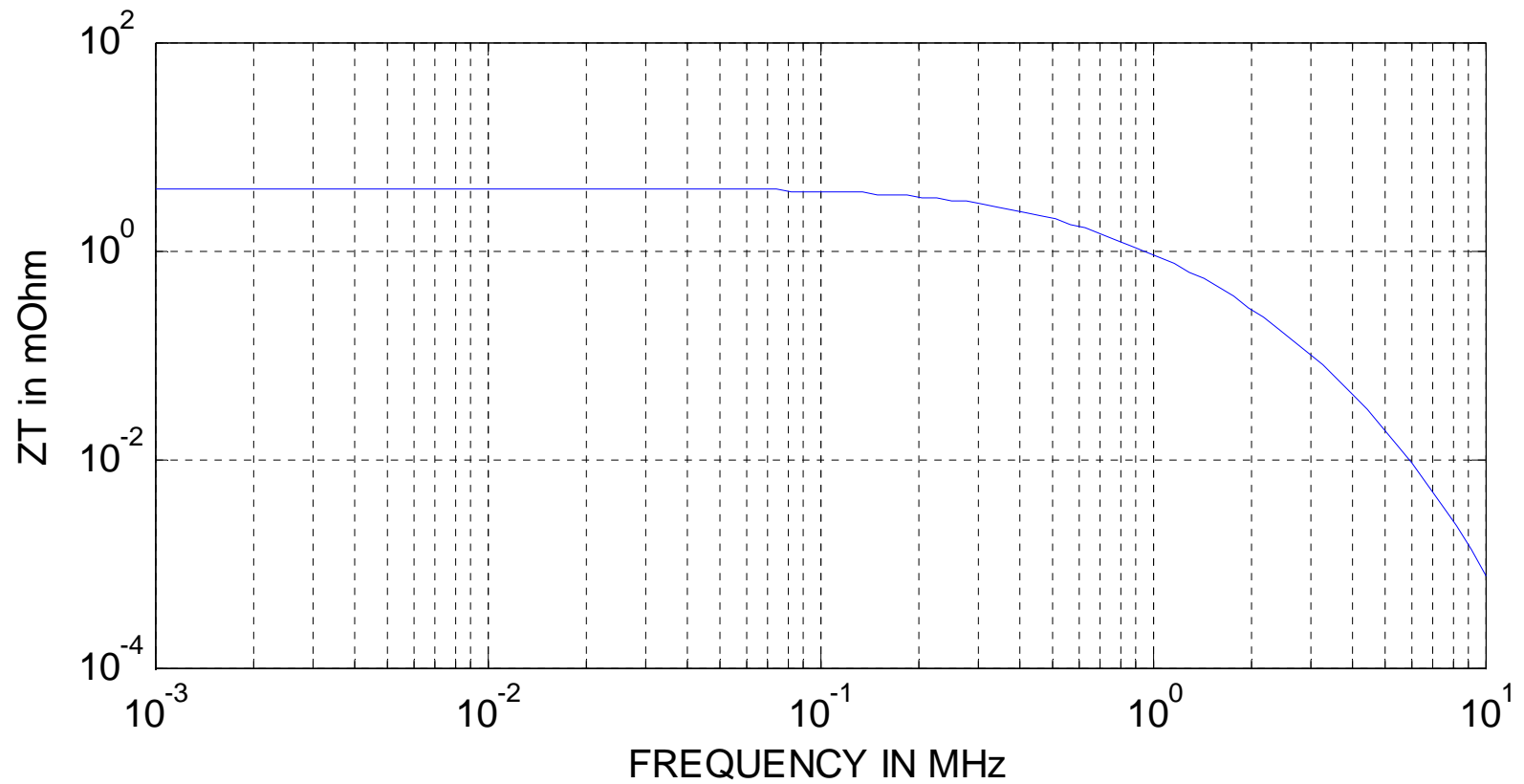


Braided Shield

- Coupling through rhombic apertures modeled by mutual inductance, M_{12} .
- More susceptible to corrosion
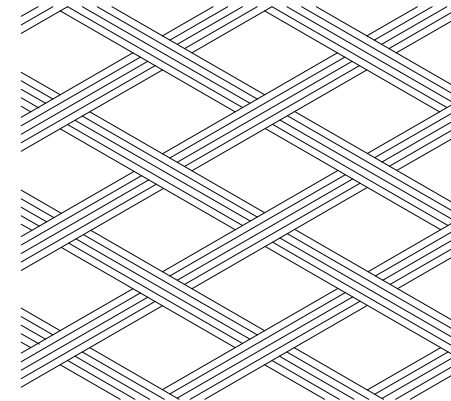
$$Z_T = R_0 \frac{(1+j)\frac{t}{\delta}}{\sinh \left[(1+j)\frac{t}{\delta} \right]} + j\omega M_{12}$$




Braided Shield

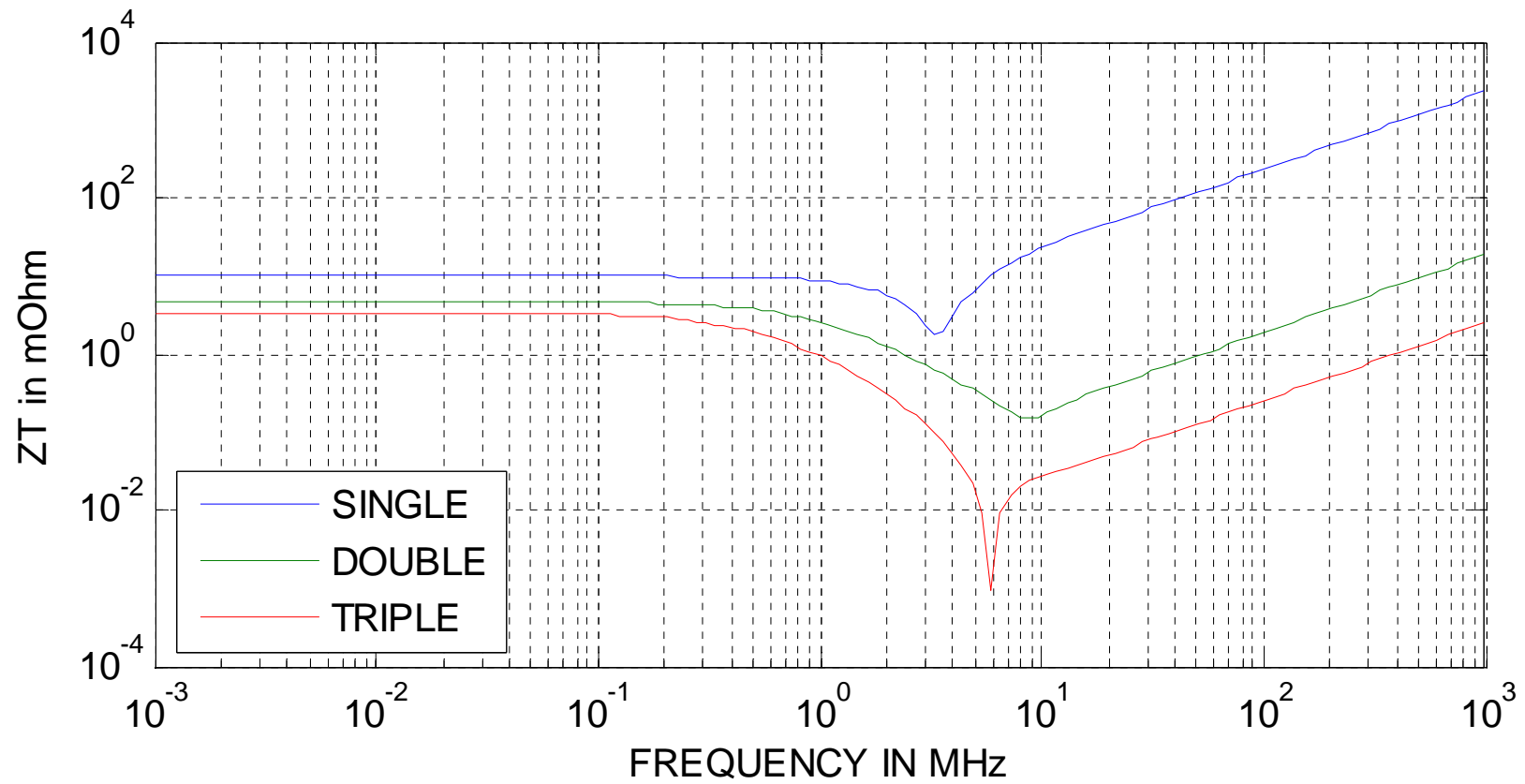


Connectors

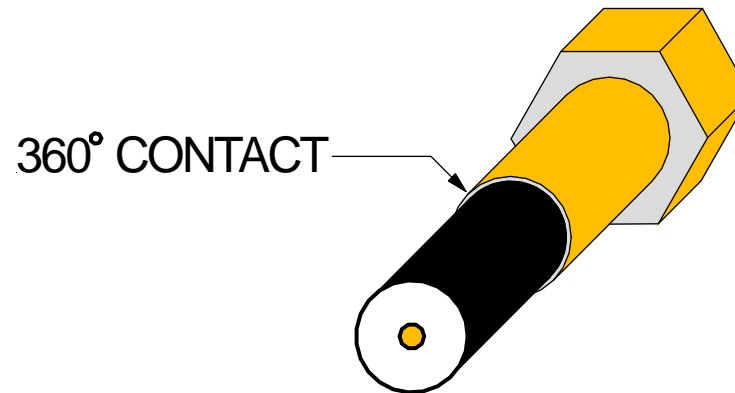
- Connectors also have transfer impedances;
 - e.g., BNC, $R_0 = 2 \text{ m}\Omega$, $M_{12} = 5 \text{ pH}$
- Cable shield must have a **360°** low-resistance contact to its connectors.



“Ground” Noise

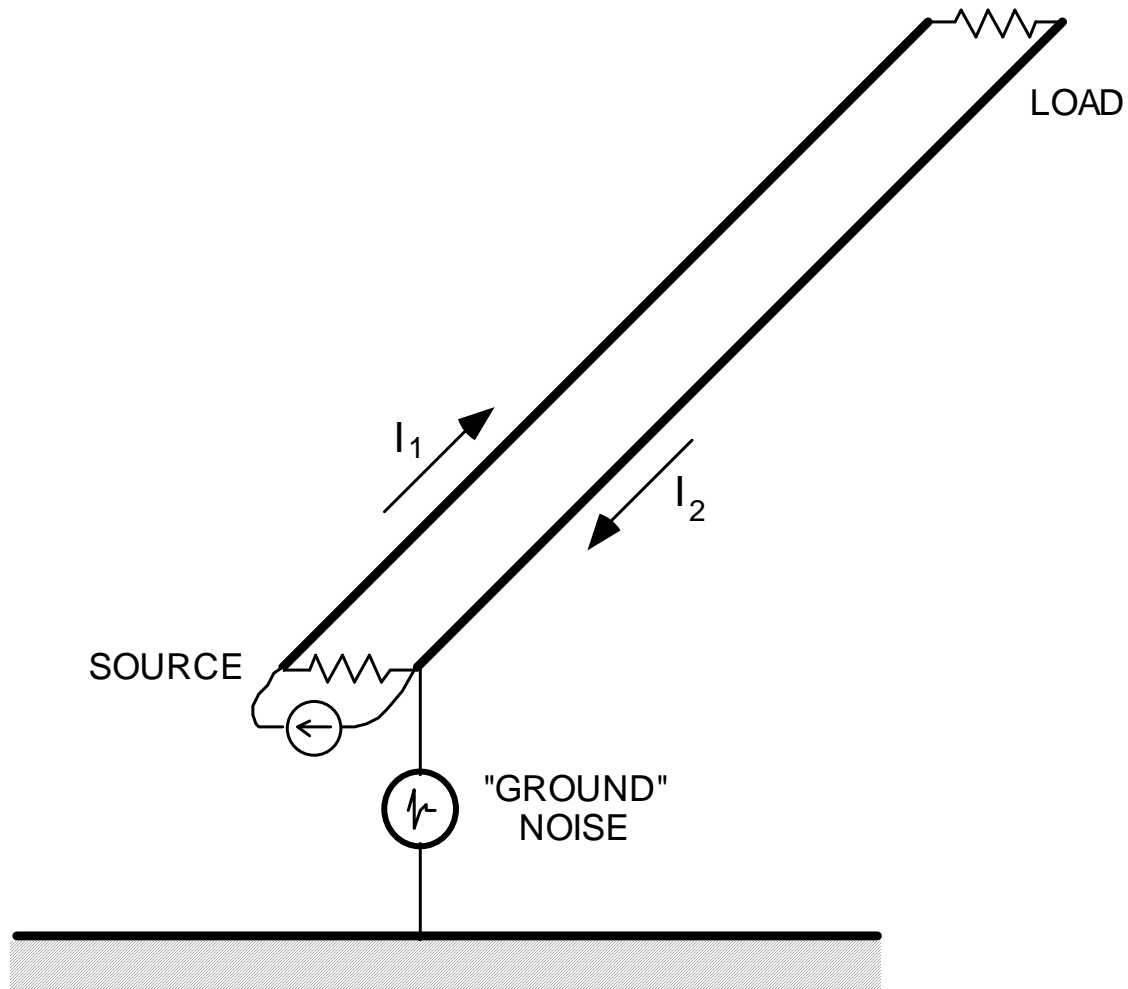


Common-Mode Excitation

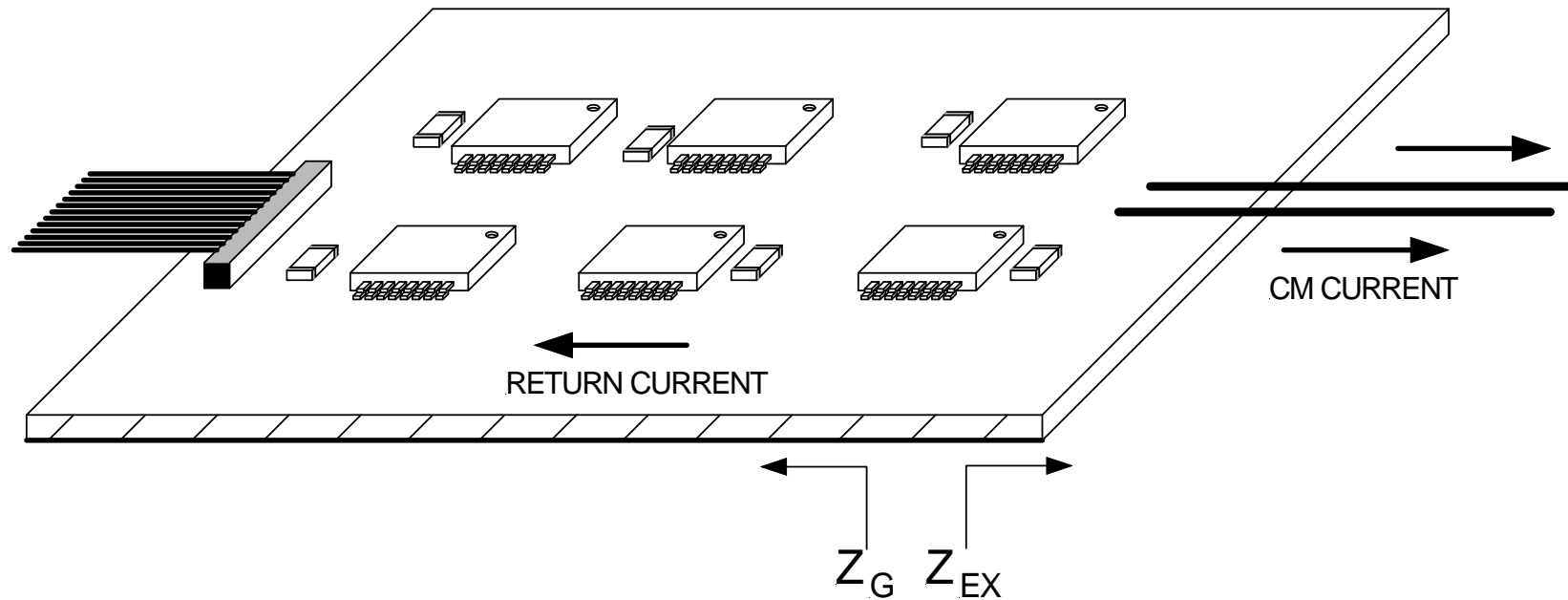

ATTACH CABLE TO QUIETER
GROUND REGIONS.


$$I_{CM} = I_{RTN} \frac{Z_G}{Z_G + Z_{EX}}$$

Cable Grounding “Island”

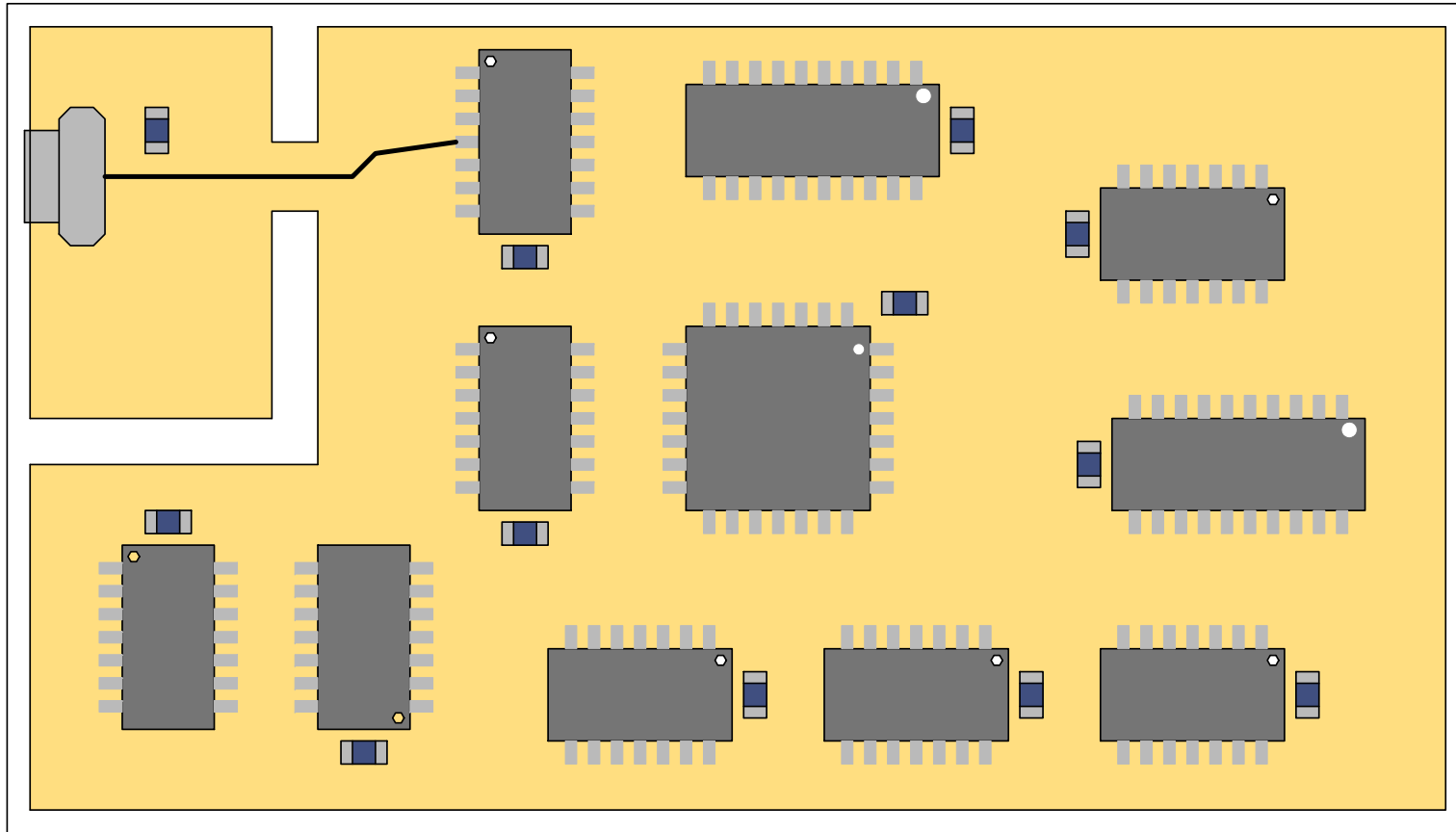


NOT AS EASY AS IT LOOKS. SIGNAL TRACES SHOULD NOT CROSS GROUND CUTOUT.


Bringing a Cable through a Shield Wall

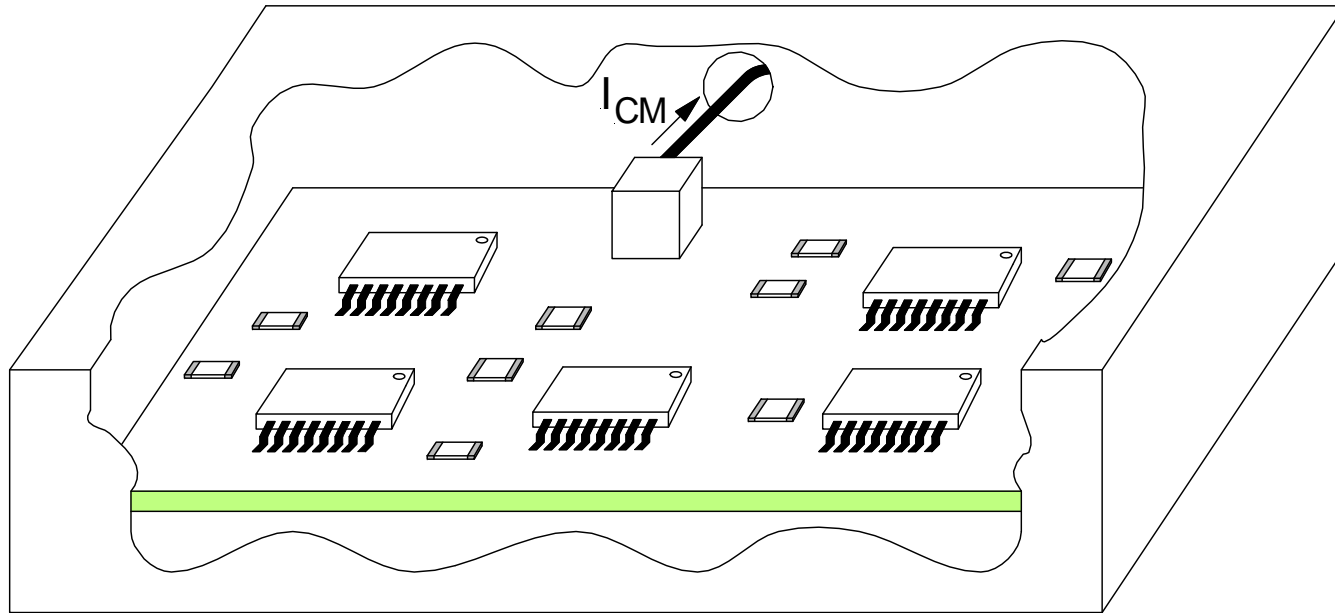

Bulkhead Connector

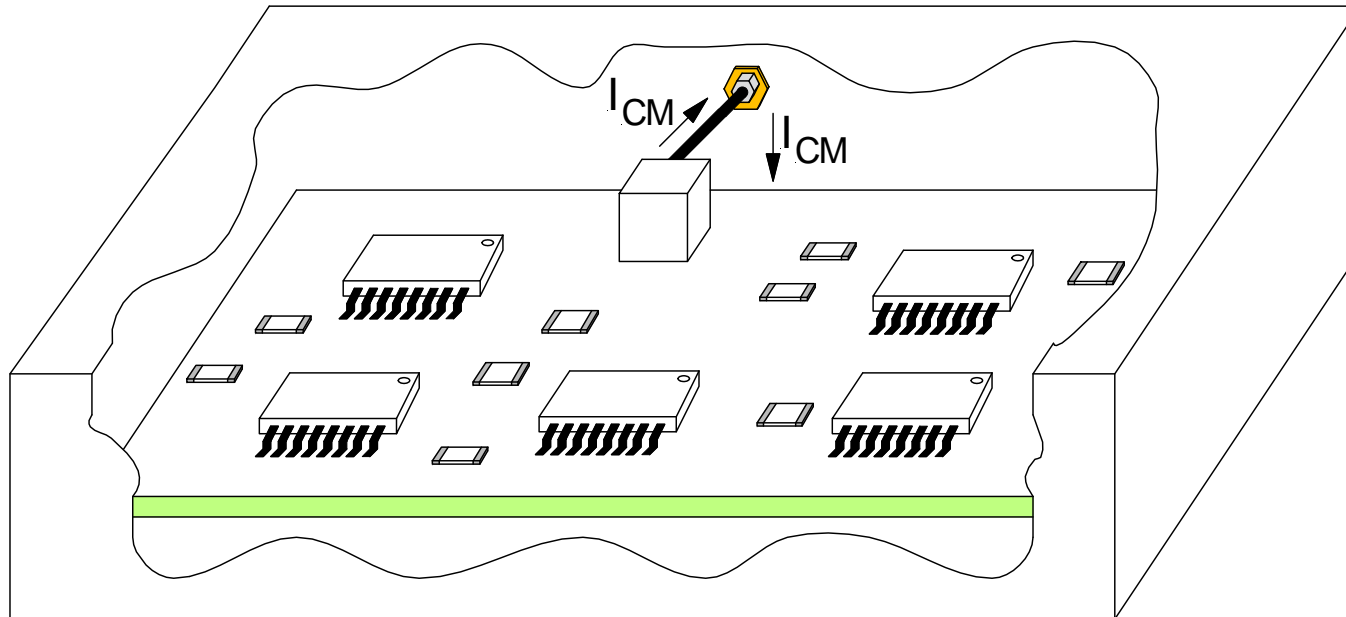


Stripping Common-Mode Current

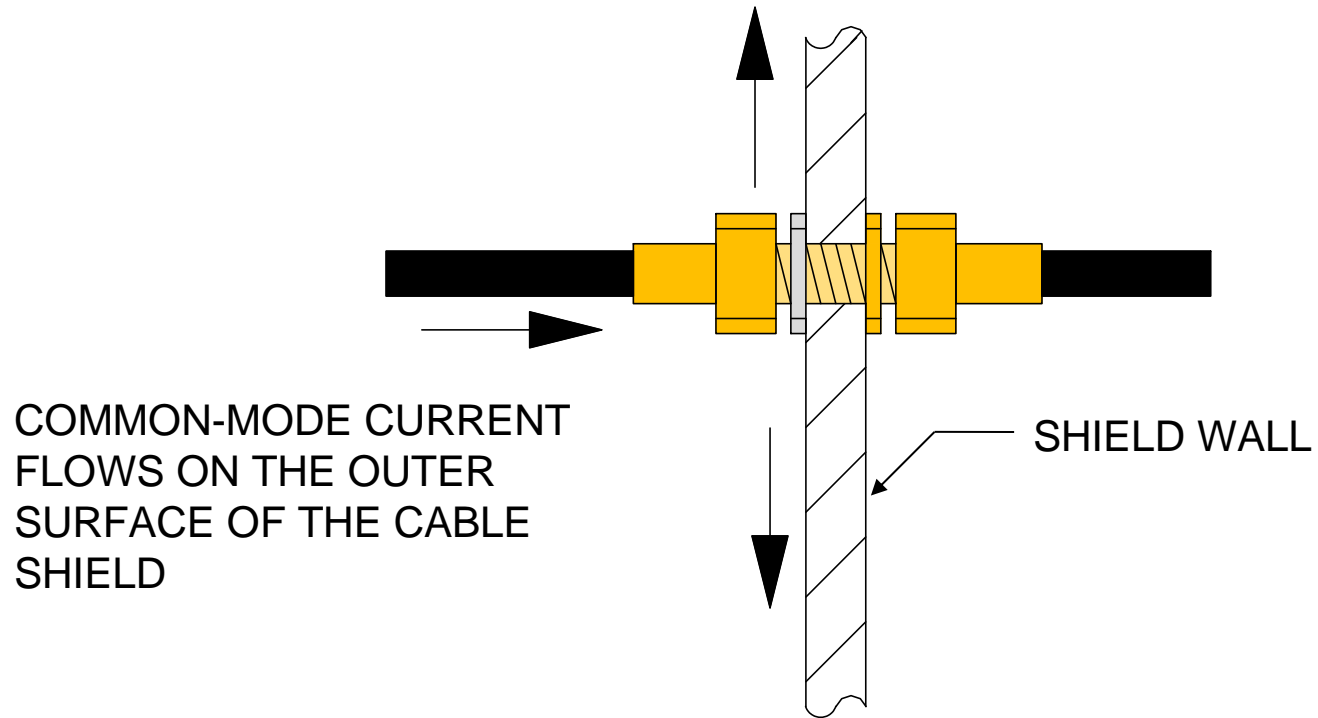

Measuring Common-Mode Current



CURRENT
PROBES

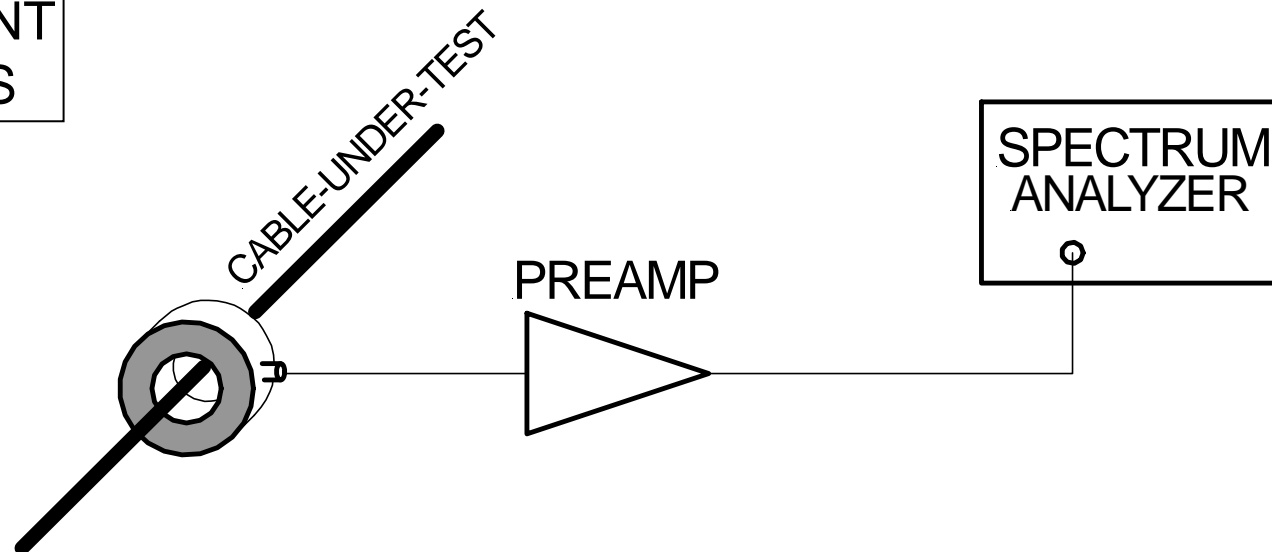

Summary of Concepts

- **Return current seeks the minimum impedance.**
- **Above the 5x shield cutoff frequency, nearly all the return current flows in the shield of a well grounded cable.**
- **Common-mode current induced by poor cable grounding flows on the outer surface of a cable shield.**

Summary of Concepts

- **A cable performs no better than its connectors.**
- **Terminate cable shields 360° to their connectors.**
- **Connecting a shield to a noisy ground produces CM current on the outer surface of the shield.**
- **Cables are best brought through a shield wall using a bulkhead connector.**

Books

- **Coupling to Shielded Cables**
E.F. Vance, John Wiley & Sons, 1978.
- **Coupling of External Electromagnetic Fields to Transmission Lines**
A.A. Smith, Jr., John Wiley & Sons, 1977.

