

Low-Power CMOS Optical Interconnect Transceivers

Samuel Palermo*



Computer Systems Laboratory
Stanford University



*Now at Intel Corp., Hillsboro, OR

Outline

- Introduction
- Optical transmitters
- Optical receiver
- Clock and data recovery
- Optical link system performance
- Conclusion

High Speed Links

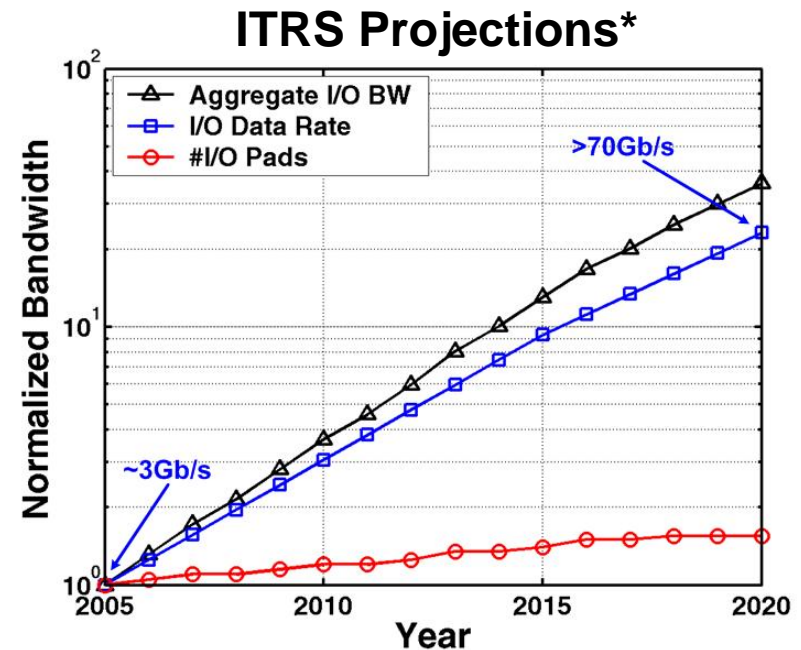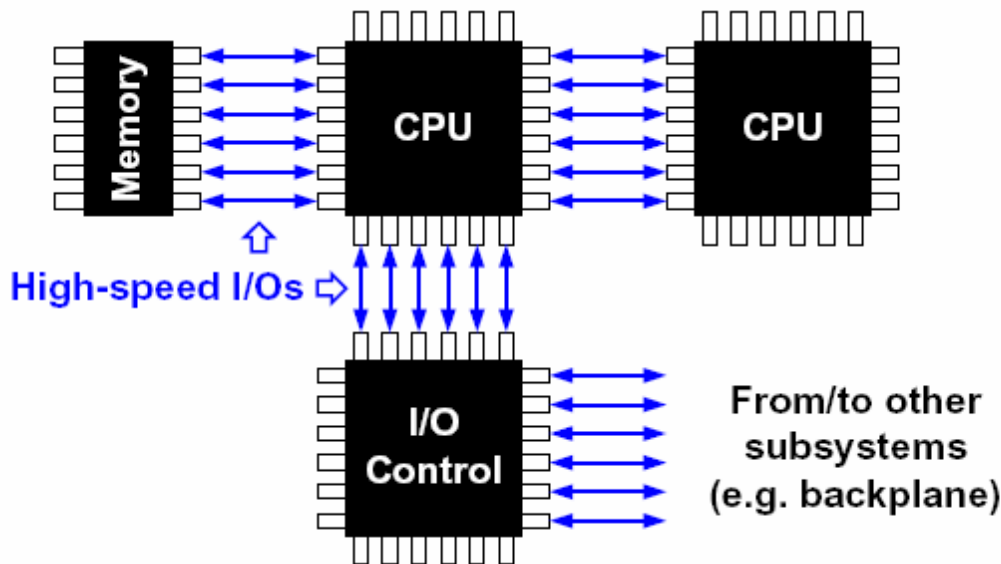
- Increasing computation power and today's networked society requires chip-to-chip I/O bandwidth to increase
 - Routers, Processor – Memory Interface




*2006 International Technology Roadmap for Semiconductors

Chip-to-Chip Electrical Interconnects

Electrical Backplane Channel

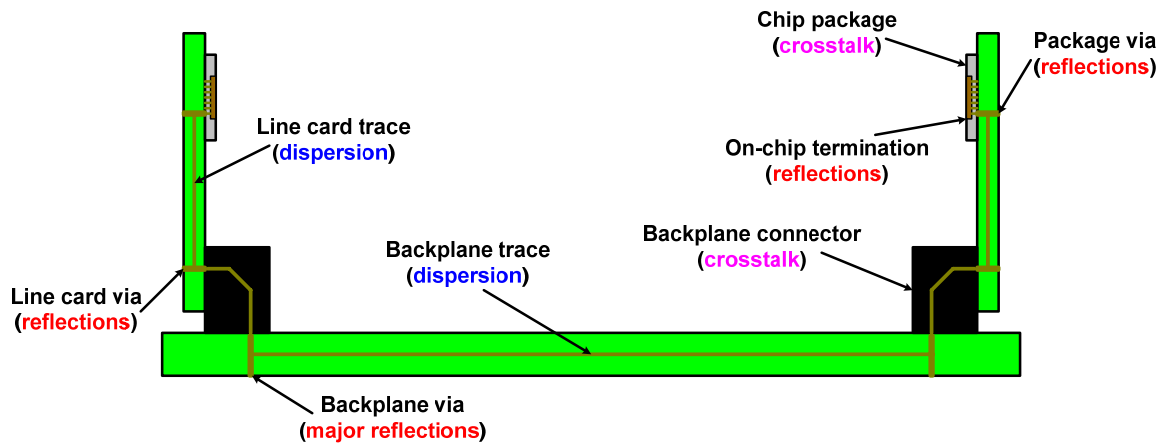


Channel Responses*

 

- Electrical channel characteristics limit performance


*V. Stojanovic and M. Horowitz, "Modeling and Analysis of High-Speed Links," *CICC*, 2003.

Chip-to-Chip Electrical Interconnects

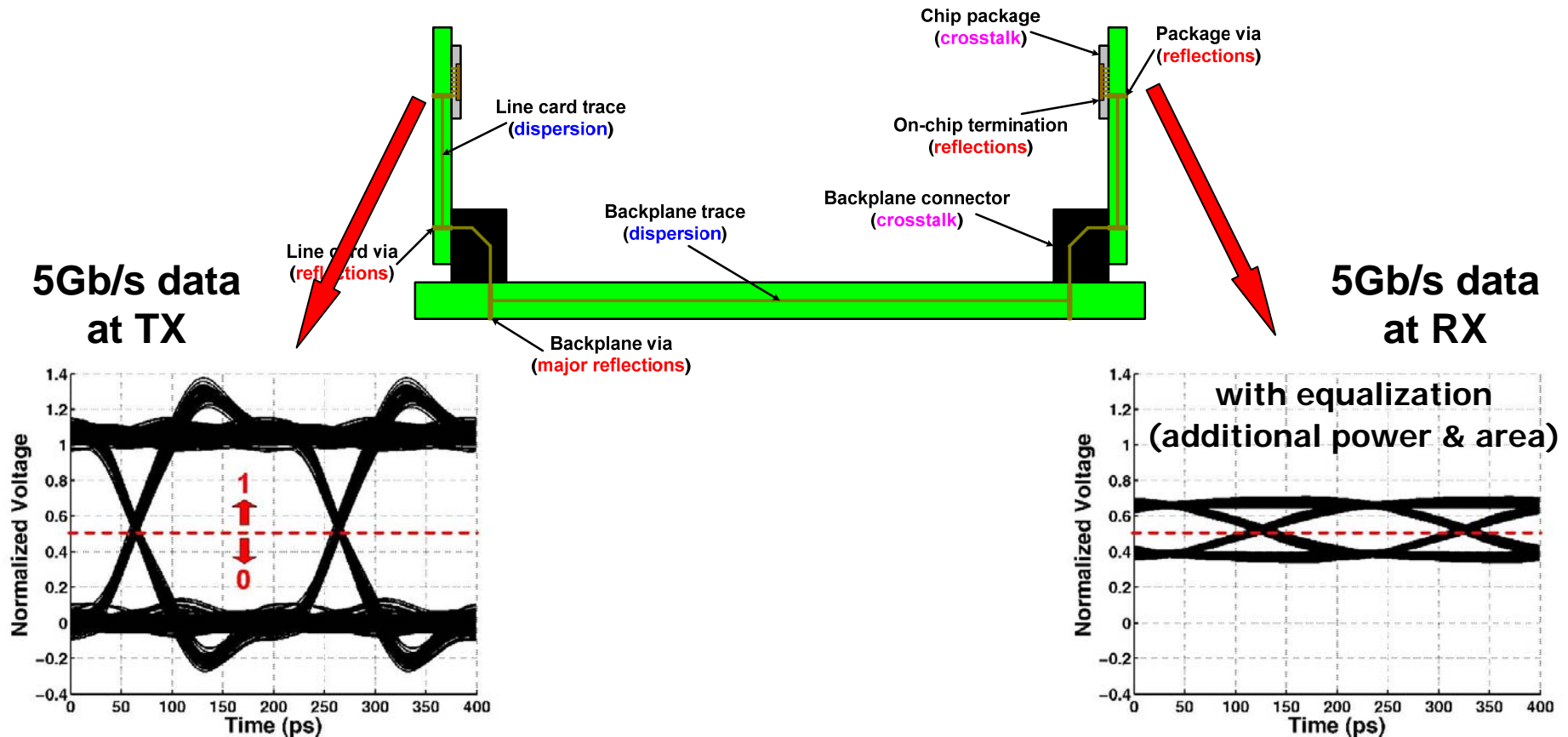

- Sophisticated equalization circuitry required
- Typical commercial electrical I/O xcvr
 - ~20mW/Gb/s at 10Gb/s

Chip-to-Chip Optical Interconnects

 


- Optical interconnects remove many channel limitations
 - Reduced complexity and power consumption
 - Potential for high information density with wavelength-division multiplexing (WDM)


Optical Sources & Detectors

- Sources

VCSEL

 


MQW Electroabsorption Modulator

 


- Detector

p-i-n Detector

 


- Integration

 

CMOS Optical Link Issues

- VCSEL bandwidth
 - Inherent device RC
 - Optical bandwidth requires high average current density
- Modulator voltage swing limited by CMOS reliability constraints
- Reduced gain/headroom in scaled technologies
 - Motivates use of integrating RX vs traditional TIA
- Dealing with mismatch
 - Offset compensation (voltage & timing)
- Power and area reduction

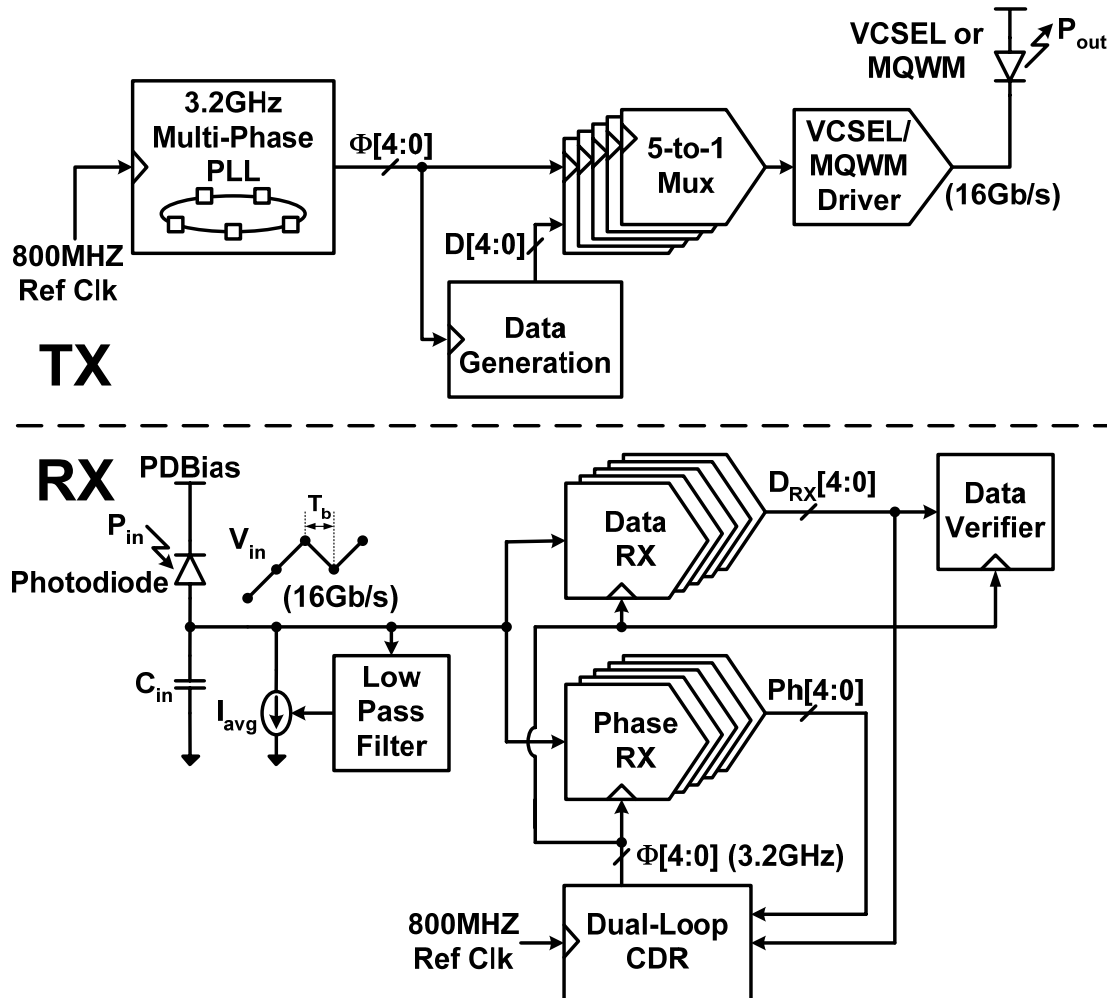90nm CMOS 16Gb/s Optical Transceiver Architecture




1. S. Palermo *et al*, "A 90nm CMOS 16Gb/s Transceiver for Optical Interconnects," *ISSCC*, 2007.
2. J. Roth, S. Palermo *et al*, "1550nm Optical Interconnect Transceiver with Low Voltage Electroabsorption Modulators Flip-Chip Bonded to 90nm CMOS," *OFC*, 2007.

Outline

- Introduction
- Optical transmitters
 - VCSEL TX
 - MQWM TX
- Optical receiver
- Clock and data recovery
- Optical link system performance
- Conclusion

VCSEL Bandwidth vs Reliability

10Gb/s VCSEL Frequency Response [1]

 

$$BW \propto \sqrt{I_{avg} - I_{TH}}$$

- Mean Time to Failure (MTTF) is inversely proportional to current density squared

$$MTTF = \frac{A}{j^2} e^{\left(\frac{E_A}{k}\right)\left(\frac{1}{T_j} - \frac{1}{373}\right)} \quad [2]$$

- Steep trade-off between bandwidth and reliability


$$MTTF \propto \frac{1}{BW^4}$$

1. D. Bossert *et al*, "Production of high-speed oxide confined VCSEL arrays for datacom applications," *Proceedings of SPIE*, 2002.
2. M. Teitelbaum and K. Goossen, "Reliability of Direct Mesa Flip-Chip Bonded VCSEL's," *LEOS*, 2004.

VCSEL TX Equalization


TX Current
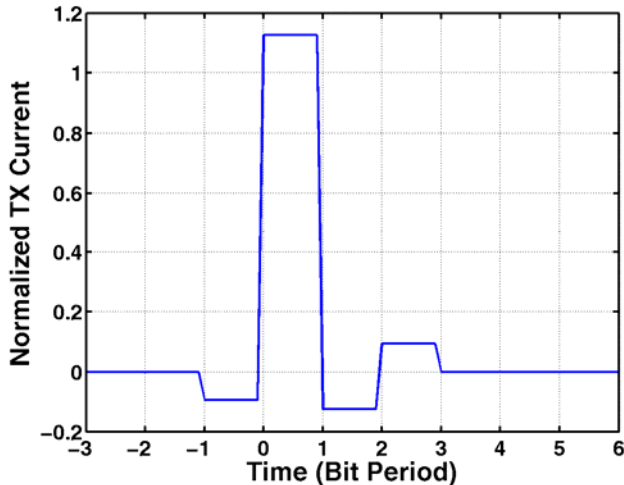
$$h(n) = I_{-1}(-1) + I_0(0) + I_1(1) + I_2(2)$$




Channel Pulse Response

$$p(n)$$

 

Received Optical Power

$$v(n)$$

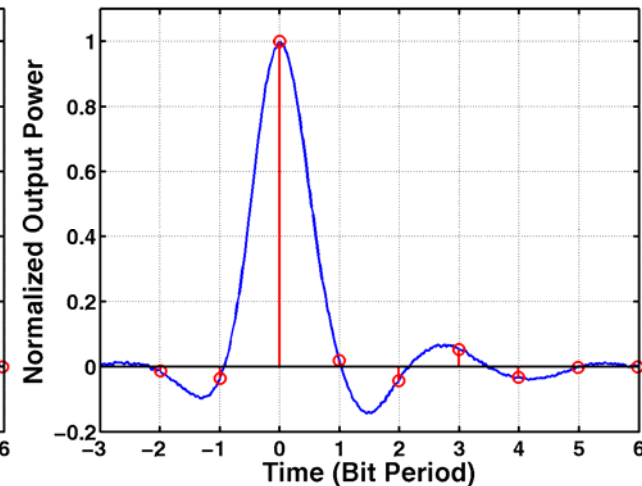


Measured pulse responses
at 17Gb/s w/ $I_{avg} = 6.7\text{mA}$


$$H_{ls} = (P^T P)^{-1} P^T Y_{des}$$

- 4-tap FIR filter – 1 precursor, 1 main, and 2 postcursor is a good compromise between power and performance


Multiplexing FIR Circuit Implementation

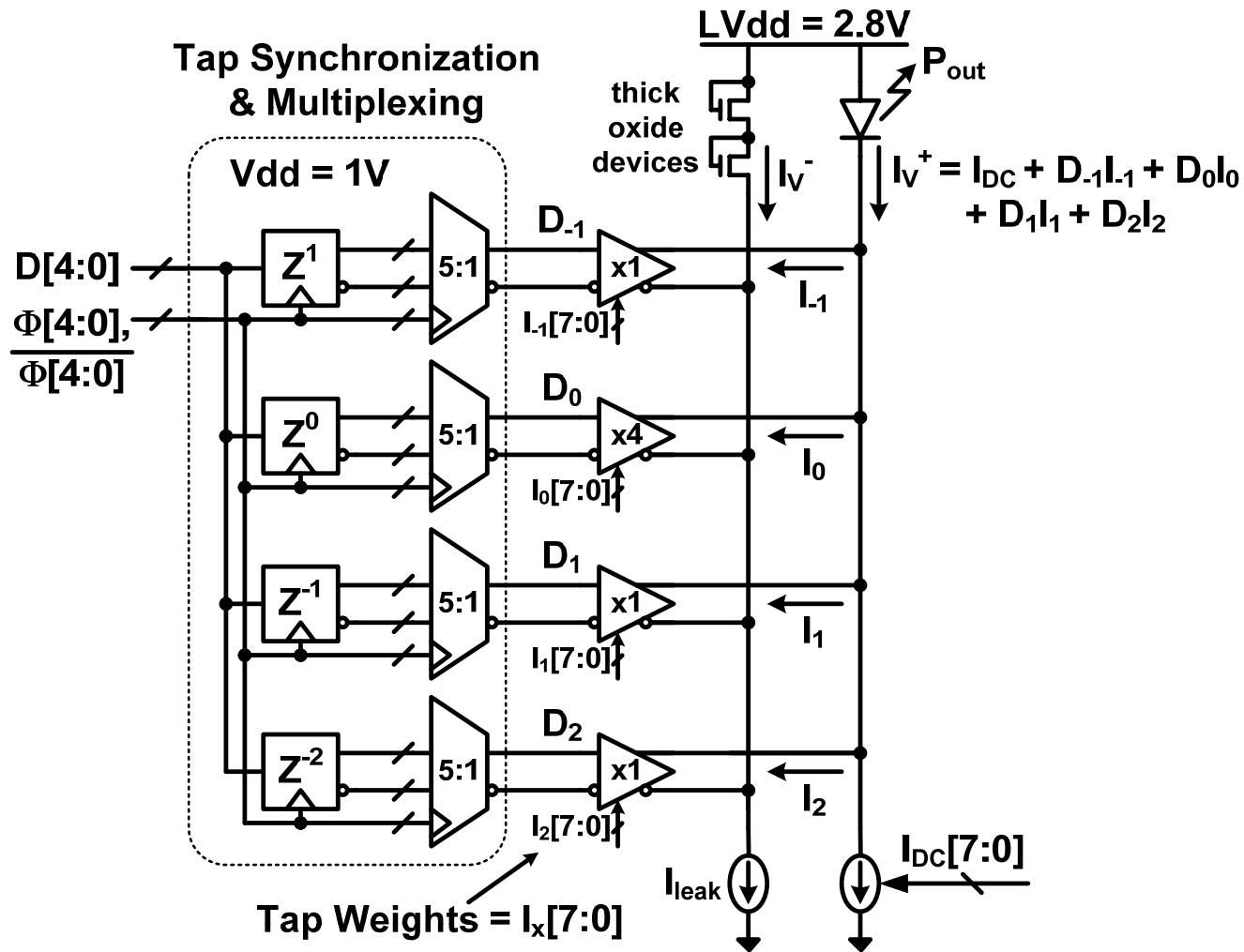

VCSEL TX Optical Testing

 

Wirebonded
10Gb/s VCSEL

 

VCSEL 16Gb/s Optical Eye Diagrams

$I_{\text{avg}} = 6.2\text{mA}$, $\text{ER} = 3\text{dB}$

No Equalization →

$I_{\text{DC}} = 4.37\text{mA}$

$I_{\text{MOD}} = 3.66\text{mA}$

w/ Equalization ↘

$I_{\text{DC}} = 3.48\text{mA}$

$I_{-1} = -0.70\text{mA}$


$I_0 = 4.36\text{mA}$

$I_1 = -0.19\text{mA}$

$I_2 = 0.19\text{mA}$



Equalization increases
vertical eye opening

45% at 16Gb/s

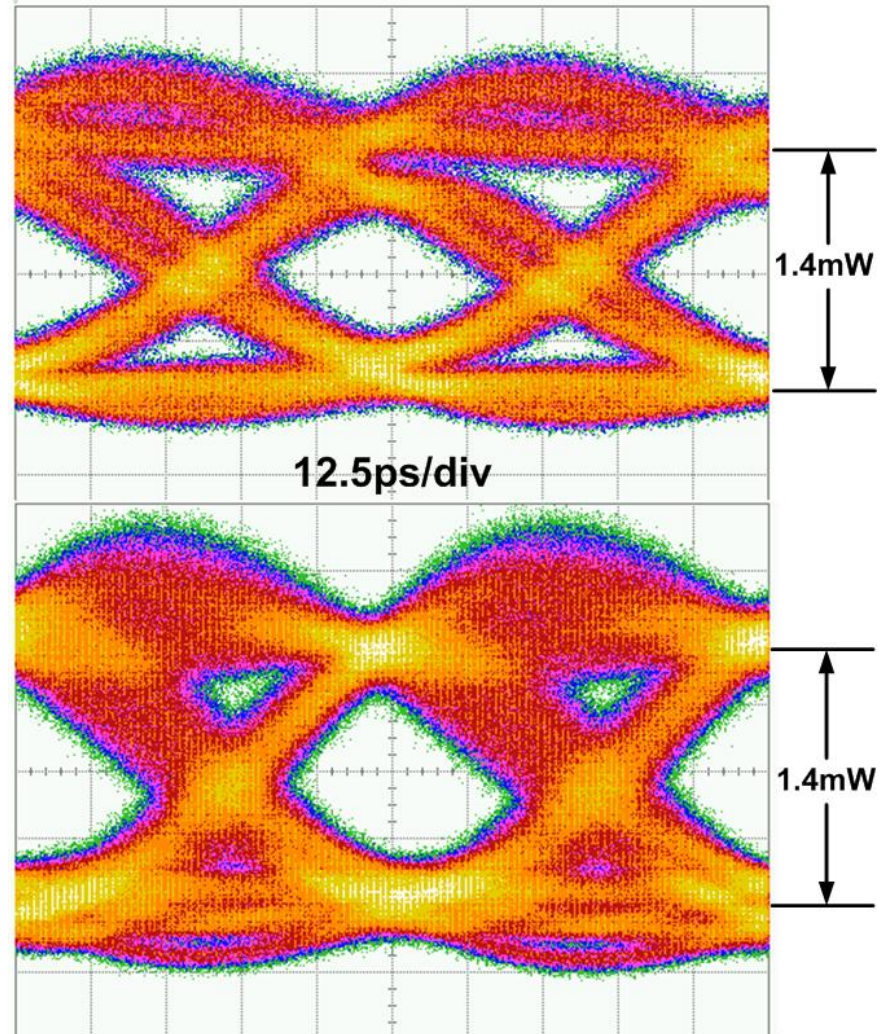

External Modulation with MQWM



QWAFEM Modulator*

  

- Absorption edge shifts with changing bias voltage due to the “quantum-confined Stark effect” and modulation occurs
- Maximizing voltage swing allows for good contrast ratio over a wide wavelength range


High-Voltage Output Stage Issues

Cascode Driver*

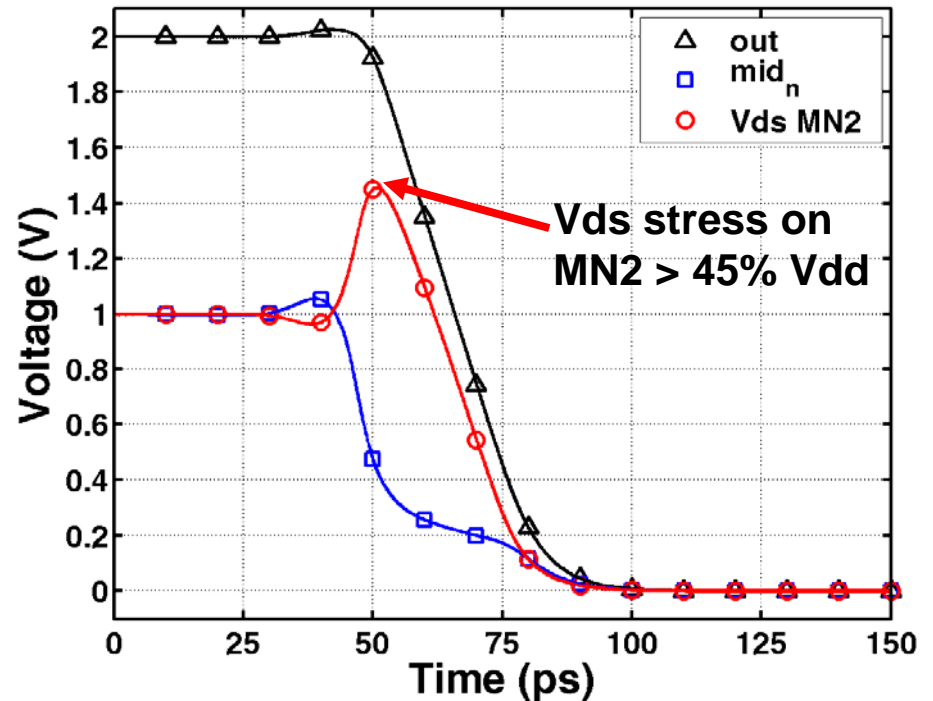 




- ☺ Cascode driver has potential for 2x Vdd drive at high speed
- ☹ Static-biased cascode suffers from V_{ds} stress during transients

Pulsed-Cascode Output Stage



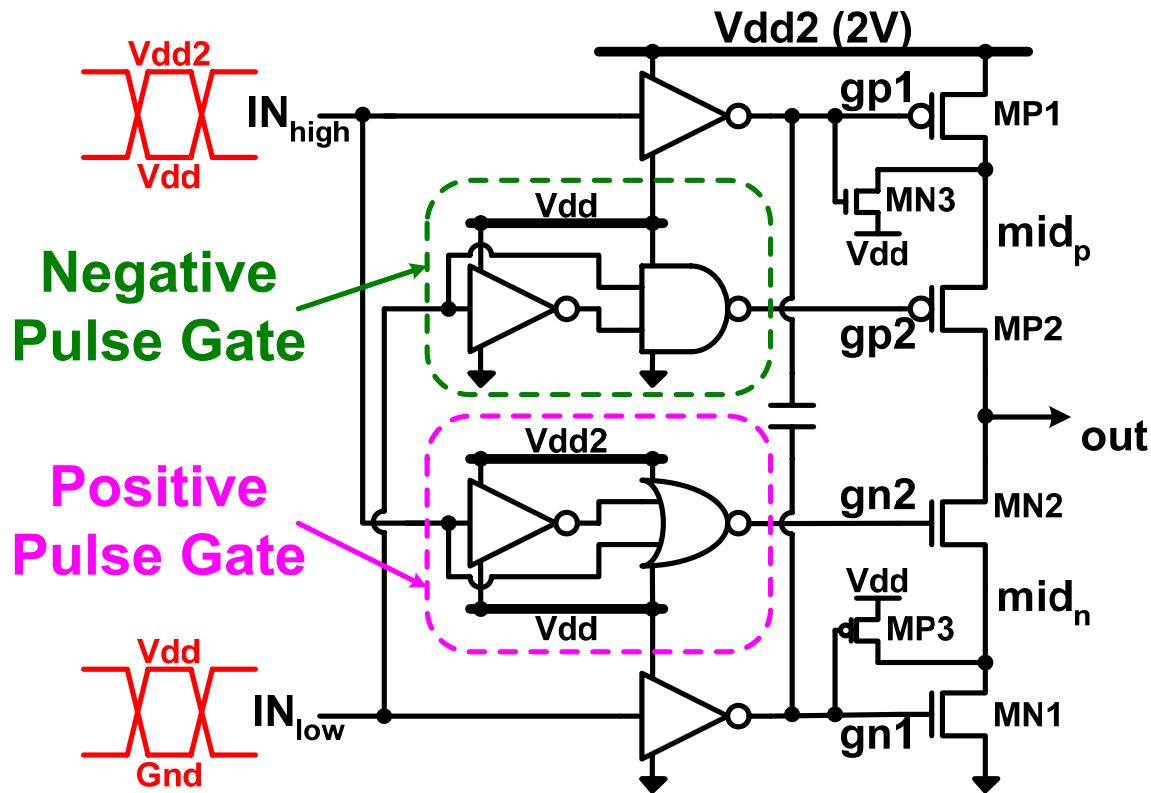


- Preserves two-transistor stack configuration for maximum speed
- Cascode transistors' gates pulsed during transitions to prevent V_{ds} overstress


Output Stage Waveforms

  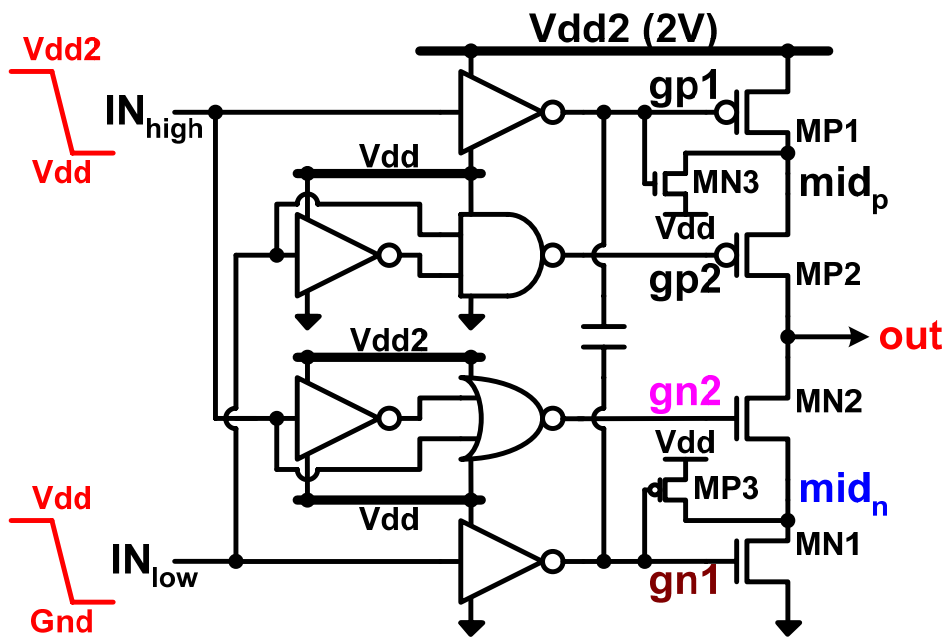

Output Stage Waveforms

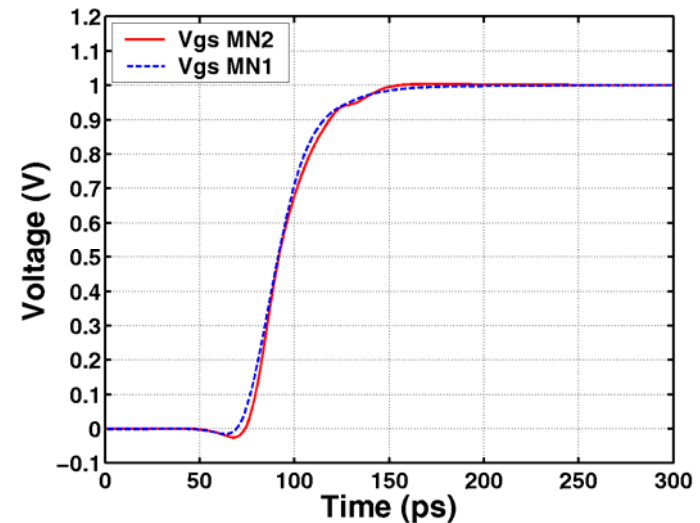
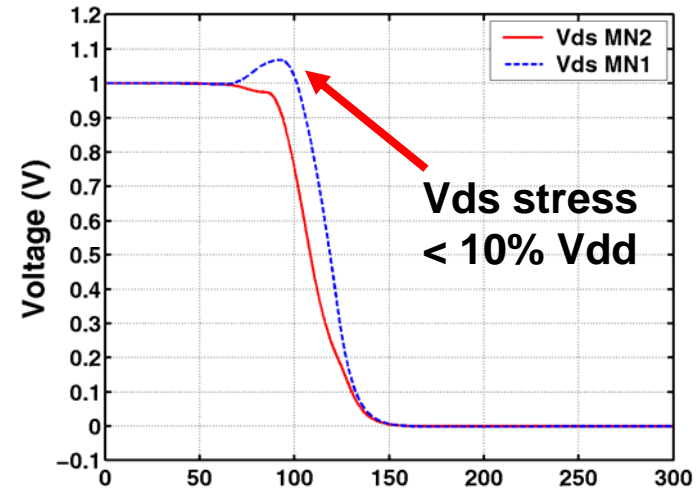
 


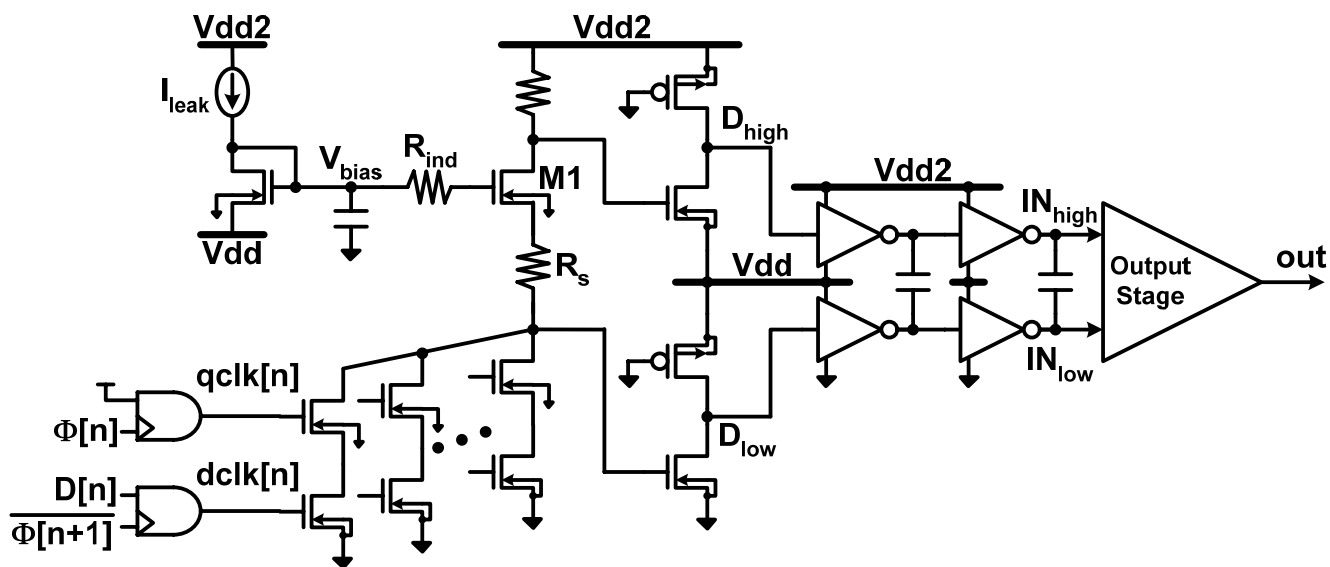Modulator TX with Level-Shifting Multiplexer




- Level-shifter combined with multiplexer
- Active inductive shunt peaking compensates multiplexer self-loading (reduces transition times by 37%)
- Slightly lower fan-out ratio in “high” signal path to compensate for level-shifting delay
- Delay Tracking
 - “High” path inverter nMOS in separate p-well
 - Metal fringe coupling capacitors perform skew compensation

MQWM TX Testing

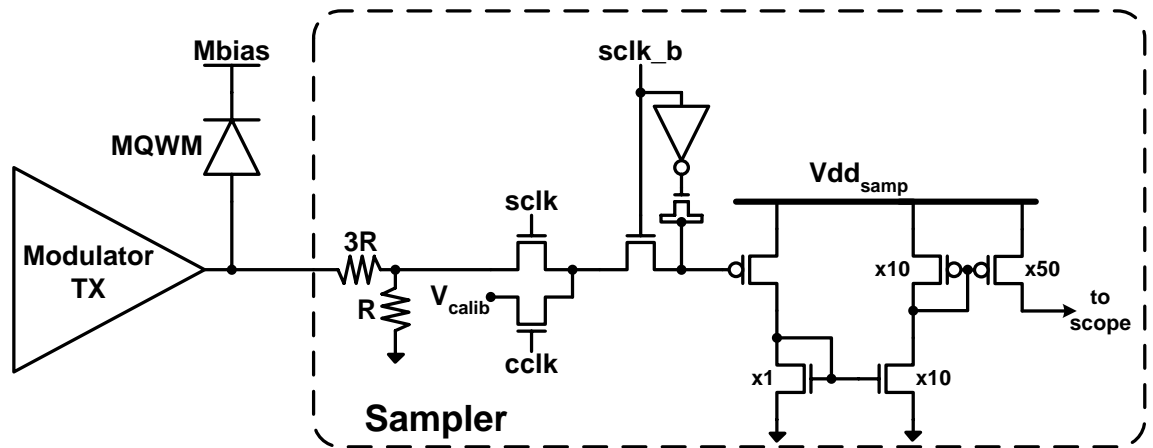  

Electrical sampler at modulator transmitter output

Modulator Driver Electrical Eye Diagram

 

- 16Gb/s data subsampled at modulator driver output node
- Experimental full optical link operation at 1.8Gb/s*
 - Limited by excessively high contact resistance

*J. Roth, S. Palermo *et al*, "An optical interconnect transceiver at 1550nm using low voltage electroabsorption modulators directly integrated to CMOS," *JLT*, 2007.

Outline

- Introduction
- Optical transmitters
- Optical receiver
- Clock and data recovery
- Optical link system performance
- Conclusion

Optical RX Scaling Issues

- ☺ Traditionally, TIA has high R_T and low R_{in}

$$R_T = R_F \left(\frac{A}{1+A} \right)$$

$$\omega_{3dB} \approx \frac{1+A}{R_F C_{IN}}$$


- ☹ Headroom/Gain issues in 1V CMOS

- $A \approx 2 - 3$

- ☹ Power/Area Costs

$$\text{TIA } I_D \propto (R_T C_{IN})^2 f_{3dB}^4$$


$$\text{LA } I_D \propto f_{3dB}^2$$

 


$$V_A = V_{GS1} + V_{GS2} \approx 0.8 * VDD$$

$$A \approx g_{m1} R_D = \frac{\alpha(VDD - V_A)}{VOD} \approx \frac{\alpha(0.2 * VDD)}{VOD}$$

Integrating Receiver Block Diagram

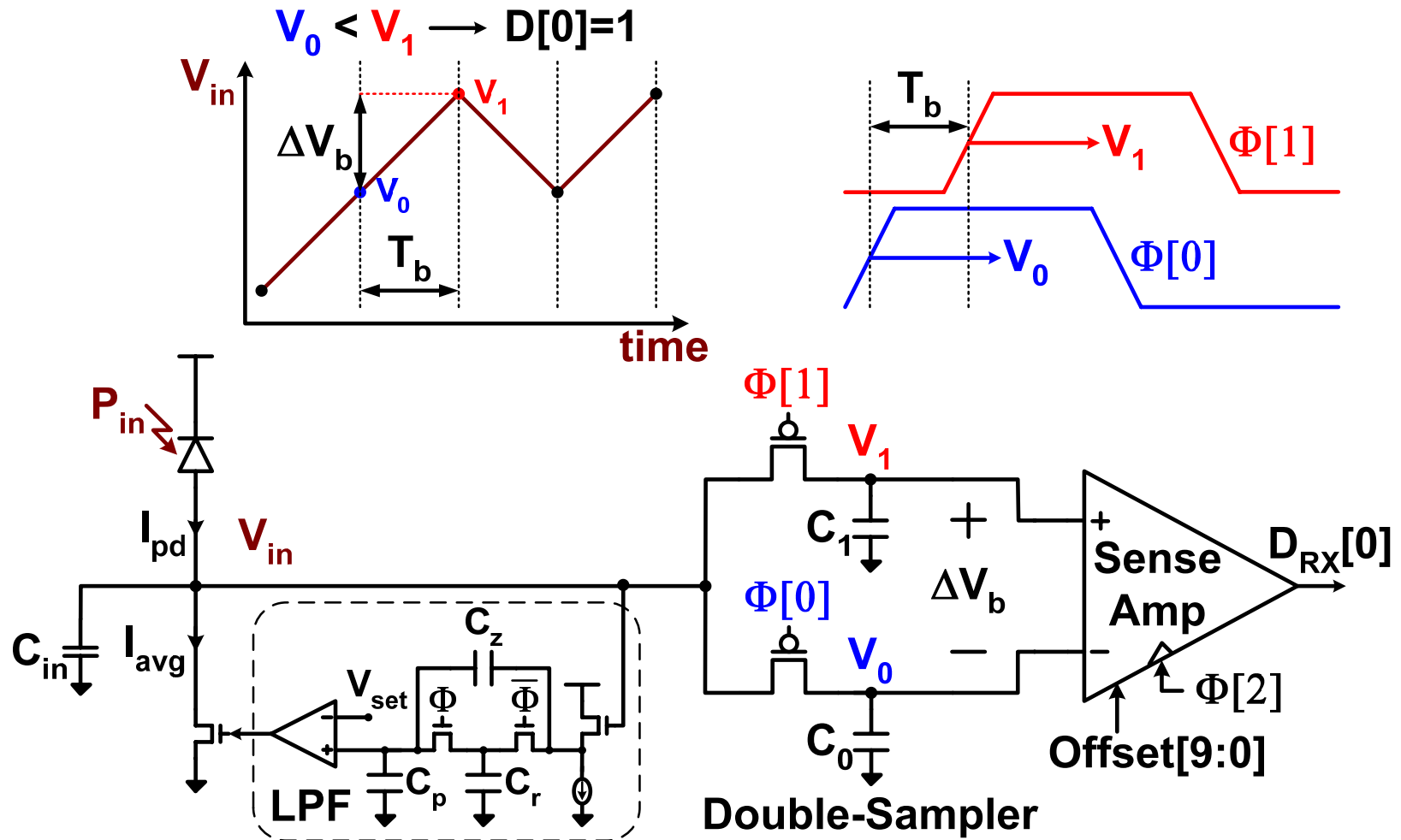


Demultiplexing Receiver

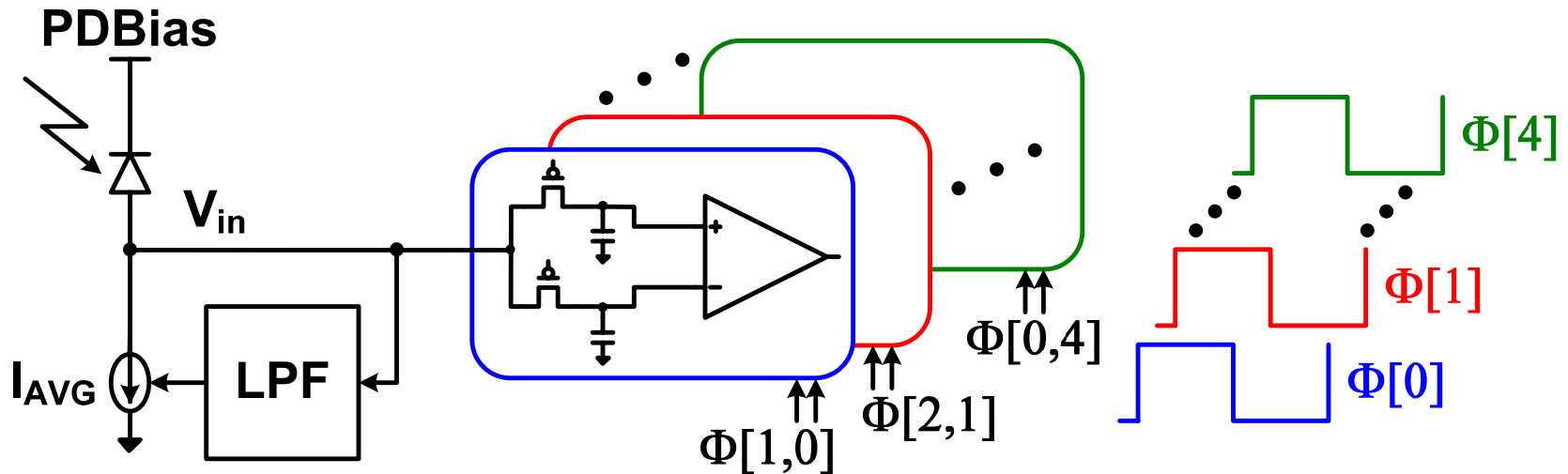


- Demultiplexing with multiple clock phases allows higher data rate
 - Data Rate = #Clock Phases x Clock Frequency
 - Gives sense-amp time to resolve data
 - Allows continuous data resolution

Clocked Sense Amplifier

 


- Offset cancelled with digitally adjustable PMOS capacitors
 - Step=2.3mV, Range=±70mV
- Kickback charge can corrupt adjacent samples
- Need high common-mode input for adequate speed

1V Modified Integrating Receiver

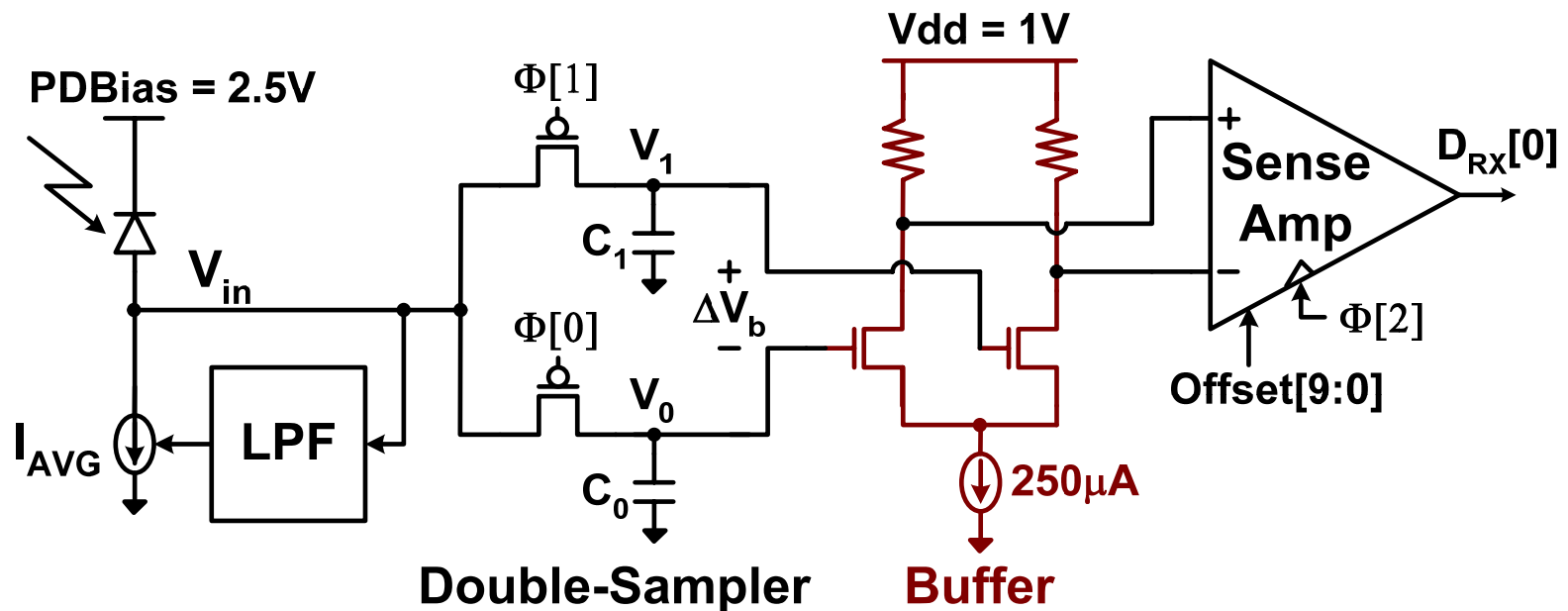

- **Differential Buffer**
 - ☺ Fixes sense-amp common-mode input for improved speed and offset performance
 - ☺ Reduces kickback charge
 - ☹ Cost of extra power and noise
- **Input Range = 0.6 – 1.1V**

Receiver Sensitivity Analysis

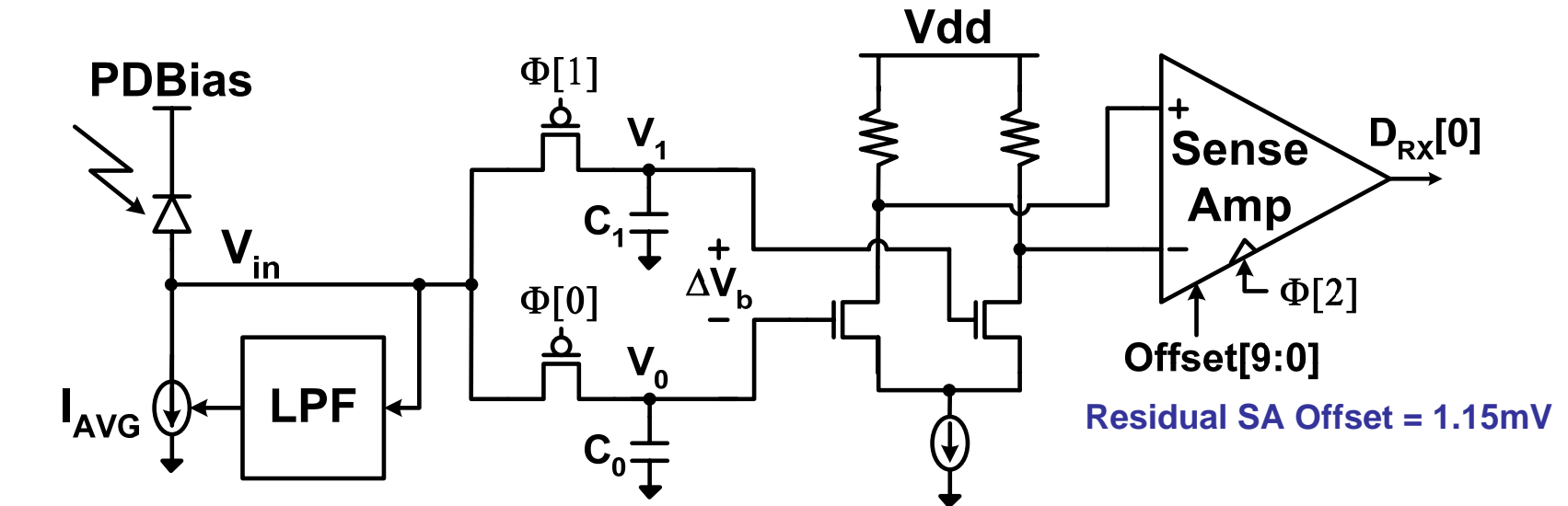

Max $\Delta V_{in}(\Delta I_{AVG}) = 0.6mV$

$$\sigma_{samp} = \sqrt{\frac{2kT}{C_{samp}}} = 0.92mV \quad \sigma_{buffer} = 1.03mV \quad \sigma_{SA} = 0.45mV$$

Clock Jitter Noise $\sigma_{clk} = \left(\frac{\sigma_j}{T_b} \right) \Delta v_b \approx 0.65mV$ at 16Gb/s

Total Input Noise $\sigma_{tot} = \sqrt{\sigma_{samp}^2 + \sigma_{buffer}^2 + \sigma_{SA}^2 + \sigma_{clk}^2} = 1.59mV$

ΔV_b for BER = $10^{-10} = 6.4\sigma_{tot} + \text{Offset} = 11.9mV$


$$P_{avg} = \frac{\Delta V_b (C_{pd} + C_{in})}{\rho T_b}$$

Gb/s	P_{avg} (dBm)
10	-9.8
16	-7.8

Outline


- Introduction
- Optical transmitters
- Optical receiver
- Clock and data recovery
- Optical link system performance
- Conclusion

Conventional Dual-Loop CDR

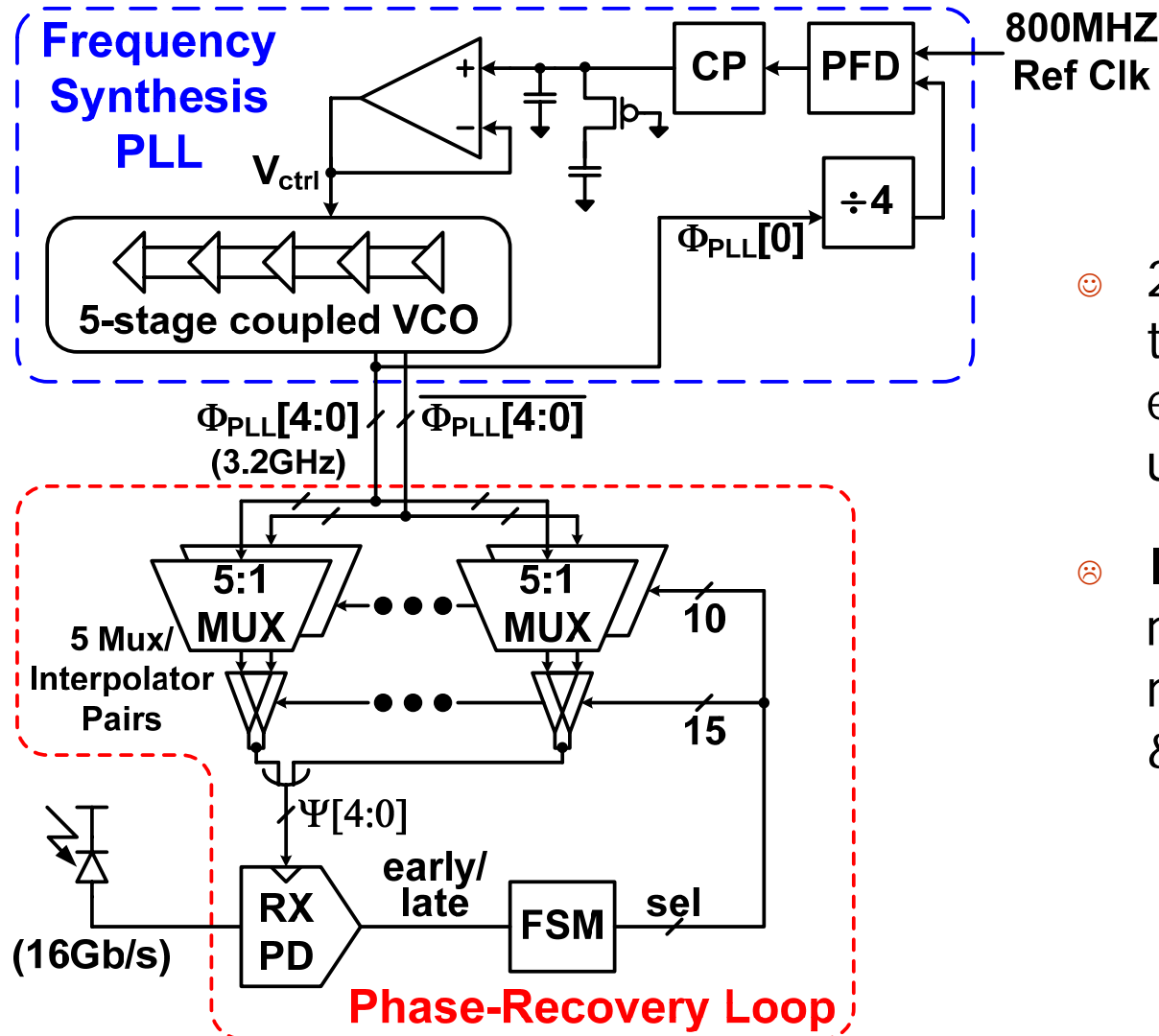


- ☺ 2 degrees of freedom to filter VCO noise & erroneous phase updates
- ☹ Input demultiplexing receiver requires multiple phase muxes & interpolators

Dual-Loop CDR w/ Feedback Interpolation

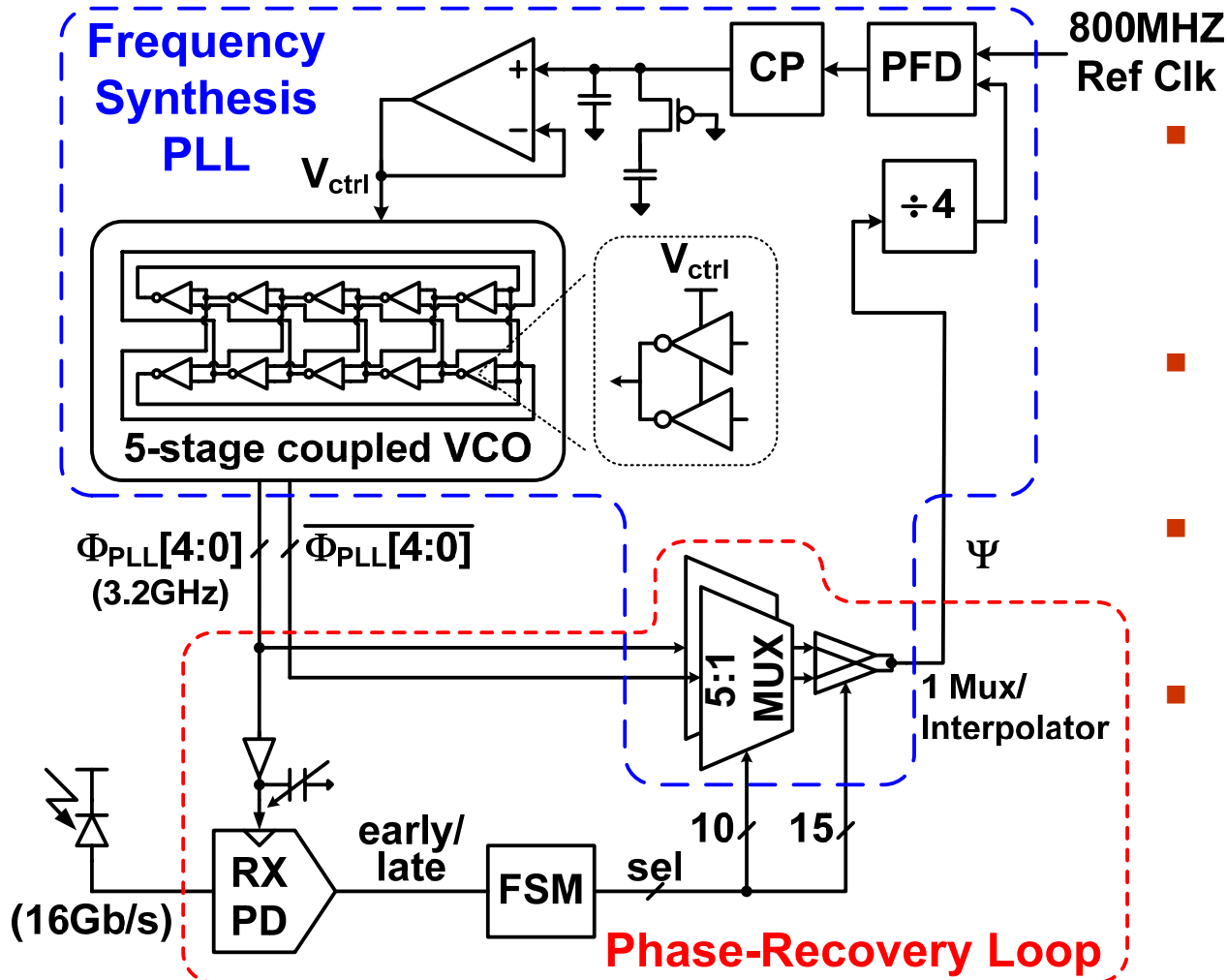

- Extends [Larsson:99] to input demultiplexing receiver
- Only one phase mux/interpolator pair
- Filtering of interpolator switching
- Path from VCO to samplers
 - Minimal Delay
 - Static – allows offset cancellation



Dual-Loop CDR w/ Feedback Interpolation

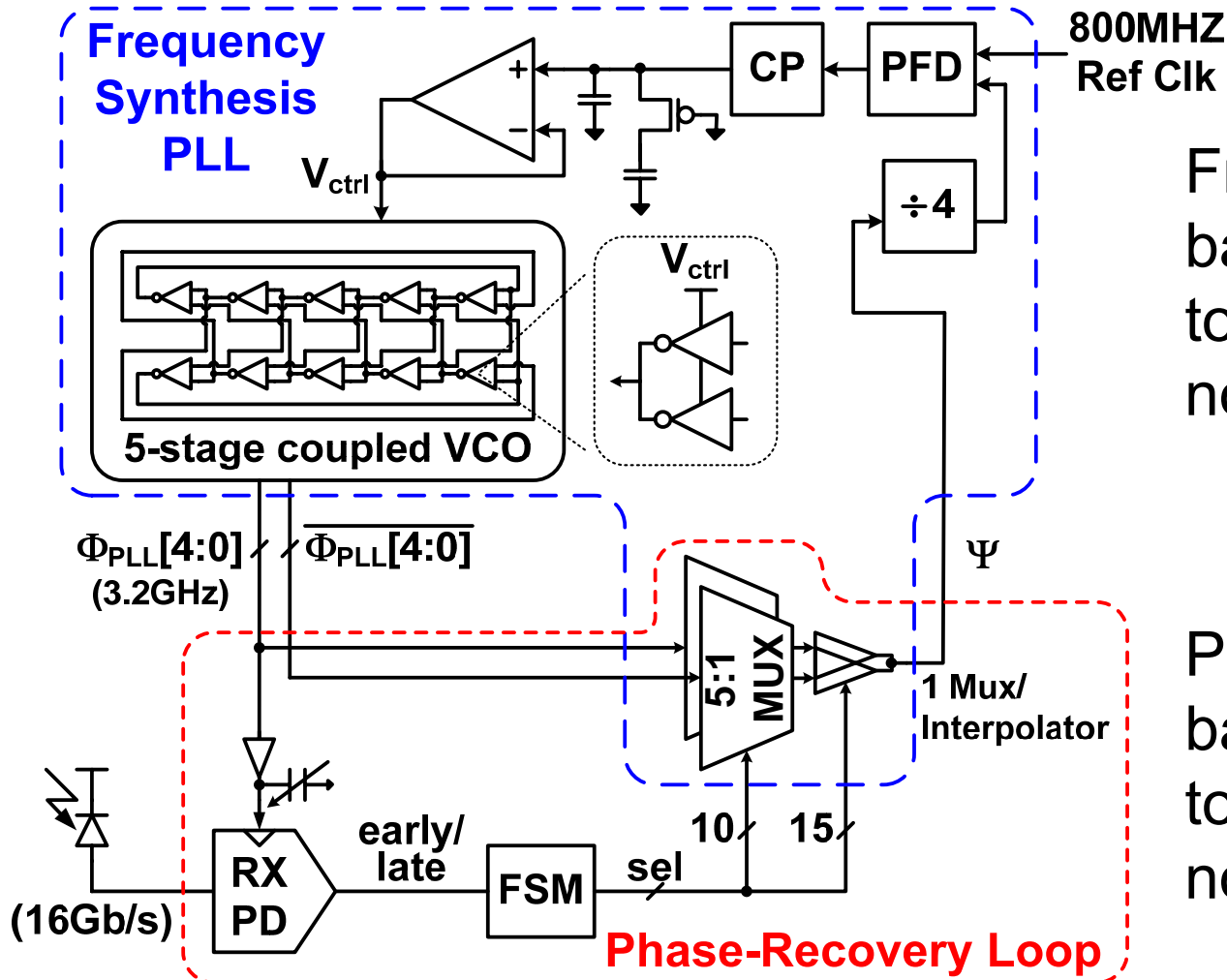

Frequency loop bandwidth = 40MHz to minimize VCO noise

Phase loop bandwidth < 4MHz to minimize input noise


Baud-Rate Phase Detection

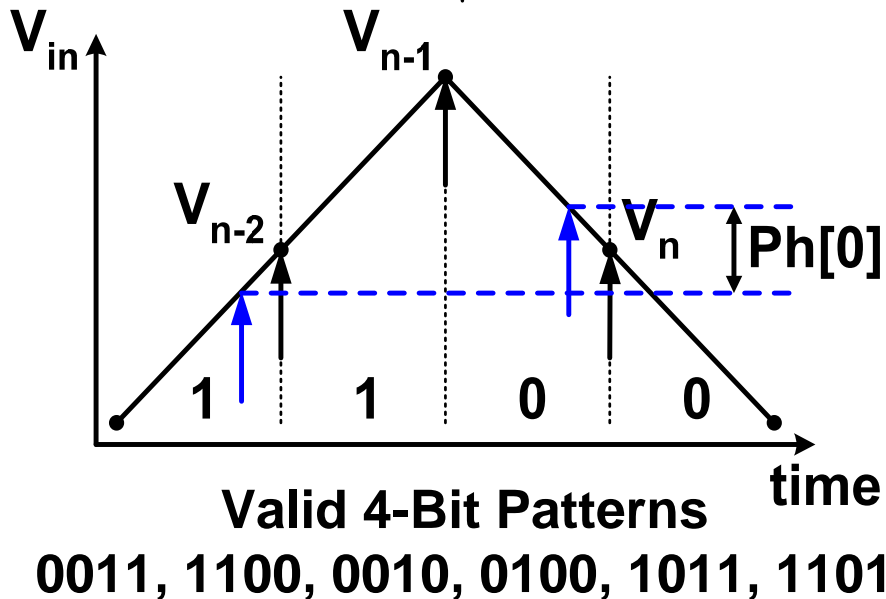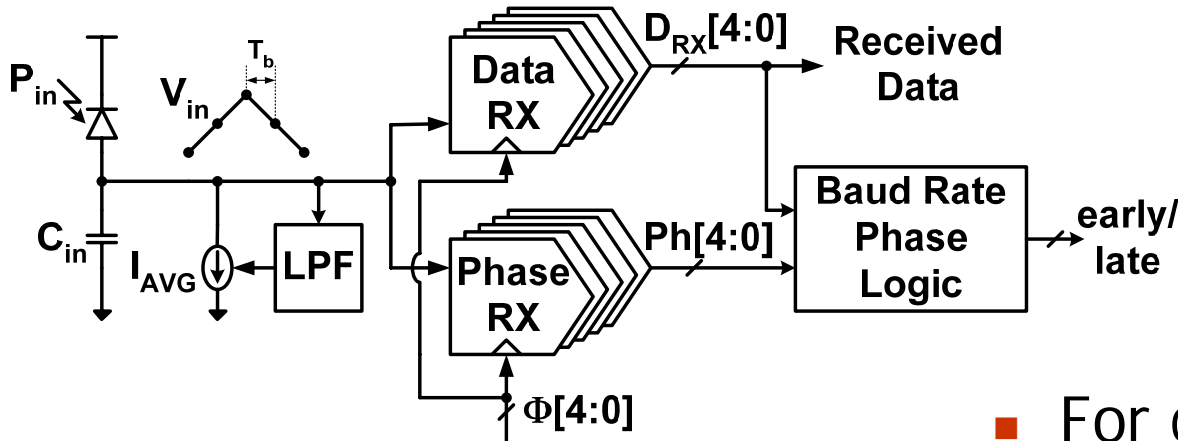


- For certain 4-bit patterns compare $V_{in}(n)$ with $V_{in}(n-2)$ [Emami:04]
- ☺ No "quadrature" phases required
- ☹ Reduces net update rate to 18.75%

Clock Recovery Performance

CDR Disabled

 


CDR Activated

 


- RX clock frequency = 3.2GHz (16Gb/s)
- Jitter increases only marginally when CDR activated
 - $1.74\text{ps}_{\text{rms}}, 12.9\text{ps}_{\text{pp}} \gg \gg 1.90\text{ps}_{\text{rms}}, 15.1\text{ps}_{\text{pp}}$
 - Sufficient filtering of input noise

Phase Correction Circuitry

Tunable Delay Clock Buffers

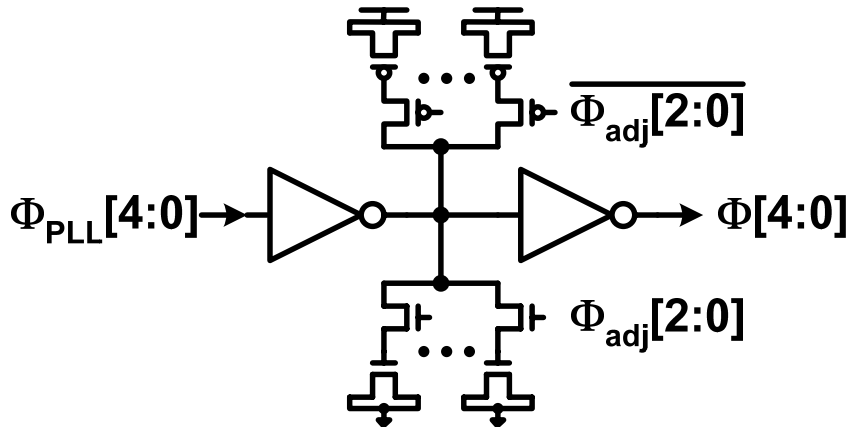

Phase Correction Performance


 


- Static phase offset corrected with tunable delay clock buffers
 - Digitally-adjustable capacitive loads
 - Phase range at 16Gb/s is $\pm 12\%$ UI


Outline

- Introduction
- Optical transmitters
- Optical receiver
- Clock and data recovery
- Optical link system performance
 - VCSEL link
- Conclusion



Optical Transceiver Testing

  

Transmitted Bits

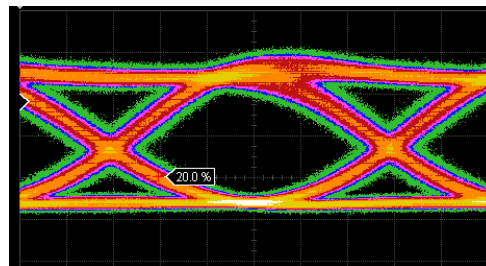


RX Input Node

  


Receiver Sensitivity

 
- Test Conditions
 - 8B/10B data patterns (variance of 6 bits)
 - Long runlength data (variance of 10 bits)
- BER < 10^{-10}



Transceiver Power Consumption

 

Power Breakdown at 16Gb/s


 


- Power at 16Gb/s = 129mW (8.1mW/Gb/s)
- Power scales with data rate
 - Mostly CMOS circuitry
 - Integrating RX sensitivity improves at lower data rates

Transceiver Performance Summary

Technology	90nm CMOS
Supply Voltages	Vdd=1V, LVdd=2.8V, PDBias=2.5V
Data Rate	5 - 16Gb/s
Extinction Ratio	3dB
Average Optical Launch Power	3.1dBm
RX Input Capacitance	440fF
RX Sensitivity (BER=10 ⁻¹⁰)	
10Gb/s	12.5mV (-9.6dBm)
16Gb/s	20.2mV (-5.4dBm)
Area	0.105mm ²
Power at 16Gb/s	129mW (8.1mW/Gb/s)

  Optical vs Electrical XCVR Performance Comparisons



- Compares favorably due to simple equalization circuitry
- Should scale well
 - Better VCSEL technology
 - Lower capacitance photodetectors
 - Higher data rates \Rightarrow More equalization for electrical channels

Conclusion



- Optical interconnects provide a path to reducing the I/O bandwidth problem
- Proposed optical interconnect architecture is suitable for large scale integration in current/future CMOS technologies
 - VCSEL TX equalizer allows low current operation
 - Reliable MQWM TX capable of $2 \cdot V_{dd}$ voltage drive
 - Low voltage integrating receiver
 - Baud-rate clock recovery

Acknowledgments

- Profs Mark Horowitz, Azita Emami, and David Miller
- Jon Roth for optics/device design of modulator link
- CMP and STMicroelectronics for chip fabrication
- ULM Photonics for VCSELs
- Albis Optoelectronics for photodetectors
- MARCO-IFC for funding support
- Sh. Palermo for encouragement and support


Backup Slides

Equalization Performance

 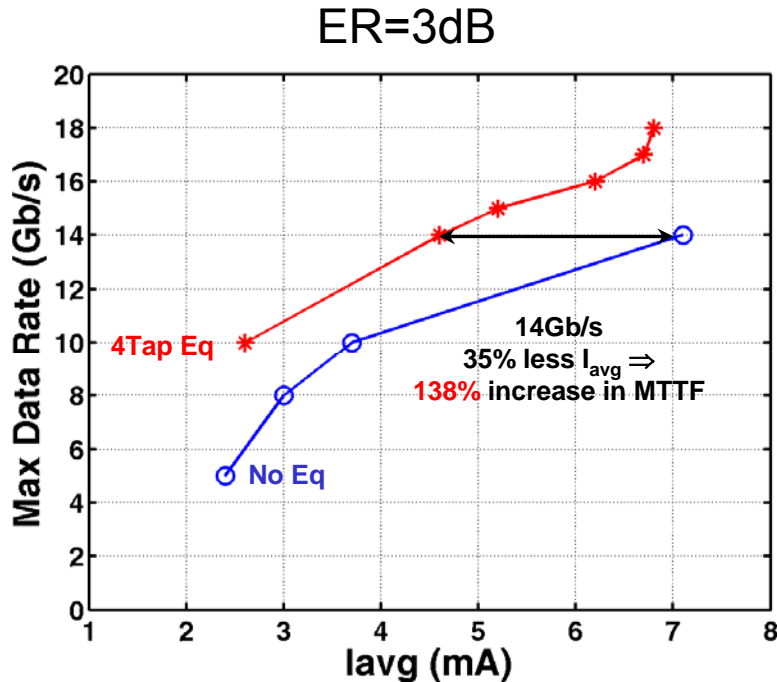


- Maximum data rate vs average current
 - Min 80% eye opening & <40% overshoot
- Equalization allows lower average current for a given data rate
- Linear equalizer limited by VCSEL nonlinearity

13Gb/s Power w/ different tap

 


VCSEL TX Power vs Data Rate & Tap

FCB Channel

 


Wirebond Channel

 


Modulator Driver Reliability Simulations

Maximum nMOS Voltages

 


Maximum pMOS Voltages

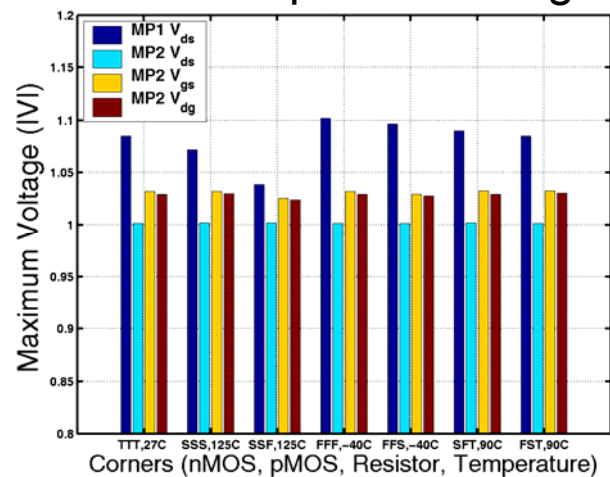

- Transient with random data
- Corner simulations show no output stage voltages exceed 11% of nominal Vdd
- Monte Carlo simulations show tight distributions ($\sigma < 15\text{mV}$)

MN1 V_{DS} Distribution

 

Coupling Capacitor Skew Compensation Performance

