

# **A Pulse-Based CMOS Ultra-Wideband Transmitter for WPANs**

Murat Demirkan\*

Solid-State Circuits Research Laboratory  
University of California, Davis

\*Now with Agilent Technologies, Santa Clara, CA

03/20/2008

# Outline

- Motivation (Why UWB?)
- FCC Emission Limits
- Antenna Characterization
- UWB Transmitter Design
- Wide Tuning-Range VCO Design
- Summary

# Outline

- Motivation (Why UWB?)
- FCC Emission Limits
- Antenna Characterization
- UWB Transmitter Design
- Wide Tuning-Range VCO Design
- Summary

# Motivation

- **Consumers demand indoor wireless connectivity**
- **Current WLAN/WPAN solutions insufficient**
  - 802.11a/g → 54Mbps (WLAN)\*
  - Bluetooth → 3Mbps (WPAN)
- **High data-rate applications:**
  - Wireless USB (480Mbps)
  - Real time AV Streaming (HDTV), AV Conference

\*w/o MIMO

## Motivation Cont.'d

**Shannon's Law:** The theoretical maximum information rate of a channel in bits per second is

$$C = BW \cdot (1 + \log_2 SNR)$$

**UWB can provide very high data rates at low transmit power levels compared to narrowband**


Low SNR 

- implement in low-cost CMOS
- Power Amplifier not required

# Outline

- Motivation (Why UWB?)
- FCC Emission Limits
- Antenna Characterization
- UWB Transmitter Design
- Wide Tuning-Range VCO Design
- Summary

# FCC Limits

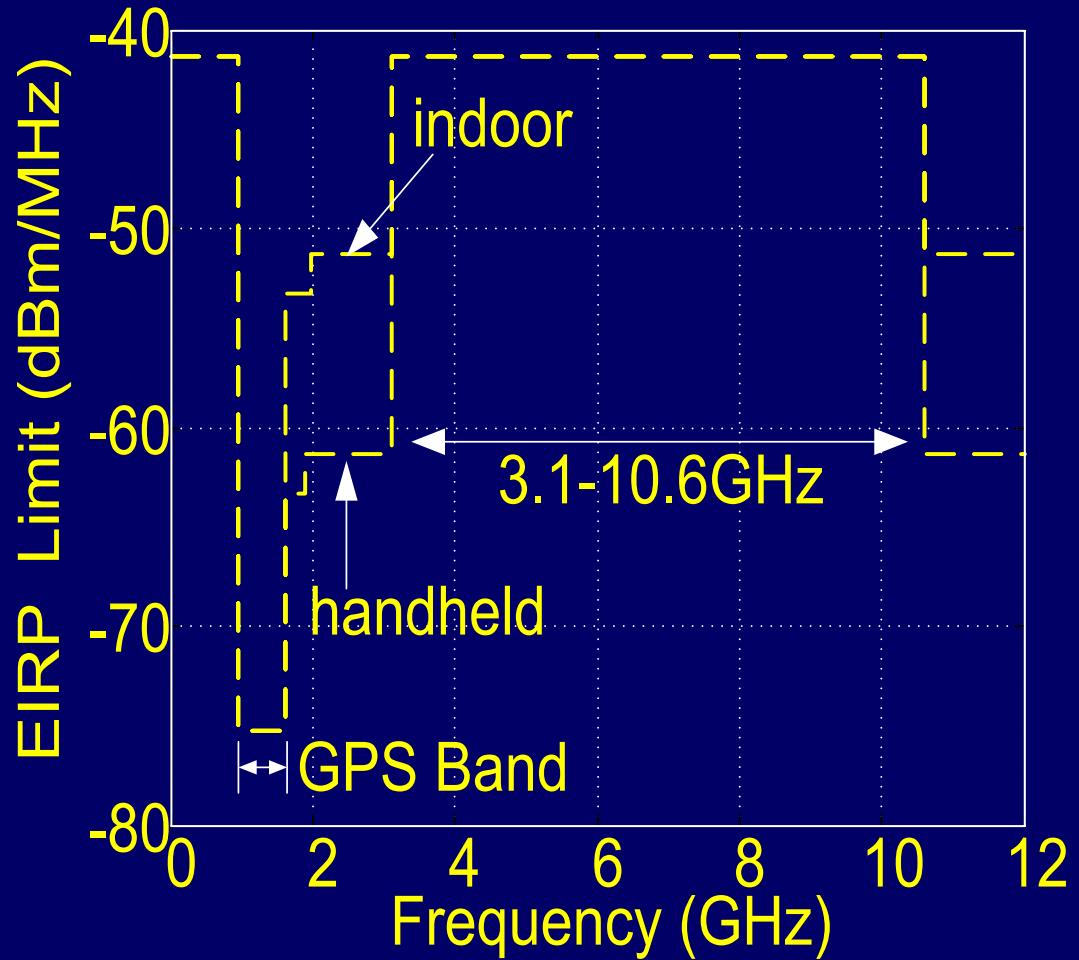

**FCC:**

UWB device has  
 $BW_{frac} > 0.2$  or  $BW > 500\text{MHz}$

$$BW_{frac} = \frac{2(f_H - f_L)}{f_H + f_L} = \frac{BW}{f_c}$$

**Peak power limit:**

0 dBm EIRP within  
50 MHz of  $f_c$


# Outline

- Motivation (Why UWB?)
- FCC Emission Limits
- Antenna Characterization
- UWB Transmitter Design
- Wide Tuning-Range VCO Design
- Summary

# UWB Antenna Modeling

- **Narrowband Antennas are frequency independent ( $Z_{in}=Z_o$ , Gain)**
- **UWB radios operate in 3.1-10.6GHz ( $Z_{in}(\omega)$ ,  $H(\omega)$ )**
  - Need to simulate EIRP before fabrication
  - Need a circuit-level model to facilitate design
  - Simple lumped models are NOT adequate

# Modeling UWB Antennas

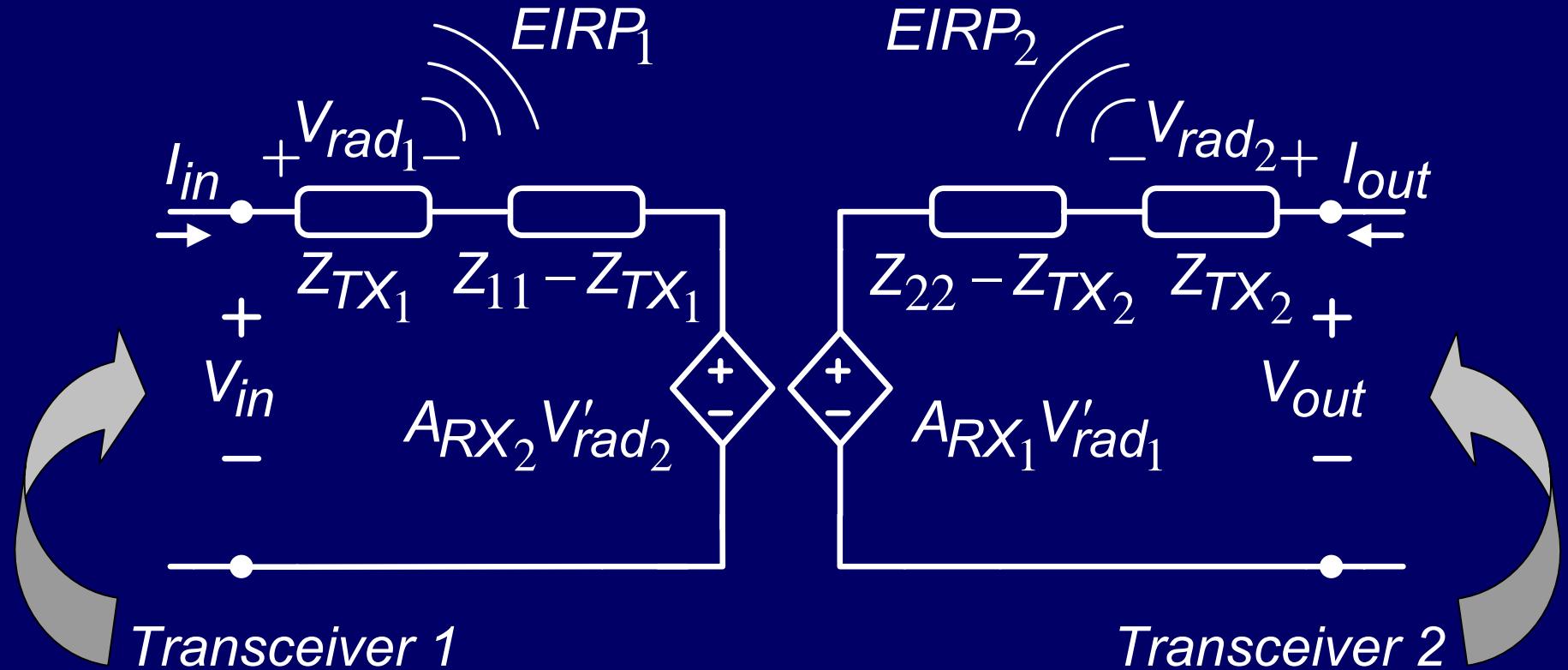


**Bilateral equivalent circuit model for the  
2-antenna network.**

# Outline

- Motivation (Why UWB?)
- FCC Emission Limits
- Antenna Characterization
- UWB Transmitter Design
- Wide Tuning-Range VCO Design
- Summary


# Pulse Generation Methods

Up-Conversion:

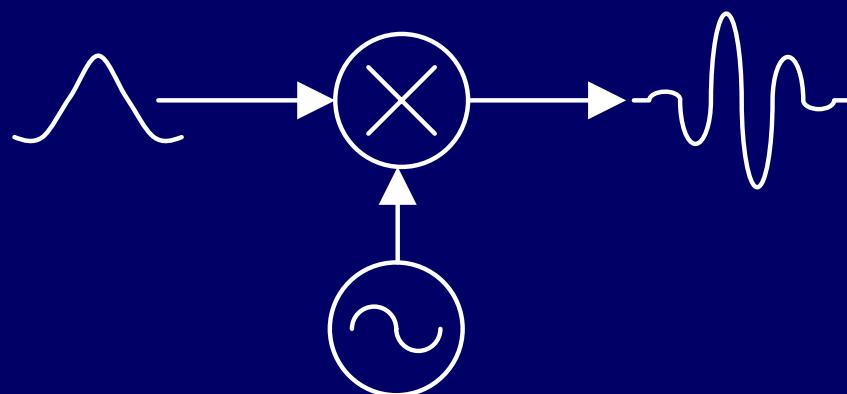

ISSCC 2005  
[Iida et al.]

Filtering:

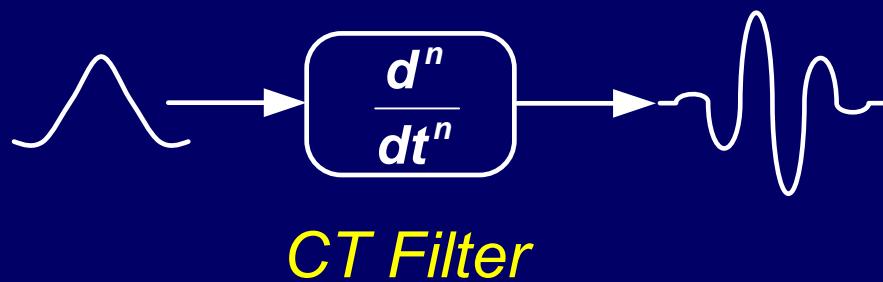


ISSCC 2006  
[Zheng et al.]

*CT Filter*


# FIR Pulse Generator

DT-FIR Filter:

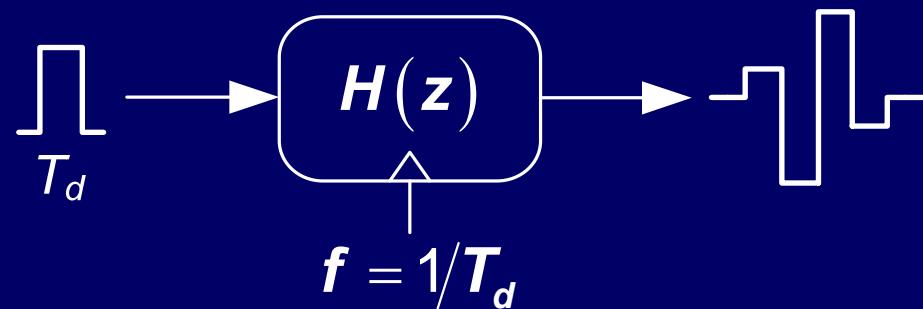


$$H(z) = (1 - z^{-1})^N$$

This work:

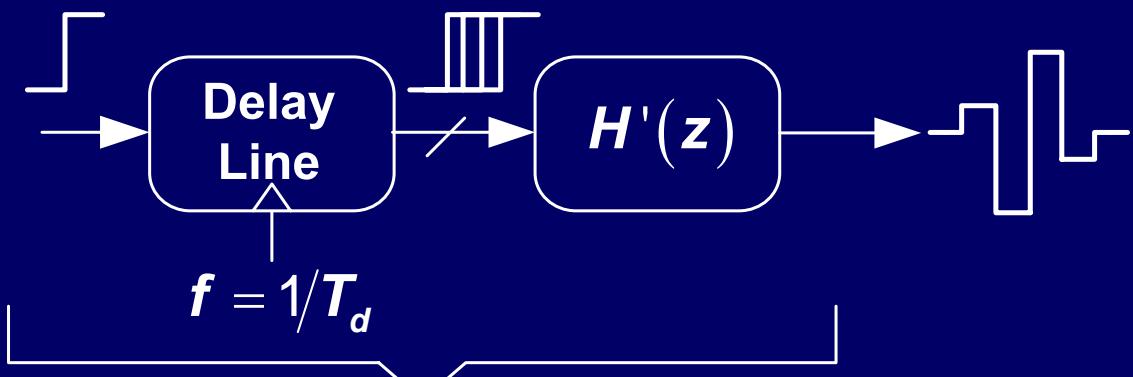


$$H'(z) = (1 - z^{-1})H(z) = (1 - z^{-1})^{N+1}$$


# Transmitter Architecture

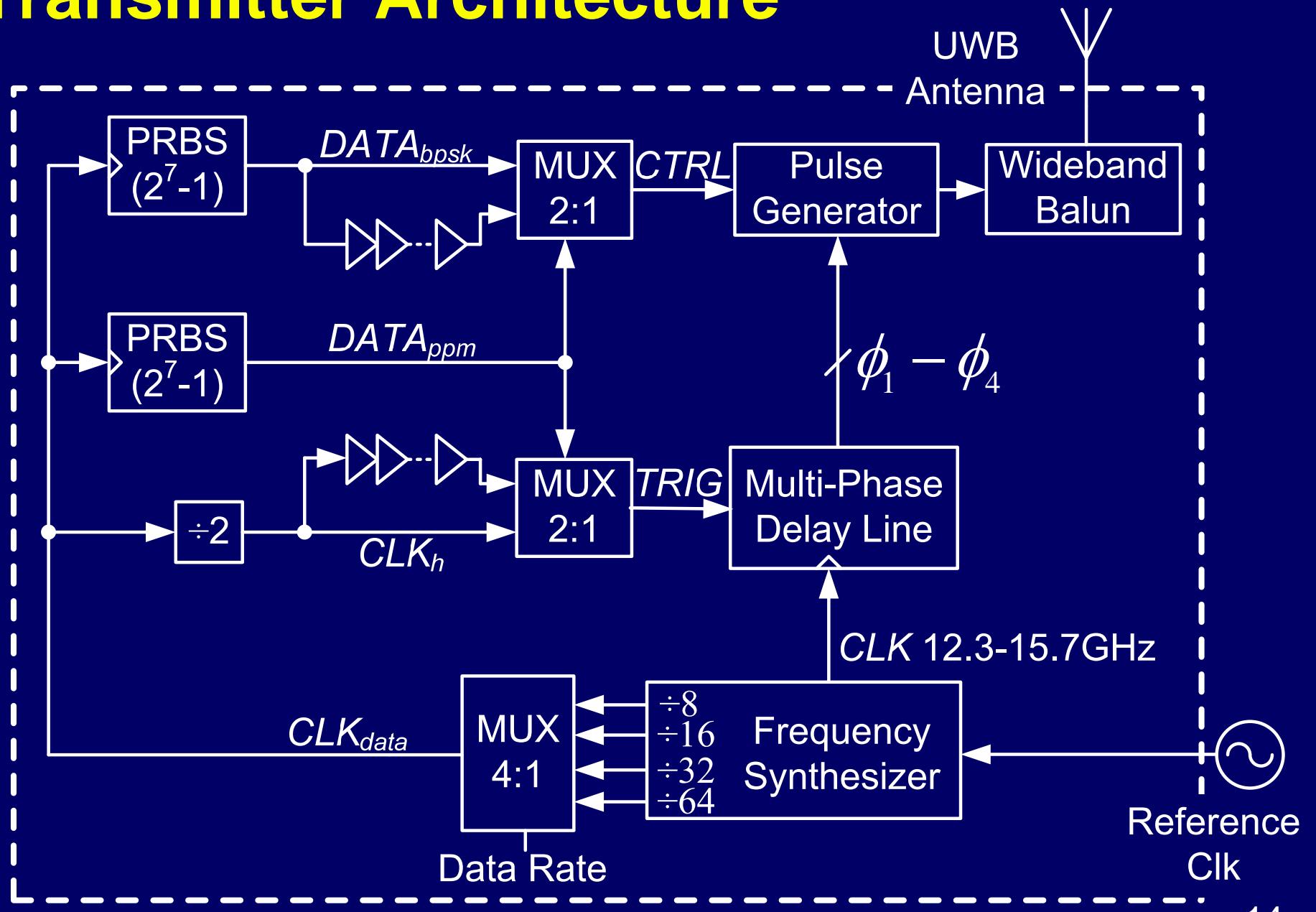


# Transmitter Architecture

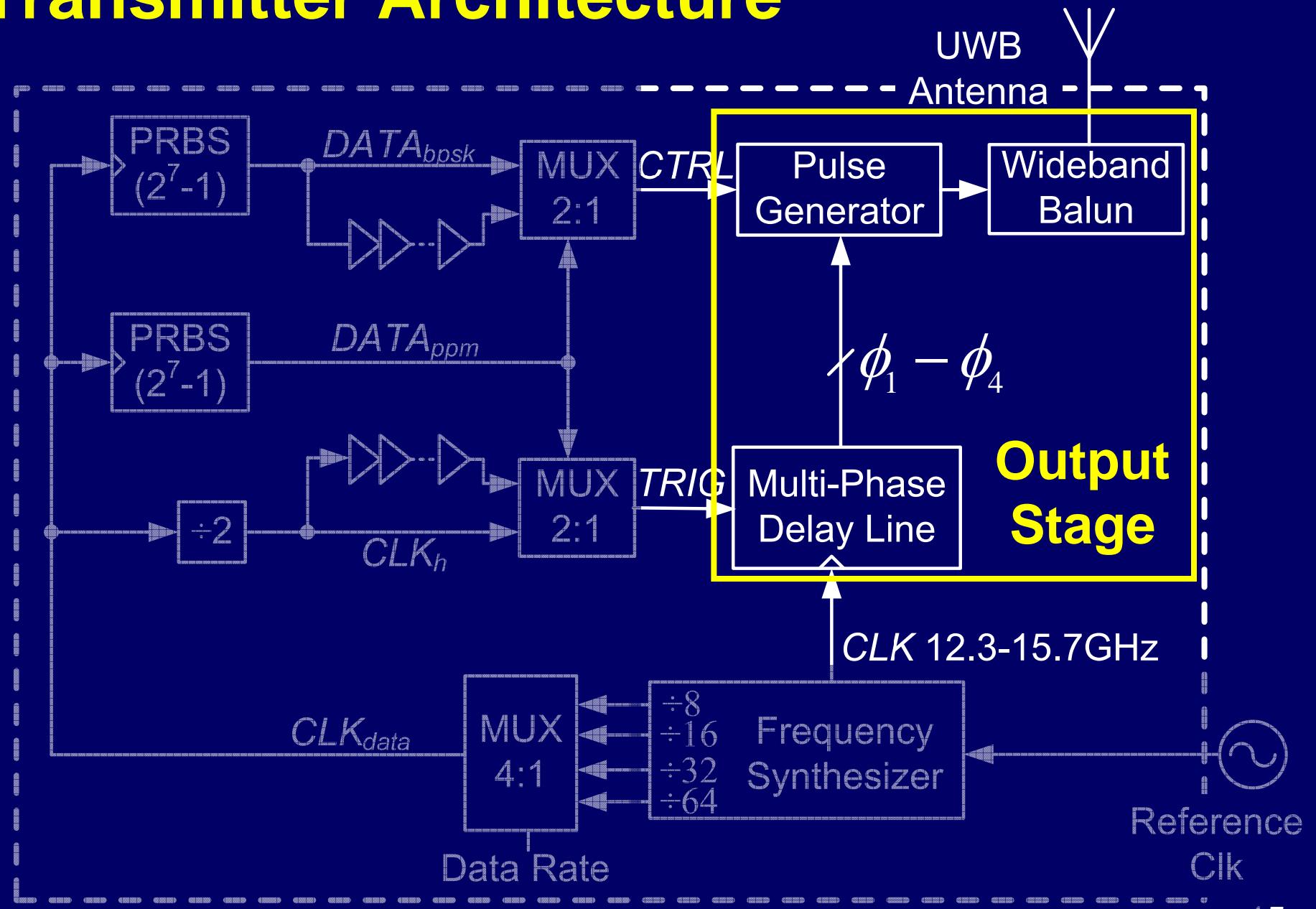



# Transmitter Architecture

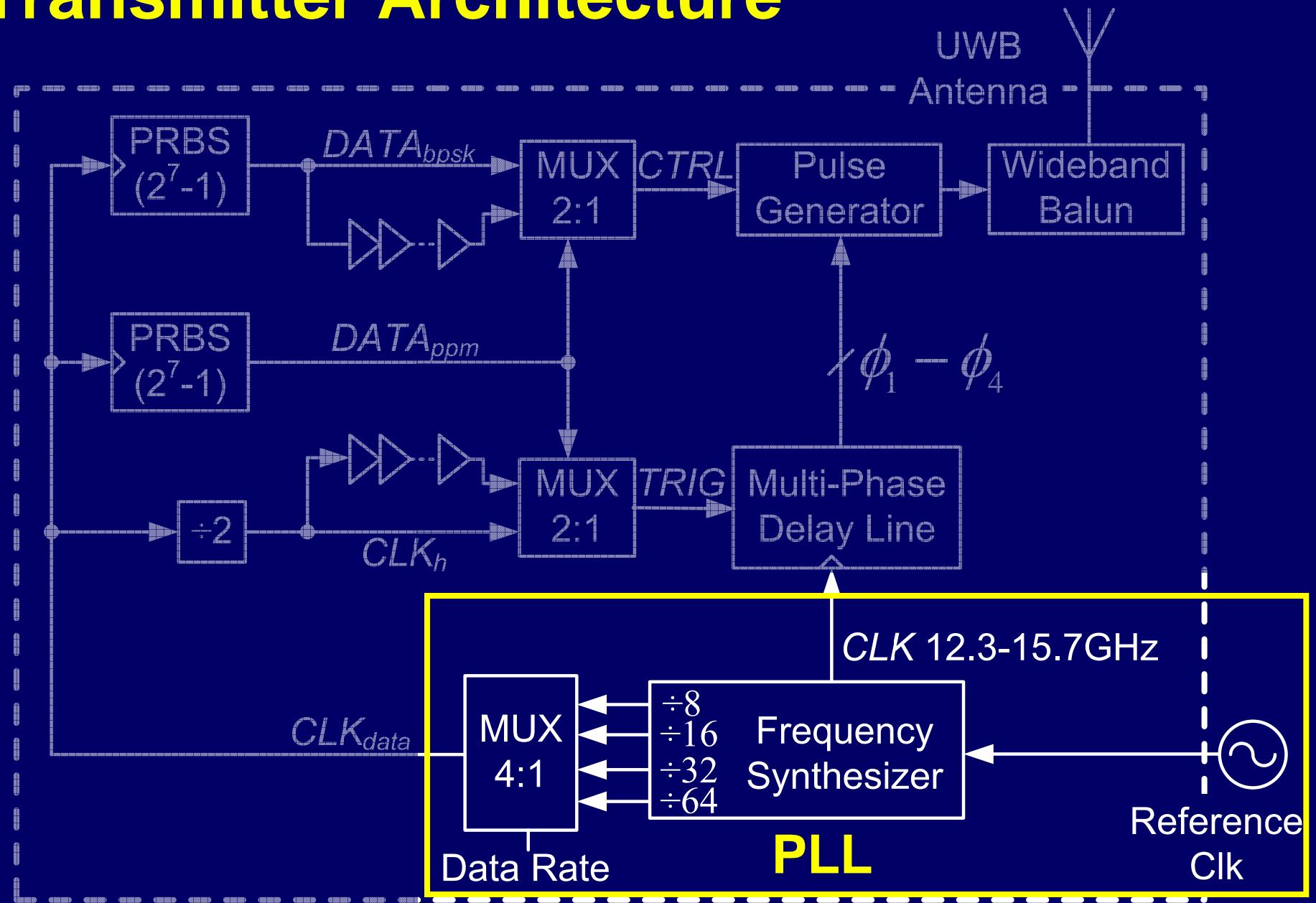



# Transmitter Architecture

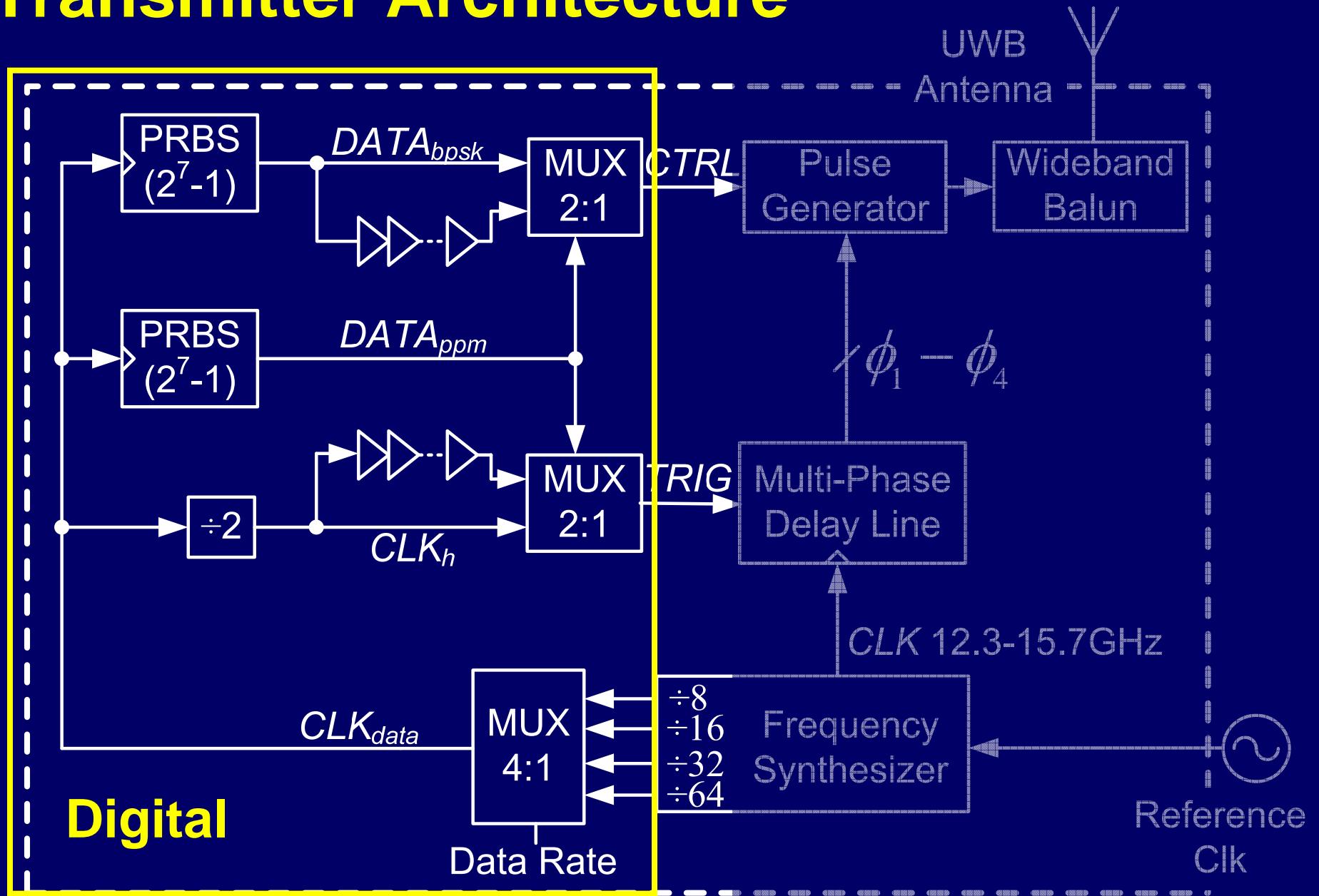


# Output Stage

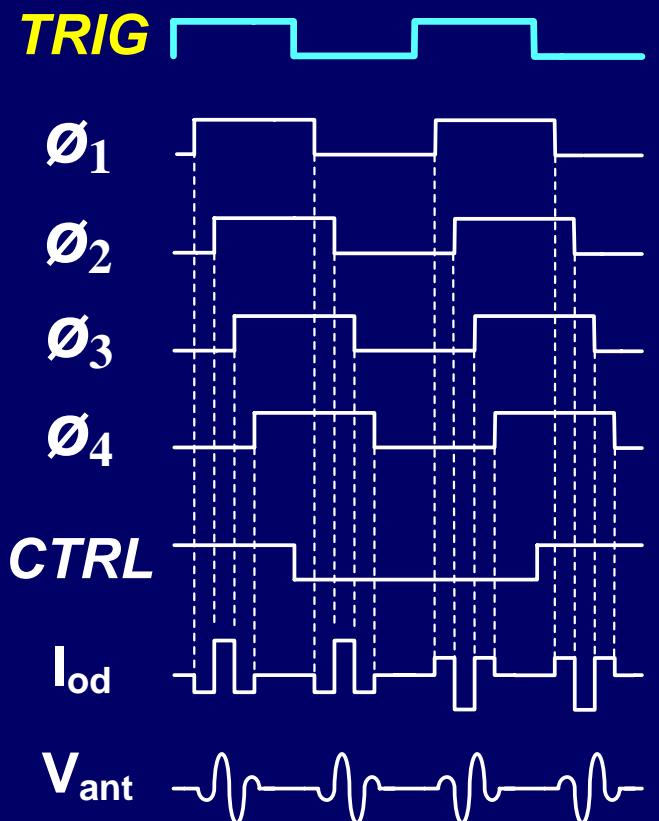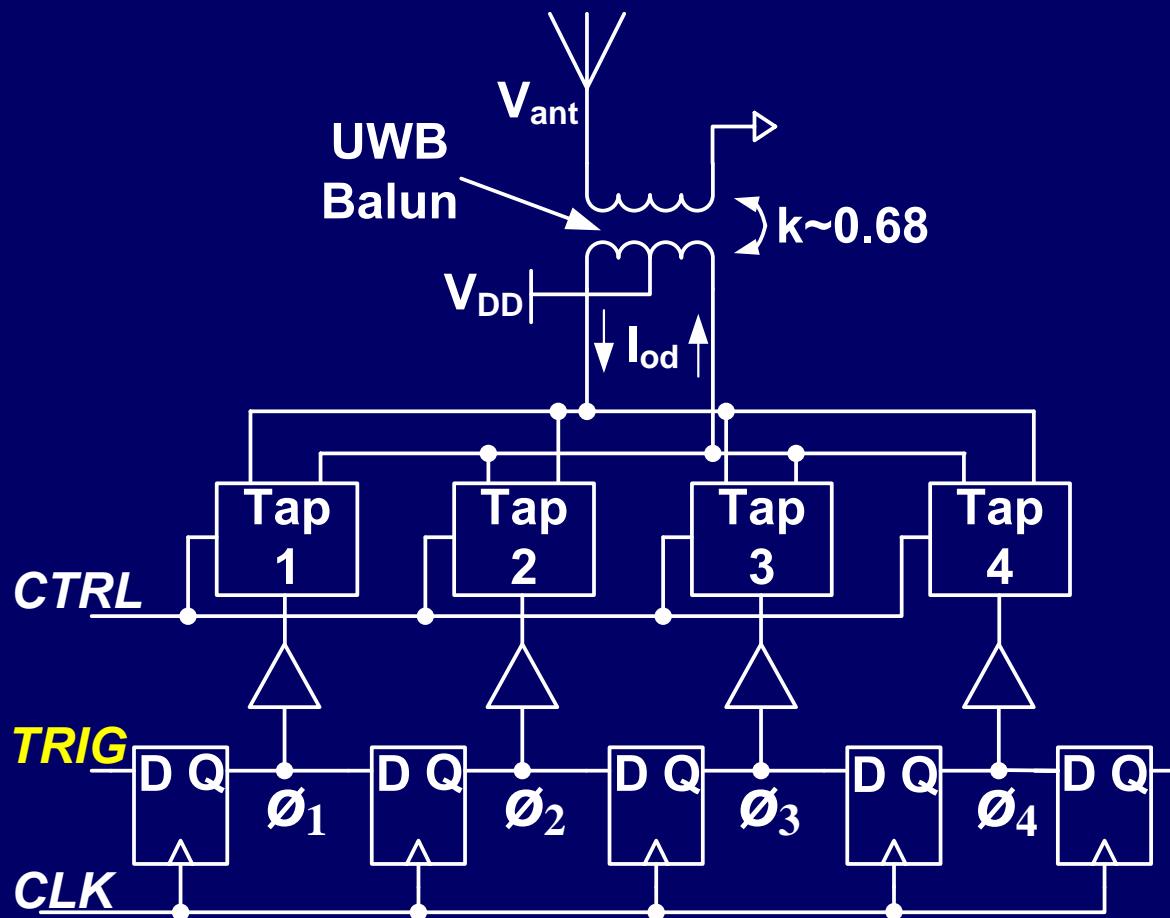



# Output Stage

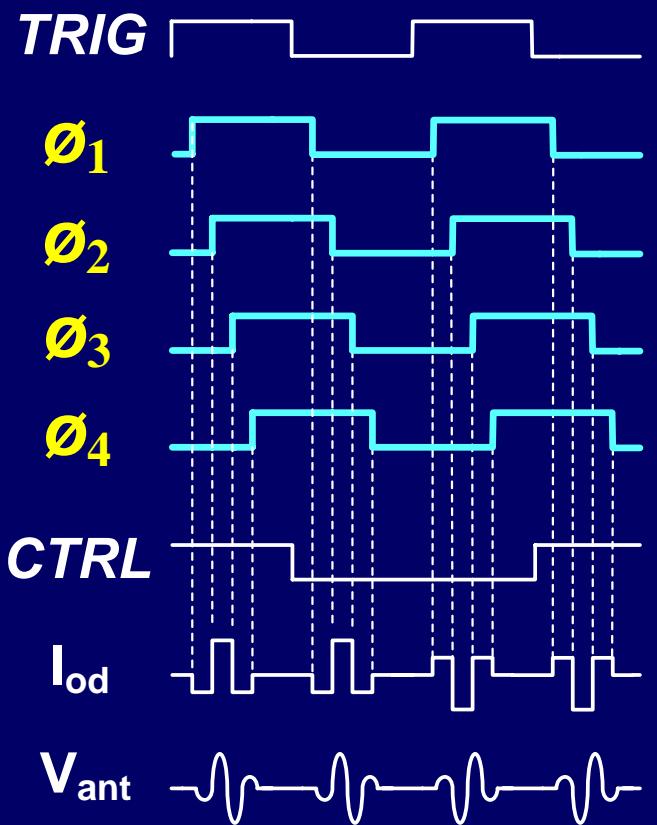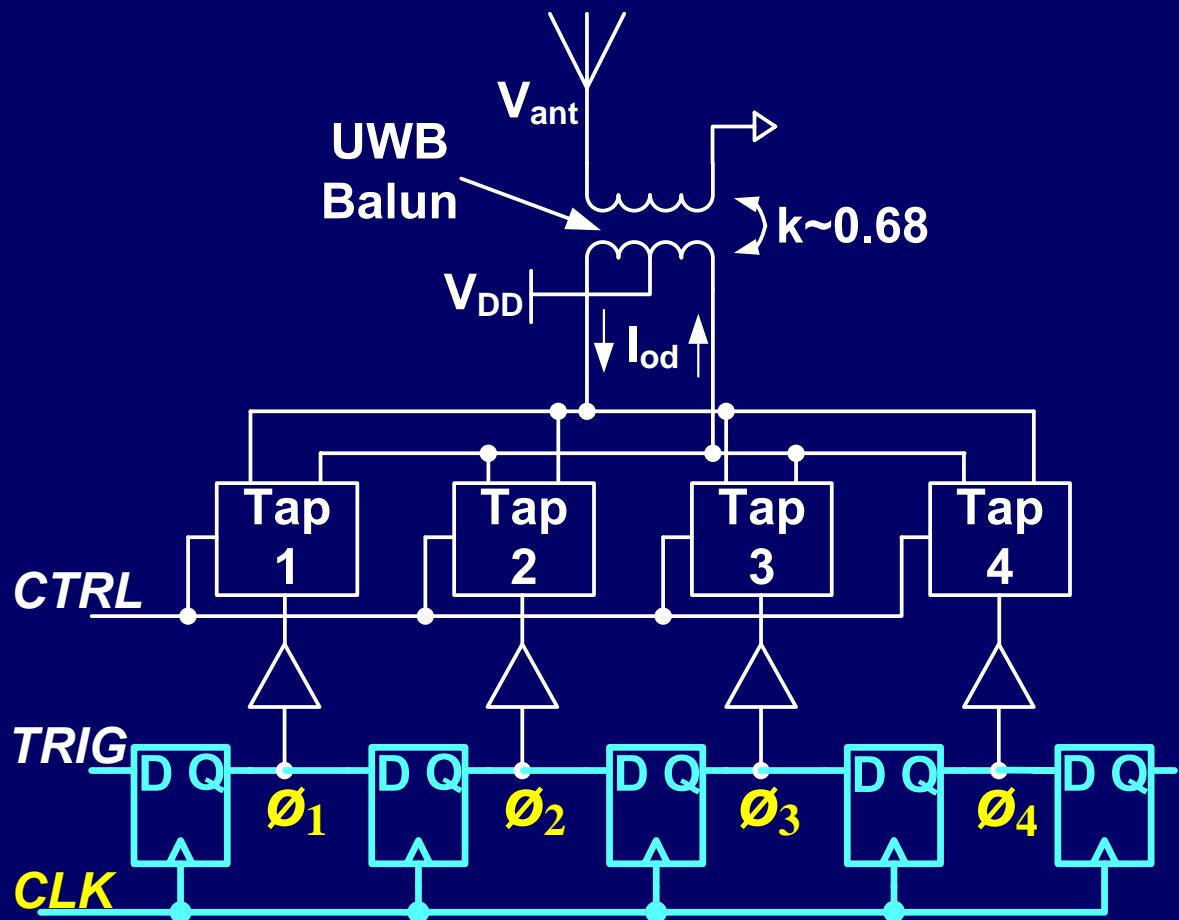


# Output Stage

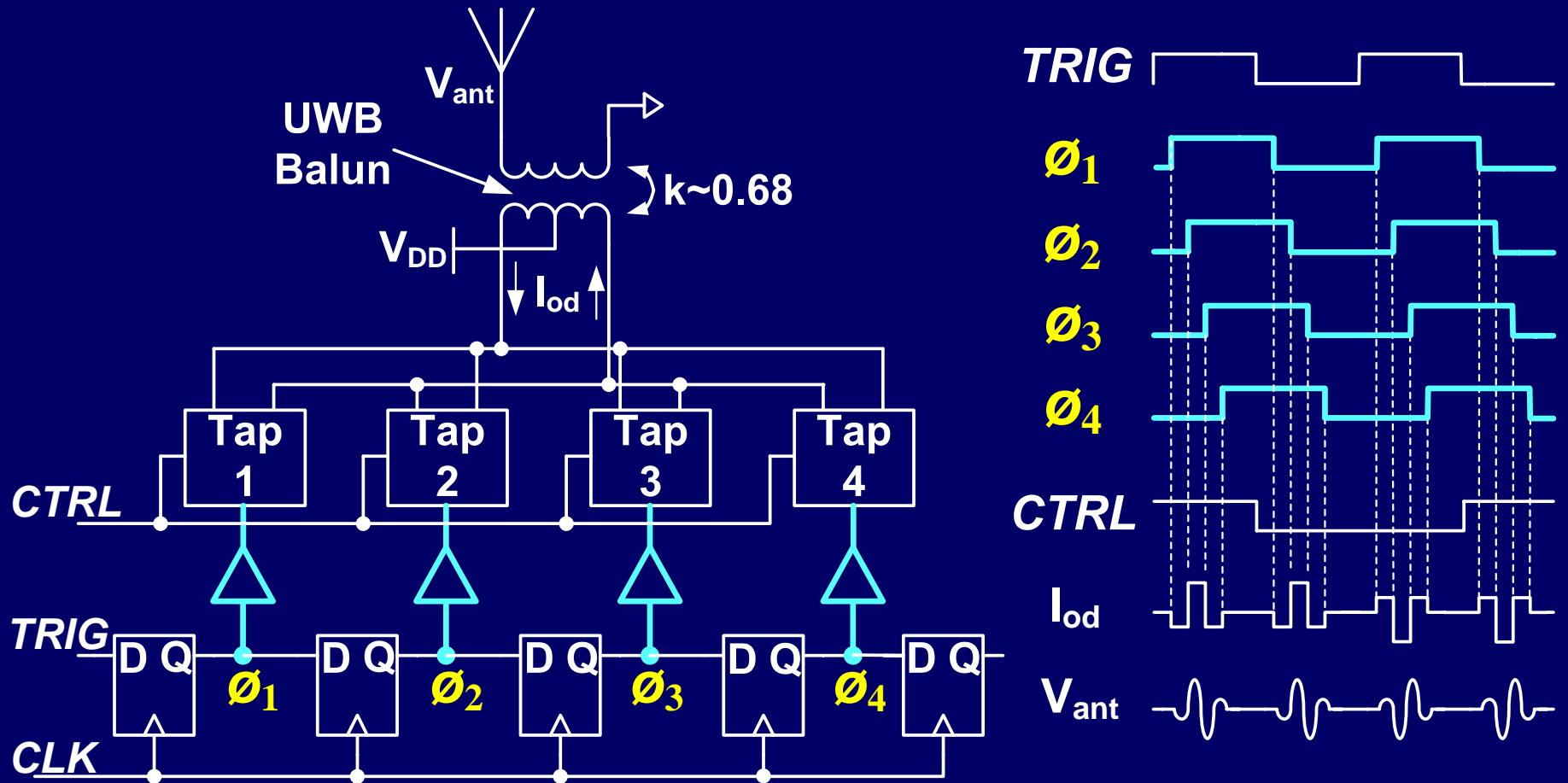



# Output Stage

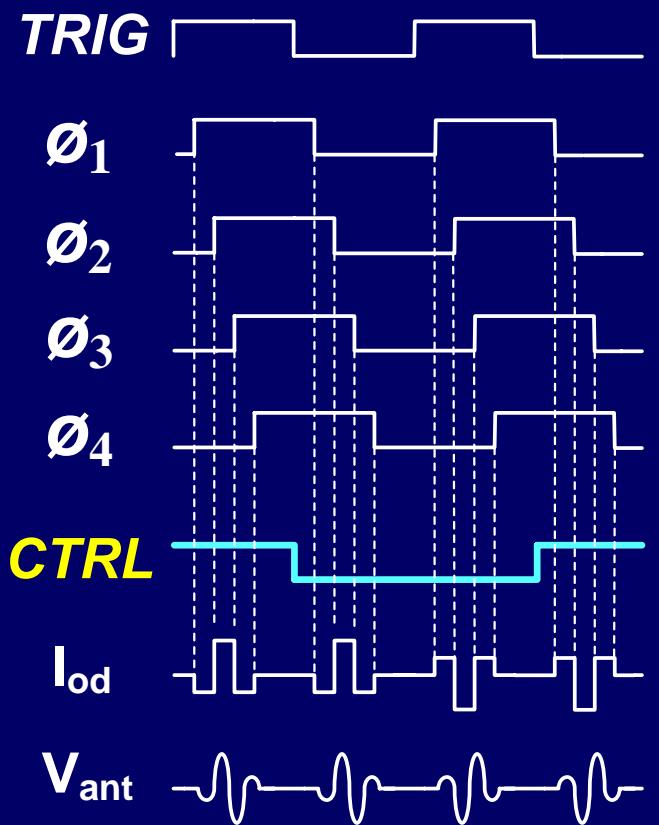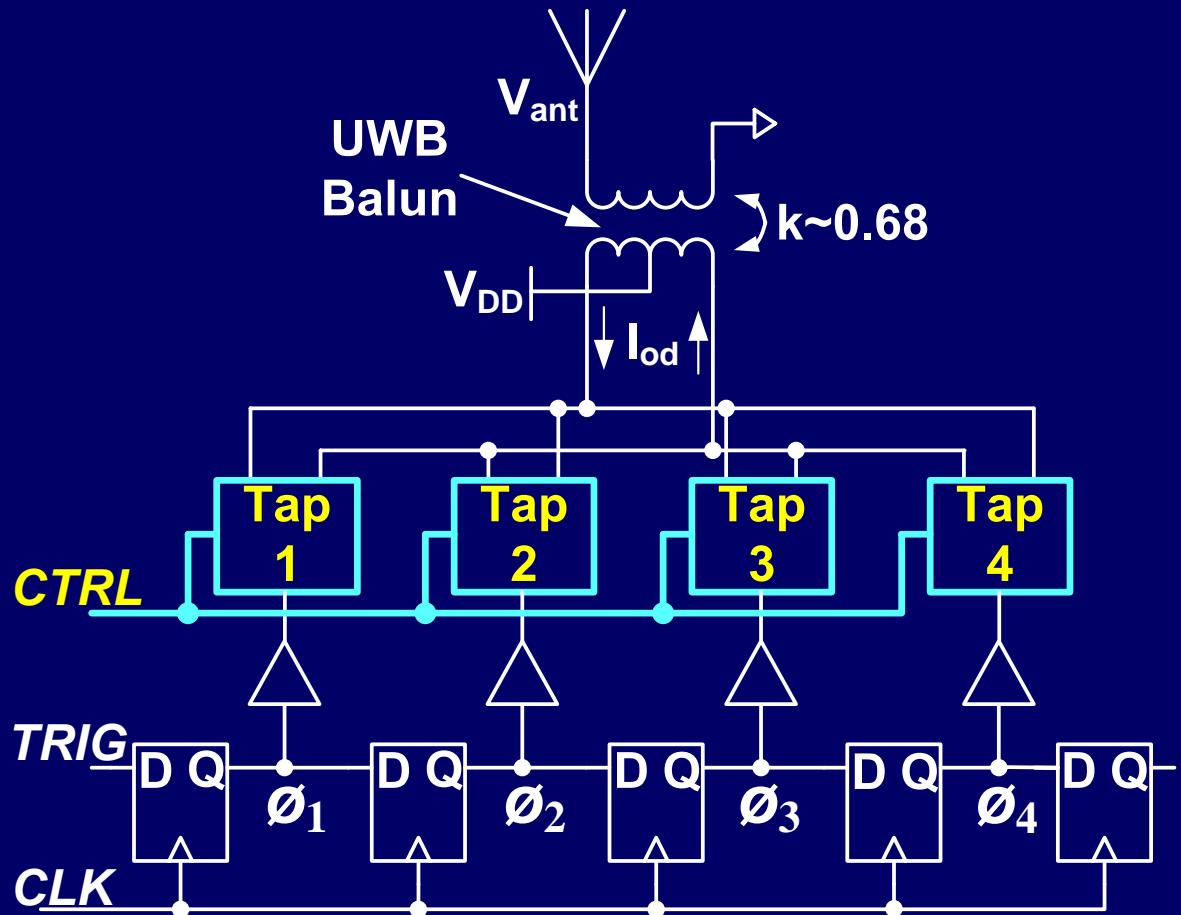



# Output Stage

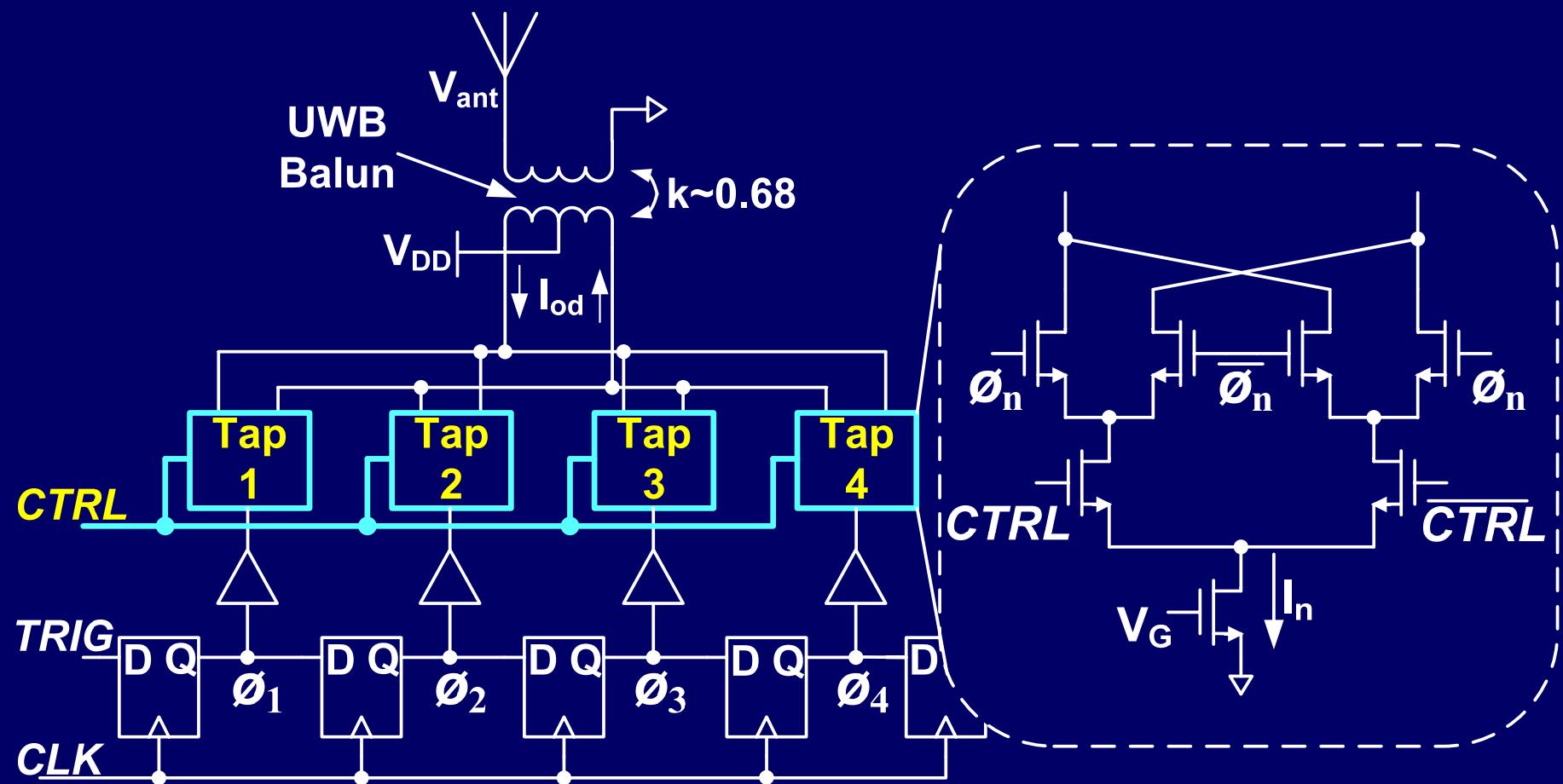


# Output Stage

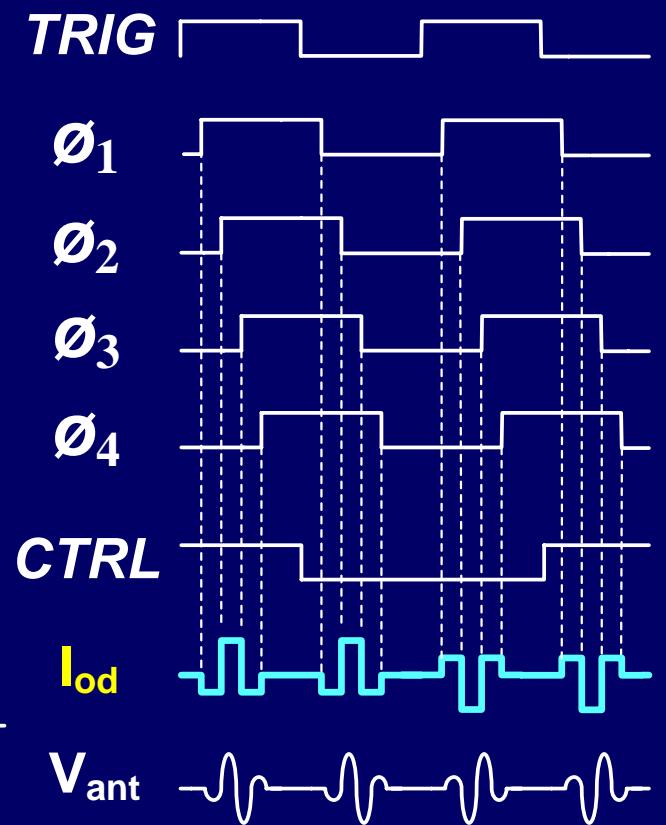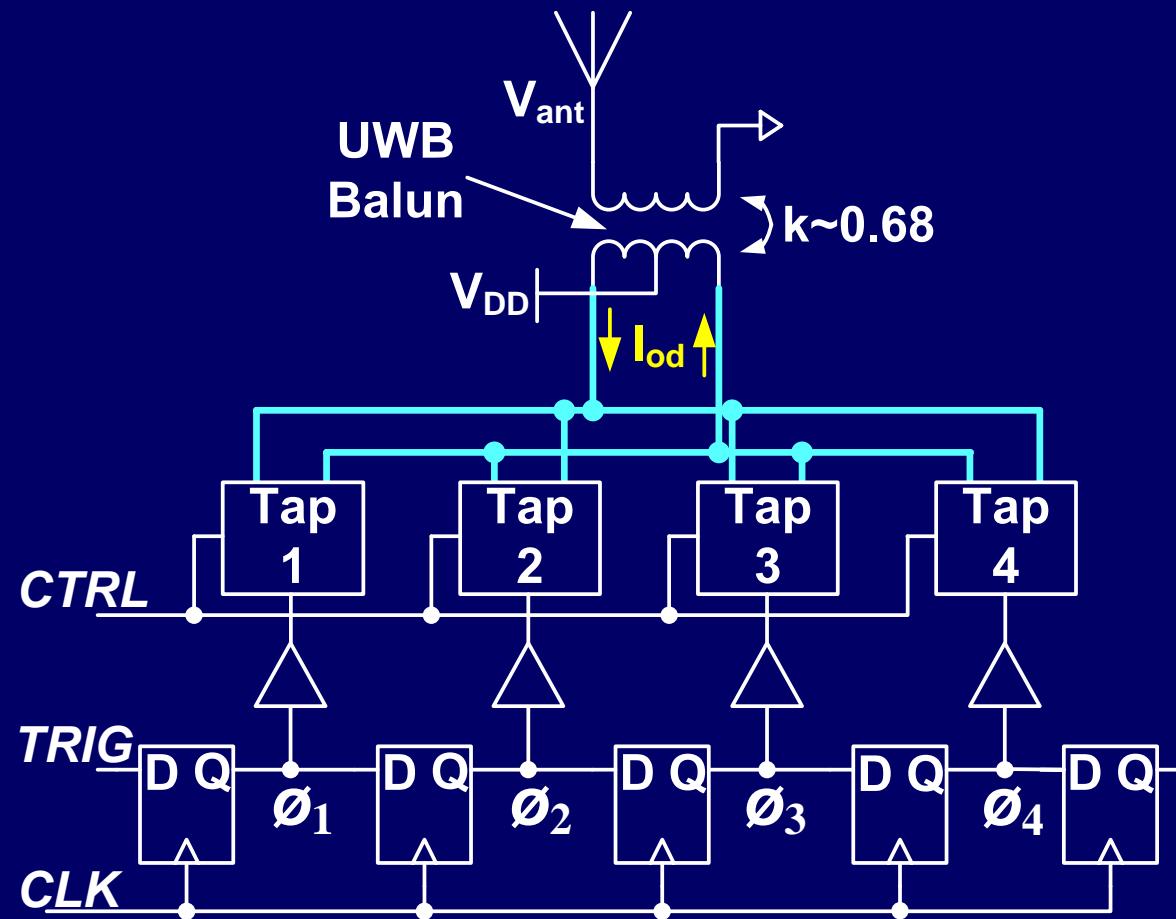

# Output Stage

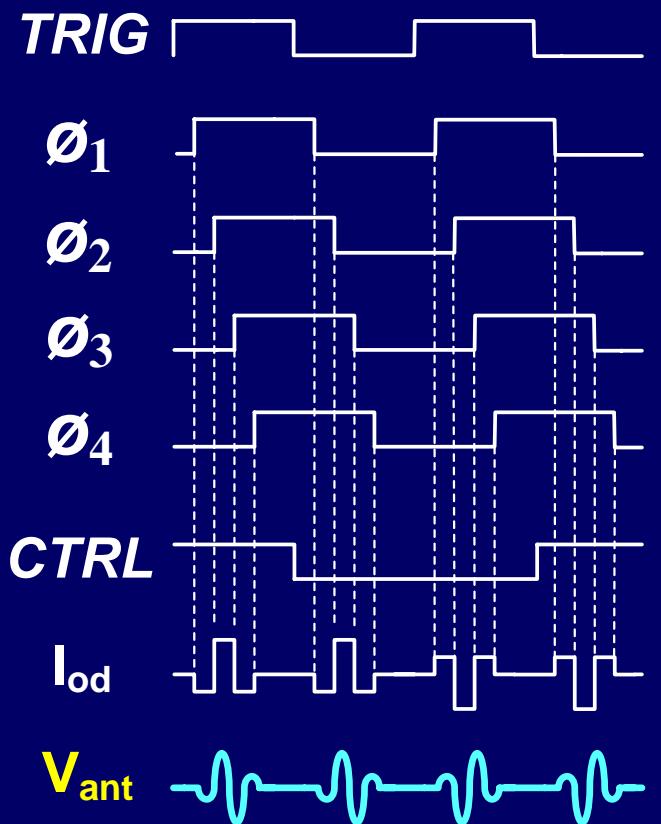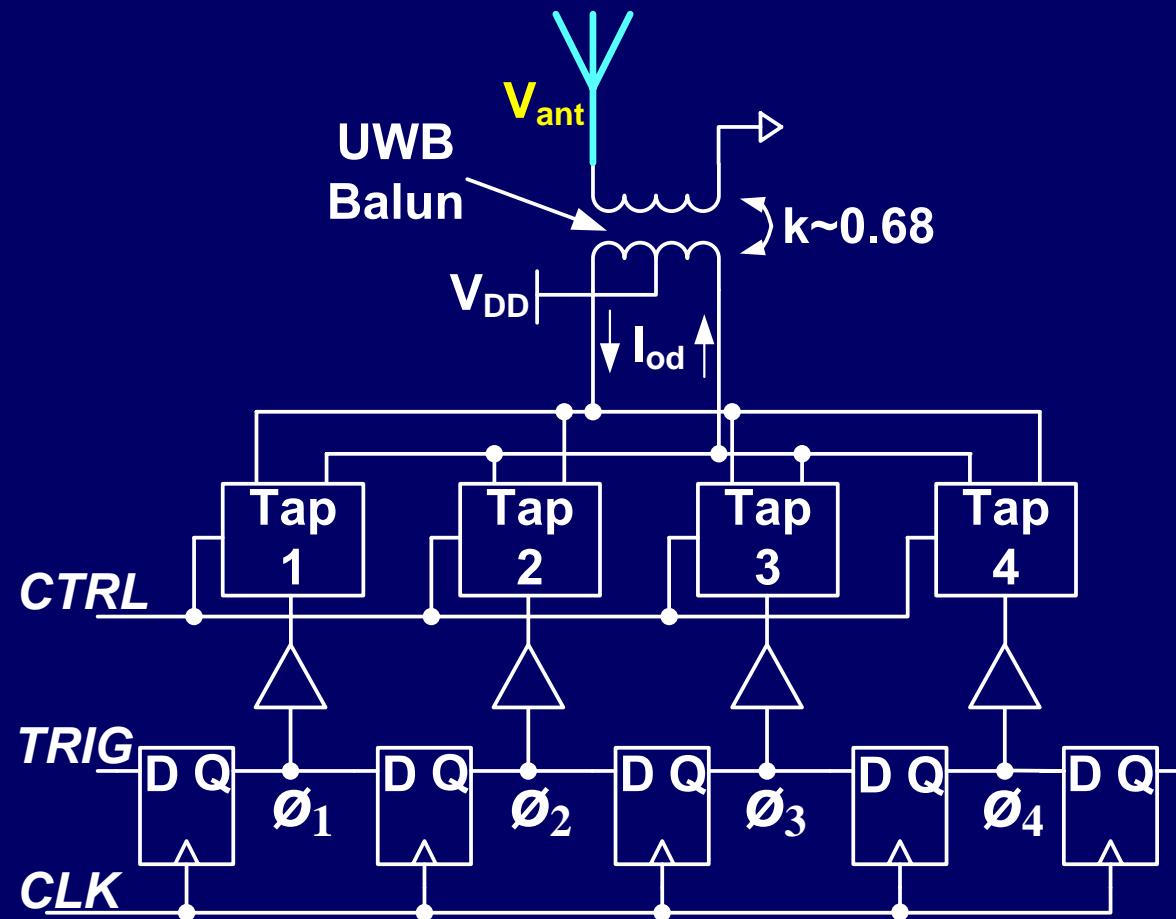


# Frequency Synthesizer (PLL)

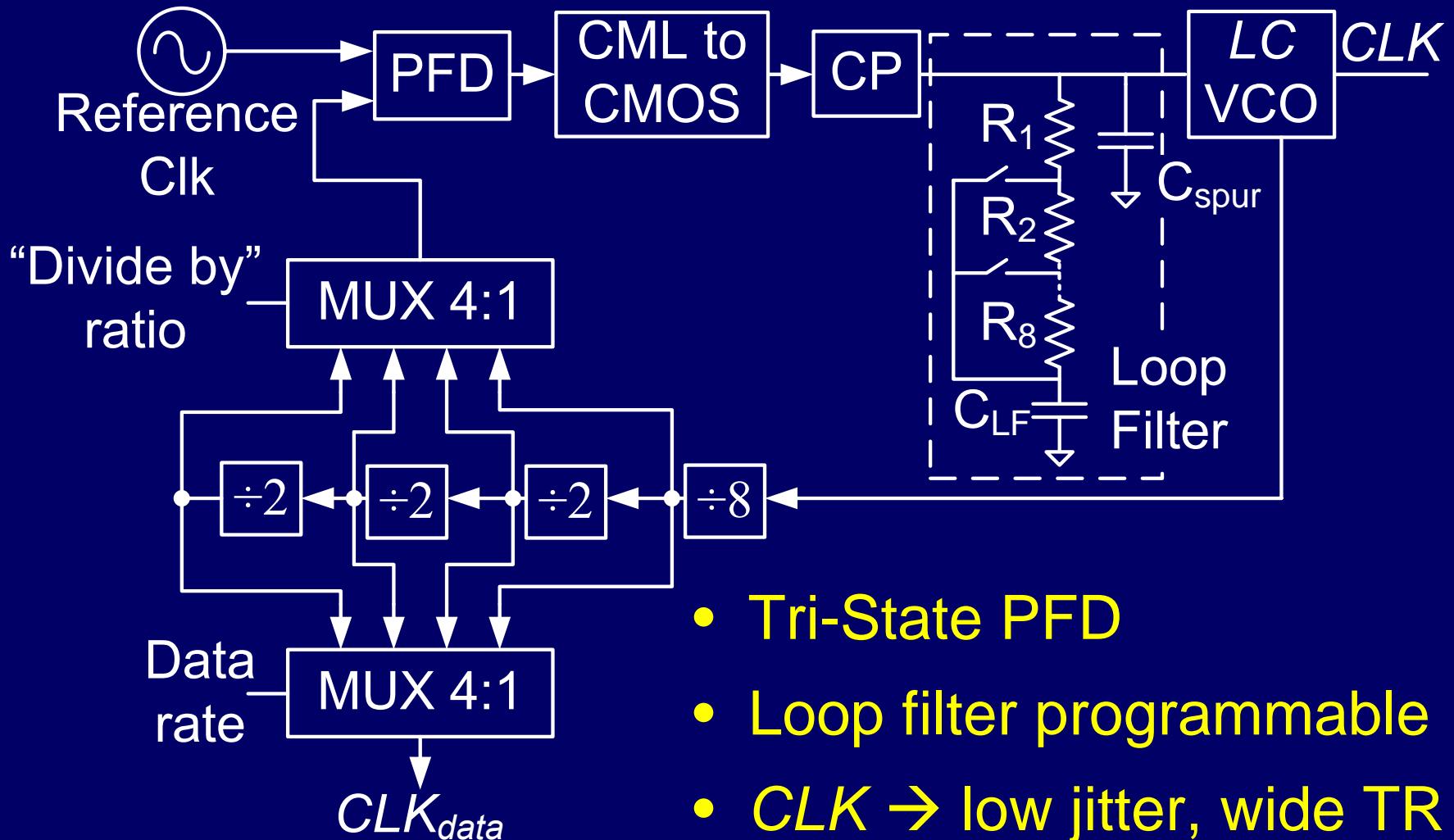


- Tri-State PFD
- Loop filter programmable
- $CLK \rightarrow$  low jitter, wide TR

# Charge Pump

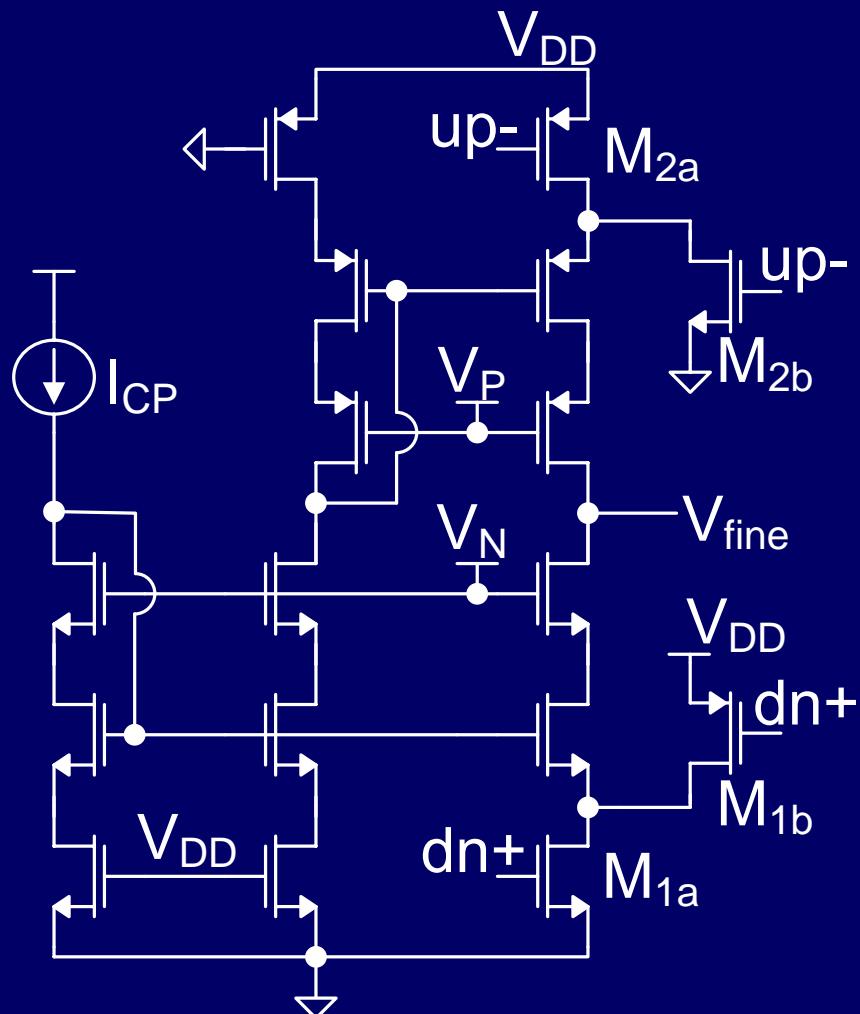


- Single-ended design for simplicity
- Low-voltage cascode current mirrors
- $M_{1a}$  and  $M_{2a}$  are switches
- $M_{1b}$  and  $M_{2b}$  provide discharge path

# Voltage Controlled Oscillator

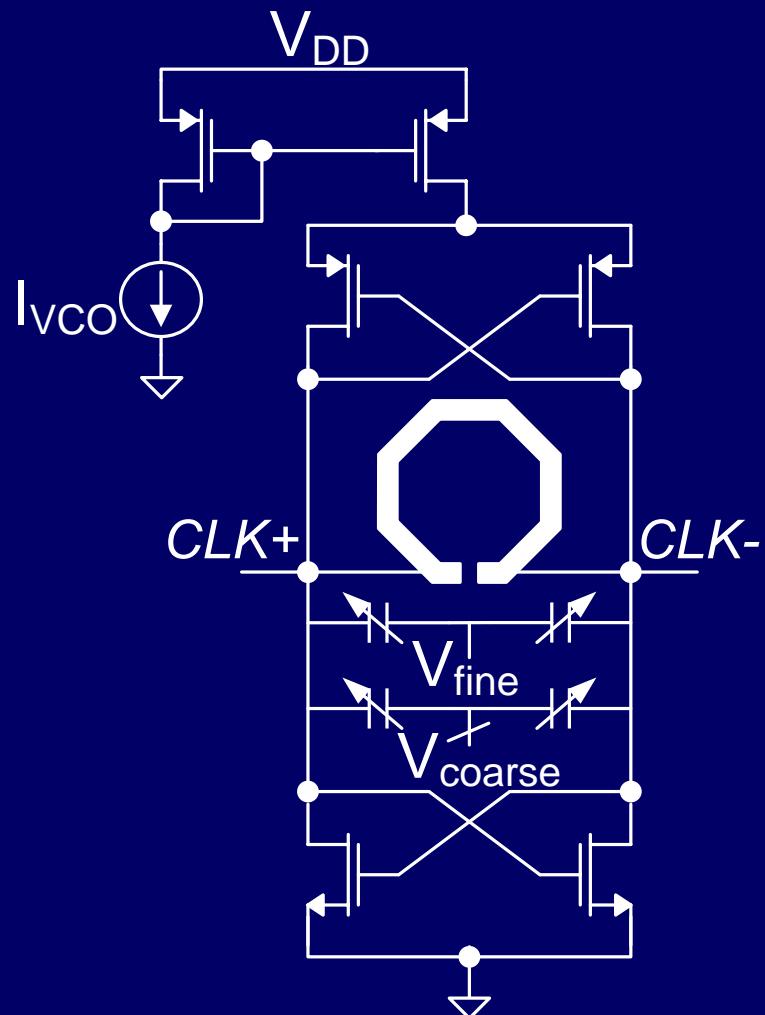


- Single-loop inductor
- AMOS varactors for fine and coarse tuning
- Cross-coupled CMOS
  - Sets bias for AMOS
  - Reduces 1/f noise upconversion


# Measured Phase Noise at 14.4GHz

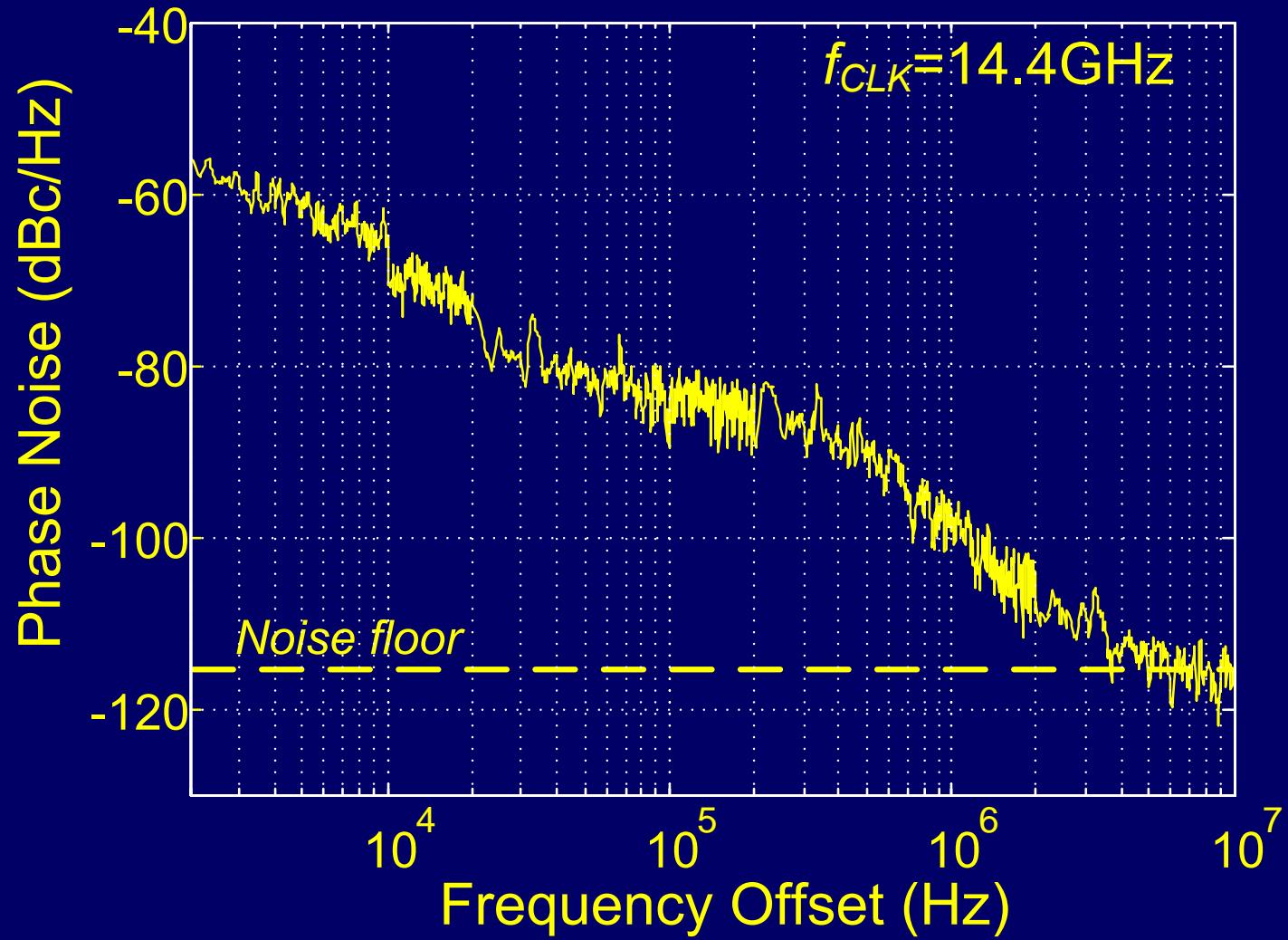

# Simulated and Measured Pulses

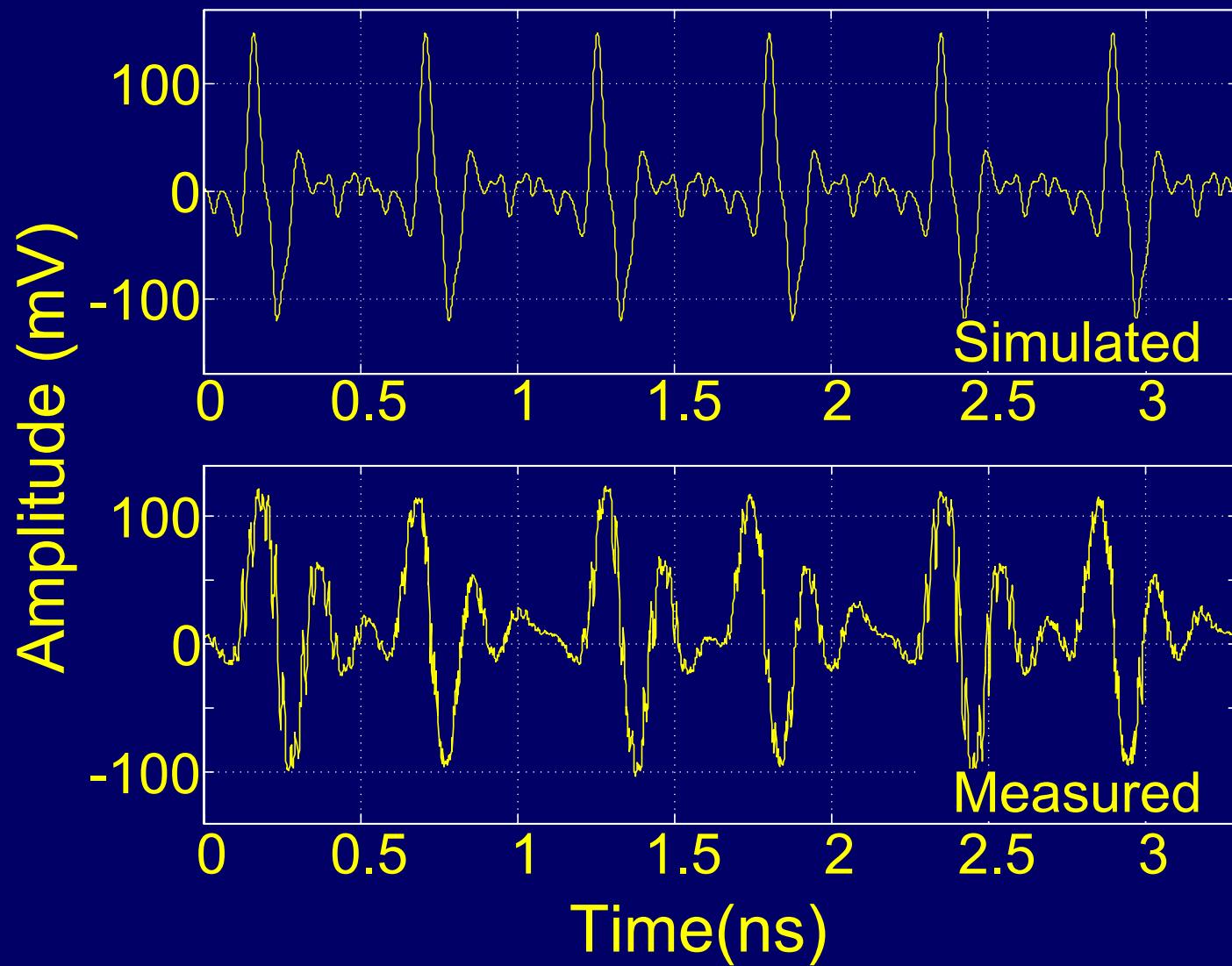


# Measured EIRP

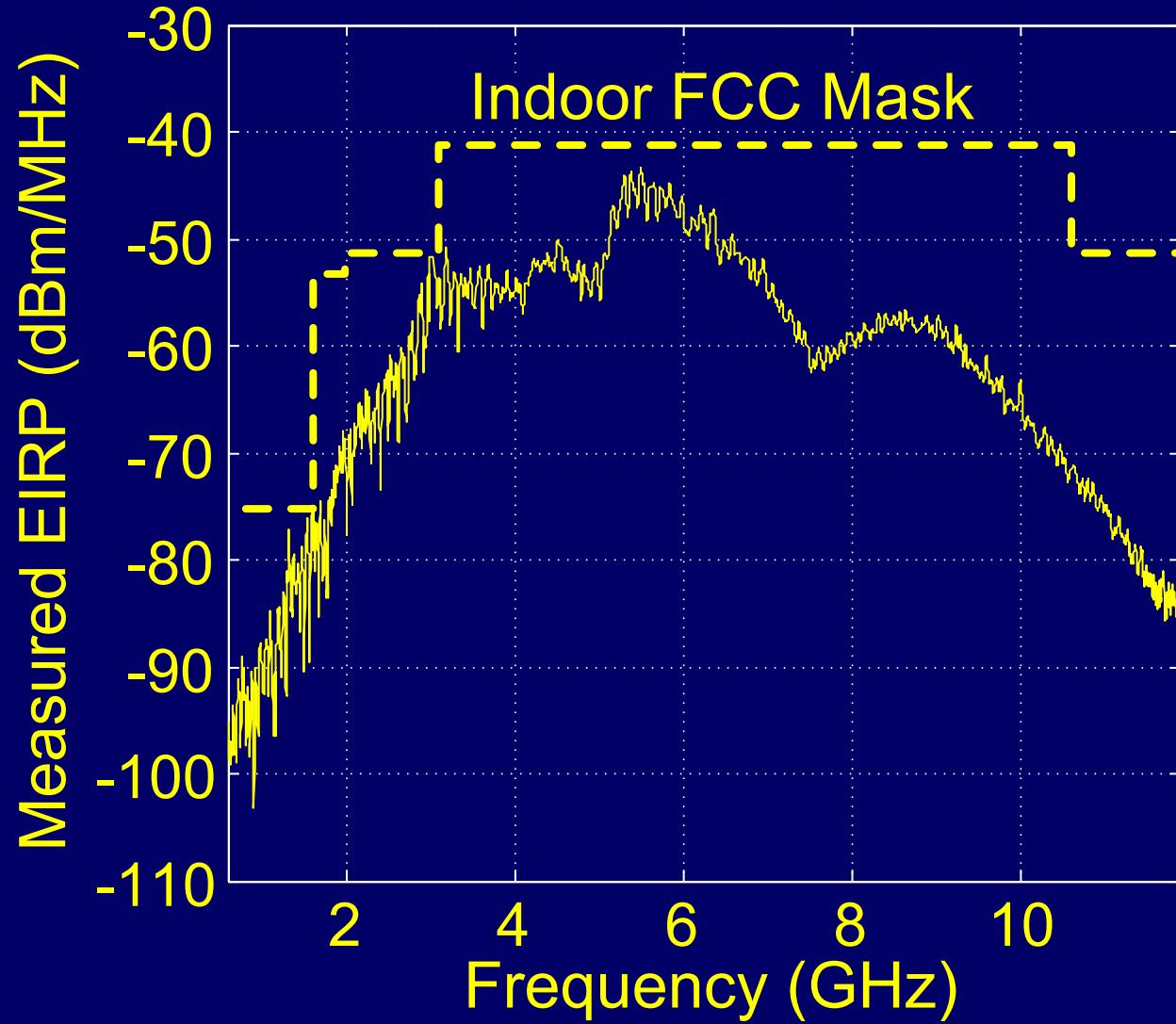

# Performance Summary at 25°C

Technology	90nm CMOS
Die Area	2.83mm <sup>2</sup>
Max. Pulse Rate	1.8Gpulses/s
Max. Pulse Amplitude	220mVpp
Modulation	BPSK+PPM
VCO Range	12.3-15.7GHz
Jitter (rms)	1.9ps
Jitter (peak-to-peak)	15.1ps
Supply Voltage	1.0V
<u>Power Dissipation</u>	
<i>Pulse Generator</i>	129mW
<i>PLL</i>	98mW
<i>Test-Mode Circuitry</i>	143mW
Total Transmitter Power	227mW
Energy/Pulse	126pJ/pulse

# Die Micrograph

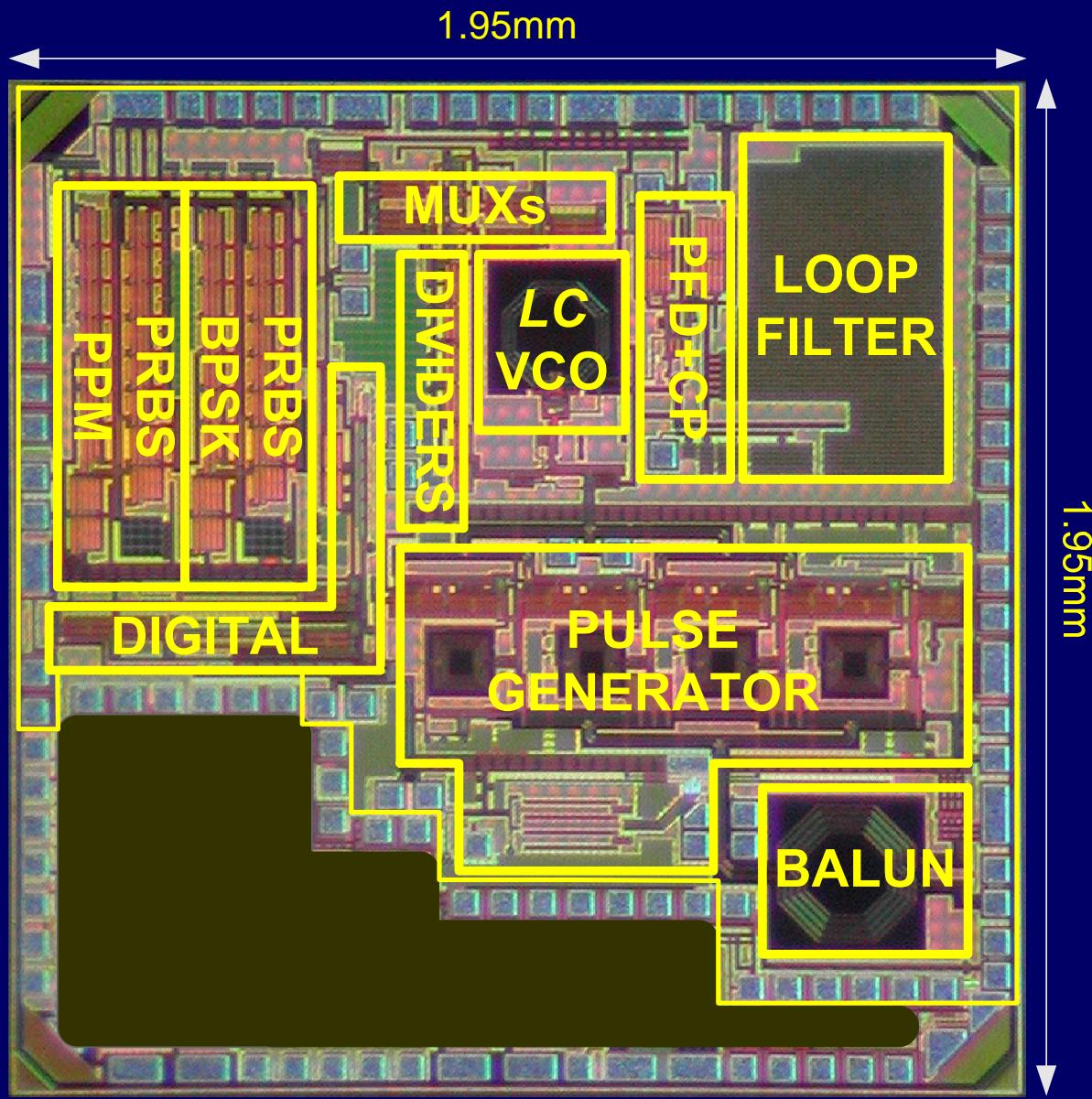

# Outline


- Motivation (Why UWB?)
- FCC Emission Limits
- Antenna Characterization
- UWB Transmitter Design
- Wide Tuning-Range VCO Design  
(with Stephen Bruss)
- Summary

# Motivation

- How can we improve the tuning range of a conventional *LC* VCO without increasing phase noise and area significantly?
- **Key observation:** Capacitor Q is low at high frequencies ( $Q_C=1/\omega RC$ ) but inductor Q is high!

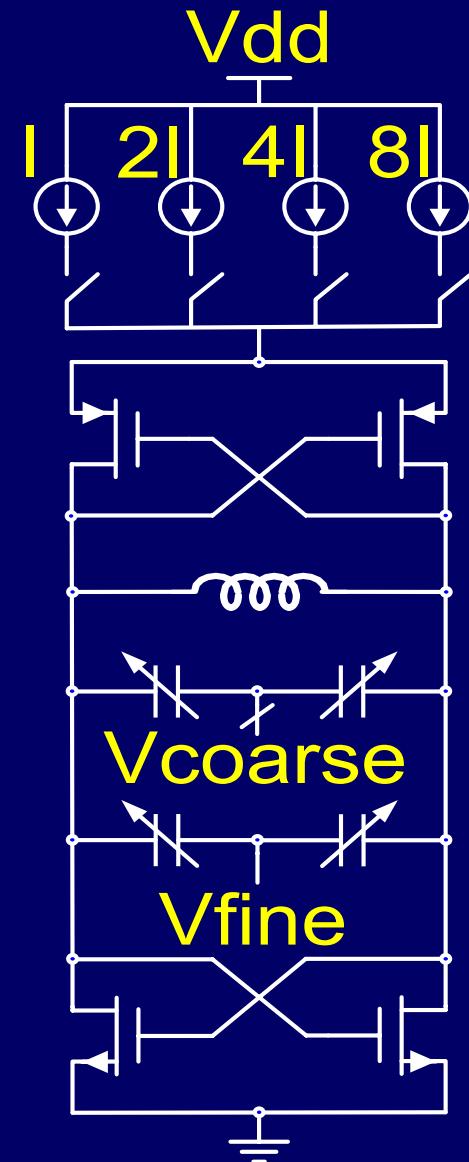
# VCO1: Single-inductor LC VCO

- Built as reference for comparison
- Inductor
  - Single-turn
  - Uses both M8 & M9
  - Has high self resonant freq.
  - Flat  $L$  and  $Q$  vs. Frequency
- AMOS varactors
  - Fine tuning ( $K_{VCO} = 150\text{MHz/V}$ )
  - Coarse tuning (Binary weighted)



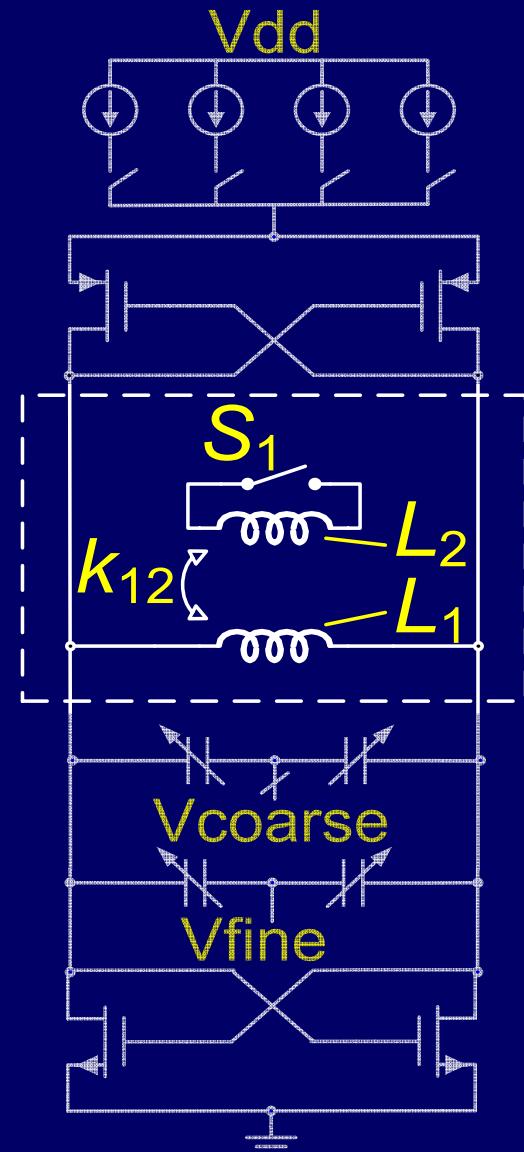
# VCO2: LC VCO with one extra coil

- Coil  $L_2$  mutually coupled to  $L_1$
- When  $S_1$  is OPEN
  - No Eddy Currents in  $L_2$
  - Inductance is  $L_1$
- When  $S_1$  is CLOSED
  - Eddy Current flow in  $L_2$
  - Inductance drops to  $L_1 - k_{12}^2 L_2$



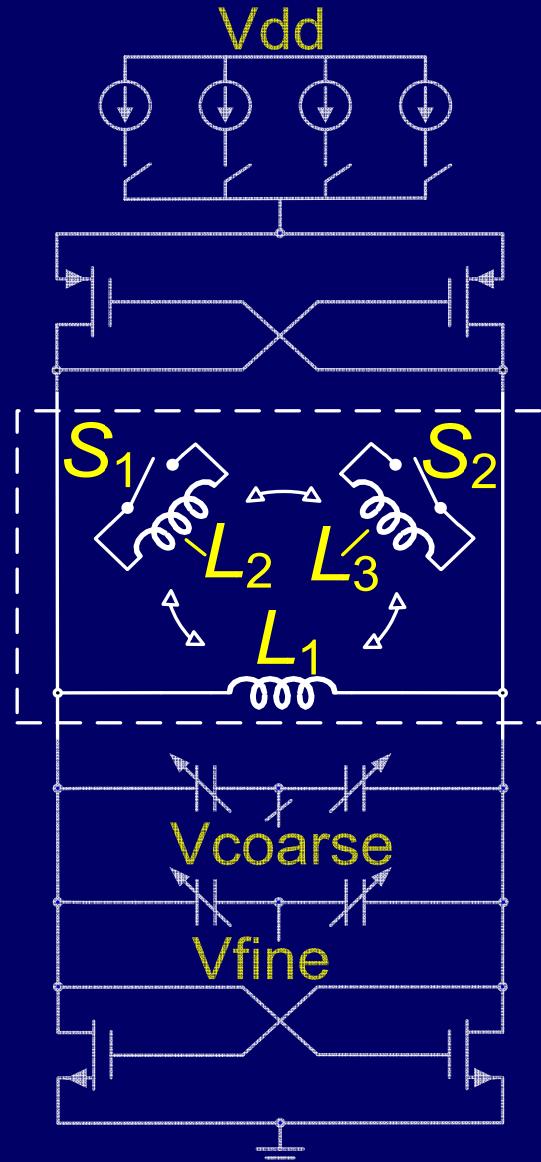
# VCO3: LC VCO with two extra coils

- Coils  $L_2$  and  $L_3$  are mutually coupled to  $L_1$
- Switches  $S_1$  and  $S_2$  control currents in  $L_2$  and  $L_3$
- Four frequency bands




# Resonator Layout

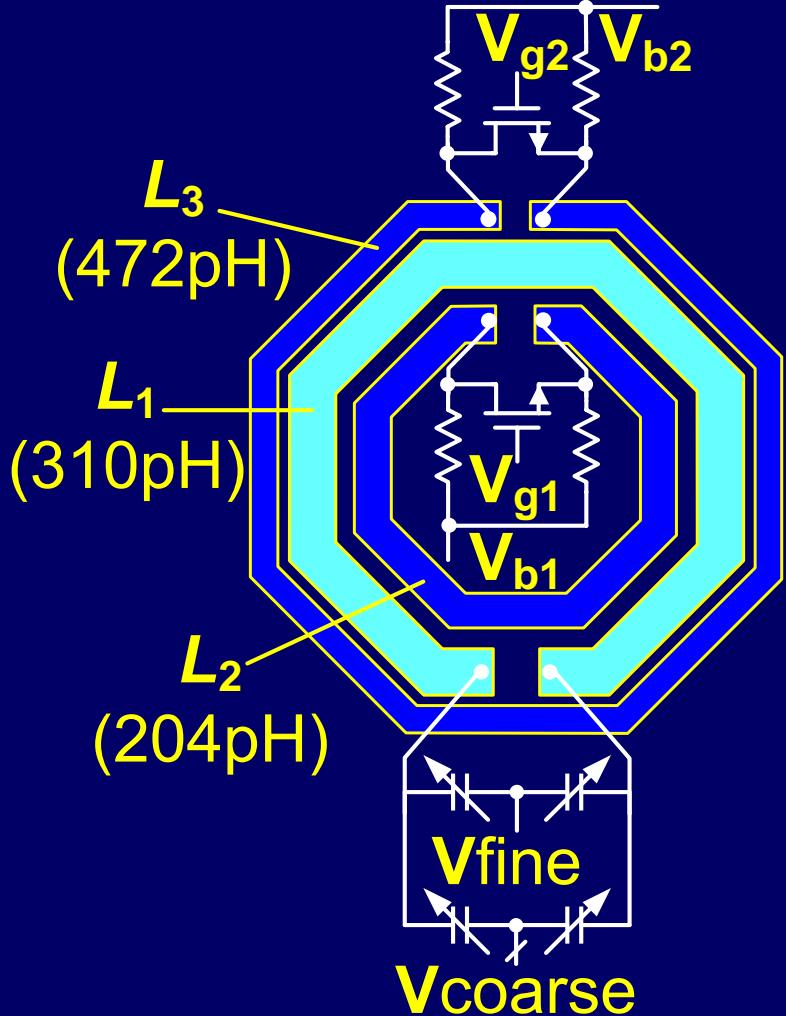


- Extra coils add small area
- $L_2$  &  $L_3$  biased independently
  - Set  $V_{b1}$  &  $V_{b2}$  to opposite polarity of  $V_{g1}$  &  $V_{g2}$
  - Improves  $(Q \times \text{TR})$  by 1.6
- Switch size critical ( $R_{on}$ ,  $C_{off}$ )

# Measured Phase Noise at 13GHz

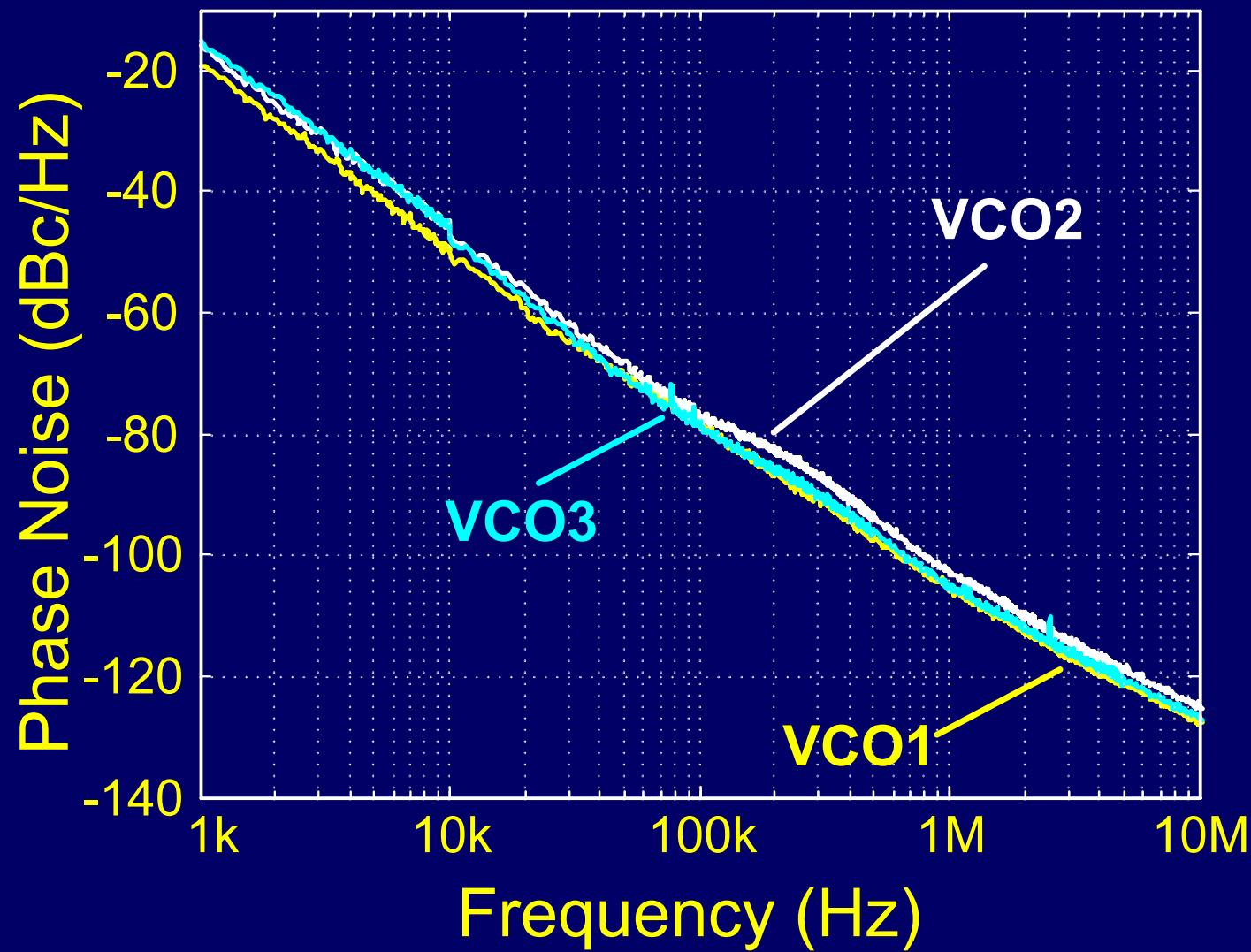


# Phase Noise at 1MHz offset

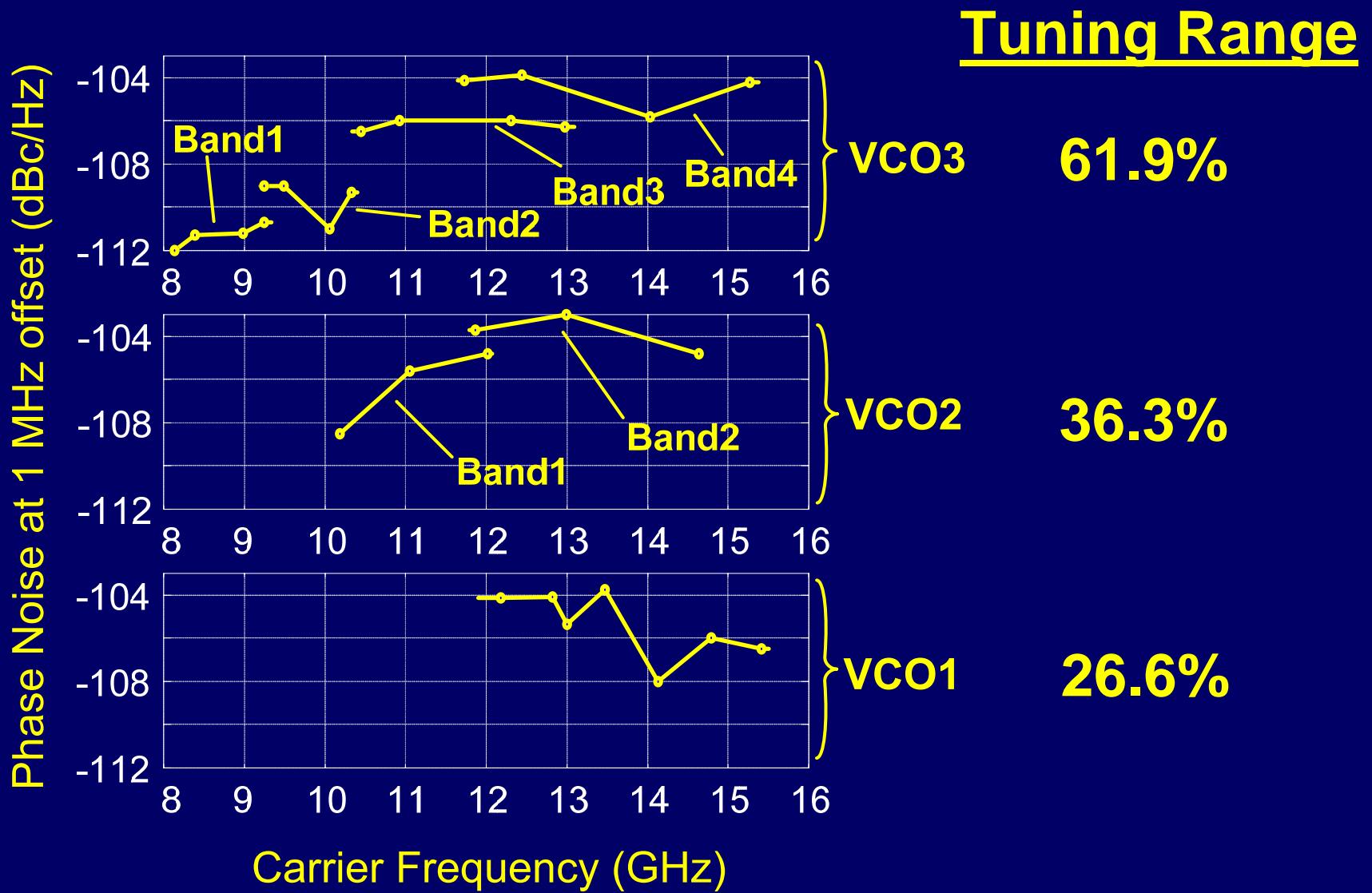


# Performance Summary at 25°C

	VCO1	VCO2	VCO3
<b>Process</b>	90nm CMOS	90nm CMOS	90nm CMOS
<b>Power Supply</b>	1.2V	1.2V	1.2V
<b>Center Frequency</b>	13.7GHz	12.4GHz	11.8GHz
<b>Tuning Range</b>	26.6%	36.3%	61.9%
<b>Power</b>	2.81mW	5.65mW	7.7mW

# Performance Comparison

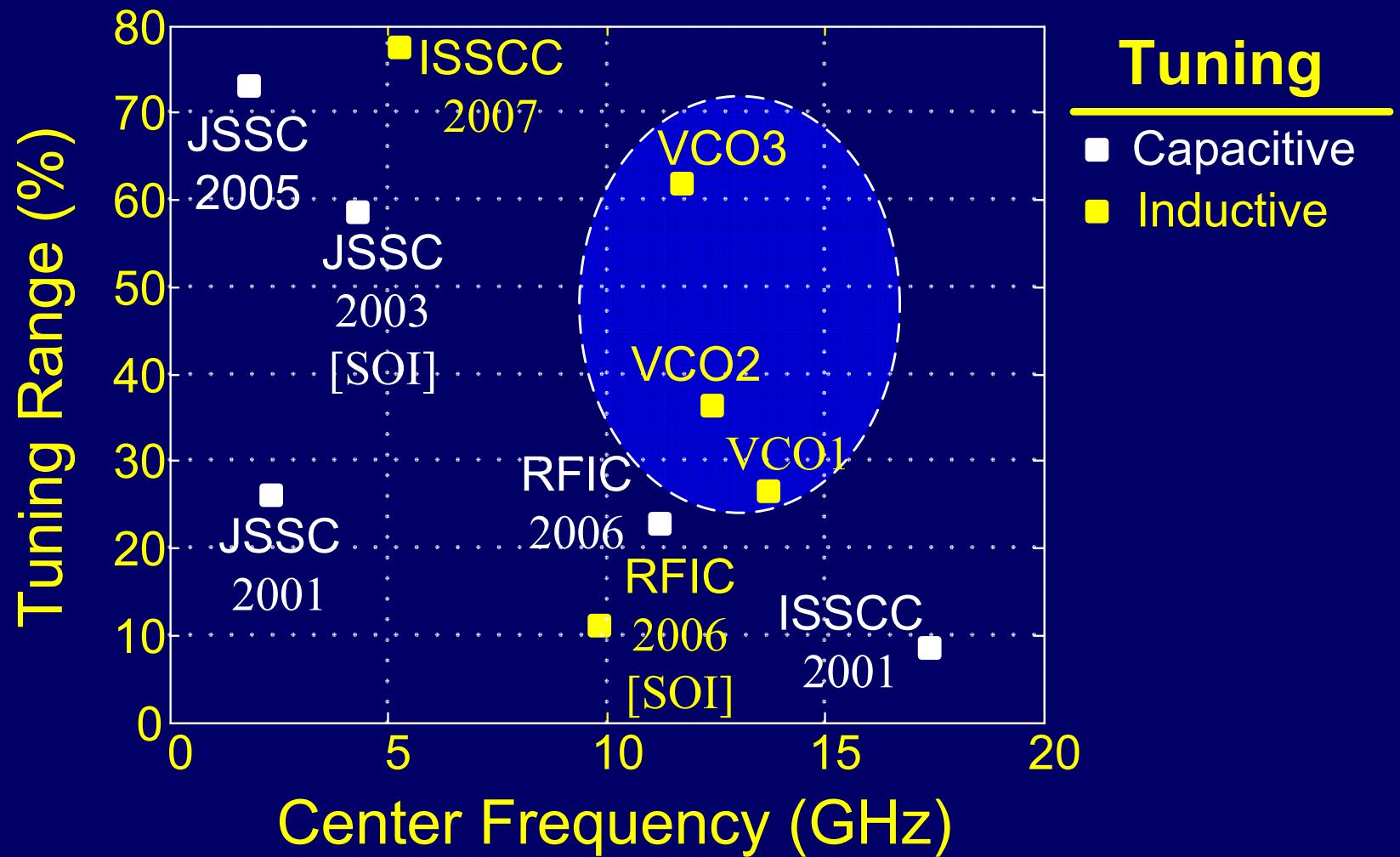


# Performance Comparison

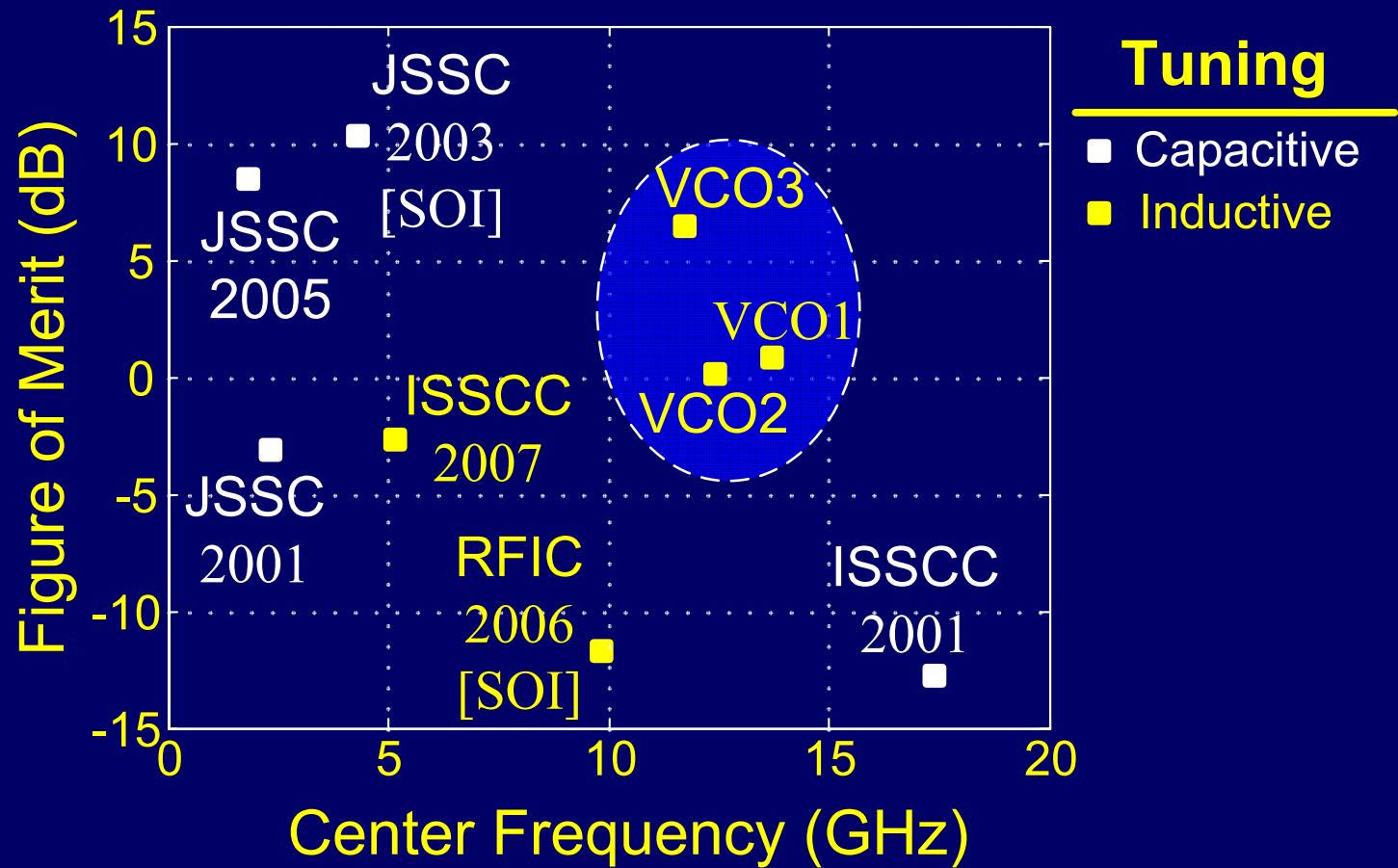

$$FOM = 10 \log \left[ \frac{kT}{P} \cdot \left( \frac{f_{\max} - f_{\min}}{f_{\text{off}}} \right)^2 \right] - PN(f_{\text{off}}) \quad [\text{Ham, Hajimiri, JSSC 01}]$$

# Die Micrograph

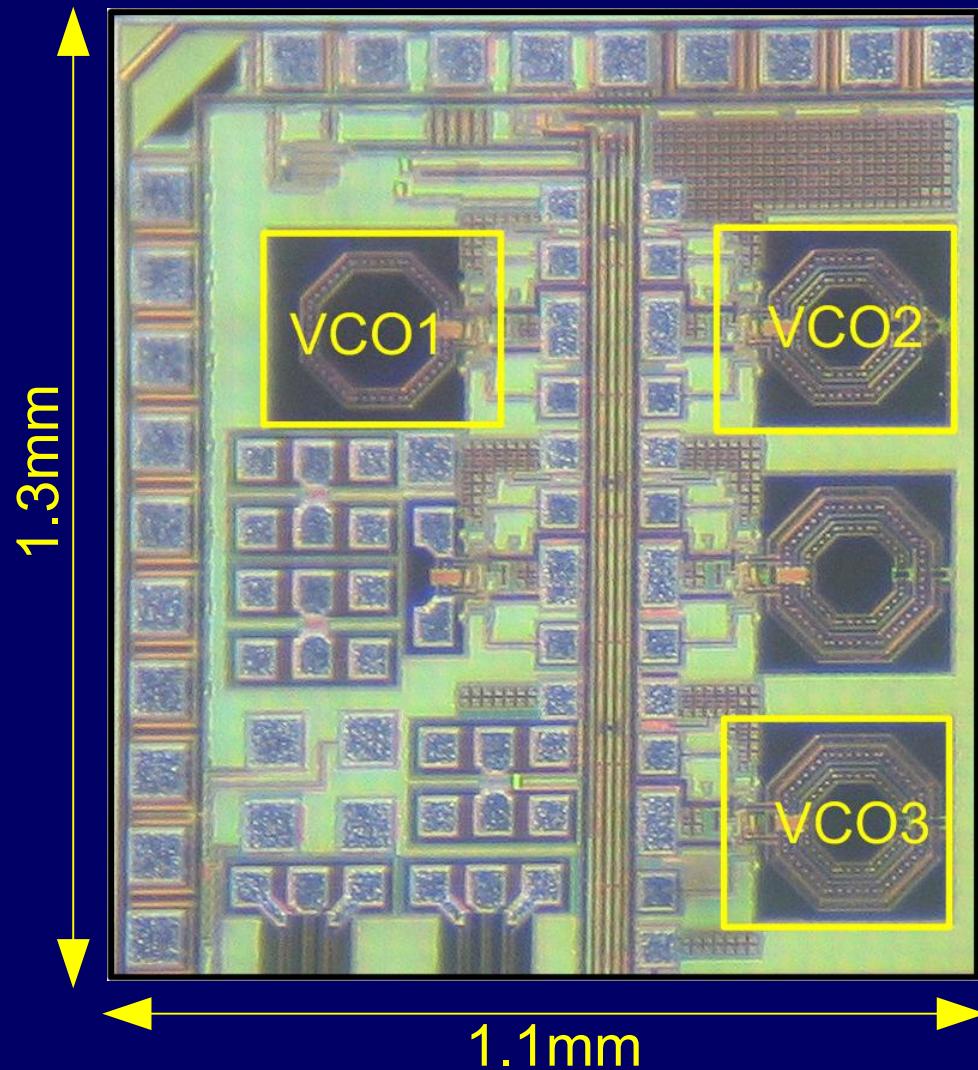

# Outline

- Motivation (Why UWB?)
- FCC Emission Limits
- Antenna Characterization
- UWB Transmitter Design
- Wide Tuning-Range VCO Design
- Summary

# Summary

- **Modeling of UWB Antennas in RF Circuit Simulators**
- **A new pulse-based UWB transmitter architecture**
- **A Method to improve tuning ranges of conventional  $LC$  VCOs using switched coupled-inductors**

# Acknowledgements

- **Advisor: Prof. Richard R. Spencer**
- **Professors P.J. Hurst, A. Knoesen, B. Kolner, S. H. Lewis, A. H. Pham and D. Yankelevich** for their generous help
- **Stephen P. Bruss (VCO Project)**
- **Dan Oprica and the IEEE SCV SSCS**
- **Fabrications were graciously provided by TSMC**
- **Research was supported by:**  
Agilent, Broadcom, Intel, Marvell, TDK, Texas Instruments and the UC MICRO Program

**-END-**