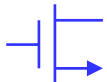


Analog Circuit Design with Submicron Transistors

Bernhard Boser
UC Berkeley


Department of Electrical Engineering and Computer Sciences

boser@eecs.berkeley.edu




Analog Circuit Design

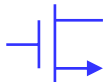- Objective:
Translate circuit specifications
(gain, bandwidth, dynamic range, ...) into transistor sizes and bias currents
- Challenge:
Accurate device models for deep submicron transistors
 - “Square-law model”
 - Simulation models (BSIM, EVK, ...)
 - “Model” for analog design




Device Model Objectives

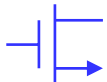- Device Physics
- Simulation / Verification
 - Accuracy, efficiency
- (Analog) Circuit Design
 - Relate device characteristics to circuit specifications
 - E.g.
 - Bandwidth
 - Gain
 - Power dissipation
 - Dynamic range (noise)
 - Accurate, simple




Device Parameters for Analog Design

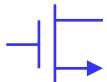- Large signal
 - Current $I_D \rightarrow$ power dissipation
 - Minimum $V_{DS} \rightarrow$ available signal swing
- Small signal
 - Transconductance $g_m \rightarrow$ speed / voltage gain
 - Capacitances $C_{GS}, C_{GD}, \dots \rightarrow$ speed
 - Output impedance $r_o \rightarrow$ voltage gain



Metrics for Design

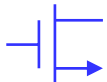- Transistor Objectives: High transconductance
 - Without large I_D
 - Without large C_{GS}
- Figures of Merit
 - Current efficiency $\frac{g_m}{I_D}$
 - Transit frequency $\frac{g_m}{C_{gs}}$




Current Efficiency

- “Square-law transistor”:


$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$
$$= \frac{2I_D}{V_d^{sat}} \quad \leftarrow \text{Overdrive voltage}$$

 
- High efficiency \rightarrow low overdrive voltage



Current Efficiency g_m/I_D

 

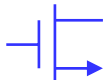- High efficiency is good for low power
- Higher g_m/I_D at low V_{GS}
- Approaches BJT for $V_{GS} < V_{TH}$
 $g_m/I_C = 1/V_t \sim 40 \text{ V}^{-1}$
- Weak dependence on transistor type and process




Transit Frequency ω_T

- Unity current-gain bandwidth

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$
$$\approx \frac{\mu V_d^{sat}}{L^2} \quad (\text{square-law model})$$




Efficiency g_m/I_D versus f_T

 


Speed-Efficiency
Tradeoff


NMOS faster than
PMOS

 

Device Scaling

 

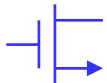Short channel devices are significantly faster!




Current Efficiency vs Transient frequency

- Tradeoff:


$$\frac{g_m}{I_D} \propto \frac{1}{V_d^{sat}}$$
$$\omega_T \propto V_d^{sat}$$

- What about:

 
$$\frac{g_m}{I_D} \times \omega_T \propto \frac{\mu}{L^2}$$



Device Figure-of-Merit

 


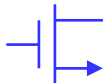Peak performance for low $V_{GS} - V_{TH}$




Device Scaling for Analog Circuits

 - “Moore’s Law”
 - L_{\min} decreases $\sim 2x$ every 5 years
 - $L_{\min} = 10\mu\text{m}$ in 1970, 90nm in 2004
- Benefits (for analog circuits):
 - Higher speed: increase g_m/C_{gs} while keeping g_m/I_D constant
 - Lower power: increase g_m/I_D while keeping bandwidth (g_m/C_{gs}) constant
- In both cases, reducing L is advantageous!



Short Channel Devices

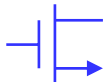- Short channel effects
 - Velocity saturation
 - Mobility degradation (thin oxide)
- Prior considerations assume “square law” models and ignore these effects
 - Significant discrepancies
- Let’s fix this ...



Efficiency g_m/I_D

- Important design parameter ... but a little unusual: units 1/V
- Let's define


$$V^* = \frac{2I_D}{g_m} \quad \Leftrightarrow \quad \frac{g_m}{I_D} = \frac{2}{V^*}$$

e.g. $V^* = 200\text{mV} \rightarrow g_m/I_D = 10 \text{ V}^{-1}$

- Square-law devices only: $V^* = V_{GS} - V_{TH} = V_{\text{dsat}}$


Square law :
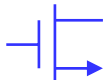
$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2I_D}{V^*}$$



Saturation Voltage versus V^*

 - Saturation voltage
 - Minimum V_{DS} for “high” output resistance
 - Poorly defined: transition is smooth in practical devices
- “Long channel” (square law) devices:
 - $V_{GS} - V_{TH} = V_{dsat} = V_{ov} = V^*$
 - Significance:
 - Channel pinch-off



$$I_D \sim V_{dsat}^2$$

Analog Circuit Design with Submicron Transistors

© 2004 B. Boser 16

- Boundary between triode and saturation

Design Example

Example: Common-source amp

$a_{v0} > 100$, $f_u = 100\text{MHz}$ for $C_L = 5\text{pF}$


DC Analysis DC1

Device Vgs

sweep from 800m to 900m (1001 steps)


AC Analysis AC1

log sweep from 1k to 10G (101 steps)

 


- $a_{v0} > 100 \rightarrow L = 0.5\mu\text{m}$
- $g_m \approx 2\pi f_u C_L = 3.14\text{mS}$
- High f_T (small C_{GS}): $V^* = 250\text{mV}$

 
$$I_D = \frac{g_m V^*}{2} = 393\mu\text{A}$$



Device Sizing




 


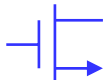- Pick L 0.5 μm
- Pick V^* 250mV
- Determine g_m 3.14mS
- $I_D = 0.5 g_m V^*$ 393 μA
- W from graph
(generate with SPICE)
 - $W = 10\mu m (393\mu A / 103\mu A)$
= 38 μm
- **Create such graphs for several device length' for design reference**





Common Source Example



Common-Source Open-Loop Voltage Gain

  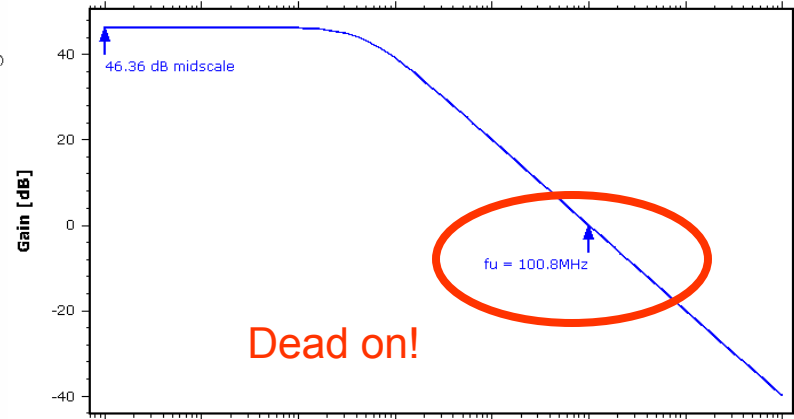 

Device Sizing Chart

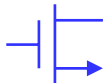 


Device Sizing Chart

 
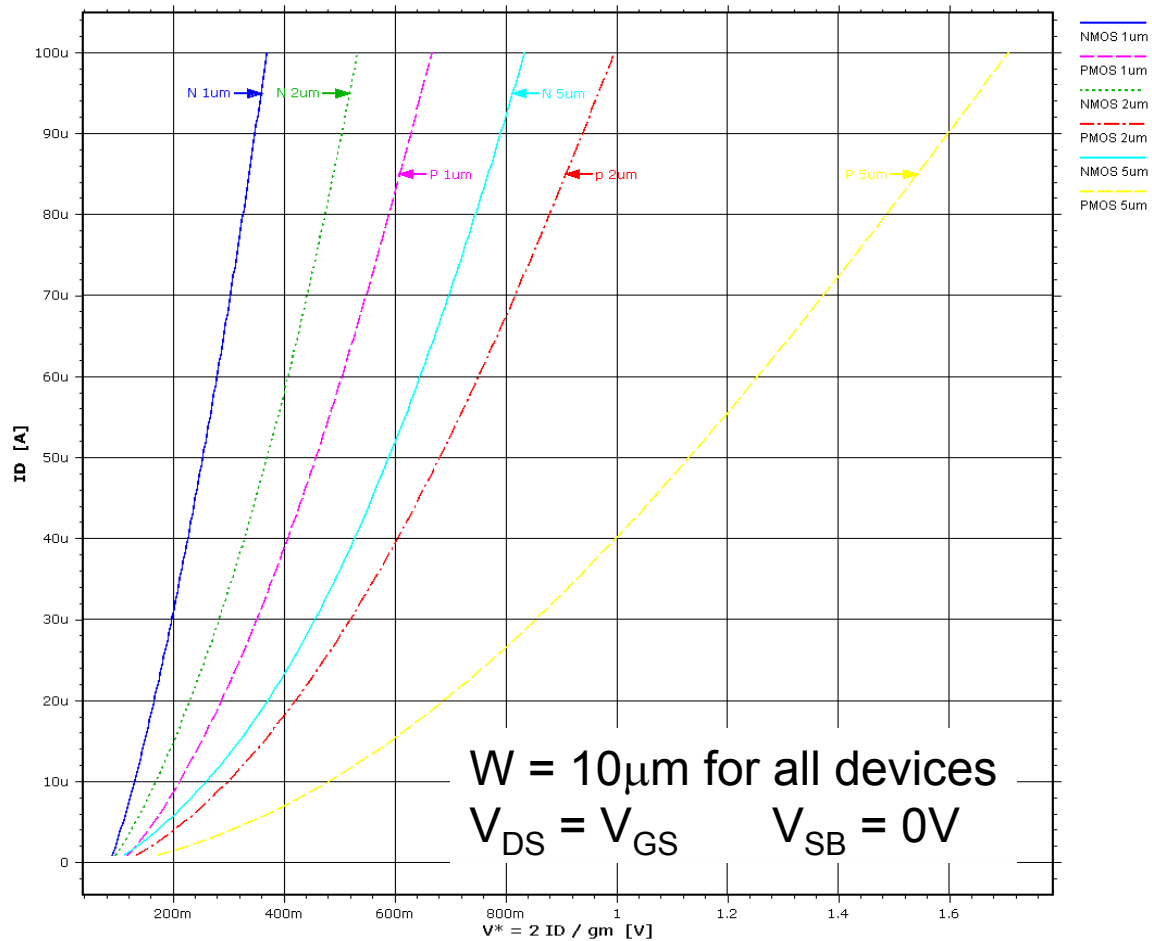


Device Parameters for Analog Design

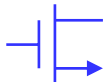
- Large signal
 - Current $I_D \rightarrow$ power dissipation
 - Minimum $V_{DS} \rightarrow$ available signal swing
- Small signal
 - Transconductance $g_m \rightarrow$ speed / voltage gain
 - Capacitances $C_{GS}, C_{GD}, \dots \rightarrow$ speed
 - Output impedance $r_o \rightarrow$ voltage gain





Output Resistance r_o

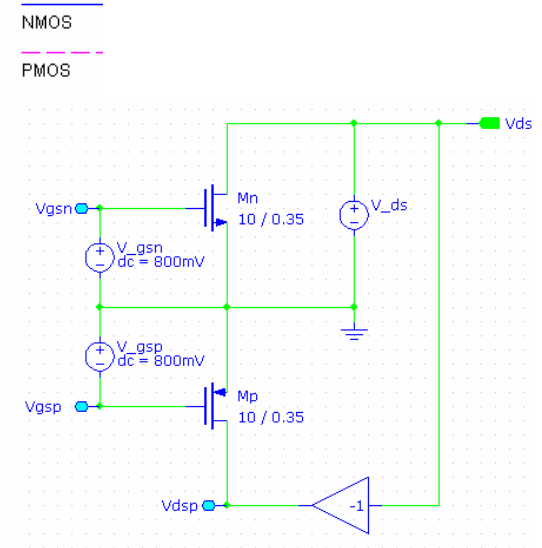 

 Hopeless to model this with a simple equation (e.g. $g_{ds} = \lambda I_D$)



Process Variations for r_o

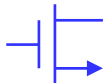 

Open-loop Gain a_{v0}


Intrinsic gain $a_{v0} = g_m * r_o$

Adjust I_d to set g_m/I_d ratio


DC Analysis

Device V1


sweep from 300m to 3 (100 steps)

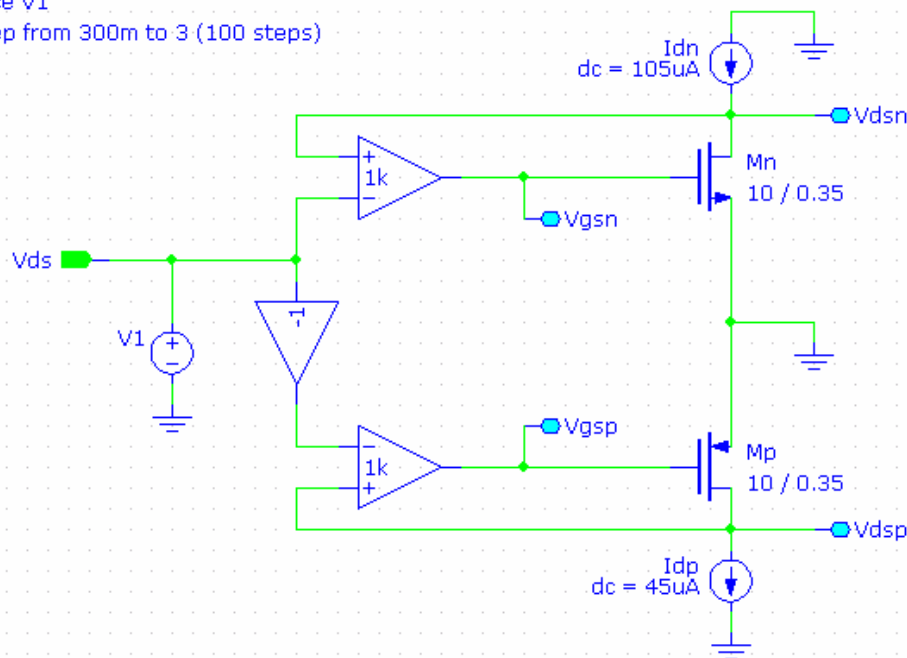


More useful than r_o

 

 
Gain, $a_{v0} = g_m r_o$ ($g_m/I_D = 10/V$)



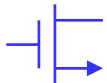- Strong tradeoff: a_{v0} versus V_{DS} range
- **Create such plots for several device length' for design reference**




 Gain, $a_{v0} = g_m r_o$ ($g_m/I_D = 10/V$)




$L \uparrow \rightarrow a_{v0} \uparrow$


like long channel device

 


Technology Trend

 

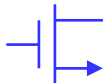
Short channel devices suffer from reduced per transistor gain





Transistor Gain Detail

 

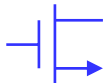
For practical V_{DS} the effect the “short-channel” gain penalty is less severe (remember: worst case V_{DS} is what matters!)




Current Sources (Biasing)

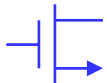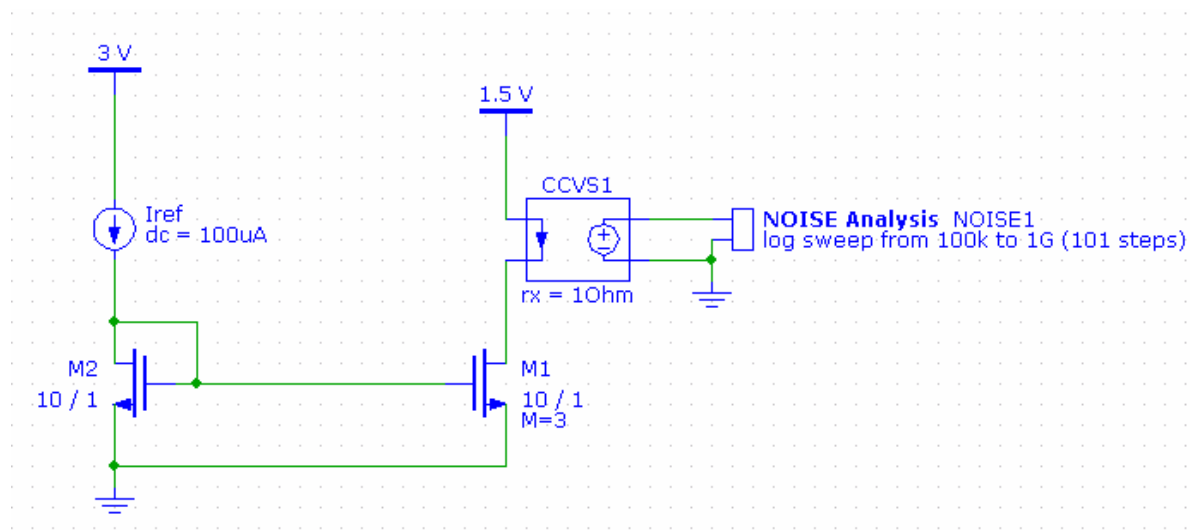



Cascoding

 


How choose V_{bias2} ?

 

Output Resistance

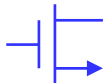 


$$R_{out} = f(k)$$

 


$$V_{DS1} = kV_1^*$$

How choose k? Issues:

 
- Swing versus R_o
- Large k useful only for large V_{min} simultaneously
- Note: small or no penalty for large k and small V_{min}
- \rightarrow typically choose $k > 1$



High-Swing Bias Example

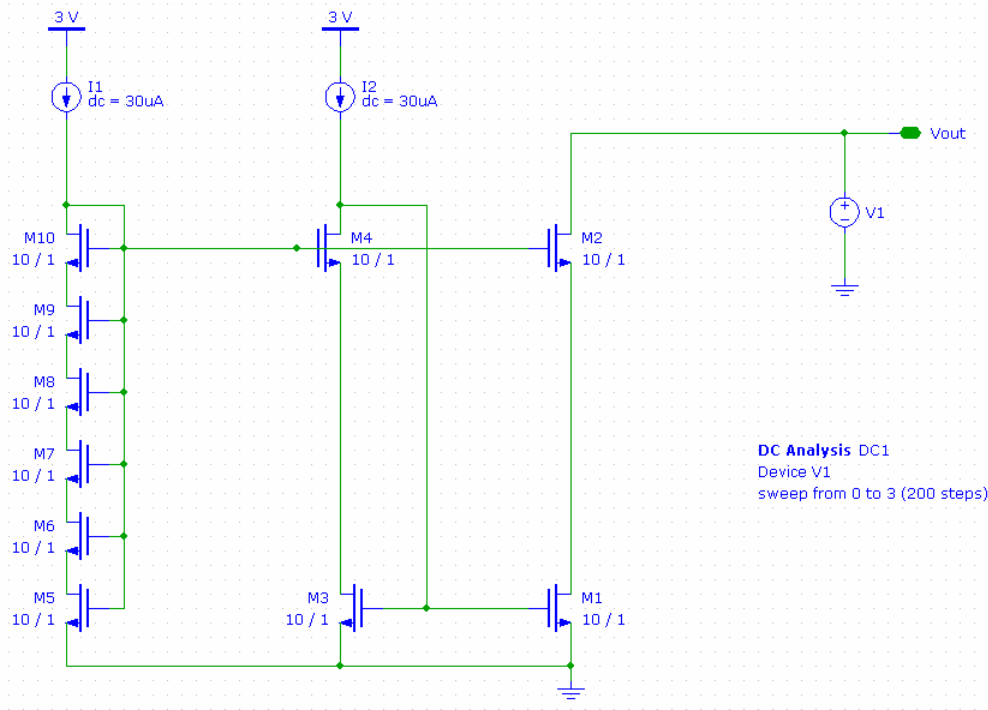

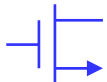
- M5 ... M10 replace quarter size device
- All devices same size
- Less sensitive to body-effect
- $L_{\text{current-source}} = L_{\text{cascode}}$




Noise

$$\begin{aligned}\overline{i_{on}^2} &= \overline{i_{d1}^2} + M^2 \overline{i_{d2}^2} \\ &= 4k_B T \gamma (g_{m1} + M^2 g_{m2}) \Delta f \\ &= 4k_B T \gamma g_{m1} (1 + M) \Delta f \\ &= 4k_B T \frac{1}{R_N} \Delta f\end{aligned}$$
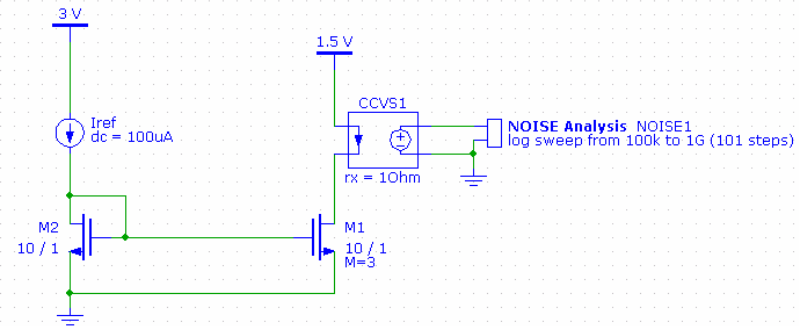
$$\begin{aligned}R_N &= \frac{1}{g_{m1}} \frac{\gamma^{-1}}{1 + M} \\ &= \frac{r_o}{a_{v0}} \frac{\gamma^{-1}}{1 + M} \ll R_o = r_o\end{aligned}$$



 - M2 (and I_{ref} !) can add noise
 - Choose small M (power penalty), or
 - Filter at gate of M1
- Current source FOMs
 - Output resistance R_o
 - Noise resistance R_N
 - **Active sources boost R_o , not R_N**




V_{\min} versus Noise

$$V_{\min} = k \times V^* \quad \text{typ. } k = 1 \dots 2$$

$$R_N = \frac{1}{g_{m1}} \frac{\gamma^{-1}}{1+M}$$
$$= \frac{V_{\min}}{2KI_D} \frac{\gamma^{-1}}{1+M}$$

 - Voltage required for large R_o (saturation): $V_{\min} \sim V^*$ (based on intuition from square-law model)
- Minimizing noise (for given I_D):
→ large R_N
→ **large V_{\min} ($k \gg 1$)**
- At odds with signal swing (to maximize the dynamic range)




Bipolar's, GaAs, ...

$$\overline{i_{on}^2} = \underbrace{\overline{i_{cn}^2} \left| \frac{1}{1 + g_m R_E} \right|^2}_{\text{BJT}} + \underbrace{\overline{i_{Rn}^2} \left| \frac{g_m R_E}{1 + g_m R_E} \right|^2}_{R_E} \Delta f \quad (\overline{i_b^2} = 0)$$


a) $g_m R_E = 0$ $\overline{i_{on}^2} = 2k_B T g_m \Delta f$
 $R_N = \frac{2}{g_m} = \frac{2V_t}{I_C}$ set by I_C

 b) $g_m R_E \gg 1$ $\overline{i_{on}^2} = 4k_B T \frac{1}{R_E} \Delta f$
 $R_N = R_E = \frac{V_{\min}}{I_C} \frac{V_{\min} - V_{ce}^{sat}}{V_{\min}}$

compare $R_{N,MOS} = \frac{V_{\min}}{I_D} \frac{\gamma^{-1}}{2K}$




 - BJT and R_E contribute noise
- Increasing R_E lowers overall noise
- BJT and MOS exhibit essentially same noise / V_{\min} tradeoff
- Lowest possible noise source is a resistor (and large V_{\min} , V_{DD})



Small Signal Design Summary

- Determine g_m (from design objectives)
- Pick L
 - Short channel \rightarrow high f_T
 - Long channel \rightarrow high r_o , a_{v0}
- Pick $V^* = 2I_D/g_m$
 - Small $V^* \rightarrow$ large signal swing
 - High $V^* \rightarrow$ high f_T
 - Dynamic range: $P_{sig} \sim 1/V^*$, $P_{noise} \sim V^*$
- Determine I_D (from g_m and V^*)
- Determine W (SPICE / plot)
- **Accurate for short channel devices \rightarrow key for design**

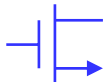

Device Parameter Summary

Device Parameter	Circuit Implications
V^*	<ul style="list-style-type: none"> • Current efficiency, g_m/I_D • Power dissipation (I_D) • Speed (g_m) • Cutoff frequency, $f_T \rightarrow$ phase margin • Headroom, $V_{DS,min}$
L	<ul style="list-style-type: none"> • Cutoff frequency, $f_T \rightarrow$ phase margin • Intrinsic transistor gain (a_{v0})
W	<ul style="list-style-type: none"> • Obtain from L, I_D • Self loading (C_{GS}, C_{DB}, \dots)

