
Digitally Assisted A/D Conversion- Trading off Analog Precision for Computing Power

SCV SSC Chapter Meeting

May 15, 2003

Boris Murmann, PhD Candidate
University of California, Berkeley
bmurmann@eecs.berkeley.edu

Outline


- ❑ Motivation
- ❑ Digitally Assisted Pipelined ADC
 - Circuit Concepts
 - Experimental Results
- ❑ Other Work & Future Opportunities
- ❑ Conclusion

“The Digital Revolution”


	1974	2002	Rate of Change
Transistor Feature Size	6 μ m	0.13 μ m	0.7x every 2-3 years
Lead μ P Transistors/die	5000	\approx 200,000,000	2x every 1.8 years
Lead μ P Performance	0.3 MIPS	\approx 10,000 MIPS	2x every 1.9 years

[Moore, ISSCC 2003]

ADC vs. μ P Performance

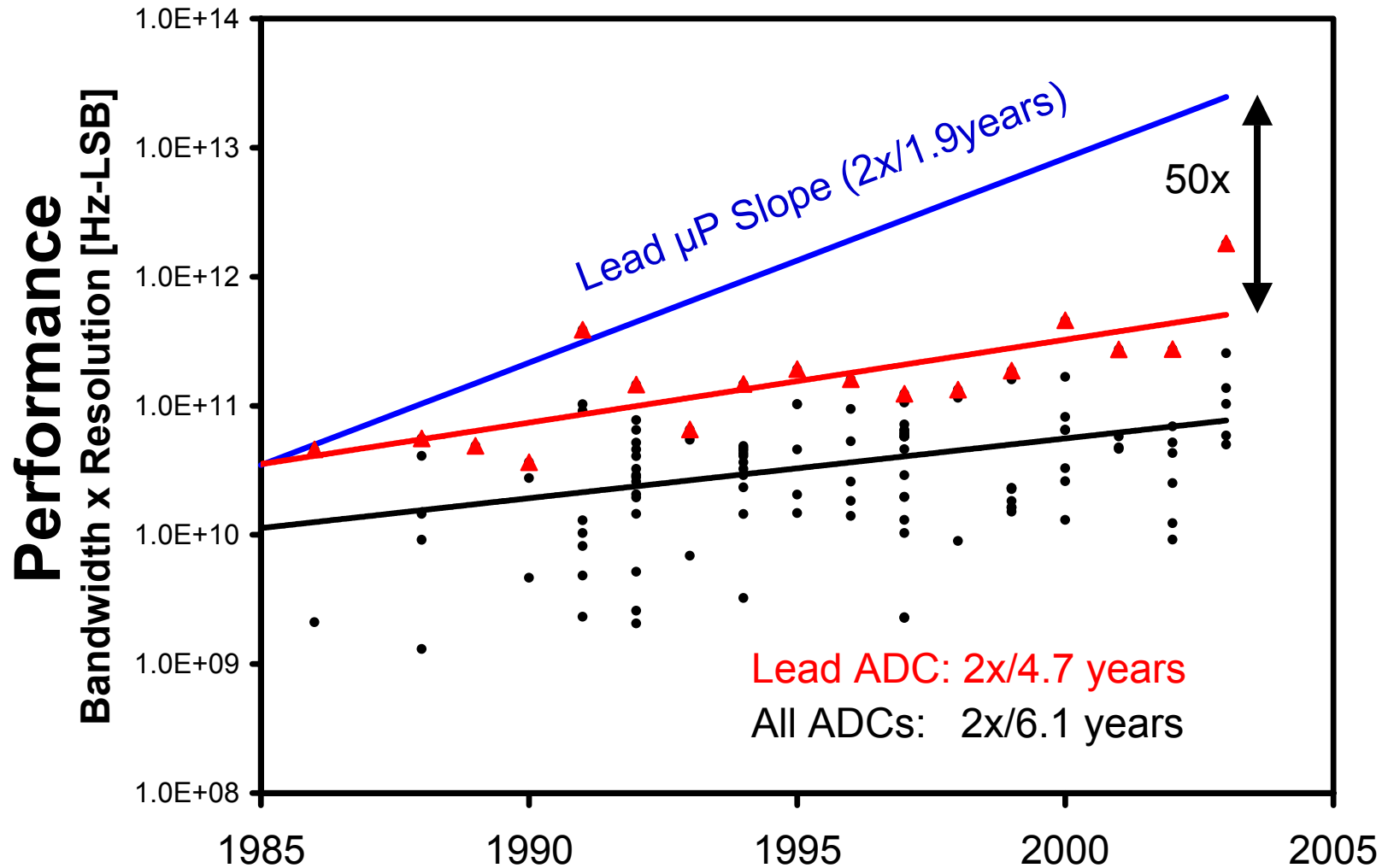


Modern Application

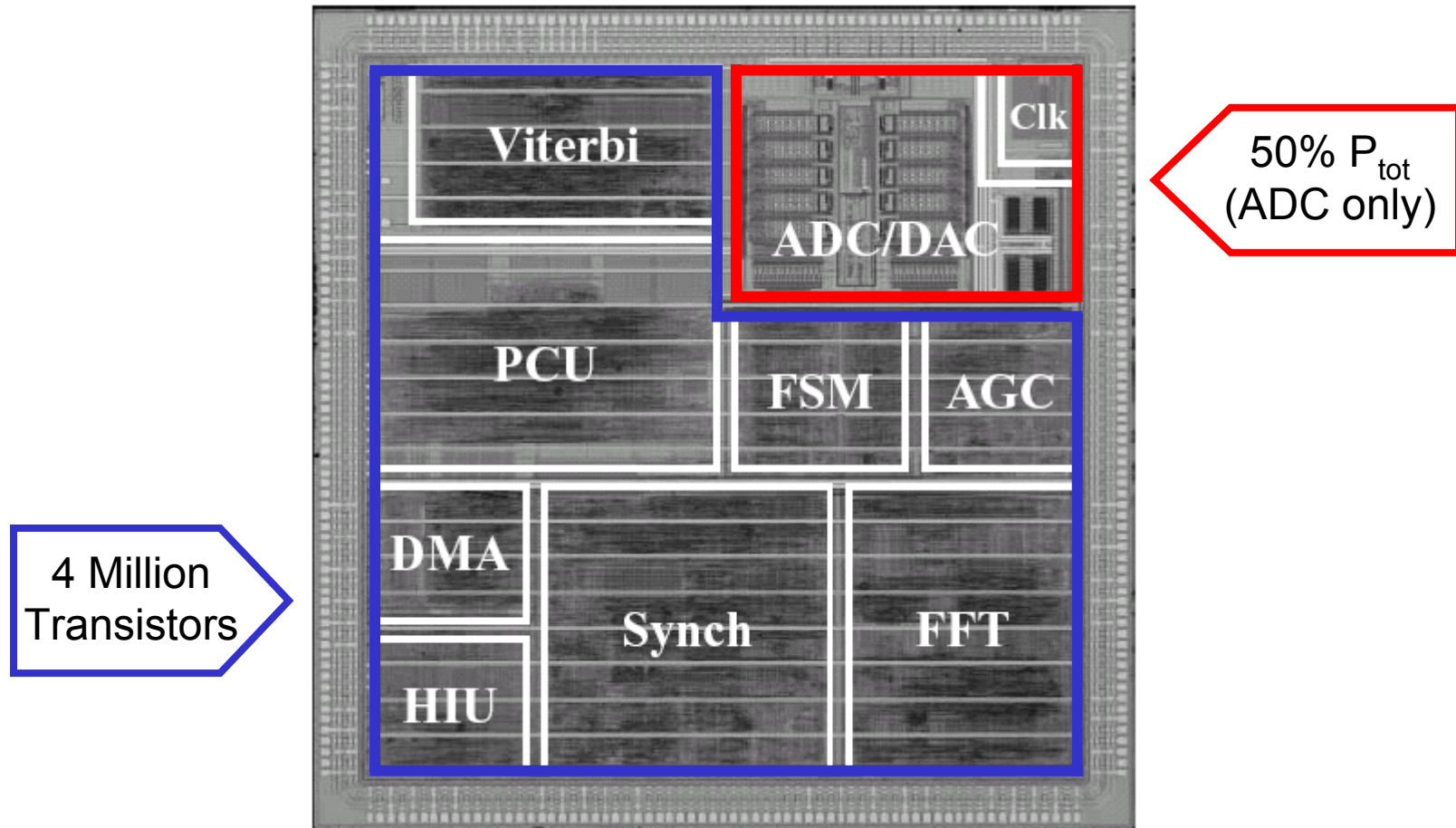

802.11 Baseband Processor
[Thomson et. al., ISSCC 2002]

Proposed Approach

 


- Relax analog domain precision & complexity
 - ⇒ Reduced power consumption
 - ⇒ Improved deep sub- μm compatibility
 - ⇒ Higher speed (?)
- Recover conversion accuracy in digital domain
- “Digitally Assisted A/D Conversion”

Outline


- Motivation
- Digitally Assisted Pipelined ADC
 - Circuit Concepts
 - Analog Errors & Digital Compensation
 - Correction Parameter Estimation & Tracking
 - Experimental Results
- Other Work & Future Opportunities
- Conclusion

Generic Pipelined ADC

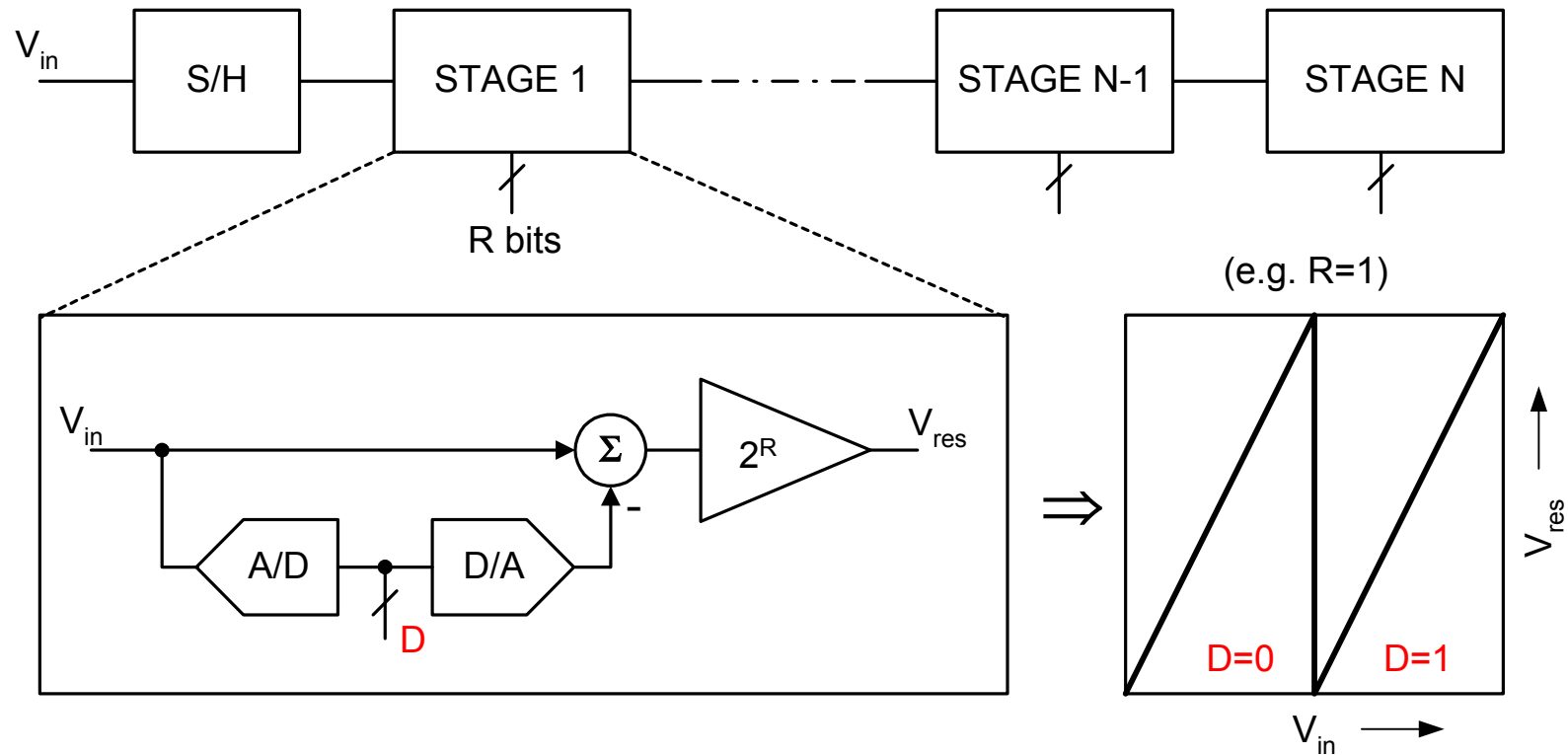

- Predominant topology for wide performance range:
10-14 bits, 10-200MHz


Relax Analog Precision?

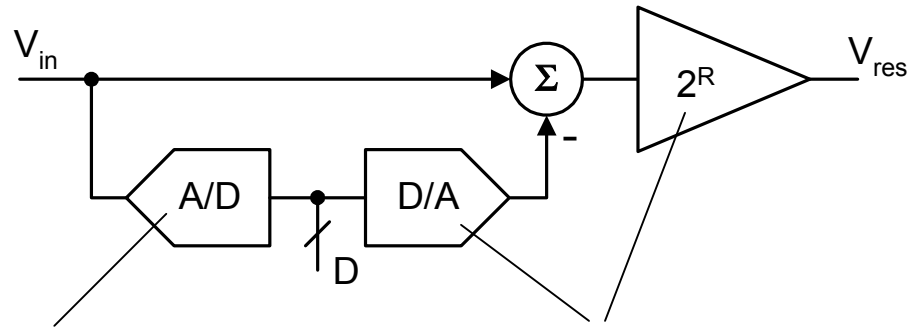

“Digital correction“ helps
tolerate large sub A/D errors
[Lewis, 1987]

“Digital calibration“ removes
D/A and linear gain error by
adjusting digital weights
[Karanicolas, 1993]

Relax Analog Precision?

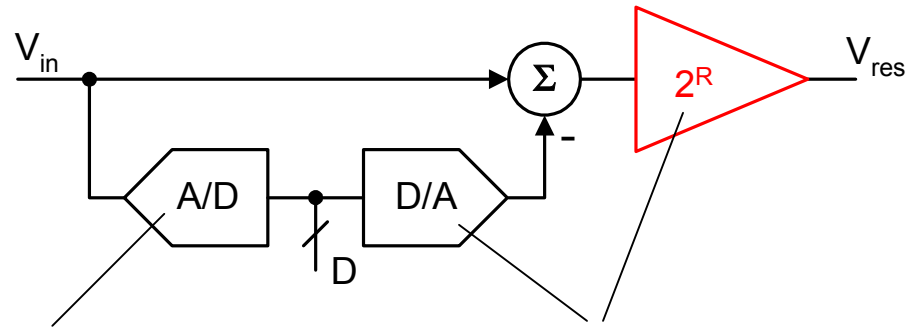


“Digital correction“ helps tolerate large sub A/D errors
[Lewis, 1987]

“Digital calibration“ removes D/A and linear gain error by adjusting digital weights
[Karanicolas, 1993]

- ❑ Remaining burden: Fast, highly linear gain element
- ❑ 50-70% of total pipeline ADC power is consumed by interstage amplifiers

Conventional Gain Element


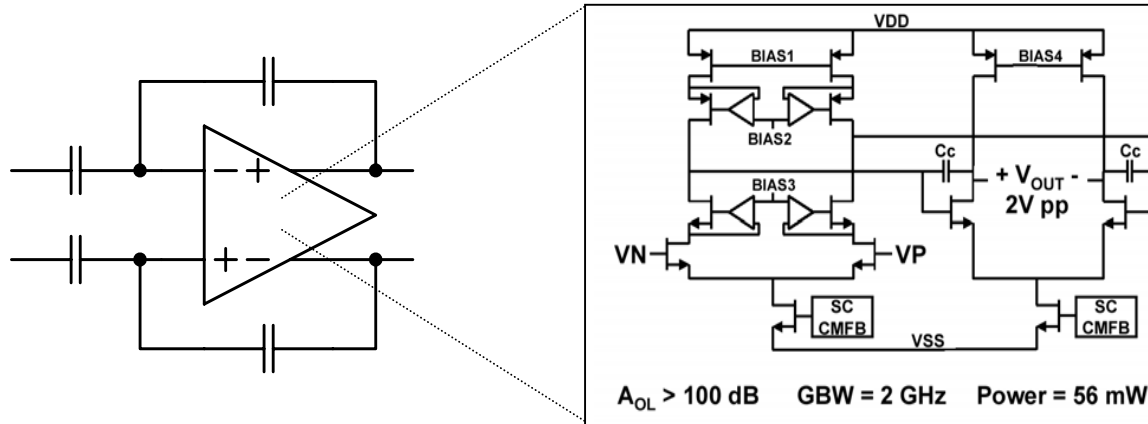


E.g. [Kelly, ISSCC 2001]



- ❑ Electronic feedback linearizes, desensitizes
- ❑ High gain requirement costs headroom and/or additional stages \Rightarrow power penalty
- ❑ Semiconductor technology trend: Decreasing VDD and low intrinsic device gain!

Alternatives

Precision Amplifier

 
 


“Low loop gain”

  


Power ↓
Precision ↓
Sensitivity ↑

“Open loop”

  



Power ↓↓
Precision ↓↓
Sensitivity ↑↑

Precision Requirements

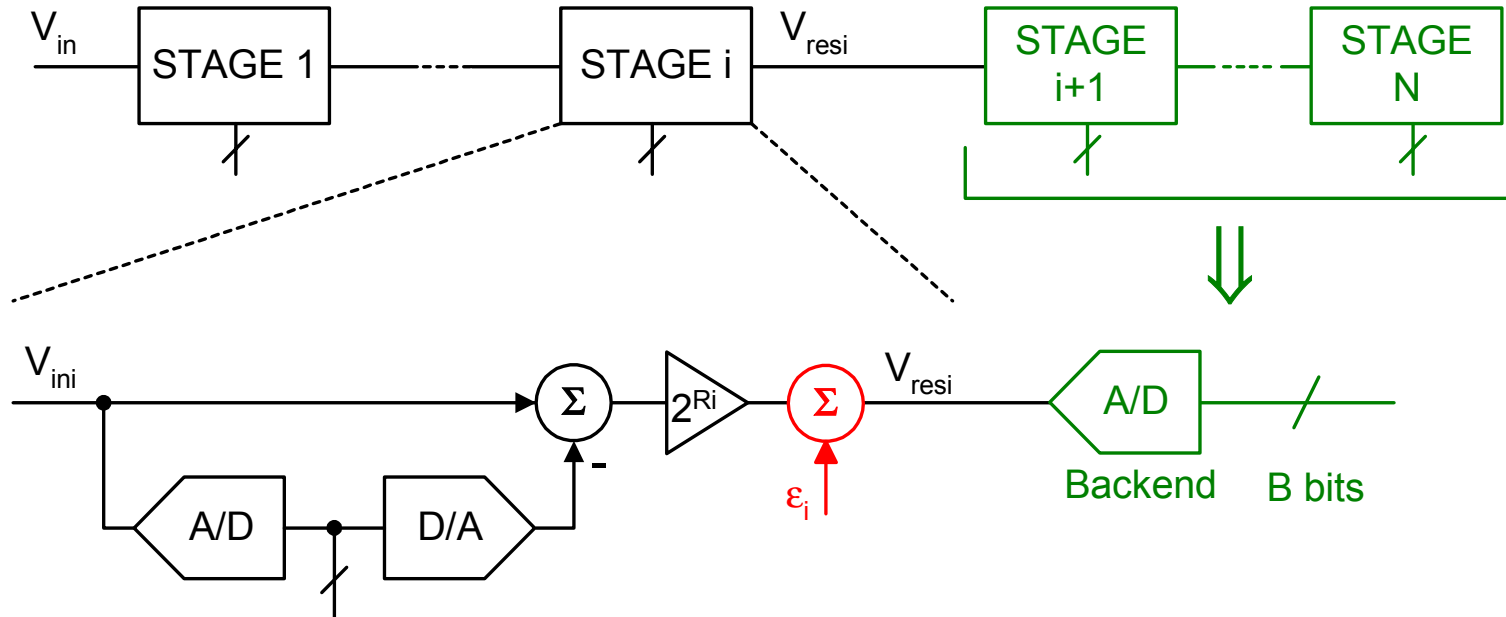

- Residue errors must be $< \frac{1}{2}$ LSB of “backend converter”
- E.g. 3-bit Stage1 in 12-bit converter \Rightarrow 9-bit backend
 $\Rightarrow \epsilon_1 < 0.1\%$

Basic Amplifier Considerations

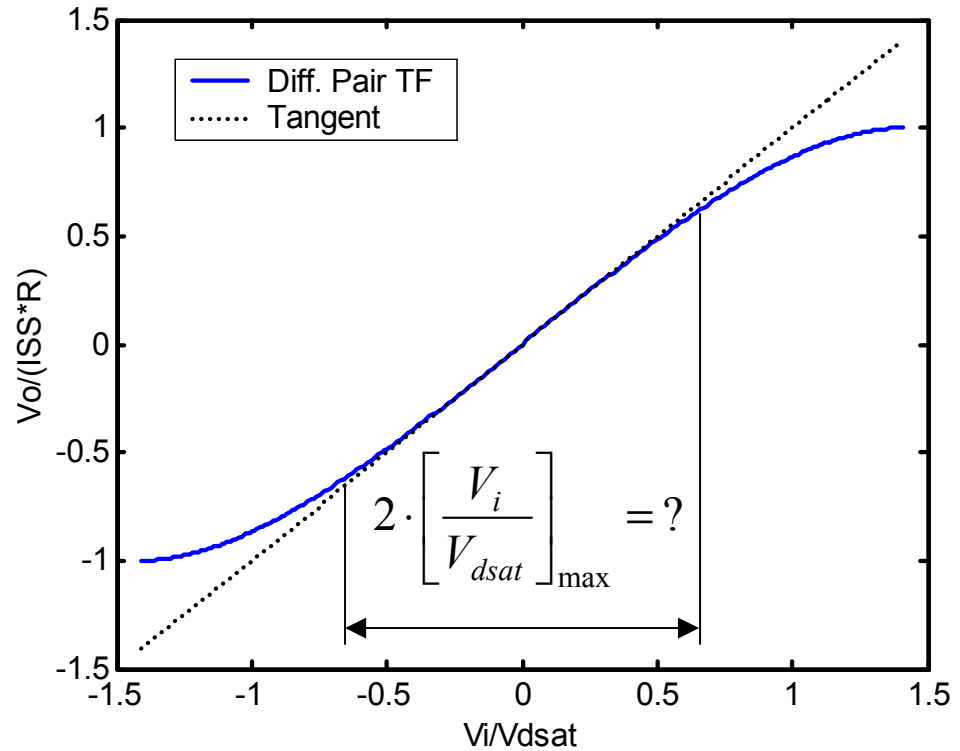 

- ❑ Example: Simplest possible topology
- ❑ What fraction of transfer function should be used?


Transfer Function Nonlinearity

$$\frac{V_0}{I_{SS}R} = \left(\frac{V_i}{V_{dsat}}\right) + \frac{1}{4} \frac{\Delta\beta}{\beta} \left(\frac{V_i}{V_{dsat}}\right)^2 - \frac{1}{8} \left(\frac{V_i}{V_{dsat}}\right)^3 - \frac{1}{128} \left(\frac{V_i}{V_{dsat}}\right)^5 - \dots$$

2nd order
(Device Mismatch)


3rd order
(Gain Compression)

5th order

 

- ❑ 3rd order error unavoidable
- ❑ 5th and higher order error small for $|V_{imax}| \leq 0.5V_{dsat}$
- ❑ Desirable to neglect high order terms
- ❑ Design implications?

Design Example

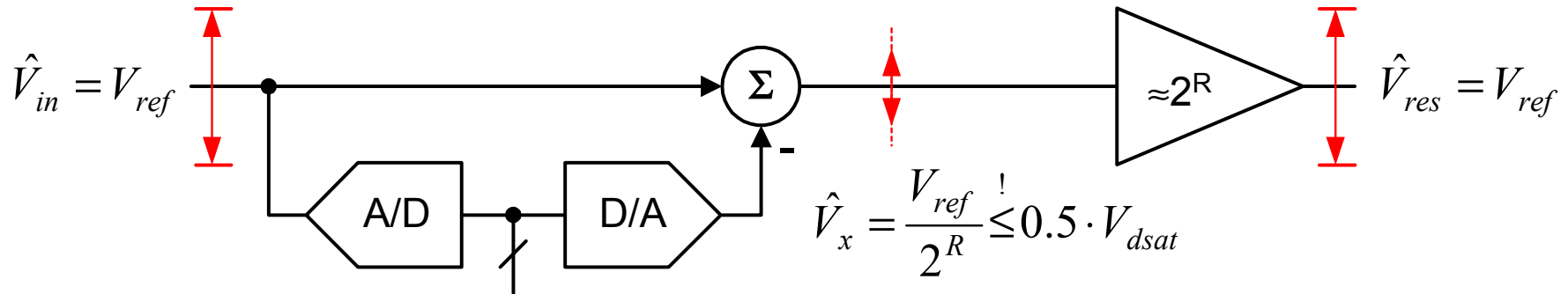


V_{ref}	R	\hat{V}_x	V_{dsat}
1V	1	500 mV	$\geq 1V$
	2	250 mV	$\geq 500 \text{ mV}$
	3	125 mV	$\geq 250 \text{ mV}$
	4	62.5 mV	$\geq 125 \text{ mV}$

X (headroom, g_m/I_D)
✓


- Simple diff. pair “practical” for stage resolution $R > 2$
- Third order error model sufficient in this case

Pipeline Stage Model

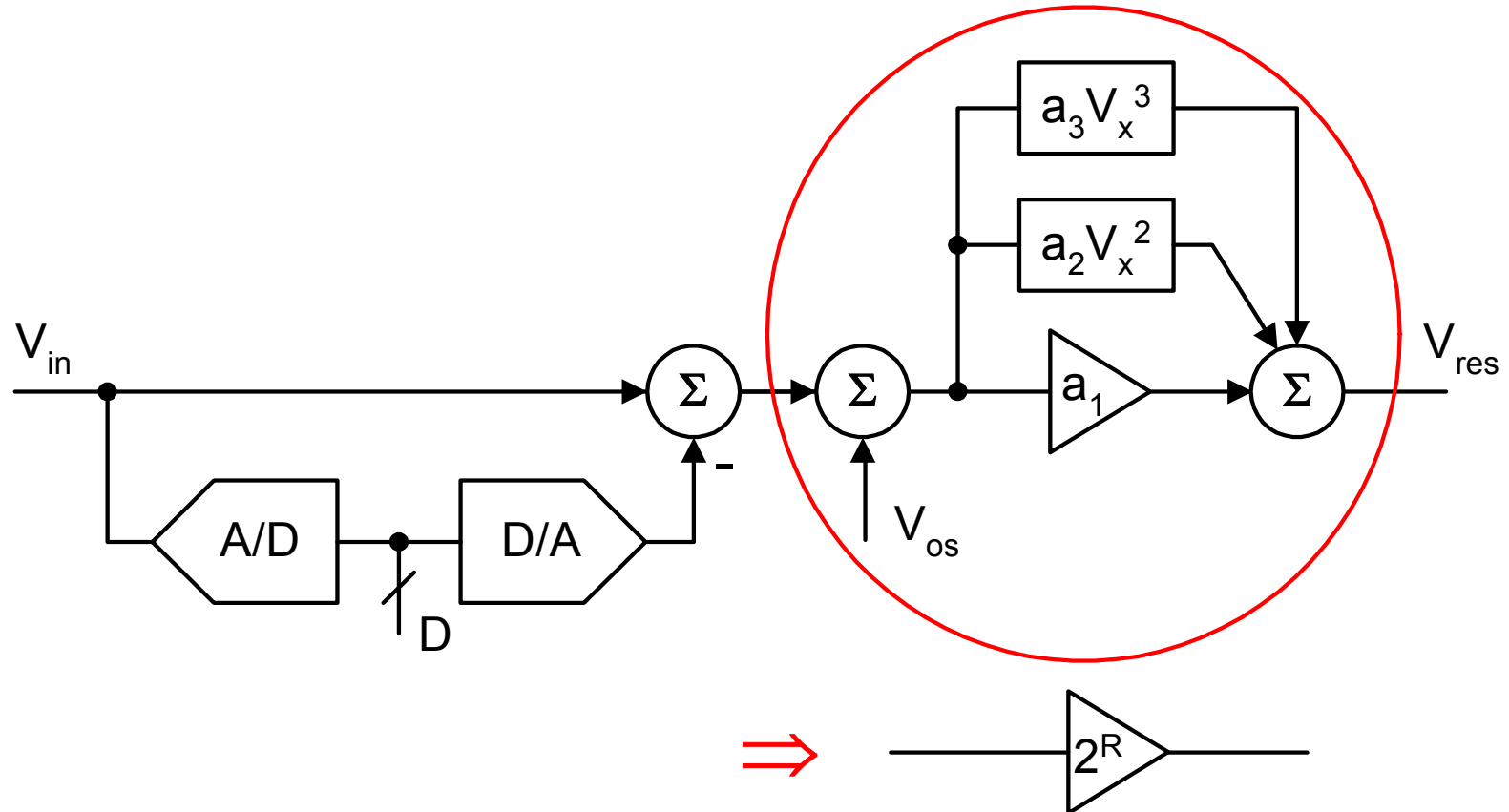


□ How can we correct errors digitally ?

Offset Pushthrough

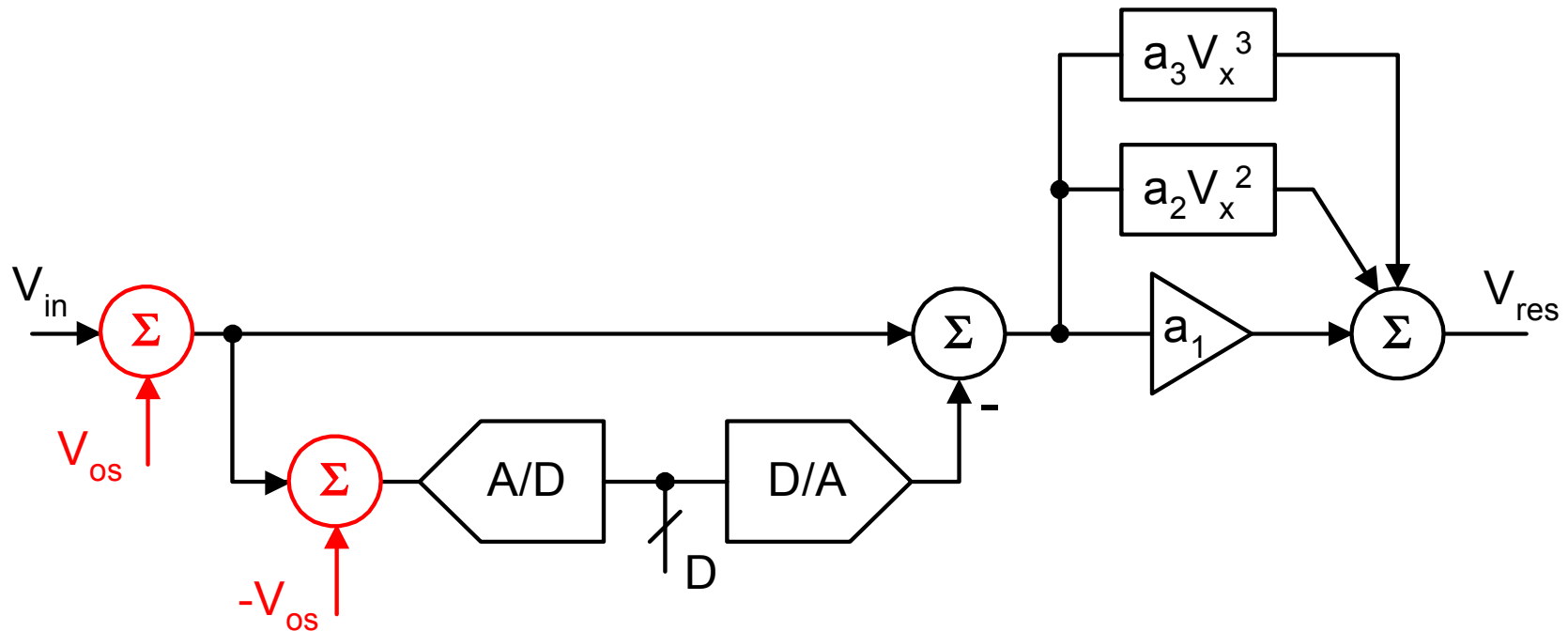


- ❑ Input referred converter offset, does not harm linearity
- ❑ Equivalent sub-A/D offset can be addressed with digital RSD arithmetic [Lewis, 1987]

Gain Error Pushthrough

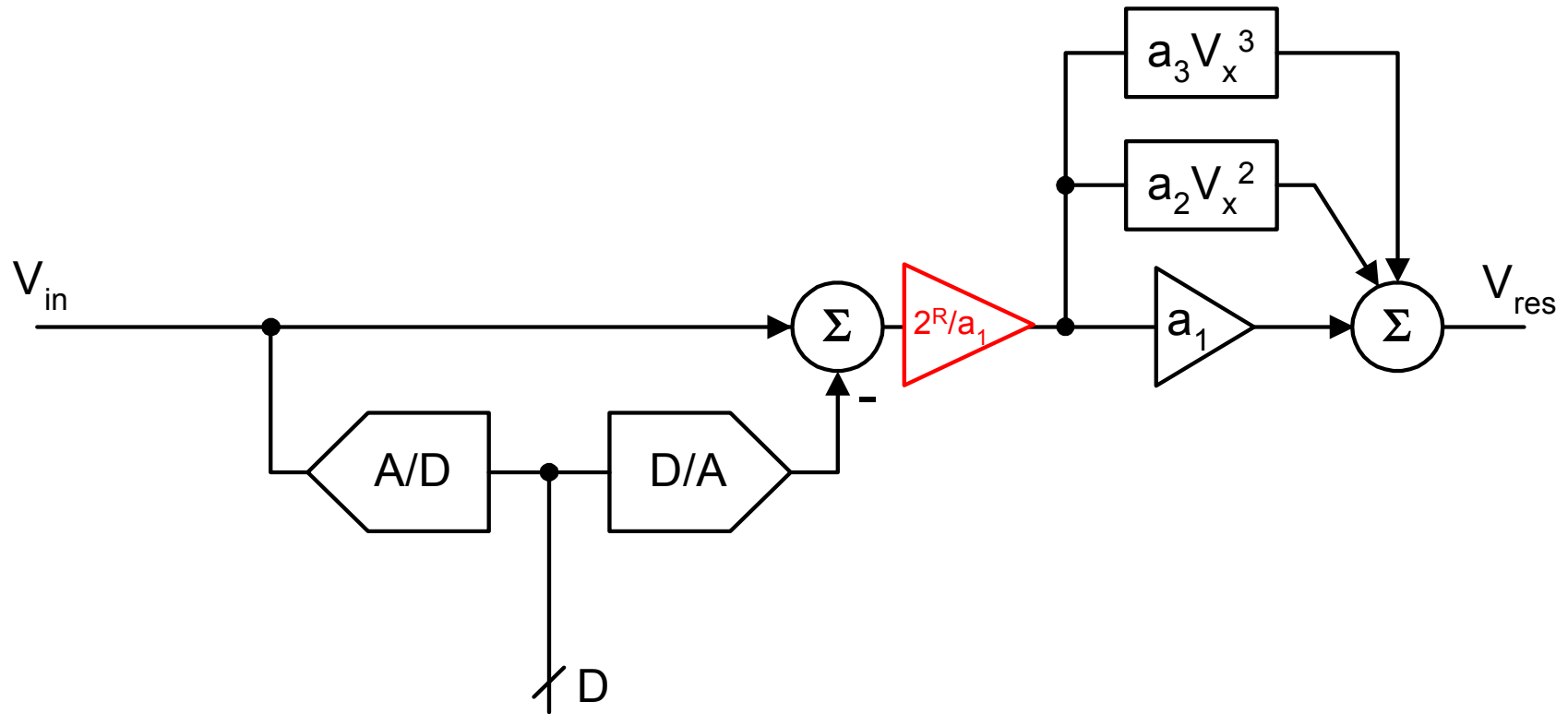


Gain Error Pushthrough

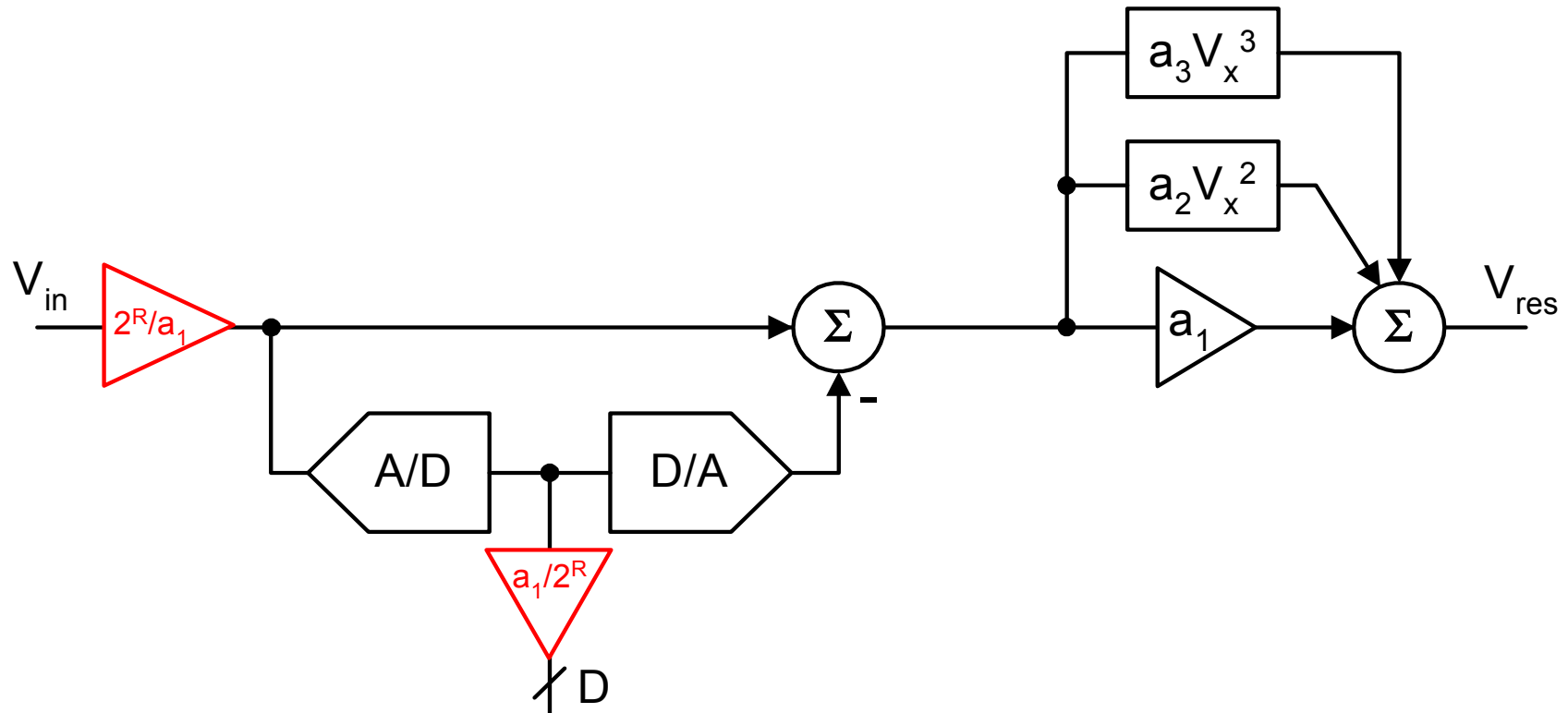

- ❑ Correct digital weight of sub-conversion [Karanicolas, 1993]
- ❑ Results in (often) tolerable input referred gain error

Second Order Cancellation

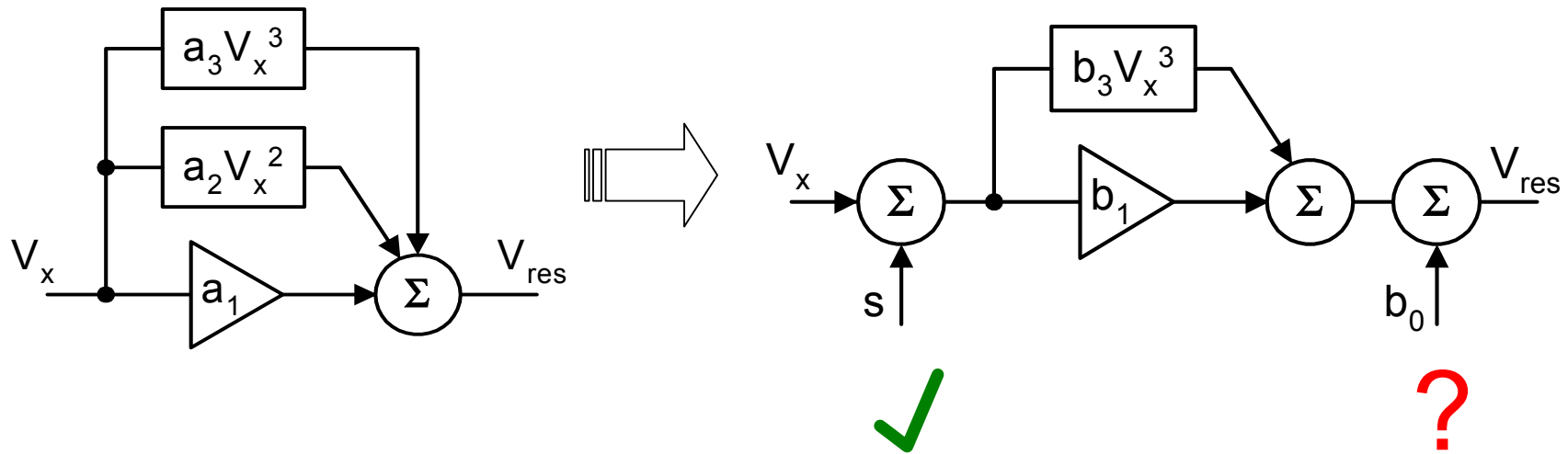


If $a_3 \neq 0$:

$$a_1x + a_2x^2 + a_3x^3 = b_0 + b_1(x - s) + b_3(x - s)^3$$


$$\left[\text{With: } b_3 = a_3 \quad b_1 = a_1 - \frac{a_2^2}{3a_3} \quad b_0 = \frac{2a_2^3}{27a_3^2} - \frac{a_1a_2}{3a_3} \quad s = \frac{a_2}{3a_3} \right]$$

Use of Digitized Residue

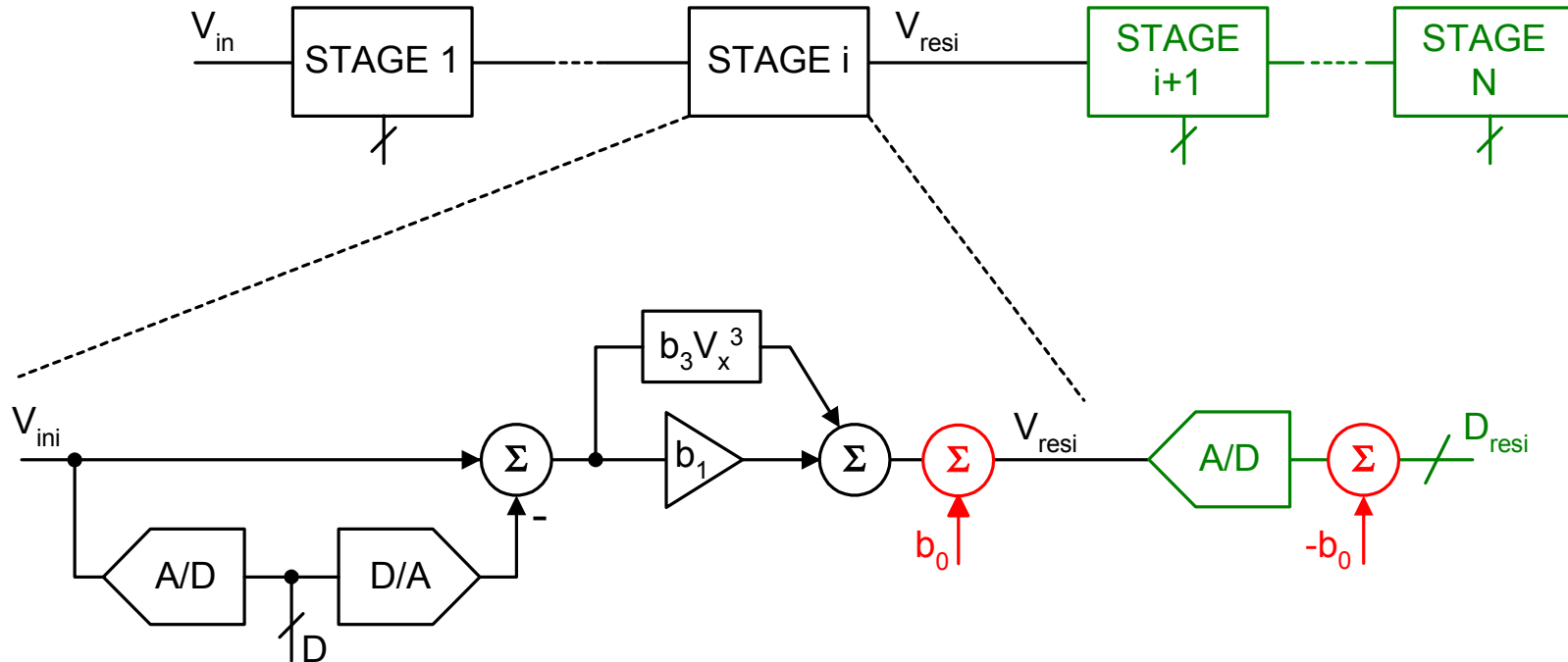


- ❑ Compensate error using digital backend representation of residue
- ❑ Add 1-2 bits to backend to reduce quantization error

Third Order Correction

 


Third Order Correction

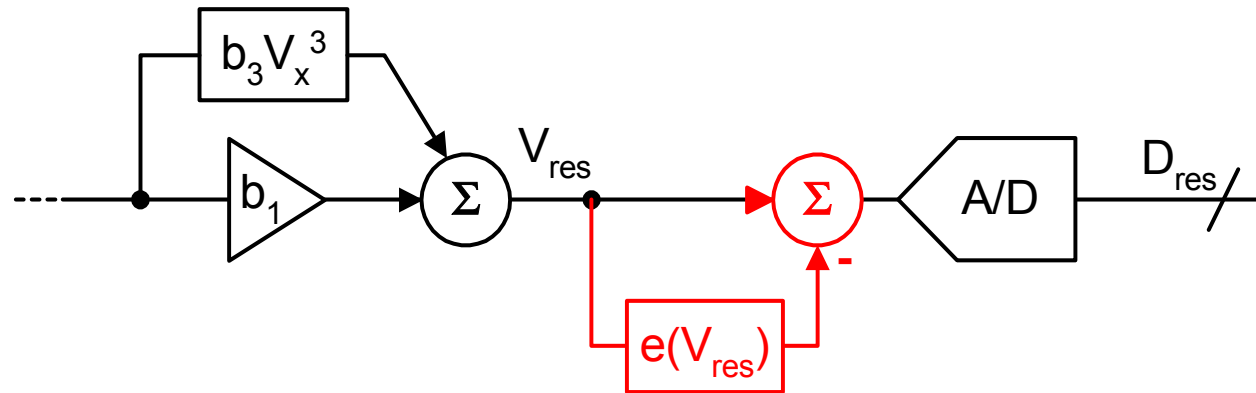


$$e(V_{res}) = V_{res} - 2 \sqrt{-\frac{1}{3p_3}} \cos \left[\frac{\pi}{3} + \frac{1}{3} \cos^{-1} \left(\frac{V_{res}}{2 \cdot \sqrt{-\frac{1}{27p_3}}} \right) \right] \quad \text{with: } p_3 = \frac{b_3}{b_1^3} < 0$$

Third Order Correction

 

- ❑ Single-parameter correction function can be pre-computed and stored in look-up table (ROM)
- ❑ Small ROM size achievable through continuous data compression methods

Complete Digital Correction

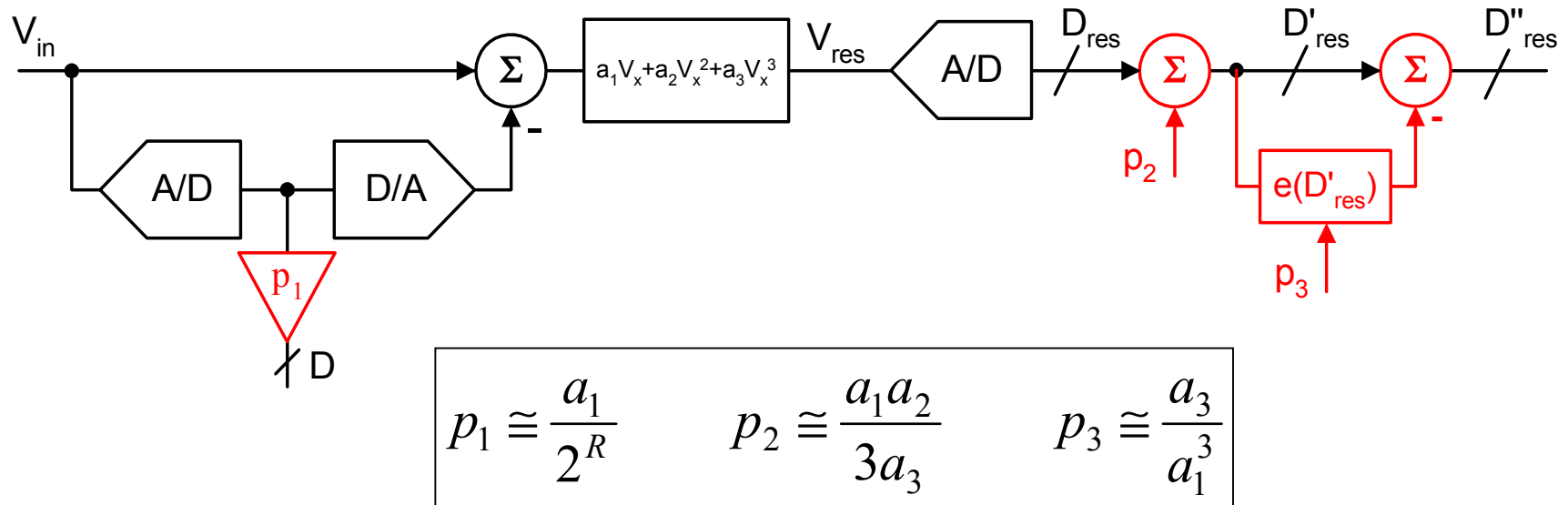


- How can we measure/calibrate parameters in digital domain?

Outline


- Motivation
- Digitally Assisted Pipelined ADC
 - Circuit Concepts
 - Analog Errors & Digital Compensation
 - Correction Parameter Estimation & Tracking
 - Experimental Results
- Other Work & Future Opportunities
- Conclusion

Calibration Concept

Classical Approach:

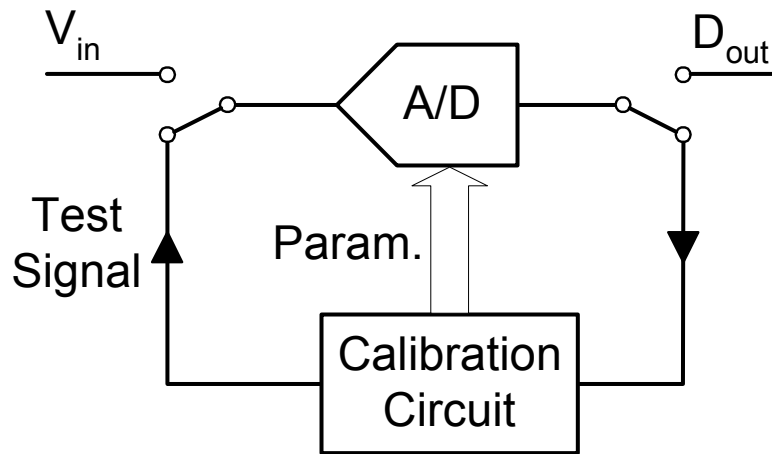


Problem:

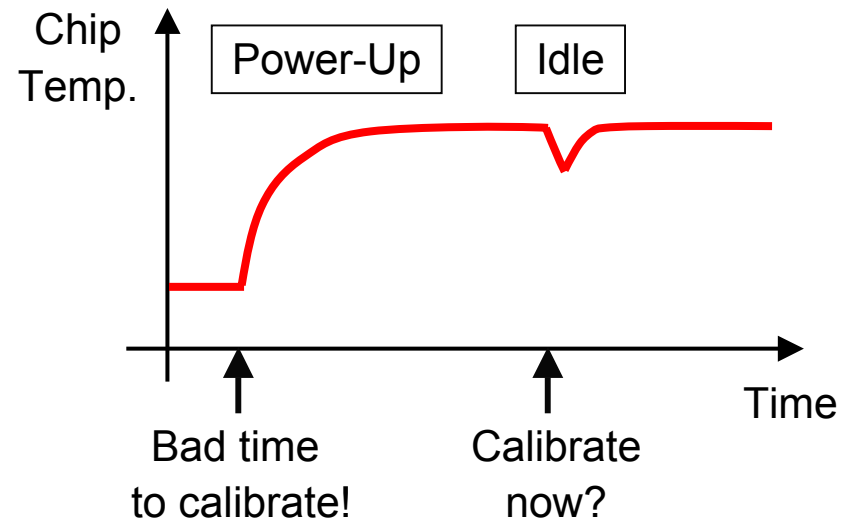

- ❑ Correction parameters depend on temperature, etc.
- ❑ Classical "foreground calibration" unfeasible
- ❑ Need continuous "background calibration" during normal A/D operation


Key: Two-Residue Pipeline Stage

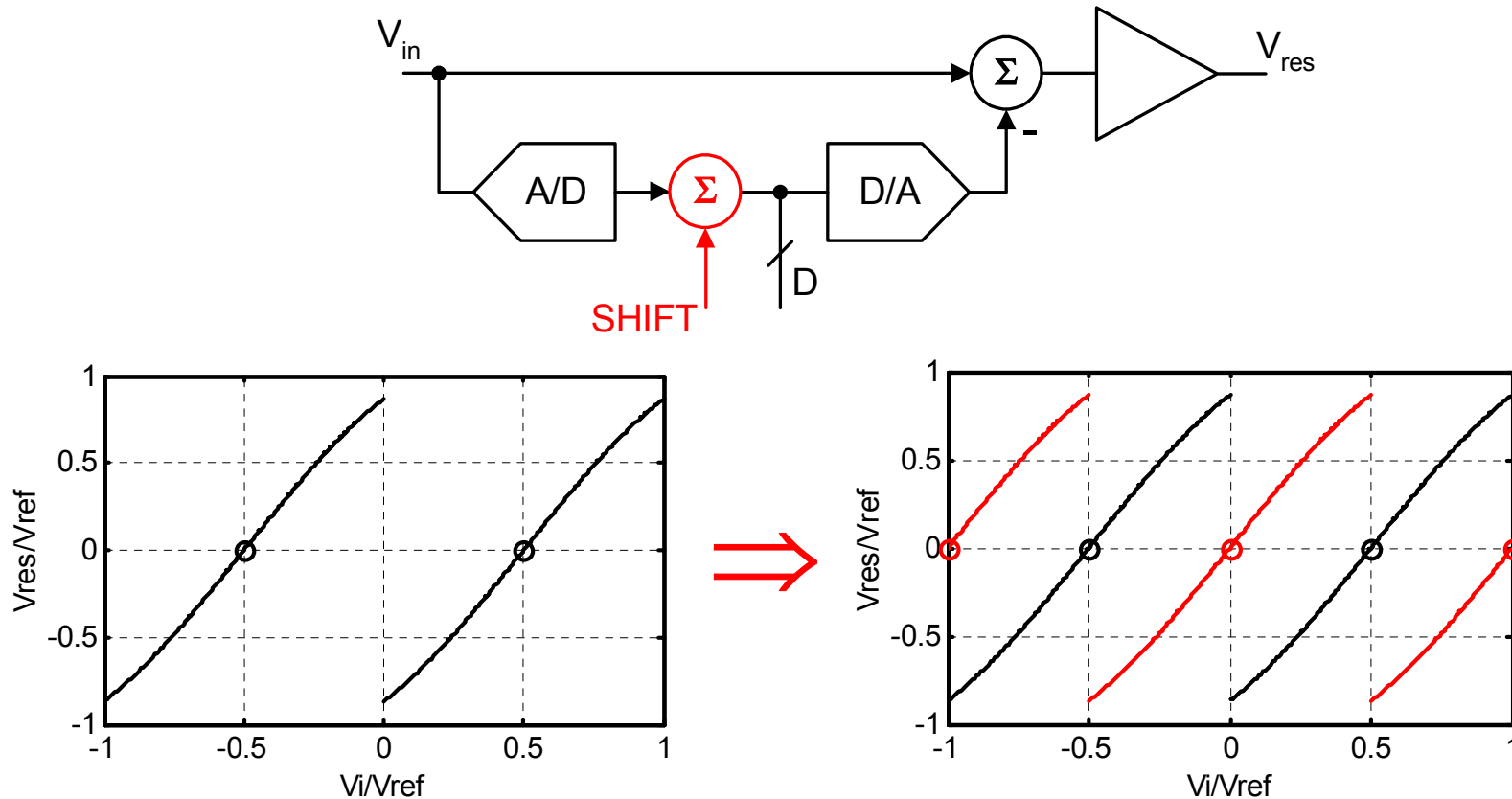


- ❑ Add: Digital SHIFT signal, redundant A/D and D/A states
- ❑ Can carry out conversion on “red” or “black” segments

Digitized Segment ($a_2=0$)

no calibration: $h_1 < h_2$

 


perfect calibration: $h_1 = h_2$

 


- ❑ Idea: Measure h_1 , h_2 and force difference to 0
- ❑ How to measure without interrupting A/D operation?
- ❑ Solution: Statistics based measurement

Distance Estimation (1)

 


- For each input sample “fair coin toss” [independent of $V_{in}(k)$] decides red/black

Distance Estimation (2)

 


- Simple input model: *stationary* random process
- Count # of codes $\leq q$ in “black channel” \rightarrow cumulative histogram $CH_{\text{ref}}(q)$

Distance Estimation (3)

 

- Place counter array in “red channel”
- After n samples, find “red” count that is closest to $CH_{\text{ref}}(q) \Rightarrow$ Distance Estimator H^*

Distance Estimation (4)

 


Can show:

$$\lim_{n \rightarrow \infty} E(H^*) \rightarrow h$$

$$\text{var}(H^*) \cong \frac{F(v_q) \cdot 2^{2B}}{n \cdot f(v_q)^2}$$


- ❑ Estimation fails if signal not “busy” around v_q
- ❑ Detectable!

LMS Loop

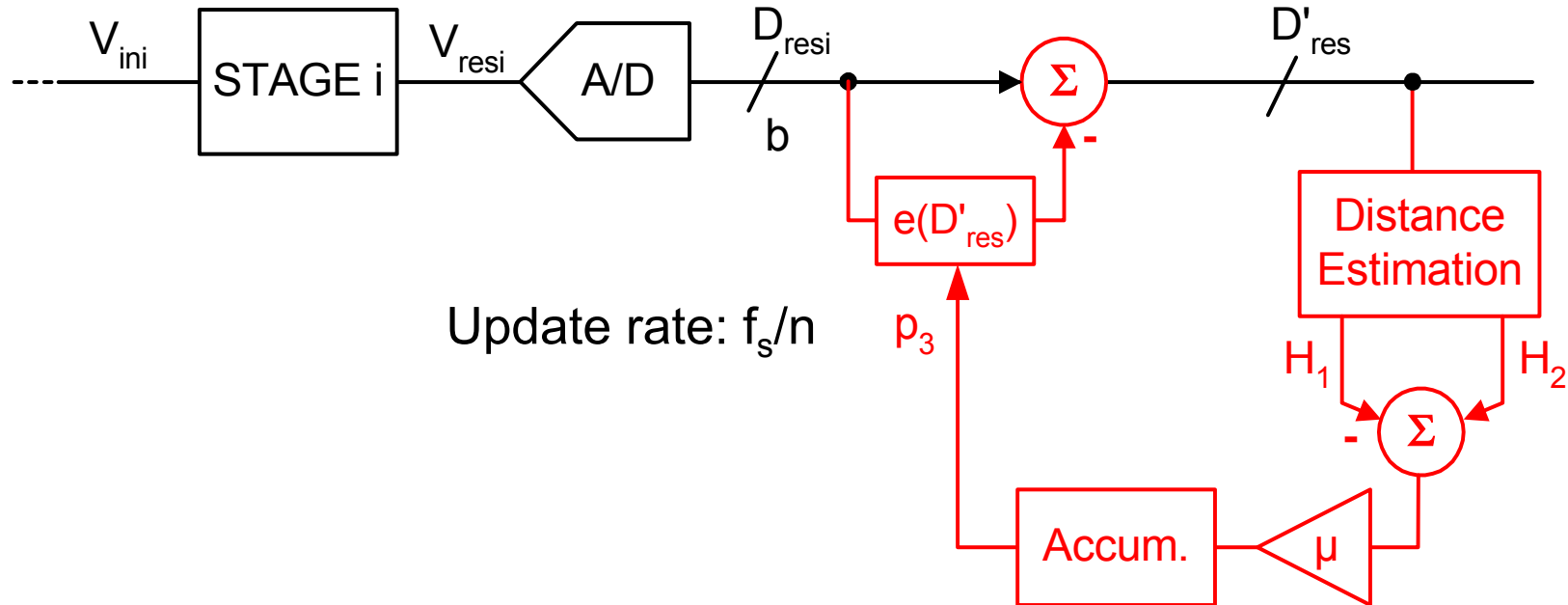

- ❑ Accumulator forces average $H_2 - H_1$ to zero
- ❑ Tradeoff: Residual variance of p_3 vs. tracking time constant
- ❑ Straightforward extension to track p_1, p_2

Tracking Time Constant

 

$$\tau_{AVG} \cong \frac{0.6 \cdot k^2 \cdot 2^{2B}}{f_s \cdot \epsilon^2}$$

Example :

$k = 3$

Confidence

$B = N - 3$

Backend res. [bits]

$f_s = 100\text{MHz}$



Sampling rate

$\epsilon = 0.5$

LSB precision

- ❑ Example: N bit converter with 3-bit Stage1, uniform input distribution
- ❑ Must address/attenuate potentially faster variations in analog domain

On-Chip Temperature Variations

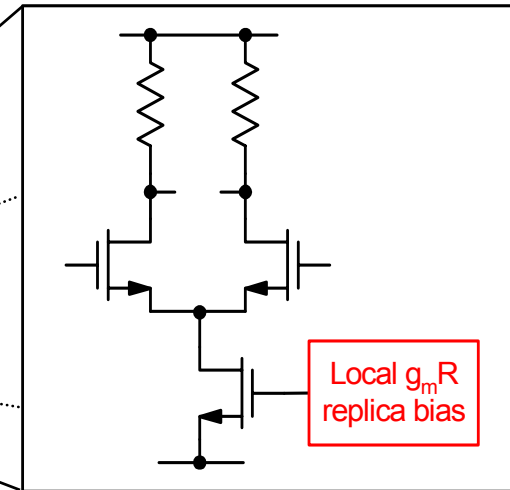 

Rule of thumb, $d=200\mu\text{m}$:
 $\Delta T_{\text{remote}} / \Delta T_{\text{local}} > 10$, $\tau=100\mu\text{s}$


Solutions:

- ❑ Local replica biasing
- ❑ Keep distance to “hot spots”, common centroid layout

Outline


- Motivation
- **Digitally Assisted Pipelined ADC**
 - Circuit Concepts
 - Experimental Results
- Other Work & Future Opportunities
- Summary

Die Photograph

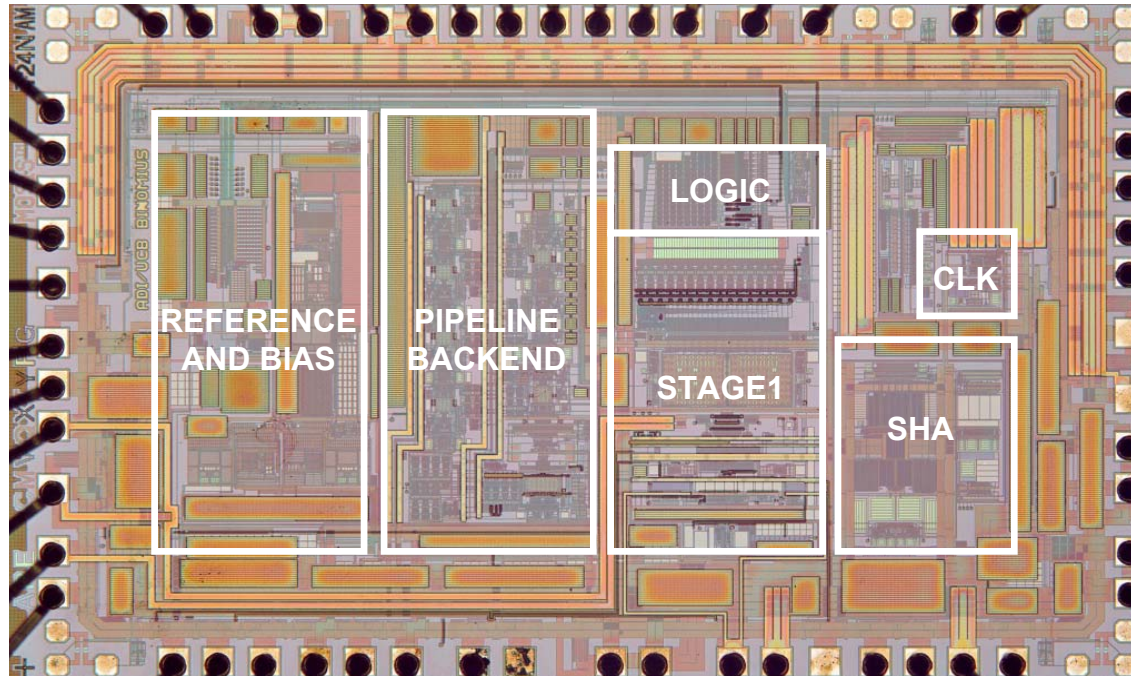


- ❑ “Proof of concept“: 12bit, 75MHz ADC, 0.35 μ m
- ❑ Re-used commercial part (Analog Devices AD9235)
- ❑ Modified only 3-bit Stage1 \rightarrow Open-loop
- ❑ Digital post-processor off-chip (FPGA)

Open Loop Pipeline Stage

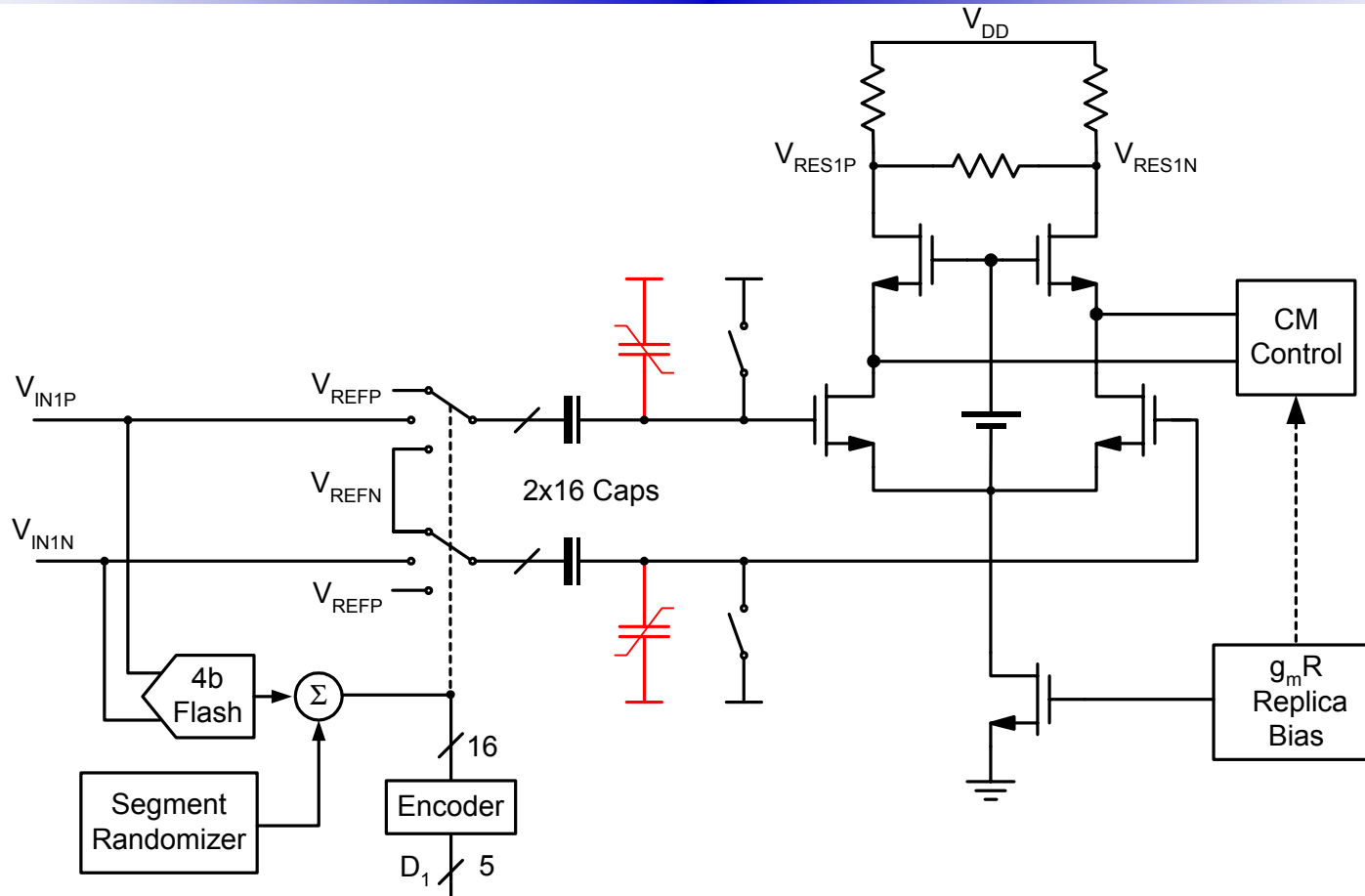


- Open-loop \Rightarrow “New” second order circuit effects


Measured INL

 

Measured INL

 


INL Zoom (Post-Proc. ON)



 


Measurement Results: Tracking

WITH REPLICA BIAS

 

WITH CONSTANT BIAS

   

Performance Summary

Technology	0.35 μ m CMOS	
Supply Voltage	3V	
Resolution	12b	
Conversion Rate	75 MSamples/sec	
	With Calibration	Without Calibration
SNR $f_{in}=1\text{MHz}$ $f_{in}=40\text{MHz}$	68.2 dB 67 dB	48 dB
THD $f_{in}=1\text{MHz}$ $f_{in}=40\text{MHz}$	-76 dB -74 dB	-50 dB
SFDR $f_{in}=1\text{MHz}$ $f_{in}=40\text{MHz}$	80 dB 76 dB	52 dB
DNL	-0.5, +0.5 LSB	-1, 0.6 LSB
INL	-0.9, +0.6 LSB	-19, +16 LSB
Power Dissipation		
ADC Core	290 mW	
Output Drivers	24 mW	

- With calibration: Within data sheet of commercial part (AD9235)!

Digital Post-Processor

- ❑ Only 1st and 3rd order correction (p_1 and p_3)
- ❑ Synthesis & Place/Route results using 0.35 μ m CMOS library:


Post-Processor

8400 gates


64kBit ROM

64 Bytes RAM

Σ 1.4 mm²

 

Stage1 Power Breakdown

 

Prototype Summary

- ❑ Open-loop residue amplification
 - Reduces ADC power consumption
 - Improves deep sub- μm compatibility
 - May help in pushing attainable speed

- ❑ Resulting analog errors
 - “Slow” \rightarrow statistics based digital calibration
 - “Fast” \rightarrow analog domain techniques

- ❑ Judicious combination of digital and analog techniques \Rightarrow feasible, low overhead solution

Continuation Work

- ❑ Optimized deep sub- μm design
- ❑ Multi-stage calibration
- ❑ Cash in on simplified circuits
 - Push conversion speed
 - Explore architectural simplifications to lower power
- ❑ Work in progress at Berkeley: 12b, 200MS/s, 200mW, power 4x below state-of-the art!
- ❑ At Analog Devices: Commercial implementation for embedded applications in fine line technology

Outline

- Motivation
- Digitally Assisted Pipelined ADC
 - Circuit Concepts
 - Experimental Results
- **Other Work & Future Opportunities**
- Conclusion


Recent Digitally Assisted ADCs

Work	Target		Issues addressed			
	Performance	Low power	Amplifier Errors		Matching, Offset	Deep sub- μm compatib.
			Lin.	Nonlin.		
Murmann, ISSCC 2003 Pipeline		√	√	√		√
Jamal, ISSCC 2002 Time Interleaved	√				√	
Yu, ISSCC 2001 Pipeline	√		√		√	
Ming, ISSCC 2001 Pipeline			√		√	


- ❑ So far: initial attempts, proof of concept studies
- ❑ Expected breakthrough: new, tailored ADC architectures

Dynamic Error Compensation

Static Error Model

 


Dynamic Error Model

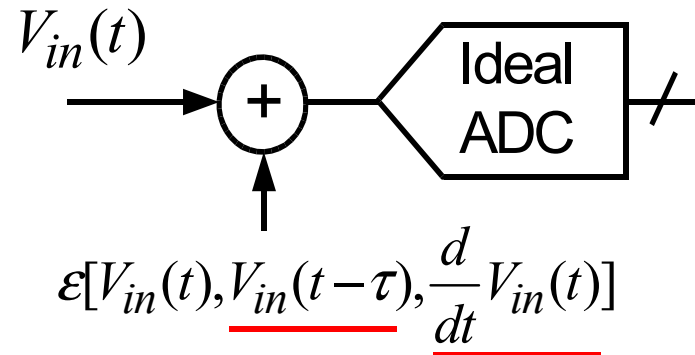

- ❑ Dynamic errors limit spurious & distortion performance many ADCs
- ❑ Today: Lots of effort to mitigate dynamic errors through analog domain design techniques
- ❑ Future opportunity: Digital compensation!
- ❑ Feasible solution to be demonstrated

Need More “Digitally Assisted Analog”

 - ❑ Don't care only about ADC!
- ❑ Broad, multidisciplinary, system oriented approach to address showstoppers in entire analog signal chain:
 - Transducers, sensors
 - Transmission media
 - A/D and D/A conversion interfaces



Conclusion

- ❑ Demonstrated feasible concept for digitally assisted pipelined ADC
- ❑ Lots of room to explore digital post-processing techniques beyond recent efforts
- ❑ Visions:
 - New ADC topologies that are tailored to maximally benefit from digital assistance
 - System level: Expand on compensation of analog signal path nonidealities