

High Performance Digital Fractional-N Frequency Synthesizers

**Michael Perrott
October 16, 2008**

**Copyright © 2008 by Michael H. Perrott
All rights reserved.**


Why Are Digital Phase-Locked Loops Interesting?

- **PLLs are needed for a wide range of applications**
 - Communication systems (both wireless and wireline)
 - Digital processors (to achieve GHz clocks)
- **Performance is important**
 - Phase noise can limit wireless transceiver performance
 - Jitter can be a problem for digital processors
- **The standard analog PLL implementation is problematic in many applications**
 - Analog building blocks on a mostly digital chip pose design and verification challenges
 - The cost of implementation is becoming too high ...

Can digital phase-locked loops offer excellent performance with a lower cost of implementation?


Just Enough PLL Background ...

What is a Phase-Locked Loop (PLL)?

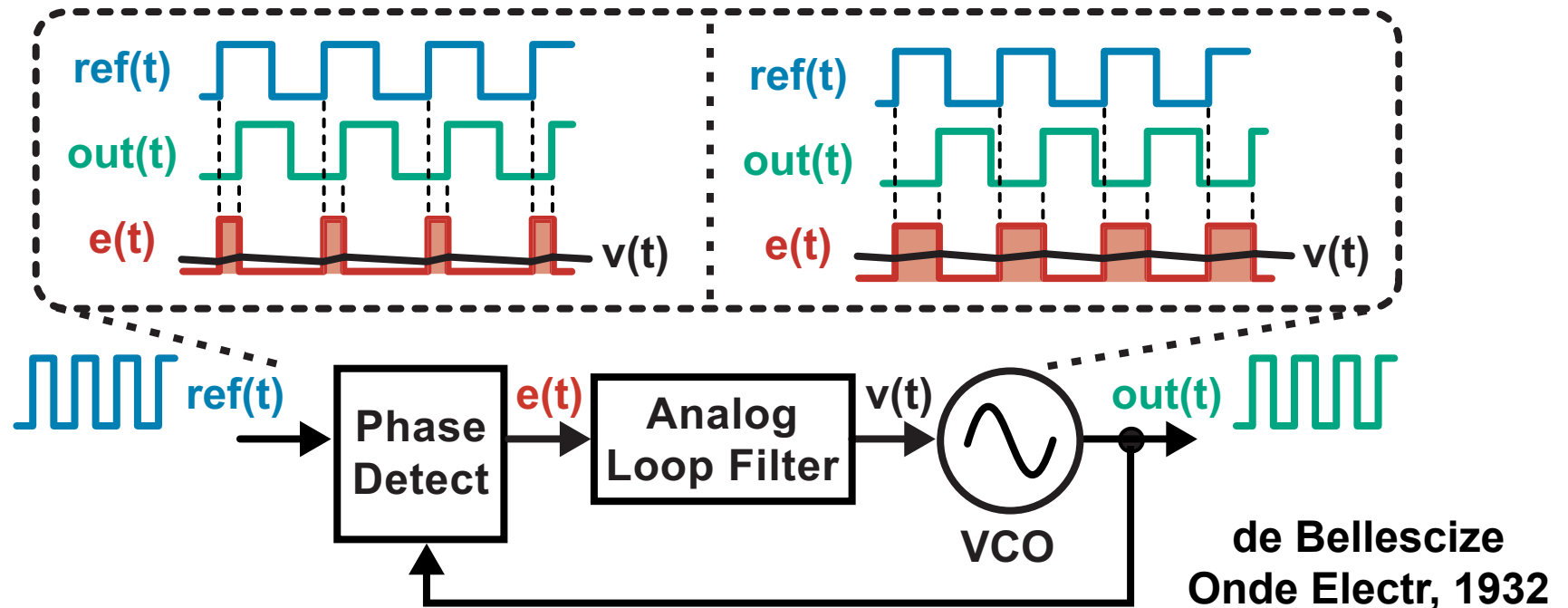

- VCO efficiently provides oscillating waveform with variable frequency
- PLL synchronizes VCO frequency to input reference frequency through feedback
 - Key block is phase detector
 - Realized as *digital gates* that create pulsed signals


Integer-N Frequency Synthesizers

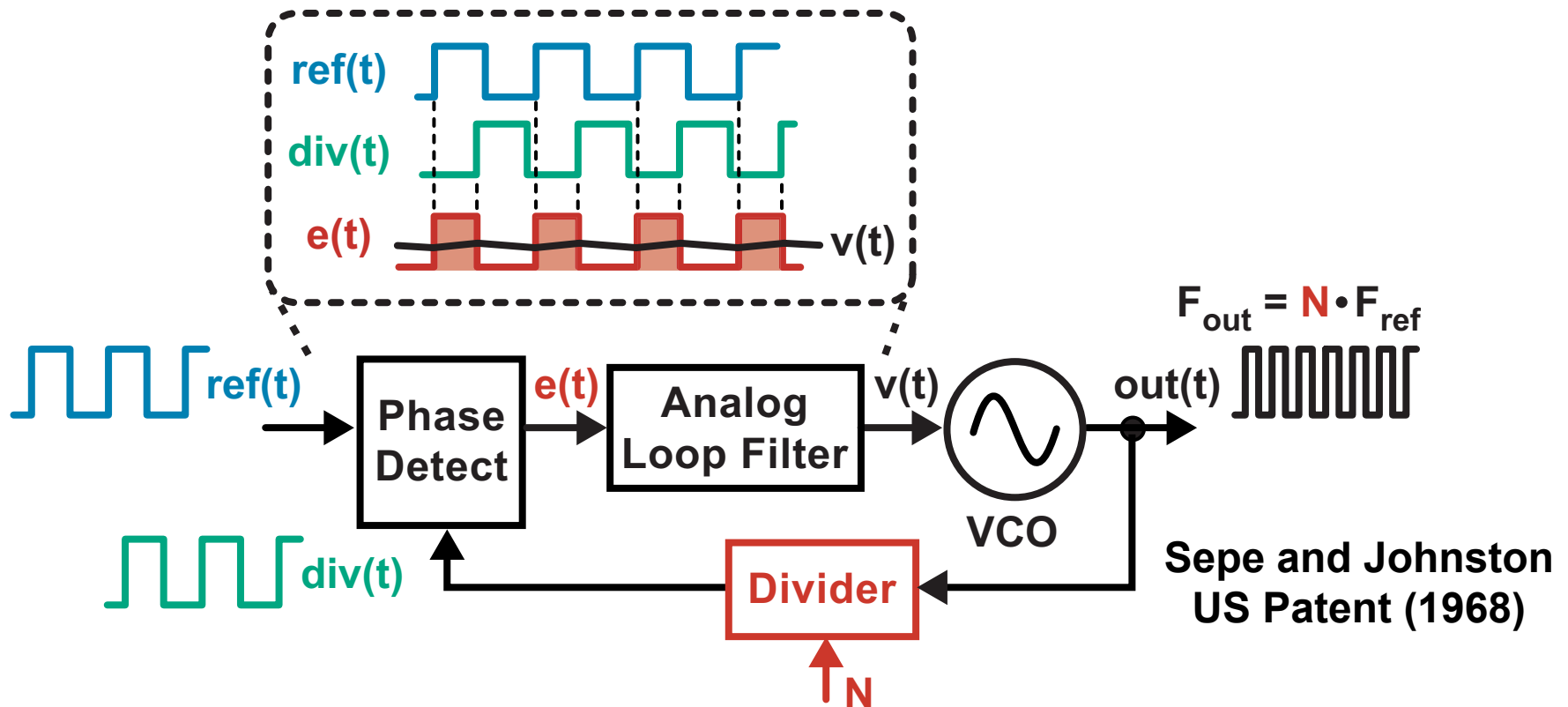

- Use digital counter structure to divide VCO frequency
 - Constraint: must divide by integer values
- Use PLL to synchronize reference and divider output

Output frequency is digitally controlled


Fractional-N Frequency Synthesizers

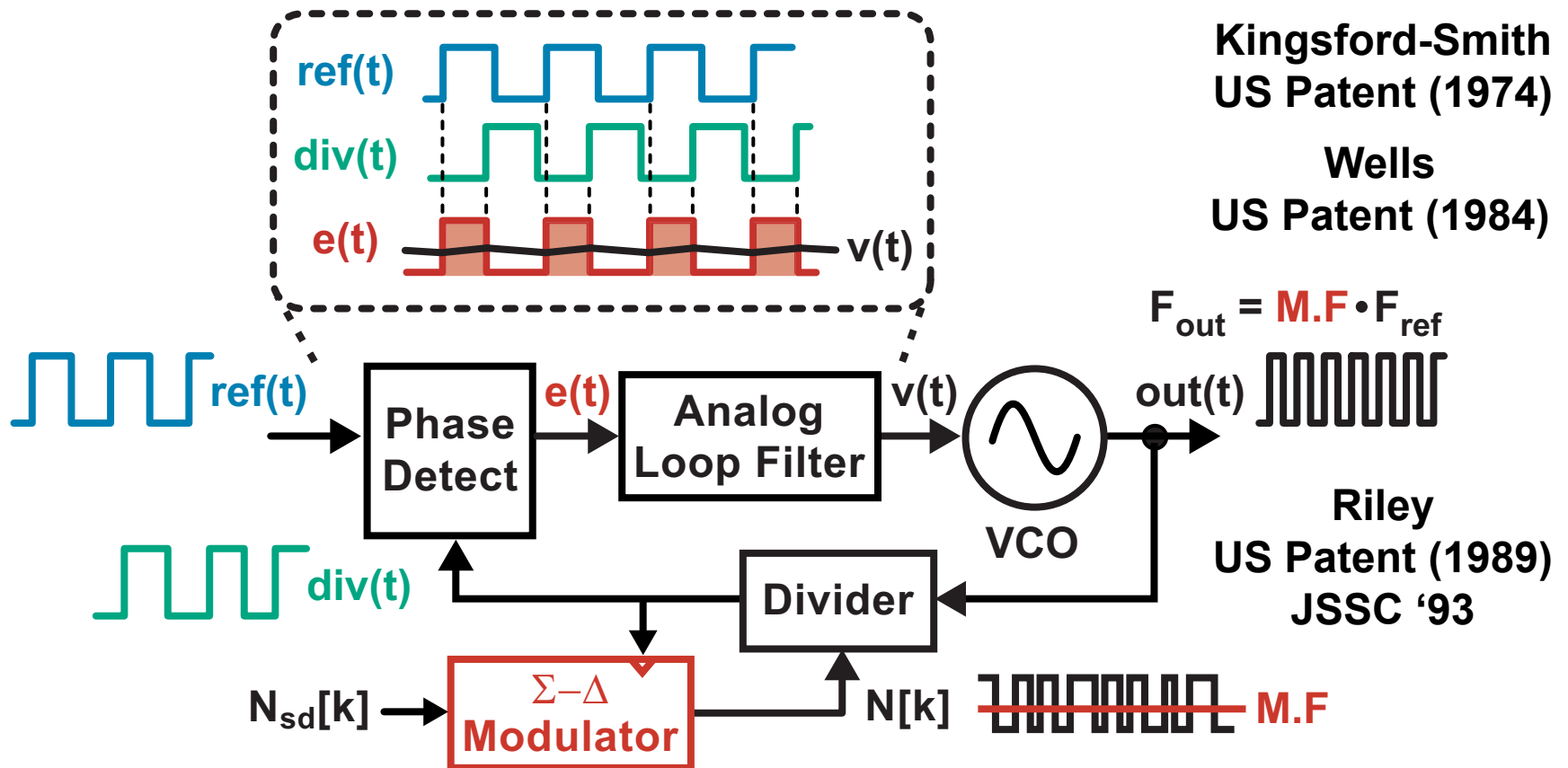


- Dither divide value to achieve fractional divide values
 - PLL loop filter smooths the resulting variations

Very high frequency resolution is achieved

The Issue of Quantization Noise

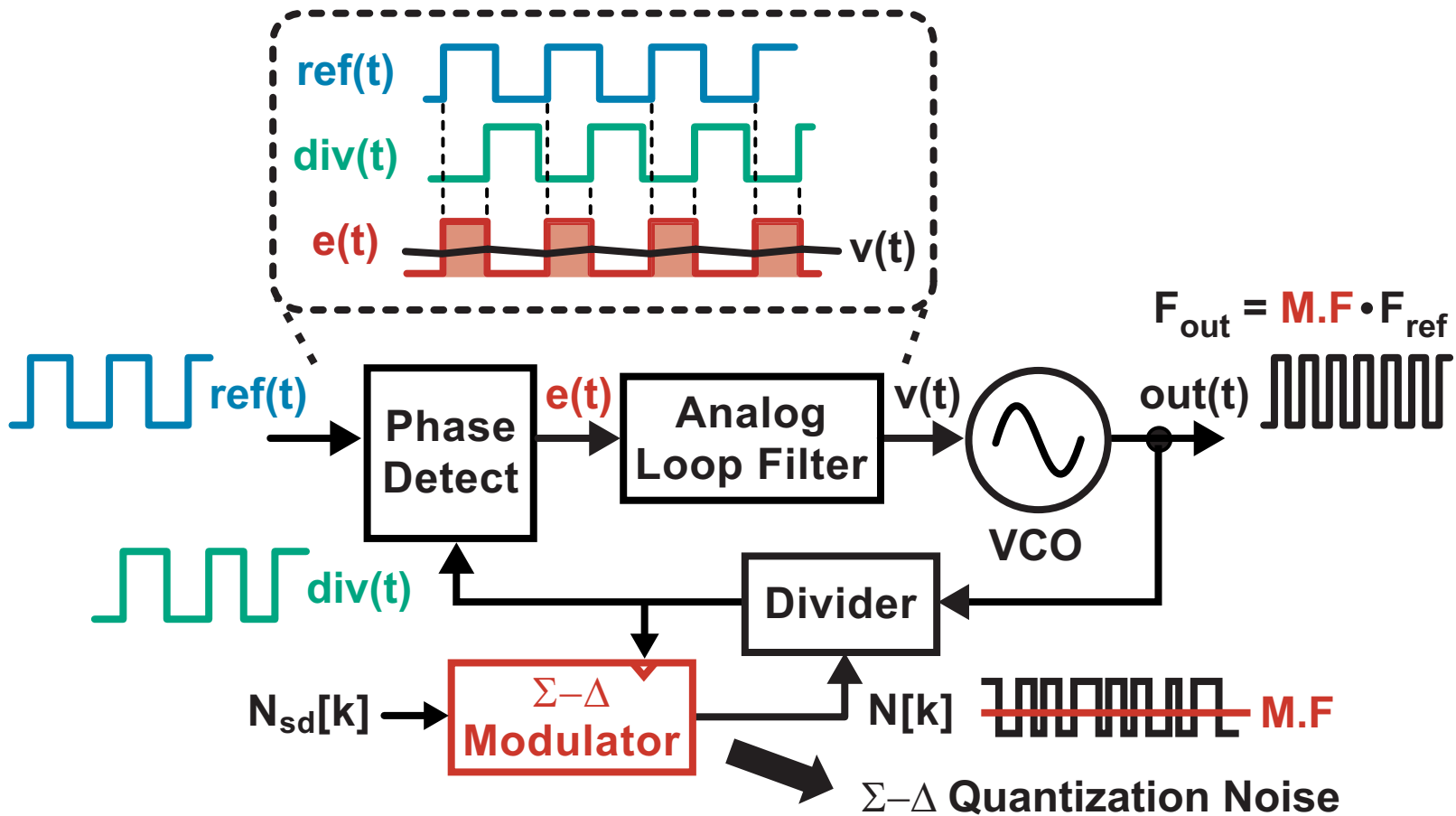


 - Limits PLL bandwidth
- Increases linearity requirements of phase detector




Striving for a Better PLL Implementation

Analog Phase Detection

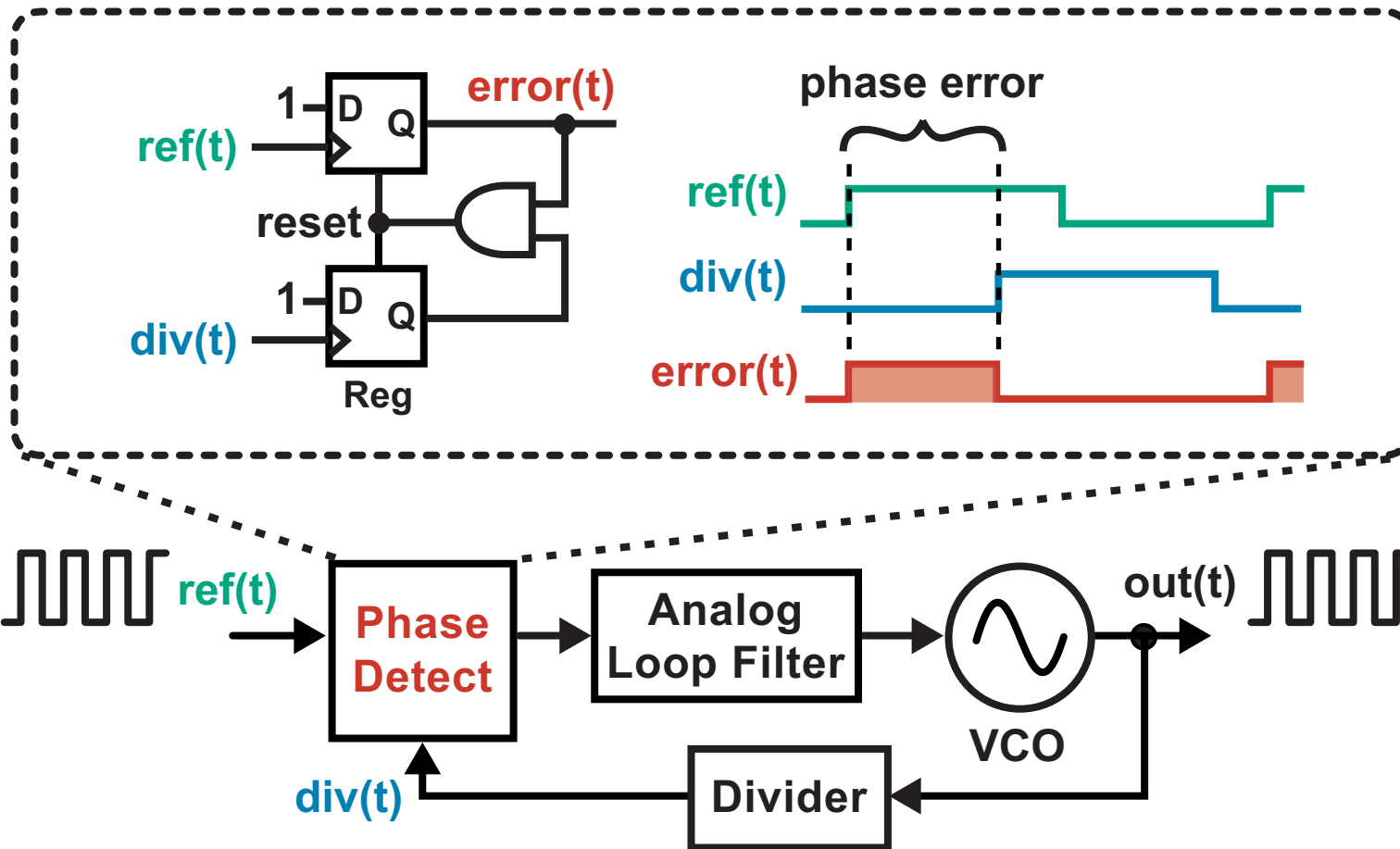


- Pulse width is formed according to phase difference between two signals
- Average of pulsed waveform is applied to VCO input

Tradeoffs of Analog Approach

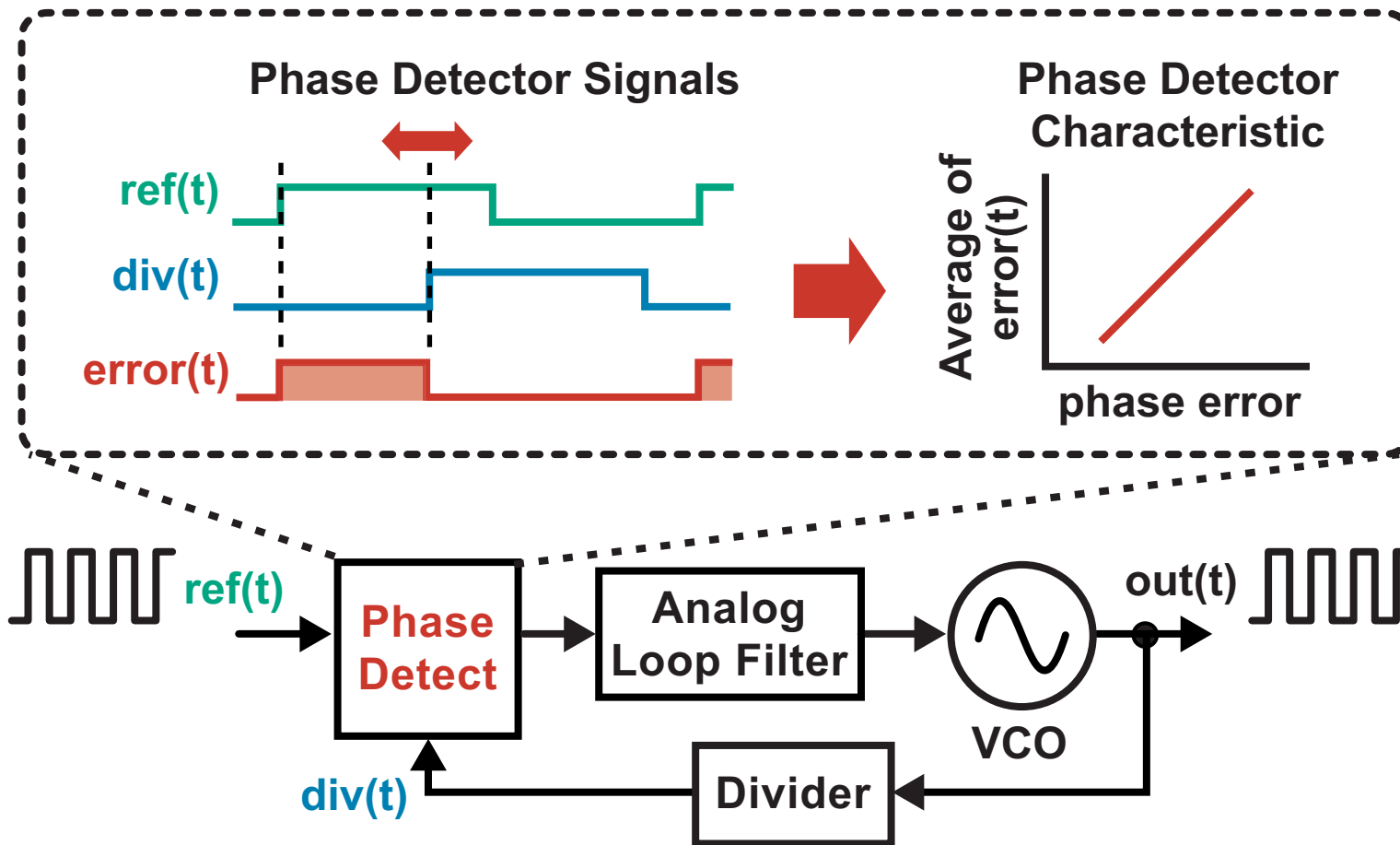



- **Benefit:** average of pulsed output is a continuous, linear function of phase error
- **Issue:** analog loop filter implementation is undesirable

Issues with Analog Loop Filter

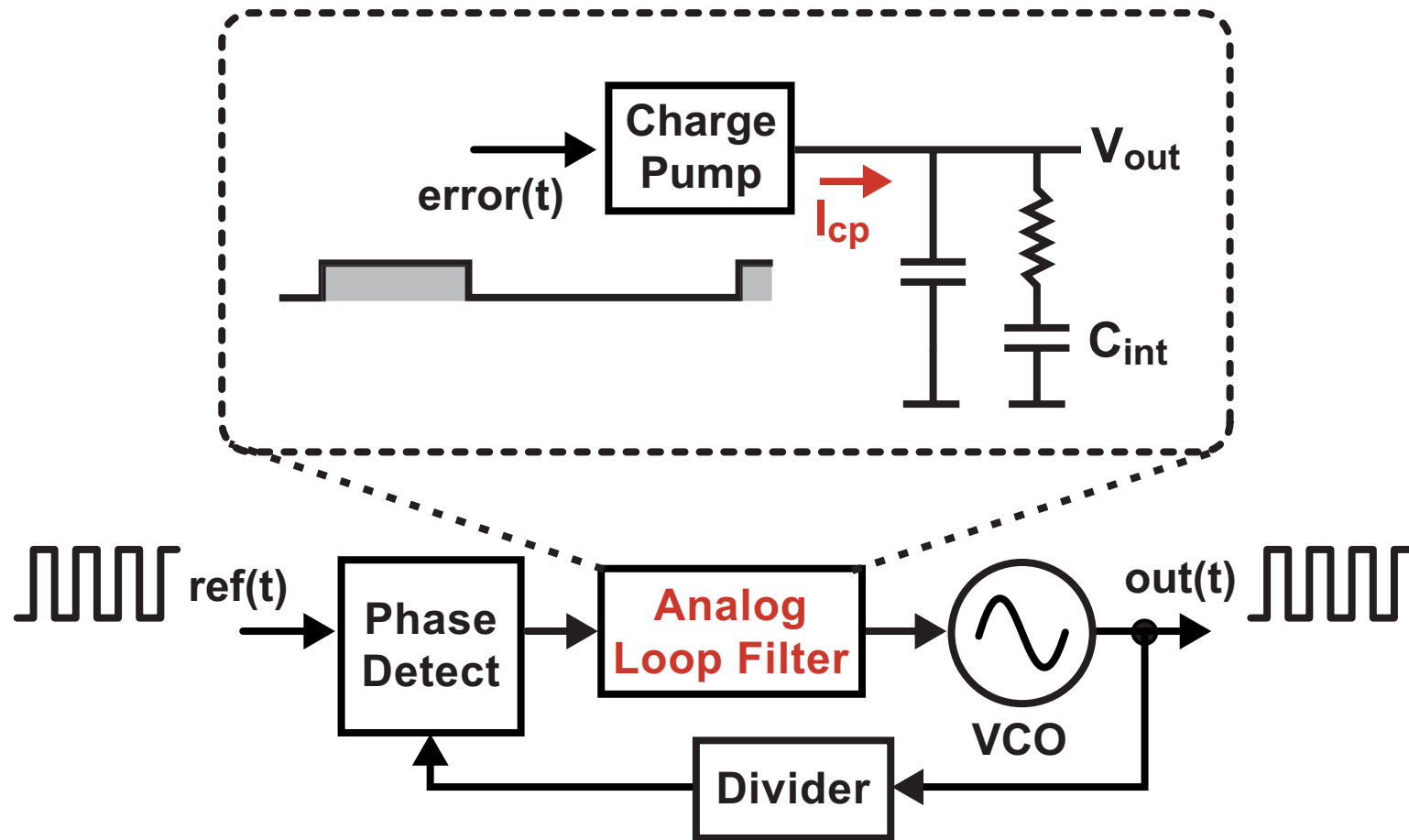

- Charge pump: output resistance, mismatch
- Filter caps: leakage current, *large area*


Going Digital ...

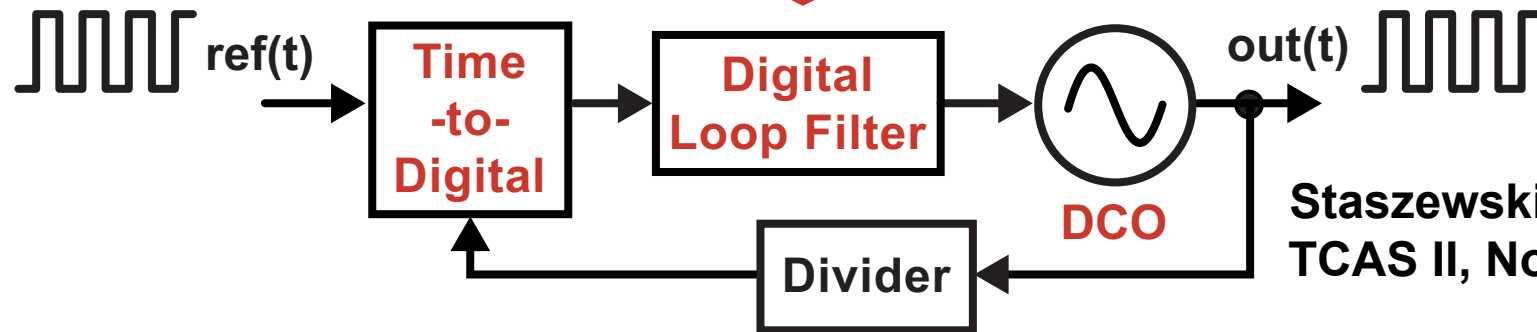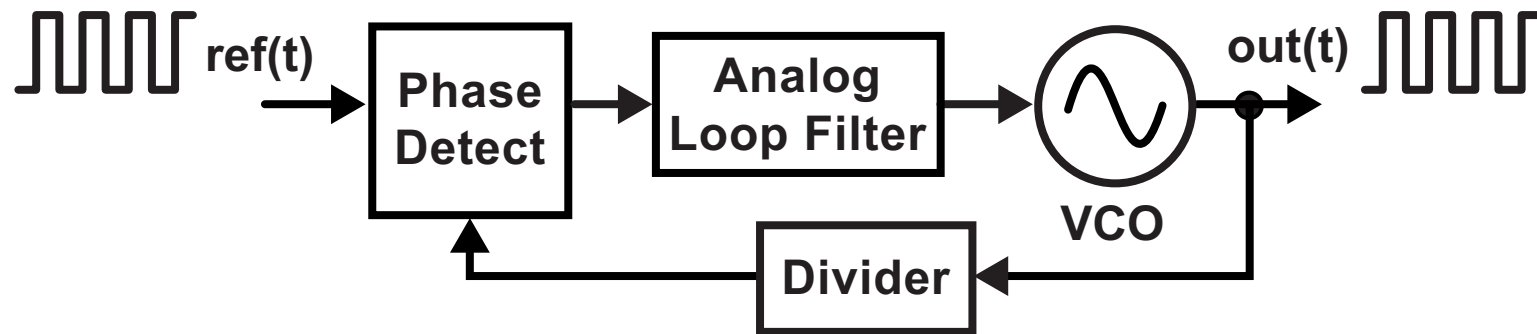

Staszewski et. al.,
TCAS II, Nov 2003



- Digital loop filter: compact area, insensitive to leakage
- Challenges:
 - Time-to-Digital Converter (TDC)
 - Digitally-Controlled Oscillator (DCO)

Classical Time-to-Digital Converter

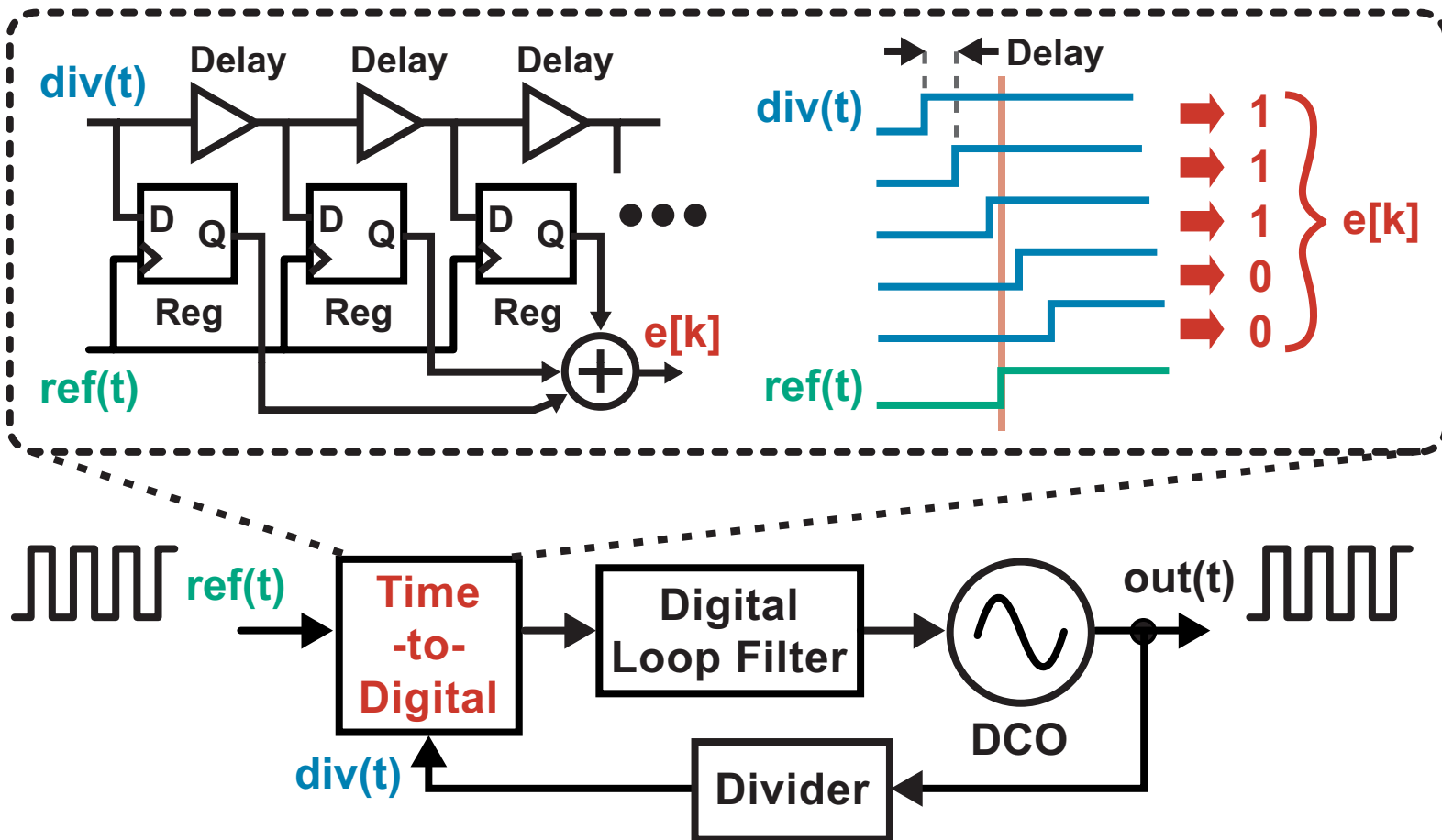

- Resolution set by a “Single Delay Chain” structure
 - Phase error is measured with delays and registers
- Corresponds to a flash architecture

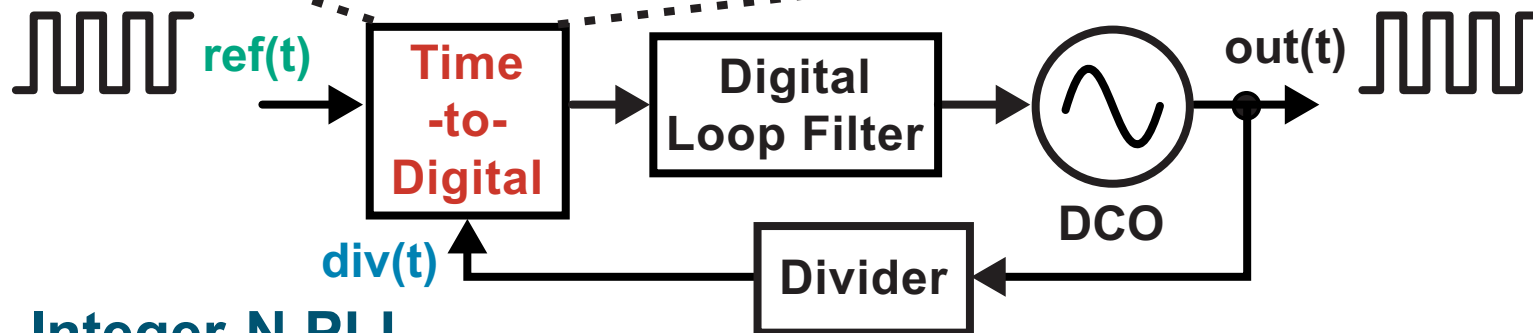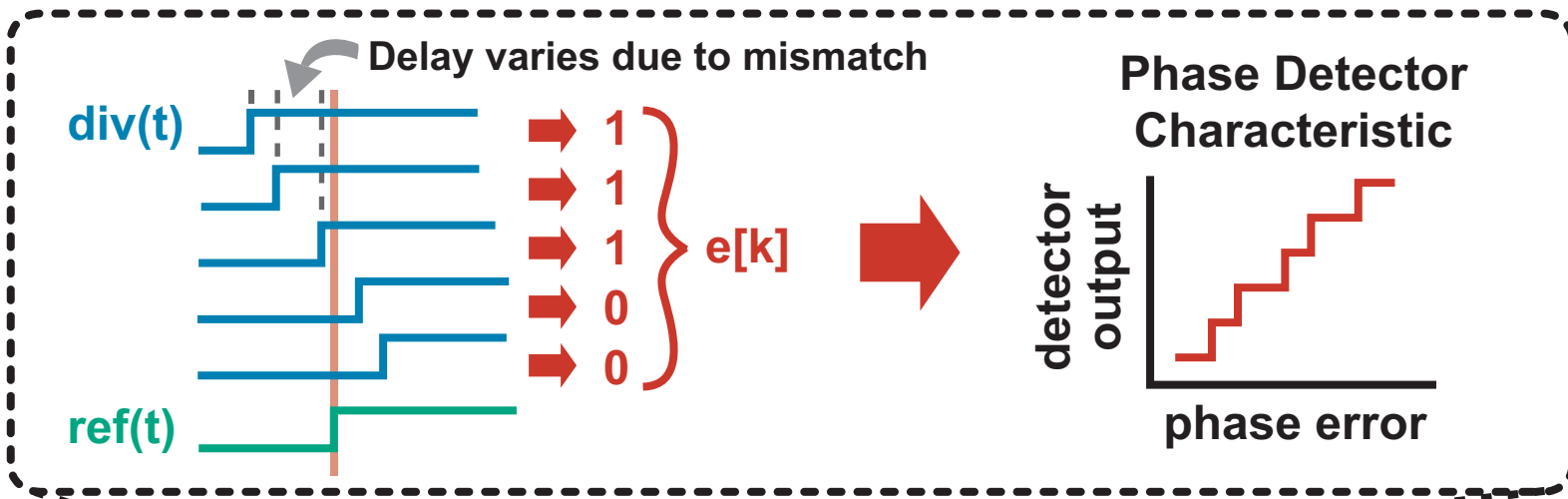Impact of Limited Resolution and Delay Mismatch




- Integer-N PLL
 - Limit cycles due to limited resolution (unless high ref noise)
- Fractional-N PLL
 - Fractional spurs due to non-linearity from delay mismatch

Examine Noise Performance: *Narrow-Bandwidth Case*

Assumptions:

 - TDC $\Delta T = 20\text{ps}$
- carrier freq. = 3.6GHz
- reference freq. = 50MHz
- PLL BW = 50kHz
- 3rd order $\Delta\Sigma$




- VCO noise dominates performance everywhere ...
- Don't need very high TDC resolution
- $\Delta\Sigma$ fractional-N quantization noise is not an issue

Examine Noise Performance: *Wide-Bandwidth Case*

Assumptions:

 - TDC $\Delta T = 20\text{ps}$
- carrier freq. = 3.6GHz
- reference freq. = 50MHz
- PLL BW = 500kHz
- 3rd order $\Delta\Sigma$




- Noise dominated by TDC at low frequencies
- Noise dominated by $\Delta\Sigma$ fractional-N noise at high frequencies

To Meet High Performance Applications like GSM....

Assumptions:


- TDC $\Delta T = 6\text{ps}$
- carrier freq. = 3.6GHz
- reference freq. = 50MHz
- PLL BW = 500kHz
- 3rd order $\Delta\Sigma$ (20dB lower)

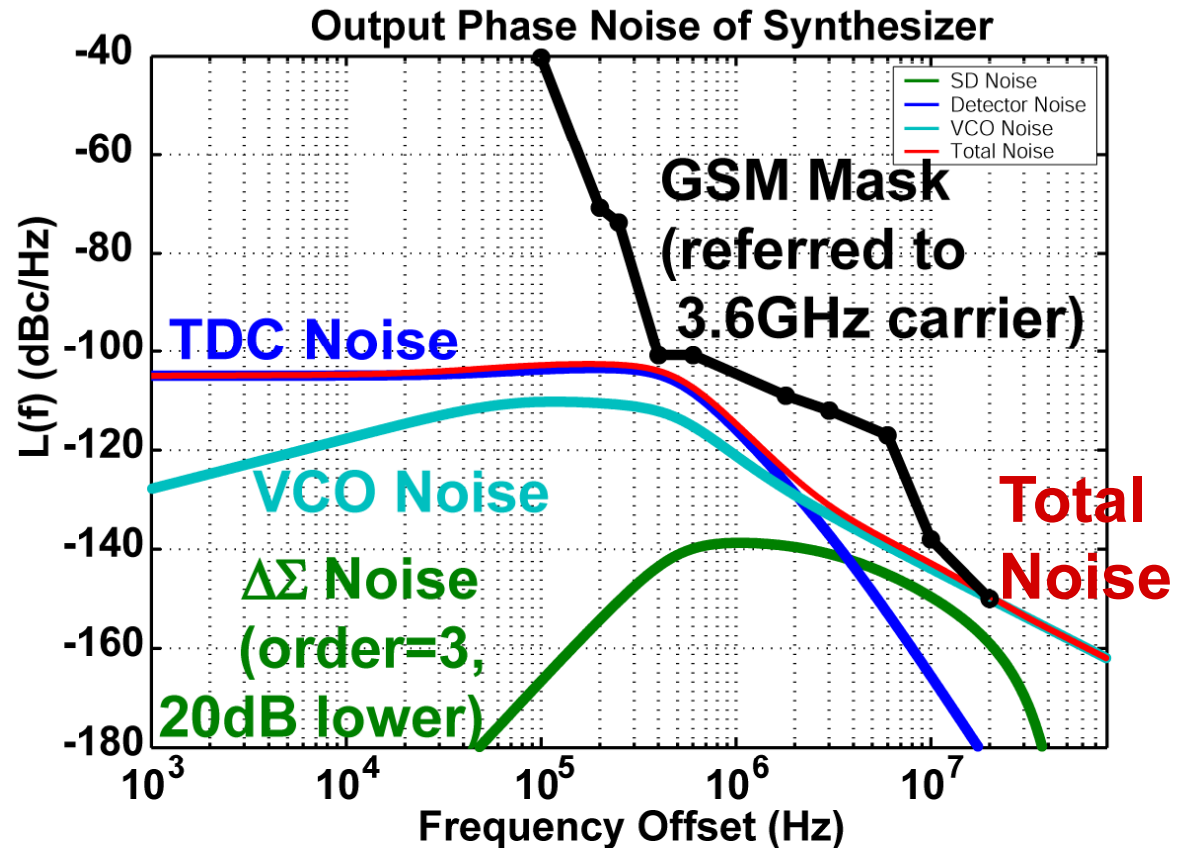

Need 6-ps TDC resolution and 20dB cancellation of $\Delta-\Sigma$ fractional-N noise to achieve 500kHz bandwidth


*Can We Improve the **Effective** Resolution of
Time-to-Digital Conversion?*

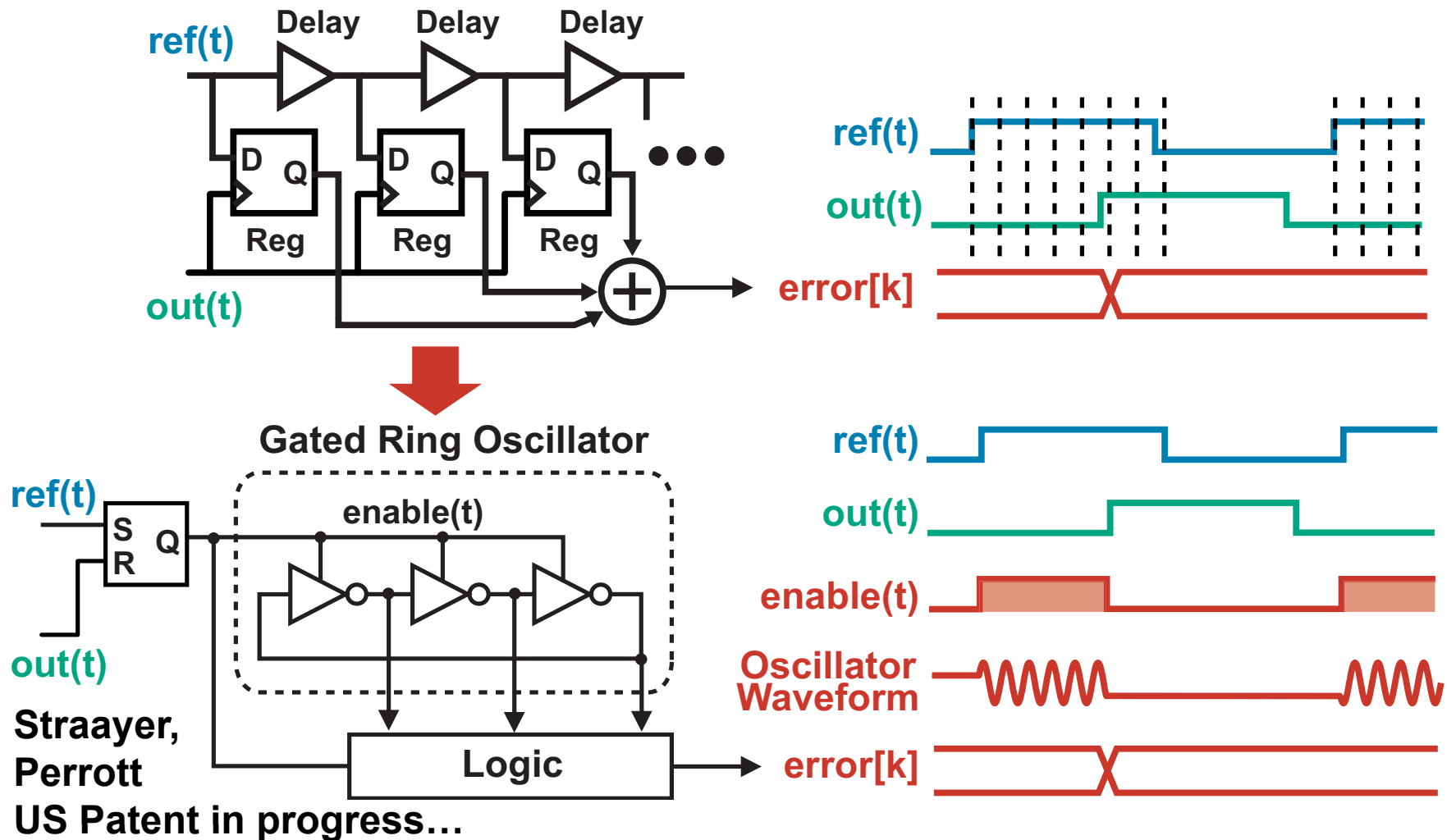Proposed Approach: A Better Time-to-Digital Converter




- This is a simplified view
 - We will need a few slides to properly explain this ...

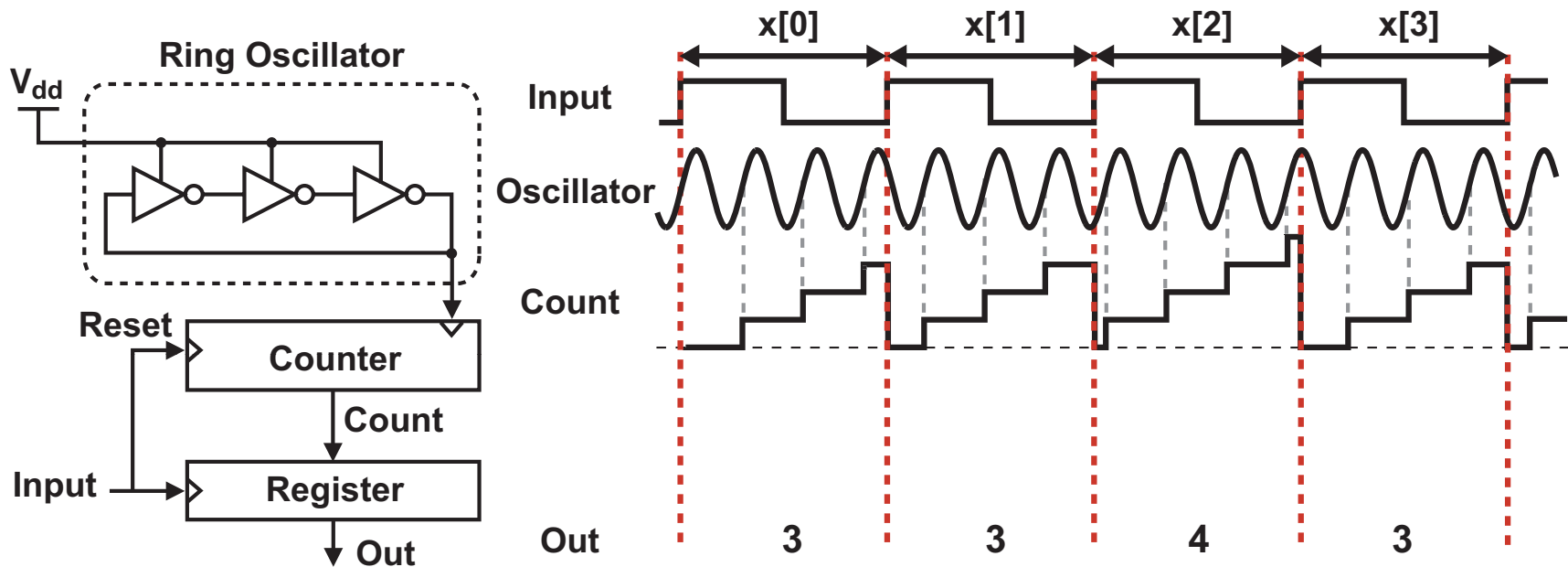Consider Measurement of the Period of a Signal




- Use digital logic to count number of oscillator cycles during each input period
 - Assume that oscillator period is much smaller than that of the input
- Note: output count per period is not consistent
 - Depends on starting phase of oscillator within a given measurement period

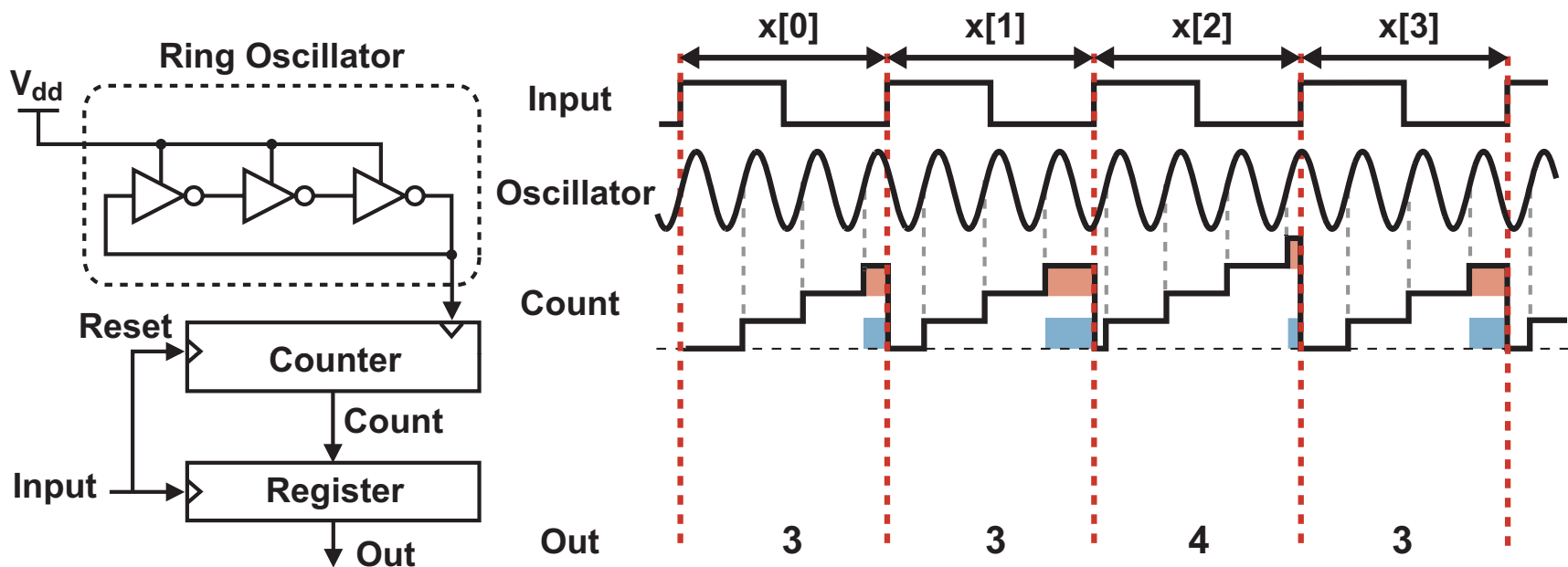Examine Quantization Error in Measurements



- Quantization error varies according to starting phase of the oscillator within a given measurement period
 - Leads to *scrambling* of the quantization noise
- But there is something rather special about the scrambling action ...

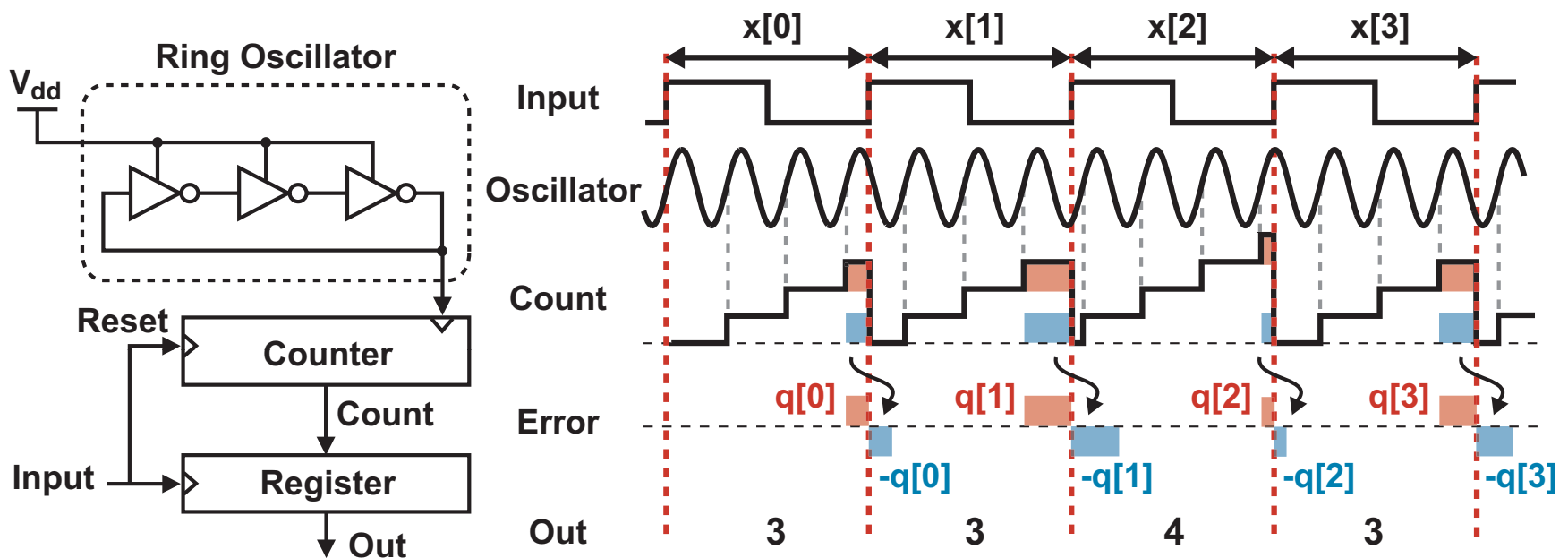A Closer Examination of Quantization Noise



- Calculate impact of quantization noise in time:


$$\begin{aligned} out[k] &= x[k] + error[k] \\ &= x[k] + q[k] - q[k-1] \end{aligned}$$

- Take Z-transform:

$$Out(z) = X(z) + (1 - z^{-1})Q(z)$$


Quantization noise is first order noise shaped!

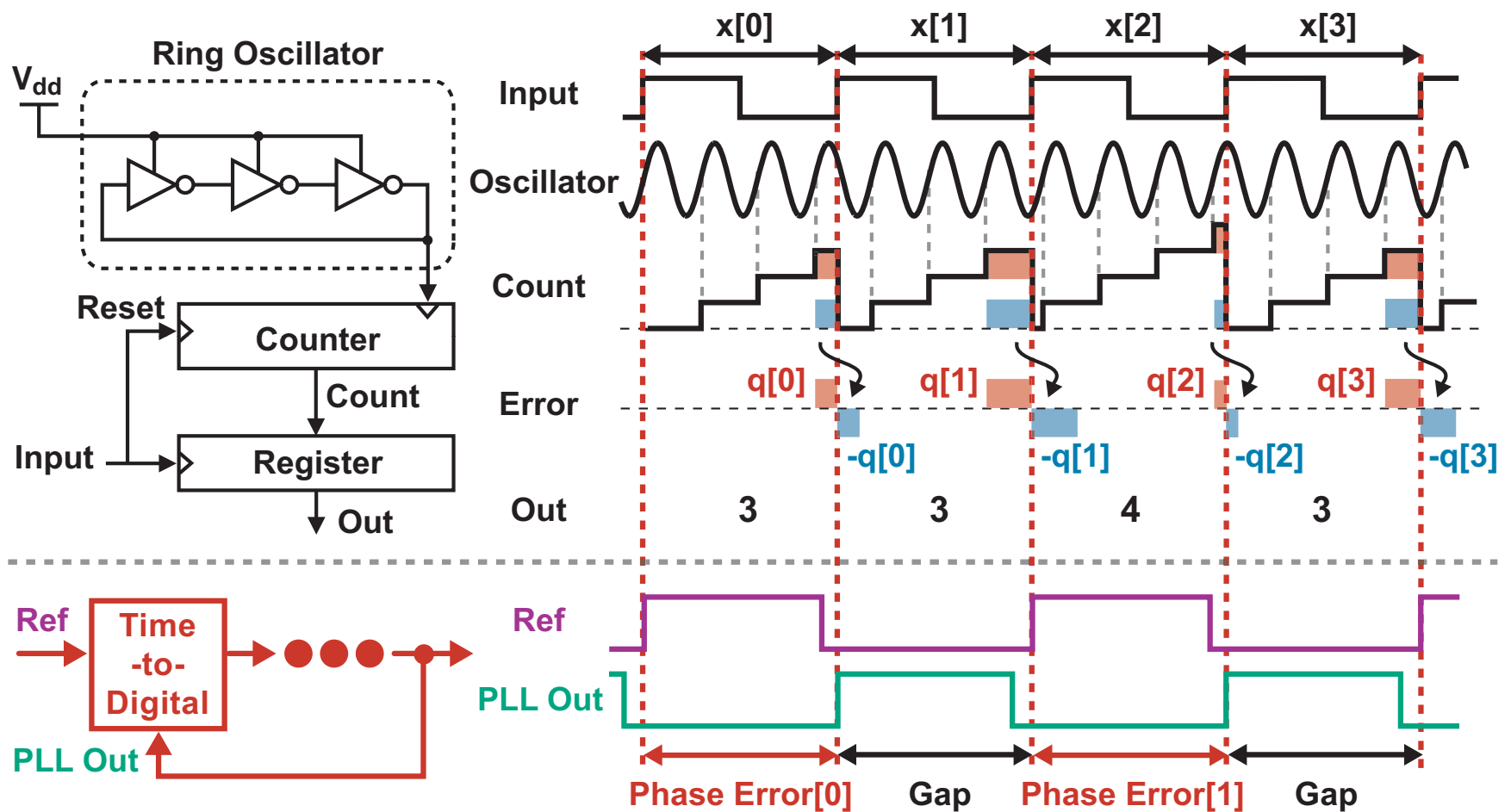Relating to Phase Error Between Two Signals



- **Measurement of phase error between two signals requires gaps between measurements**
 - What is the implication of such gaps?

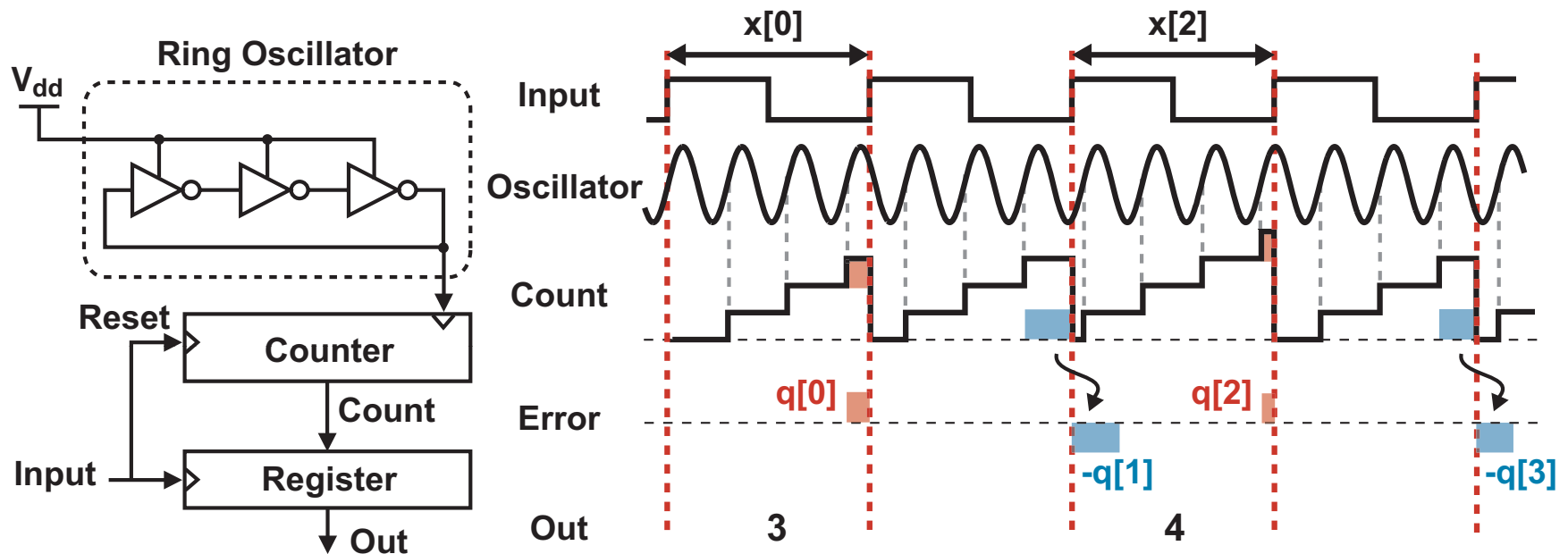The Impact of Non-Consecutive Measurements




- Consider measuring input period every *other* cycle
 - Analogous to phase measurement *between* two signals
- Key observation:
 - Quantization noise is no longer first order noise shaped!

Is there a way to restore noise shaping?


Proposed GRO TDC Structure

A Gated Ring Oscillator (GRO) TDC

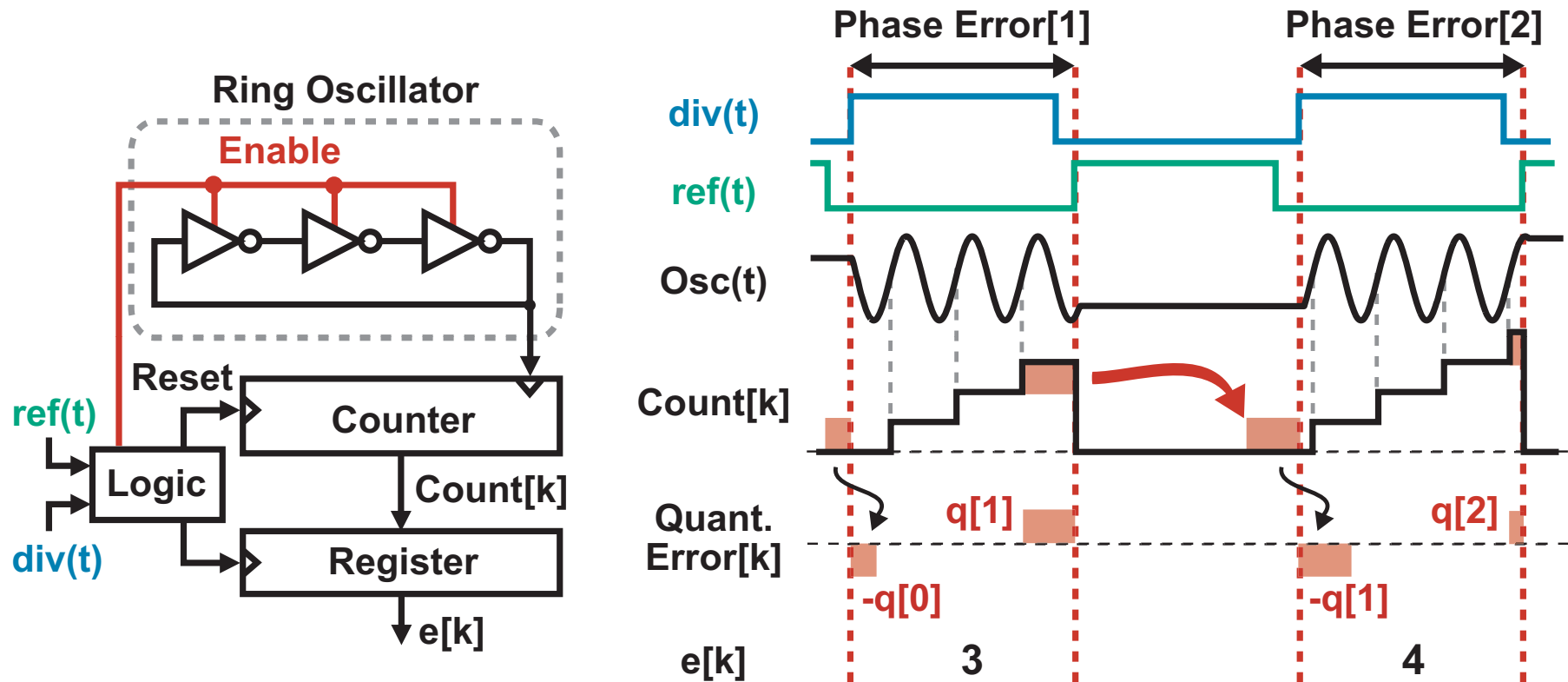


- Enable ring oscillator only during measurement intervals
 - Hold the state of the oscillator between measurements
- Quantization error becomes first order noise shaped!
 - $e[k] = Phase Error[k] + q[k] - q[k-1]$
 - Averaging dramatically improves resolution!

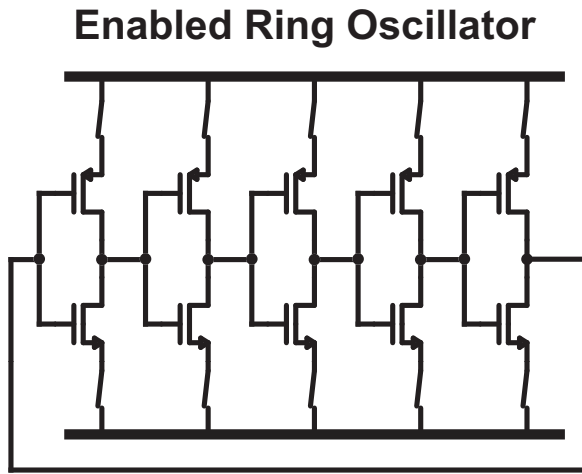Simple gated ring oscillator inverter-based core




(a)

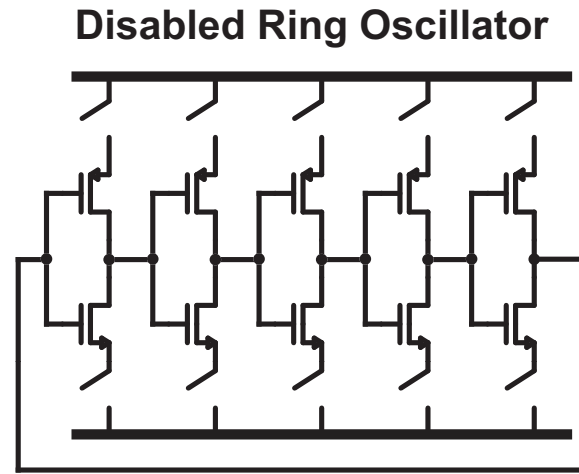


(b)

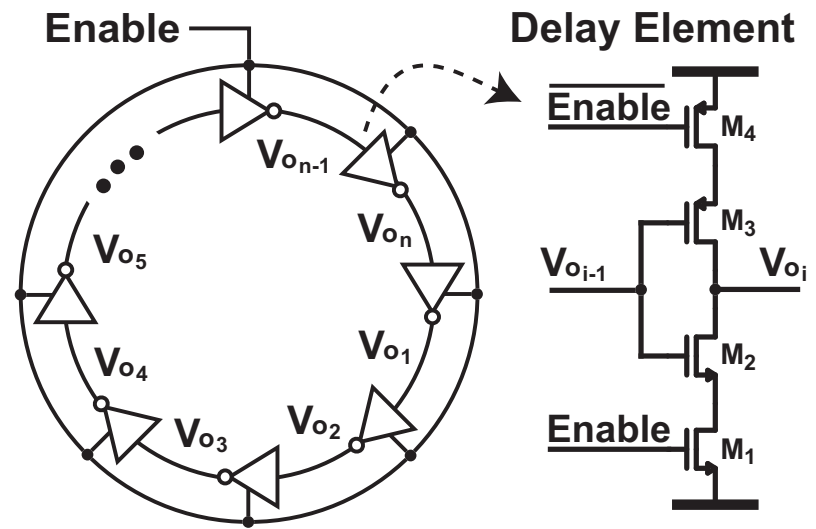
Gate the oscillator by switching the inverter cores to the power supply



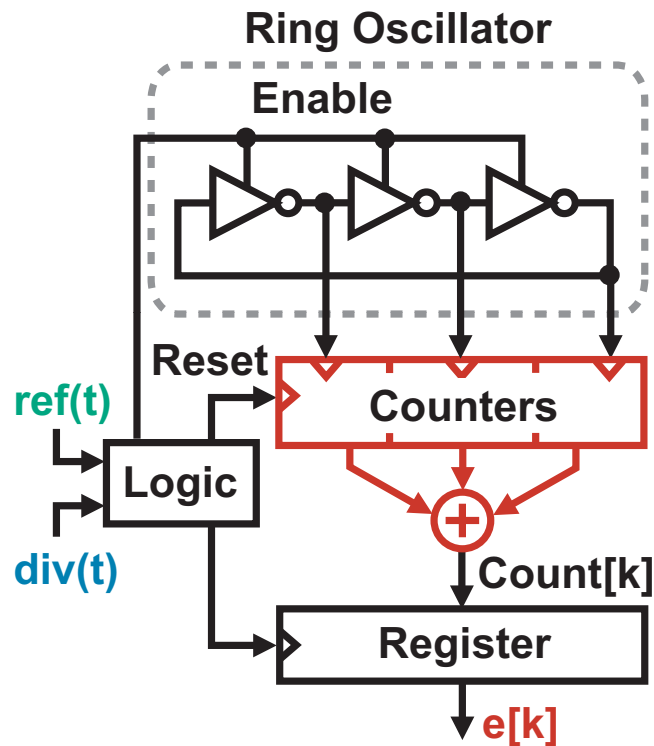Improve Resolution By Using All Oscillator Phases




Helal, Straayer, Wei,
Perrott VLSI 2007

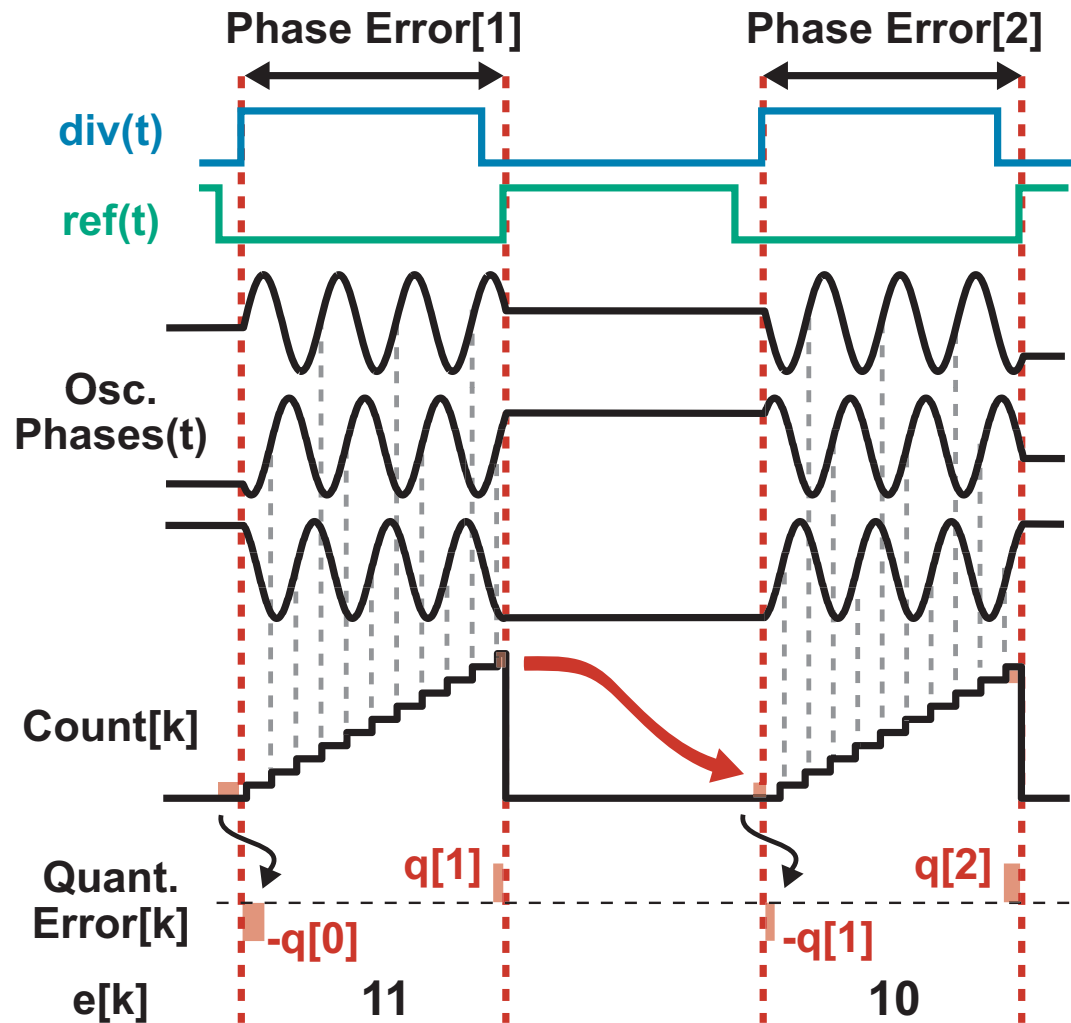


- Raw resolution is set by inverter delay
- Effective resolution is dramatically improved by averaging

GRO TDC Also Shapes Delay Mismatch

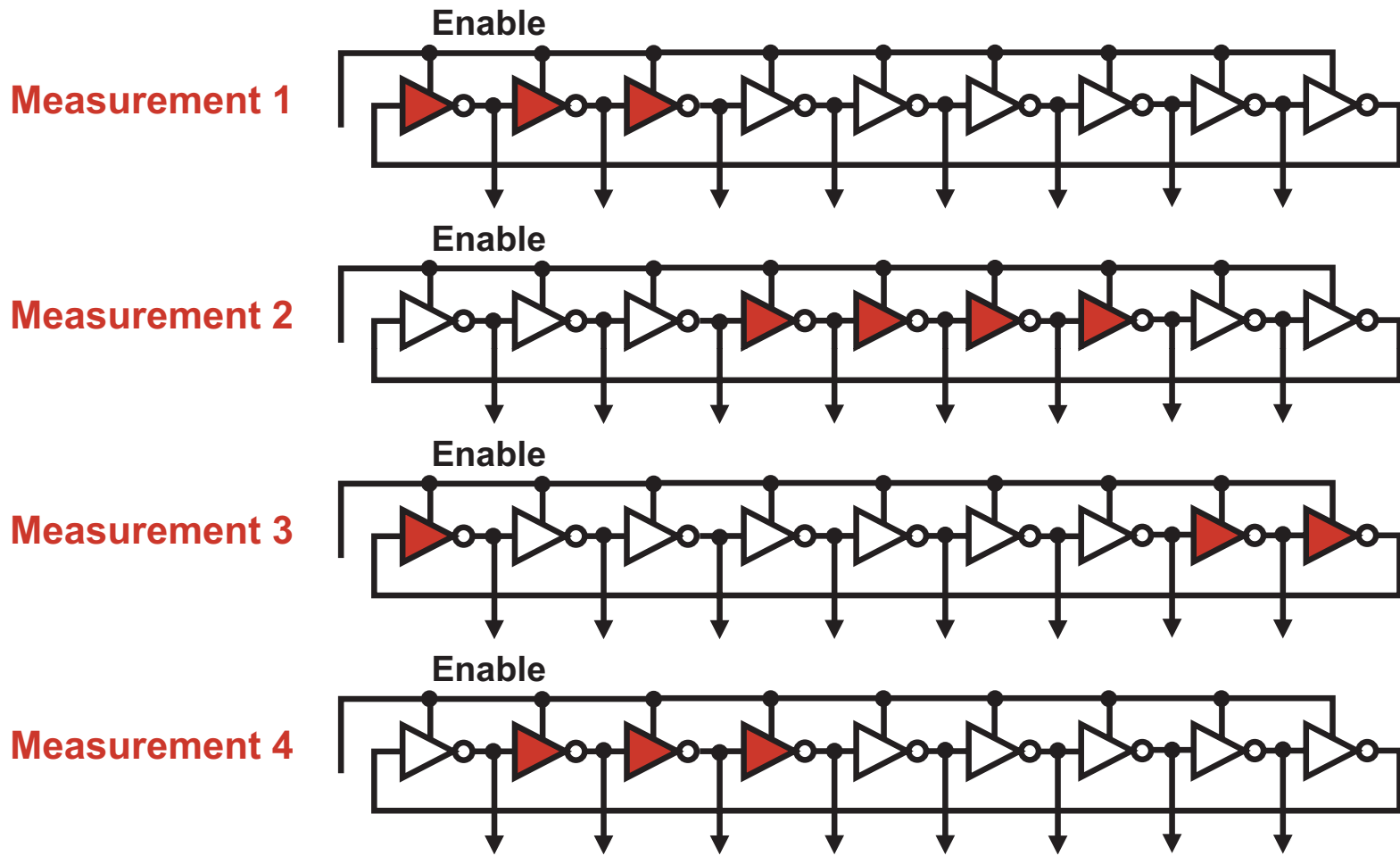


- Barrel shifting occurs through delay elements across different measurements
 - Mismatch between delay elements is first order shaped!


First Generation GRO Prototype

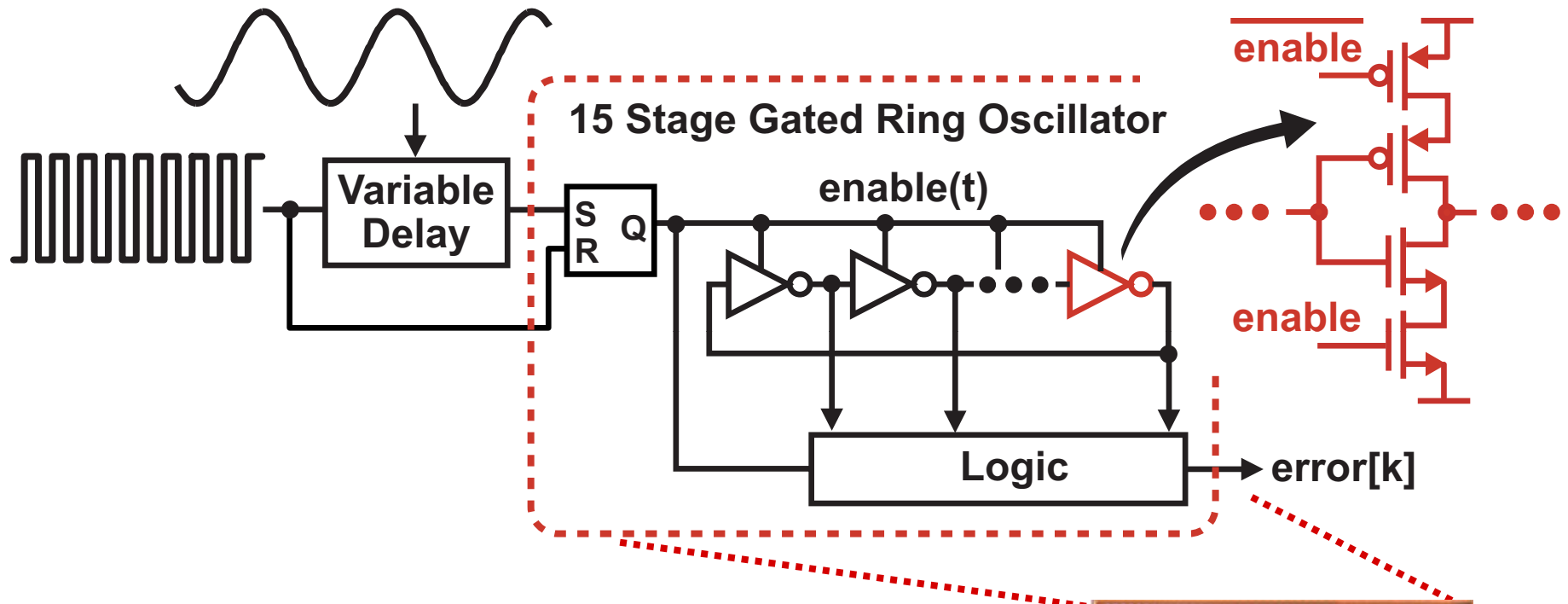

 - GRO implemented as a custom 0.13u CMOS IC
- External setup consists of signal source and variable delay
 - Test issue: variable delay is nonlinear




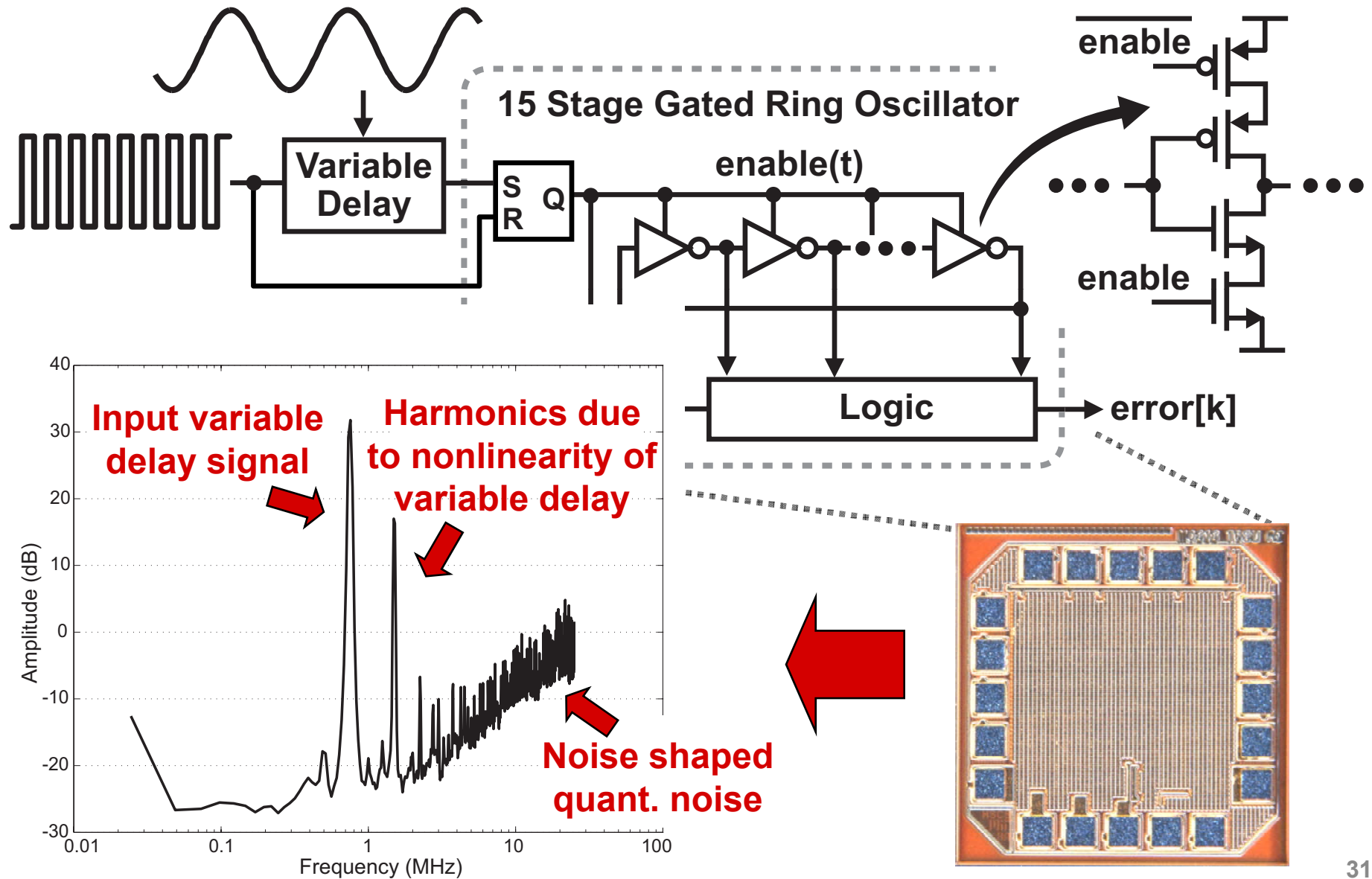Measured GRO Results Confirm Noise Shaping




Next Generation GRO: Multi-path oscillator concept

**Single Input
Single Output**

 


**Multiple Inputs
Single Output**

 


- Use multiple inputs for each delay element instead of one
- Allow each stage to optimally begin its transition based on information from the entire GRO phase state
- Key design issue is to ensure primary mode of oscillation

Multi-path inverter core

 


Lee, Kim, Lee
JSSC 1997

(a) Asymmetrically skewed inverter

 


Mohan, et. al.,
CICC 2005



(b) Multiple skewed inverters

 

(c) Unrestricted connections

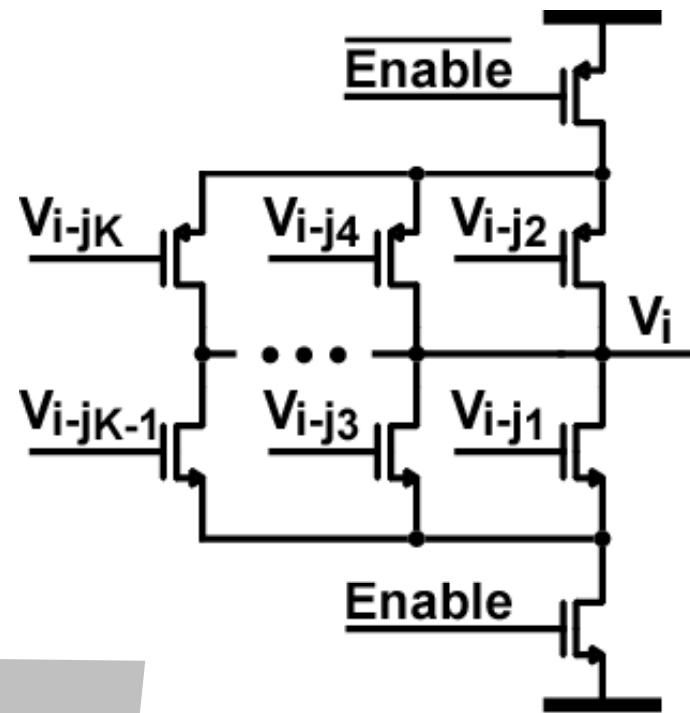

 
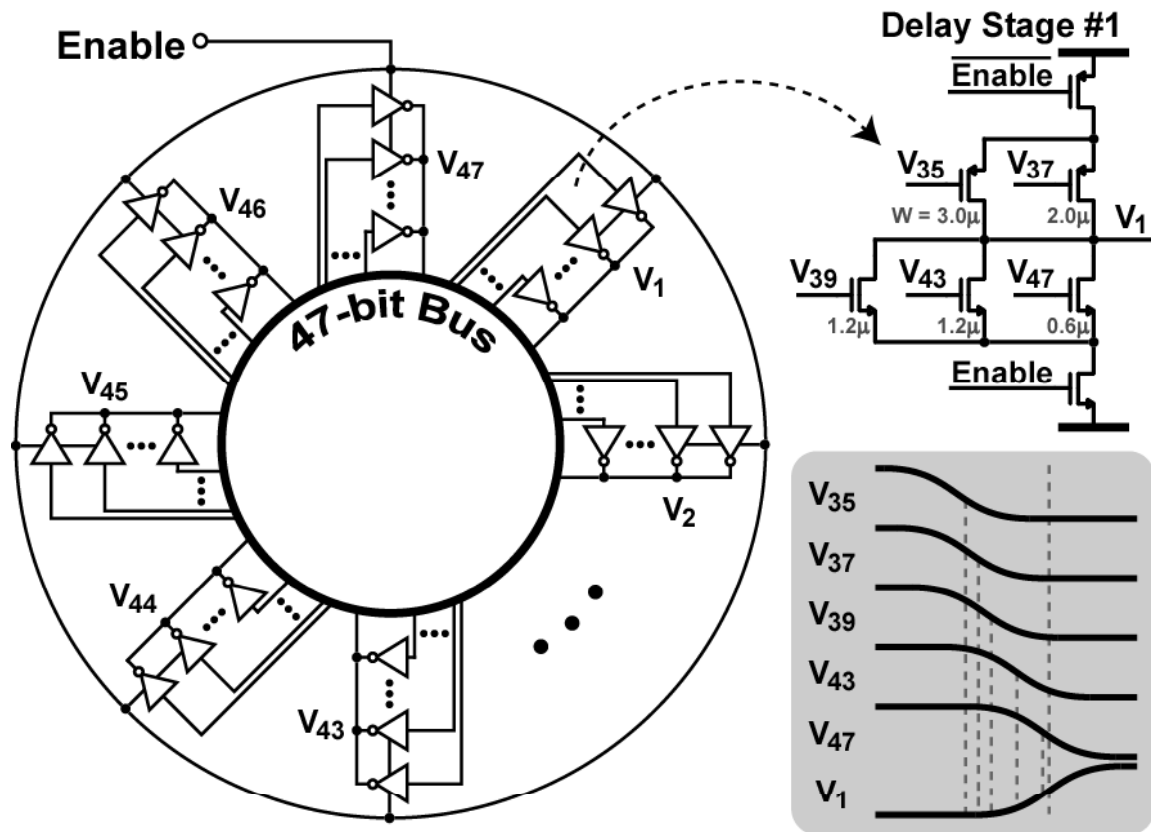
Proposed Multi-Path Gated Ring Oscillator TDC



Hsu, Straayer, Perrott
ISSCC 2008

- Oscillation frequency near 2GHz with 47 stages...
- Reduces effective delay per stage by a factor of 5-6!
- Represents a factor of 2-3 improvement compared to previous multi-path oscillators

 
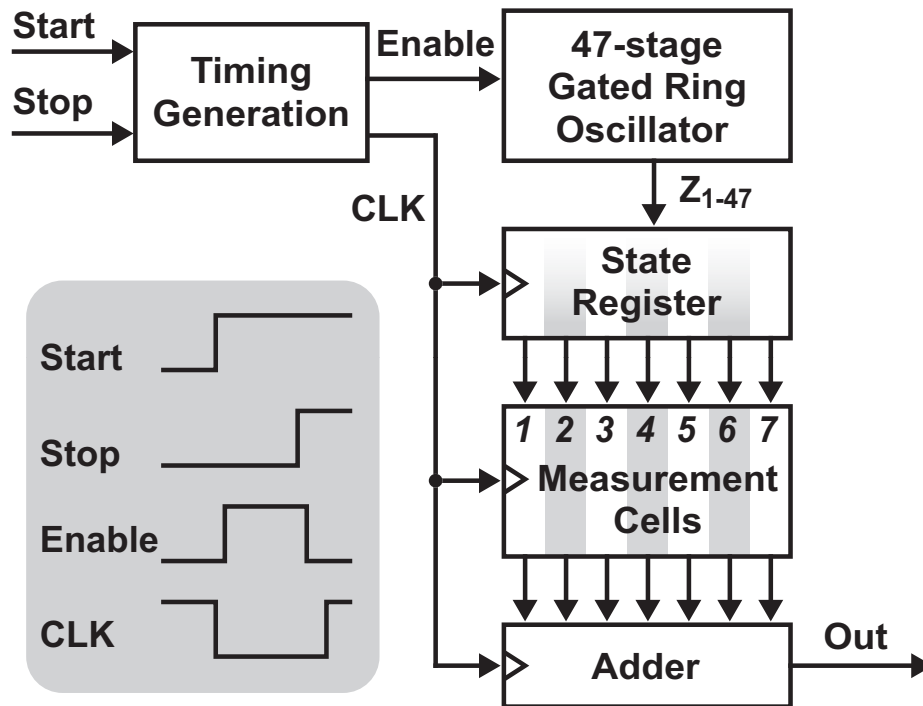
Prototype 0.13 μm CMOS Multi-Path GRO-TDC



Straayer, Perrott
VLSI 2008

- **Two implemented versions:**
 - 8-bit, 500Msps
 - 11-bit, 100Msps version
- **2-21mW power consumption depending on input duty cycle**


Measured noise-shaping of multi-path GRO

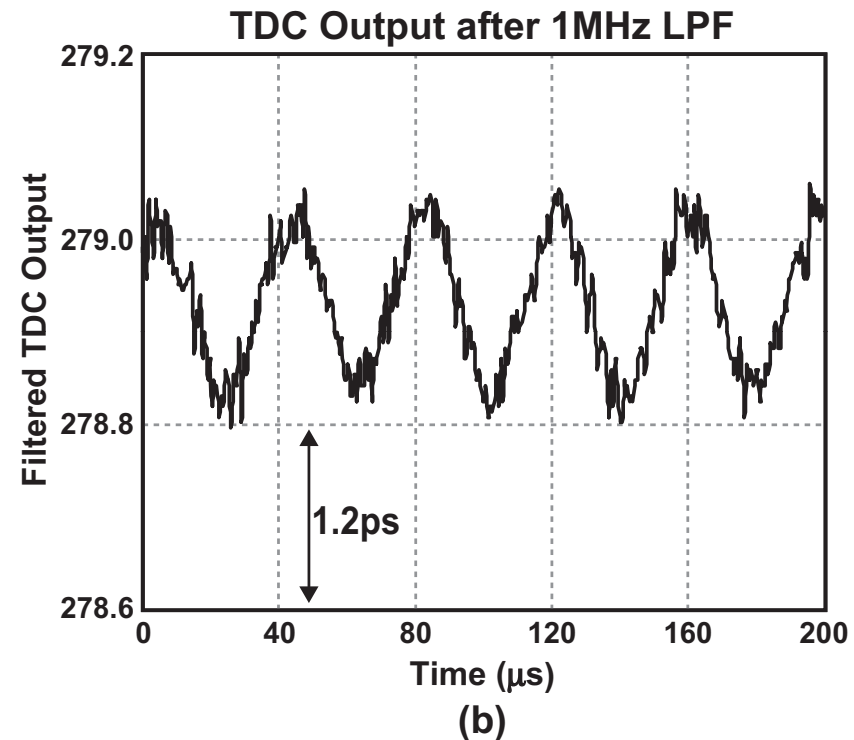 

- Data collected at 50Mps
- More than 20dB of noise-shaping benefit
- 80fs_{rms} integrated error from 2kHz-1MHz
- Floor primarily limited by 1/f noise (up to 0.5-1MHz)


***Can We Reduce Sigma-Delta
Quantization Noise Caused by Divider Dithering?***

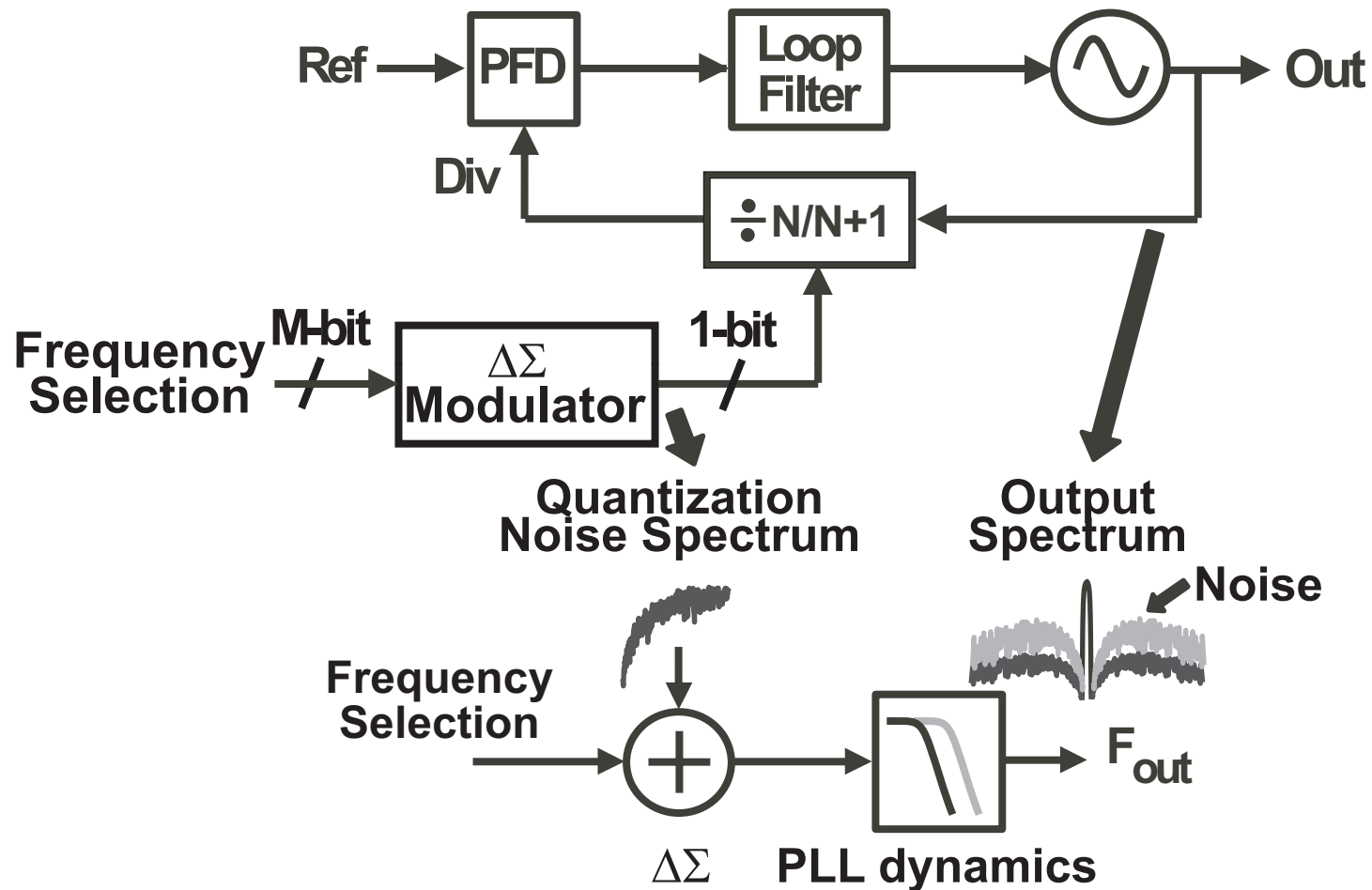The Nature of the Quantization Noise Problem



- Increasing PLL bandwidth increases impact of $\Delta\Sigma$ fractional-N noise
 - Cancellation offers a way out!

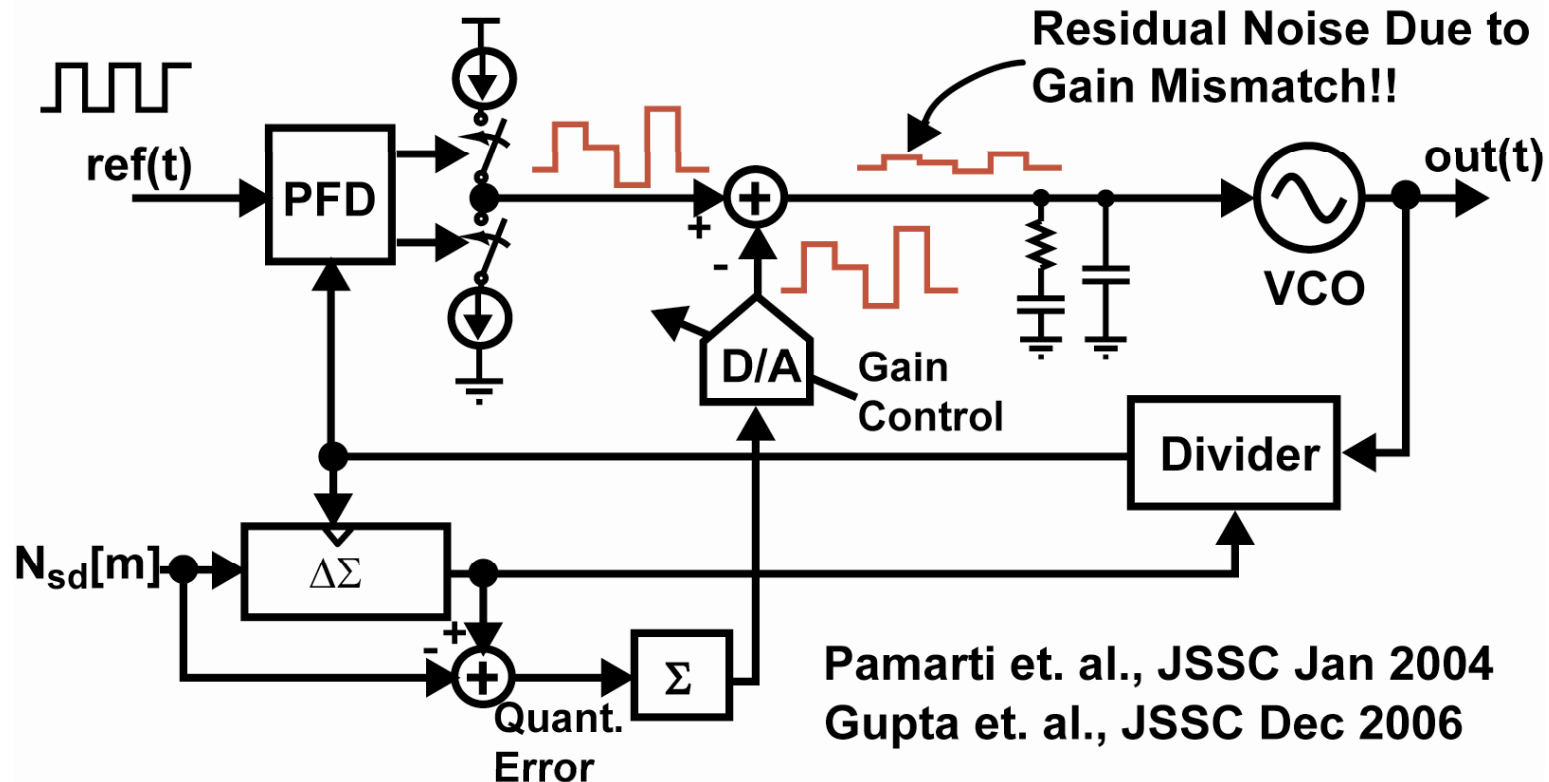
Previous Analog Quantization Noise Cancellation



- Phase error due to $\Delta\Sigma$ is predicted by accumulating $\Delta\Sigma$ quantization error
- Gain matching between PFD and D/A must be precise


Matching in *analog* domain limits performance

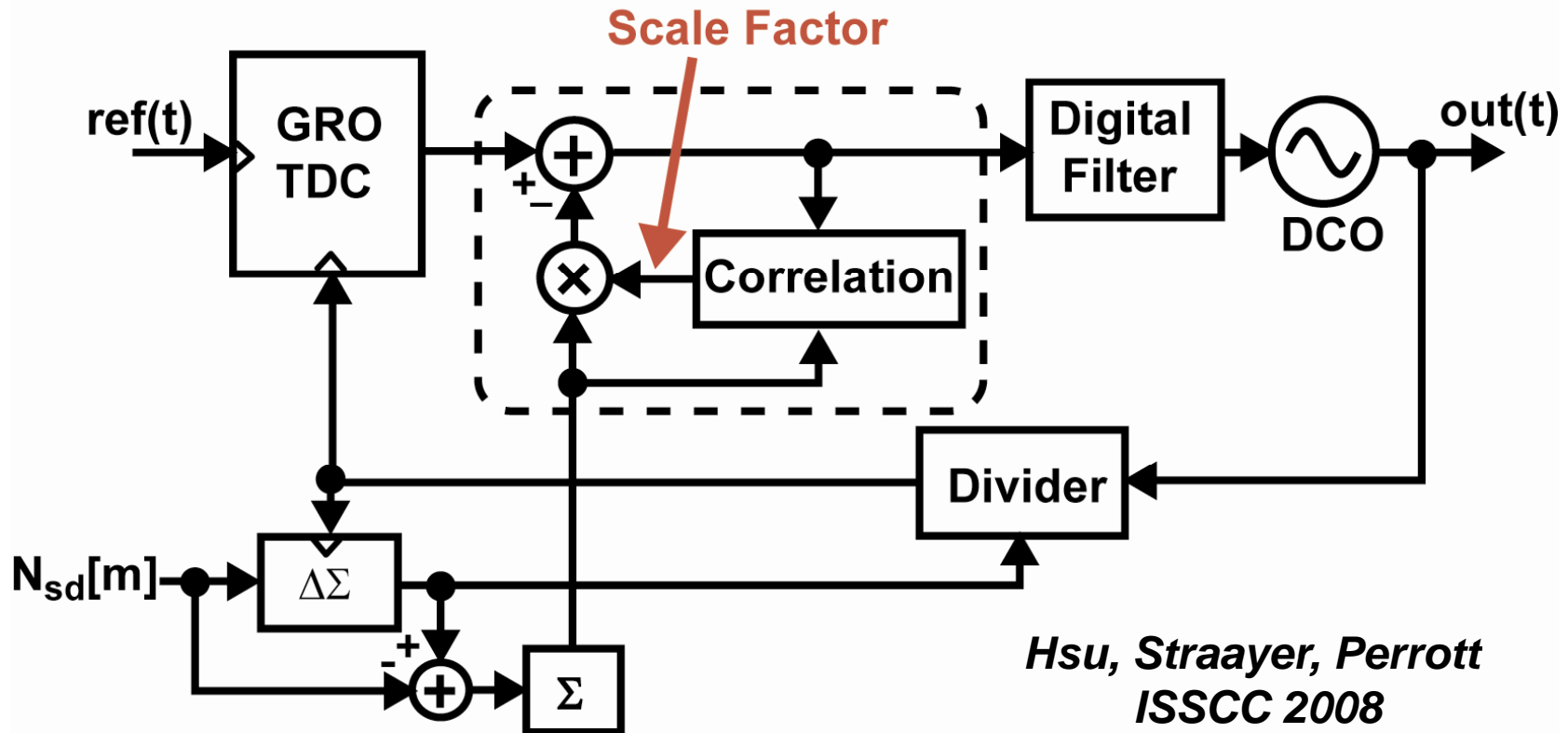Proposed All-digital Quantization Noise Cancellation




- Scale factor determined by simple digital correlation
- Analog non-idealities such as DC offset are completely eliminated

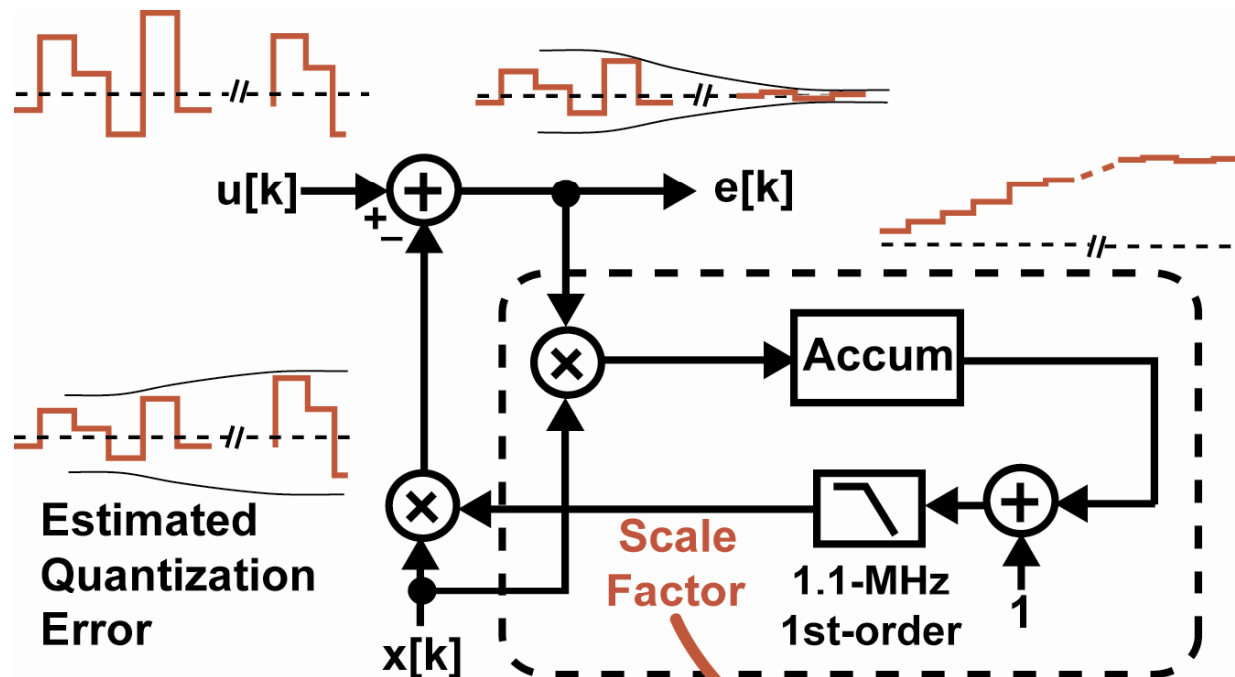
Details of Proposed Quantization Noise Cancellation



 - Correlator out is accumulated and filtered to achieve scale factor
 - Settling time chosen to be around 10 us
- See *analog* version of this technique in *Swaminathan et.al., ISSCC 2007*




Proposed Digital Wide BW Synthesizer

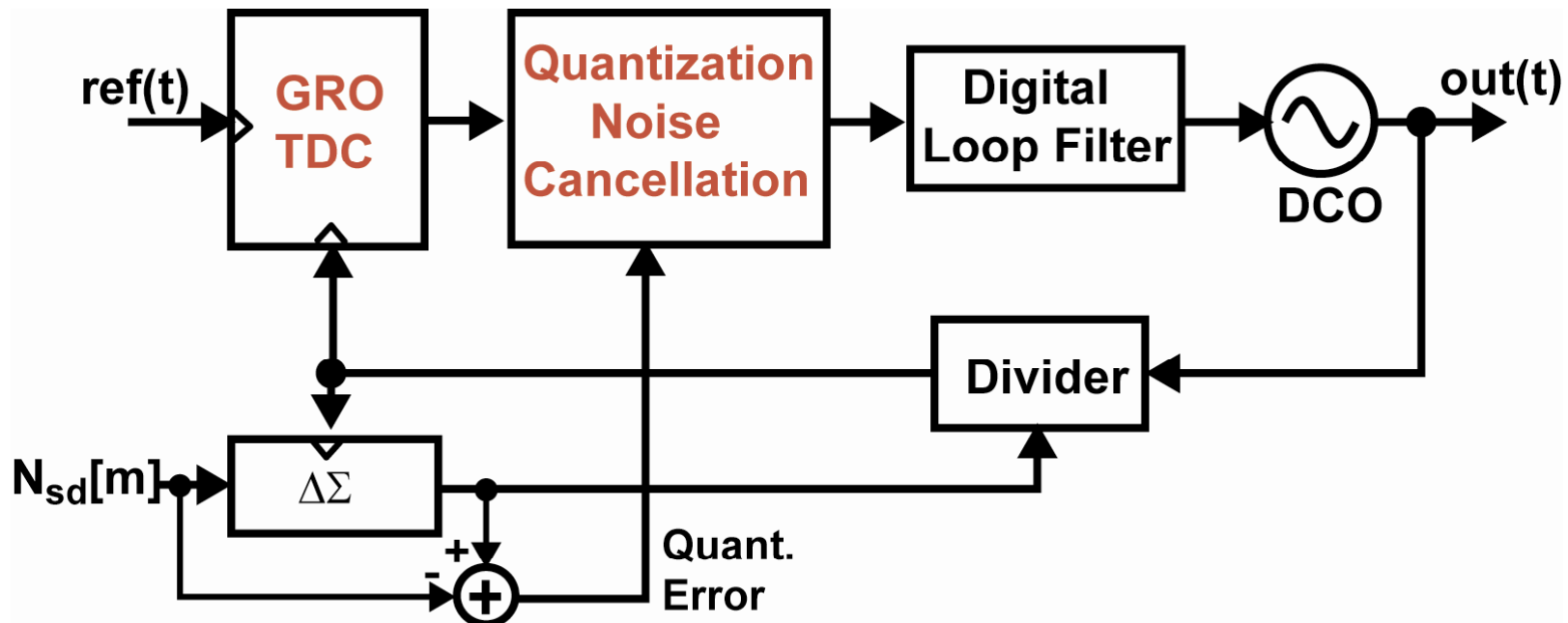


- **Gated-ring-oscillator (GRO) TDC** achieves low in-band noise
- **All-digital quantization noise cancellation** achieves low out-of-band noise
- **Design goals:**
 - 3.6-GHz carrier, 500-kHz bandwidth
 - <-100dBc/Hz in-band, <-150 dBc/Hz at 20 MHz offset

Overall Synthesizer Architecture

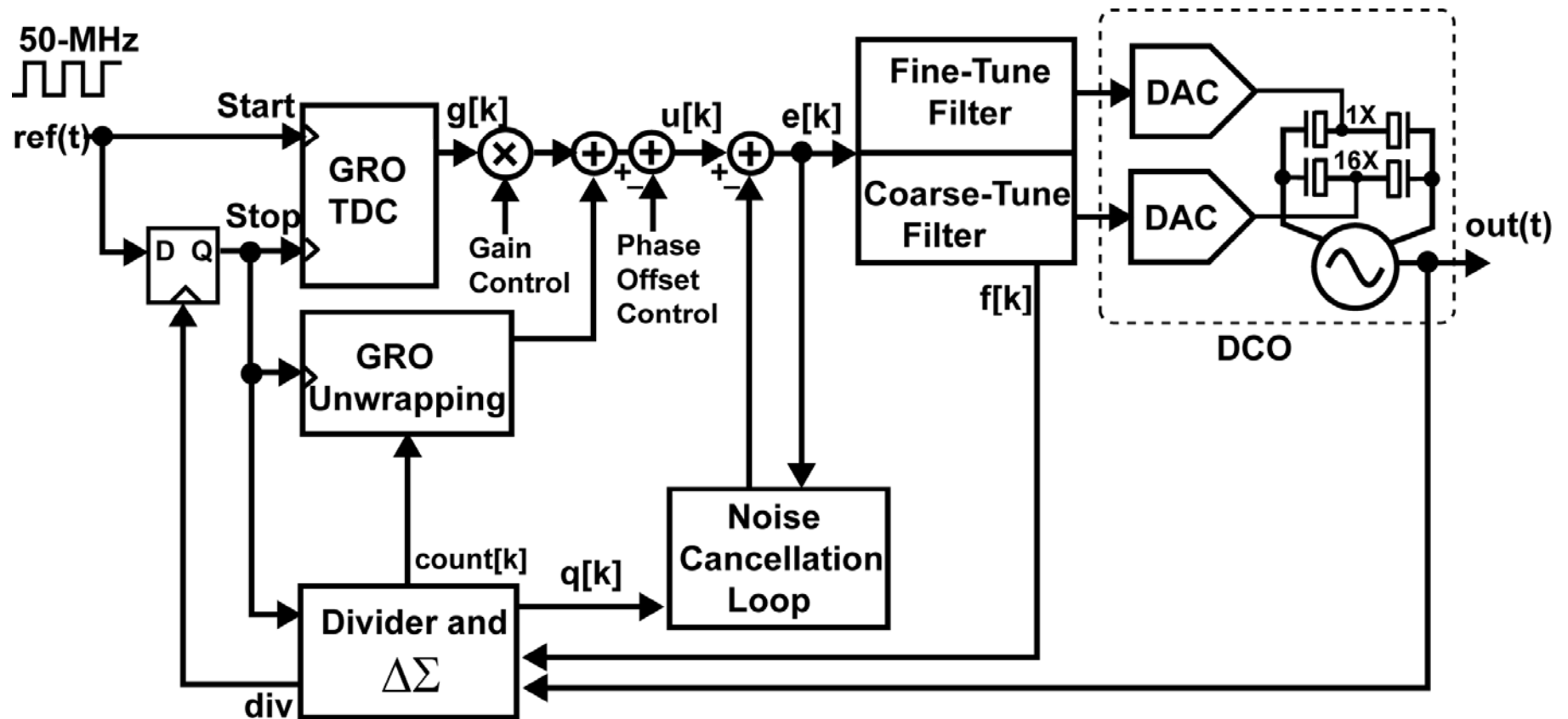

Note: Detailed behavioral simulation model available at <http://www.cppsim.com>


Dual-Port LC VCO

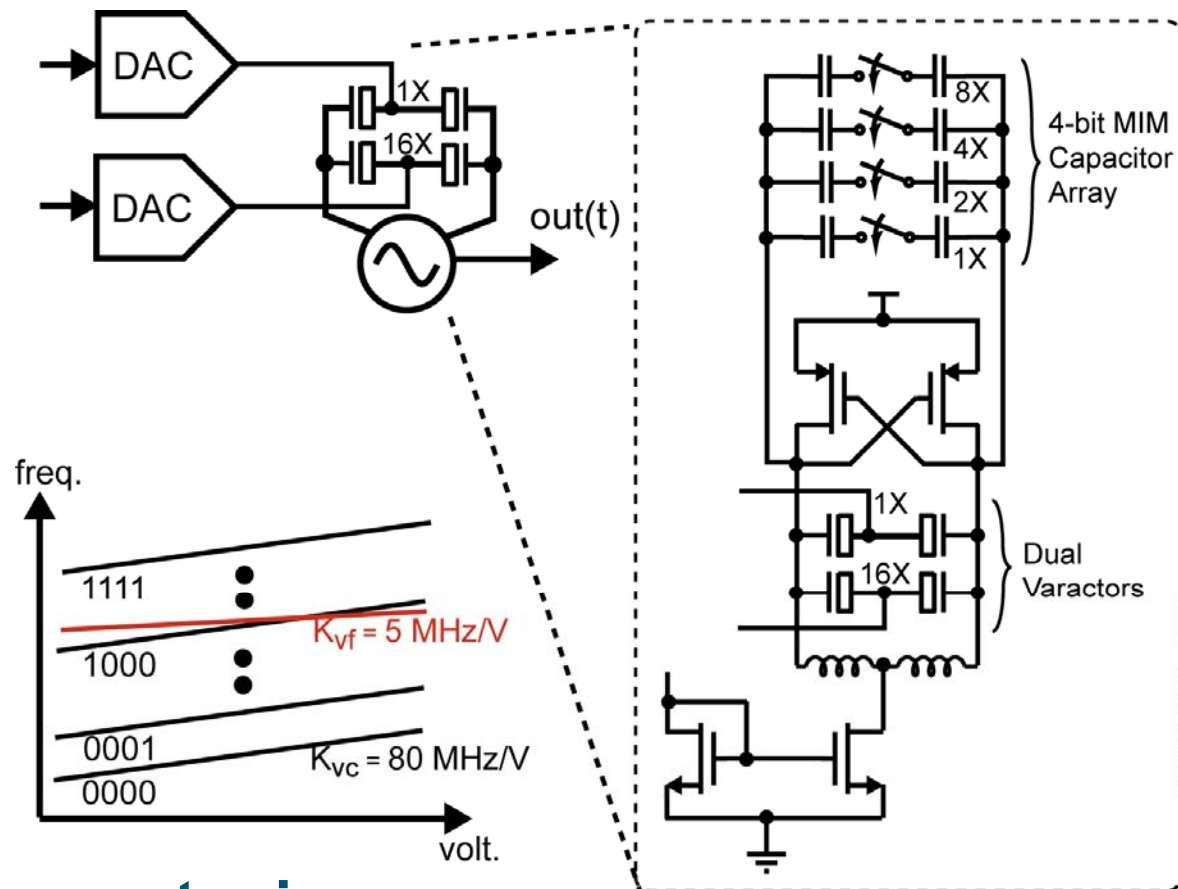

■ Frequency tuning:

- Use a small 1X varactor to minimize noise sensitivity
- Use another 16X varactor to provide moderate range
- Use a four-bit capacitor array to achieve 3.3-4.1 GHz range

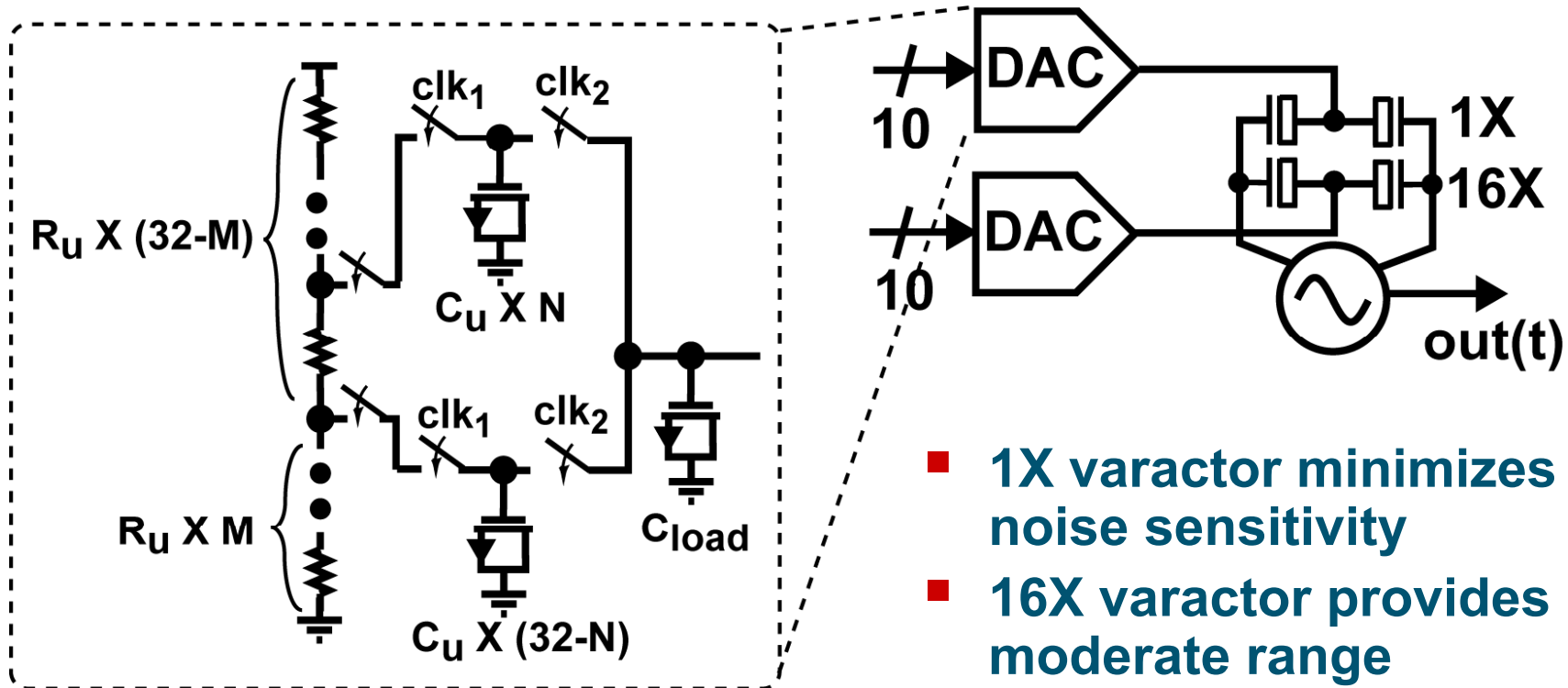Digitally-Controlled Oscillator with Passive DAC




- **Goals of 10-bit DAC**

- Monotonic
- Minimal active circuitry and no transistor bias currents
- Full-supply output range


- **1X varactor minimizes noise sensitivity**
- **16X varactor provides moderate range**
- **A four-bit capacitor array covers 3.3-4.1GHz**

Operation of 10-bit Passive DAC (Step 1)

 


- 5-bit resistor ladder; 5-bit switch-capacitor array
- Step 1: *Capacitors Charged*
 - Resistor ladder forms $V_L = M/32 \cdot V_{DD}$ and $V_H = (M+1)/32 \cdot V_{DD}$, where M ranges from 0 to 31
 - N unit capacitors charged to V_H , and $(32-N)$ unit capacitors charged to V_L

Operation of 10-bit Passive DAC (Step 2)

 


- **Step 2: Disconnect Capacitors from Resistors, Then Connect Together**
 - Achieves DAC output with first-order filtering
 - Bandwidth = $32 \cdot C_u / (2\pi \cdot C_{load}) \cdot 50\text{MHz}$
 - Determined by capacitor ratio
 - Easily changed by using different C_{load}

Now Let's Examine Divider ...

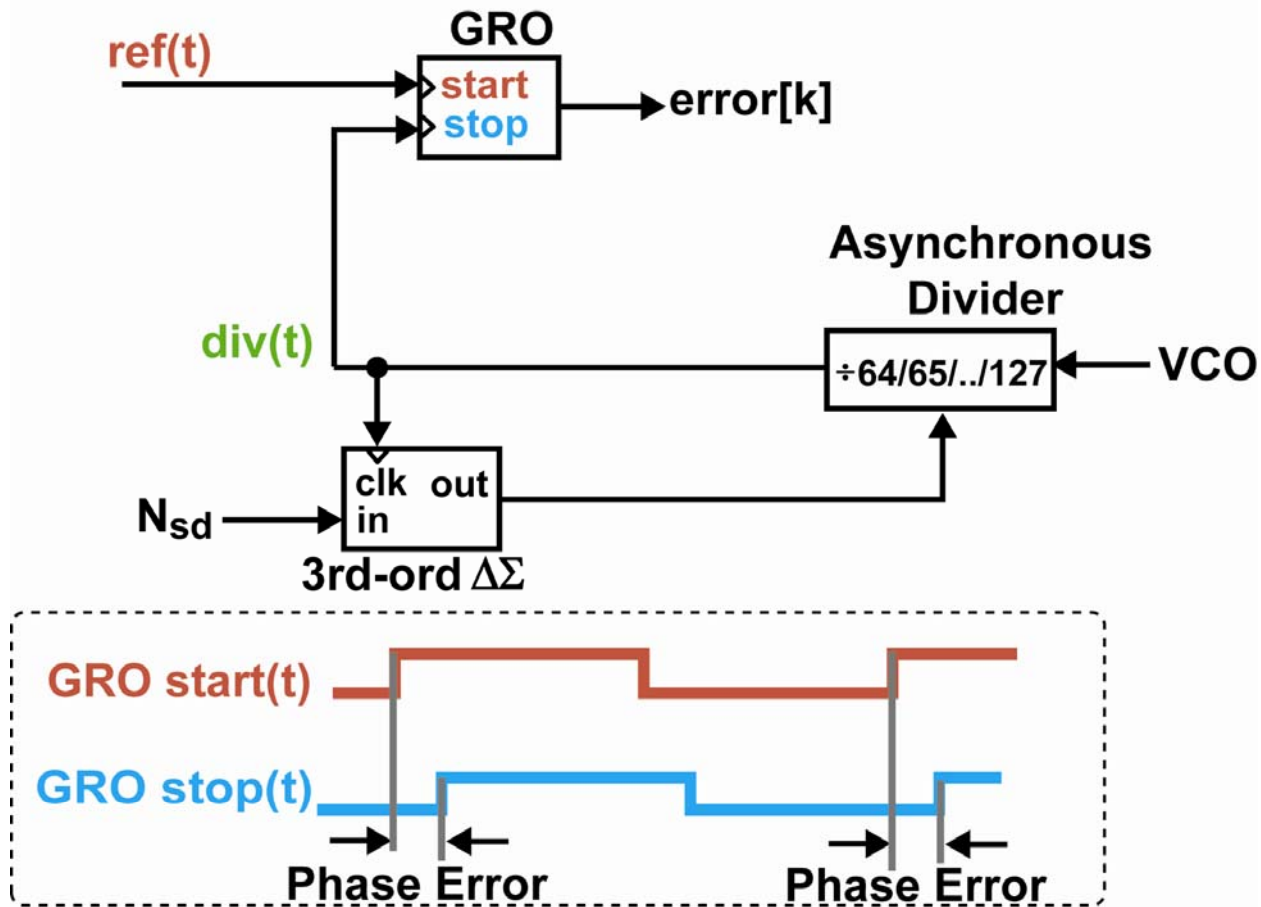


- **Issues:**
 - GRO range must span entire reference period during initial lock-in

Proposed Divider Structure

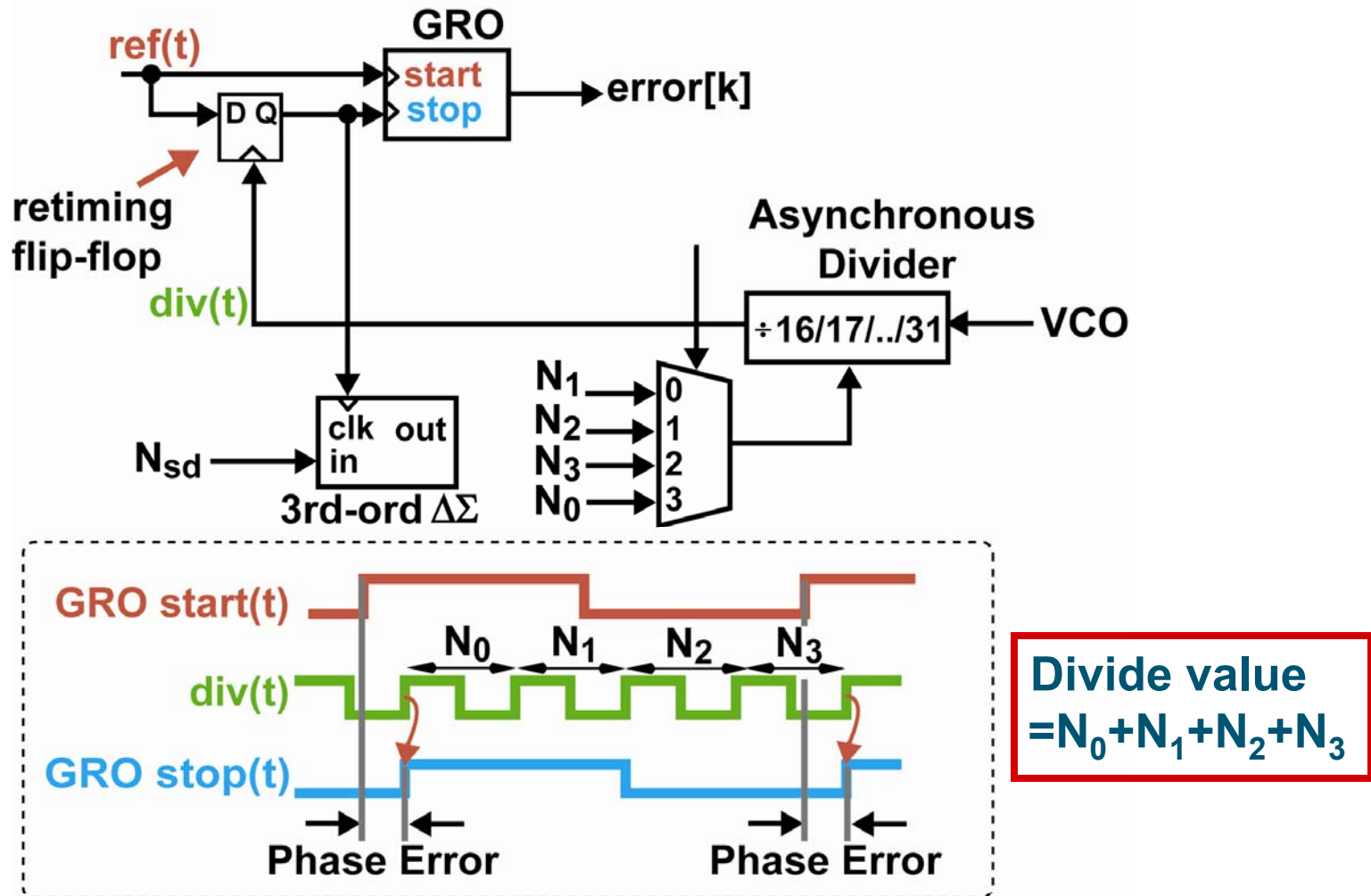


- Resample reference with 4x division frequency
 - Lowers GRO range to one fourth of the reference period

Proposed Divider Structure (cont'd)

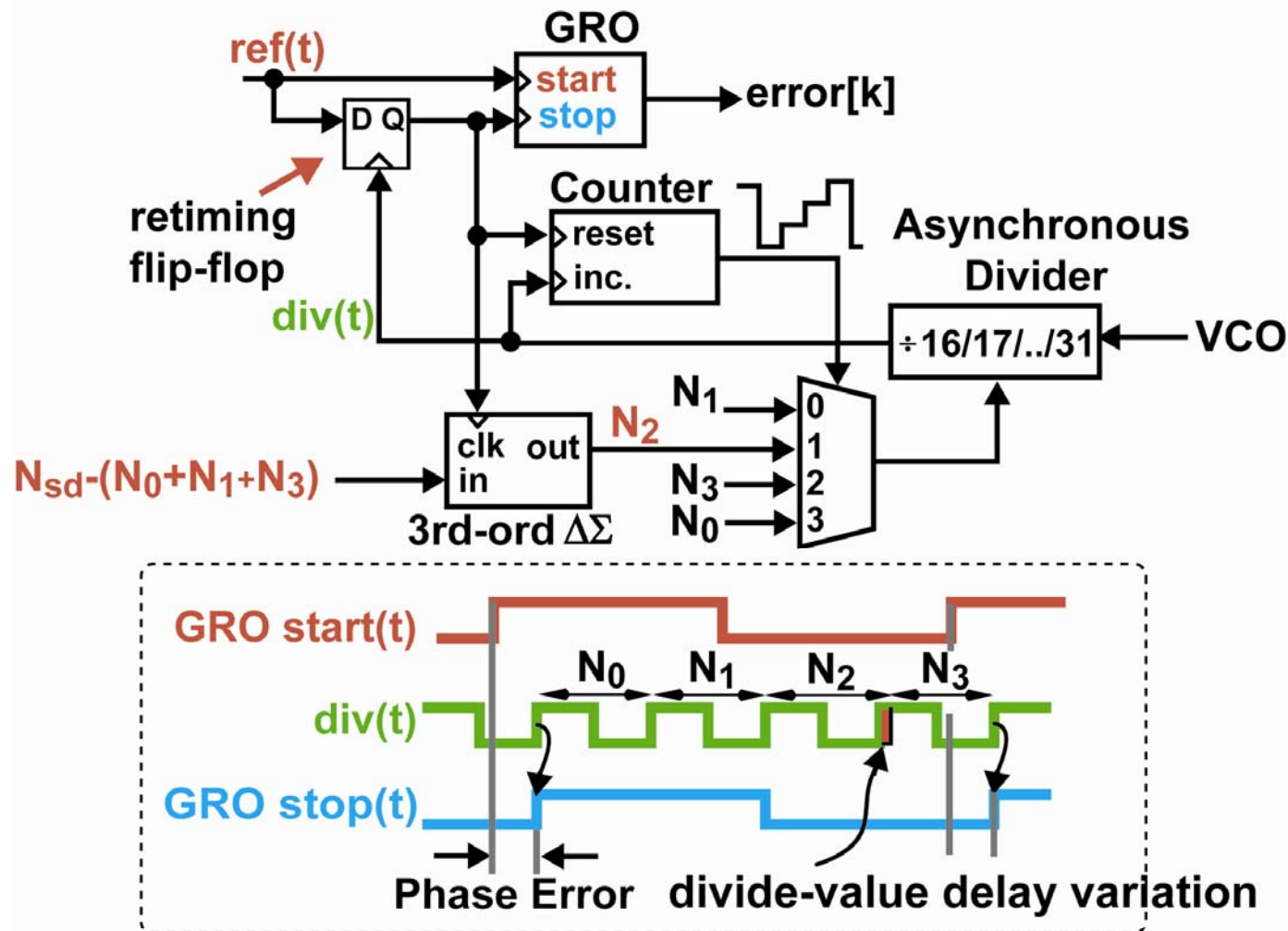


- Place $\Delta\Sigma$ dithered edge away from GRO edge
 - Prevents extra jitter due to divide-value dependent delay

Dual-Path Loop Filter

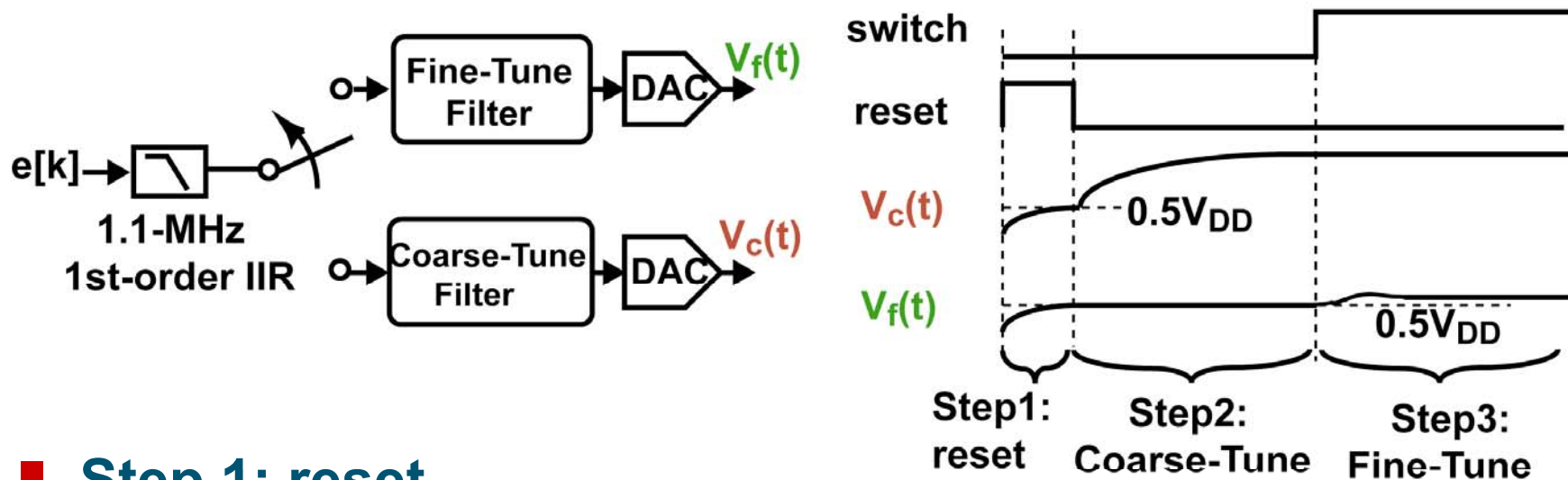


- **Step 1: reset**
- **Step 2: frequency acquisition**
 - $V_c(t)$ varies
 - $V_f(t)$ is held at midpoint
- **Step 3: steady-state lock conditions**
 - $V_c(t)$ is frozen to take quantization noise away
 - $\Delta\Sigma$ quantization noise cancellation is enabled

Fine-Path Loop Filter

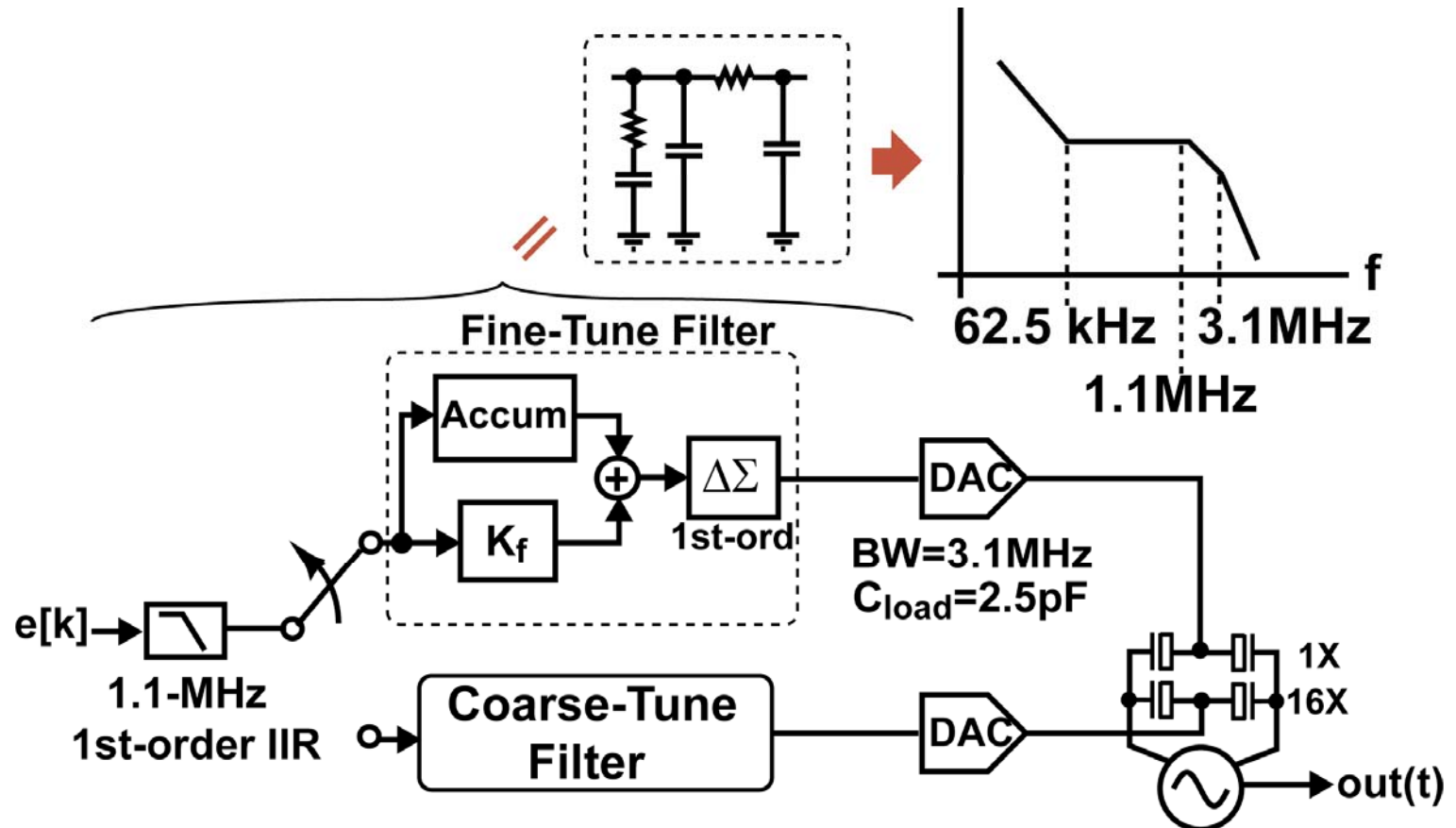



- Equivalent to an analog lead-lag filter
 - Set zero (62.5kHz) and first pole (1.1MHz) digitally
 - Set second pole (3.1MHz) by capacitor ratio
- First-order $\Delta\Sigma$ reduces in-band quantization noise

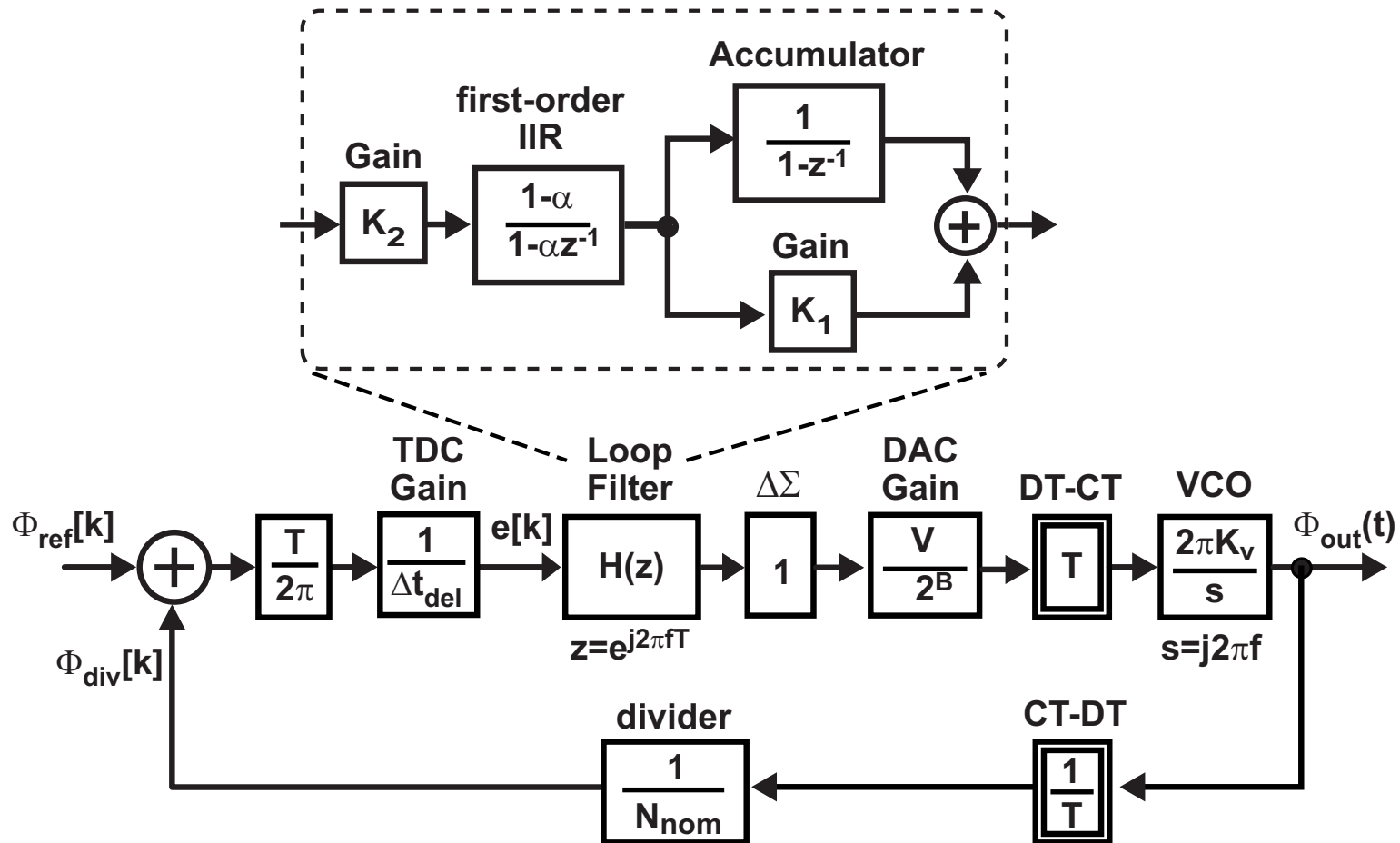Linearized Model of PLL Under Fine-Tune Operation




- Standard lead-lag filter topology but implemented in digital domain
 - Consists of accumulator plus feedforward path

 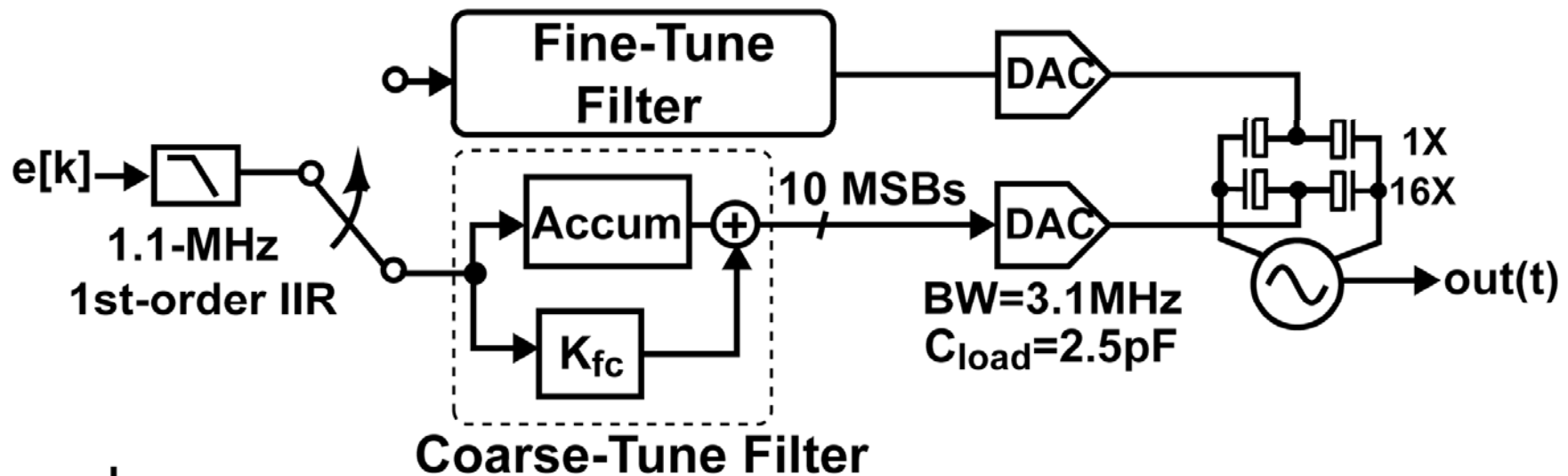Same Technique Poses Problems for Coarse-Tune




- DAC thermal noise impacts performance due to the higher coarse VCO gain
 - Can we somehow lower the DAC bandwidth?

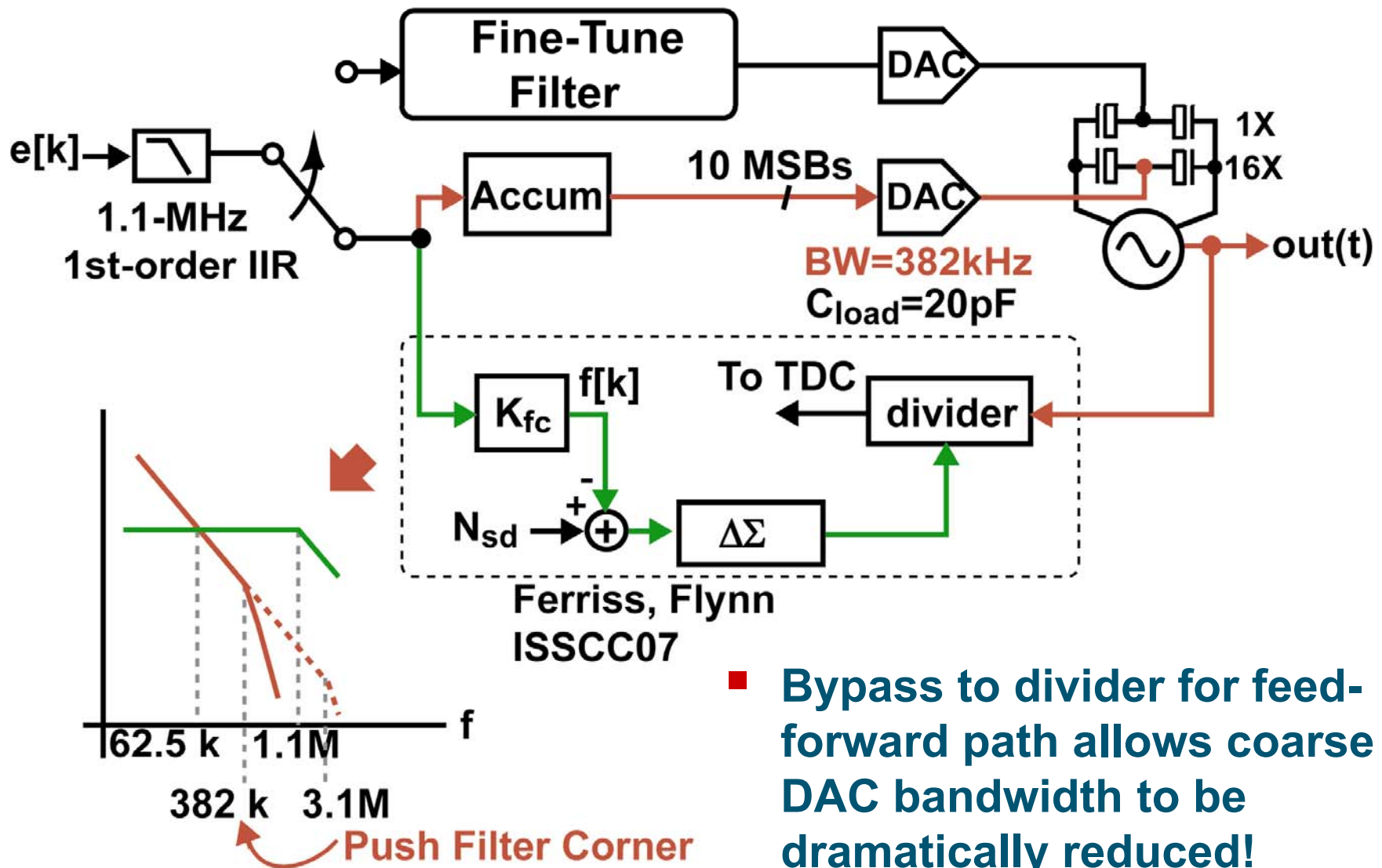Fix: Leverage the Divider as a Signal Path




- Bypass to divider for feed-forward path allows coarse DAC bandwidth to be dramatically reduced!

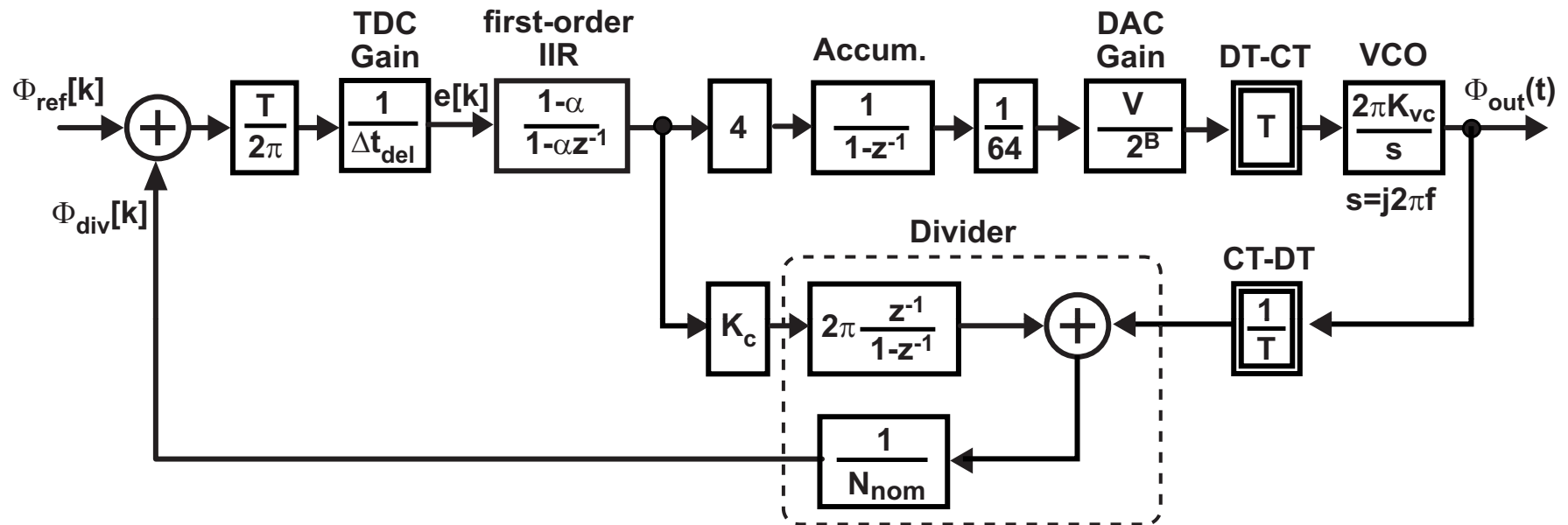Linearized Model of PLL Under Coarse-Tune Operation



- **Routing of signal path into Sigma-Delta controlling the divider yields a feedforward path**
 - Adds to accumulator path as both signals pass back through the divider
 - Allows reduction of coarse DAC bandwidth
 - Noise impact of coarse DAC on VCO is substantially lowered

Die Photo

 


- 0.13- μm CMOS
- Active area: 0.95 mm²
- Chip area: 1.96 mm²
- V_{DD} : 1.5V
- Current:
 - 26mA (Core)
 - 7mA (VCO output buffer at 1.1V)

GRO-TDC:


- 2.3mA
- 157X252 μm^2

Power Distribution of Prototype IC

 


- Notice GRO and digital quantization noise cancellation have only minor impact on power (and area)

Measured Phase Noise at 3.67GHz

 


- Suppresses quantization noise by more than 15 dB
- Achieves 204 fs (0.27 degree) integrated noise (jitter)
- Reference spur: -65dBc

Calculation of Phase Noise Components

 

- See wideband digital synthesizer tutorial available at <http://www.cppsim.com>

Measured Worst Spurs over Fifty Channels

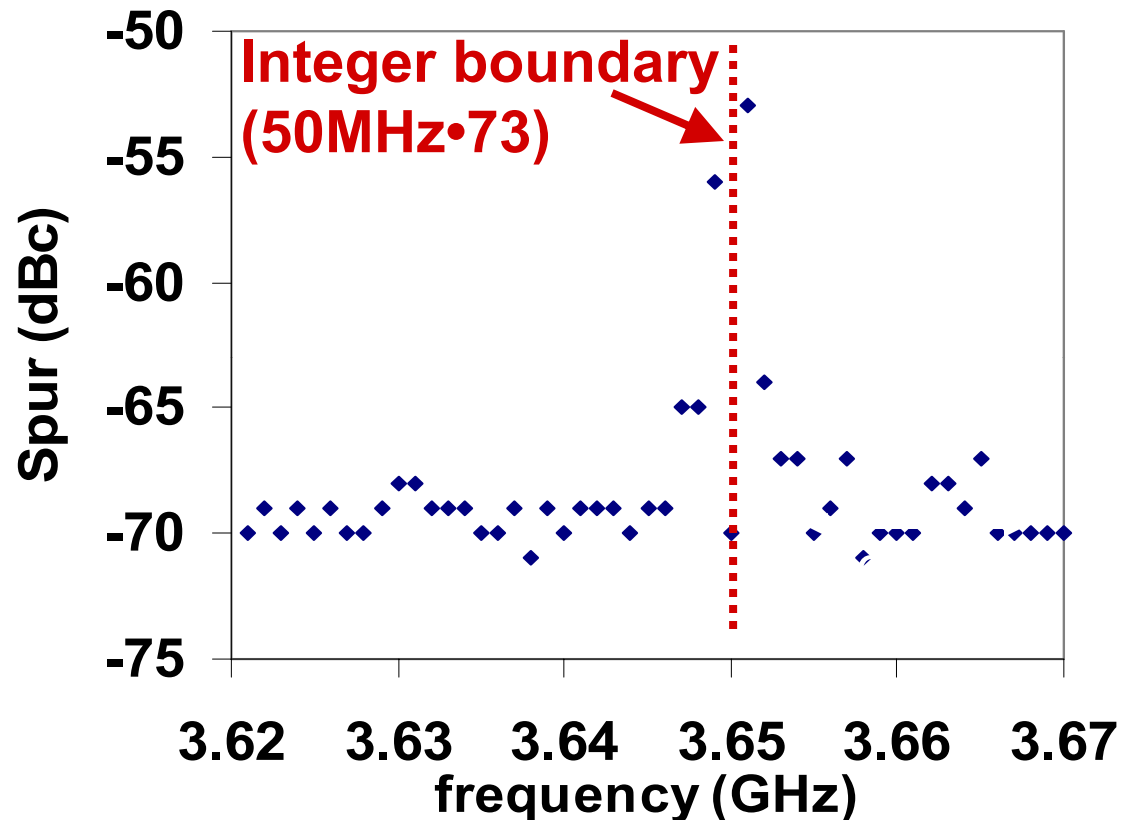

- Tested from 3.620 GHz to 3.670 GHz at intervals of 1 MHz
 - Worst spurs observed close to integer-N boundary (multiples of 50 MHz)
- -42dBc worst spur observed at 400kHz offset from boundary

Conclusions

- Digital Phase-Locked Loops look extremely promising for future applications
 - Very amenable to future CMOS processes
 - Excellent performance can be achieved
- A low-noise, wide-bandwidth digital $\Delta\Sigma$ fractional-N frequency synthesizer is achieved with
 - High performance *noise-shaping* GRO TDC
 - Quantization noise cancellation in *digital* domain
- Key result: < 250 fs integrated noise with 500 kHz bandwidth

Innovation of future digital PLLs will involve joint circuit/algorithm development