



POWER – PERFORMANCE OPTIMIZATION METHODS FOR DIGITAL CIRCUITS

Radu Zlatanovici



zradu@eecs.berkeley.edu

<http://www.eecs.berkeley.edu/~zradu>

Department of Electrical Engineering and Computer Sciences
University of California, Berkeley


Power and Performance with Scaling

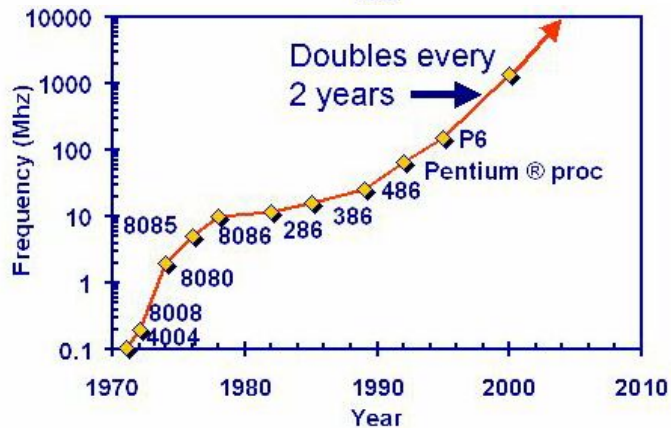 - ▶ If we continue doing business as usual, both dynamic and leakage power will be a problem...



From S. Borkar, Intel

...chips are getting hot...

 


...and phones leaky!



- Need to deliver maximum performance under power constraints

A Common Problem

 

- › Need to reduce power by 30%, while willing to give up 3% of performance
- › What to do:
 - › Decrease supply?
 - › Increase thresholds?
 - › Downsize?
 - › Downsize latches or logic?
 - › Use dual supplies?
 - › Re-pipeline?
 - › Parallelize?


Outline



- Design as a power – performance optimization problem
- Fundamentals of circuit optimization
- Design examples
- Dealing with variations
- Conclusions


- **Collaborative effort:**
 - Students: R. Zlatanovici, D. Markovic, L.-T. Pang, J. Garrett, S. Kao
 - Faculty: B. Nikolic, R. Brodersen

Power – Performance Optimization

 


OPTIMAL POWER – PERFORMANCE TRADEOFF CURVE

Power Limited Operation

 


**Achieve the highest performance
under the power cap**

Power Limited Operation

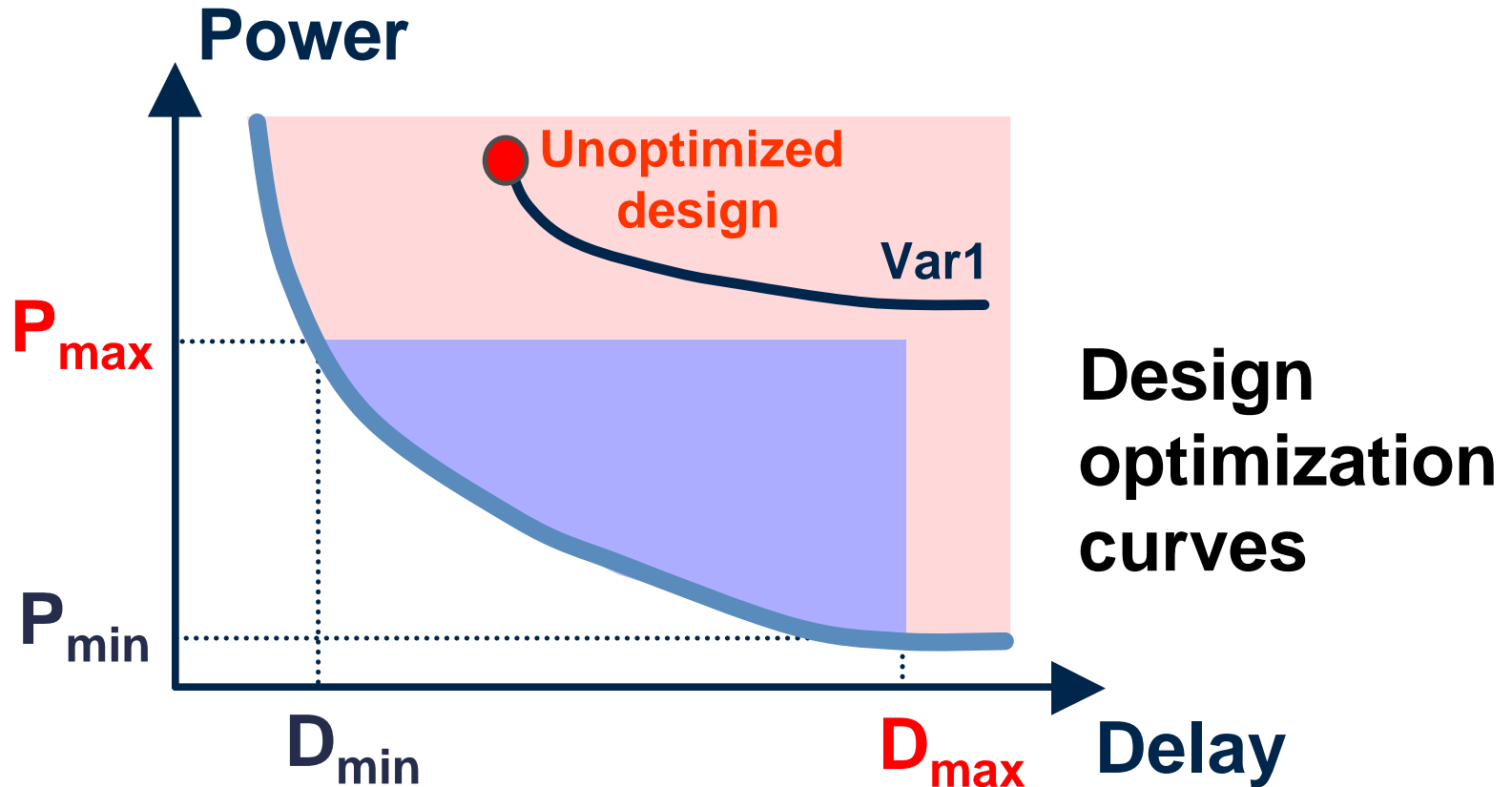


**Achieve the highest performance
under the power cap**

Power Limited Operation

 


**Achieve the highest performance
under the power cap**

Power Limited Operation

 

How far away are we from the optimal solution?


Power Limited Operation

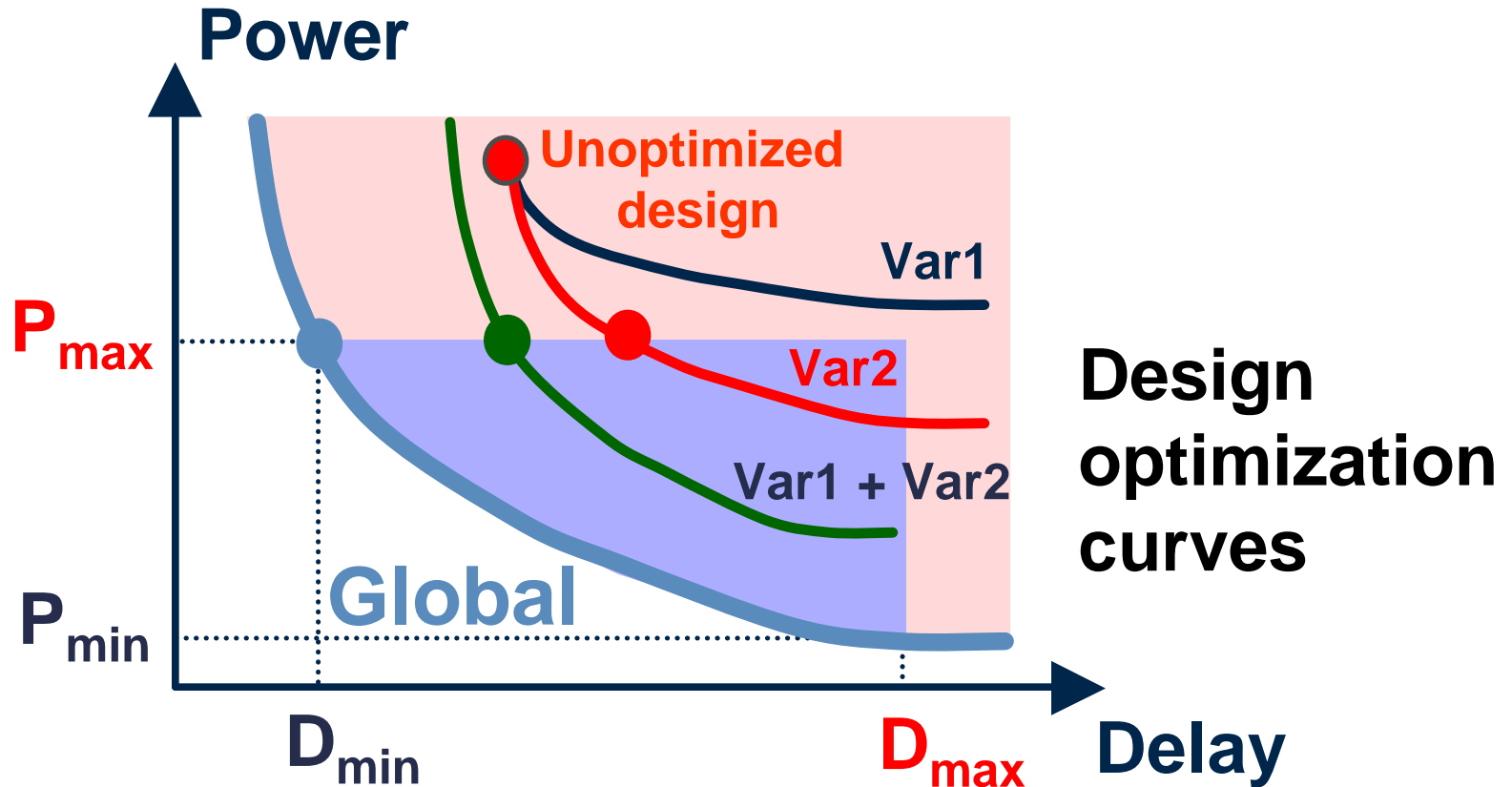

Global optimum – best performance


Design Optimization

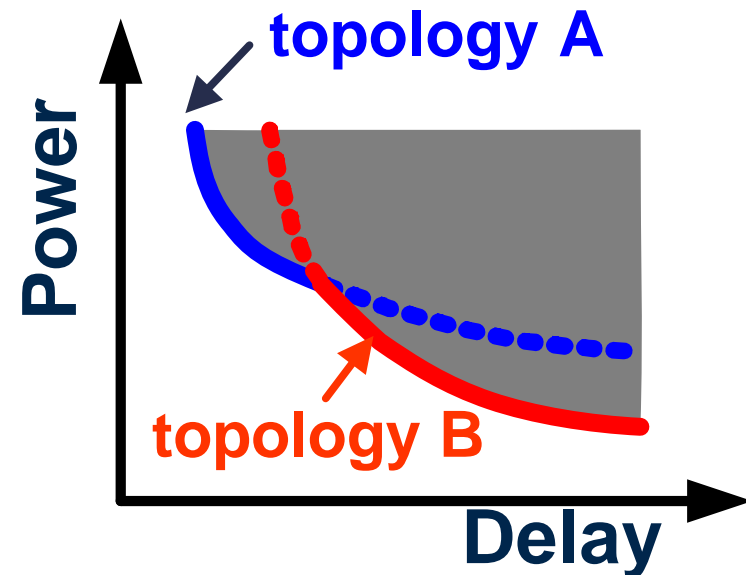- ▶ There are many sets of parameters to adjust:
 - ▶ Circuit
(sizing, supply, threshold)
 - ▶ Logic style
(domino, static, pass-gate, ...)
 - ▶ Block topology
(adder: CLA, CSA, RCA,...)
 - ▶ Micro-architecture
(parallel, pipelined)



Design Optimization

 - ▶ There are many sets of parameters to adjust:
 - ▶ Circuit
(sizing, supply, threshold)
 - ▶ Logic style
(domino, static, pass-gate, ...)
 - ▶ Block topology
(adder: CLA, CSA, RCA, ...)
 - ▶ Micro-architecture
(parallel, pipelined)



Globally optimal boundary curve:
pieces of E-D curves for
different topologies

Outline



- ▶ Design as a power – performance optimization problem
- ▶ **Fundamentals of circuit optimization**
- ▶ Design examples
- ▶ Dealing with variations
- ▶ Conclusions

Optimization Problem

$$\min_{x \in R^n} f(x)$$

subject to


$$g_i(x) \leq 0 \quad i = 1..m$$

$$h_j(x) = 0 \quad j = 1..p$$


- Very difficult in the general case
- Optimality not guaranteed

Convex Optimization

 - f, g_i – convex, h_j – linear
- Key property: every local minimum is a **global** minimum
- Optimality **guaranteed**



Circuit Optimization

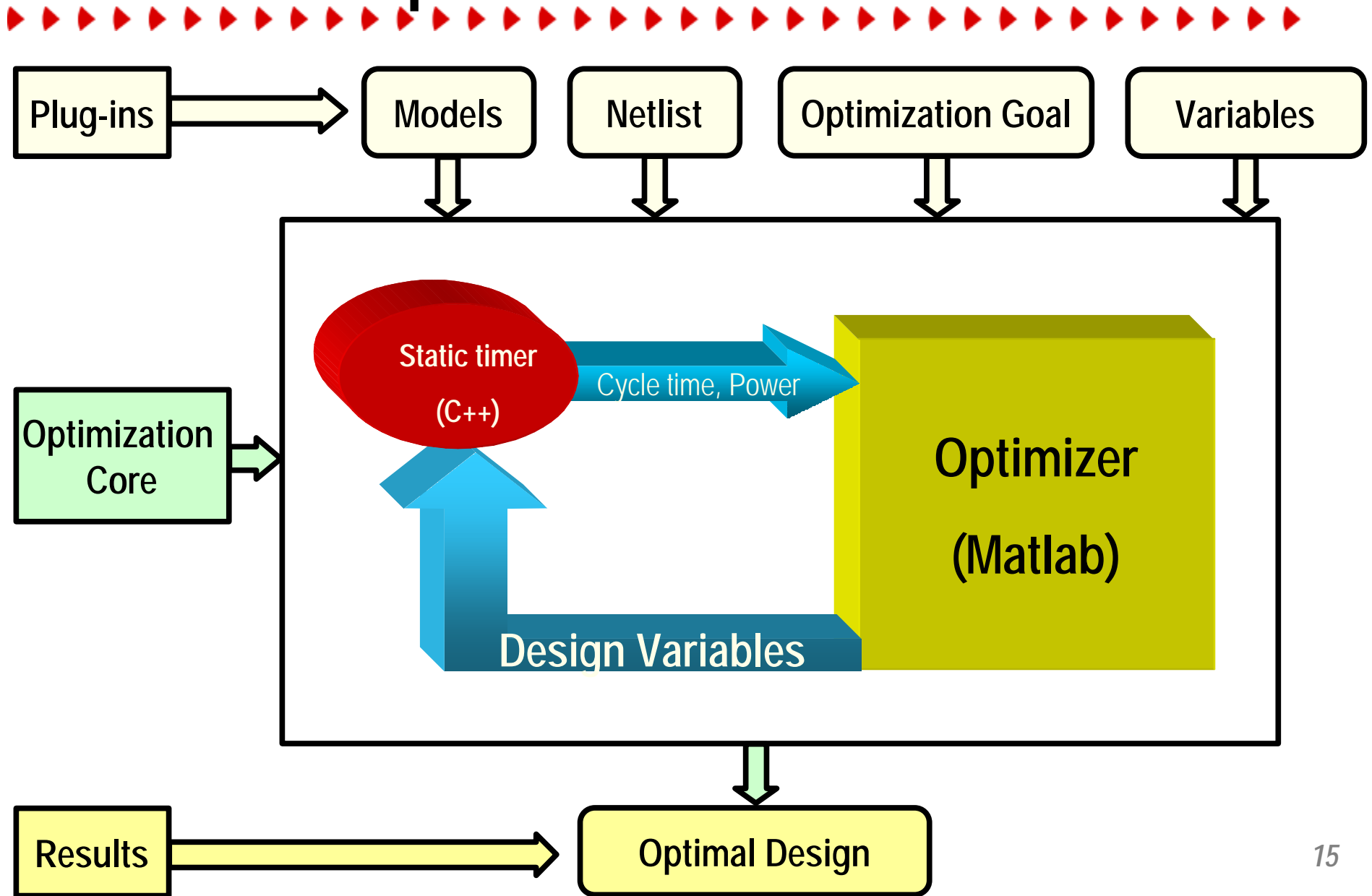

Power Constrained Optimization Problem


Minimize DELAY
subject to
Maximum POWER

Constraints:


- Maximum output slew
- Maximum internal slew
- Maximum input capacitance
- Minimum sizes

Basic Result:

- Power - Performance tradeoff curve

 

PD, PD², P²D ... : Obsolete

 

ALL P-D METRICS ARE INCLUDED IN THE TRADEOFF CURVE

Choice of Models

ANALYTICAL

- Limited accuracy
- + Fast parameter extraction
- + Provide insight in the operation of the circuit
- + Can exploit their mathematical properties to help optimization
 - Target: convex optimization

TABULATED


- + Very accurate
- Slow to generate
- No insight in the operation of the circuit
- Can't guarantee convexity
- Optimization is "blind"
- ☞ If convex models are any good, the optimization problem is not very "non-convex"

Logical Effort: Delay of a Logic Path

$$t_D = p + g \cdot \frac{C_L}{C_{in}}$$

$$C_{in} = g \cdot C_{inv} \cdot W$$
 
$$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$$



$$D = \sum_{i=1}^N p_i + g_i \cdot \frac{C_{load,i}}{C_{in,i}} = \sum_{i=1}^N p_i + \sum_{i=1}^N g_i \cdot \frac{b_i g_{i+1} W_{i+1}}{g_i W_i}$$

Posynomial Functions

- Definition of a posynomial:

$$p(x) = \sum_j \mathbf{g}_j \prod_{i=1}^n x_i^{\mathbf{a}_{ij}} \quad \mathbf{a}_{ij} \in R \quad \mathbf{g}_j \in R^+$$

- A posynomial can be converted to a convex function using a simple change of variables: $x_i = e^{z_i}$ for $x_i \geq 0$
- Logical effort delay is posynomial
 - Fishburn, ICCAD '85: Elmore delay formula can be written as a posynomial
- Switching energy is linear in $W_i \rightarrow$ posynomial
- Convex optimization with posynomials is called **geometric programming**

V_{DD} - Dependent Analytical Delay Model

- ▶ Gate equivalent resistance can be computed from analytical saturation current models (a reduced form of the BSIM3v3 equation)


$$R_{EQ} = \frac{1}{V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{V_{DS} dV_{DS}}{I_{DSAT}} = \frac{3}{4} \frac{V_{DD} (\mathbf{b}_1 V_{DD} + \mathbf{b}_0 + V_{DD} - V_{TH})}{W \cdot K (V_{DD} - V_{TH})^2} \left(1 - \frac{7V_{DD}}{9V_A}\right)$$

- ▶ Include supply and threshold dependency in the delay model:



$$d = c_2 R_{EQ}(W, V_{DD}, V_{TH}) + c_1 R_{EQ}(W, V_{DD}, V_{TH}) \cdot \frac{C_L}{C_{in}} + (\mathbf{h}_0 + \mathbf{h}_1 V_{DD}) t_{s,in}$$

- ▶ Accurate over a **reasonable yet limited** range of fanouts (2.5-6), supplies and threshold (+/- 30%)
 - ▶ Most datapath blocks are within this range
- ▶ **Compatible with convex optimization**
 - ▶ Captures dependencies on V_{DD} and V_{TH} → they can be optimization variables

Vdd and W Optimization

 

Vth, Vdd and W Optimization

  


Outline



- Design as a power – performance optimization problem
- Fundamentals of circuit optimization
- **Design examples**
- Dealing with variations
- Conclusions



Dual V_{DD} ALU in Domino Logic

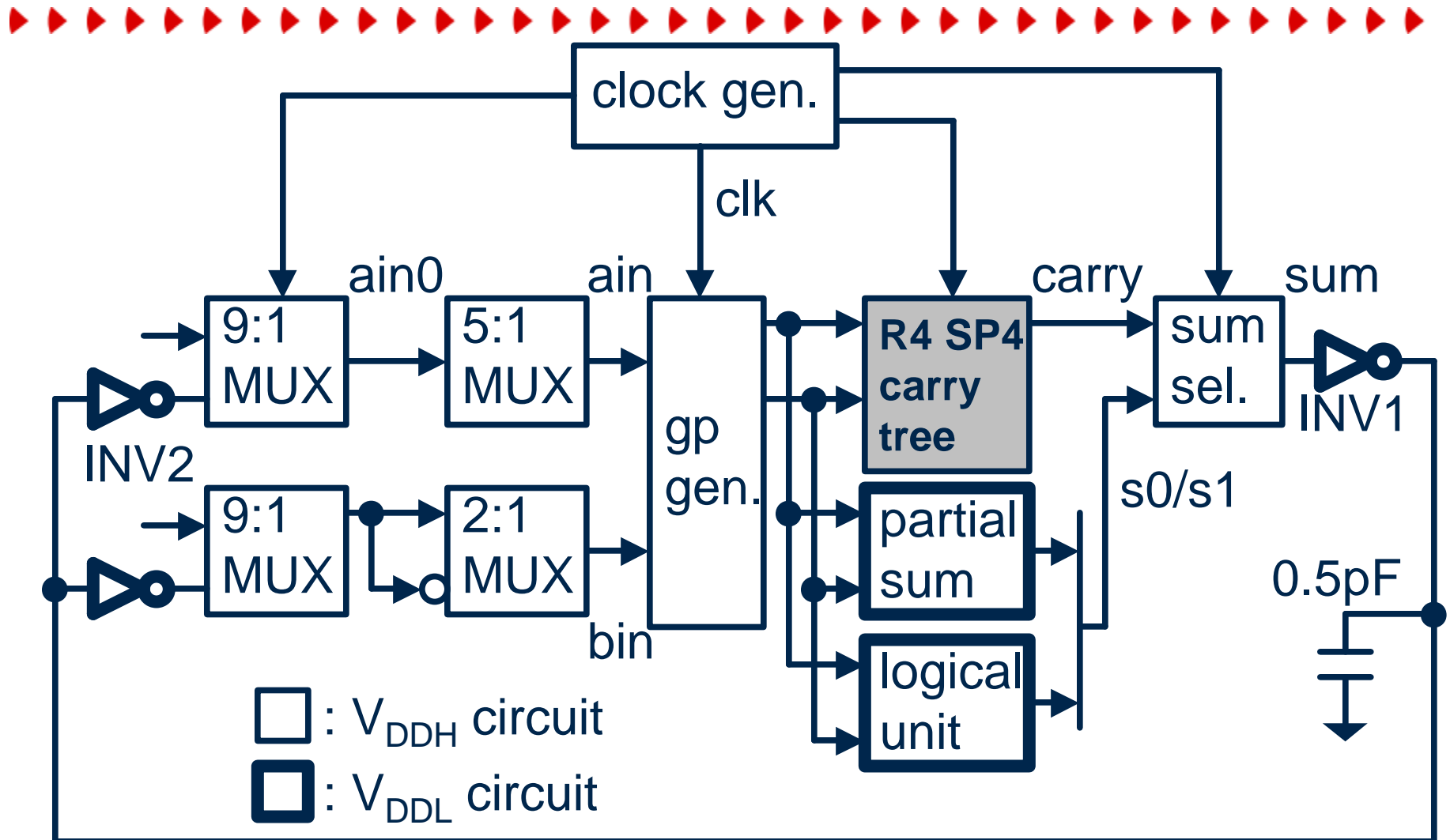

Y. Shimazaki, R. Zlatanovici, B. Nikolic: A Shared – Well Dual – Supply – Voltage 64-bit ALU

ISSCC'03, JSSC 03/2004

Extending the Space: Dual Supply

 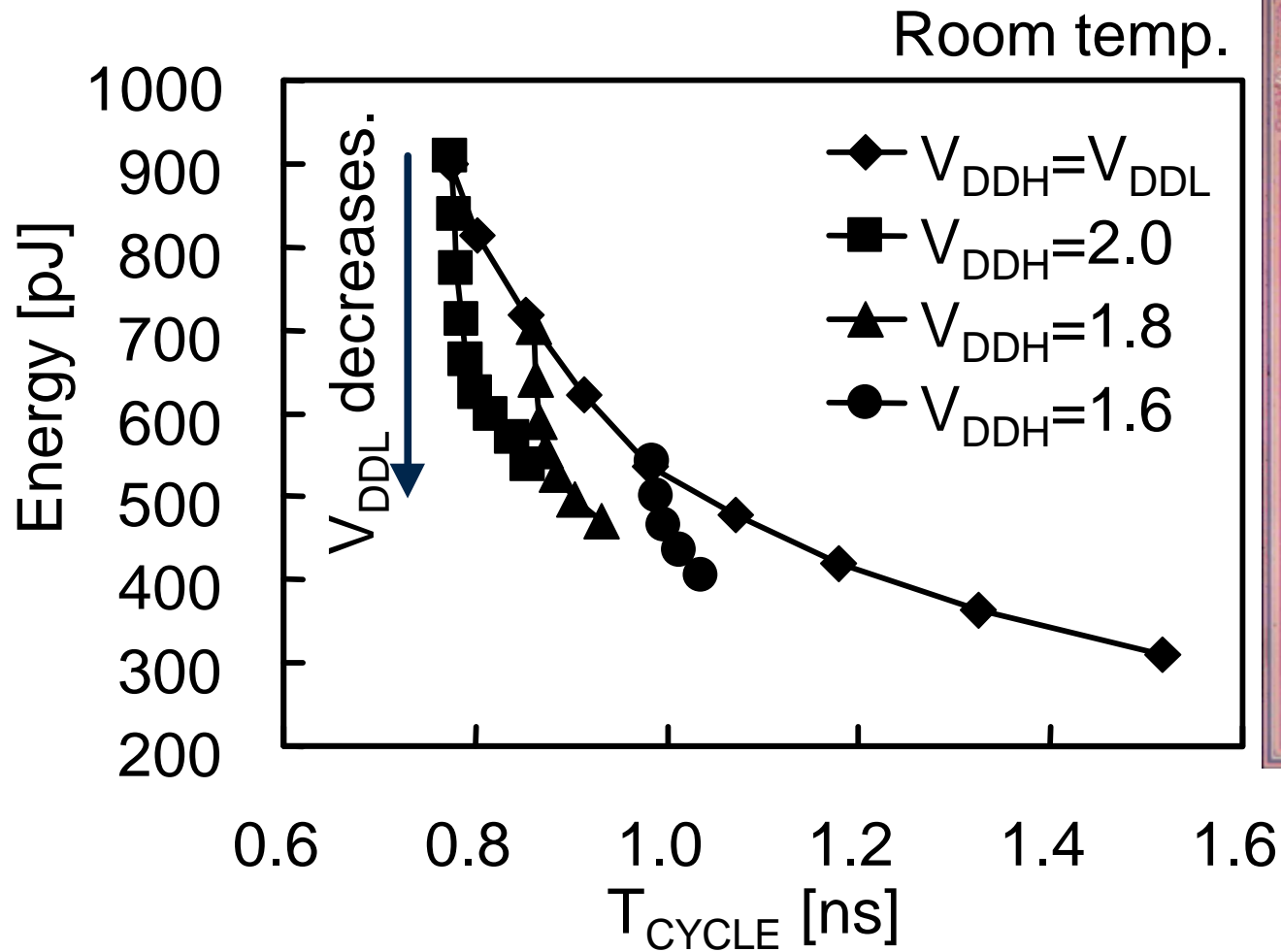


CLA Adders in E-D Space

- ▶ Adders are common in critical paths
- ▶ **CLA adders:**
 - ▶ Many designs, commonly used in practice
 - ▶ Recent interest in sparse adders
 - ▶ No fair comparison in energy – delay space
- ▶ **This work:**
 - ▶ Optimization of representative 64-bit adders in energy – delay space
 - ▶ Optimal 64-bit adder design


64-Bit CLA Adders

- Generic 64-bit adder block diagram

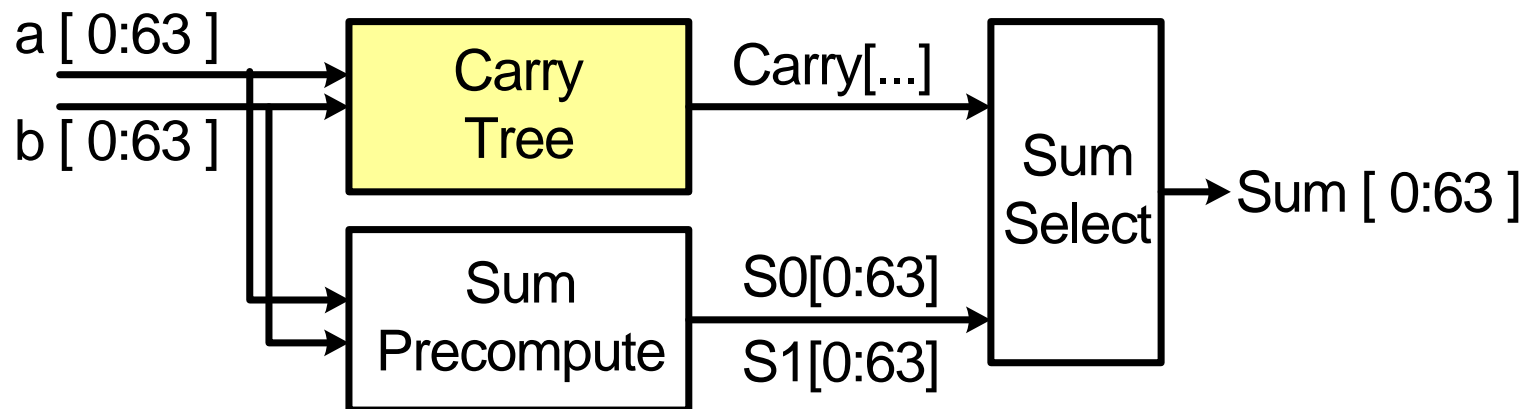

- Classical CLA, Ling equations
- Static, single-rail domino, compound domino logic
- Radix-2 and radix-4 carry trees
- Full and sparse trees (sparseness of 2 and 4)
- Use tabulated delay and analytical energy models (switching, leakage)


Equation Set Comparison

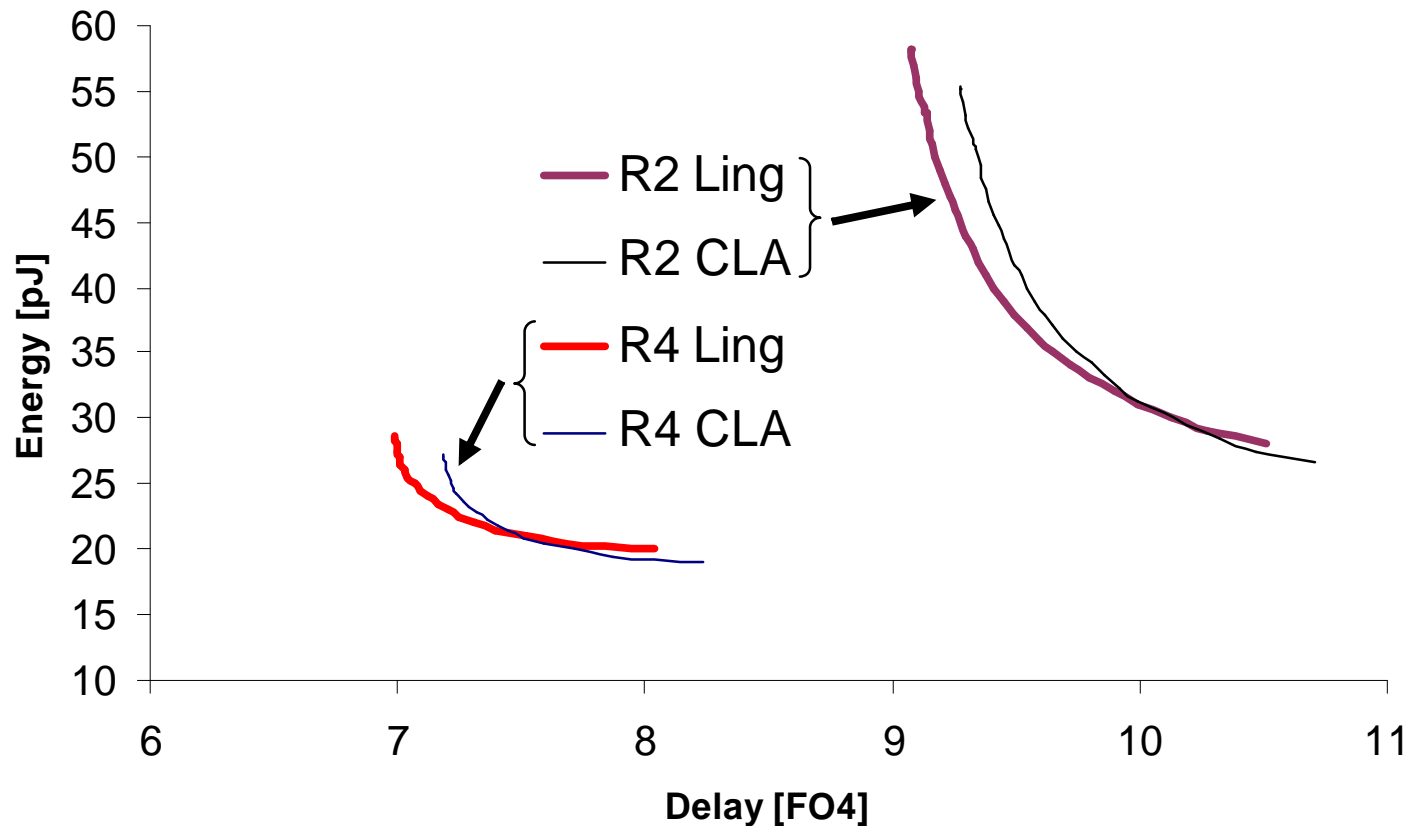

Ling adders achieve shorter delays
Radix-4 are faster than radix-2

Choosing a Logic Style

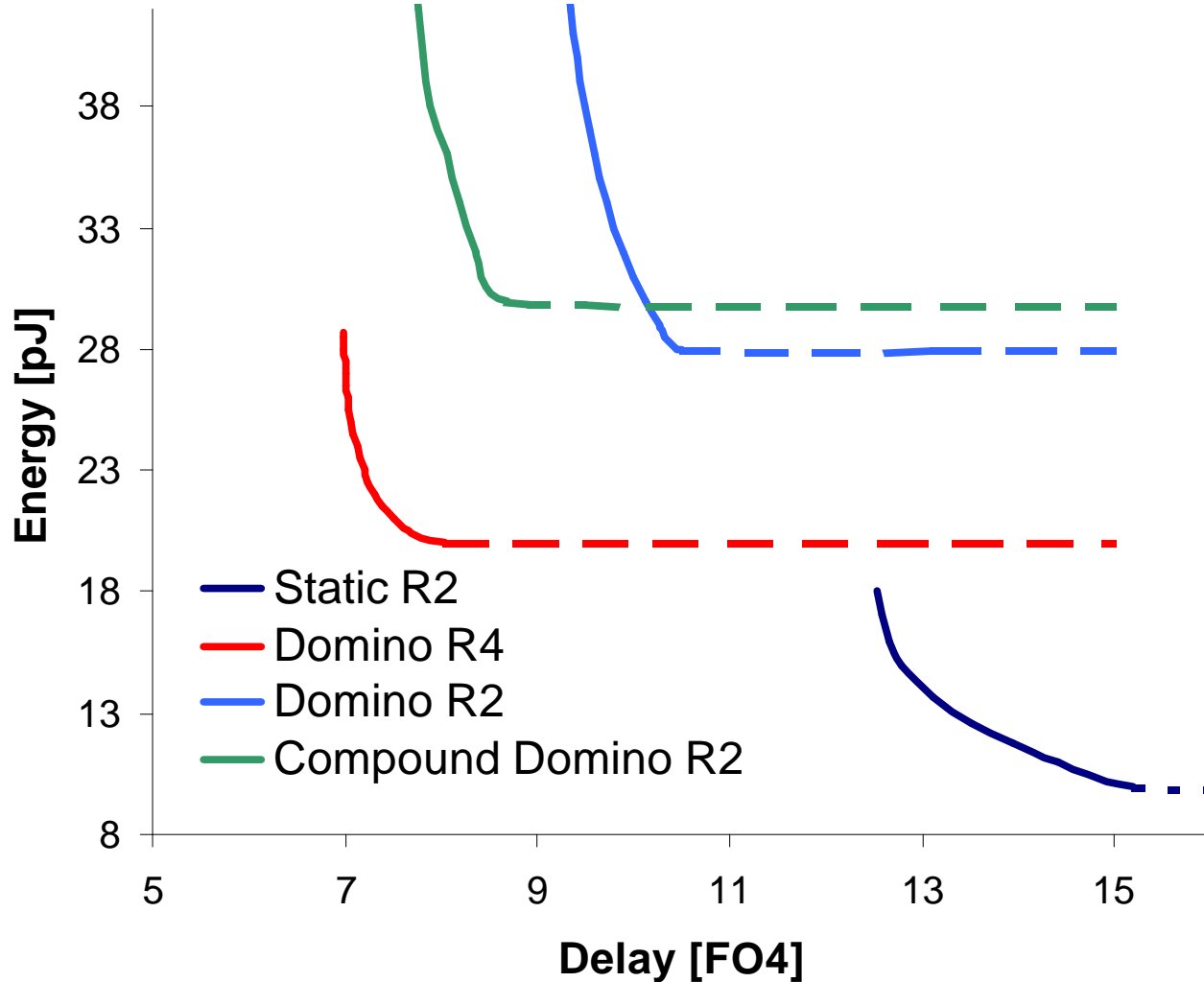
- Static adders are low power but slow
- Domino logic is the choice for short cycle times




Full vs. Sparse Trees



R2 Full

 


R2 SP2

 

Sparse trees:

- Heavier load on the carry tree
- Reduced input loading
- More complex sum precompute gates


Proof of Existence: Fastest Adder

 

- ▶ Radix-4 sparse-2 domino Ling adder
- ▶ Technology:
 - ▶ 90 nm 1P 7M
 - ▶ $V_{DD} = 1\text{ V}$
- ▶ Performance:
 - ▶ Delay: 210 ps (post – layout simulation)
 - ▶ Energy: 9.1 pJ / cycle (optimization tool)
- ▶ Core dimensions: 417.3 mm x 75.3 mm
- ▶ Chip to be taped out 11/1/04



*with Sean Kao

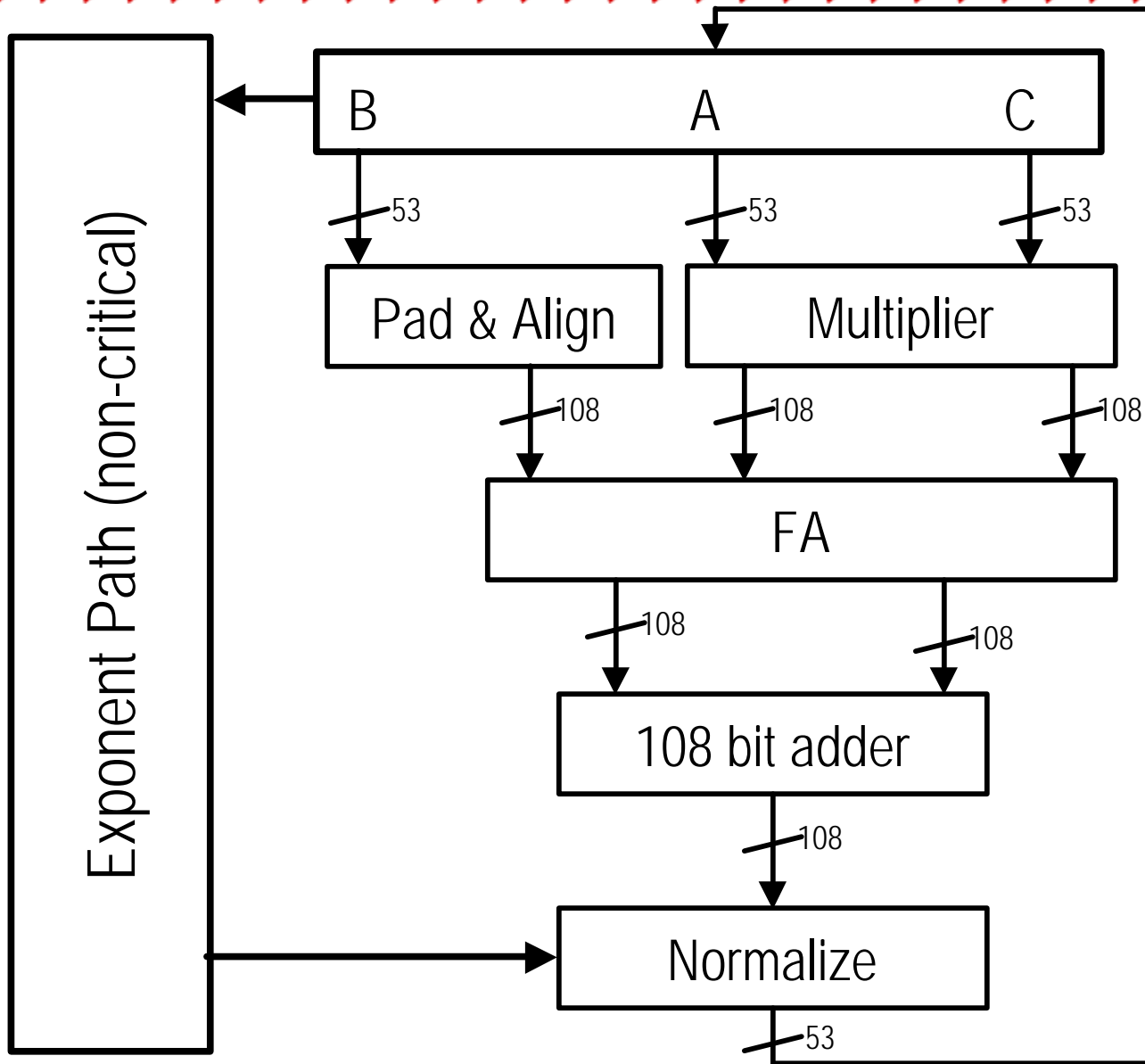Micro-Architecture Optimization: Power4 FPU



- ▶ 5 cycles
- ▶ 2-phase clocking
- ▶ Static CMOS

Optimizing Pipelined Circuits

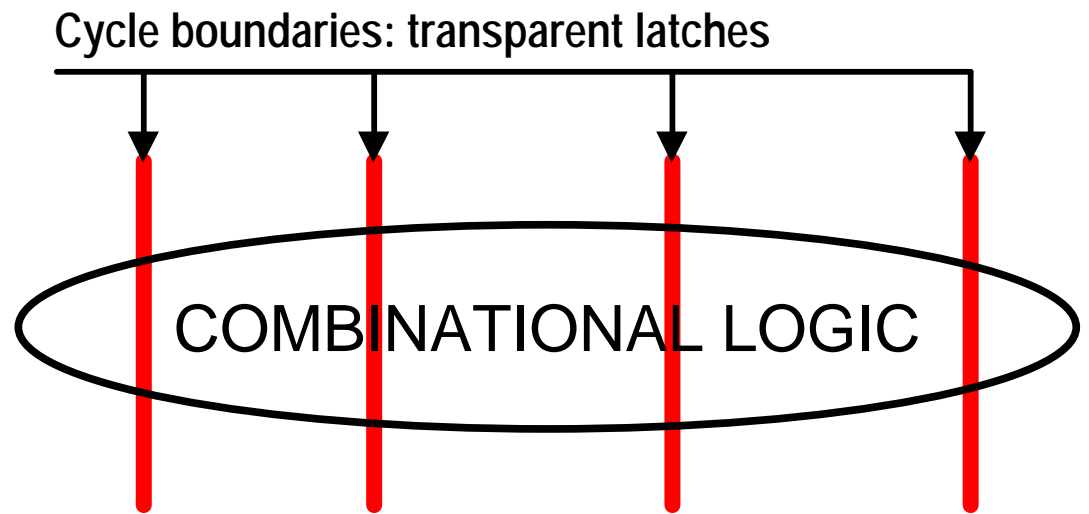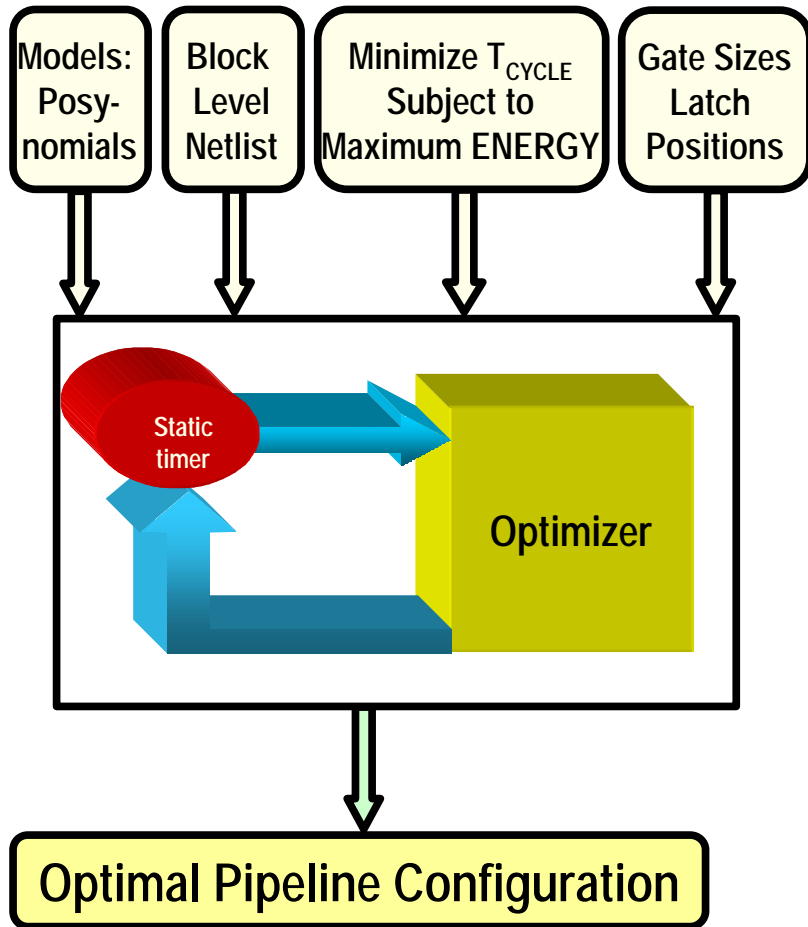

- Fix pipeline depth
- Find shortest cycle time for fixed cutset
- Search for optimum cutset

Work in progress...




Outline



- ▶ Design as a power – performance optimization problem
- ▶ Fundamentals of circuit optimization
- ▶ Design examples
- ▶ **Dealing with variations**
- ▶ Conclusions

Robust Optimization

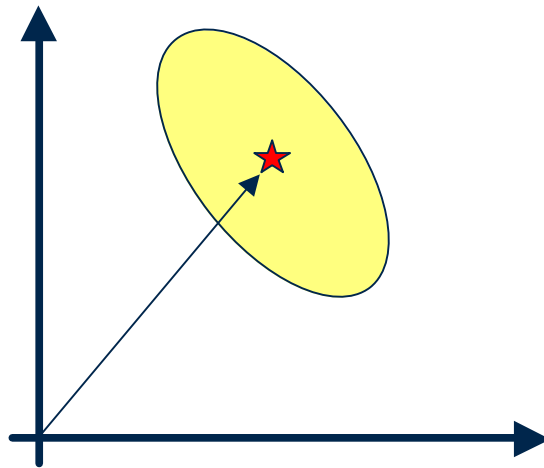- ▶ Parameters are within an **ellipsoid** centered on the nominal values
- ▶ Optimize the **worst case**



- ▶ Compatible with convex optimization for the presented analytical models
- ▶ Problem: computing the ellipsoid

Stochastic Optimization for Yield

- Parameters are **random variables** centered on the nominal values
- Optimize for a desired **yield**

$$\begin{array}{l} \min_{x \in R^n} f(x) \\ \text{subject to} \\ g_i(x) \leq 0 \quad i = 1..m \end{array}$$




$$\begin{array}{l} \min_{x \in R^n} f(x) \\ \text{subject to} \\ P(g_i(x) \leq 0, \quad i = 1..m) \geq h \end{array}$$

- Compatible with convex optimization under certain conditions
 - Convex analytical models
 - Jointly Gaussian parameters
- Problem: finding the distributions of the parameters, especially the **correlations**


Impact of Layout on Variations

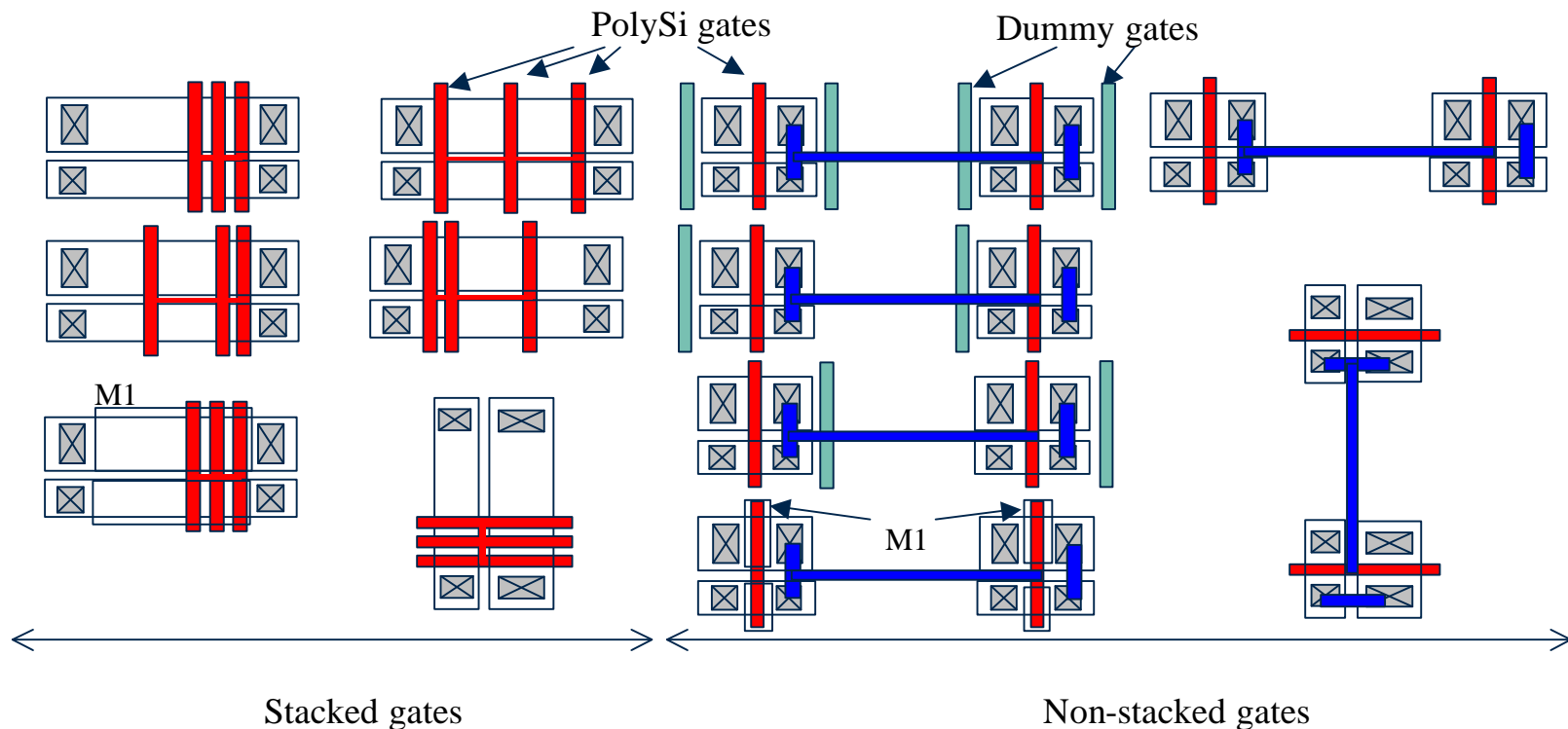- ▶ Stacked gates vs. non-stacked gates (e.g. gates vs. buffers)
- ▶ Proximity effects, orientation of gates, metal layer above gate (annealing)



Test Chip

 - 90nm 1P 7M
- $V_{DD} = 1\text{ V}$
- $1.55 \times 1.17\text{ mm}^2$
- Taped out 9/04
- To be packaged and tested
- Measurements will provide statistical data for the stochastic optimizer



Conclusions



Power and performance are the two sides of the same coin.
The connection: the **power – performance tradeoff curve**.

- Built a suite of stackable tools to design “**power – performance optimal** circuits”
- Design space explorations:
 - Different optimization variables
 - Various levels of abstraction
 - Impact of variations
- Experimented the tool suite on various designs
 - Dual-supply ALU
 - CLA Adders in the E-D space