

LOSSLESS FEEDBACK AMPLIFIERS

George D. Vendelin

Fellow, IEEE

January 9, 2003

Coauthor : Luke Yu-Hsun Huang & Calvin Chi-Chung Chien

Outline


- Introduction
- References/History
- High Gain Amp – Mason's Unilateral Gain 1954
- LNA (F_{min} with $S_{11}' = 0$) – Vendelin 1975
- HPA (P_{1dBc} with $S_{22}' = 0$) – Dual of LNA
- Circuit Topologies which allow low frequency Stability
- Examples
- Future Research
- Conclusions

REFERENCES/HISTORY

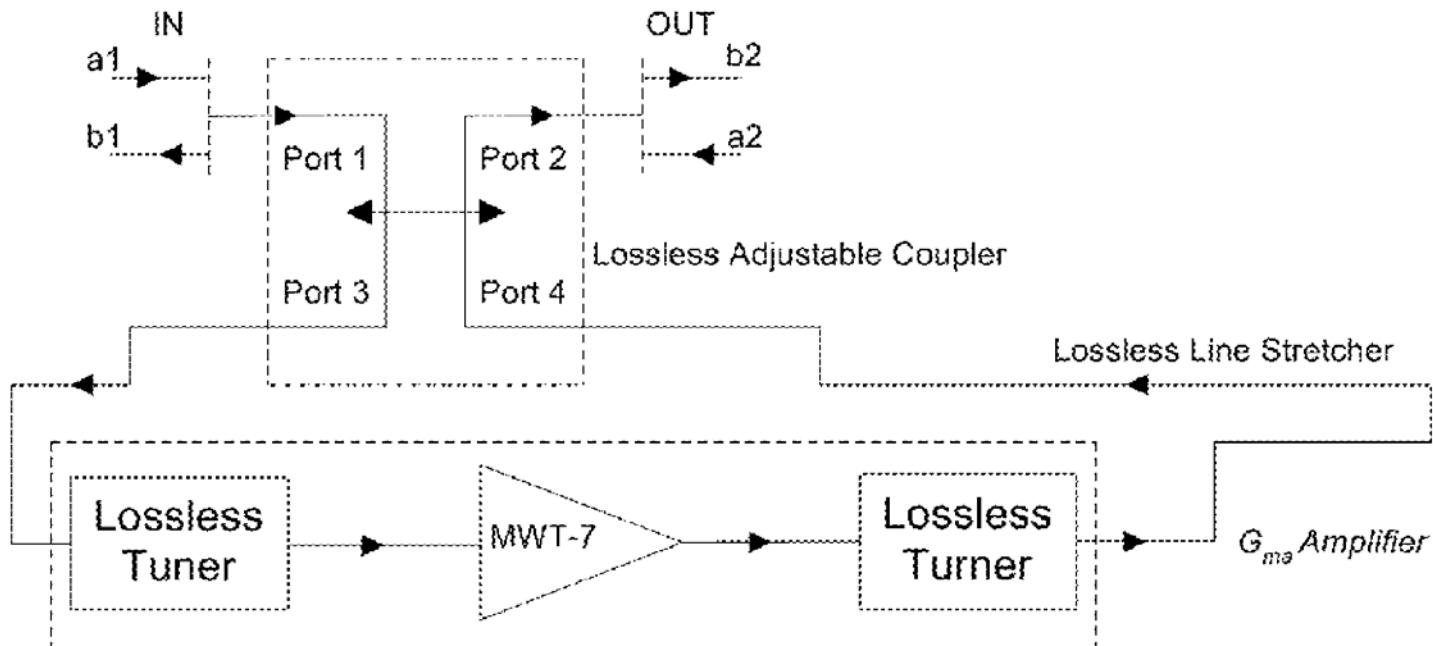1. S. J. Mason, "Power Gain in Feedback Amplifiers," Trans. IRE Professional Group on Circuit Theory, vol. CT-1, no. 2, pp. 20-25, June **1954**.
2. C. C. Cheng, "Neutralization and unilateralization," IRE Trans. Circuit Theory, vol. CT-2, no. 2, pp. 138-145, June **1955**.
3. L. Besser, "Stability Consideration of Low-Noise Transistor Amplifiers with Simultaneous Noise and Power Match," MTT Symposium, pp. 327-329, **1975**.
4. G. D. Vendelin, "Feedback Effects on The Noise Performance of GaAs MESFETS," MTT Symposium, pp. 324-326, **1975**.
5. G. D. Vendelin, "Feedback Effects in the GaAs MESFET Model," IEEE Trans. MTT, pp. 383-385, June **1976**.
6. M. S. Gupta, "Power Gain in Feedback Amplifiers, a Classic Revisited," IEEE Trans. MTT, vol. 40, no. 5, pp. 864-879, May **1992**.
7. Y. H. Huang, C. C. Chien, G. D. Vendelin, "Exact Analysis of Maximum Available Gain and Unilateral Gain Including Phase Angle of S21," IEEE Microwave and Wireless Components Letters, March **2003**.
8. G. D. Vendelin, A. M. Pavio, and U. L. Rohde, *Microwave Circuit Design Using Linear and Nonlinear Techniques*, 2ed Edition, Wiley, to be published, 2003.

Three types of Lossless FB-Amps – (1) High Gain Amplifiers (HGA)

- Unilateral Gain
 - Using lossless feedback network to make y_{12} and z_{12} approach zero to achieve high gain.



High Gain Amplifiers (HGA)


- Mason's Unilateral Gain ($U = 1$ at F_{max})

$$U = \left| \left(S_{21}/S_{12} \right) - 1 \right|^2 / \left[2 \left| k S_{21}/S_{12} \right| - \operatorname{Re}(S_{21}/S_{12}) \right]$$

- How to unilateralize an active device?
 - 1955, C. C. Cheng showed 5 ways :
 - Series-Series feedback
 - Parallel-Parallel feedback
 - Series-Parallel feedback
 - Parallel-Series feedback
 - Series-oppositely Parallel feedback

High Gain Amplifiers (HGA)

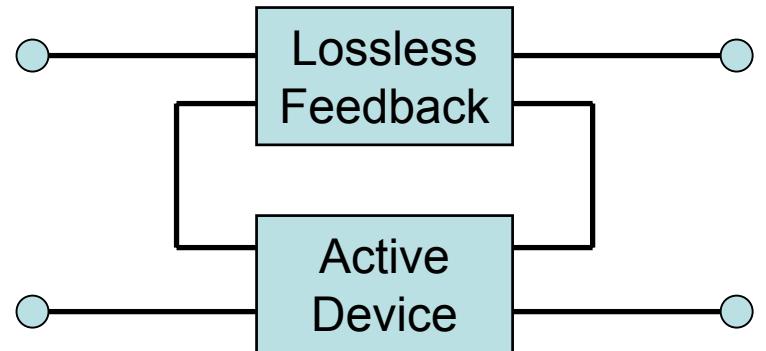- General Design Procedure :
 - Build the bias circuits for the active device.
Find S, Y, and Z-parameters of the device.
 - Choose proper feedback networks to unilateralize the active device.
 1. $\text{Im}(Y_{12}) = - \text{Im}(Y_{12FB})$
 2. $\text{Im}(Z_{12}) = - \text{Im}(Z_{12FB})$
 3. Optimize for U







High Gain Amplifiers (HGA)

- Determine the values of feedback elements for $S_{12} = 0$.
$$S = \begin{bmatrix} 0 & 0 \\ \sqrt{U} \angle \theta & 0 \end{bmatrix}$$
- Match the input and output impedance to the system characteristic impedance (Z_0). Make sure that the matching networks include **shunt inductors** to stabilize the amplifier.
- Use stability circle method to verify the stability. If the circuit is still unstable, series a resistor to the shunt inductor of the input or output.

Stability Considerations

Matching Topologies :

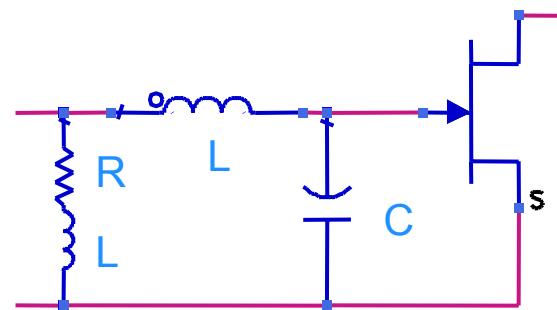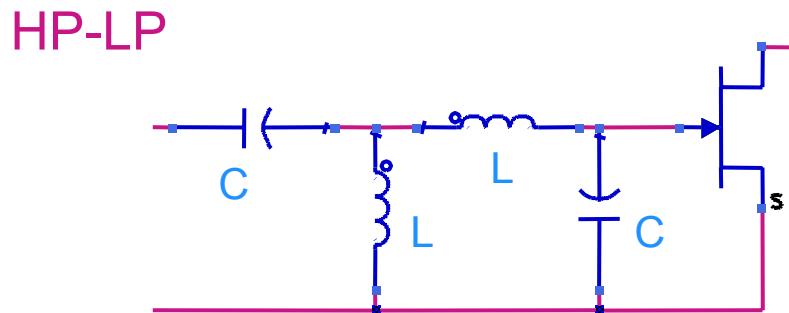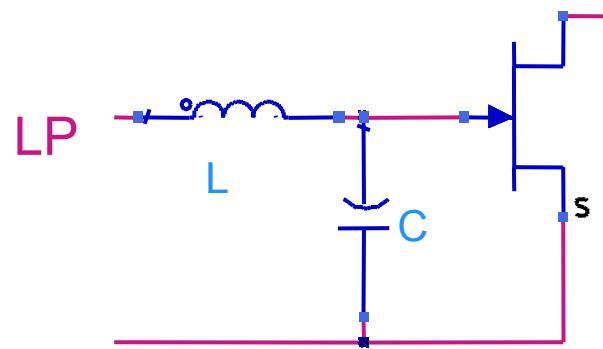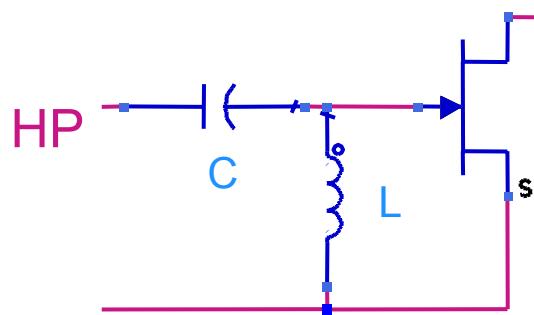



Resistor will help at low frequency.

Example for HGA

- Unilateral Amplifier

$U = 15 \text{ dB}$



$G_{ma} = 10 \text{ dB}$

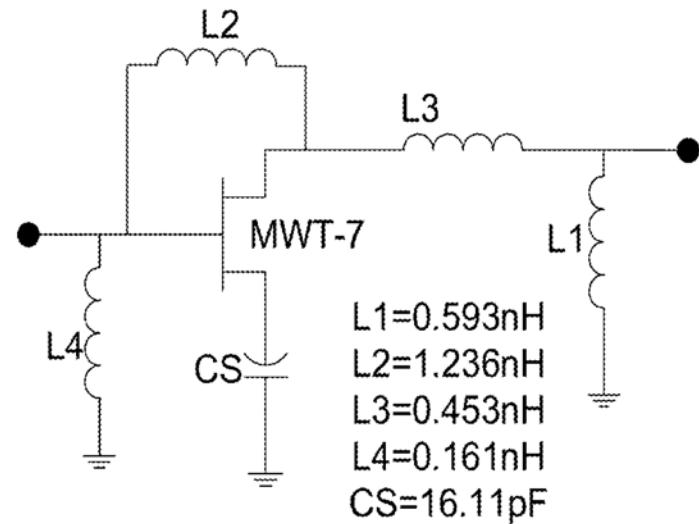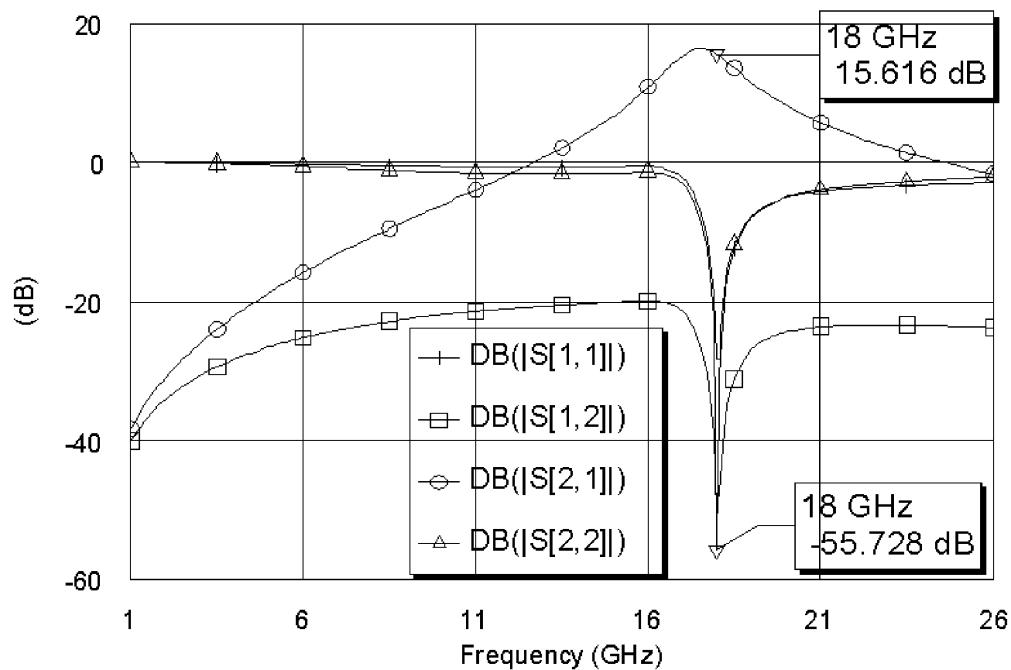

Example for HGA


Stability Circles:

Blue lines are input Stability Circles.
Pink lines are output Stability Circles.
The concepts of the method are
 $|\Gamma_G S_{11}'| < 1$ and $|\Gamma_L S_{22}'| < 1$.

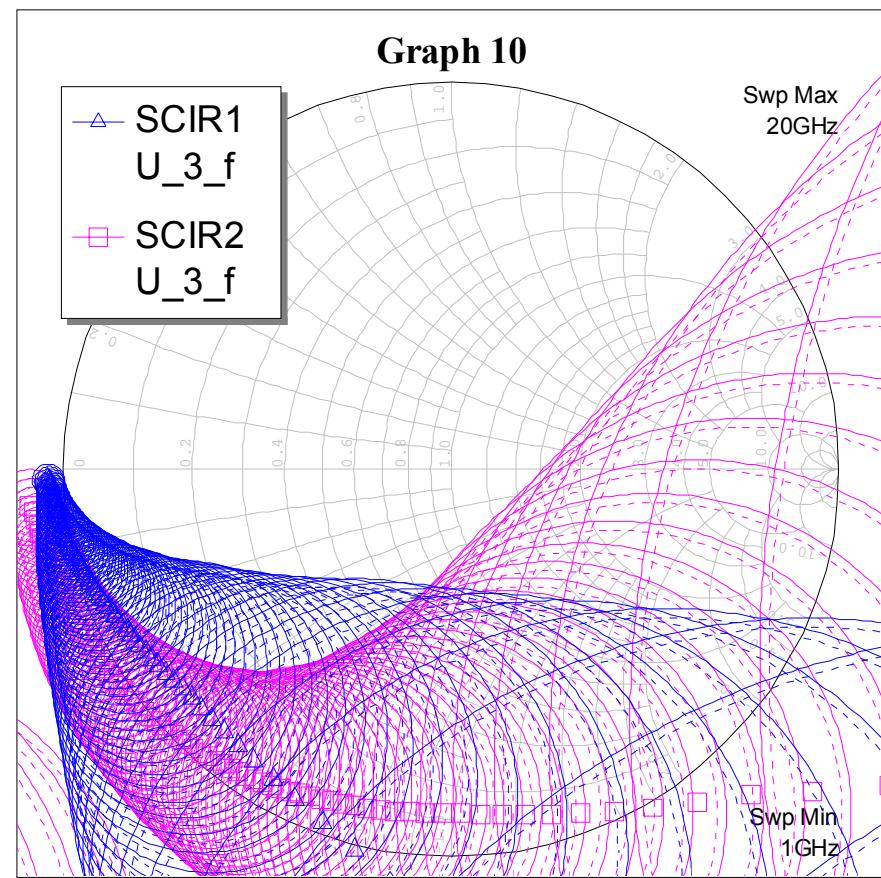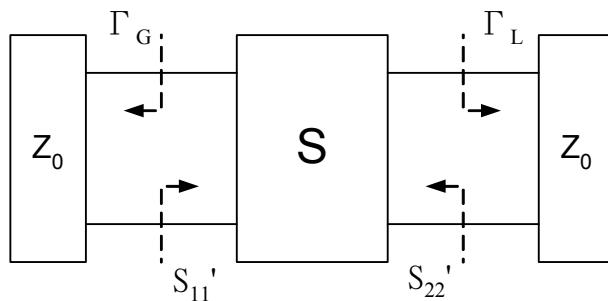

Three types of Lossless FB-Amps – (2) Low Noise Amplifiers (LNA)

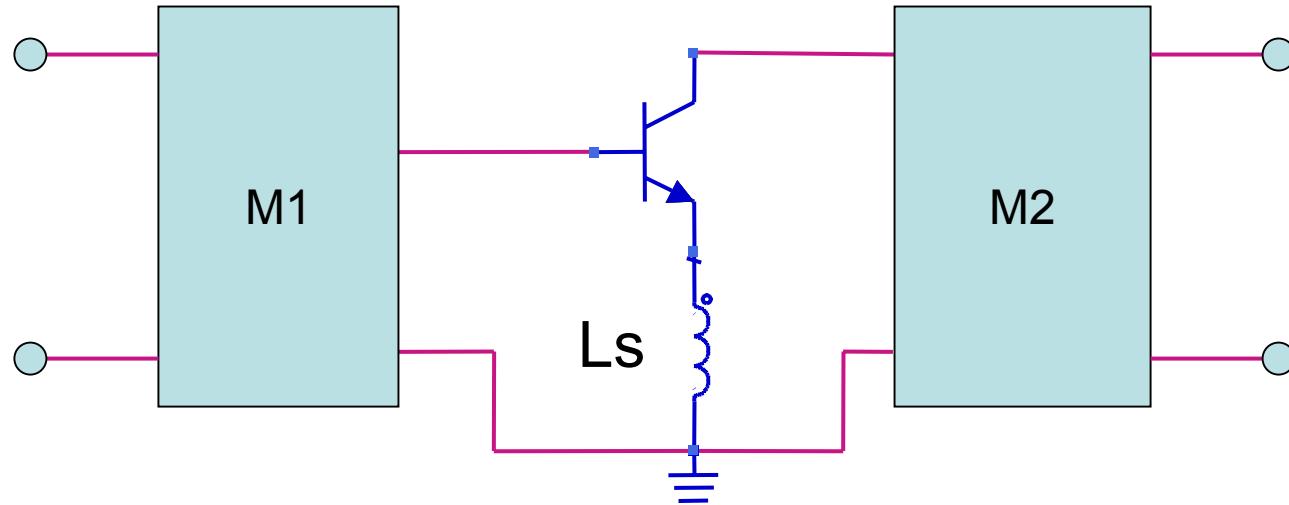- Using lossless feedback network (For example L_s) and M_1 to achieve low noise with $S_{11}'=0$.
- L_s resonates C_{gs} .



Low Noise Amplifiers (LNA)

- LNA

- $G_A = |S_{21}|^2 (1 - |\Gamma_G|^2) / \left(|1 - S_{22}\Gamma_G|^2 (1 - |S_{11}|^2) \right)$

- $S_{11}' = 0$

- $F = F_{\min}$

Uses common lead inductor to resonate
input capacitor

$$\mathbf{S} = \begin{bmatrix} 0 & S_{12} \angle \theta_2 \\ \sqrt{G_A} \angle \theta_1 & 0 \end{bmatrix}$$


Three types of Lossless FB-Amps – (3) High Power Amplifiers (HPA)

- Maximum Power
 - Make Z_{load} load impedance for maximum power output.
 - Class A Operation for best Linearity.

m2
 $V_{DS} = 1.500$
 $V_{GS} = 0.500000$
 $I_{DS,i} = 6.824$

m1
 $V_{DS} = 7.500$
 $V_{GS} = -0.300000$
 $I_{DS,i} = 3.555$

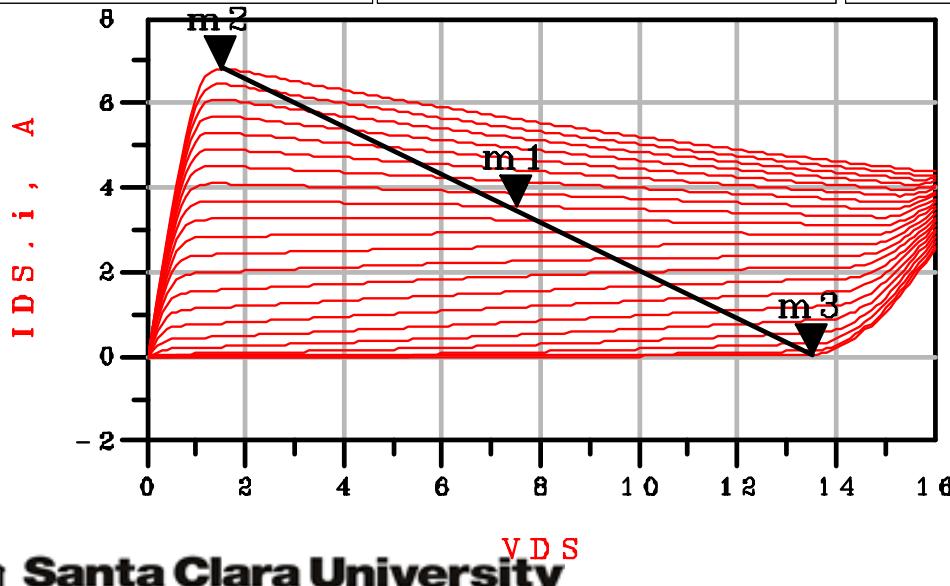m3
 $V_{DS} = 13.500$
 $V_{GS} = -1.600000$
 $I_{DS,i} = 0.038$



10W design ; $V_{m2}=1.5V$

$I_{max}=6.8A$; $V_{m1}=V_{bias}=7.5V$

$R_{load}=2(V_{bias}-V_{m2})/I_{max}$

$P_{out}=I_{max}(V_{bias}-V_{m2})/4$




High Power Amplifiers (HPA)

- HPA
 - $G = |S_{21}|^2 (1 - |\Gamma_L|^2) / [|1 - S_{22} \Gamma_L|^2 (1 - |S_{11}'|^2)]$
 - $S_{22}' = 0$
- Use losses FB to give $P_{out} = P_{1dBc}$ when $S_{22}' = 0$.


$$S = \begin{bmatrix} 0 & S_{12} \angle \theta_4 \\ \sqrt{G} \angle \theta_3 & 0 \end{bmatrix}$$
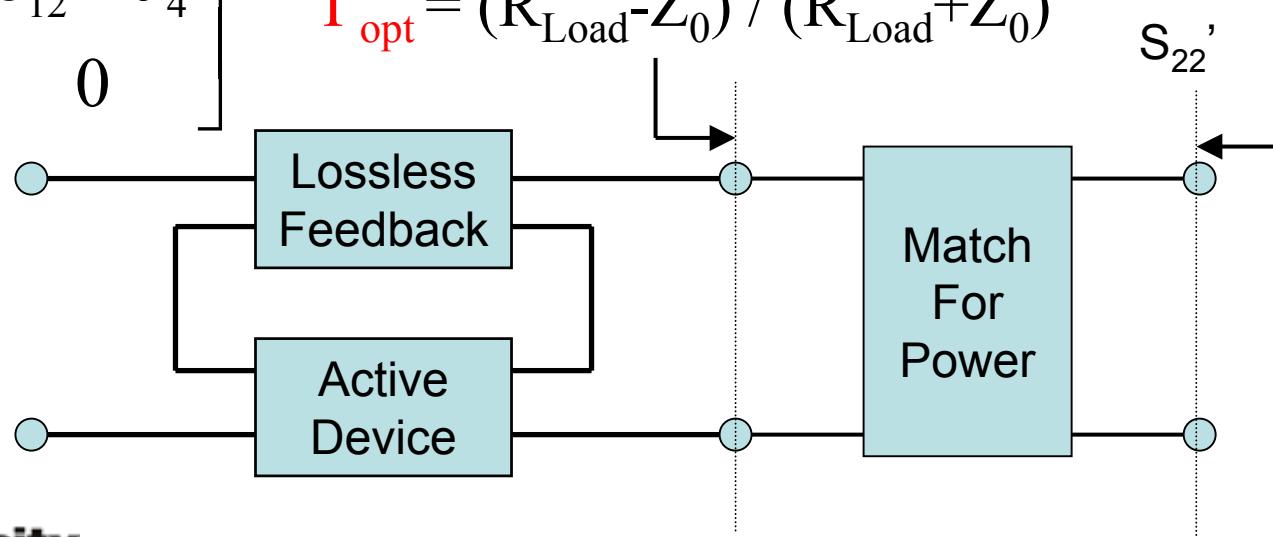
$$\Gamma_{opt} = (R_{Load} - Z_0) / (R_{Load} + Z_0)$$



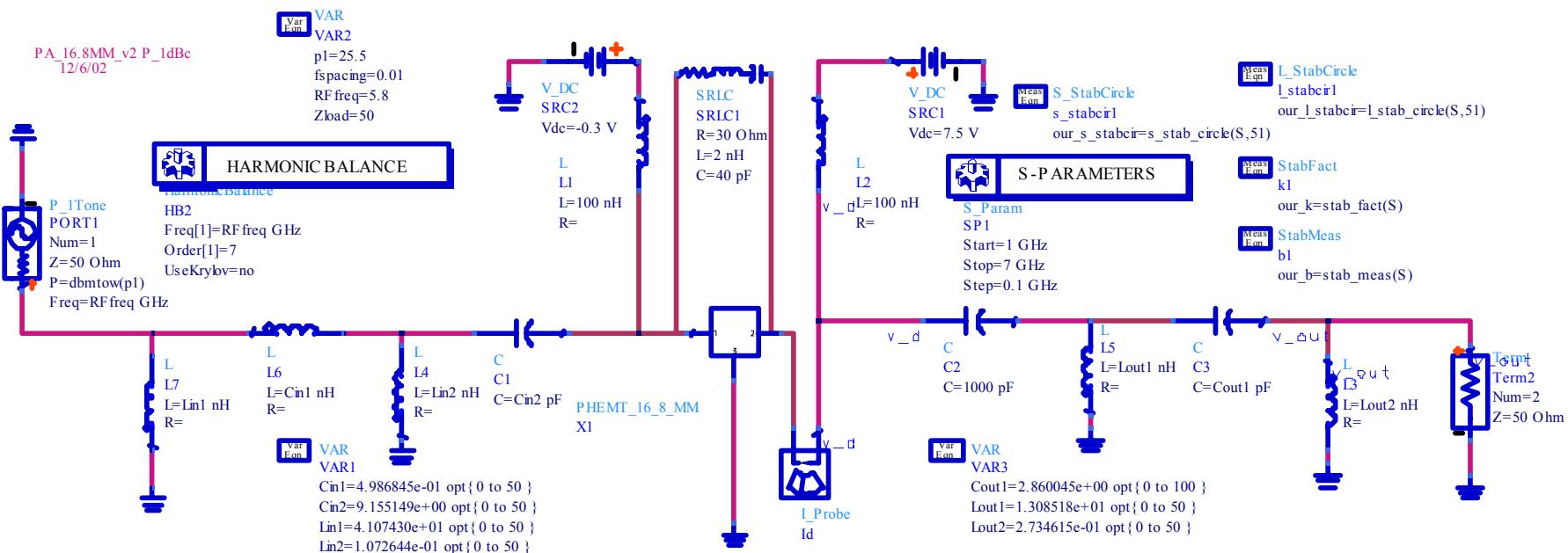Example for HPA (10W PA)

- $150\text{um} \times 8 \times 14 = 16.8 \text{ mm}$. PHEMT at 5.8GHz.
- 10 W output = 40 dBm for $P_{1\text{dBc}}$; TOI= $P_{1\text{dBc}} + 10\text{dBm}$.
- PAE = 45% ; $R_{\text{load}} = 1.2 \text{ Ohms}$.







Example for HPA (10W PA)

- Design Procedure :
 1. Get the I_{ds} Vs V_{ds} curves using the curve tracer. Choose the bias point.
 2. Choose the load line for high power and high linearity.
 3. Design the output match for the load line.
 4. Get the P_{1dBc} .
 5. Check the dynamic load line.
 6. Check S_{11}' . Design the input match for S_{11}' .



Example for HPA (10W PA)

7. Get TOI.
8. Check for stability.
9. Put a feedback on.
10. Adjust as required to meet the specifications.
Use no resistors. For TOI, a resistor may be necessary.

Example for HPA (10W PA)

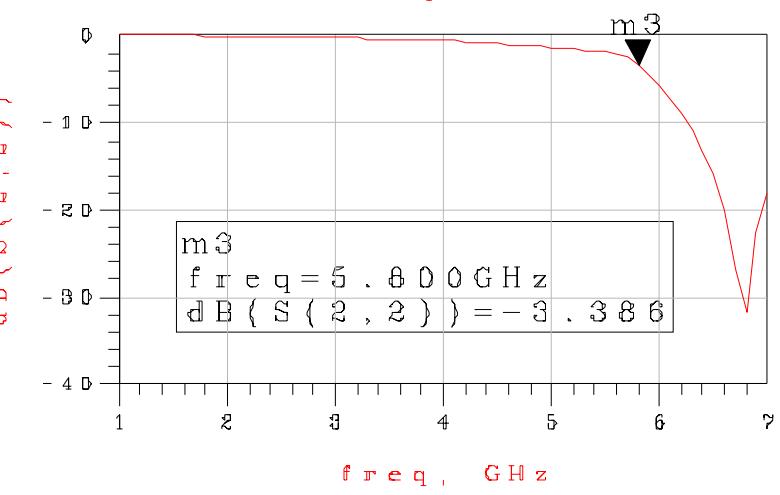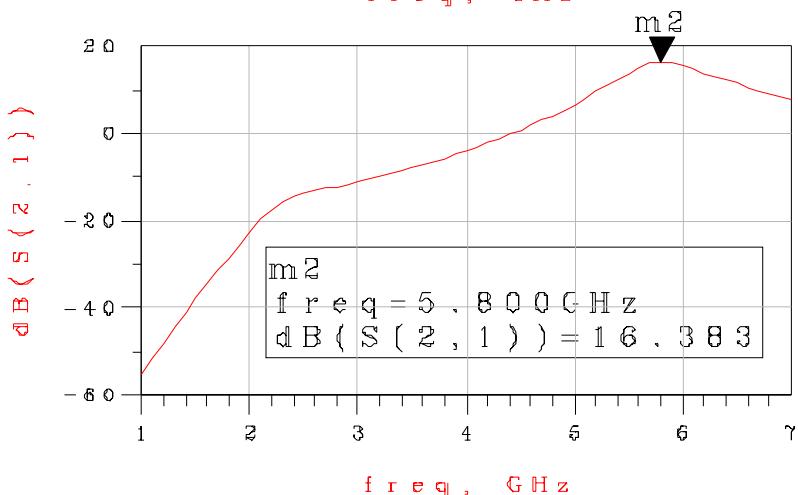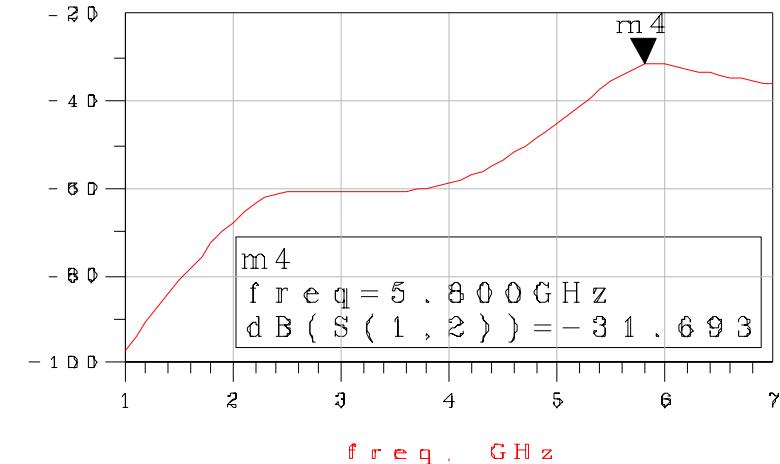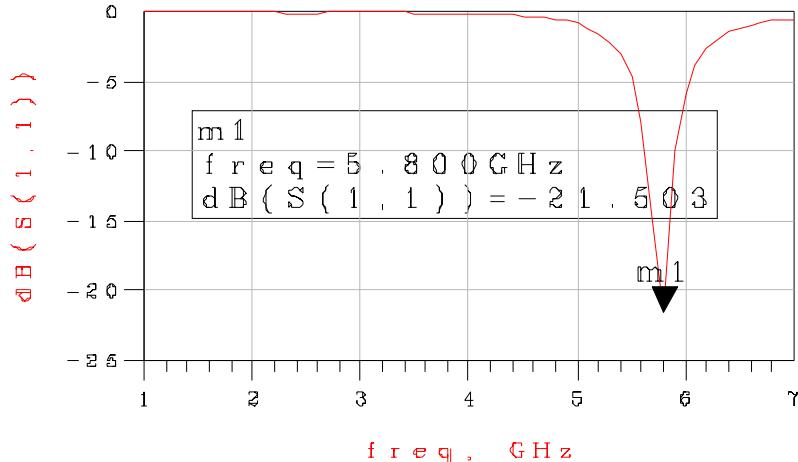


Example for HPA (10W PA)

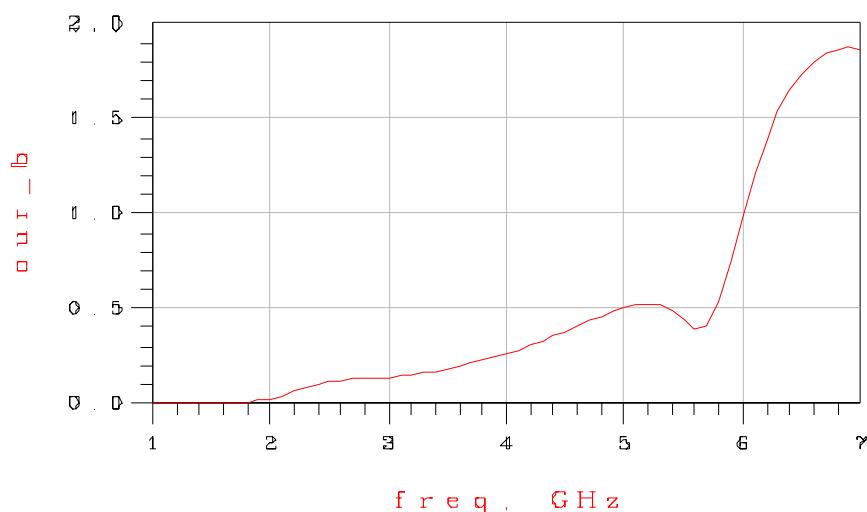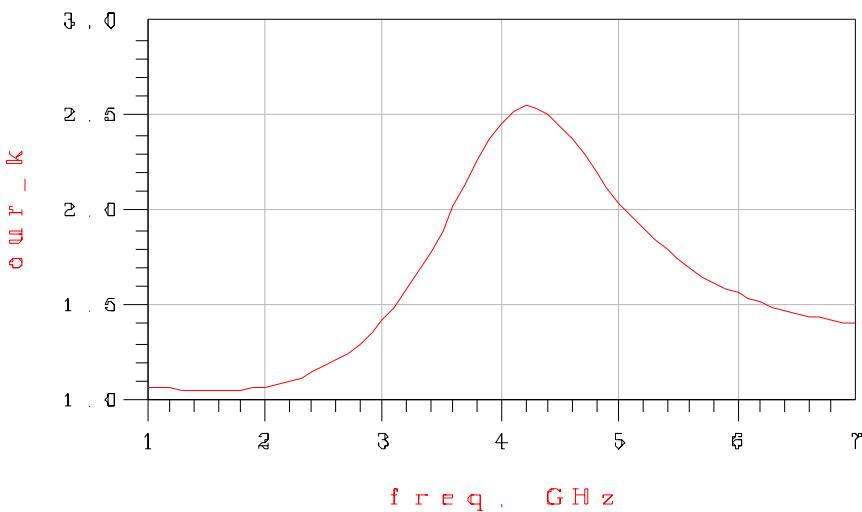

$K > 1$ & $B > 0$. The circuits is unconditional stable.

Example for HPA (10W PA)

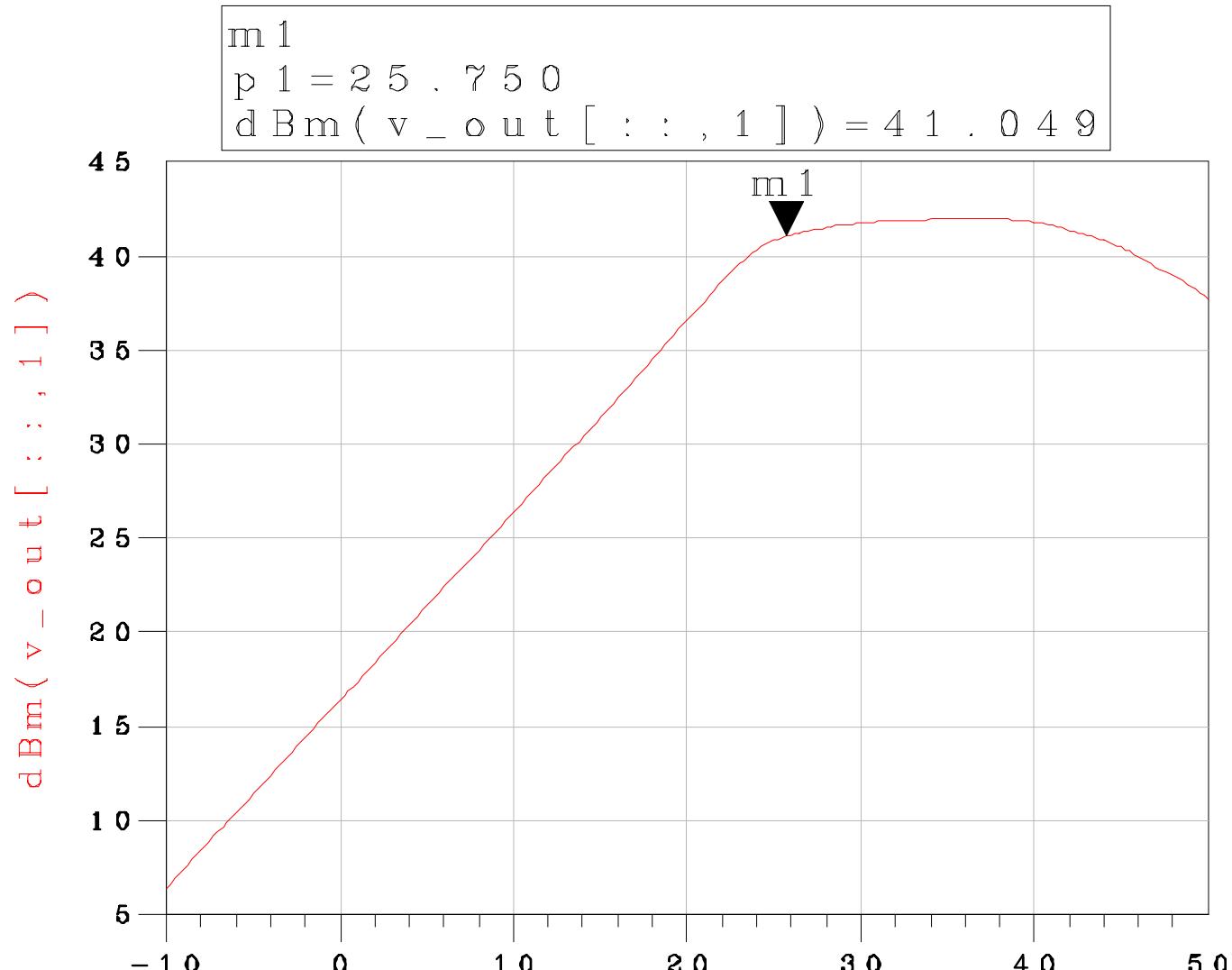


Example for HPA (10W PA)

TOI

RF freq	our_ipo
5.700	50.746
5.800	52.125
5.900	53.855

old - new

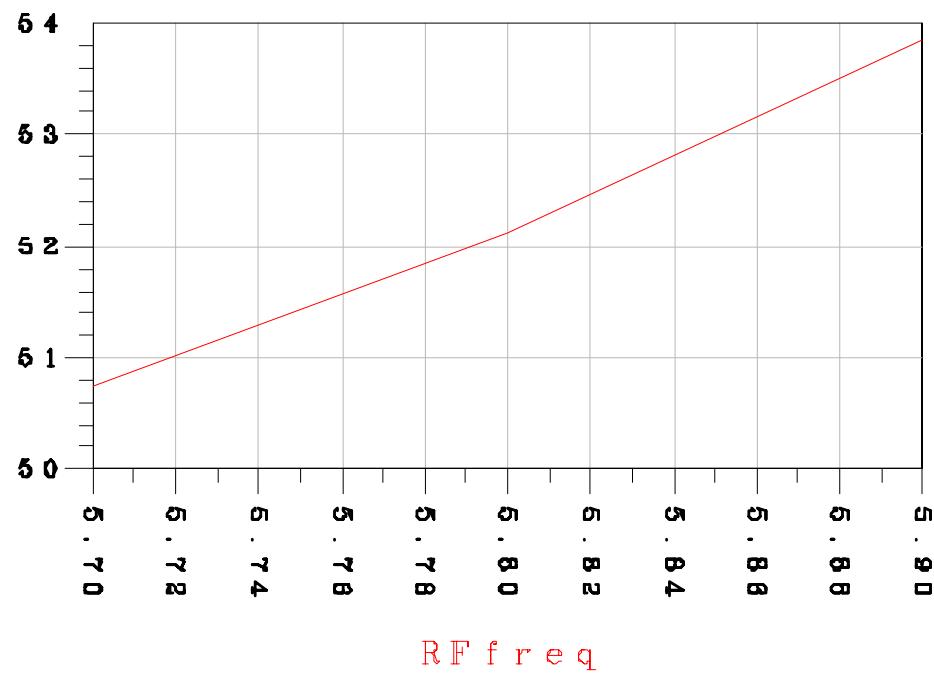


Future Research

- Future Research on HPA.
 - LNA has been published for F_{\min} & $S_{11}' = 0$.
 - HPA has not been analytically solved for P_{1dBc} & $S_{22}' = 0$.
- Explain cause of $\text{Re}(Y_{12}) < 0$ for FET.
 - For BJT, $\text{Re}(Y_{12}) > 0$.
 - For FET, $\text{Re}(Y_{12}) < 0$. 1976, Vendelin.

Future Research

Y Parameter
Equivalent Circuits.

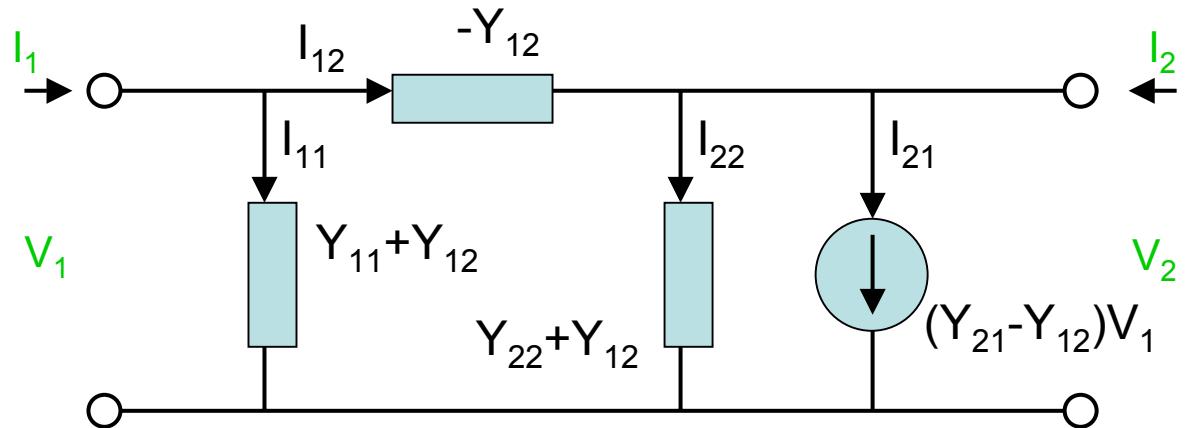


- $I_{11} = (Y_{11} + Y_{12}) V_1 ; \quad I_{12} = (-Y_{12})(V_1 - V_2) .$
- $I_{21} = (Y_{21} - Y_{12}) V_1 ; \quad I_{22} = (Y_{22} + Y_{12}) V_2 .$
- $I_1 = I_{11} + I_{12} = (Y_{11} + Y_{12}) V_1 + (-Y_{12})(V_1 - V_2)$
 $= Y_{11}V_1 + Y_{12}V_2 .$
- $I_2 = (Y_{21} - Y_{12}) V_1 + (Y_{22} + Y_{12}) V_2 - (-Y_{12})(V_1 - V_2)$
 $= Y_{21}V_1 + Y_{22}V_2 .$


Future Research

Y_{12} Resistor

BJT $R_f > 0.$

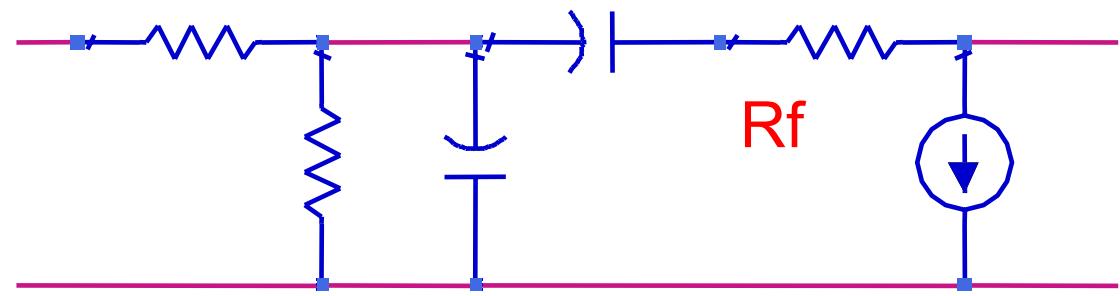

FET $R_f < 0.$ (Low Freq.)

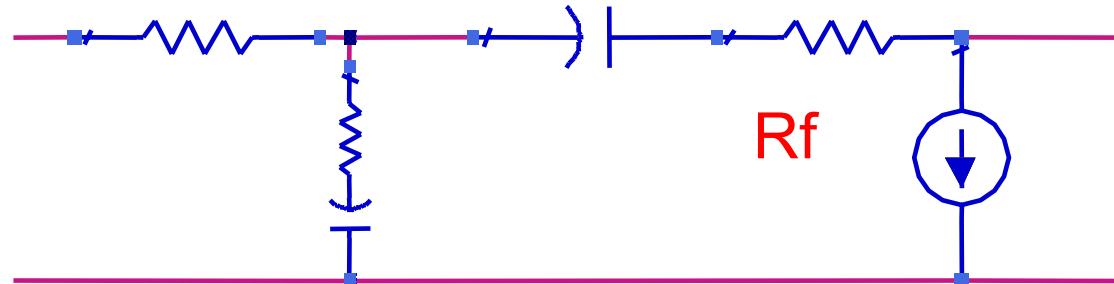

REFERENCES/HISTORY

1. S. J. Mason, "Power Gain in Feedback Amplifiers," Trans. IRE Professional Group on Circuit Theory, vol. CT-1, no. 2, pp. 20-25, June **1954**.
2. C. C. Cheng, "Neutralization and unilateralization," IRE Trans. Circuit Theory, vol. CT-2, no. 2, pp. 138-145, June **1955**.
3. L. Besser, "Stability Consideration of Low-Noise Transistor Amplifiers with Simultaneous Noise and Power Match," MTT Symposium, pp. 327-329, **1975**.
4. G. D. Vendelin, "Feedback Effects on The Noise Performance of GaAs MESFETS," MTT Symposium, pp. 324-326, **1975**.
5. G. D. Vendelin, "Feedback Effects in the GaAs MESFET Model," IEEE Trans. MTT, pp. 383-385, June **1976**.
6. M. S. Gupta, "Power Gain in Feedback Amplifiers, a Classic Revisited," IEEE Trans. MTT, vol. 40, no. 5, pp. 864-879, May **1992**.
7. Y. H. Huang, C. C. Chien, G. D. Vendelin, "Exact Analysis of Maximum Available Gain and Unilateral Gain Including Phase Angle of S21," IEEE Microwave and Wireless Components Letters, March **2003**.
8. G. D. Vendelin, A. M. Pavio, and U. L. Rohde, *Microwave Circuit Design Using Linear and Nonlinear Techniques*, 2ed Edition, Wiley, to be published, **2003**.

Conclusions

- Lossless feedback improves performance of HGA, LNA, & HPA.
- Stability is a biggest issue.
- Read IEEE Microwave Wireless Components Letters, March 2003 for details
- Read 2nd Edition of Wiley Book due Sep. 2003