

IEEE Houston Section Continuing Education On Demand

Seminar

Night 1 and Night 2

Presentation Code: 505

September 29-30, 2015

**Basic Power System and Symmetrical Components Calculations
Review**

BASIC POWER SYSTEM AND SYMMETRICAL COMPONENTS CALCULATIONS - REVIEW

- **Synopsis:**

Electrical Engineering basis of analysis, formulas, data, per unit calculations, “rule of thumb.” Review of Fortescue theory and critical assumptions, unbalance system analysis (faults and voltage unbalance).

Application, concerns and examples. Phase domain analysis of unbalance systems and comparison with Symmetrical Components methodology.

AGENDA

- What are the “power system calculations”
- Why basic calculations/shortcuts?
- Fundamentals
- The Per Unit Method
- Fortescue Theory
- Symmetrical Components
- Faults and Sequence Networks
- Component Modeling
- Phase Domain Modeling
- Where to Find Data for Calculations

**WHAT ARE THE
“POWER SYSTEM CALCULATIONS”**

WHAT ARE THE “POWER SYSTEM CALCULATIONS”

- A **calculation** is a deliberate process for transforming one or more inputs into one or more results, with variable change
- Electrical network (circuits) theory with simplifications or “easy” electrical engineering
- Complex math or degenerated form complex math

**WHY BASIC
CALCULATIONS/SHORTCUTS?**




WHY BASIC CALCULATIONS/SHORTCUTS?

- History
 - Overwhelming
 - Lack of tools
 - Answer: speed and quality
- Approximate solution(s)
- Data interpretation
- Solution evaluation and interpretation

WHY BASIC CALCULATIONS/SHORTCUTS?

Most common causes of errors in circuit analysis:

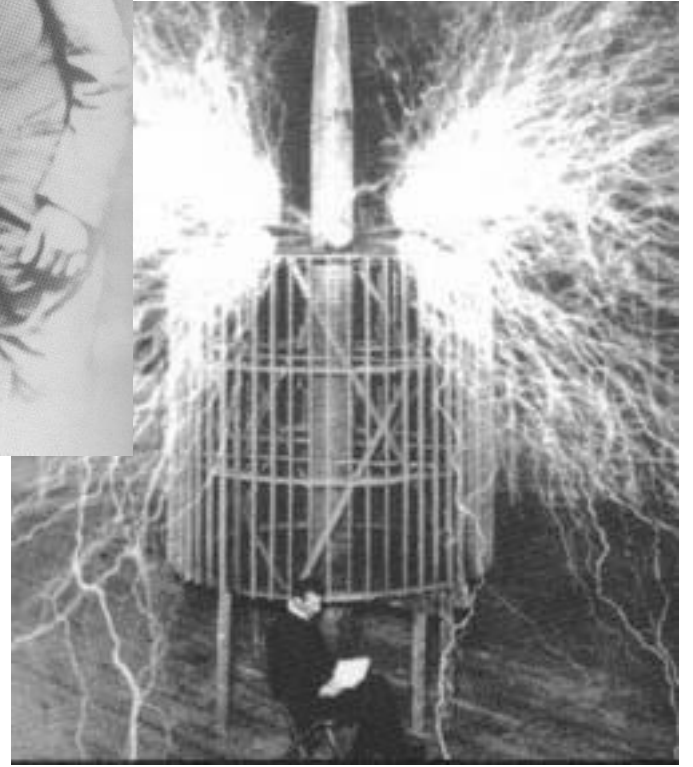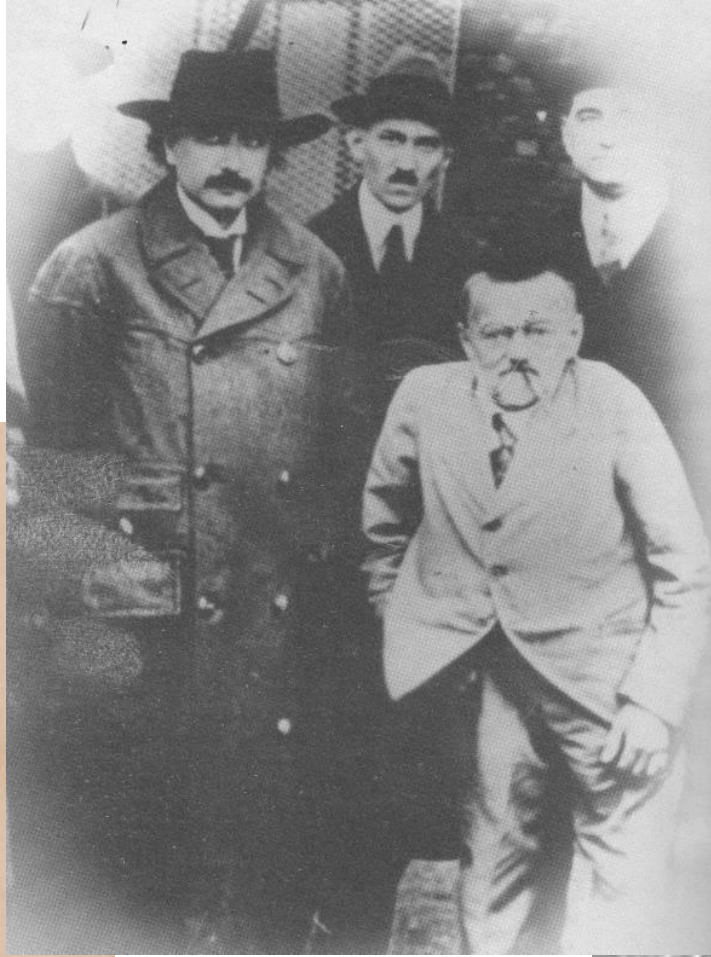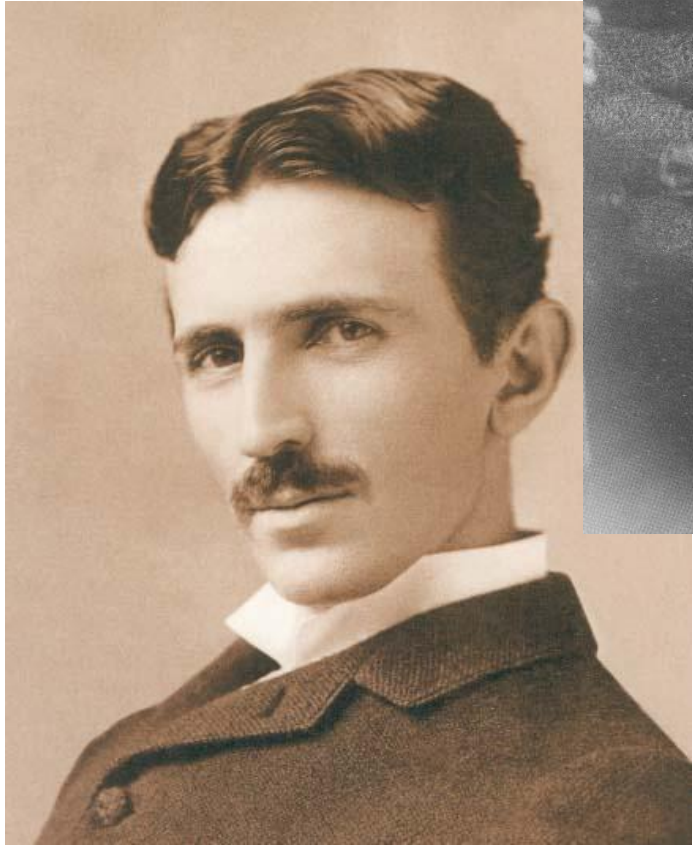- Failure to use a valid analytical procedures
- Misapplication of “cookbook” method(s)
- Improper use of a valid solution method
- Inaccurate simplifying assumption
- Improper model



FUNDAMENTALS

FUNDAMENTALS

- Definitions, acronyms, tagging and symbols
- Linearity and superposition
- Base elements and related equations, Ohm's Law
- Kirchhoff's laws
- The Thevenin and Norton equivalent circuit
- DC and AC
- The per unit method
- The symmetrical components analysis and related
- Some complex math
- The sinusoidal forcing function
- The phasors representation
- The single phase equivalent circuit

DEFINITION ACRONYMS, TAGGING AND SYMBOLS

- $u(t), i(t)$ - instantaneous AC values of voltage and current at particular time t
- $u_{DC}(t), i_{DC}(t)$ - instantaneous DC value of voltage and current at particular time t
- U_m, I_m - root-mean-square (rms), one-cycle values of the sinusoidal voltage and current waveforms, or maximum values
- U, I - root-mean-square (rms) voltage or current; module value of vector
- U_p, I_p - peak or crest (ANSI) voltage
- $\underline{U}, \underline{I}, \underline{S}$ - complex numbers or vectors
- ω - angular line frequency; $\omega = 2 \cdot \pi f$ with $f \equiv 60\text{Hz}$ system frequency for the signal
- α - "shift" angle in relation to assumed origin; in this case it is assumed in relation to voltage; shift depends on type of load (resistive, capacitive, inductive) in the system; negative sign in front of the α reflects assumed convention for the circuit analysis;



$$\alpha = \text{atan}\left(\frac{\omega \cdot L}{R}\right) = \text{atan}\left(\frac{X}{R}\right)$$

DEFINITION ACRONYMS, TAGGING AND SYMBOLS

R, L, C	- lumped resistance, inductance and capacitance
r, l, c	- distributed resistance, inductance and capacitance
j, i	- imaginary operator
η , eff	- efficiency
a	- 120 degree symmetrical component rotational operator
<u>Z</u>	- impedance; complex number (vector) i.e. $\underline{Z} = R + j(X_L - X_C)$
$ \underline{Z} $, Z	- module value of impedance (scalar)
X_C	- capacitive reactance
X_L	- inductive reactance
U_n , I_n	- nominal system or apparatus parameters line-line voltage or line current (ANSI); rating of the system or apparatus are defined in standards - (IEC) nominal system line voltage
U_R , I_R	- (IEC) rated equipment line-line voltage or line current

LINEARITY

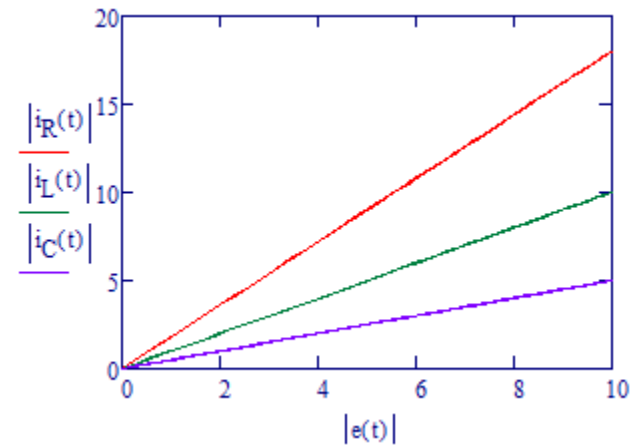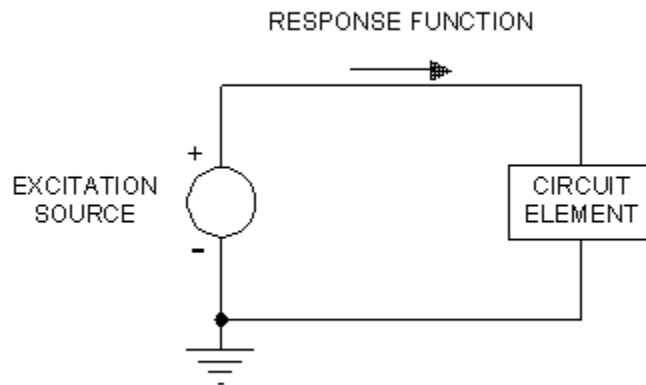
- DC Circuits:
 - The current doubles if the voltage is doubled.
- AC Circuits:
 - The frequency of the driving voltage is held constant, the current doubles if the voltage is doubled.



In this example, excitation is sinusoidal ideal voltage source and circuits elements are resistance, reactance or capacitance.

LINEARITY

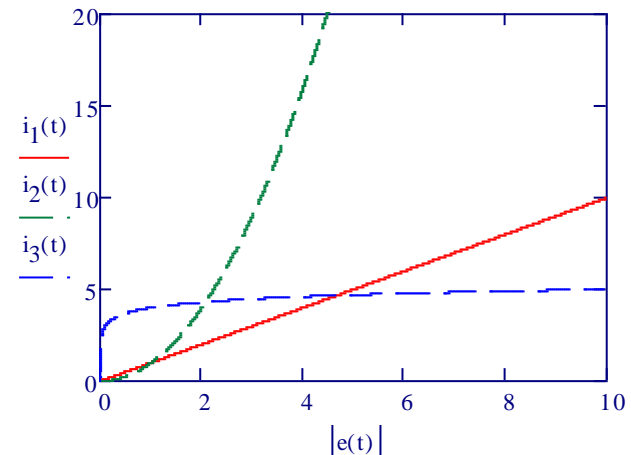- For the chosen excitation function of voltage and the chosen response function of current, both hidden-GREEN and hidden-BLUE are examples of the response characteristic of a nonlinear element.



LINEARITY

- With the circuit element represented by any of the response curves shown in Figures, the circuit will, in general, become nonlinear for a different response function (for example Power)
- An important limitation of linearity, therefore, is that it applies only to responses that are linear for the circuit conditions described (that is, a constant impedance circuit will yield a current that is linear with voltage).
- This restraint must be recognized in addition to the previously mentioned limitations of constant source excitation frequency for AC circuits and constant circuit element impedances for AC or DC circuits. Excitation sources, if not independent, must be linearly dependent. This restraint forces a source to behave just as would a linear response (which, by definition, is also linearly dependent).

SUPERPOSITION

- This very powerful principle is a direct consequence of linearity and can be stated as follows:
 - In any linear network containing several DC or fixed frequency AC excitation sources (voltages), the total response (current) can be calculated by algebraically adding all the individual responses caused by each independent source acting alone. All other sources inactivated (voltage sources shorted by their internal impedances, current sources opened). The equation written is for the sum of the currents from each individual source V_1 and V_2 . Although Figure also illustrates a way this principle might actually be used, more often its main application is in support of other calculating methods. The only restraint associated with superposition is that the network should be linear. All limitations associated with linearity apply.

SUPERPOSITION

- Only applies to linear circuits and elements
- Best explained by example:
 - Example 1

SUPERPOSITION

- Example 1 – AC and AC Sources

$$I_{V1} + I_{V2} = I_L$$

$$I_{V1} = I_{c1}$$


$$I_L = I_{c2}$$

$$\begin{pmatrix} Z_1 + Z_2 & -Z_2 \\ -Z_2 & Z_2 + Z_L \end{pmatrix} \cdot \begin{pmatrix} I_{c1} \\ I_{c2} \end{pmatrix} = \begin{pmatrix} V_1 - V_2 \\ V_2 \end{pmatrix}$$

$$I_{V1} := \frac{V_1}{(Z_1 + \|(Z_2, Z_L))} \cdot \|(Z_2, Z_L) \cdot \frac{1}{Z_L} = 0.667 \text{ A}$$

$$I_{V2} := \frac{V_2}{(Z_2 + \|(Z_1, Z_L))} \cdot \|(Z_1, Z_L) \cdot \frac{1}{Z_L} = 0.333 \text{ A}$$

$$I_L := I_{V1} + I_{V2} = 1 \text{ A}$$

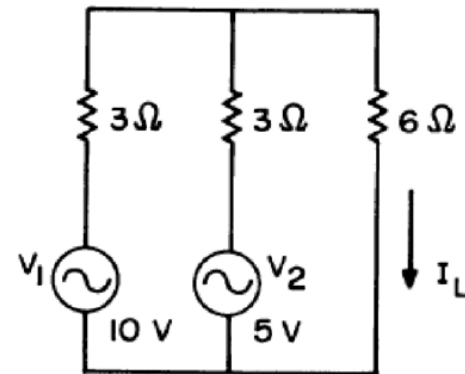

SUPERPOSITION

- The non-applicability of superposition is why all but the very simplest nonlinear circuits are almost impossible to analyze using hand calculations.
- Although most real circuit elements are nonlinear to some extent, they can often be accurately represented by a linear approximation.
- Solutions to network problems involving such elements can be readily obtained. Problems involving complex networks having substantially nonlinear elements can practically be solved only through the use of certain simplification procedures, or **through the adjustment of calculated results to correct for nonlinearity.** **But both of these approaches can potentially lead to significant inaccuracy.** Tiresome iterative calculations performed in an instant by the digital computer make more accurate solutions possible when the nonlinear circuit elements can be described mathematically.

MORE ABOUT LINEARITY

- Linearization makes it possible to use tools for studying linear systems to analyze the behavior of a nonlinear function near a given point with certain restrictions.
- Based on the **Hartman-Grobman** or **Linearization Theorem**, it is an theorem about the local behavior of dynamical systems in the neighborhood of a hyperbolic fixed point.
- In simplicity, the theorem states that the behavior of a dynamical system near a hyperbolic fixed point is qualitatively the same as the behavior of its linearization near the origin. Therefore when dealing with such fixed points we can use the simpler linearization of the system to analyze its behavior.

MORE ABOUT LINEARITY

- Linearization makes it possible to use tools for studying linear systems to analyze the behavior of a nonlinear function near a given point with certain restrictions. The linearization of a function is the first order term of its Taylor expansion around the point of interest.
- For a system defined by the equation,

$$\frac{d\mathbf{x}}{dt} = \mathbf{F}(\mathbf{x}, t)$$

the linearised system can be written as for example

$$\frac{d\mathbf{x}}{dt} = D\mathbf{F}(\mathbf{x}_0, t) \cdot (\mathbf{x} - \mathbf{x}_0)$$


where: x_0 is the point of interest and $DF(x_0, t)$ is the Jacobian of $F(x)$ evaluated at point x_0 .

MORE ABOUT LINEARITY

- Typical power system analysis tools steady-state / approximation of phasor methods i.e. use linearization models that are a simplified differential equation models around operating point of 50 or 60 Hz.
- Only electromagnetic transient software (EMTP) types use nonlinear differential equation for modeling with some approximation for some other attributes to find solution(s).
- How approximation is achieved is shown on example of Synchronous Machine

MORE ABOUT LINEARITY

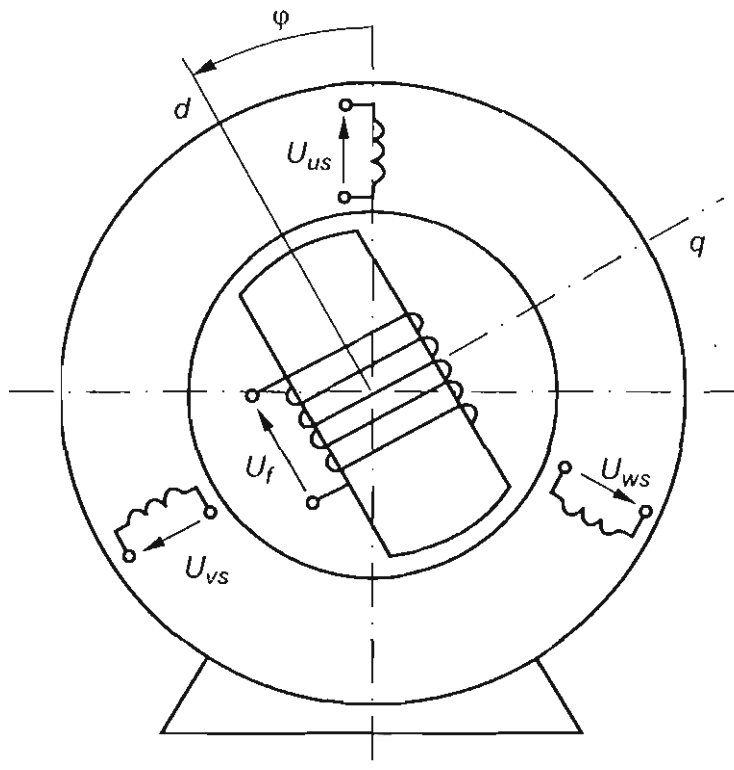- Synchronous Machine - General-Nonlinear Model



$$\mathbf{u}_s = \mathbf{R}_s \mathbf{i}_s + \frac{d}{dt} \mathbf{M}_{ss} \mathbf{i}_s + \frac{d}{dt} \mathbf{M}_{sf} \mathbf{i}_f$$

$$\mathbf{u}_f = \mathbf{R}_f \mathbf{i}_f + \frac{d}{dt} \mathbf{M}_{fs} \mathbf{i}_s + \frac{d}{dt} \mathbf{M}_{ff} \mathbf{i}_f$$

$$J \frac{d^2 \phi}{dt^2} + k_d \frac{d\phi}{dt} = T_m + T_e = T_m + \frac{1}{2} \frac{\partial}{\partial \phi} \left[\mathbf{i}_s^T \mathbf{i}_f \right] \begin{bmatrix} \mathbf{M}_{ss} & \mathbf{M}_{sf} \\ \mathbf{M}_{fs} & \mathbf{M}_{ff} \end{bmatrix} \begin{bmatrix} \mathbf{i}_s \\ \mathbf{i}_f \end{bmatrix}$$

MORE ABOUT LINEARITY

- Synchronous Machine – Park's Model

$$\mathbf{T} = \sqrt{\frac{2}{3}} \begin{bmatrix} \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \cos\varphi & \cos(\varphi - 120^\circ) & \cos(\varphi - 240^\circ) \\ -\sin\varphi & -\sin(\varphi - 120^\circ) & -\sin(\varphi - 240^\circ) \end{bmatrix}$$

$$u_d = R_s i_d + \frac{d}{dt} \psi_d - \dot{\varphi} \psi_q$$

$$u_q = R_s i_q + \frac{d}{dt} \psi_q + \dot{\varphi} \psi_d$$

$$u_f = R_f i_f + \frac{d}{dt} \psi_f$$

$$J \frac{d^2 \varphi}{dt^2} + k_d \frac{d\varphi}{dt} = T_e + T_m$$

$$T_e = \psi_d i_q - \psi_q i_d$$

MORE ABOUT LINEARITY

- Synchronous Machine – Steady State $U_s = \text{const}$

$$i_{us} = \sqrt{\frac{2}{3}}(I_d \cos \varphi - I_q \sin \varphi) = \frac{U_{sm} \cos \vartheta - E_{fm}}{X_d} \cos(\omega_0 t + \varphi_0) + \frac{U_{sm} \sin \vartheta}{X_q} \sin(\omega_0 t + \varphi_0) =$$

$$= \frac{U_{sm} \cos \vartheta - E_{fm}}{X_d} \sin(\omega_0 t + \vartheta) - \frac{U_{sm} \sin \vartheta}{X_q} \cos(\omega_0 t + \vartheta)$$

$$\begin{bmatrix} U_d \\ U_q \end{bmatrix} = \sqrt{\frac{3}{2}} U_{sm} \begin{bmatrix} \sin \vartheta \\ \cos \vartheta \end{bmatrix}$$

$$I_d = \sqrt{\frac{3}{2}} \frac{U_{sm} \cos \vartheta - E_{fm}}{X_d}$$

$$I_q = -\sqrt{\frac{3}{2}} \frac{U_{sm}}{X_q} \sin \vartheta$$

$$J \frac{d^2 \varphi}{dt^2} + k_d \frac{d \varphi}{dt} = T_e + T_m$$

$$T_e = -\frac{1}{\omega_0} \left[\frac{3}{2} \frac{U_{sm} E_{fm}}{X_d} \sin \vartheta + \frac{3}{4} U_{sm}^2 \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\vartheta \right]$$

MORE ABOUT LINEARITY

- Synchronous Machine – Steady State $U_s = \text{const}$

$$i_{us} = \sqrt{\frac{2}{3}}(I_d \cos \varphi - I_q \sin \varphi) = \frac{U_{sm} \cos \vartheta - E_{fm}}{X_d} \cos(\omega_0 t + \varphi_0) + \frac{U_{sm} \sin \vartheta}{X_q} \sin(\omega_0 t + \varphi_0) =$$

$$= \frac{U_{sm} \cos \vartheta - E_{fm}}{X_d} \sin(\omega_0 t + \vartheta) - \frac{U_{sm} \sin \vartheta}{X_q} \cos(\omega_0 t + \vartheta)$$

$$\begin{bmatrix} U_d \\ U_q \end{bmatrix} = \sqrt{\frac{3}{2}} U_{sm} \begin{bmatrix} \sin \vartheta \\ \cos \vartheta \end{bmatrix}$$

$$I_d = \sqrt{\frac{3}{2}} \frac{U_{sm} \cos \vartheta - E_{fm}}{X_d}$$

$$I_q = -\sqrt{\frac{3}{2}} \frac{U_{sm}}{X_q} \sin \vartheta$$


$$J \frac{d^2 \varphi}{dt^2} + k_d \frac{d \varphi}{dt} = T_e + T_m$$

$$T_e = -\frac{1}{\omega_0} \left[\frac{3}{2} \frac{U_{sm} E_{fm}}{X_d} \sin \vartheta + \frac{3}{4} U_{sm}^2 \left(\frac{1}{X_q} - \frac{1}{X_d} \right) \sin 2\vartheta \right]$$

BASE ELEMENTS - INDEPENDENT SOURCES


Voltage

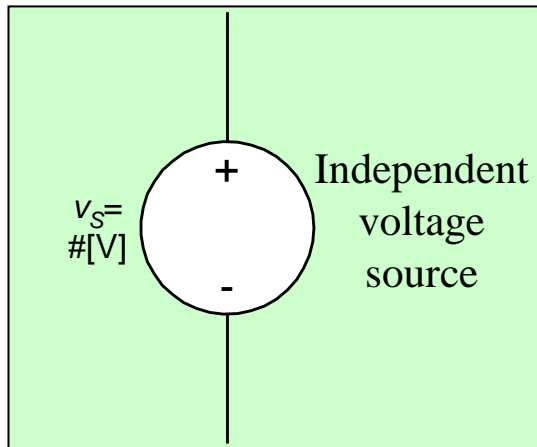- A voltage source maintains a voltage across its terminals no matter what you connect to those terminals



Current

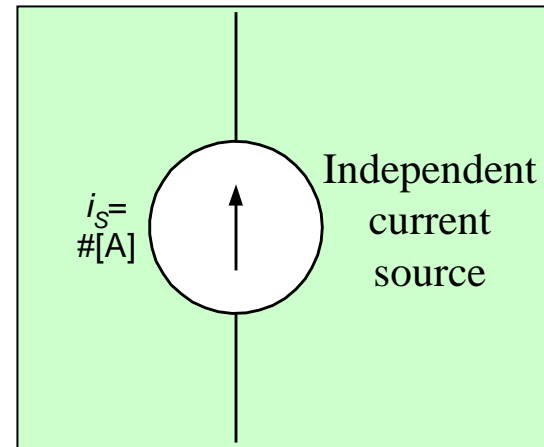- A current source is a two-terminal circuit element that maintains a current through its terminals




BASE ELEMENTS – R, L, C

Resistor

- Obeys the expression

$$R = \frac{v_R}{i_R}$$

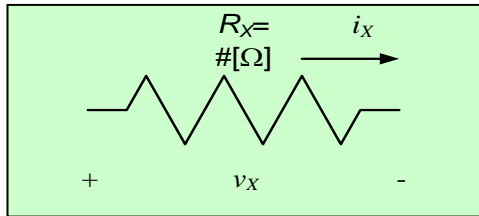


Inductor

- Obeys the expression

$$v_L = L_X \frac{di_L}{dt}$$
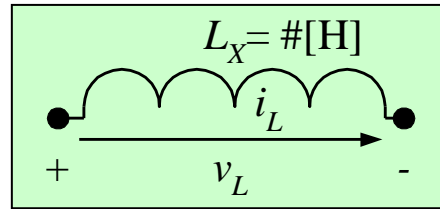
$$i_L(t) = \frac{1}{L_X} \int_{t_0}^t v_L(s) ds + i_L(t_0),$$




v_L is the voltage across the inductor, and i_L is the current through the inductor, L_X is called the inductance, and $i_L(t_0)$ is initial condition

Capacitor

- Obeys the expression

$$i_C = C_X \frac{dv_C}{dt}$$
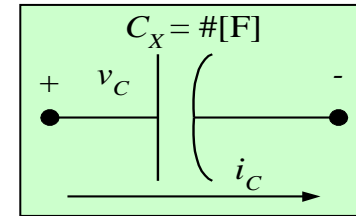
$$v_C(t) = \frac{1}{C_X} \int_{t_0}^t i_C(s) ds + v_C(t_0),$$



v_C is the voltage across the capacitor, and i_C is the current through the capacitor, C_X is called the capacitance, and $v_C(t_0)$ is initial condition

BASE ELEMENTS – R, L, C


Resistor

Inductor


Capacitor

Passive Sign Convention


$$R_X = \frac{v_X}{i_X}$$

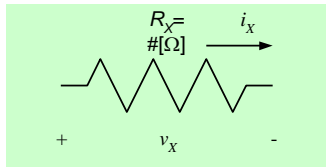

$$v_L = L_X \frac{di_L}{dt}$$

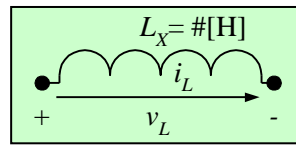


$$i_C = C_X \frac{dv_C}{dt}$$

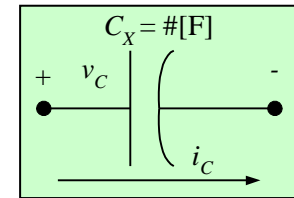


Passive Sign Convention


$$R_X = -\frac{v_X}{i_X}$$

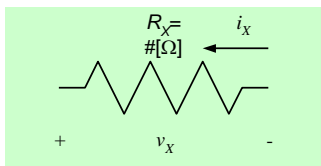

$$v_L = -L_X \frac{di_L}{dt}$$

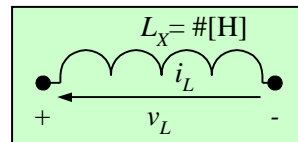

$$i_C = -C_X \frac{dv_C}{dt}$$

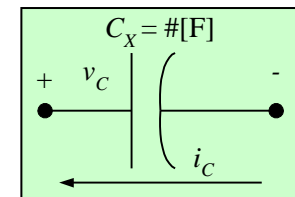

BASE ELEMENTS – R, L, C

Resistor

Inductor

Capacitor

Energy
Stored

N/A

$$W_L = \frac{1}{2} \cdot L_x \cdot i_x^2$$

$$W_C = \frac{1}{2} \cdot C_x \cdot v_x^2$$

Series
Connection

$$R_{EQ} = \sum_{i=1}^N R_i$$

$$L_{EQ} = \sum_{i=1}^N L_i$$

$$\frac{1}{C_{EQ}} = \sum_{i=1}^N \frac{1}{C_i}$$

Parallel
Connection

$$\frac{1}{R_{EQ}} = \sum_{i=1}^N \frac{1}{R_i}$$

$$\frac{1}{L_{EQ}} = \sum_{i=1}^N \frac{1}{L_i}$$

$$C_{EQ} = \sum_{i=1}^N C_i$$

KIRCHHOFF'S LAWS


- Kirchhoff's Current Law (KCL)
 - The algebraic (or signed) summation of currents through any closed surface must equal zero.

- Kirchhoff's Voltage Law (KVL)
 - The algebraic (or signed) summation of voltages around any closed loop must equal zero.

KIRCHHOFF'S LAWS

- Node
- Close Loop

- Example 1
- Example 2

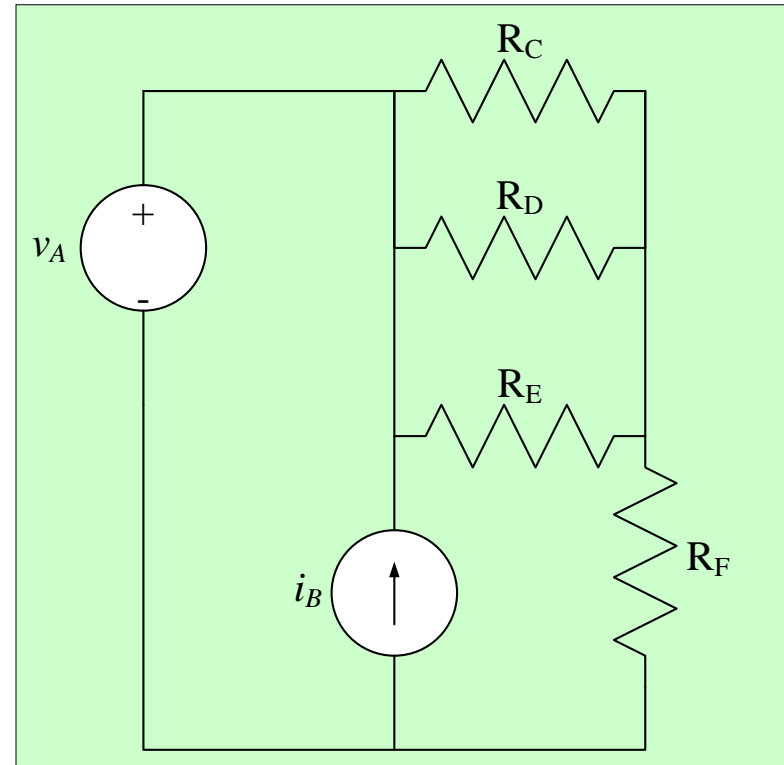


THE THEVENIN AND NORTON EQUIVALENT CIRCUITS

- Why?
 - Per unit calcs
 - Symmetrical components calcs
- Example of measurement, expectation, real value and explanation using Thevenin equivalent circuit


THE THEVENIN EQUIVALENT CIRCUITS

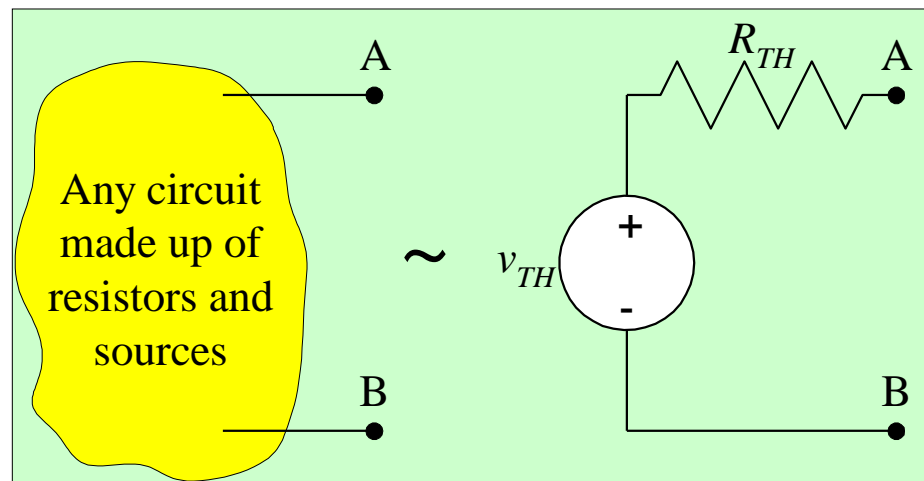- Any circuit made up of resistors and sources, viewed from two terminals of that circuit, is equivalent to a voltage source in series with a resistance.



THE NORTON EQUIVALENT CIRCUITS

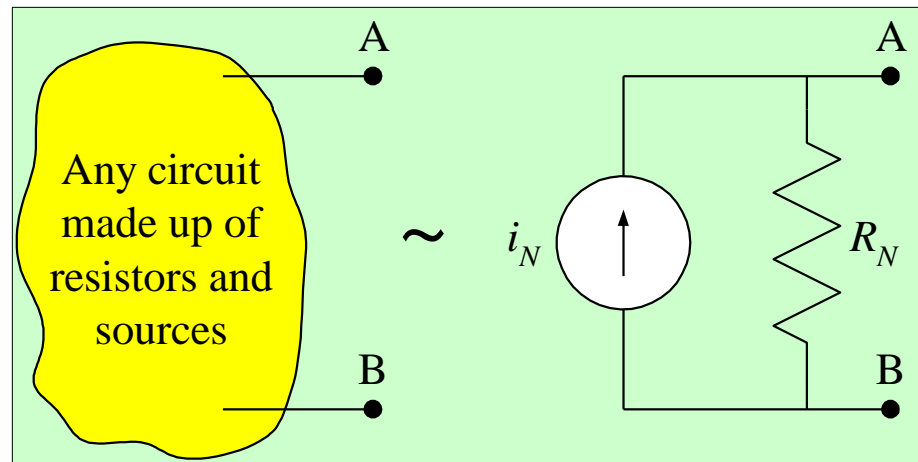- Any circuit made up of resistors and sources, viewed from two terminals of that circuit, is equivalent to a current source in parallel with a resistance.



SINUSOIDAL FORCING FUNCTION


- It is a most fortunate truth in nature that the excitation sources (driving voltage) for electrical networks, in general, have a sinusoidal character and can be represented by a sine wave type periodic functions
- A sinusoid is a *sine wave* or a *cosine wave*
- Sinusoids can represent many functions, but we will concentrate on voltages or currents, as a function of time
- The only restraint associated with the use of the sinusoidal forcing function concept is that the circuit must be comprised of linear elements, that is, R , L , and C are constant as current or voltage varies

SINUSOIDAL FORCING FUNCTION

There are two important consequences of this circumstance:

- First, although the response (current) for a complex R, L, C network represents the solution to at least one second-order differential equation, the result will also be a sinusoid of the same frequency as the excitation and different only in magnitude and phase angle. The relative character of the current with respect to the voltage for simple $R, L,$ and C circuits is also shown in previous figure.
- The second important concept is that when the sine wave shape of current is forced to flow in a general impedance network of $R, L,$ and C elements, the voltage drop across each element will always exhibit a sinusoidal shape of the same frequency as the source. The sinusoidal character of all the circuit responses makes the application of the superposition technique to a network with multiple sources surprisingly manageable. The necessary manipulation of the sinusoidal terms is easily accomplished using the laws of vector algebra.

SINUSOIDAL FORCING FUNCTION

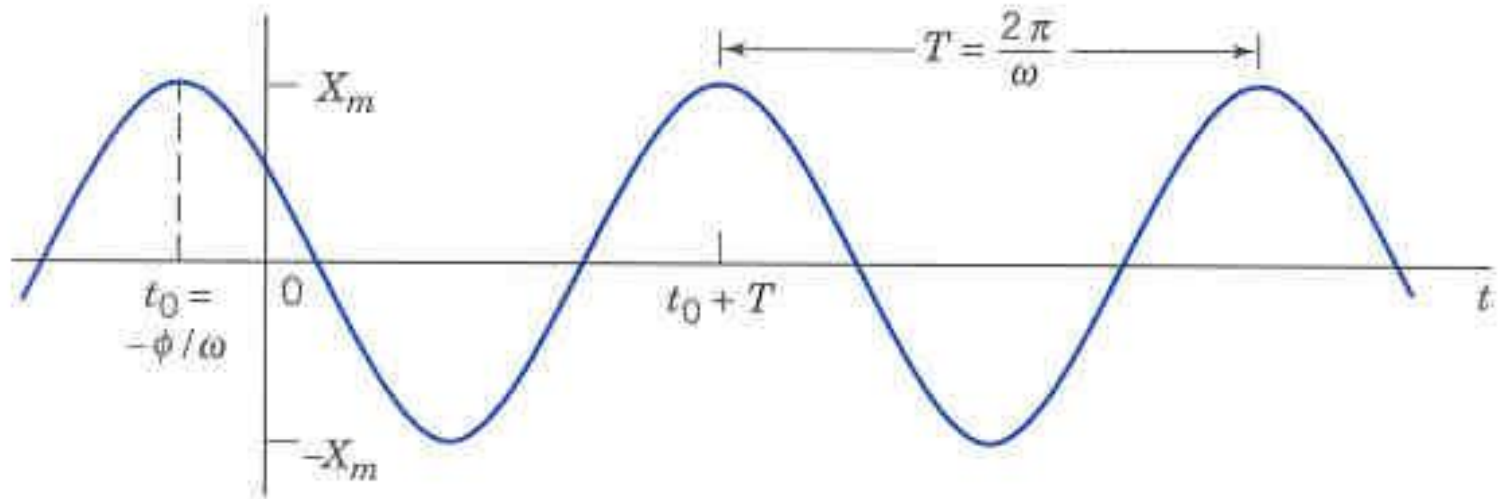


$$x(t) = X_m \cos(\omega t + \phi)$$

$$X_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} (x^2(t)) dt}$$

$$X_{rms} = \frac{X_m}{\sqrt{2}}$$

SINUSOIDAL FORCING FUNCTION

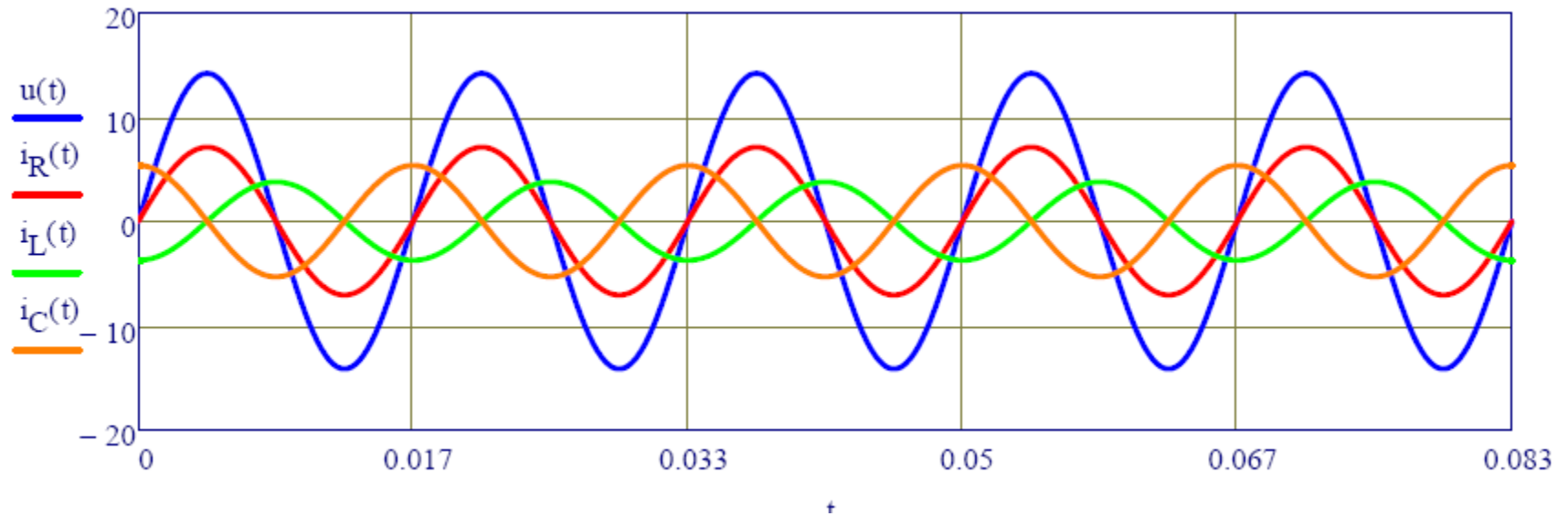

$$u(t) := \sqrt{2} \cdot U \cdot \sin(\omega \cdot t + \Theta)$$

$$i_R(t) := \sqrt{2} \cdot \frac{U}{R} \cdot \sin(\omega \cdot t + \Theta)$$

$$i_L(t) := \sqrt{2} \cdot \frac{U}{\omega \cdot L} \cdot \sin(\omega \cdot t + \Theta - 90\text{deg})$$

$$i_C(t) := \sqrt{2} \cdot U \cdot C \cdot \omega \cdot \sin(\omega \cdot t + \Theta + 90\text{deg})$$

SINUSOIDAL FORCING FUNCTION

- Limits
 - Linear elements
 - Independent on changes in voltage or current
- Results of the calculations contain sine wave type periodic functions
- Frequency of the calculations results sine wave type periodic functions is same as the source frequency

PHASORS

- A phasor is a transformation of a sinusoidal voltage or current to phase (or phasor; complex) domain
- Using phasors, and the techniques of phasor analysis, solving circuits with sinusoidal sources gets much easier, but...
- Only the steady state value of a solution is obtained with the phasor transform technique. Transient nature of sinusoidal voltage or current effect is lost in transformation.


PHASORS

When forcing source is in form

$$v_S(t) = V_m \cos(\omega t + \phi).$$

solution to the circuit equation
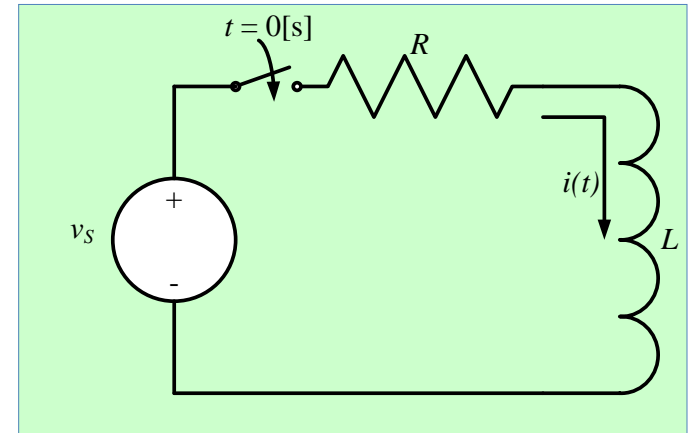
$$V_m \cos(\omega t + \phi) = L \frac{di(t)}{dt} + i(t)R,$$



is in form

$$i(t) = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\phi - \tan^{-1} \frac{\omega L}{R}\right) e^{-\frac{R}{L}t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R}\right).$$

You can note that ***solution varies with time...***

PHASORS

You can note that solution varies with time...

$$i(t) = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\phi - \tan^{-1} \frac{\omega L}{R}\right) e^{-\frac{R}{L}t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R}\right)$$

This part of the solution varies with time as a decaying exponential. In fact, you may recognize that it has a time constant $\tau = L/R$. After several time constants, it will die away and become relatively small. We call this part of the solution the **transient response**.

Only the steady state value of a solution is obtained with the phasor transform technique.

This part of the solution varies with time as a sinusoid. In fact, you may recognize that it is a sinusoid with the same frequency as the source, but with different amplitude and phase. This part of the solution does not die out with time. We call this part of the solution the **steady-state response**.

$$i_{ss}(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R}\right)$$

PHASORS

Instantaneous value representation is not convenient and efficient for analysis of electrical circuits. This is why sinusoidal instantaneous voltages and currents as time functions are usually replaced with the phasor notation.

$$f(t) = K_m \cdot \sin(\omega \cdot t + \Phi) = \sqrt{2} \cdot K \cdot \sin(\omega \cdot t + \Phi) = \text{Im}(\underline{\mathbf{K}} \cdot e^{j \cdot \omega \cdot t})$$

Where:

\mathbf{K} - complex number; note vector notation (underlined \mathbf{K}) with magnitude of $\sqrt{2} \cdot K$ or K_m and phase Φ and is defined as the phasor related to the sinusoidal function $f(t)$, thus

$$\underline{\mathbf{K}} = \sqrt{2} \cdot K \cdot (\cos(\Phi) + j \cdot \sin(\Phi)) = (\sqrt{2}K) (\sphericalangle) \Phi$$

In new format, current and voltage time function are represented by complex vectors in following way:

$$\underline{\mathbf{U}} = U (\sphericalangle) \Phi_u$$

$$\underline{\mathbf{I}} = I (\sphericalangle) \Phi_i$$

PHASORS

Consequently impedance is defined as:

$$\underline{Z} = \frac{\underline{U}}{\underline{I}} = \frac{[U (\angle) \Phi_u]}{[I (\angle) \Phi_i]}$$

and power is defined as:

$$\underline{S} = \underline{U} \cdot \bar{\underline{I}} = [U (\angle) \Phi_u] \cdot [I (\angle) -\Phi_i] = U \cdot I \cdot \cos(\Phi_u - \Phi_i) + j \cdot U \cdot I \cdot \sin(\Phi_u - \Phi_i)$$

with module value equal to:

$$|\underline{S}| = \sqrt{[(U \cdot I \cdot \cos(\Phi_u - \Phi_i))]^2 + [(j \cdot U \cdot I \cdot \sin(\Phi_u - \Phi_i))]^2} = S = U \cdot I$$

$$S^2 = P^2 + Q^2$$

and definition of the power factor:

$$\text{PF} = \cos(\Phi_u - \Phi_i) = \frac{P}{S}$$

PHASORS

For sinusoidal function

$$u(t) := \sqrt{2} \cdot 10 \cdot \sin(\omega \cdot t + \theta) \text{ with phase shift angle } \theta := -35\text{deg}$$

and applying transformation to complex domain (i.e. ignore rotating time space vector represented by $e^{j \cdot \omega \cdot t}$ from equation:



$$f(t) = \sqrt{2} \cdot U \cdot \sin(\omega \cdot t + \theta) = \text{Im}(\underline{U} \cdot e^{j \cdot \omega \cdot t}) = \text{Im}\left[\left[(\sqrt{2}U) \angle \theta\right] \cdot e^{j \cdot \omega \cdot t}\right]$$

we obtain following:

$$\underline{U} := \left(\text{z2r}\theta\left(\sqrt{2} \cdot 10 \cdot e^{-j \cdot 15\text{deg}}\right) \right) = "(10.8847 \angle -57.3^\circ)"$$

$$\underline{U} := \sqrt{2} \cdot 10 \cdot e^{-j \cdot \theta} = 11.5846 + 8.1116j$$

PHASORS

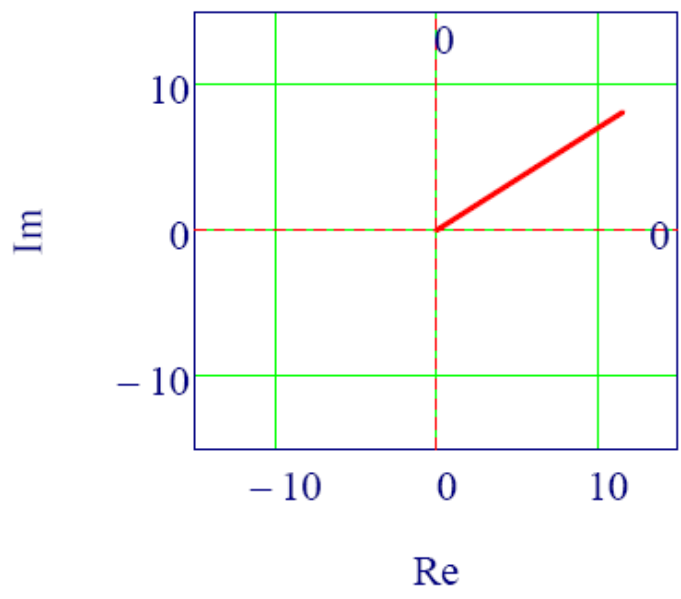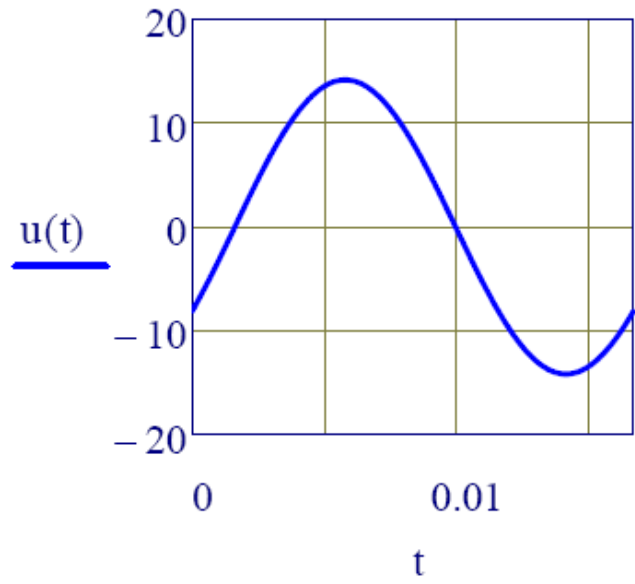


THE SINGLE-PHASE EQUIVALENT CIRCUIT


- Powerful tool for simplifying the analysis of balanced three-phase circuits, yet its restraints are probably most often disregarded. Its application is best understood by examining a three-phase diagram of a simple system and its single-phase equivalent.
- If a three-phase system has a perfectly balanced symmetrical source excitation (voltage) and load, as well as equal series and shunt system and line impedances connected to all three phases, imagine a conductor (shown as a dotted line) carrying no current connected between the effective neutrals of the load and the source. Under these conditions, the system can be accurately described by single phase equivalent

THE SINGLE-PHASE EQUIVALENT CIRCUIT


- Three Phase Diagram

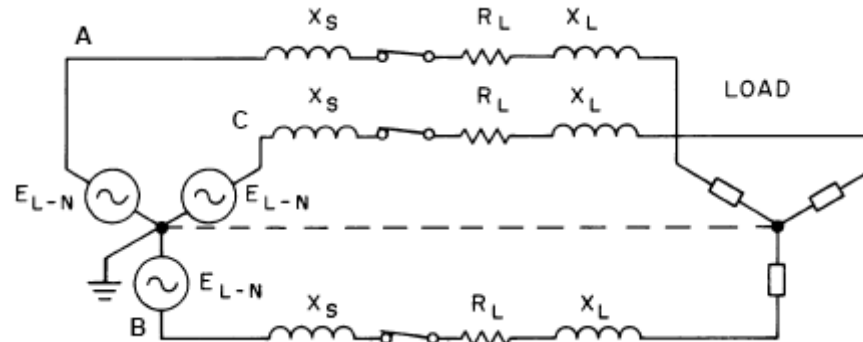

- Simplification / diagrams

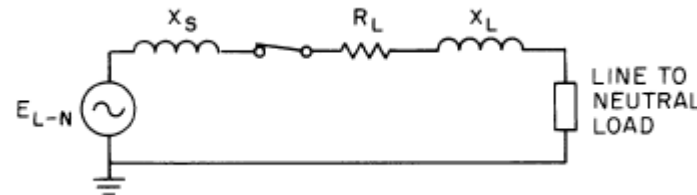

Single Phase Equivalent

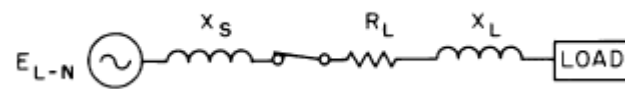


Single Line Impedance Diagram

THE SINGLE-PHASE EQUIVALENT CIRCUIT


- The single-phase equivalent circuit is particularly useful since the solution to the classical loop equations is much easier to obtain than for the more complicated three-phase network. To determine the complete solution, it is only necessary to realize that the other two phases will have responses that are shifted by 120° and 240° but are otherwise identical to the reference phase.
- Anything that upsets the balance of the network renders the model **invalid**. A subtle way this might occur during asymmetrical faults.
- Neither the single-phase equivalent nor the single-line diagram representation is valid when unbalance or asymmetry occurs.
- The single-phase and the single-line diagram representations would imply that the load has been disconnected, it continues to be energized by single-phase power. This can cause serious damage to motors and result in unacceptable operation of certain load apparatus.

THE SINGLE-PHASE EQUIVALENT CIRCUIT


- Three Phase Diagram

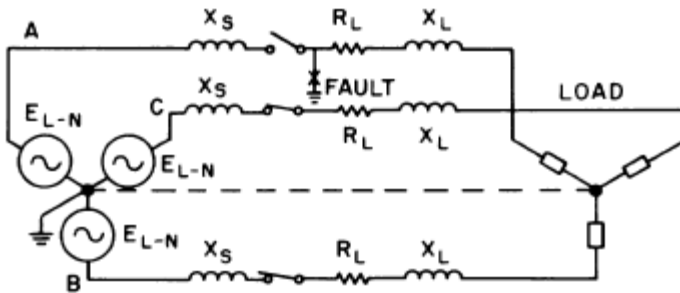

- Single Phase Equivalent

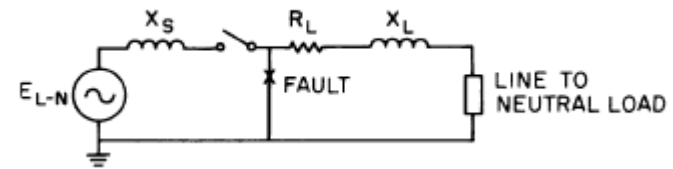

- Single Line Impedance Diagram

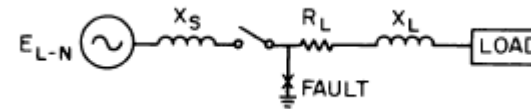

THE SINGLE-PHASE EQUIVALENT CIRCUIT

- Restraints for this calculations:
 - Symmetry of the electrical system, including all switching devices and applied load.
 - Any of the other previously described restraints that apply to the analytical technique being used in combination with the single-phase equivalent.

THE PER UNIT METHOD

THE PER UNIT METHOD

- Definition:

A **per-unit system** is the expression of system quantities as fractions of a defined base unit quantity of the same type.

$$\text{system quantity [pu]} = \frac{\text{system quantity [in actual unit]}}{\text{system quantity}_{base} \text{ [in actual unit]}}$$

System quantities are power, voltage, current, frequency, impedance, admittance, torque, inertia etc.

THE PER UNIT METHOD

- Advantages Of Per Unit

- *Equipment Parameters.* For a given type of equipment, and disregarding the size and voltage, the parameters in per unit are within a narrow, known range
- *Eliminate Turn Ratio.* For two adjacent networks of different voltage levels, if the selected base power is the same throughout and the selected base voltages match the turn ratio of the transformer between the networks, then all quantities in per unit have the same value regardless of which voltage level they are defined. In essence, the transformer is eliminated.
- *Eliminate Coefficients.* For almost all equations with quantities defined in per unit, the numerical coefficients are eliminated.
- *Voltage.* In per unit, the line-to-neutral voltage equals the phase-to-phase voltage, and during normal operation both quantities are close to unity.

THE PER UNIT METHOD

- Per unit conversion requires us to select a base quantities
- How do we make the selection?
 - Answer: Select two quantities as the base from the following: voltage, current, power, impedance, admittance
- Which do we choose?
 - Answer: Generally choose voltage and power.

THE PER UNIT METHOD

- Why Voltage and Power?
 - *Voltage.* For each voltage level in our system, we know the rated voltage of equipment, and even if loading changes, the voltage does not deviate too much from the rated value.
 - *Power.* The range of power flowing in a section of the system is quadratically related with the voltage. As such, the range of expected power flow is known for an area. Note, for transmission level analysis, it is customary to select a base power of 100 MVA.

Note: The base power is usually selected to be the same for the entire network.

THE PER UNIT METHOD

- Select base quantities

$$V_{base} = V_{phase-phase}$$

$$S_{base} = S_{3phase}$$

- Voltage:

- Usually selected as the nominal phase-to-phase voltage at each voltage level

- Power:

- Usually selected in the range of 3-phase power flowing in the network (i.e. whatever network is being analyzed)
- It is customary to select a base power of 10 or 100 MVA.
- The base power is usually selected to be the same for the entire network.

THE PER UNIT METHOD

- Conversion

- Each piece of equipment is different
- Selection of base quantities could be different
- Analysis requires common base

- Power Conversion

$$S_{new.base} [pu] = S_{old.base} [pu] * \frac{S_{old.base} [in\ actual\ units]}{S_{new.base} [in\ actual\ units]}$$

- Impedance Conversion

$$Z_{new.base} [pu] = Z_{old.base} [pu] * \frac{Z_{old.base} [\Omega]}{Z_{new.base} [\Omega]}$$

$$Z_{new.base} [pu] = Z_{old.base} [pu] * \left(\frac{V_{old.base} [V]}{V_{new.base} [V]} \right)^2 * \left(\frac{S_{new.base} [VA]}{S_{old.base} [VA]} \right)$$

THE PER UNIT METHOD

Single phase 1ϕ power and voltage case

$$U_{\text{base}} \equiv 69\text{kV}$$

$$S_{\text{base}} \equiv 100\text{MVA} \quad P_{\text{base}} := S_{\text{base}}$$

$$Q_{\text{base}} := P_{\text{base}}$$

$$I_{\text{base}} := \frac{S_{\text{base}}}{U_{\text{base}}}$$

$$Z_{\text{base}} := \frac{U_{\text{base}}}{I_{\text{base}}}$$

$$Z_{\text{base}} := \frac{U_{\text{base}}^2}{S_{\text{base}}}$$

$$Y_{\text{base}} := Z_{\text{base}}^{-1}$$

$$Z_{\text{pu}}(Z_{\Omega}) := \frac{Z_{\Omega}}{Z_{\text{base}}}$$

$$Y_{\text{pu}}(Y_S) := \frac{Y_S}{Y_{\text{base}}}$$

$$I_{\text{pu}}(I_A) := \frac{I_A}{I_{\text{base}}}$$

$$U_{\text{pu}}(U_V) := \frac{U_V}{U_{\text{base}}}$$

$$P_{\text{pu}}(P_W) := \frac{P_W}{S_{\text{base}}}$$

$$Q_{\text{pu}}(Q_{\text{VAr}}) := \frac{Q_{\text{VAr}}}{S_{\text{base}}}$$

$$S_{\text{pu}}(S_{\text{VA}}) := \frac{S_{\text{VA}}}{S_{\text{base}}}$$

THE PER UNIT METHOD

EXAMPLE:

An impedance $\underline{Z} := (2 + 2j)\Omega$ is connected to a single phase circuit with following parameters: base power $S_b := 5000\text{kVA}$ and base voltage $U_b := 10\text{kV}$. Calculate I_b , Z_b and $\underline{Z}_{\text{pu}}$ of circuit and connected impedance.

Solution:

$$I_b := \frac{S_b}{U_b} = 500 \text{ A}$$
$$Z_b := \frac{U_b}{I_b} = 20 \Omega$$
$$\underline{Z}_{\text{pu}} := \frac{\underline{Z}}{Z_b} = (0.1 + 0.1j) \cdot \text{pu}$$

THE PER UNIT METHOD

EXAMPLE:

Data for following single phase circuit is:

$$S_b := 5\text{MVA}$$


$$U_p := 1000\text{V}$$

$$Z_p = 20\Omega$$

$$U_s := 100\text{V}$$

$$Z_s := 0.8\Omega$$

Calcualte: I_{p_pu} , I_{s_pu}

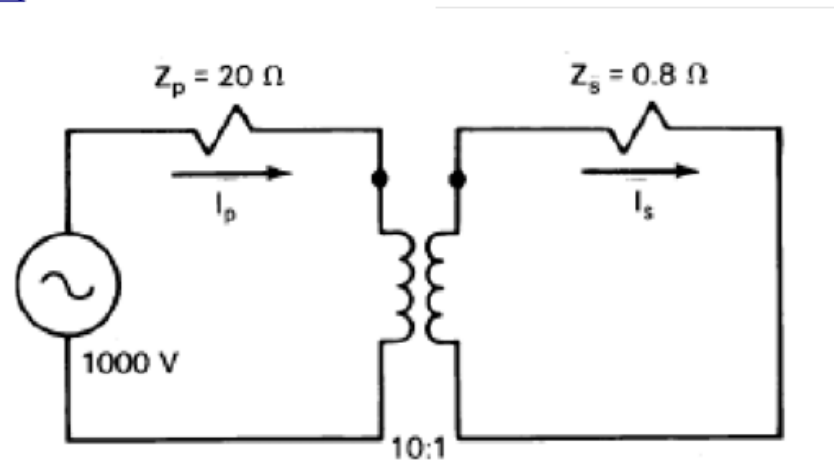

THE PER UNIT METHOD

Solution:

$$S_b = 5 \cdot \text{MVA}$$

$$U_{b_P} := U_P$$

$$Z_{b_P} := \frac{U_{b_P}^2}{S_b} = 0.2 \Omega$$

$$Z_{P_pu} := \frac{Z_P}{Z_{b_P}} = 100 \cdot \text{pu}$$

$$U_{P_pu} := \frac{U_P}{U_{b_P}} = 1.00 \cdot \text{pu}$$

$$I_{b_P} := \frac{S_b}{U_{b_P}} = 5 \cdot \text{kA}$$

$$I_{P_pu} = I_{S_pu} \quad \text{and}$$

$$I_P := I_{P_pu} \cdot I_{b_P} = 10 \text{ A}$$

$$S_b = 5 \cdot \text{MVA}$$

$$U_{b_S} := U_S$$

$$Z_{b_S} := \frac{U_{b_S}^2}{S_b} = 0.002 \Omega$$

$$Z_{S_pu} := \frac{Z_S}{Z_{b_S}} = 400 \cdot \text{pu}$$

$$I_{b_S} := \frac{S_b}{U_{b_S}} = 50 \cdot \text{kA}$$

$$I_{P_pu} := \frac{U_{P_pu}}{Z_{P_pu} + Z_{S_pu}} = 0.002$$

$$I_S := I_{P_pu} \cdot I_{b_S} = 100 \text{ A}$$

THE PER UNIT METHOD

Three phase 3 ϕ power and voltage case

Relating to equations for 1 ϕ

$$S_{\text{base}} = 3 \cdot U_{\text{base_phase}} \cdot I_{\text{base_phase}}$$

"...customarily, rated kVA is given for the three phases and rated voltage is line-to-line voltage." *per E. Clarke*

$$U_{\text{base}} = U_{\text{LL}} \quad I_{\text{base}} = I_{\text{L}}$$

$$S_{\text{base}} = \sqrt{3} \cdot U_{\text{base}} \cdot I_{\text{base}}$$

$$I_{\text{base}} := \frac{S_{\text{base}}}{\sqrt{3} \cdot U_{\text{base}}}$$

$$Z_{\text{base}} := \frac{\left(\frac{U_{\text{base}}}{\sqrt{3}} \right)^2}{\frac{S_{\text{base}}}{3}}$$

THE PER UNIT METHOD

$$Z_{\text{base}} := \frac{U_{\text{base}}^2}{S_{\text{base}}}$$

$$Y_{\text{base}} := Z_{\text{base}}^{-1}$$

$$Z_{\text{pu}}(Z_{\Omega}) := \frac{Z_{\Omega}}{Z_{\text{base}}}$$

$$Y_{\text{pu}}(Y_S) := \frac{Y_S}{Y_{\text{base}}}$$

$$I_{\text{pu}}(I_A) := \frac{I_A}{I_{\text{base}}}$$

$$U_{\text{pu}}(U_V) := \frac{U_V}{U_{\text{base}}}$$

$$P_{\text{pu}}(P_W) := \frac{P_W}{S_{\text{base}}}$$

$$Q_{\text{pu}}(Q_{\text{VAr}}) := \frac{Q_{\text{VAr}}}{S_{\text{base}}}$$

$$S_{\text{pu}}(S_{\text{VA}}) := \frac{S_{\text{VA}}}{S_{\text{base}}}$$


$$Z_{\text{new}} = Z_{\text{old}} \cdot \left(\frac{U_{\text{old}}}{U_{\text{new}}} \right)^2 \cdot \frac{S_{\text{new}}}{S_{\text{old}}}$$

THE PER UNIT METHOD

Example

This is a multiple stage example. For the system shown below:

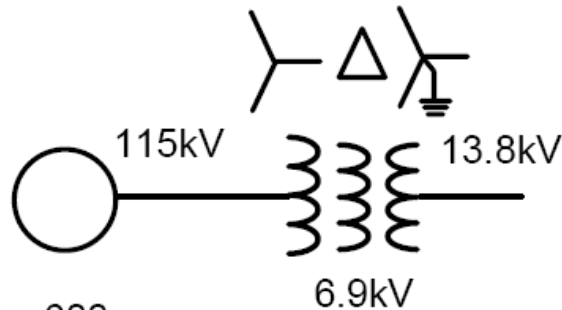- a. Determine the source and equivalent star reactances of the transformer on a 30 MVA base.



$MVA_{sc}=600$

$X_{hx}=10\%$ on 30MVA

$X_{hy}=22.5\%$ on 15MVA

$X_{xy}=10\%$ on 10MVA

$h=115kV, x = 13.8kV, y = 6.9kV$

Source Data (at 115kV):

$MVA_{sc} := 600MVA$

Transformer data:

$S_b := 30MVA$

$V_{b_h} := 115kV$

$V_{b_y} := 6.9kV$

$V_{b_x} := 13.8kV$

THE PER UNIT METHOD

Compute Source Impedance:

Two options to compute per unit source impedance:

$$X_{\text{source_pu}} := \frac{S_b}{\text{MVA}_{\text{sc}}} = 0.05 \text{ pu}$$

$$X_{\text{source}} := \frac{(115\text{kV})^2}{\text{MVA}_{\text{sc}}} = 22.042 \Omega$$

$$Z_{b_h} := \frac{V_{b_h}^2}{S_b} = 440.833 \Omega$$

$$X_{s_pu} := \frac{X_{\text{source}}}{Z_{b_h}} = 0.05 \text{ pu}$$

Note that:

$$X_{s_pu} = \frac{\frac{(115\text{kV})^2}{\text{MVA}_{\text{sc}}}}{\frac{V_{b_h}^2}{S_b}} = \frac{S_b}{\text{MVA}_{\text{sc}}}$$

Compute Transformer Impedances for T-equivalent:

$$X_{h_x} := 0.1 \text{ pu}$$

$$S_{b_hx} := 30 \text{ MVA}$$

$$X_{h_y} := 0.225 \text{ pu}$$

$$S_{b_hy} := 15 \text{ MVA}$$

$$X_{x_y} := 0.11 \text{ pu}$$

$$S_{b_xy} := 10 \text{ MVA}$$

THE PER UNIT METHOD

Change of MVA base calculations.

$$X_{hx_pu} := \frac{S_b}{S_{b_hx}} \cdot X_{h_x} \quad X_{hx_pu} = 0.1 \text{ pu}$$

$$X_{hy_pu} := \frac{S_b}{S_{b_hy}} \cdot X_{h_y} \quad X_{hy_pu} = 0.45 \text{ pu}$$

$$X_{xy_pu} := \frac{S_b}{S_{b_xy}} \cdot X_{x_y} \quad X_{xy_pu} = 0.33 \text{ pu}$$

Find Z_h , Z_x and Z_y

$$X_h := (0.5) \cdot (X_{hy_pu} + X_{hx_pu} - X_{xy_pu}) \quad X_h = 0.11 \text{ pu}$$

$$X_x := (0.5) \cdot (X_{hx_pu} + X_{xy_pu} - X_{hy_pu}) \quad X_x = -0.01 \text{ pu}$$

$$X_y := (0.5) \cdot (X_{xy_pu} + X_{hy_pu} - X_{hx_pu}) \quad X_y = 0.34 \text{ pu}$$

Use the same values for the positive, negative and zero sequence networks.

THE PER UNIT METHOD

B. Sequence Networks: Ignore loads. Include impact of delta tertiary winding and ungrounded Y on 115kV.

$$X_1 := X_{s_pu} + X_h + X_x \quad X_1 = 0.15 \text{ pu}$$

$$X_2 := X_{s_pu} + X_h + X_x \quad X_2 = 0.15 \text{ pu}$$

$$X_0 := X_y + X_x \quad X_0 = 0.33 \text{ pu}$$

C. Three phase fault currents at 13.8 kV terminals (ignore load)

$$V_f := j \cdot 1.0 \text{ pu}$$

$$I_{af} := \frac{V_f}{j \cdot X_1} \quad I_{af} = 6.667 \text{ pu}$$

Positive Sequence Rotation:

$$I_{abc} := I_{af} \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} \quad \overrightarrow{|I_{abc}|} = \begin{pmatrix} 6.667 \\ 6.667 \\ 6.667 \end{pmatrix} \quad \overrightarrow{\arg(I_{abc})} = \begin{pmatrix} 0 \\ -120 \\ 120 \end{pmatrix} \text{ deg}$$

THE PER UNIT METHOD

D. SLG fault at 13.8kV terminals

$$I_0 := \frac{V_f}{j \cdot X_1 + j \cdot X_2 + j \cdot X_0}$$

$$I_0 = 1.587 \text{ pu}$$

$$I_1 := I_0$$

$$I_2 := I_0$$

$$I_{abc_SLG} := A \cdot \begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix}$$

$$\overrightarrow{|I_{abc_SLG}|} = \begin{pmatrix} 4.762 \\ 0 \\ 0 \end{pmatrix}$$

$$\overrightarrow{\arg(I_{abc_SLG})} = \begin{pmatrix} 0 \\ 116.565 \\ 116.565 \end{pmatrix} \text{ deg}$$

$$I_{b_x} := \frac{S_b}{\sqrt{3} \cdot V_{b_x}} = 1255.109 \text{ A} \quad I_{a_x} := I_{abc_SLG_0} \cdot I_{b_x}$$

$$|I_{a_x}| = 5976.711 \text{ A}$$

E. Phase to neutral voltages at fault

$$V_1 := V_f - j \cdot X_1 \cdot I_1$$

$$V_1 = 0.762i \text{ pu}$$

$$V_0 := -j \cdot X_0 \cdot I_0$$

$$V_0 = -0.524i \text{ pu}$$

$$V_2 := -j \cdot X_2 \cdot I_2$$

$$V_2 = -0.238i \text{ pu}$$

$$V_{abcSLG} := A \cdot \begin{pmatrix} V_0 \\ V_1 \\ V_2 \end{pmatrix}$$

$$\overrightarrow{|V_{abcSLG}|} = \begin{pmatrix} 0 \\ 1.169 \\ 1.169 \end{pmatrix}$$

$$\overrightarrow{\arg(V_{abcSLG})} = \begin{pmatrix} -90 \\ -42.216 \\ -137.784 \end{pmatrix} \text{ deg}$$

THE PER UNIT METHOD

F. Find the phase currents and phase to neutral voltages on the 115kV side of the transformer.

Now $I_0 := 0$ pu since neutral of the Y is ungrounded. I1 and I2 unaffected.

$$I_{abcSLG} := A \cdot \begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix} \quad \overrightarrow{|I_{abcSLG}|} = \begin{pmatrix} 3.175 \\ 1.587 \\ 1.587 \end{pmatrix} \quad \overrightarrow{\arg(I_{abcSLG})} = \begin{pmatrix} 0 \\ 180 \\ 180 \end{pmatrix} \text{deg}$$

$$I_{b_h} := \frac{S_b}{\sqrt{3} \cdot V_{b_h}} \quad I_{a_h} := I_{b_h} \cdot I_{abcSLG_0} \quad |I_{a_h}| = 478.137 \text{ A}$$

$$V_1 := V_f - j \cdot X_{s_pu} \cdot I_1 \quad V_1 = 0.921 \text{ i pu}$$

$$V_2 := -j \cdot X_{s_pu} \cdot I_2 \quad V_2 = -0.079 \text{ i pu}$$

$$V_0 := -j \cdot X_0 \cdot I_0 \quad V_0 = 0 \text{ pu}$$

$$V_{abcSLG} := A \cdot \begin{pmatrix} V_0 \\ V_1 \\ V_2 \end{pmatrix} \quad \overrightarrow{|V_{abcSLG}|} = \begin{pmatrix} 0.841 \\ 0.963 \\ 0.963 \end{pmatrix} \quad \overrightarrow{\arg(V_{abcSLG})} = \begin{pmatrix} 90 \\ -25.906 \\ -154.094 \end{pmatrix} \text{deg}$$

THE PER UNIT METHOD

G. Current in the delta for the fault on 13.8kV bus

$$I_0 := I_1 \quad I_1 := 0 \text{ pu} \quad I_2 := 0$$

$$I_{abcSLG} := A \cdot \begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix} \quad \overrightarrow{|I_{abcSLG}|} = \begin{pmatrix} 1.587 \\ 1.587 \\ 1.587 \end{pmatrix} \quad \overrightarrow{\arg(I_{abcSLG})} = \begin{pmatrix} 0 \\ 0 \\ 0 \end{pmatrix} \text{ deg}$$

$$I_b := \frac{S_b}{3 \cdot V_{b_y}} = 1449.275 \text{ A} \quad I_b \cdot I_0 = 2300.437 \text{ A} \quad I_{a_y} := I_b \cdot I_0 = 2300.437 \text{ A}$$

THE PER UNIT METHOD

H. Make an ampere-turn check for the currents in the windings

$$N1 \cdot I1 + N2 \cdot I2 + N3 \cdot I3 = 0$$

$$N_{h_h} := \frac{115}{115} \quad N_{h_h} = 1$$

$$N_{h_y} := \frac{6.9}{\frac{115}{\sqrt{3}}} \quad N_{h_y} = 0.104$$

$$N_{h_x} := \frac{\frac{13.8}{\sqrt{3}}}{\frac{115}{\sqrt{3}}} \quad N_{h_x} = 0.12$$

$$At_{115} := N_{h_h} \cdot |I_{a_h}| \quad At_{115} = 478.137 \text{ A}$$

$$At_{13.8} := N_{h_x} \cdot |I_{a_x}| \quad At_{13.8} = 717.205 \text{ A}$$

$$At_{6.9} := N_{h_y} \cdot |I_{a_y}| \quad At_{6.9} = 239.068 \text{ A}$$

$$\text{Sum} := At_{115} - At_{13.8} + At_{6.9}$$

$$\text{Sum} = 0 \text{ A}$$

FORTESCUE THEORY



FORTESCUE THEORY

- Fortescue presented paper⁽¹⁾ demonstrating that an unbalanced set of N phasors in any polyphase system could be expressed as the sum of N-1 balanced N-phase systems of different phase sequence and one zero-phase sequence system. Set of phase-sequence system is known as symmetrical components set for a three phase system.
- The paper⁽¹⁾ was judged to be the most important power engineering paper in the twentieth century.
- Note: three phase system is a special case of a polyphase signal

(1) Fortescue, Charles. L. "Method of Symmetrical Co-Ordinates Applied to the Solution of Polyphase Networks" , AIEE Transactions, *vol. 37, part II, pages 1027-1140 (1918)*. Annual convention of the AIEE (American Institute of Electrical Engineers).

URL: <http://www.energyscienceforum.com/files/fortescue/methodofsymmetrical.pdf>

SYMMETRICAL COMPONENTS

SYMMETRICAL COMPONENTS

- What are Symmetrical Components?
 - Any set of N *unbalanced phasors* — that is, any such “polyphase” signal — can be expressed as the sum of N symmetrical sets of balanced phasors.
 - Only a single frequency component is represented by the phasors. This is overcome by using techniques such as Fourier or Laplace transforms.
 - Absolutely general and rigorous and can be applied to both steady state and transient problems.
 - It is thoroughly established as preeminently the only effective method of analyzing general polyphase network problems

SYMMETRICAL COMPONENTS

- Three-Phase System Symmetrical Components
 - Three sets of symmetrical components, where each set is referred to as a *sequence*.
 - First set of phasors, called the *positive sequence*, has the same phase sequence as the system under study (say A-B-C)
 - The second set, the *negative sequence*, has the reverse phase sequence (A-C-B)
 - The third set, the *zero sequence*, phasors *A*, *B* and *C* are in phase with each other.
 - Method converts *any set of three phasors* (phase domain) into three sets of *symmetrical phasors*, which makes asymmetric analysis easily achievable.

SYMMETRICAL COMPONENTS

- For three phase system, set of three phasors X_a , X_b , and X_c can be represented as a sum of three sequence vector sets

$$\underline{X}_a = \underline{X}_{a0} + \underline{X}_{a1} + \underline{X}_{a2}$$

$$\underline{X}_b = \underline{X}_{b0} + \underline{X}_{b1} + \underline{X}_{b2}$$

$$\underline{X}_c = \underline{X}_{c0} + \underline{X}_{c1} + \underline{X}_{c2}$$

where

\underline{X}_{a0} , \underline{X}_{b0} , \underline{X}_{c0} - the zero sequence set

\underline{X}_{a1} , \underline{X}_{b1} , \underline{X}_{c1} - the positive sequence set

\underline{X}_{a2} , \underline{X}_{b2} , \underline{X}_{c2} - the negative sequence set

SYMMETRICAL COMPONENTS

- Only one set of sequence values are unique, i.e. for one phase sequences 0, 1, 2 (usually phase A). Remaining phases can be determined from unique sequence.
- In symmetrical components analysis, a complex operator “ λ ” is defined by the Fortescue theory for N-phase system. When applied to three phase (i.e. $n=3$, $i=2$), we define popular notation and manipulation vector “ a ”:

$$\lambda_i = e^{j \cdot \frac{2 \cdot \pi}{n} \cdot (i-1)} = e^{j \cdot \frac{2 \cdot \pi}{3} \cdot (2-1)} = e^{j \cdot \frac{2 \cdot \pi}{3}} = e^{j \cdot 120\text{deg}}$$

- For three phase system

$$\lambda_2 = \underline{a} = e^{j \cdot 120\text{deg}}$$

SYMMETRICAL COMPONENTS

- Some of useful properties of “a” ...

rectangular notation

$$\underline{a} := -\frac{1}{2} + j \cdot \frac{\sqrt{3}}{2} = -0.5 + 0.87i$$

$$\underline{a}^2 = -0.5 - 0.87i$$

$$\underline{a}^3 = 1$$

$$\underline{a}^4 = -0.5 + 0.87i$$

$$\underline{a}^5 = -0.5 - 0.87i$$

$$\underline{a} + \underline{a}^2 + 1 = 0$$

$$\underline{a} + \underline{a}^2 = -1$$

$$\underline{a} - \underline{a}^2 = 1.73i$$

$$\underline{a}^2 - \underline{a} = -1.73i$$

$$1 - \underline{a} = 1.5 - 0.87i$$

$$1 - \underline{a}^2 = 1.5 + 0.87i$$

$$\underline{a} - 1 = -1.5 + 0.87i$$

$$\underline{a}^2 - 1 = -1.5 - 0.87i$$

$$1 + \underline{a} = 0.5 + 0.87i$$

$$1 + \underline{a}^2 = 0.5 - 0.87i$$

polar notation

$$z_{2r\theta}(\underline{a}) = "(1 \angle 120^\circ)"$$

$$z_{2r\theta}(\underline{a}^2) = "(1 \angle -120^\circ)"$$

$$z_{2r\theta}(\underline{a}^3) = "(1 \angle 0^\circ)"$$

$$z_{2r\theta}(\underline{a}^4) = "(1 \angle 120^\circ)"$$

$$z_{2r\theta}(\underline{a}^5) = "(1 \angle -120^\circ)"$$

$$z_{2r\theta}(\underline{a} + \underline{a}^2) = "(1 \angle 180^\circ)"$$

$$z_{2r\theta}(\underline{a} - \underline{a}^2) = "(1.7321 \angle 90^\circ)"$$

$$z_{2r\theta}(\underline{a}^2 - \underline{a}) = "(1.7321 \angle -90^\circ)"$$

$$z_{2r\theta}(1 - \underline{a}) = "(1.7321 \angle -30^\circ)"$$

$$z_{2r\theta}(1 - \underline{a}^2) = "(1.7321 \angle 30^\circ)"$$

$$z_{2r\theta}(\underline{a} - 1) = "(1.7321 \angle 150^\circ)"$$

$$z_{2r\theta}(\underline{a}^2 - 1) = "(1.7321 \angle -150^\circ)"$$

$$z_{2r\theta}(1 + \underline{a}) = "(1 \angle 60^\circ)"$$

$$z_{2r\theta}(1 + \underline{a}^2) = "(1 \angle -60^\circ)"$$


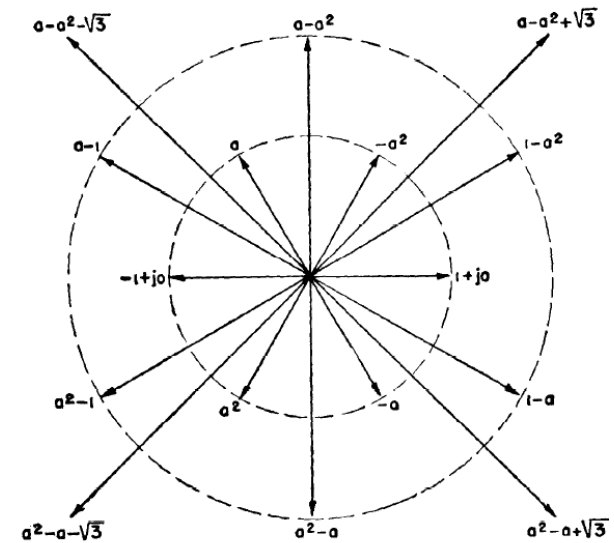


Fig. 2—Properties of the vector operator a .




Reference [2]

SYMMETRICAL COMPONENTS

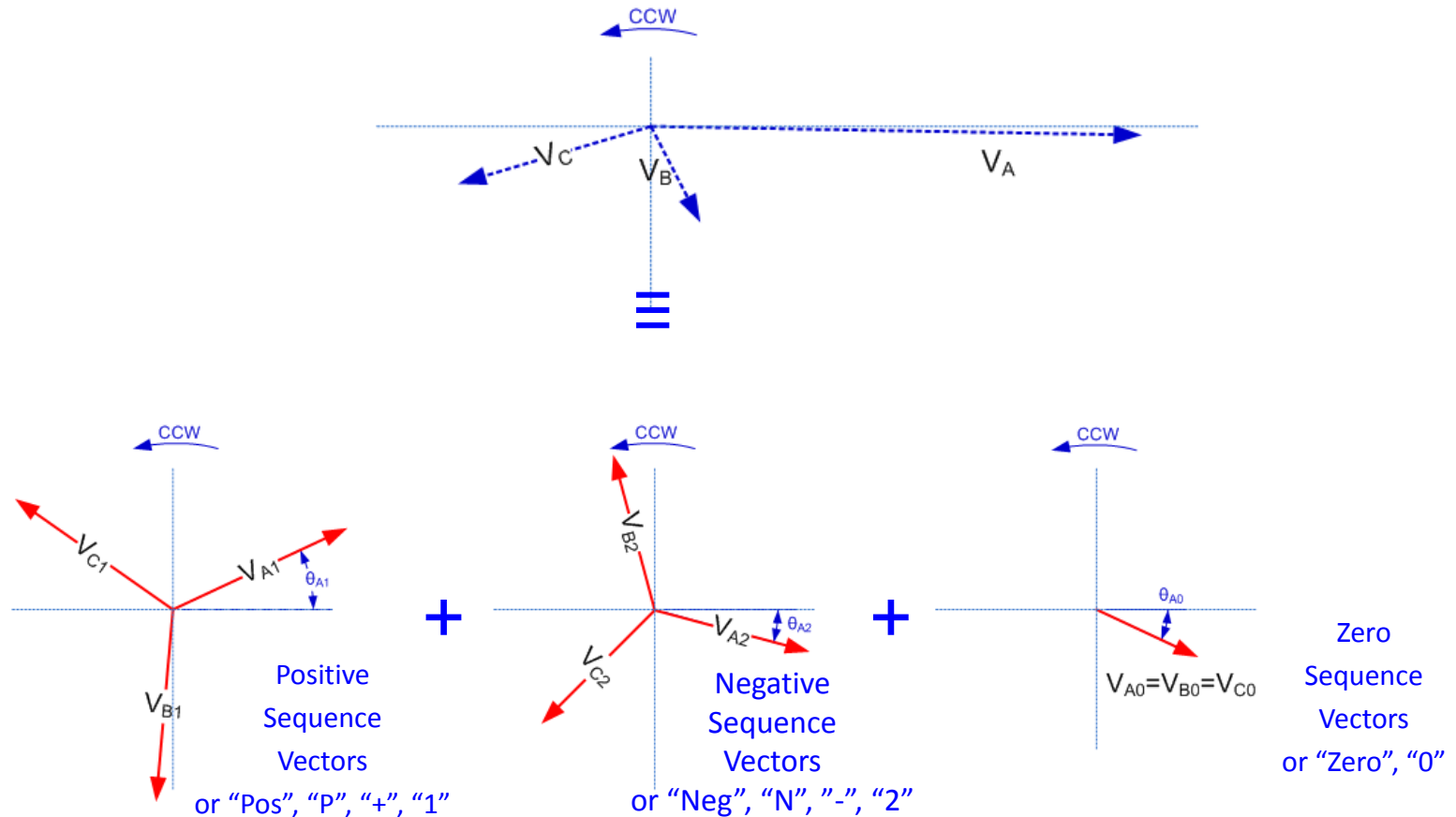- Let's consider unbalanced voltage phasors of the three phase system (i.e. unbalanced set)



SYMMETRICAL COMPONENTS

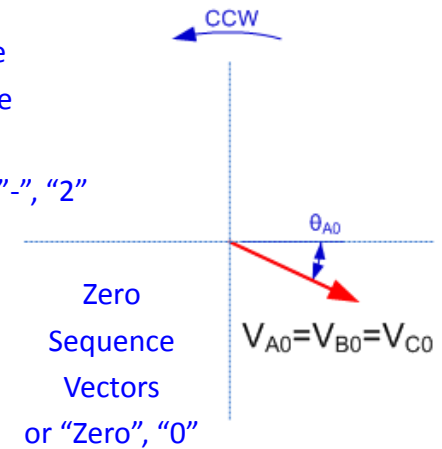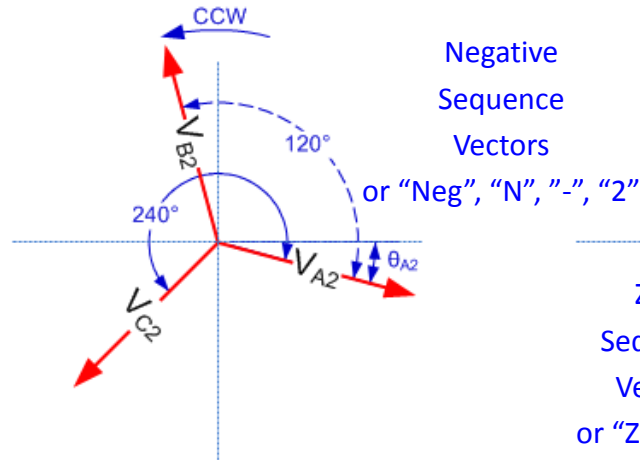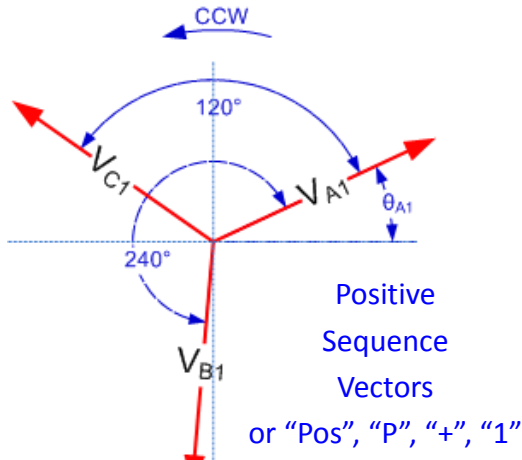

$$\underline{X}_{a1}$$

$$\underline{X}_{b1} = \underline{X}_{a1} \cdot \underline{a}^2$$

$$\underline{X}_{c1} = \underline{X}_{a1} \cdot \underline{a}$$

$$\underline{X}_{a2}$$

$$\underline{X}_{b2} = \underline{X}_{a2} \cdot \underline{a}$$

$$\underline{X}_{c2} = \underline{X}_{a2} \cdot \underline{a}^2$$

$$\underline{X}_{a0}$$

$$\underline{X}_{b0} = \underline{X}_{a0}$$

$$\underline{X}_{c0} = \underline{X}_{a0}$$

Or

$$\underline{X}_a = \underline{X}_{a0} + \underline{X}_{a1} + \underline{X}_{a2}$$

$$\underline{X}_b = \underline{X}_{b0} + \underline{X}_{b1} + \underline{X}_{b2} = \underline{X}_{a0} + \underline{X}_{a1} \cdot \underline{a}^2 + \underline{X}_{a2} \cdot \underline{a}$$

$$\underline{X}_c = \underline{X}_{c0} + \underline{X}_{c1} + \underline{X}_{c2} = \underline{X}_{a0} + \underline{X}_{a1} \cdot \underline{a} + \underline{X}_{a2} \cdot \underline{a}^2$$

SYMMETRICAL COMPONENTS

$$X_{abc} \rightarrow X_{012}$$

$$X_{abc} = A \cdot X_{012}$$

$$\begin{pmatrix} \underline{X}_a \\ \underline{X}_b \\ \underline{X}_c \end{pmatrix} = \frac{1}{h} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a}^2 & \underline{a} \\ 1 & \underline{a} & \underline{a}^2 \end{pmatrix} \cdot \begin{pmatrix} \underline{X}_{a0} \\ \underline{X}_{a1} \\ \underline{X}_{a2} \end{pmatrix}$$

$$A = \frac{1}{h} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a}^2 & \underline{a} \\ 1 & \underline{a} & \underline{a}^2 \end{pmatrix}$$

$$X_{012} \rightarrow X_{abc}$$

$$X_{012} = A^{-1} \cdot X_{abc}$$

$$\begin{pmatrix} \underline{X}_{a0} \\ \underline{X}_{a1} \\ \underline{X}_{a2} \end{pmatrix} = \frac{h}{3} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a} & \underline{a}^2 \\ 1 & \underline{a}^2 & \underline{a} \end{pmatrix} \cdot \begin{pmatrix} \underline{X}_a \\ \underline{X}_b \\ \underline{X}_c \end{pmatrix}$$


$$A^{-1} = \frac{h}{3} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a} & \underline{a}^2 \\ 1 & \underline{a}^2 & \underline{a} \end{pmatrix}$$

Note: $h = 1$ for the Fortescue transformation (this presentation)

$h = \sqrt{3}$ for the power invariant transformation

SYMMETRICAL COMPONENTS

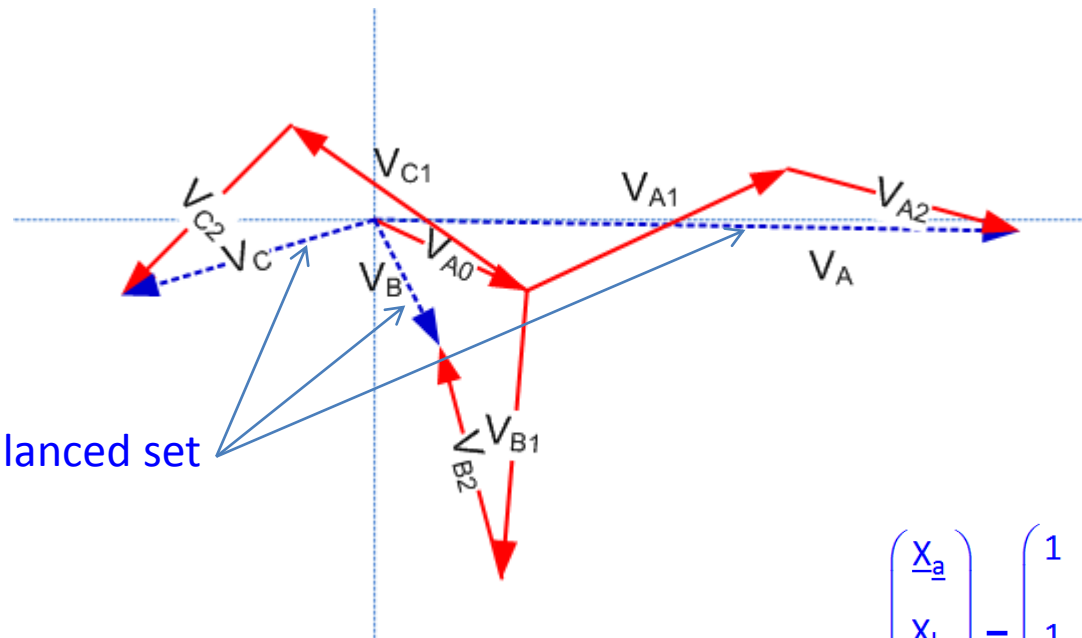- Per phase voltage sets summation of symmetrical components to obtain an unbalanced set






Three phase unbalanced set

$$\begin{pmatrix} \underline{X}_a \\ \underline{X}_b \\ \underline{X}_c \end{pmatrix} = \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a}^2 & \underline{a} \\ 1 & \underline{a} & \underline{a}^2 \end{pmatrix} \cdot \begin{pmatrix} \underline{X}_{a0} \\ \underline{X}_{a1} \\ \underline{X}_{a2} \end{pmatrix}$$

SYMMETRICAL COMPONENTS

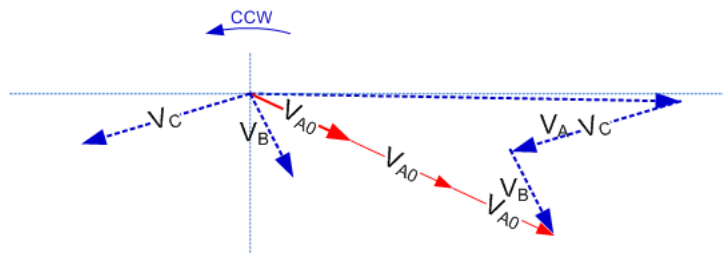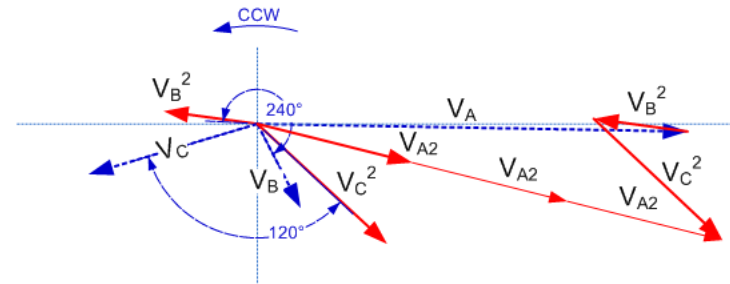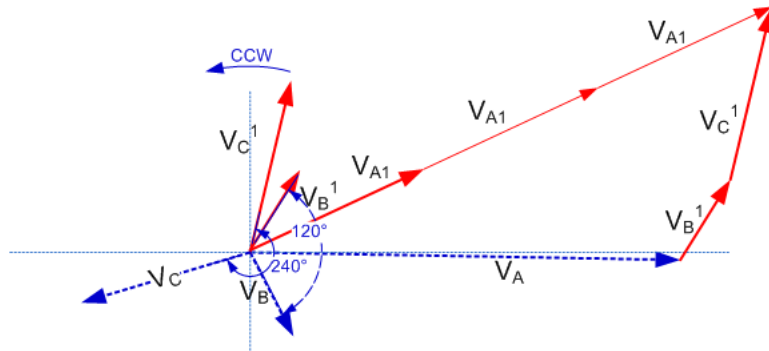- Per phase voltage sets summation of unbalanced set with “a” transformation to obtain an symmetrical components



$$\begin{pmatrix} \underline{X}_{a0} \\ \underline{X}_{a1} \\ \underline{X}_{a2} \end{pmatrix} = \frac{1}{3} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a} & \underline{a}^2 \\ 1 & \underline{a}^2 & \underline{a} \end{pmatrix} \cdot \begin{pmatrix} \underline{X}_a \\ \underline{X}_b \\ \underline{X}_c \end{pmatrix}$$

SYMMETRICAL COMPONENTS

- Example S1

$$\mathbf{I}_{abc} := \begin{pmatrix} I_a \\ I_b \\ I_c \end{pmatrix} = \begin{pmatrix} 10 \\ -5 - 8.66i \\ -5 + 8.66i \end{pmatrix} \text{ A} \quad \text{z2r}\theta\text{M}(\mathbf{I}_{abc}) = \begin{pmatrix} "(10 \angle 0^\circ)" \\ "(10 \angle -120^\circ)" \\ "(10 \angle 120^\circ)" \end{pmatrix}$$

$$\mathbf{I}_{012} = \begin{pmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{pmatrix} \quad \mathbf{I}_{012} := \mathbf{S}^{-1} \cdot \mathbf{I}_{abc} \quad \text{z2r}\theta\text{M}(\mathbf{I}_{012}) = \begin{pmatrix} "(0 \angle -28.8634^\circ)" \\ "(10 \angle 0^\circ)" \\ "(0 \angle -90^\circ)" \end{pmatrix} \text{ A}$$

$$\mathbf{V}_{abc} := \begin{pmatrix} V_a \\ V_b \\ V_c \end{pmatrix} = \begin{pmatrix} 7 \\ -16i \\ -2.11 + 4.53i \end{pmatrix} \text{ V} \quad \text{z2r}\theta\text{M}(\mathbf{V}_{abc}) = \begin{pmatrix} "(7 \angle 0^\circ)" \\ "(16 \angle -90^\circ)" \\ "(5 \angle 115^\circ)" \end{pmatrix} \text{ V}$$

$$\mathbf{V}_{012} = \begin{pmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{pmatrix} \quad \mathbf{V}_{012} := \mathbf{S}^{-1} \cdot \mathbf{V}_{abc} \quad \text{z2r}\theta\text{M}(\mathbf{V}_{012}) = \begin{pmatrix} "(4.1554 \angle -66.9203^\circ)" \\ "(8.974 \angle 16.3181^\circ)" \\ "(3.4929 \angle 158.1249^\circ)" \end{pmatrix} \text{ V}$$


SYMMETRICAL COMPONENTS

- Example S2

$$V_a := 8V \cdot e^{j \cdot 0\text{deg}}$$

$$V_b := 6V \cdot e^{j \cdot -90\text{deg}}$$
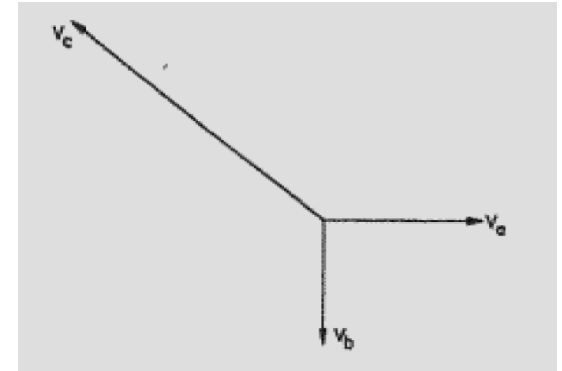
$$V_c := 16V \cdot e^{j \cdot 143.1\text{deg}}$$



$$\begin{pmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{pmatrix} := \mathbf{S}^{-1} \cdot \begin{pmatrix} V_a \\ V_b \\ V_c \end{pmatrix} = \begin{pmatrix} -1.6 + 1.2i \\ 9.3 + 3.09i \\ 0.29 - 4.29i \end{pmatrix} \text{ V}$$

$$\text{z2r}\theta\text{M} \begin{pmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{pmatrix} = \begin{pmatrix} "(2 \angle 143.0498^\circ)" \\ "(9.8049 \angle 18.385^\circ)" \\ "(4.3047 \angle -86.0854^\circ)" \end{pmatrix} \text{ V}$$





$$\begin{pmatrix} V_{b0} \\ V_{b1} \\ V_{b2} \end{pmatrix} := \begin{pmatrix} V_{a0} \\ a^2 \cdot V_{a1} \\ a \cdot V_{a2} \end{pmatrix} = \begin{pmatrix} -1.6 + 1.2i \\ -1.97 - 9.6i \\ 3.57 + 2.4i \end{pmatrix} \text{ V}$$

$$\text{z2r}\theta\text{M} \begin{pmatrix} V_{b0} \\ V_{b1} \\ V_{b2} \end{pmatrix} = \begin{pmatrix} "(2 \angle 143.0498^\circ)" \\ "(9.8049 \angle -101.615^\circ)" \\ "(4.3047 \angle 33.9146^\circ)" \end{pmatrix} \text{ V}$$

$$\begin{pmatrix} V_{c0} \\ V_{c1} \\ V_{c2} \end{pmatrix} := \begin{pmatrix} V_{a0} \\ a \cdot V_{a1} \\ a^2 \cdot V_{a2} \end{pmatrix} = \begin{pmatrix} -1.6 + 1.2i \\ -7.33 + 6.51i \\ -3.87 + 1.89i \end{pmatrix} \text{ V}$$

$$\text{z2r}\theta\text{M} \begin{pmatrix} V_{c0} \\ V_{c1} \\ V_{c2} \end{pmatrix} = \begin{pmatrix} "(2 \angle 143.0498^\circ)" \\ "(9.8049 \angle 138.385^\circ)" \\ "(4.3047 \angle 153.9146^\circ)" \end{pmatrix} \text{ V}$$

SYMMETRICAL COMPONENTS

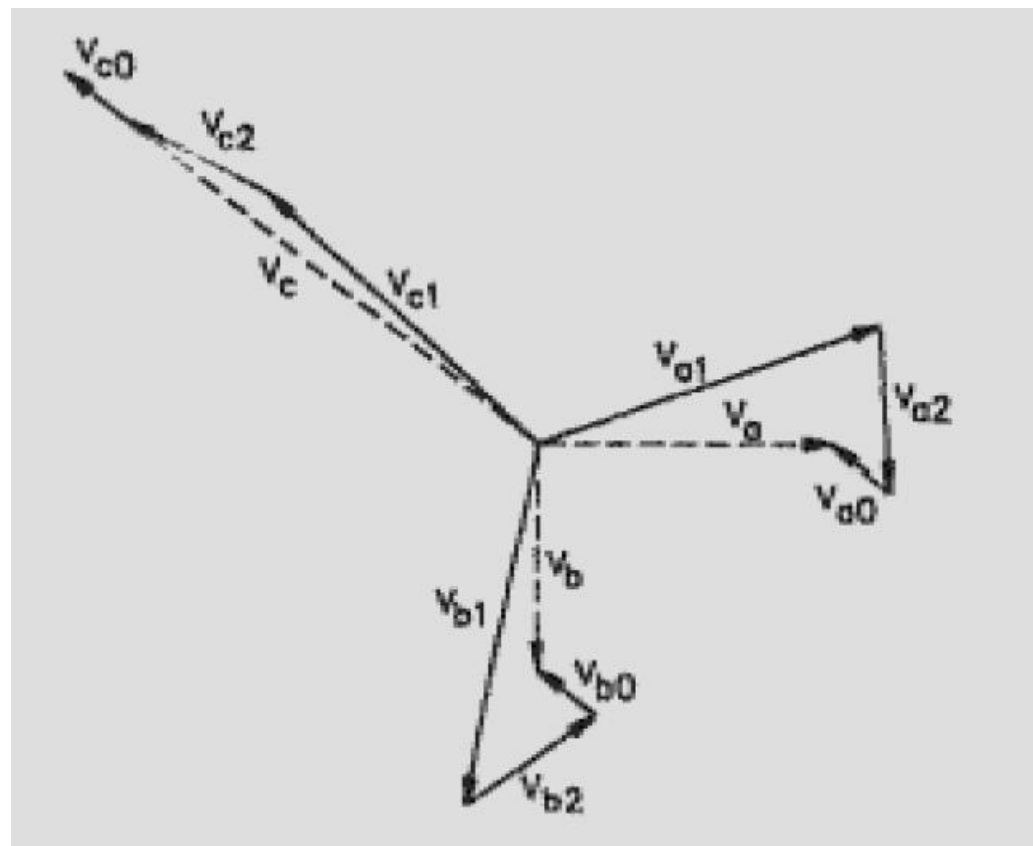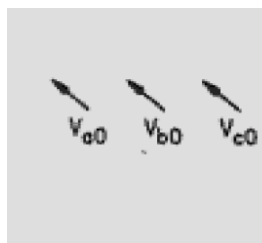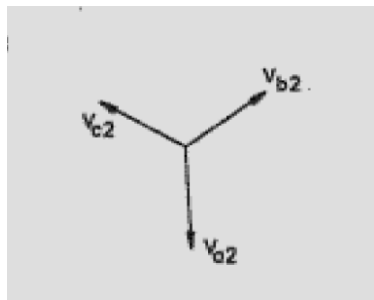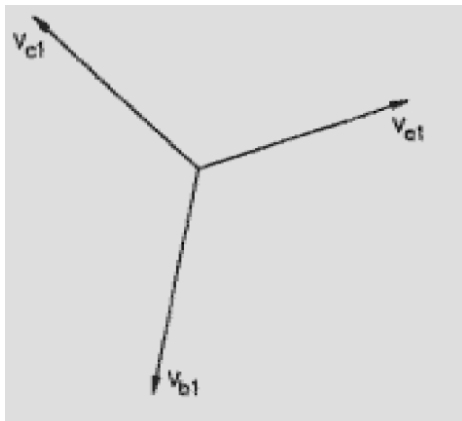

SYMMETRICAL COMPONENTS

- Comments & Notes:
 - Transformations apply only to balanced and symmetrical systems before unbalance occurs. Symmetrical networks can be solved using single phase techniques.
 - The transformations apply only for linear systems, that is, systems with constant parameters (impedance, admittance) independent of voltages and currents.
 - The quantities used for X_{abc} can be phase-to-neutral or phase-to-phase voltages, or line or line-to-line currents.
 - For some connections, the zero sequence component is always zero.
 - With symmetrical components we solve three interconnected symmetrical networks using single phase analysis.
 - Once solved, we use transformation equations to obtain phase quantities.

SYMMETRICAL COMPONENTS

- On equipment Modeling:
 - Symmetrical components has advantage that parameters in system components are easier to define as each sequence is a symmetrical three phase case, the parameters can be defined using typical three-phase tests.
 - In unbalanced and/or unsymmetrical systems modeling, the parameters cannot be defined using standard tests. As a result, symmetrical components principle cannot be used in systems that are unbalanced and/or unsymmetrical.

SYMMETRICAL COMPONENTS

- Complex Power with symmetrical components:

$$S_{abc} = \begin{pmatrix} \underline{V}_{an} & \underline{V}_{bn} & \underline{V}_{cn} \end{pmatrix} \cdot \begin{pmatrix} \underline{I}_a \\ \underline{I}_b \\ \underline{I}_c \end{pmatrix} = \underline{V}_{abc.n}^T \cdot \underline{I}_{abc}$$

Knowing,

$$\underline{V}_{abc.n} = \mathbf{A} \cdot \underline{V}_{012} \quad \underline{I}_{abc} = \mathbf{A} \cdot \underline{I}_{012}$$

Substituting

$$S_{abc} = (\mathbf{A} \cdot \underline{V}_{012})^T \cdot \overline{(\mathbf{A} \cdot \underline{I}_{012})} = \underline{V}_{012}^T \cdot \mathbf{A}^T \cdot \overline{\mathbf{A} \cdot \underline{V}_{012}}$$

Note that:

$$\mathbf{A}^T \cdot \overline{\mathbf{A}} = \begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{pmatrix} \cdot 3$$

$$S_{abc} = 3 \cdot \underline{V}_{012}^T \cdot \overline{\underline{V}_{012}} = 3(\underline{V}_{a0} \cdot \overline{\underline{I}_{a0}} + \underline{V}_{a1} \cdot \overline{\underline{I}_{a1}} + \underline{V}_{a2} \cdot \overline{\underline{I}_{a2}})$$

Note: For general case, with $h := \sqrt{3}$ i.e. power invariant transformation

$$S_{abc} = \frac{3}{h^2} (\underline{V}_{a0} \cdot \overline{\underline{I}_{a0}} + \underline{V}_{a1} \cdot \overline{\underline{I}_{a1}} + \underline{V}_{a2} \cdot \overline{\underline{I}_{a2}})$$

SYMMETRICAL COMPONENTS

- Consider the following D-Line (i.e series component):


$$Z_{aa} \neq Z_{bb} \neq Z_{cc}$$

$$Z_{ab} \neq Z_{bc} \neq Z_{ca}$$

$$Z_{ab} = Z_{ba}$$

$$Z_{bc} = Z_{cb}$$

$$Z_{ac} = Z_{ca}$$

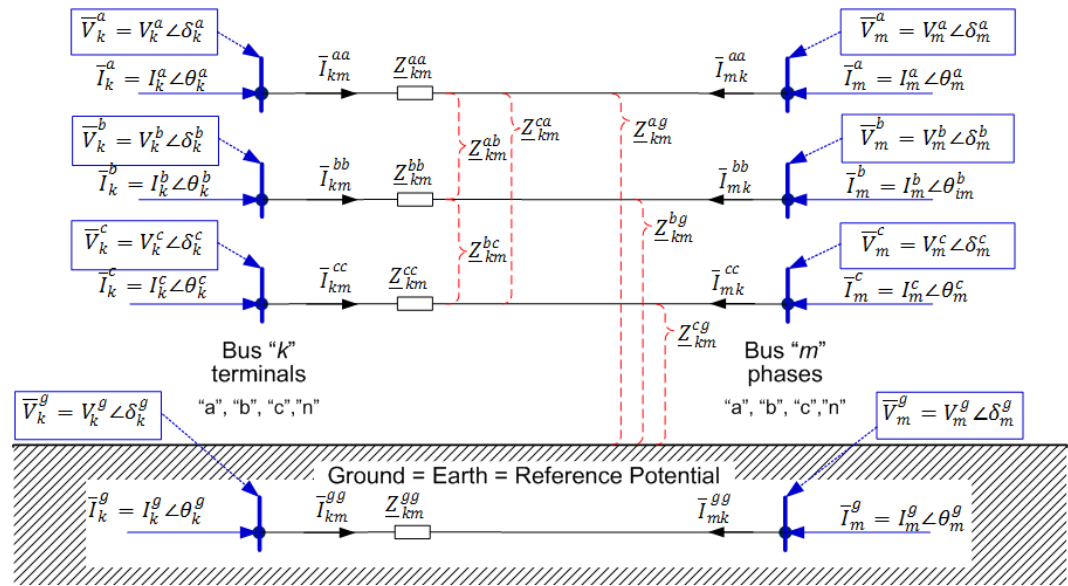

$$\begin{pmatrix} V_{km.a} \\ V_{km.b} \\ V_{km.c} \end{pmatrix} = \begin{pmatrix} Z_{km.aa} & Z_{km.ab} & Z_{km.ac} \\ Z_{km.ba} & Z_{km.bb} & Z_{km.bc} \\ Z_{km.ca} & Z_{km.cb} & Z_{km.cc} \end{pmatrix} \cdot \begin{pmatrix} I_{km.a} \\ I_{km.b} \\ I_{km.c} \end{pmatrix}$$

SYMMETRICAL COMPONENTS

- Transformation to Symmetrical Components....

$$V_{km.abc} = Z_{km} \cdot I_{km.abc}$$

$$A \cdot V_{km.012} = Z_{km.abc} \cdot A \cdot I_{km.012}$$

$$V_{km.012} = A^{-1} \cdot Z_{km.abc} \cdot A \cdot I_{km.012}$$

$$V_{km.012} = Z_{km.012} \cdot I_{km.012}$$

$$Z_{km.012} = \begin{pmatrix} Z_{S0} + 2 \cdot Z_{M0} & Z_{S2} - Z_{M2} & Z_{S1} - Z_{M1} \\ Z_{S1} - Z_{M1} & Z_{S0} - Z_{M0} & Z_{S2} + 2 \cdot Z_{M2} \\ Z_{S2} - Z_{M2} & Z_{S1} + 2 \cdot Z_{M1} & Z_{S0} - Z_{M0} \end{pmatrix}$$

Where:

$$Z_{S0} = \frac{1}{3} \cdot (Z_{aa} + Z_{bb} + Z_{cc})$$

$$Z_{S1} = \frac{1}{3} \cdot (Z_{aa} + a \cdot Z_{bb} + a^2 \cdot Z_{cc})$$

$$Z_{S2} = \frac{1}{3} \cdot (Z_{aa} + a^2 \cdot Z_{bb} + a \cdot Z_{cc})$$

$$Z_{M0} = \frac{1}{3} \cdot (Z_{bc} + Z_{ca} + Z_{ab})$$

$$Z_{M1} = \frac{1}{3} \cdot (Z_{bc} + a \cdot Z_{ca} + a^2 \cdot Z_{ab})$$

$$Z_{M2} = \frac{1}{3} \cdot (Z_{bc} + a^2 \cdot Z_{ca} + a \cdot Z_{ab})$$

SYMMETRICAL COMPONENTS

- Note a problem... For example the positive sequence voltage drop

$$V_{km.1} = (Z_{S1} - Z_{M1}) \cdot I_{a0} + (Z_{S0} - Z_{M0}) \cdot I_{a1} + (Z_{S2} + 2 \cdot Z_{M2}) \cdot I_{a2}$$

depends upon not only I_{a1} but I_{a0} and I_{a2} as well. This means there is mutual coupling between sequences. Also, $Z_{mn.012}$ is not symmetric, therefore mutual effect is not reciprocal.

- How to “decouple” sequences?
 - In general, there are three cases of decoupling, but only one is useful (Case 2)

SYMMETRICAL COMPONENTS

– Case 1:

Self and mutual impedances are symmetric with respect to phase “A”

$$Z_{bb} = Z_{cc} \quad Z_{S0} = \frac{1}{3} \cdot (Z_{aa} + 2Z_{bb})$$

$$Z_{ab} = Z_{ca} \quad Z_{S1} = Z_{S2} = \frac{1}{3} \cdot (Z_{aa} - Z_{bb})$$

$$Z_{M0} = \frac{1}{3} \cdot (Z_{bc} + 2 \cdot Z_{ab})$$

$$Z_{M1} = Z_{M2} = \frac{1}{3} \cdot (Z_{bc} - Z_{ab})$$

$$Z_{km.012} = \begin{pmatrix} Z_{S0} + 2 \cdot Z_{M0} & Z_{S2} - Z_{M2} & Z_{S1} - Z_{M1} \\ Z_{S1} - Z_{M1} & Z_{S0} - Z_{M0} & Z_{S2} + 2 \cdot Z_{M2} \\ Z_{S2} - Z_{M2} & Z_{S1} + 2 \cdot Z_{M1} & Z_{S0} - Z_{M0} \end{pmatrix}$$

– Mutual coupling between sequences is not eliminated.

SYMMETRICAL COMPONENTS

– Case 2:

Self and mutual impedances are equal in all three phases:

$$Z_{S0} = Z_{aa} \quad Z_{S1} = Z_{S2} = 0$$

$$Z_{M0} = Z_{bc} \quad Z_{M1} = Z_{M2} = 0$$

$$Z_{km.012} = \begin{pmatrix} Z_{S0} + 2 \cdot Z_{M0} & \cancel{Z_{S2} + 2 \cdot Z_{M2}} & \cancel{Z_{S1} + 2 \cdot Z_{M1}} \\ \cancel{Z_{S1} + 2 \cdot Z_{M1}} & Z_{S0} - Z_{M0} & \cancel{Z_{S2} + 2 \cdot Z_{M2}} \\ \cancel{Z_{S2} + 2 \cdot Z_{M2}} & \cancel{Z_{S1} + 2 \cdot Z_{M1}} & Z_{S0} - Z_{M0} \end{pmatrix} = \begin{pmatrix} Z_{S0} + 2 \cdot Z_{M0} & 0 & 0 \\ 0 & Z_{S0} - Z_{M0} & 0 \\ 0 & 0 & Z_{S0} - Z_{M0} \end{pmatrix}$$

- Off diagonal terms eliminated.
- Matrix is reciprocal and no coupling between sequences. This is the case that is used in all Symmetrical Components calculations.


SYMMETRICAL COMPONENTS

Network equation and diagram
for series component


$$\underline{V}_{km.012} = \underline{Z}_{km.012} \cdot \underline{I}_{km.012}$$

$$\begin{pmatrix} V_{km.0} \\ V_{km.1} \\ V_{km.2} \end{pmatrix} = \begin{pmatrix} Z_{S0} + 2 \cdot Z_{M0} & 0 & 0 \\ 0 & Z_{S0} - Z_{M0} & 0 \\ 0 & 0 & Z_{S0} - Z_{M0} \end{pmatrix} \cdot \begin{pmatrix} I_{km.0} \\ I_{km.1} \\ I_{km.2} \end{pmatrix}$$


Positive Sequence Network

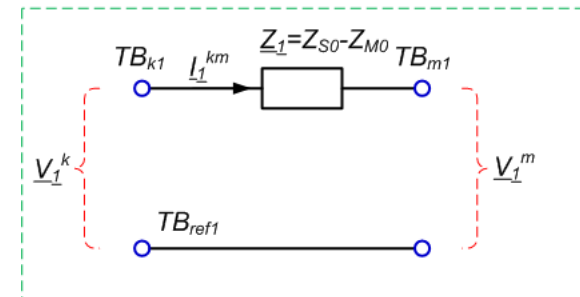

Negative Sequence Network

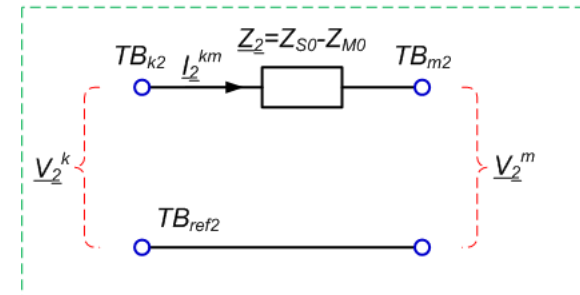

Zero Sequence Network

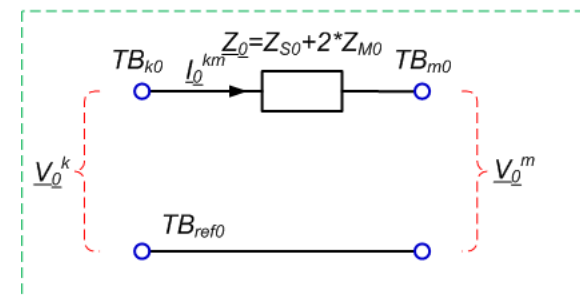

SYMMETRICAL COMPONENTS

- In the matrix modeling, the components in three-phase system exhibit characteristics in phase domain as follow:

– Complete symmetry component

$$\begin{bmatrix} \underline{Z}_S & \underline{Z}_m & \underline{Z}_m \\ \underline{Z}_m & \underline{Z}_S & \underline{Z}_m \\ \underline{Z}_m & \underline{Z}_m & \underline{Z}_S \end{bmatrix} \quad \text{where} \quad \underline{z}_S \quad \text{- self impedance}$$

$$\underline{z}_m \quad \text{- mutual impedance}$$

– Circulant symmetry component

$$\begin{bmatrix} \underline{Z}_S & \underline{Z}_m & \underline{Z}_n \\ \underline{Z}_n & \underline{Z}_S & \underline{Z}_m \\ \underline{Z}_m & \underline{Z}_n & \underline{Z}_S \end{bmatrix} \quad \text{where} \quad \underline{z}_S \quad \text{- self impedance}$$

$$\underline{z}_m, \underline{z}_n \quad \text{- mutual impedances}$$

– Unbalanced component

$$\begin{bmatrix} \underline{Z}_{11} & \underline{Z}_{12} & \underline{Z}_{13} \\ \underline{Z}_{21} & \underline{Z}_{22} & \underline{Z}_{23} \\ \underline{Z}_{31} & \underline{Z}_{32} & \underline{Z}_{33} \end{bmatrix} \quad \text{where} \quad \underline{z}_{11}, \underline{z}_{22}, \underline{z}_{33} \quad \text{- self impedances in relation to each}$$

phase (in general not equal to each others),


$$\underline{z}_{12}, \underline{z}_{13}, \underline{z}_{21}, \underline{z}_{23}, \underline{z}_{31}, \underline{z}_{33} \quad \text{- mutual impedance between}$$

each of phases primitive impedances
(in general not equal to each other's and
dependent on the mutual couplings).

UNBALANCE NETWORKS MODELING PRINCIPLES


NETWORKS MODELING – UNBALANCED SOURCE WITH BALANCED CIRCUIT

- Symmetrical 3-phase circuit powered up with symmetrical (balanced) generator:
 - » Circuit currents are symmetrical; i.e. there are symmetrical components of current and voltages with symmetrical impedances but only positive sequence (for CCW rotation)
- Symmetrical 3-phase circuit powered up with unsymmetrical (unbalanced) generator
 - » Circuit currents are unsymmetrical; i.e. there are 0, 1, and 2 symmetrical components of current and voltages with symmetrical impedances in circuit

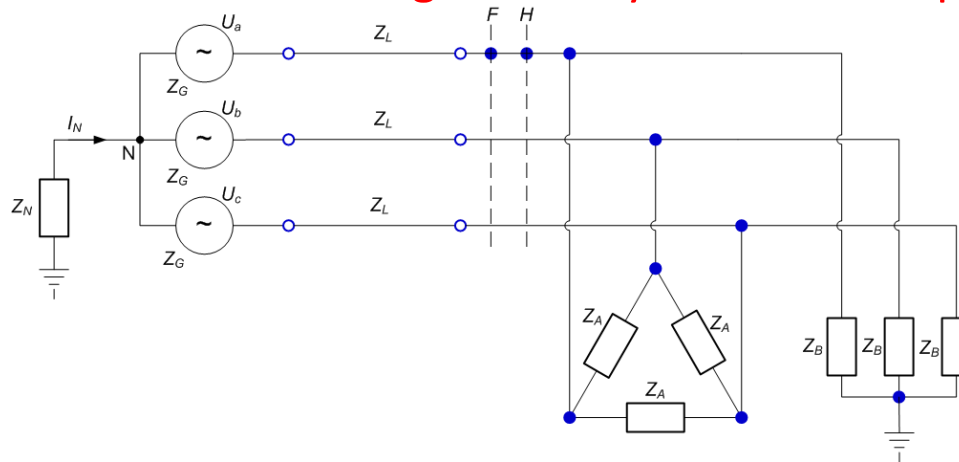


NETWORKS MODELING – UNBALANCED SOURCE WITH BALANCED CIRCUIT

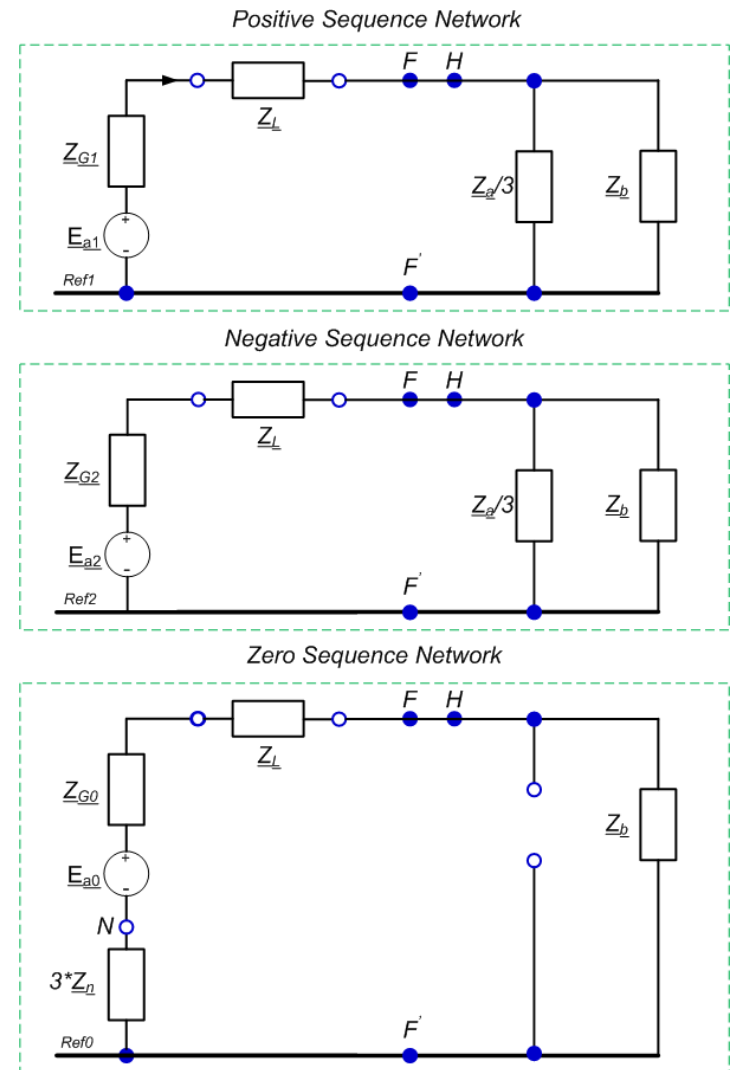- In symmetrical circuits, we can analyze each symmetrical component of current and voltage independent of other components networks (i.e. networks are “decoupled”). This results in three independent networks.
- Currents & voltages can be calculated for symmetrical network with unbalanced generator.




NETWORKS MODELING – SHUNT UNBALANCE

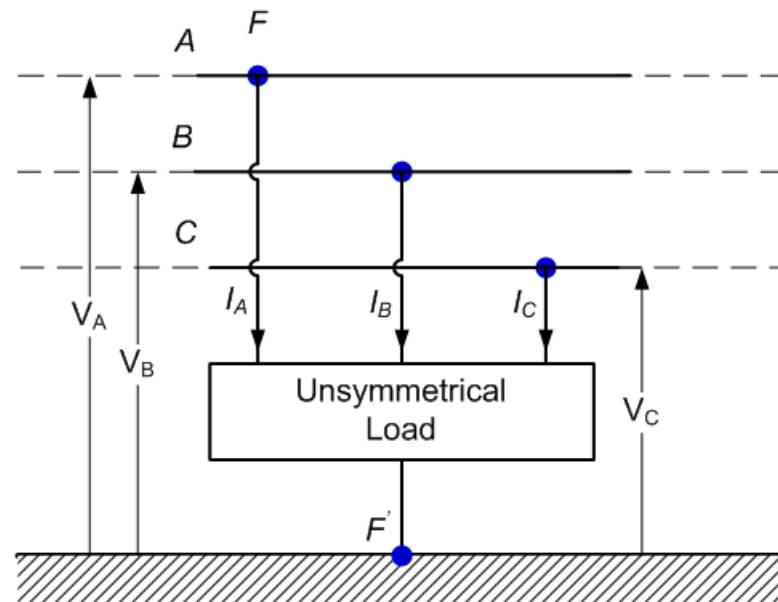- Usually, 3-phase circuits are powered up with symmetrical (balanced) generators, but in certain operating conditions, symmetry in network is lost due to unsymmetrical load (i.e. fault)






NETWORKS MODELING – SHUNT UNBALANCE

- In order to utilize symmetrical components methodology, different approach from previous method has to be developed.
 - » In place where unbalanced load was connected (point F), power sources with voltages U_A , U_B , and U_C equal to voltages at point F are connected; i.e. unbalanced generator replaced unbalanced load.
 - » No current flow and voltage values in the circuit are altered.
 - » As a result, we are analyzing balanced circuit with unbalanced generator.

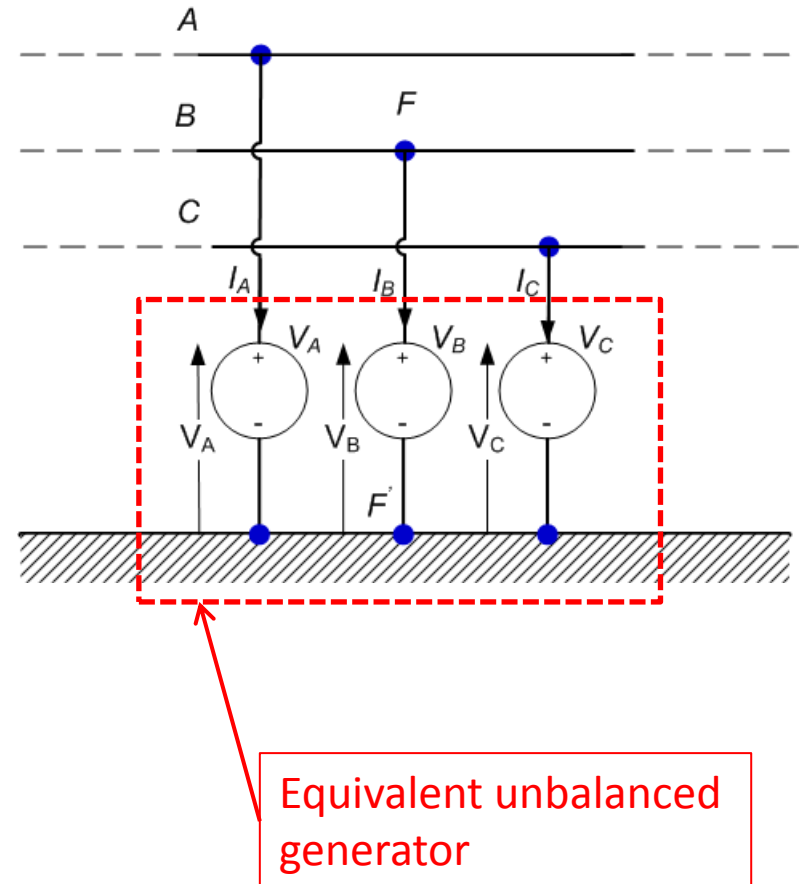

NETWORKS MODELING – SHUNT UNBALANCE

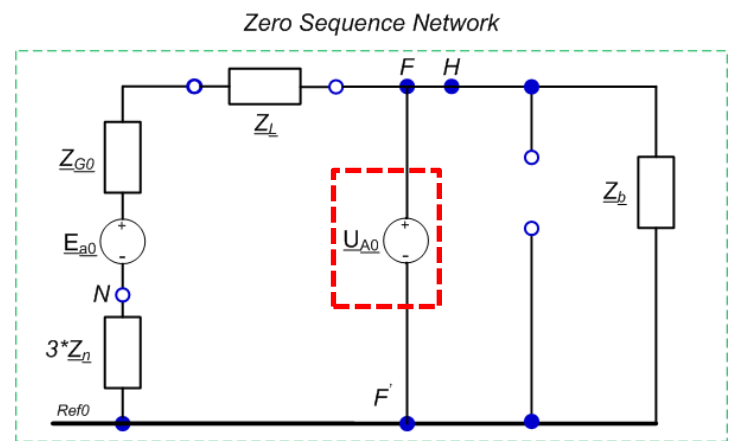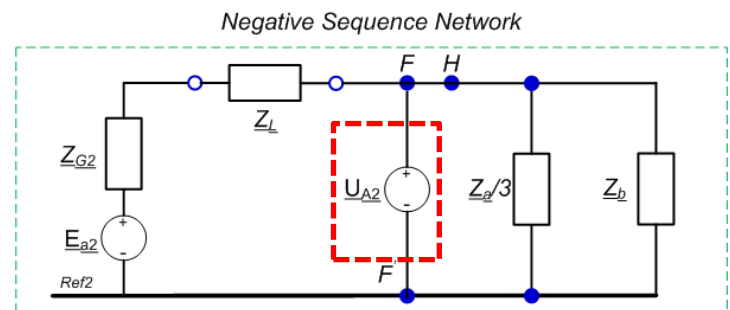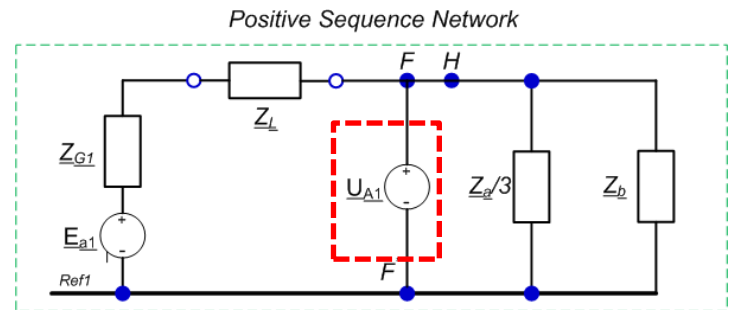- After converting U_A , U_B , and U_C to symmetrical components voltages U_0 , U_1 , and U_2 , they are inserted in the network.



NETWORKS MODELING – SHUNT UNBALANCE

- Utilizing Thevenin Theorem

$$\frac{1}{Z_1} = \frac{1}{Z_{G1} + Z_L} + \frac{1}{\frac{1}{3} \cdot Z_a} + \frac{1}{Z_b}$$

$$\frac{1}{Z_2} = \frac{1}{Z_{G2} + Z_L} + \frac{1}{\frac{1}{3} \cdot Z_a} + \frac{1}{Z_b}$$

$$\frac{1}{Z_0} = \frac{1}{Z_{G0} + Z_L + 3 \cdot Z_N} + \frac{1}{Z_b}$$

- Circuit solution is described by

$$\underline{U}_1 = \underline{E}_1 - Z_1 \cdot \underline{I}_1$$

$$\underline{U}_2 = \underline{E}_2 - Z_2 \cdot \underline{I}_2$$

$$\underline{U}_0 = \underline{E}_0 - Z_0 \cdot \underline{I}_0$$


$$\underline{U}_1 = \underline{E}_1 - Z_1 \cdot \underline{I}_1$$

$$\underline{U}_2 = -Z_2 \cdot \underline{I}_2$$


$$\underline{U}_0 = -Z_0 \cdot \underline{I}_0$$

For balanced and symmetrical generator


Positive Sequence Network

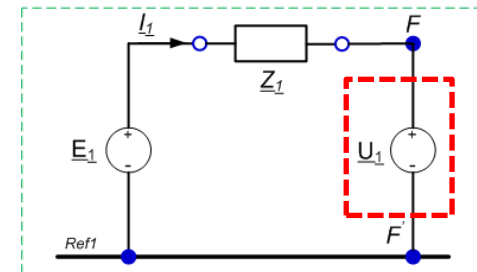

Negative Sequence Network

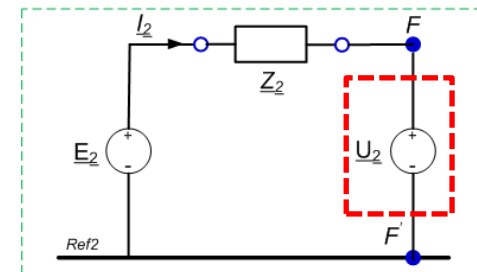

Zero Sequence Network

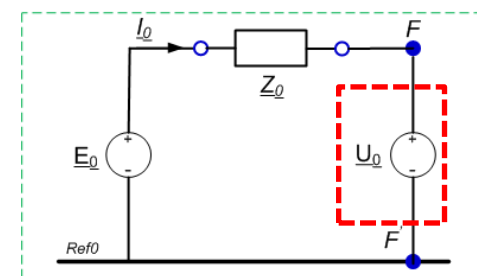

NETWORKS MODELING – BALANCED SOURCE WITH BALANCED CIRCUIT & UNBALANCED LOAD

- Example

$$\underline{I}_B = 0$$


$$\underline{I}_C = 0$$

$$\underline{U}_A = \underline{I}_A \cdot \underline{Z}_f$$

$$\begin{pmatrix} \underline{I}_0 \\ \underline{I}_1 \\ \underline{I}_2 \end{pmatrix} = \frac{1}{3} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a} & \underline{a}^2 \\ 1 & \underline{a}^2 & \underline{a} \end{pmatrix} \cdot \begin{pmatrix} \underline{I}_A \\ 0 \\ 0 \end{pmatrix} = \frac{1}{3} \cdot \begin{pmatrix} \underline{I}_A \\ \underline{I}_A \\ \underline{I}_A \end{pmatrix}$$

$$\underline{I}_0 = \underline{I}_1 = \underline{I}_2$$
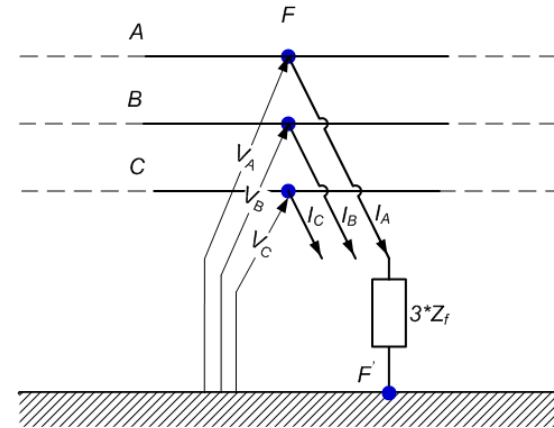
$$\underline{U}_A = \underline{I}_A \cdot \underline{Z}_f$$




NETWORKS MODELING – BALANCED SOURCE WITH BALANCED CIRCUIT & UNBALANCED LOAD

- Example

$$\underline{U}_0 + \underline{U}_1 + \underline{U}_2 = 3 \cdot \underline{l}_1 \cdot \underline{Z}_f$$


$$-Z_0 \cdot \underline{l}_0 + \underline{E}_1 - Z_1 \cdot \underline{l}_1 - Z_2 \cdot \underline{l}_2 = 3 \cdot \underline{l}_1 \cdot \underline{Z}_f$$
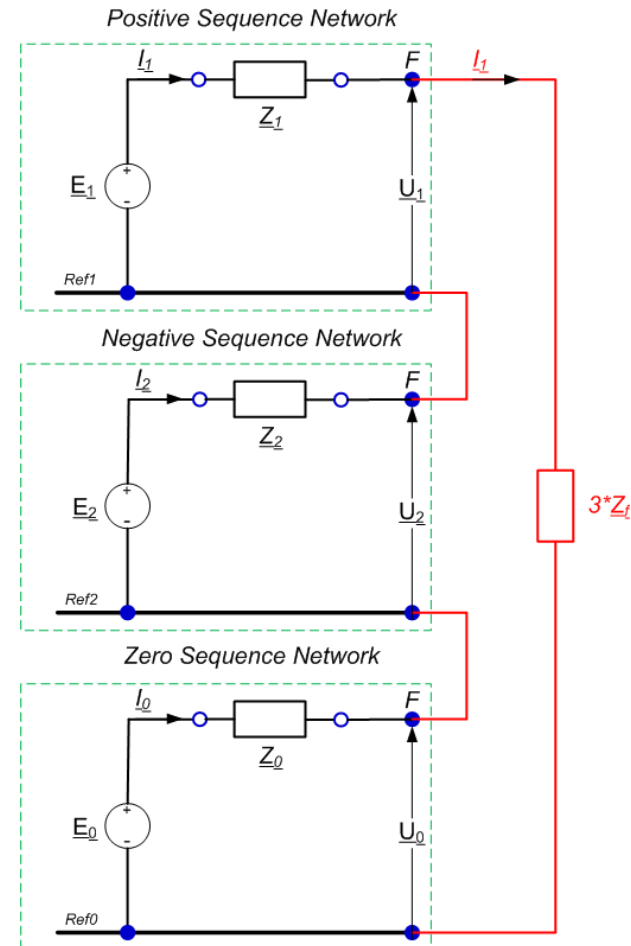
$$\underline{l}_1 = \frac{\underline{E}_1}{\underline{Z}_1 + \underline{Z}_2 + \underline{Z}_0 + 3 \cdot \underline{Z}_f}$$




NETWORKS MODELING – SERIAL UNBALANCE

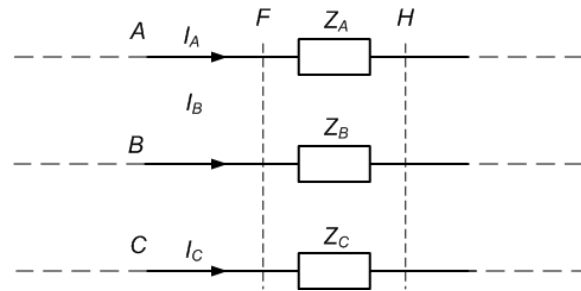- Usually, 3-phase circuits are powered up with symmetrical (balanced) generators, but in certain operating conditions, symmetry in network is lost due to unsymmetrical load (i.e. fault)



NETWORKS MODELING – SERIAL UNBALANCE




- In order to utilize symmetrical components methodology, different approach from previous method has to be developed.
 - » In place where unbalanced load was connected (point F), power sources with voltages U_A , U_B , and U_C equal to voltages at point F are connected; i.e. unbalanced generator replaced unbalanced load.
 - » No current flow and voltage values in the circuit are altered.
 - » As a result, we are analyzing balanced circuit with unbalanced generator.

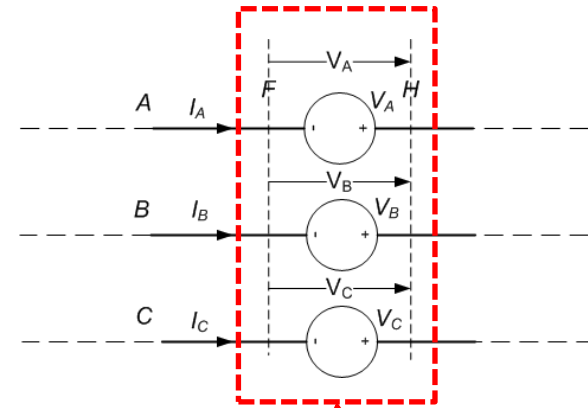

Equivalent unbalanced generator

NETWORKS MODELING – SERIAL UNBALANCE

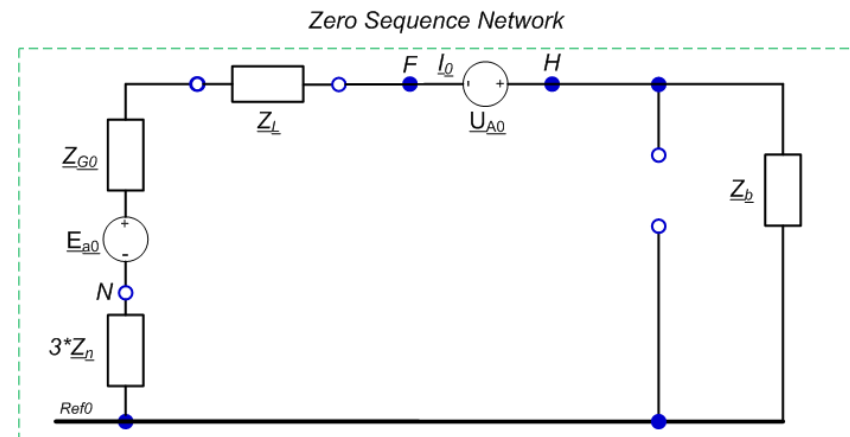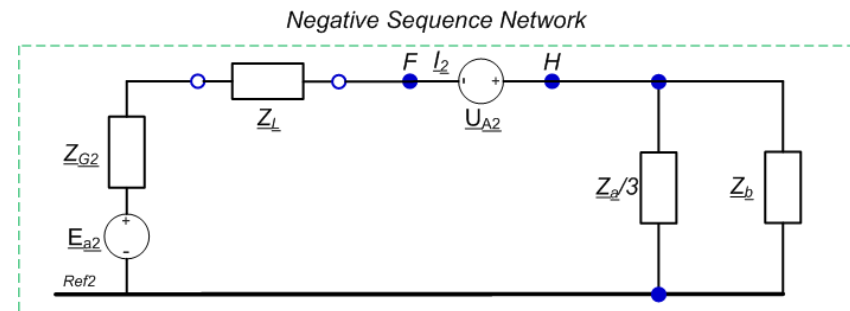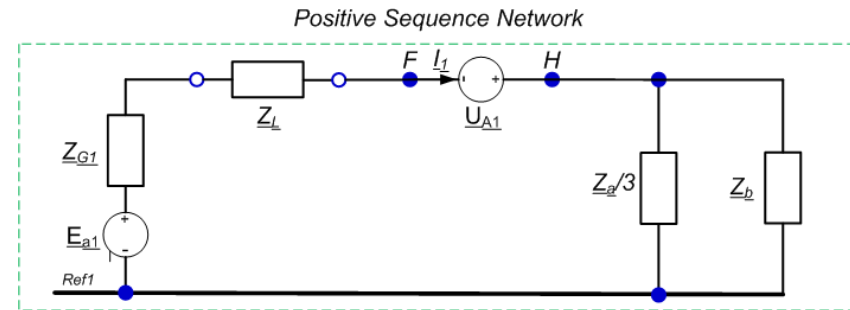- After converting U_A , U_B , and U_C to symmetrical components voltages U_0 , U_1 , and U_2 , they are inserted in the network.



NETWORKS MODELING – SERIAL UNBALANCE

- Utilizing Thevenin Theorem

$$Z_1 = Z_{G1} + Z_L + \frac{\frac{1}{3} \cdot Z_a \cdot Z_b}{\frac{1}{3} \cdot Z_a + Z_b}$$

$$Z_2 = Z_{G2} + Z_L + \frac{\frac{1}{3} \cdot Z_a \cdot Z_b}{\frac{1}{3} \cdot Z_a + Z_b}$$

$$Z_0 = Z_{G0} + Z_L + 3 \cdot Z_N + Z_b$$

- Circuit solution is described by

$$\underline{U}_1 = \underline{E}_1 - Z_1 \cdot \underline{I}_1$$

$$\underline{U}_2 = \underline{E}_2 - Z_2 \cdot \underline{I}_2$$




$$\underline{U}_0 = \underline{E}_0 - Z_0 \cdot \underline{I}_0$$

$$\underline{U}_1 = \underline{E}_1 - Z_1 \cdot \underline{I}_1$$

$$\underline{U}_2 = -Z_2 \cdot \underline{I}_2$$

$$\underline{U}_0 = -Z_0 \cdot \underline{I}_0$$

For balanced and symmetrical generator

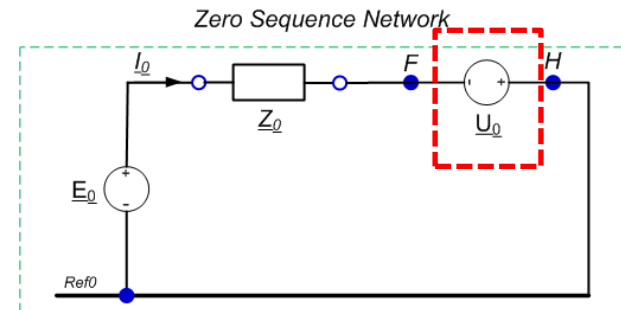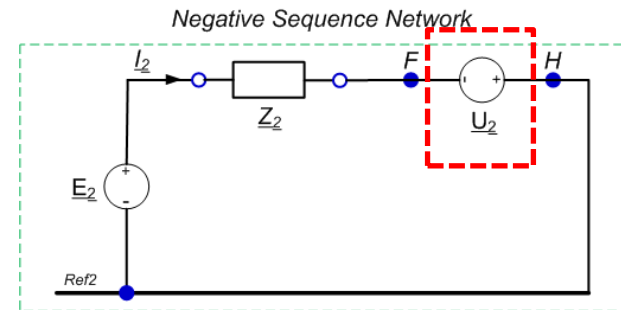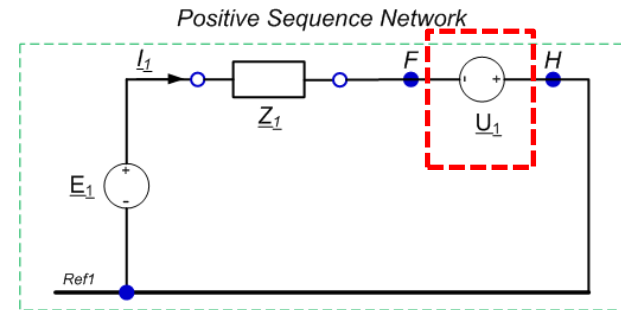

NETWORKS MODELING – SERIAL UNBALANCE

- Example

$$\underline{I}_A = 0$$

$$U_B = U_C = 0$$


$$\begin{pmatrix} \underline{U}_0 \\ \underline{U}_1 \\ \underline{U}_2 \end{pmatrix} = \frac{1}{3} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a} & \underline{a}^2 \\ 1 & \underline{a}^2 & \underline{a} \end{pmatrix} \cdot \begin{pmatrix} \underline{U}_A \\ 0 \\ 0 \end{pmatrix} = \frac{1}{3} \cdot \begin{pmatrix} \underline{U}_A \\ \underline{U}_A \\ \underline{U}_A \end{pmatrix}$$

$$\underline{U}_0 = \underline{U}_1 = \underline{U}_2$$

$$\underline{I}_A = 0$$

$$\begin{pmatrix} \underline{I}_a \\ \underline{I}_b \\ \underline{I}_c \end{pmatrix} = \begin{pmatrix} 1 & 1 & 1 \\ 1 & \underline{a}^2 & \underline{a} \\ 1 & \underline{a} & \underline{a}^2 \end{pmatrix} \cdot \begin{pmatrix} \underline{I}_{a0} \\ \underline{I}_{a1} \\ \underline{I}_{a2} \end{pmatrix}$$
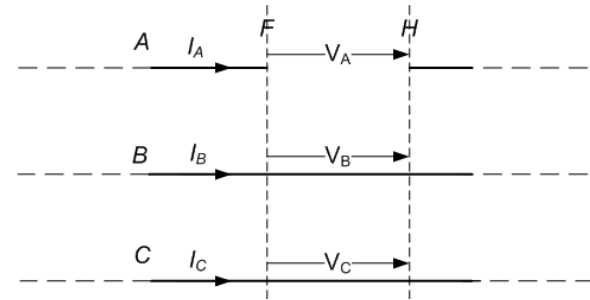
$$\underline{I}_A = \underline{I}_{a0} + \underline{I}_{a1} + \underline{I}_{a2} = 0$$



NETWORKS MODELING – SERIAL UNBALANCE

- Example

$$\underline{I}_A = \underline{I}_{a0} + \underline{I}_{a1} + \underline{I}_{a2} = 0$$

$$-Z_0 \cdot \underline{I}_0 = -Z_2 \cdot \underline{I}_2$$

$$\underline{I}_0 = \frac{Z_2 \cdot \underline{I}_2}{Z_0}$$

$$\frac{Z_2 \cdot \underline{I}_2}{Z_0} + \underline{I}_1 + \underline{I}_2 = 0$$

$$\underline{I}_2 = -\underline{I}_1 \cdot \frac{Z_0}{Z_0 + Z_2}$$

$$\underline{I}_0 = \frac{Z_2}{Z_0} \cdot \left(-\underline{I}_1 \cdot \frac{Z_0}{Z_0 + Z_2} \right) = -\underline{I}_1 \cdot \frac{Z_2}{Z_0 + Z_2}$$

$$\underline{U}_1 = \underline{E}_1 - Z_1 \cdot \underline{I}_1$$

$$\underline{U}_2 = -Z_2 \cdot \underline{I}_2$$

$$\underline{U}_0 = -Z_0 \cdot \underline{I}_0$$

NETWORKS MODELING – SERIAL UNBALANCE


- Example

$$\underline{U}_0 = \underline{U}_1 = \underline{U}_2 = -Z_2 \cdot I_2 = -Z_2 \cdot \left(-I_1 \cdot \frac{Z_0}{Z_0 + Z_2} \right) = I_1 \cdot \frac{Z_2 \cdot Z_0}{Z_0 + Z_2}$$


$$\underline{U}_1 = \underline{E}_1 - Z_1 \cdot I_1$$

$$I_1 \cdot \frac{Z_2 \cdot Z_0}{Z_0 + Z_2} = \underline{E}_1 - Z_1 \cdot I_1$$
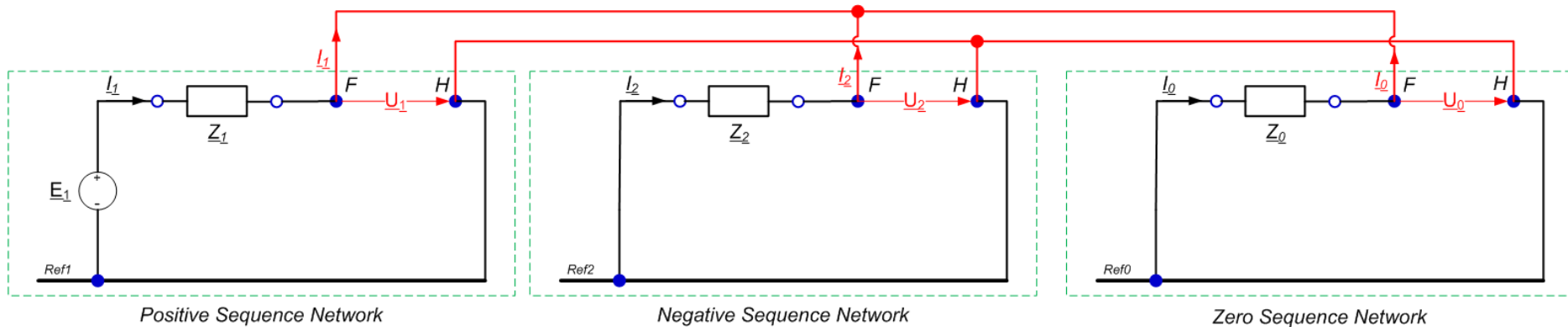
$$I_1 = \frac{\underline{E}_1}{Z_1 + \frac{Z_2 \cdot Z_0}{Z_0 + Z_2}}$$



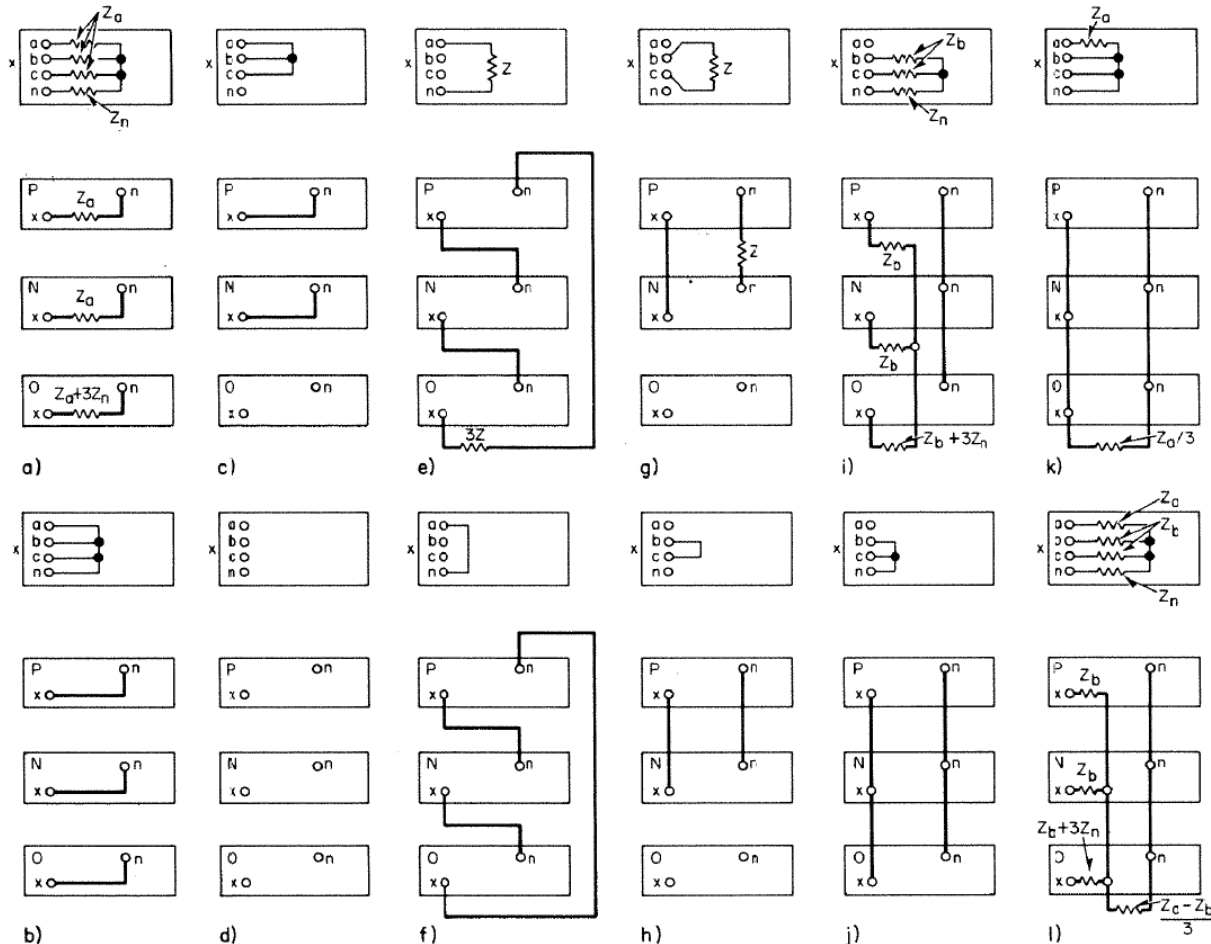
NETWORKS UNBALANCE MODELING – SHUNT FAULTS



Note:

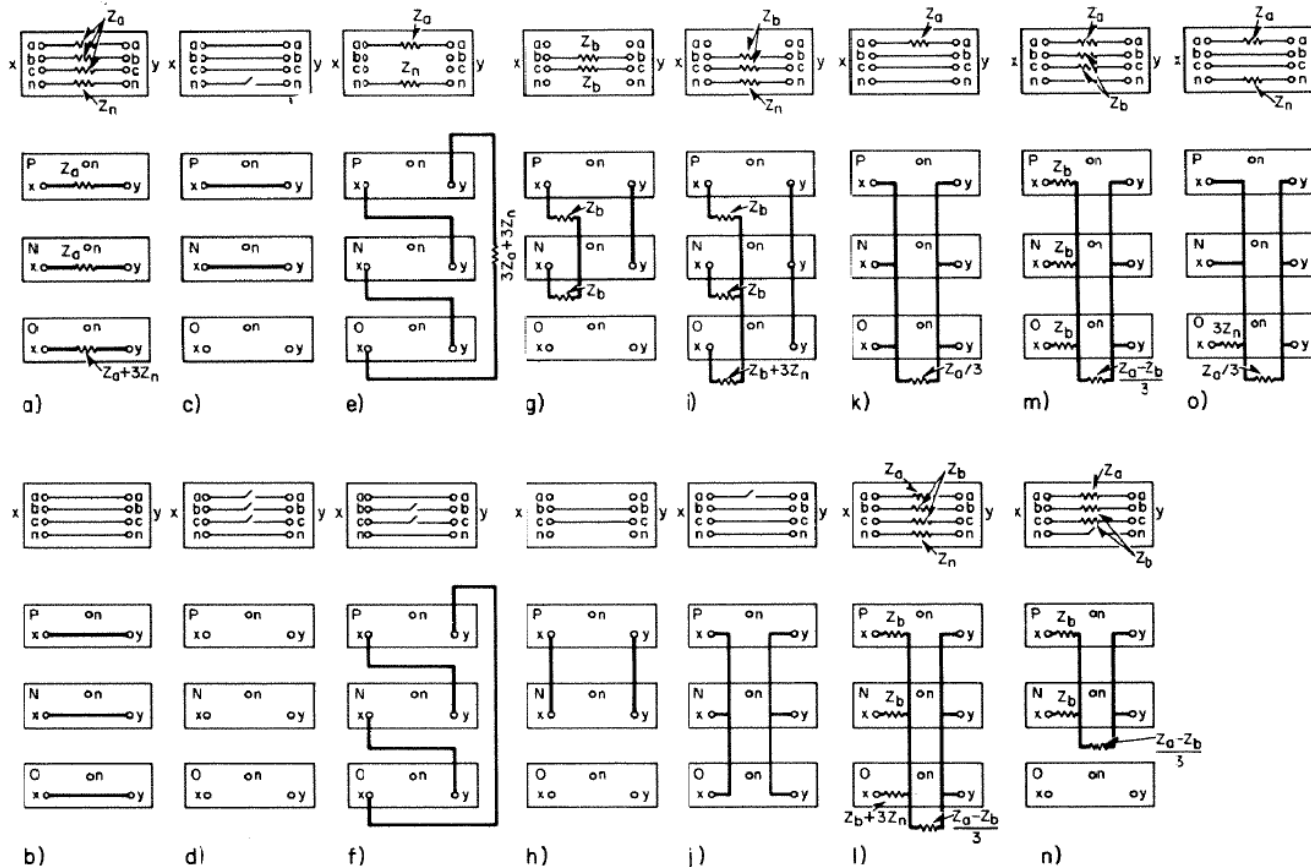- a) Balanced load or three-line-to-ground fault with impedances.
- b) A three-line-to-ground fault.
- c) A three-phase fault.
- d) A shunt circuit open.
- e) A line-to-ground fault through an impedance.
- f) A line-to-ground fault.
- g) A line-to-line fault through impedance.
- h) A line-to-line fault.
- i) A two-line-to-ground fault with impedance.
- j) A two-line-to-ground fault.
- k) A three-line-to-ground fault with impedance in phase a.
- l) Unbalanced load or three-line-to-ground fault with impedance.







NETWORKS UNBALANCE MODELING – SERIES FAULTS



Note:

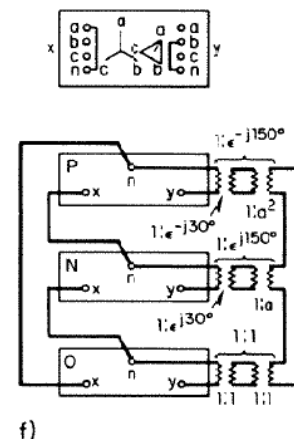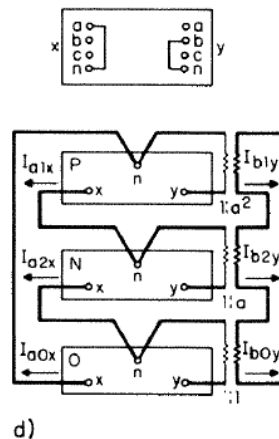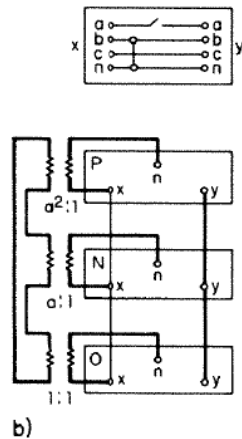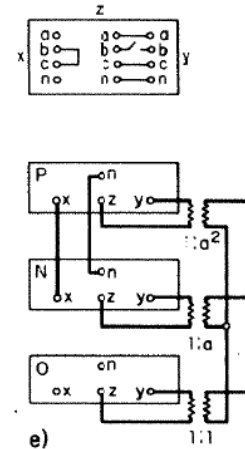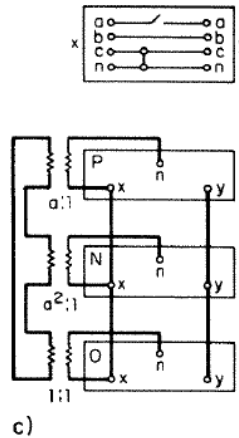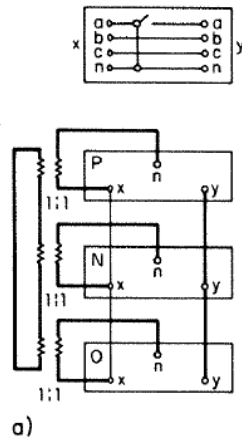- a) Equal impedances in three phases.
- b) Normal conditions.
- c) Neutral open.
- d) Any three or four phases open.
- e) Phases b and c open, impedances in phases a and neutral.
- f) Phases b and c open.
- g) Phases a and neutral open, impedance in b and c.
- h) Phases a and neutral open.
- i) Phase a open, impedances in b, c, and neutral.
- j) Phase a open.
- k) Impedance in phase a.
- l) Equal impedances in b and c phases, and neutral.
- m) Equal impedances in b and c phases.
- n) Equal impedances in b and c phases, neutral open.
- o) Impedances in phase a and neutral.

NETWORKS UNBALANCE MODELING – SIMULTANEOUS FAULTS / CROSS COUNTRY



Note:

- a) One phase open and a fault to ground.
- b) Phase a open and a b-phase-to-ground fault.
- c) Phase a open and c-phase-to-neutral fault.

- d) Phase a-to-ground fault at x and a b-phase-to-ground fault at y.
- e) A b-to-c fault at x, and b phase open z to y.
- f) Phase a-to-neutral fault at x, phase b-to-neutral fault on other side of star-delta transformer bank at y. x is taken as the reference point.

COMPONENTS MODELING

COMPONENTS MODELING

- Utility Sources and AC Generators
- Induction Machines
- Transformers
- Transmission Lines
- Notes on modeling

COMPONENTS MODELING – UTILITY SOURCES

- Request data from utility
 - Define inter-tie point location (GIS or other)
 - Define what is required:
 - I_{3ph} with X/R
 - I_{1ph} with X/R
 - Ops Conditions: max, min, normal
 - Special:

Future growth
Other prediction for
PCC (or POI)

The following information was provided in per unit on a 100MVA base @ 138kV:

System Configuration/ Scenario	Three Phase (I_A)	Single Phase ($3I_0$)	Thevenin's Equivalent Voltage Source	Thevenin's Equivalent System Impedance (p.u.)					
				Positive		Negative		Zero	
				Z	X/R	Z	X/R	Z	X/R
Both 138kV Lines In-Service	6620 MVA	4314 MVA	1.031 p.u.	0.0161	9.8	0.1595	9.7	0.0417	5.7
Ckt #84 to Channelview Out-of-Service	2513 MVA	1618 MVA	1.032 p.u.	0.0424	9.7	0.0424	9.6	0.1110	5.8
Ckt #84 to Jacinto Out-of-Service	4284 MVA	2729 MVA	1.032 p.u.	0.0249	9.5	0.0249	9.4	0.0674	5.5


COMPONENTS MODELING – UTILITY SOURCES

- Utility is modeled as a fixed source with fixed impedances
- ANSI methodology allows for close by generation but does not adjust impedance. It is expected that system engineer does this calcs on his own per application (i.e. decrement curve calcs).


$$R = \frac{1}{(1 + XR^2)^{\frac{1}{2}}} \cdot Z$$

$$X = \frac{XR}{(1 + XR^2)^{\frac{1}{2}}} \cdot Z$$


Positive Sequence Network

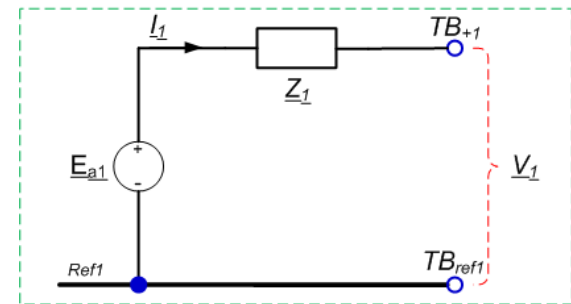

Negative Sequence Network

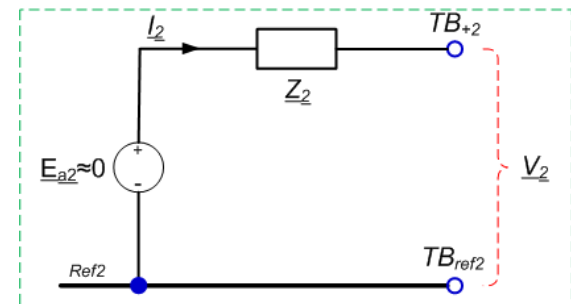

Zero Sequence Network

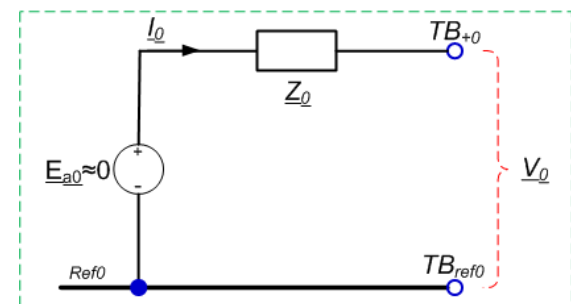

COMPONENTS MODELING – AC GENERATOR

- Fault Behavior
 - Sudden change in voltage and current, such as those in faults, produces transients
 - Armature current divided into two components:
 - Symmetrical AC component – whose associated component in the field is a DC current
 - DC component – whose associated component in the field is an AC current

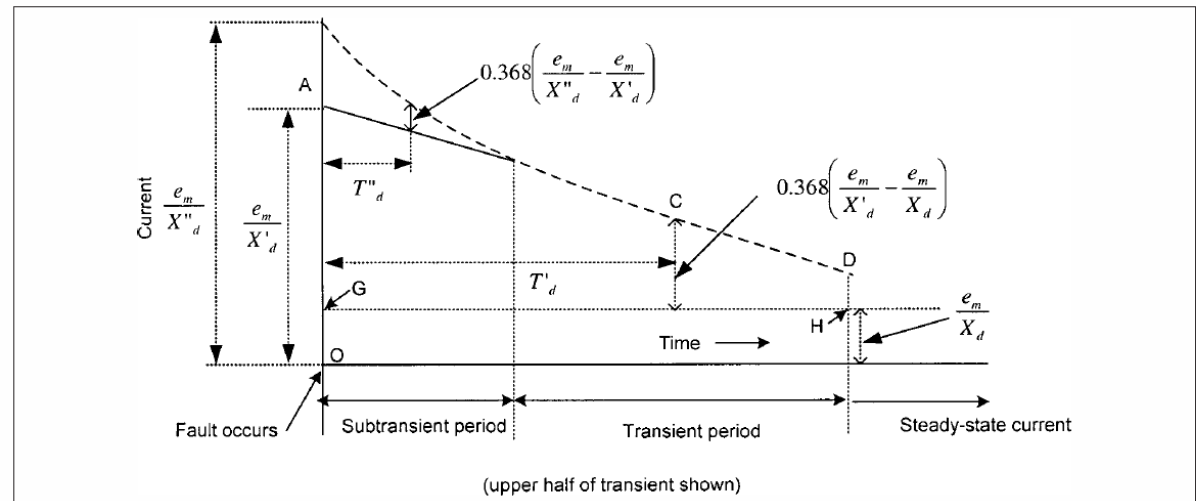


FIGURE 10-5 Decaying ac component of the short-circuit current from the instance of occurrence of fault to steady state. The subtransient, transient, and steady-state periods and decay characteristics of short-circuit current are shown.

COMPONENTS MODELING – AC GENERATOR

- Reactances change with time, i.e. model changes with time

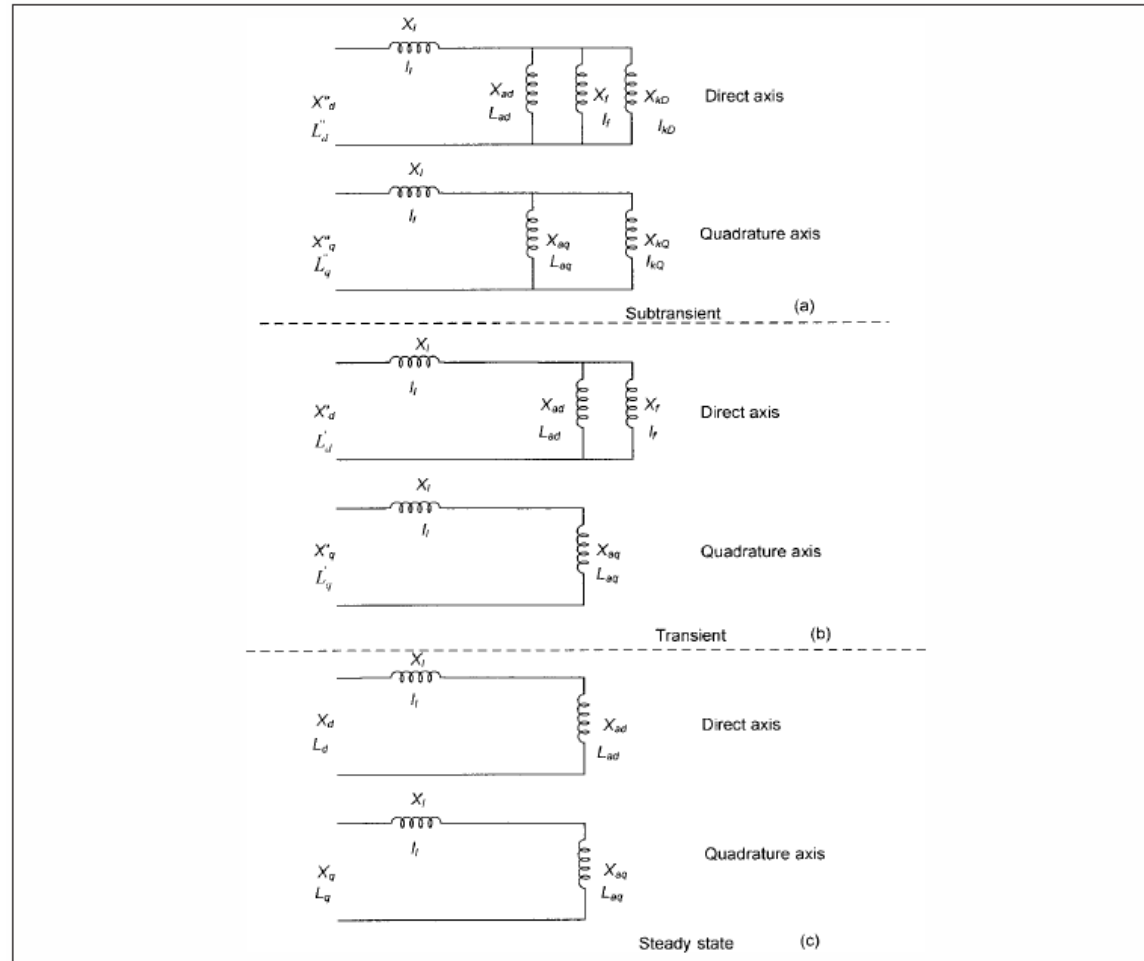


FIGURE 10-6 Equivalent circuits of a synchronous generator during subtransient, transient, and steady-state periods after a terminal fault.

COMPONENTS MODELING – AC GENERATOR

- Symmetrical Component Modeling
 - Principle concern is with symmetrical component and its associated constants
 - DC component often eliminated from studies
 - Usually not necessary to apply or set protective relays
 - If necessary (e.g. circuit breaker applications), various factors are available from standards, manufacturers, or other sources
 - For synchronous machines, symmetrical AC component can be resolved into three distinct components
 - Subtransient component – the double prime ($''$) values
 - Transient component – the single prime ($'$) values
 - The steady-state component

COMPONENTS MODELING – AC GENERATOR

- Subtransient Component
 - Occurs during commencement of fault
 - Subtransient reactance (X_d'') *approaches armature* leakage reactance but is higher as a result of damper windings, and so on.
 - Subtransient time constant (T_d'') *is very low* (because damper windings have relatively high resistance), typically around 0.01–0.05 seconds

COMPONENTS MODELING – AC GENERATOR

- Transient Component
 - Armature current demagnetizes the field and decrease flux linkages with the field winding
 - Transient reactance (X_d') *includes effect of both* armature and field leakages and is higher than armature leakage reactance, and thus higher than the subtransient reactance
 - Transient time constant (T_d') *varies typically from 0.35 to 3.3 seconds*
- Steady-State Component
 - Transient eventually decays
 - For faults, eventually becomes unsaturated direct axis reactance (X_d)

COMPONENTS MODELING – AC GENERATOR

- Negative Sequence

- Subtransient reactance can be measured by blocking the rotor with the field winding shorted and applying single phase voltage across any two terminals
- As position of rotor is changed, measured reactance varies considerably if machine has salient poles without dampers (and very little damper winding exists) or if the machine has a round rotor
- For negative sequence, similar phenomenon exists except rotor is at $2f$ with relation to field set up by applied voltage
- Good approximation: $X_2 = \frac{1}{2}(X_d'' + X_q'')$


COMPONENTS MODELING – AC GENERATOR

- Zero Sequence
 - Varies quite a lot
 - Depends largely on pitch and breadth factors of armature winding
 - Generally, X_0 is much smaller than X_1 and X_2 values


COMPONENTS MODELING – AC GENERATOR

Close and Remote Generation

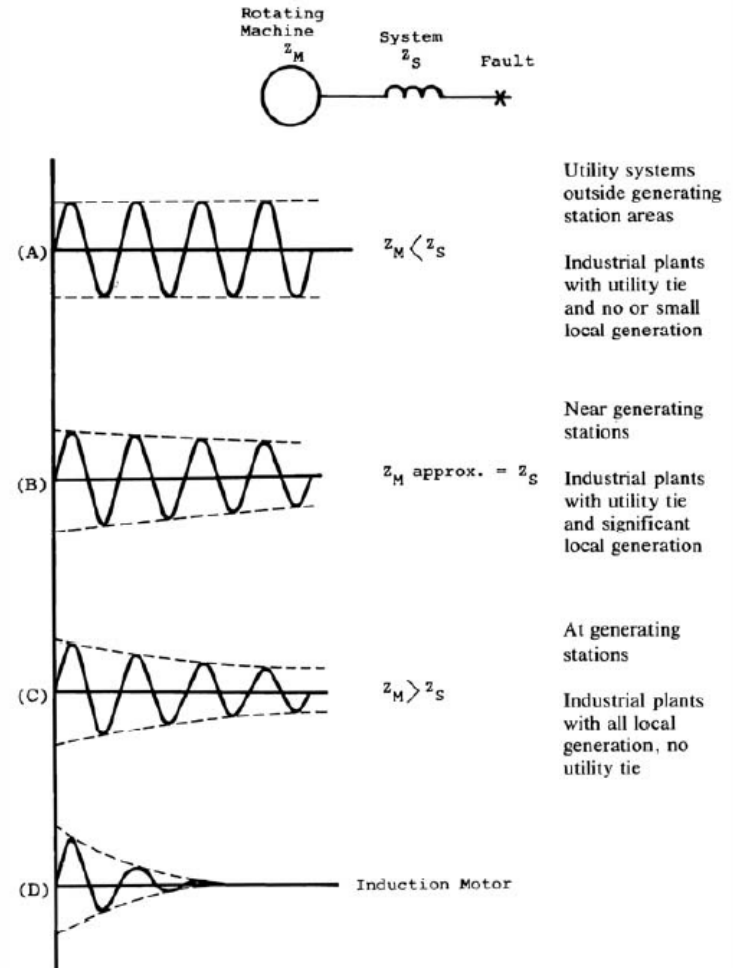
- Assume $X_1 = X_2$
- Calculate X_1 from 3PH fault duty
- Calculate X_0 from SLG fault duty




COMPONENTS MODELING – AC GENERATOR

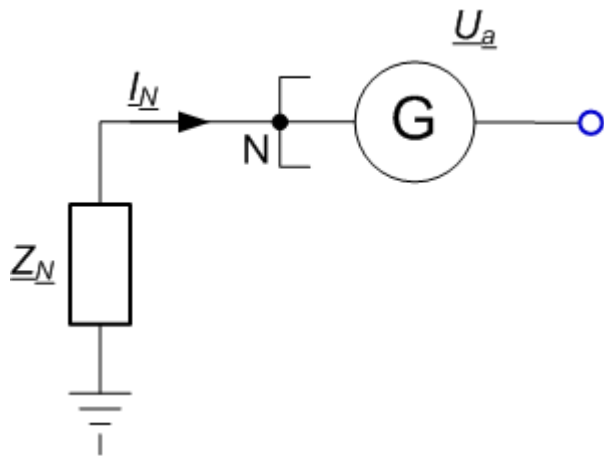


Positive Sequence Network

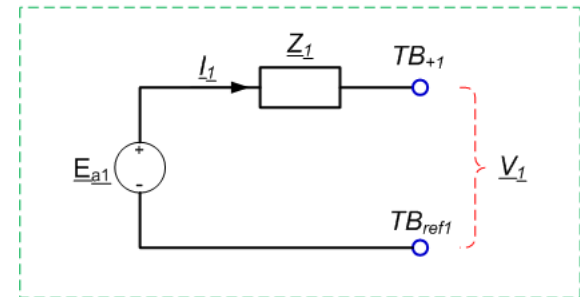

Negative Sequence Network

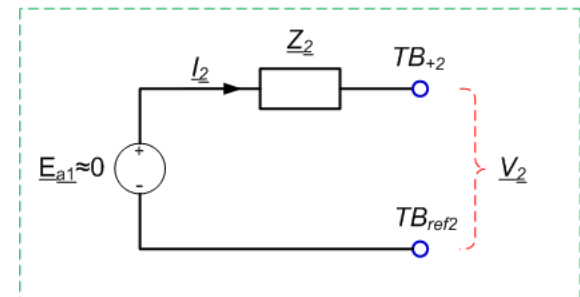

Zero Sequence Network

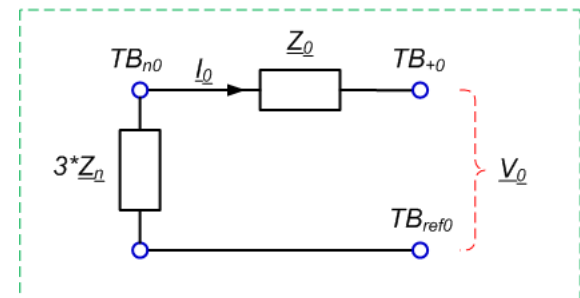

COMPONENTS MODELING – AC GENERATOR

	Two-pole		Four-pole	
	Conventional cooled	Conductor cooled	Conventional cooled	Conductor cooled
Turbine generators				
X_d (unsat)	1.65/1.0–1.75	1.85/1.5–2.25	1.65/1.0–1.75	1.85/1.5–2.25
X_q rated current	1.61/0.96–1.71	1.81/1.46–2.21	1.61/0.96–1.71	1.81/1.46–2.21
X'_d rated voltage	0.17/0.12–0.25	0.28/0.20–0.35	0.25/0.2–0.3	0.35/0.25–0.45
X''_d rated voltage	0.12/0.08–0.18	0.22/0.15–0.28	0.16/0.12–0.20	0.28/0.20–0.32
X_2 rated current	= X''_d	= X''_d	= X''_d	= X''_d
X_o rated current ⁽¹⁾				
x_p Potier reactance	0.07–0.17	0.2–0.45	0.12–0.24	0.25–0.45
r_2 ⁽²⁾	0.025–0.04	0.025–0.04	0.03–0.045	0.03–0.045
r_1 ⁽³⁾	0.004–0.011	0.001–0.008	0.003–0.008	0.001–0.008
r_a ⁽³⁾	0.001–0.007	0.001–0.005	0.001–0.005	0.001–0.005
T'_{d0}	5	5	8	6
T'_d	0.6	0.75	1.0	1.2
T''_d	0.035	0.035	0.035	0.035
T_a	0.13–0.45	0.2–0.55	0.2–0.4	0.25–0.55
H	2.5–3.5	2.5–3.5	3–4	3–4

Salient Pole Generators and Motors:

With dampers— $X'_d = 0.37/0.25–0.5$, $X''_d = 0.24/0.13–0.32$, $X_2 = X''_d$ ← X''_d

Without dampers— $X'_d = 0.35/0.25–0.5$, $X''_d = 0.32/0.20–0.5$, $X_2 = 0.4/0.3–0.45$.

Synchronous condensers:

$X'_d = 0.40$, $X''_d = 0.25$, $X_2 = 0.24$.

Notes: (1) X_o varies so critically with armature winding pitch that an average value can hardly be given. Variation is from 0.1 to 0.7 of X''_d ; (2) r_2 varies with damper resistance; (3) r_1 and r_a vary with machine rating.

COMPONENTS MODELING – AC GENERATOR

- Example of vendor provided data

DATA SHEET SYNCHRONOUS MACHINES

BASIC DATA				ELECTRICAL DATA			
Date:				Standards: NEMA MG1			
Order no.:							
Ordered by:				Gen. stator resistance: 0,0135 Ohm at 20 °C			
Destination:				Gen. rotor resistance 0,0586 Ohm at 20 °C			
Type:				Exc. stator resistance 4,7 Ohm at 20 °C			
Rated voltage:	13800	V,	60 Hz	REACTANCES Unsaturated saturated			
Rated load:	22210	kW, at p.f. 0,85		d-axis synchronous:	1,97	p.u.	1,48 p.u.
Speed:	1800	rpm		transient:	0,31	p.u.	0,24 p.u.
Rated current:	1093	A		sub transient:	0,20	p.u.	0,17 p.u.
Rated temperature:	95	°F		q-axis synchronous:	1,02	p.u.	0,76 p.u.
Method of cooling: IC616				sub transient:	0,40	p.u.	0,28 p.u.
Degree of protection: IP55				Negative sequence:	0,30	p.u.	0,23 p.u.
Mounting arrangement: IM1005				Zero sequence:	0,11	p.u.	
Insulation class Stator: F, temp rise to B				Potier reactance	0,28	p.u.	
Insulation class Rotor: F, temp rise to B				Short Circuit Ratio:	0,55		
Insulation class Exciter: F, temp rise to B				TIME CONSTANTS			
Type of excitation: brushless				d-axis transient short circuit:		1,29	sec.
Exciter type: DGBP60/15				d-axis transient open circuit:		8,2	sec.
P.M.G.: 540/40 (6000 VA; 225 V; 1 phase)				d-axis subtransient short circuit:		0,04	sec.
Exciter response: 2,39 1/sec				d-axis subtransient open circuit:		0,06	sec.
		Stator	Rotor	q-axis subtransient short circuit:		0,04	sec.
No load volt.	13	20	V	q-axis subtransient open circuit:		0,10	sec.
No load current	2,2	264	A	Armature:		0,24	sec.
Exc. rated volt.	41	56	V	Short Circuit Conditions			
Rated current	6,3	744	A	3 phase Peak	17337	A	15,9 p.u.
Ceiling volt.	73,5	110	V	3 phase RMS	6052	A	5,5 p.u.
Ceiling current	12,1	1449	A	2 phase Peak	11042	A	10,1 p.u.
Doc. nr. : 1-OPF-20024-WGN				Steady state	1853	A	1,7 p.u.
Version #: ITFM				LANG :			
				MECHANICAL PROPERTIES			
				Acceleration time Tj 3,1 sec			
				Inertia constant H 1,33 kWsec/kVA			
				Damping factor kd 16,1 MW/Hz			
				Direction of rotation: CW/CCW			
				Rotortype: salient poles			
				Poles are: massive without damperwinding			
				Shaft extension: Flange			
				LOSSES AT NOMINAL RATING			
				Friction and windage losses 160 kW			
				Core losses 146 kW			
				Stray load losses 57 kW			
				Armature I²R losses @ 95°C 63 kW			
				Field I²R losses: 42 kW			
				EFFICIENCIES, tol. on losses acc. to IEC 60034			
				4/4 3/4 1/2 1/4			
				p.f. 1.0 98,17 97,83 97,05 94,58			
				p.f. 0,85 97,92 97,64 96,91 94,49			

COMPONENTS MODELING – INDUCTION MACHINES

- Positive Sequence
 - Changes from stalled to running
 - ~ 0.15 pu stalled (X_d'')
 - 0.9–1.0 pu running
- Negative Sequence
 - Remains effectively constant
 - ~ 0.15 pu (X_d'')
- Zero Sequence
 - 0.0 if WYE ungrounded or DELTA connected

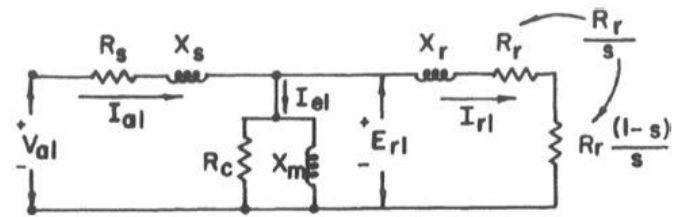


Fig. 6.18. Positive sequence induction motor equivalent circuit.

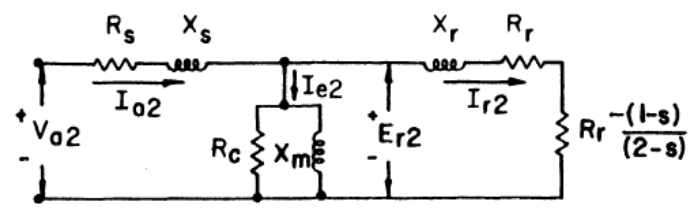


Fig. 6.20. Negative sequence induction motor equivalent circuit.

- $R_s = 0.01$ pu = Stator Resistance
- $jX_s =$ Stator Leakage Reactance at Rated Frequency
- $R_r = 0.01$ pu = Rotor Resistance
- $jX_r =$ Rotor Leakage Reactance at Rated Frequency
- $JX_m = j3.0$ pu = Shunt Exciting Reactance
- $jX = jX_s + jX_r = jX_d'' = j0.15$ pu

Values shown are typical for an induction motor and are per unit on the motor kVA and kV base

$$S = \frac{\text{Synchronous RPM} - \text{Rotor RPM}}{\text{Synchronous RPM}} = \begin{matrix} 1.0 & \text{for stalled condition} \\ 0+ & \text{for running conditions} \end{matrix}$$

COMPONENTS MODELING – INDUCTION MACHINES

Table 6.3. Approximate Constants for Three-Phase Induction Motors

Rating	Full Load Efficiency	Full Load Power Factor	Full Load Slip	R and X in per Unit*			
				$X_s + X_r^\dagger$	X_m	R_s	R_r
(HP)	(%)	(%)	(%)	(pu)	(pu)	(pu)	(pu)
Up to 5	75-80	75-85	3.0-5.0	0.10-0.14	1.6-2.2	0.040-0.06	0.040-0.06
5-25	80-88	82-90	2.5-4.0	0.12-0.16	2.0-2.8	0.035-0.05	0.035-0.05
25-200	86-92	84-91	2.0-3.0	0.15-0.17	2.2-3.2	0.030-0.04	0.030-0.04
200-1000	91-93	85-92	1.5-2.5	0.15-0.17	2.4-3.6	0.025-0.03	0.020-0.03
Over 1000	93-94	88-93	~1.0	0.15-0.17	2.6-4.0	0.015-0.02	0.015-0.025


Source: Clarke [11, vol. 2]. Used with permission of the publisher.

*Based on full load kVA rating and rated voltage.


†Assume that $X_s = X_r$ for constructing the equivalent circuit.

$$E_m = V_{a1} - jI_{a1}(X_s + X_r)$$
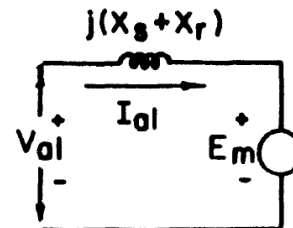
$$T_r = (X_s + X_r) / \omega_1 R_r \text{ sec}$$



POSITIVE SEQUENCE

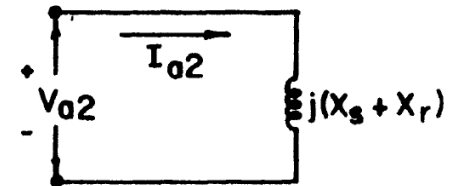

NEGATIVE SEQUENCE

COMPONENTS MODELING – TRANSFORMERS

- Modeling
 - Usually modeled as a series impedance
 - Shunt parameters can be calculated by review of transformer tests
 - Shunt parameters don't generally impact analysis
 - Transformer winding configuration determines sequence networks
 - Three winding transformers have interesting sequence networks, but close inspections shows them to be intuitive

COMPONENTS MODELING – TRANSFORMERS

No	Winding Connections	Zero Sequence Circuit	Positive or Negative Sequence Circuit
1			
2			
3			
4			
5			
6			
7			
8			
9			
10			

COMPONENTS MODELING – TRANSFORMERS

NO	Winding Connections	Zero Sequence Circuit	Positive or Negative Sequence Circuit
1			
2			
3			
4			
5			
6			

COMPONENTS MODELING – TRANSFORMERS

- 3 Winding Transformer Impedance
 - Usually given as a winding-to-winding (delta) impedances in %
 - Convert to equivalent WYE impedances for sequence network analysis
 - Often times, the base power is different for various impedances
 - Ex: 100 MVA autotransformer with 35 MVA tertiary
 - May show Z_{HM} on 100 MVA base
 - May show Z_{HL} and Z_{ML} on 35 MVA base
- Must convert delta impedance to common base before converting to equivalent WYE network

COMPONENTS MODELING – TRANSFORMERS

- 3 Winding Transformer Impedances
 - Delta-WYE Conversion Formula

$$Z_H = \frac{1}{2}(Z_{HM} + Z_{HL} - Z_{ML})$$





$$Z_M = \frac{1}{2}(Z_{ML} + Z_{HM} - Z_{HL})$$

$$Z_L = \frac{1}{2}(Z_{HL} + Z_{ML} - Z_{HM})$$

Z_{HM} = leakage impedance between the H and M windings, as measured on the H winding with M winding short-circuited and L winding open circuited; Z_{HL} = leakage impedance between the H and L windings, as measured on the H winding with L winding short-circuited and M winding open circuited; Z_{ML} = leakage impedance between the M and L windings, as measured on the M winding with L winding short-circuited and H winding open circuited.

COMPONENTS MODELING – TRANSMISSION LINES

Equivalent circuit and equations for overhead lines

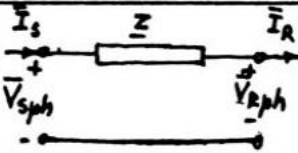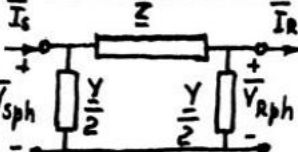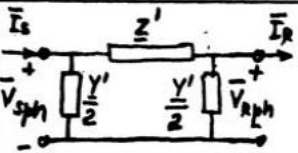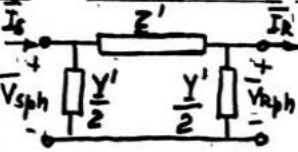Line type / Characteristics	Length range (Km/mile)	\underline{K}_z	\underline{K}_y	Equivalent circuit (π)	Equations
short-lines	$l \leq 80/50$	1	1		$\begin{cases} \bar{V}_{sph} = \bar{V}_{Rph} + \underline{Z} \bar{I}_R \\ \bar{I}_s = \bar{I}_R \end{cases}$
medium-length lines	$80/50 \leq l \leq 240/150$	1	1		$\begin{cases} \bar{V}_{sph} = (1 + \frac{\underline{Z} \underline{Y}}{2}) \bar{V}_{Rph} + \underline{Z} \bar{I}_R \\ \bar{I}_s = \underline{Y} (1 + \frac{\underline{Z} \underline{Y}}{4}) \bar{V}_{Rph} + (1 + \frac{\underline{Z} \underline{Y}}{2}) \bar{I}_R \end{cases}$
long lines	$240/150 \leq l$	$\frac{\sinh \sqrt{\underline{Z} \underline{Y}}}{\sqrt{\underline{Z} \underline{Y}}}$	$\frac{2(\cosh \sqrt{\underline{Z} \underline{Y}} - 1)}{\sqrt{\underline{Z} \underline{Y}} \sinh \sqrt{\underline{Z} \underline{Y}}}$		$\begin{cases} \bar{V}_{sph} = (1 + \frac{\underline{Z}' \underline{Y}'}{2}) \bar{V}_{Rph} + \underline{Z}' \bar{I}_R \\ \bar{I}_s = \underline{Y}' (1 + \frac{\underline{Z}' \underline{Y}'}{4}) \bar{V}_{Rph} + (1 + \frac{\underline{Z}' \underline{Y}'}{2}) \bar{I}_R \end{cases}$
	$(\frac{240/150}{320/200})^* \leq l \leq$	$1 + \frac{\underline{Z} \underline{Y}}{6} + \frac{(\underline{Z} \underline{Y})^2}{120} + \dots$	$\frac{1 + \frac{\underline{Z} \underline{Y}}{12} + \frac{(\underline{Z} \underline{Y})^2}{360} + \dots}{1 + \frac{\underline{Z} \underline{Y}}{6} + \frac{(\underline{Z} \underline{Y})^2}{120} + \dots}$		$\begin{cases} \bar{V}_{sph} = (1 + \frac{\underline{Z}' \underline{Y}'}{2}) \bar{V}_{Rph} + \underline{Z}' \bar{I}_R \\ \bar{I}_s = \underline{Y}' (1 + \frac{\underline{Z}' \underline{Y}'}{4}) \bar{V}_{Rph} + (1 + \frac{\underline{Z}' \underline{Y}'}{2}) \bar{I}_R \end{cases}$

Comment: $\underline{Z}' = \underline{K}_z \cdot \underline{Z}$; $\underline{Y}' = \underline{K}_y \cdot \underline{Y}$; *) Particular length range for long lines.

COMPONENTS MODELING – TRANSMISSION LINES

Positive and Negative Sequence Impedance

- Passive component
- Assume line symmetry and transpositions
- Calculations with simplified formula types:

$$L_1 = L_2 = \frac{\mu_0}{2\pi} \ln \frac{D_m}{D_s} \text{ [H/m]}$$

$$X = \omega L = 2\pi fL$$

$$X_1 = X_2 = 4\pi \times 10^{-7} \ln \frac{D_m}{D_s} \text{ [\Omega/m]}$$

$$R_1 = R_2 = \text{conductor AC resistance (tables)}$$

- From tables:

$$\mathbf{Z} = r_a + j(X_a + X_d)$$

COMPONENTS MODELING – TRANSMISSION LINES


- Zero Sequence Impedance
 - More involved
 - Assumptions
 - Zero sequence current divides equally between conductors
 - Conductors are parallel to ground
 - Earth is a solid with a plane surface, infinite in extent, and of uniform conductivity
 - None of the assumptions are true
 - We get acceptable error with these assumptions
 - Line design affects calculation techniques

COMPONENTS MODELING – TRANSMISSION LINES

Positive and Negative Sequence Impedance

- Cannot assume line symmetry or transpositions
 - General principle has to be applied and all self and mutual impedances are calculated from formulas
 - No tabulation of impedances
- T-line series impedance (or admittance) matrix is not symmetrical. Similarly, shunt susceptances and conductance is not symmetrical as well.

SYMMETRICAL COMPONENTS - EXAMPLES

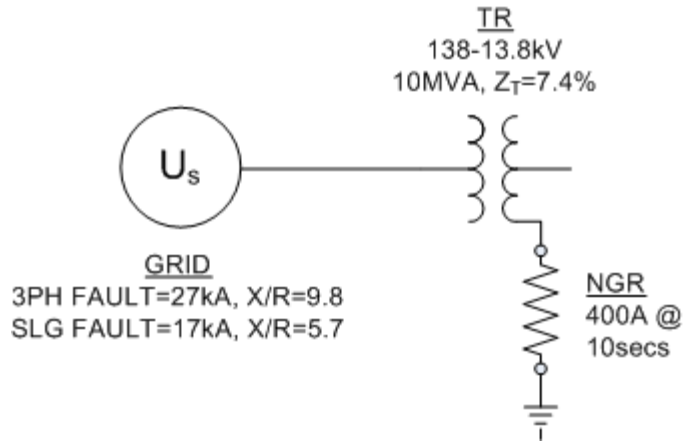

Assumptions:

$$\underline{E}_{a1} := (1 + j \cdot 0) \text{ pu} \quad \underline{E}_{a2} = \underline{E}_{a0} = 0$$

Base Quantities:

$$S_{\text{base}} := 10 \text{ MVA}$$


$$V_{\text{base1}} := 138 \text{ kV}$$

$$I_{\text{base1}} := \frac{S_{\text{base}}}{\sqrt{3} \cdot V_{\text{base1}}} = 41.84 \text{ A}$$


$$V_{\text{base2}} := 13.8 \text{ kV}$$

$$I_{\text{base2}} := \frac{S_{\text{base}}}{\sqrt{3} \cdot V_{\text{base2}}} = 418.37 \text{ A}$$


Positive Sequence Network

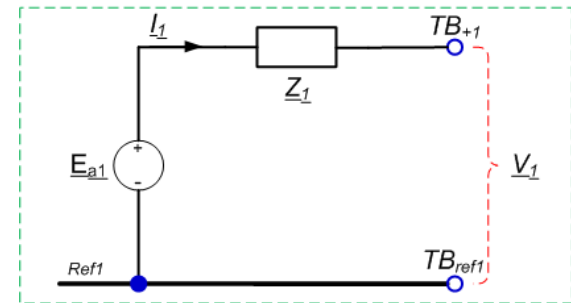

Negative Sequence Network

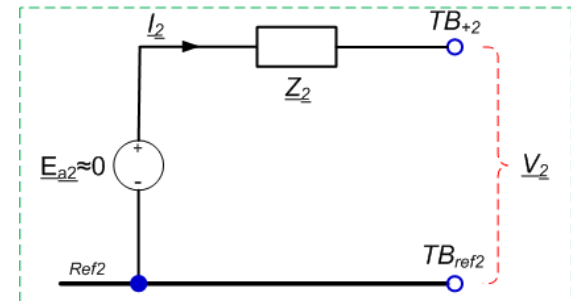


Zero Sequence Network

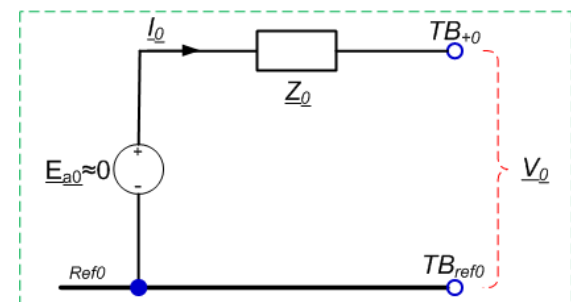


SYMMETRICAL COMPONENTS - EXAMPLES

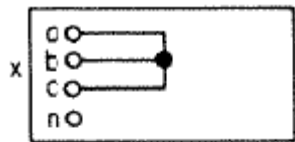
- 3PH Fault @ HS of TR, w/o Z_f , w/o ground







Positive Sequence Network

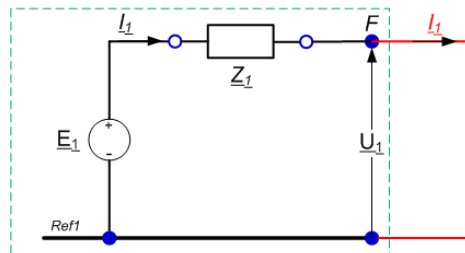

Negative Sequence Network

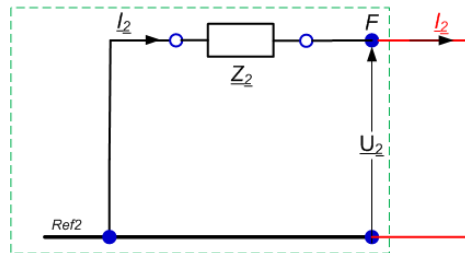

Zero Sequence Network

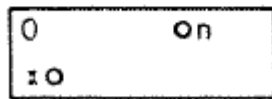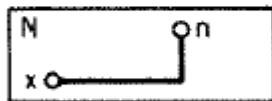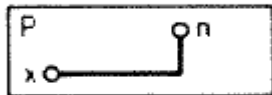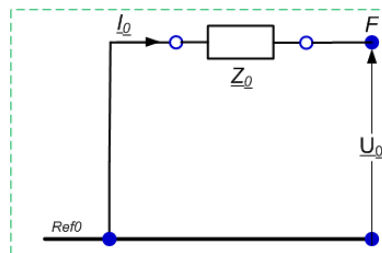

c)

$$I_{sc_3PH.a.pu} := \frac{27kA}{I_{base1}} \cdot e^{-j \cdot (\text{atan}(9.8))} = (65.51 - 642.03i) \cdot pu$$

$$z2r\theta(I_{sc_3PH.a.pu}) = "(645.3621 \angle -84.17^\circ)" \cdot pu$$

$$I_{sc_3PH.b.pu} := a^2 \cdot I_{sc_3PH.a.pu} = (-588.77 + 264.28i) \cdot pu$$

$$z2r\theta(I_{sc_3PH.b.pu}) = "(645.3621 \angle 155.83^\circ)" \cdot pu$$

$$I_{sc_3PH.c.pu} := a \cdot I_{sc_3PH.a.pu} = (523.26 + 377.75i) \cdot pu$$

$$z2r\theta(I_{sc_3PH.c.pu}) = "(645.3621 \angle 35.83^\circ)" \cdot pu$$

$$\begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix} := \frac{1}{3} \cdot \begin{pmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{pmatrix} \cdot \begin{pmatrix} I_{sc_3PH.a.pu} \\ I_{sc_3PH.b.pu} \\ I_{sc_3PH.c.pu} \end{pmatrix} = \begin{pmatrix} 0 \\ 65.51 - 642.03i \\ 0 \end{pmatrix} pu$$

$$z2r\theta M \begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} "(0 \angle 14.0362^\circ)" \\ "(645.3621 \angle -84.1737^\circ)" \\ "(0 \angle -45^\circ)" \end{pmatrix} pu$$



$$Z_1 := \frac{E_{a1}}{I_1} = (0.0001573 + 0.00154151i) pu$$

$$z2r\theta(Z_1) = "(0.0015 \angle 84.17^\circ)" pu$$

$$Z_2 = Z_1$$

SYMMETRICAL COMPONENTS - EXAMPLES

- SLG Fault @ HS of TR, w/o Z_f

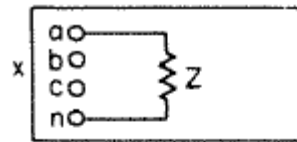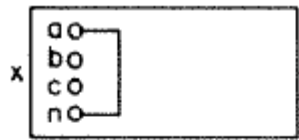

Assumptions:


$$\underline{I}_0 = \frac{\underline{E}_{a1}}{\underline{Z}_1 + \underline{Z}_2 + \underline{Z}_0 + 3 \cdot \underline{Z}_f} \quad \underline{Z}_f = 0 \quad \underline{Z}_1 = \underline{Z}_2$$

$$\underline{I}_{a0.pu} := \frac{17kA}{I_{base1}} \cdot e^{-j \cdot (\text{atan}(5.7))} = (70.22 - 400.23i) \cdot pu$$


$$z_{2r\theta}(\underline{I}_{a0.pu}) = "(406.3391 \angle -80.05^\circ)" \cdot pu$$

$$\underline{Z}_0 := \frac{\underline{E}_{a1}}{\underline{I}_{a0.pu}} - 2 \cdot \underline{Z}_1 = 0.00011066 - 0.00065905i$$
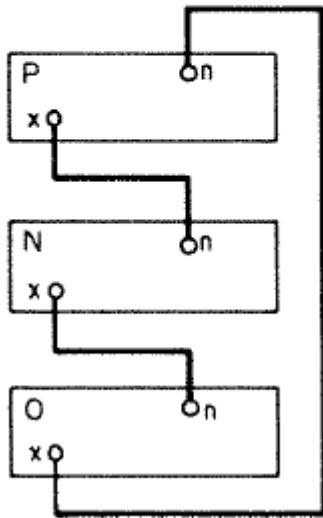
$$z_{2r\theta}(\underline{Z}_0) = "(0.0007 \angle -80.47^\circ)" \cdot pu$$







f)

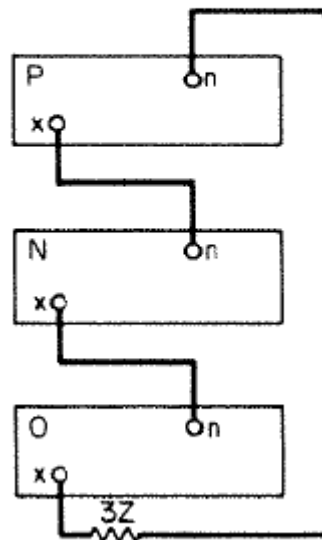




e)

SYMMETRICAL COMPONENTS - EXAMPLES

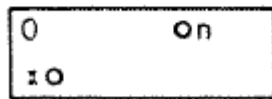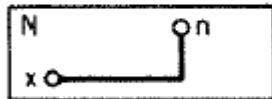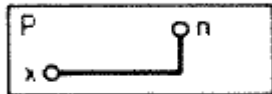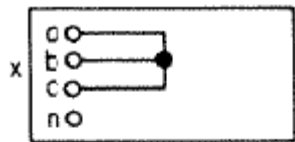- 3PH Fault @ LS of TR, w/o Z_f , w/o ground



c)

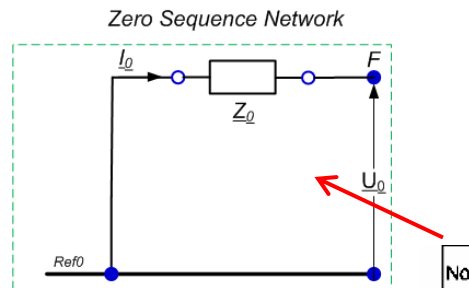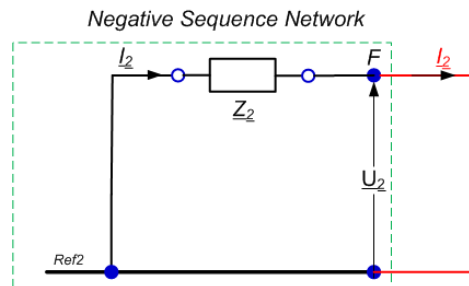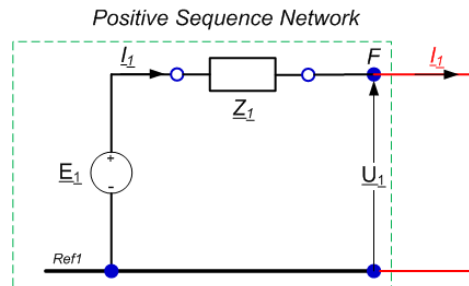

Assumptions:

$$\underline{Z}_{TR0} = \underline{Z}_{TR1} = \underline{Z}_{TR2} = j \cdot 0.074 \text{ pu} \quad \underline{Z}_1 = (0.000157 + 0.001542i) \text{ pu}$$

$$\underline{I}_1 := \frac{\underline{E}_{a1}}{\underline{Z}_1 + \underline{Z}_{TR1}} = (0.02756436 - 13.23769705i) \text{ pu}$$

$$z2r\theta(\underline{I}_1) = "(13.2377 \angle -89.88^\circ)" \text{ pu}$$


$$\begin{pmatrix} \underline{I}_a \\ \underline{I}_b \\ \underline{I}_c \end{pmatrix} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{pmatrix} \cdot \underline{I}_1 = \begin{pmatrix} 0.03 - 13.24i \\ -11.48 + 6.59i \\ 11.45 + 6.64i \end{pmatrix} \text{ pu}$$

$$z2r\theta M \begin{pmatrix} \underline{I}_a \\ \underline{I}_b \\ \underline{I}_c \end{pmatrix} = \begin{pmatrix} "(13.2377 \angle -89.8807^\circ)" \\ "(13.2377 \angle 150.1193^\circ)" \\ "(13.2377 \angle 30.1193^\circ)" \end{pmatrix} \text{ pu}$$

No	Winding Connections	Zero Sequence Circuit	Positive or Negative Sequence Circuit
1			

SYMMETRICAL COMPONENTS - EXAMPLES

- SLG Fault @ LS of TR, w/o Z_f

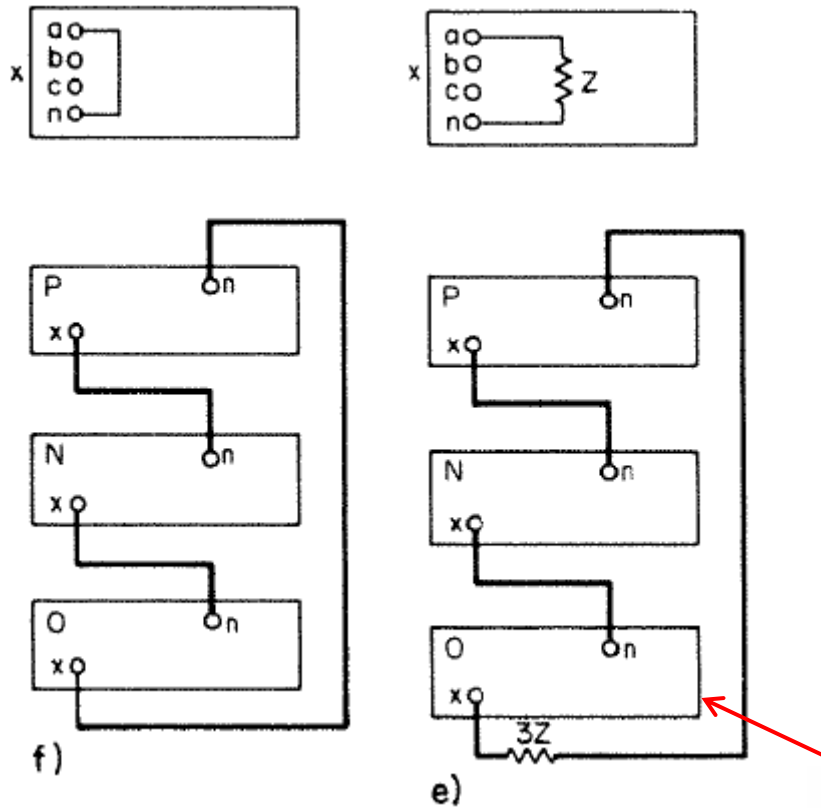

Assumptions:

$$\begin{aligned} \underline{I}_1 &= \underline{I}_2 = \underline{I}_0 & \underline{Z}_f &= 0 \\ \underline{Z}_1 &= \underline{Z}_1 + \underline{Z}_{TR} & \underline{Z}_2 &= \underline{Z}_1 & \underline{Z}_0 &= \underline{Z}_{TR} + 3 \cdot \underline{Z}_f = \underline{Z}_{TR} \end{aligned}$$

$$\underline{E}_{a1} = \underline{I}_0 \cdot (\underline{Z}_1 + \underline{Z}_2 + \underline{Z}_0 + 3 \cdot \underline{Z}_f)$$

$$\underline{E}_{a1} = \underline{I}_0 \cdot (\underline{Z}_1 + \underline{Z}_{TR} + \underline{Z}_1 + \underline{Z}_{TR} + \underline{Z}_{TR})$$

$$\underline{I}_0 := \frac{\underline{E}_{a1}}{(\underline{Z}_1 + \underline{Z}_{TR} + \underline{Z}_1 + \underline{Z}_{TR} + \underline{Z}_{TR})} = 0.00620962 - 4.44279635i$$

$$z_{2r\theta}(\underline{I}_0) = "(4.4428 \angle -89.92^\circ)" \text{ pu}$$

$$\begin{pmatrix} \underline{I}_a \\ \underline{I}_b \\ \underline{I}_c \end{pmatrix} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix} \cdot \begin{pmatrix} \underline{I}_0 \\ \underline{I}_0 \\ \underline{I}_0 \end{pmatrix} = \begin{pmatrix} 0.02 - 13.33i \\ 0 \\ 0 \end{pmatrix} \text{ pu}$$

$$z_{2r\theta M} \begin{pmatrix} \underline{I}_a \\ \underline{I}_b \\ \underline{I}_c \end{pmatrix} = \begin{pmatrix} "(13.3284 \angle -89.9199^\circ)" \\ "(0 \angle -89.8881^\circ)" \\ "(0 \angle -89.8881^\circ)" \end{pmatrix} \text{ pu}$$

No	Winding Connections	Zero Sequence Circuit	Positive or Negative Sequence Circuit
1			

DATA FOR CALCULATIONS

- In the Past...
 - Books
 - Data catalogs
 - Papers
- Present...
 - All from the Past scanned to PDF, TIFF or other...
 - http search engines
 - WWW
- Future?

DATA FOR CALCULATIONS

- <http://www.mikeholt.com/download.php?file=PDF/HardtoFindVolume1.pdf>
- <http://www.mikeholt.com/download.php?file=PDF/HardtoFind-Volume2.pdf>

ABB Inc.

HARD TO FIND INFORMATION
ABOUT DISTRIBUTION SYSTEMS

Reference Material

Subject - Hard to Find Information about Distribution Systems May 16, 2011
This newsletter was sent to 17012 newsletter subscribers

[Ask a Question](#) | [Continuing Education](#) | [Quizzes](#) | [Free Stuff](#) | [Instructors](#) | [Products](#) | [Seminars](#) | [Subscribe](#) | [Unsubscribe](#)

[[image1](#) [Post Comments](#) | [View Comments](#) | [Notify Me When Comments Are Added](#)]

Hard to Find Information About Distribution Systems – Volume 1

By Jim Burke
09/2006

There have been little tidbits of information I have accumulated over the past 40 years that have helped me understand and analyze distribution systems. I have pinned them to my wall, taped them to my computer, stuffed them in my wallet and alas, copied them for my students. Much of them are hard, if not impossible, to find in any reference book. A large percentage of them could also be classified as personal opinion so they should be used carefully. For whatever, I hope they are as useful to you as they have been to me. Over the many years, this document has taken on a life of its own. There have been many suggestions and much help from so many distribution engineers that it is impossible to thank all of you. From the new topics such as "stray voltage" and grounding" to the many surveys we've all done together (lightning, loading, etc) and finally the less serious sections like "Ways We Scare Ourselves" and " Airline Cabin Announcements", this has been a lot of fun to work on.

Jim Burke
[Click here](#) to read or download this document, (Note this document is 123 pages long, and 1,472 KB so it may take some time to download, depending on your internet speed)

Image1

2002
TION
insultant
856-3311
17-5050
JLCOES
mpus Drive
27606
.00 (USD)

THE END

REFERENCES

- [1] P. M. Anderson, *Analysis of faulted power systems*: IEEE Press, 1995.
- [2] E. Clarke, *Circuit Analysis of A-C Power Systems, Volume I*: Wiley, 1943.
- [3] E. Clarke, *Circuit Analysis of A-C Power Systems, Volume II*: Wiley, 1950.
- [4] J. Arrillaga and C. P. Arnold, *Computer analysis of power systems*. Chichester, England ; New York: Wiley, 1990.
- [5] J. Arrillaga and N. R. Watson, *Computer modelling of electrical power systems*, 2nd ed. Chichester ; New York: Wiley, 2001.
- [6] S. A. R. J W Nilsson, *Electric Circuits, 9th Edition*: Prentice Hall, 2011.
- [7] W. E. C. E. U. E. Dept, *Electric Utility Engineering Reference Book: Distribution systems*: The Corporation, 1965.
- [8] W. E. C. C. S. Engineers, *Electrical Transmission and Distribution Reference Book*: Westinghouse Corporation, 1950.
- [9] E. W. Kimbark, *Electrical Transmission of Power and Signals*: John Wiley, 1949.
- [10] W. D. Stevenson, *Elements of power system analysis*: McGraw-Hill, 1982.
- [11] "IEEE Std 141 - IEEE Recommended Practice for Electric Power Distribution for Industrial Plants (Red Book)," ed: IEEE IAS/PSE, 1994.
- [12] "IEEE Std 142 - IEEE Recommended Practice for Grounding of Industrial and Commercial Power Systems (Green Book)," ed: IEEE IAS/PSE, 2007.
- [13] "IEEE Std 399 - IEEE Recommended Practice for Industrial and Commercial Power Systems Analysis (Brown Book)," ed: IEEE IAS/PSE, 1997.
- [14] C. L. Fortescue. (1918, Method of Symmetrical Co-Ordinates Applied to the Solution of Polyphase Networks. *AIEE Transactions* 37, 1027-1140. Available: <http://www.energyscienceforum.com/files/fortescue/methodofsymmetrical.pdf>
- [15] C. S. Pierre, *A Practical Guide to Short-circuit Current Calculations*: Electric Power Consultants, 2001.
- [16] J. L. Blackburn, *Symmetrical Components for Power Systems Engineering*: CRC Press, 1993.
- [17] C. F. Wagner and R. D. Evans, *Symmetrical Components, As Applied to the Analysis of Unbalanced Electrical Circuits*: McGraw-Hill Book Company, Inc., 1933.
- [18] J. R. Carson, *Wave Propagation in Overhead Wires with Ground Return*: Bell telephone laboratories, 1926.
- [18] O. Crisan, "ECE-6127 Power Transmission and Distribution Lectures", University of Houston, 1993
- [19] D. Shattuck, "ECE-2300 Circuit Analysis Lectures", University of Houston, 2011