
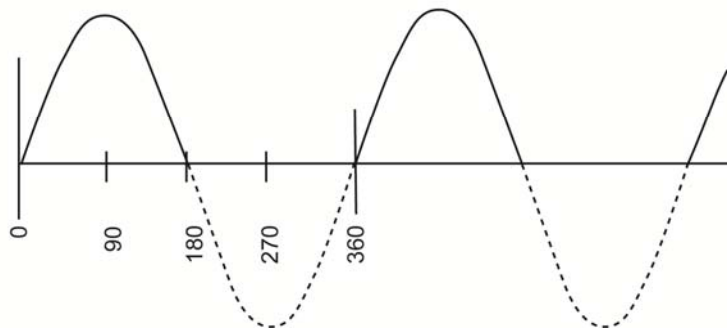


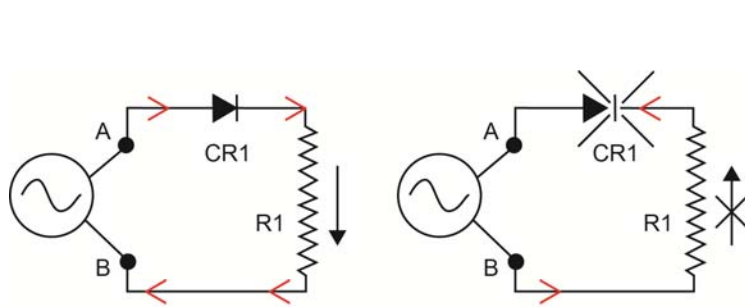



Electricity Fundamentals

Rectification (AC to DC)

- Rectifiers or diodes are used to convert AC to DC.



Half-wave rectification

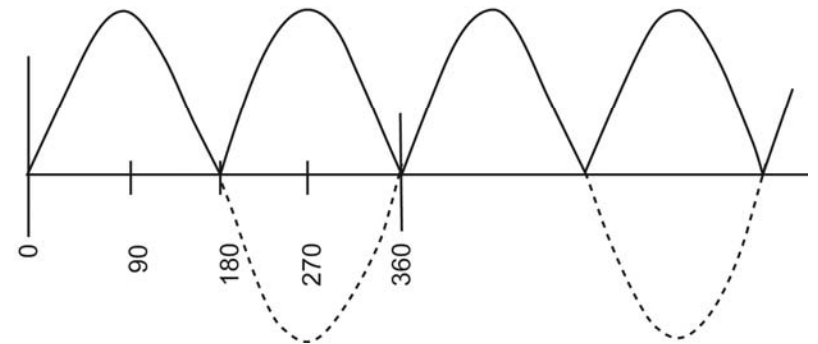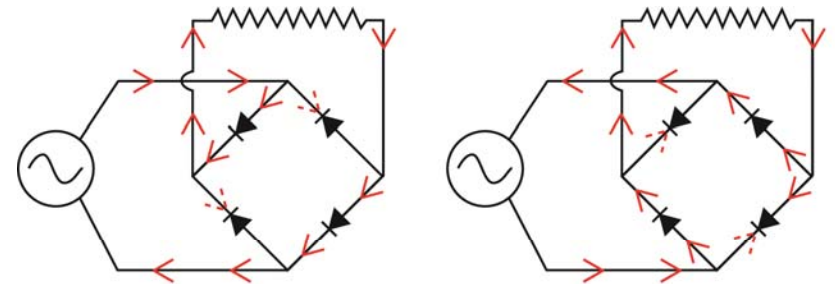

Full-wave rectification


Power

- Is the rate of doing work.
- In a DC circuit:
 - = voltage \times current (EI)
 - or, since $E = IR$, also = I^2R .
- In an alternating current circuit, there may be inductive and capacitive elements.
 - Result in the current leading or lagging the voltage.
 - Affects power.




Power (cont.)

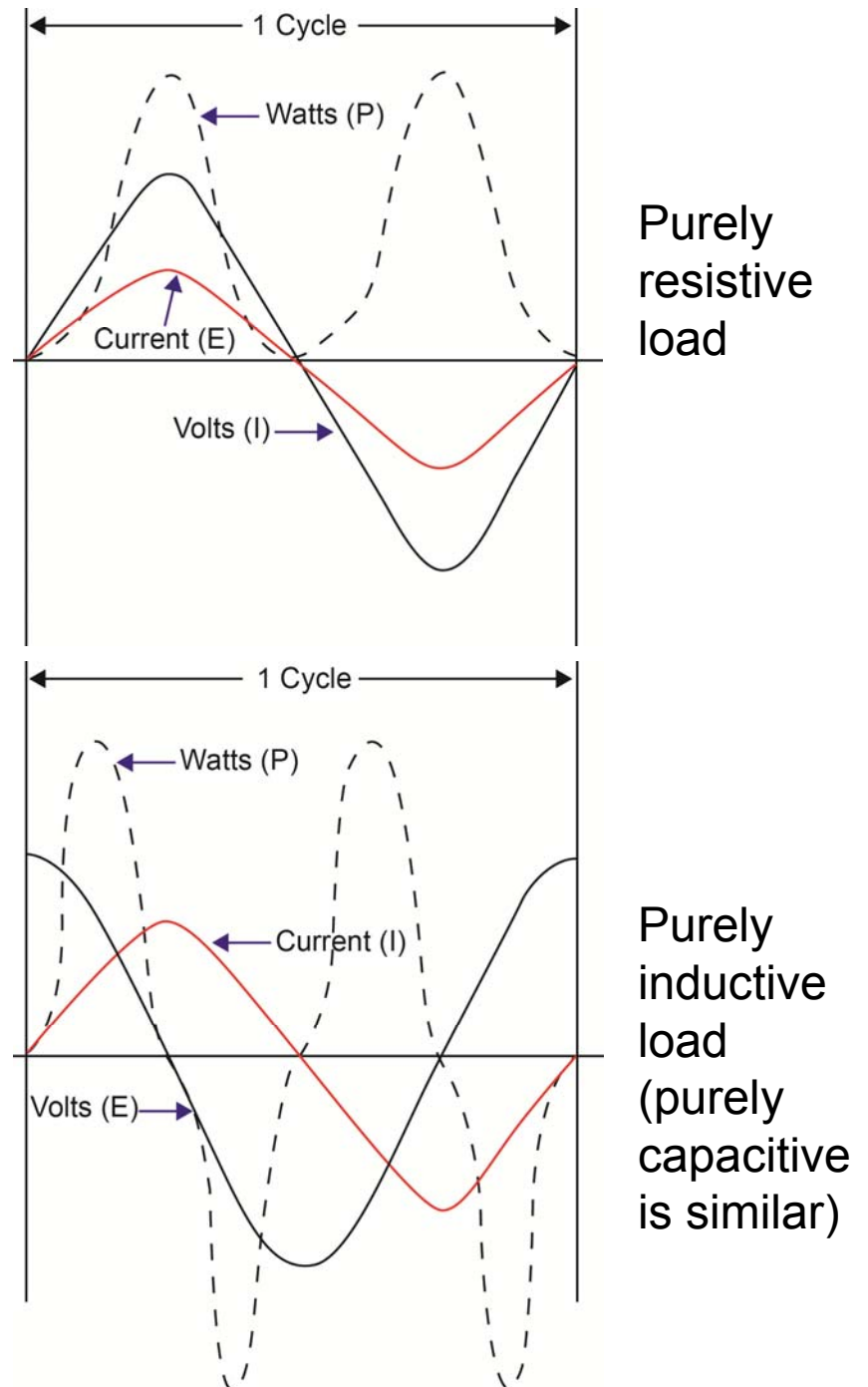- Purely resistive:
 - Voltage always aligned with current
 - Power will be zero or more.
- Purely reactive (inductive or capacitive):
 - Points where voltage is positive and current is negative and vice-versa.
 - No work is done. All power is returned to the source.




Power (cont.)

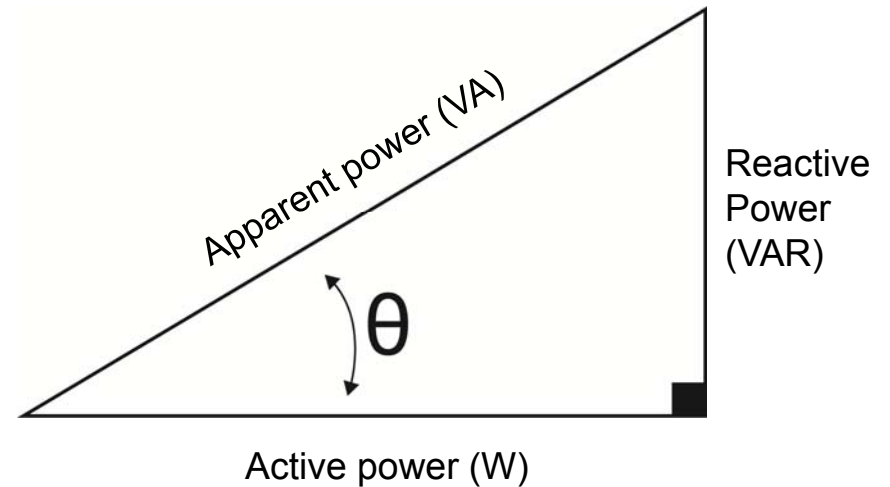- Active (real) power (W) - . Eventually produces a tangible result like heat or light ($= I^2R$).
- Reactive power (VAR) - Surges back and forth between the source and load. This power produces alternating magnetic fields in devices ($= I^2X$).
- Apparent power (VA) - Is the vector sum of active and reactive, the total needed ($= I^2Z$).



A Power Analogy

- When you drink, the froth hits your mouth first and delays the beer. Reactive power is related to the delay that occurs due to setting up alternating magnetic fields.
- Beer that then flows into your mouth and quenches your thirst is like active power flowing to the equipment being powered.
- The total amount of beer and froth in the glass represents the apparent power, which is the sum of active and reactive power.

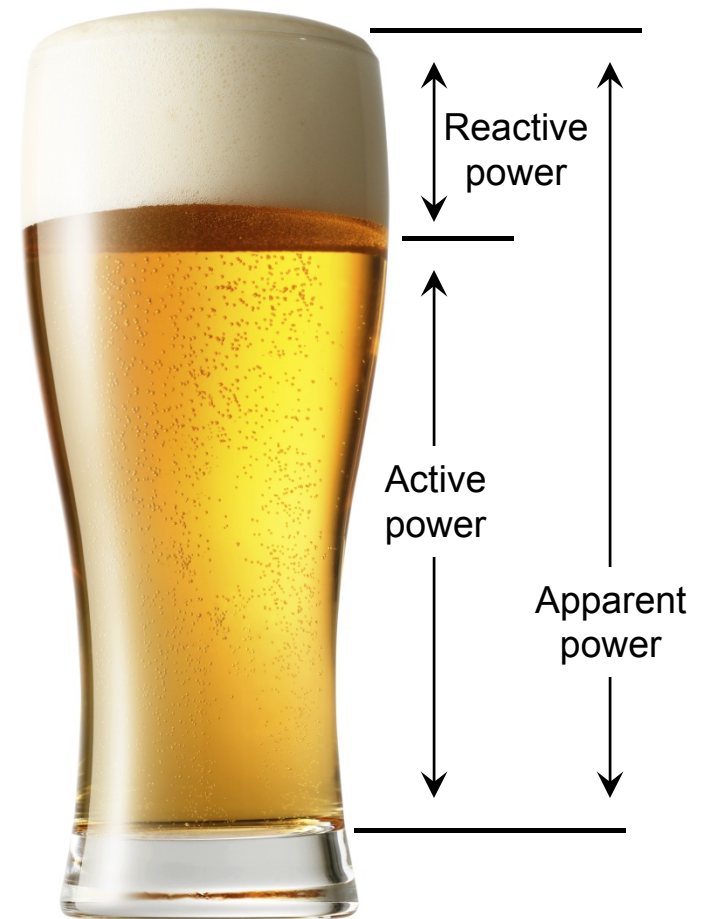

Power: Example



What are the values of the active, reactive and apparent power in our circuit?

$$60 \text{ A}$$

$$R = 60 \ \Omega$$

$$X = 80 \ \Omega$$

$$Z = 100 \ \Omega$$

$$\text{Active power} = 5 \text{ A}^2 \times 60 \ \Omega = 1500 \text{ W}$$

$$\text{Reactive power} = 5 \text{ A}^2 \times 80 \ \Omega = 2000 \text{ var}$$

$$\text{Apparent power} = 5 \text{ A}^2 \times 100 \ \Omega = 2500 \text{ VA}$$

Power Factor

- Is active power/apparent power (a ratio): Example: $1000 \text{ kW} / 1250 \text{ kVA} = 0.8 \text{ PF}$.
- Describes how much of the power produced is being used to perform work.
- Depends on the load. The generator is rated for a specific power factor.
 - 0.8 is typical.
 - 1 is called unity.
- The lower the power factor:
 - More apparent power is needed to get the job done.
 - Larger equipment is required.
 - Energy costs are higher due to increased losses in the circuit.

Power Factor: Example



What is the power factor in our circuit?

1500 W

2500 VA

$$1500 \text{ W} / 2500 \text{ VA} = 0.6 \text{ PF}$$